

Easy to build projects for everyone

# Everyday ELECTRONICS

JULY 82  
70p

## HOOKED

I MUST GET THIS  
FINISHED BEFORE  
THE TIDE COMES IN

CARAVAN BRAKE LIGHT RELAY • REFLEX TESTER  
MUSICAL PITCH PIPE • MODEL CAR LAP COUNTER



APPROVED  
**thandar**  
STOCKIST

# B.K. ELECTRONICS

## A SOUND CHOICE

APPROVED  
**thandar**  
STOCKIST

★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS  
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



6 piano type keys

**NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").** These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons  
Specification and Price: -


**15" 100 watt R.M.S.** Impedance 8ohm 59 oz magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. Price £32 each. £2.50 Packing and Carriage each.

**12" 100 watt R.M.S.** Impedance 8 ohm, 50 oz. magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. Price £23.70 each. £2.50 Packing and Carriage each

**8" 50 watt R.M.S.** Impedance 8 ohm, 20 oz magnet, 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz, Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. Price: **White cone £8.90 each. Black cone/grill £9.50 each.** P. & P. £1-25.
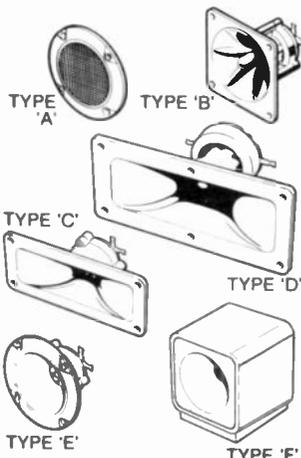
### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



**STEREO CASSETTE TAPE DECK MODULE.** Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2in x 11 1/4in. Clearance required under top panel 2 1/4in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price £26.70 + £2.50 postage and packing  
Supplementary parts for 18V DC power supply (transformer, bridge rectifier and smoothing capacitor) £3.



**1000 MONO DISCO MIXER**—completely built and tested employing modern I.C. circuitry. Can be mounted vertical or horizontal into cabinet, console, etc. Two turntable inputs (ceramic) plus aux. (tape) and mic. inputs. Headphone monitor socket. Compatible with OMP100 Power Amp. (500mV O/P). Controls: Microphone talk over switch with separate volume, treble and bass. Three main fader (level) controls with master volume, treble and bass. Monitor selector switch with monitor level control. Mains On/Off switch. Smart black finish. Size: 535 x 110 x 60mm. Power requirements: 240V A.C. Price: £39.99 + £2.25 P & P.



### B.S.R. P232 TURNTABLE

P232 Turntable ★ 'S' shaped tone arm  
★ Belt driven ★ Aluminium platter  
★ Cueing lever ★ 240 volt AC operation (50Hz)  
★ Cut-out template supplied  
★ Used as standard by Hi-Fi and Disco manufacturers  
★ Fitted with either a magnetic or ceramic cartridge, please state cartridge required  
Price £22.50 + £2.50 P & P.




### POWER AMPLIFIER MODULES

100 WATTS R.M.S.


Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. Vu meter available as an optional extra.

**SPECIFICATION:**  
Max. output power 100 watts R.M.S. (OMP 100)  
Loads: (Open and short circuit proof) 4-16 ohms  
Frequency Response: 20Hz-25KHz ± 3dB  
Sensitivity: for 100 watts 500mV at 10K

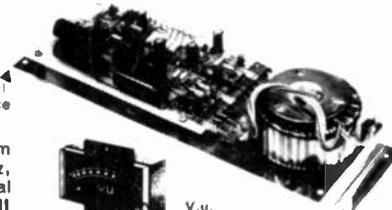T.H.D. 00 1%  
Size: 360 x 115 x 80mm  
Prices: OMP 100 £29.99 P & P £2.00  
V.u. Meter £8.50




V.u. Meter

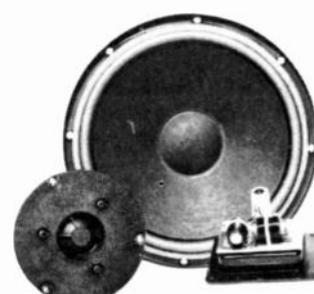

**MULLARD 40 WATT R.M.S. 8 ohm SPEAKER SYSTEM.** Designed by Mullards specialist team in Belgium. Comprising of a Mullard 8" woofer with foam surround, a Mullard 3" dome tweeter and a cleverly designed B.K. Electronics crossover combining spring loaded loudspeaker terminals and recessed mounting panel. Supplied complete with installation and cabinet details.

Price £13.90 + £1.50 P & P per kit.

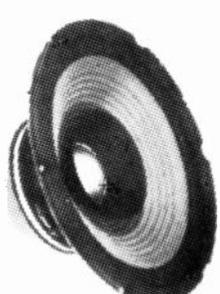**12" 80 watt R.M.S. loudspeaker.**  
A superb general purpose twin cone loudspeaker 50 oz. magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.  
Price £17.99 ea + £2.50 P & P.



# B.K. ELECTRONICS

DEPT E.E.

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.




# Everyday ELECTRONICS

VOL. 11 NO. 7

JULY 1982

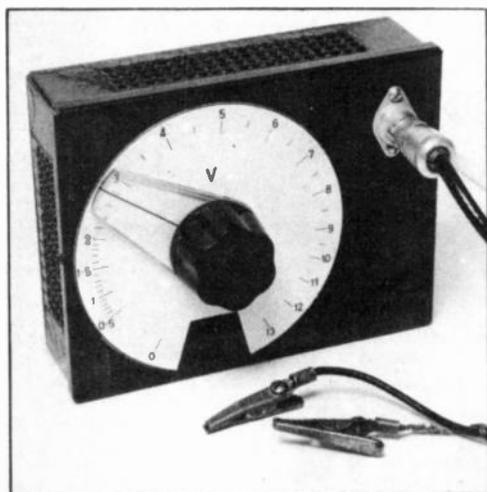PROJECTS . . . THEORY . . . NEWS . . .  
COMMENT . . . POPULAR FEATURES . . .



© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

## PROJECTS

- MODEL CAR LAP COUNTER & JUDGE** by A. P. Donleavy **442**  
Digital counter for two lane race track with win indicator
- ELECTRONIC PITCH PIPE** by I. Hickman **448**  
Compact tuning aid for the musician
- PUBLIC ADDRESS SYSTEM** by E. A. Rule **456**  
Part 3: Power amplifier assembly and wiring
- TWO-WAY INTERCOM** by E. M. Terrell **464**  
A simple solderless system for the beginner—as seen on TV
- BRAKE LIGHT RELAY** by T. R. de Vaux-Balbirnie **470**  
Safety feature for caravan or trailer brake lights
- COMPARATOR VOLTMETER** by N. P. Naughton **481**  
Robust testmeter for the workshop
- REFLEX TESTER** by D. J. Edwards **484**  
Visual response referee

## SERIES

- TEACH-IN 82** by O. N. Bishop **451**  
Part 10: Oscillators
- A.C. MAINS EXPLAINED** by A. Kenyon **474**  
Part 1: Alternating currents and voltages

## FEATURES

- EDITORIAL** **441**  
Making Contact
- FOR YOUR ENTERTAINMENT** by Barry Fox **447**  
Cable Shock, Music for Pleasure
- COUNTER INTELLIGENCE** by Paul Young **450**  
A retailer comments
- SHOP TALK** by Dave Barrington **455**  
Product news and component buying
- RADIO WORLD** by Pat Hawker G3VA **467**  
Museum Pieces, American A.M.
- EVERYDAY NEWS** **468**  
What's happening in the world of electronics
- SQUARE ONE** **476**  
Beginners' Page: Tools
- NEW PRODUCTS** **478**  
Facts and photos of instruments, equipments and tools
- CIRCUIT EXCHANGE** **488**  
A forum for readers' ideas

Our August issue will be published on Friday,  
July 16. See page 463 for details.

Readers Services ● Editorial and Advertisement Departments

## DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasing three-note harmonically related tone sequenced (not a microprocessor controlled buzz or the same old ding dong) at a touch of a button. This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V battery and push button common to most household. It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 160mW output and draws less than one 1uA from a PP3 battery when the tone ceases. Supplied complete with circuit and assembly instructions.

**IDEAL PROJECT FOR BEGINNERS—Only £5**



# KITS & COMPONENTS

## HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TD300K	Remote Control Dimmer	£14.30
MKS	Transmitter for above	£ 4.20
TD300K	Touchdimmer	£ 7.00
TDEK	Extension kit for 2-way switching for TD300K	£ 2.00
LD300K	Rotary Controlled Dimmer	£ 3.90



## TEACH-IN '82

EE MiniKit £13.50  
Parts 1-6 £7.50  
Parts 7-12 £4.50  
Special price for all kits purchased together £23.50


Woodwork not included. The above kits include all the components specified in the Tech-In '82 projects parts 1-12 plus sockets for ICs specified.

**FORGET YOUR PEN RING 5 to 10 ITS COMPONENT MAIL ORDER MADE EASY OUR NEW SALES NO. 567-8910**

**FIVE · SIX · SEVEN · EIGHT · NINE · TEN (01 OUTSIDE LONDON) THE NUMBER YOU CAN'T FORGET**
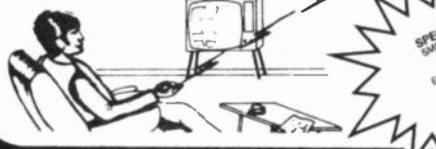
## REMOTE CONTROL

Published remote control systems tend to be quite complex requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infra-red, our KITS range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs of three analogue outputs for controlling, e.g., TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, triacs, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices. We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself—SEND US 50p and a stamped addressed envelope for your copy TODAY!



## 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



CT1000K Basic Kit	£14.90
CT1000K with white box (68/131 x 71mm)	£17.40
(Ready Bulk)	£22.50

**SPECIAL OFFER**  
SEND IN YELLOW OR FOLDER FOR EXCLUSION OF VAT ON ALL ITEMS UNTIL MAY 31ST 1982 ON WHOLE STOCK LIST

## (Shaped Leds) Red Green Yellow [Tri Colour Leds]

Rectangular (Gravestone)	16p	16p	16p
Rectangular	5x2.5mm 17p	20p	20p
Square	5x5mm 17p	20p	20p
Triangular	Δ 5mm 17p	20p	20p
Arrowhead	<12.6x5mm 17p	20p	20p

3mm & 5mm Round Red...08p Green...12p  
Clips 3mm & 5mm...03p Yellow...12p

5mm round...30p  
5mm Rectangular...32p

## [Flashing Leds]

5mm diameter Red...30p Flashing/Continuous...42p



## DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. Price £15.99



**FAST SERVICE · TOP QUALITY · LOW LOW PRICES**

No circuit is complete without a call to -

ALL PRICES EXCLUDE VAT



**ELECTRONICS**


11 Boston Road  
London W7 3SJ



TEL: 01-567 8910 ORDERS  
01-579 9794 ENQUIRIES  
01-579 2842 TECHNICAL (AFTER 3PM)

Add 50p postage & packing +18% VAT to total. Overseas Customers: Add £1.75 (Europe), £4.50 (elsewhere) for p&pb. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability. Barn to 5pm (Mon to Fri) 10am to 4pm (Sat)

## OPEN

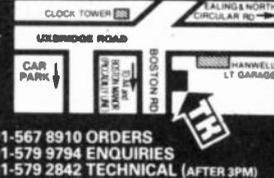

## TECHNICAL TRAINING IN ELECTRONICS, TELEVISION AND AUDIO IN YOUR OWN HOME - AT YOUR PACE

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

### City & Guilds Certificates

**Radio Amateurs Basic Electronic Engineering (Joint C&G/ICS)**

### Certificate Courses

**TV and Audio Servicing  
Radio & Amplifier Construction  
Electronic Engineering\* and Maintenance  
Computer Engineering\* and Programming  
Microprocessor Engineering\*  
TV, Radio and Audio Engineering  
Electrical Engineering\* Installation  
and Contracting**

\*Quality for IET Associate Membership



Approved by CACC



Member of ABCC

## POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_



Post to: Dept 266W  
ICS School of Electronics  
180 Stewarts Road,  
London SW8 4UJ



01-622 9911  
(All Hours)

## (DUE TO POPULAR DEMAND) EXTENDED OFFER!

As an introduction to **CRICKLEWOOD ELECTRONICS LTD.**, (Marshall's Old Shop), 40 Cricklewood Broadway, London NW2 3ET tel: 01 452 0161 Whilst stocks last and only if accompanied by this Ad.

### DESOLDERING TOOL



Now every one can afford one of these superb, anodised aluminium high pressure hand desoldering tools at nearly half our normal price. Normal Price £6.50 + VAT with this ad £3.85 + VAT. Spare Teflon screw-in noses 75p + VAT.

**JAPANESE TRANSISTORS** May not be as hard to replace as you think. Phone our equivalent service on 01 452 0161 (everyday except Wednesdays) or write. We have thousands of Transistors, ICs, LEDs in stock, as well as every conceivable type of component—Why not make **CRICKLEWOOD ELECTRONICS** your personal **ELECTRONICS HOBBY CENTRE!** We have the goods!

Now you need no longer grope in the dark. For a miniature price you can watch those volts move! See those resistors jump to life!

**THE MIGHTY MINI MULTI-TESTER** 2,000 ohms per volt. DC & AC Voltage ranges: 10v, 50v, 250v, 1000v. DC current ranges 100mA. Resistance ohms x 10, ohms x 100db from -10db to +22db. Mirror arc scale, overload protected, complete with battery, test leads & instructions. Usual price £8.65 + VAT; with this Ad: £4.95 + VAT.



### ORDER FORM

Name \_\_\_\_\_

Address \_\_\_\_\_

..... Desoldering tools @ £3.85 = £.....  
..... Spare Teflon noses @ .75 = £.....  
..... Mighty Mini Testers @ £4.95 = £.....

Postage, packing and Insurance @ 60p per one device 25p for each additional device

Sub total £.....  
Add 15% VAT £.....  
£.....

I enclose cheque no/P.O. no. \_\_\_\_\_  
Alternatively please credit my VISA/ACCESS no. \_\_\_\_\_

Signature \_\_\_\_\_  
This offer applies to UK only. Please allow 7-10 days delivery. Overseas customers please do not add VAT but allow enough to cover postage.

**TRADE ENQUIRIES WELCOME.**  
**CRICKLEWOOD ELECTRONICS LTD.**  
40 Cricklewood Broadway, London NW2 3ET tel 01 452 0161



# Beginners' luck

**30% OFF**  
10 selected kits  
for first-time  
builders



Shortwave  
Listener's  
Receiver

With Heathkit, you're all set for a great deal. And not just big savings.

Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need




Digital Clock

is there. Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud

of. Because you built it yourself.

There are 10 great kits to start you off. An interesting choice of a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

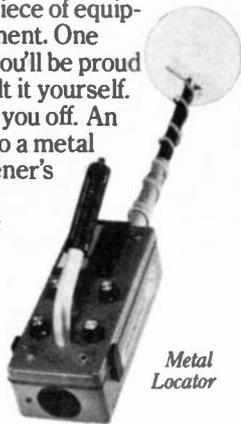All at 30% off to first-timers. Send for your catalogue right now for a start.




Metal  
Locator



Windspeed and Direction  
Indicator

To Heath Electronics (UK) Limited, Dept ( EE 7 ), Bristol Road, Gloucester GL2 6EE.

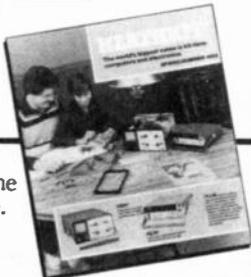

EE 7

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name \_\_\_\_\_  
Address \_\_\_\_\_



**HEATH** You build on our experience


# HEATHKIT


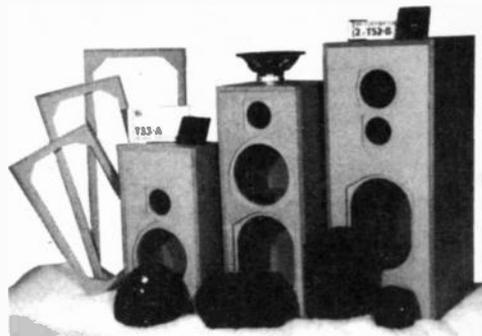
## Constructor Series Speakers

IT'S  
SO  
EASY

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit. No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of.



Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc.

The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl.

Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.

Prices: CS1 (B110B/T27A)	£110 pr. inc. VAT, plus carr./ins. £ 5
CS1A (B110A/T27A)	£103 pr. inc. VAT, plus carr./ins. £ 5
CS3 (B200G/T33A)	£129 pr. inc. VAT, plus carr./ins. £10
CS5 (B200G/BD139B/T33A)	£192 pr. inc. VAT, plus carr./ins. £15
CS7 (B139B/B110B/T33A)	£250 pr. inc. VAT, plus carr./ins. £15



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

1982 Catalogue — £1.50 post free



Lightning service on telephoned credit card orders!



# BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

**Free!**

Brochure without obligation to :-

**British National Radio & Electronic School**  
READING, BERKS. RG1 1BR

Name .....  
Address .....

EE/7/815

BLOCK CAPS PLEASE

# Rapid Electronics

Tel: 0206 36412  
Hill Farm Industrial Estate  
Boxted  
Colchester Essex CO4 5RD



LINEAR	ICL7106	790	LM358	50	LM3914	200	NE570	400	TL064	96	
★555 CMOS	ICL7111	85	LM377	150	LM3915	220	NE571	400	TL071	30	
★556 CMOS	ICL7621	180	LM380	80	LM13600	120	RC4136	68	TL072	50	
	LM7622	180	LM381	120	MC1310	150	RC4558	60	TL074	195	
709	ICL8038	320	LM382	120	MC1496	68	SL480	170	TL081	25	
★741	ICL8211A	200	LM384	130	★ML922	400	SL490	250	TL082	45	
746	IC LM7224	73	★LM386	85	ML924	195	SN178477	250	TL084	95	
9400CJ	350	CM7555	80	LM387	120	ML925	210	SP8629	250	TL170	50
AY-3-1270	40	LF351	45	LM393	100	ML926	140	TBA1205	70	★LA2240	120
AY-3-8910	60	LF353	85	LM709	25	ML927	140	TBA800	60	ULN2003	85
AY-3-8912	825	LF356	90	LM711	60	ML928	140	TBA810	96	ULN2004	90
CA3048	60	LM10	360	LM725	350	ML929	140	TBA820	90	ZN414	100
CA3080	65	LM301A	25	LM733	75	MM5387A	485	TBA850	290	ZN423	135
CA3089	215	LM311	70	★LM741	80	NE529	125	TDA1008	320	ZN424	135
CA3090A	375	LM318	120	LM747	75	NE331	150	★TDA1022	525	ZN425E	350
CA3130E	90	LM324	40	LM458	40	NE544	295	ZN426E	330	ZN426E	330
CA3140E	45	LM334Z	100	LM2917	200	★NE555	16	TDA1024	125	ZN427E	650
CA3161E	100	LM335Z	125	LM3900	50	★NE556	45	★TDA1024	125	ZN428E	480
CA3189	290	LM339	50	LM3909	78	NE586	150	TL061	40	ZN429	285
★CA320E	110	LM348	65	LM3911	120	★NE587	100	TL062	60	ULN1034E	200

CMOS	★4017	42	4036	275	4055	95	4082	16	4502	60	4509	150
4000	10	4019	25	4040	50	4060	85	4086	60	4507	38	4534
★4001	10	4020	50	4041	60	4063	85	4089	125	4508	150	4538
4002	12	4021	50	4042	45	★4066	30	★4093	30	4510	50	4543
4006	50	4022	50	4043	50	4067	295	4094	120	★4511	50	4549
4007	15	4023	18	4044	50	4068	18	4095	75	4512	50	4553
4008	48	4024	33	4045	60	4069	18	4097	290	4514	120	4555
4009	24	4025	32	4046	60	4070	15	4098	75	4515	120	4556
4010	24	★4026	80	4048	48	4071	15	4099	90	4516	85	4559
★4011	11	4027	24	★4049	25	4072	15	4100	50	★4518	40	4560
4012	15	4028	50	★4050	25	4073	15	4101	100	4520	70	4584
★4013	25	4029	60	4051	45	4075	15	4103	100	4521	130	4585
4014	50	4030	30	4052	60	4076	50	4104	100	4522	70	4724
4015	50	4031	125	4053	50	4077	15	4105	100	4523	80	
★4016	20	4034	45	4054	85	4081	14	4108	95	4528	78	

LS TTL	LS21	12	LS76	18	LS125	26	LS181	37	LS221	54	LS365	30
LS00	11	LS26	14	LS83	40	LS132	42	LS163	37	LS240	89	LS366
LS01	11	LS27	12	LS85	52	LS136	28	LS164	43	LS242	75	LS368
LS02	11	LS30	12	LS86	19	LS138	32	LS165	75	LS243	75	LS373
LS03	12	LS32	13	LS90	28	LS139	32	LS166	75	LS244	60	LS374
LS04	12	LS33	15	LS92	32	LS140	32	LS167	75	LS245	60	LS375
LS05	13	LS35	13	LS93	28	LS147	150	LS173	85	LS247	50	LS377
LS06	12	LS40	13	LS95	40	LS148	85	LS174	45	LS251	35	LS378
LS09	12	LS42	32	LS96	95	LS151	38	LS175	45	LS257	35	LS390
LS10	12	LS47	38	LS107	40	LS153	40	LS190	45	LS258	35	LS393
LS11	12	LS48	38	LS109	21	LS154	90	LS191	45	LS259	75	LS399
LS12	12	LS51	14	LS112	21	LS155	35	LS192	45	LS266	22	LS454
LS13	12	LS53	15	LS92	32	LS140	32	LS173	85	LS270	150	
LS14	12	LS54	18	LS114	22	LS157	30	LS195	38	LS279	35	
LS15	12	LS74	18	LS122	38	LS158	30	LS196	50	LS283	40	
LS20	12	LS75	22	LS123	38	LS160	37	LS197	60	LS353	88	

TTL	7413	18	7442	32	7480	48	74107	25	74155	40	74177	45
7400	11	7416	24	7446	65	7483	40	74121	25	74157	30	74180
7401	11	7417	24	7447	60	7485	60	74122	40	74160	60	74181
7402	11	7420	15	7448	60	7486	60	74123	40	74161	50	74182
7403	12	7421	20	7450	16	7489	180	74125	35	74162	50	74190
7404	13	7422	20	7451	16	7490	21	74126	35	74163	50	74191
7405	15	7427	22	7453	16	7491	45	74132	30	74164	50	74192
7406	24	7428	26	7454	16	7492	25	74141	60	74165	50	74193
7407	25	7430	14	7460	16	7493	25	74145	50	74167	150	74194
7408	14	7432	25	7472	25	7494	30	74147	90	74170	125	74195
7409	14	7434	25	7473	28	7495	35	74148	70	74173	60	74196
7410	14	7438	25	7474	20	7496	40	74150	55	74174	60	74197
7411	16	7437	25	7475	26	7497	95	74153	40	74175	55	74198
7412	18	7440	15	7476	30	74100	60	74154	55	74176	40	74199

TRANSISTORS	BC548	10	BC549	10	BC550	10	BC551	10	BC552	10	BC553	10
AC125	35	BC157	10	BC158	10	BC159	10	BC160	45	BC161	45	BC162
★AC128	20	BC160	45	BC172	16	BC173	16	BC174	16	BC175	16	BC176
AC176	25	BC168C	10	BD115	10	BC178	16	BC179	16	BC180	16	BC181
AC187	22	BC169C	10	BD131	35	BC182	16	BC183	16	BC184	16	BC185
AC188	22	BC170	10	BD133	35	BC186	16	BC187	16	BC188	16	BC189
AD142	120	BC171	10	BD135	35	BC190	16	BC191	16	BC192	16	BC193
AD149	00	BC172	8	BD136	35	BC194	16	BC195	16	BC196	16	BC197
AD161	48	BC177	16	BD138	35	BC198	16	BC199	16	BC200	16	BC201
AD162	48	BC178	16	BD139	35	BC202	16	BC203	16	BC204	16	BC205
AF124	60	BC179	16	BD140	35	BC206	16	BC207	16	BC208	16	BC209
AF126	60	BC182	10	BD141	35	BC210	16	BC211	16	BC212	16	BC213
AF139	48	★BC182L	8	BD142	35	BC214	16	BC215	16	BC216	16	BC217
AF186	70	BC183	10	BD143	35	BC218	16	BC219	16	BC220	16	BC221
AF239	75	BC183L	10	BD144	35	BC222	16	BC223	16	BC224	16	BC225
BC107	10	BC184	10	BD206	110	BC226	16	BC227	16	BC228	16	BC229
BC107B	12	★BC184L	7	BD222	85	BC230	16	BC231	16	BC232	16	BC233
★BC108	8	BC212	10	BF150	35	BC234	16	BC235	16	BC236	16	BC237
BC108B	12	BC212L	10	BF151	35	BC238	16	BC239	16	BC240	16	BC241
BC108C	12	BC213	10	BF152	35	BC242	16	BC243	16	BC244	16	BC245
★BC109	8	BC213L	10	BF153	35	BC246	16	BC247	16	BC248	16	BC249
BC109C	12	BC214	10	BF154	35	BC250	16	BC251	16	BC252	16	BC253
BC114	22	★BC214L	8	BF195	12	BC254	16	BC255	16	BC256	16	BC257
BC115	22	BC237	8	BF197	12	BC258	16	BC259	16	BC260	16	BC261
BC117	22	BC238	8	MPF102	40	BC262	16	BC263	16	BC264	16	BC265
BC119	35	BC208	15	MPF104	40	BC266	16	BC267	16	BC268	16	BC269
BC131	40	BC327	14	MPF105	40	BC270	16	BC271	16	BC272	16	BC273
BC134	40	BC328	14	MPSA06	25	BC274	16	BC275	16	BC276	16	BC277
BC140	30	★BF244B	22	MPSA12	30	BC278	16	BC279	16	BC280	16	BC281
BC141	30	BC338	14	MPSA55	30	BC282	16	BC283	16	BC284	16	BC285
BC142	30	BC347	30	MPS55B	45	BC286	16	BC287	16	BC288	16	BC289
BC143	30	BC357	30	MPS55S	45	BC290	16	BC291	16	BC292	16	BC293

# E.E. PROJECT KITS

I.C.s  
TRANSISTORS  
CAPACITORS

TOOLS  
RESISTORS  
HARDWARE

CASES  
KITS

# MAGENTA

Make us your No. 1 SUPPLIER OF KITS AND COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller(tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project—you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- 2k RAM PACK Apr 82 less case £12.89  
V.C.O. SOUND EFFECTS UNIT Apr 82 £10.81  
LIGHT ACTUATED SWITCH Apr 82 £17.52  
CAMERA OR FLASH GUN TRIGGER Mar 82. £11.60 less tripod bushes.  
POCKET TUNER Mar 82. £3.47.  
GUITAR TUNER Mar 82. £14.65.  
CAR OVERHEATING ALARM. Feb. 82. £8.99.  
SIMPLE STABILISED POWER SUPPLY. Jan. 82. £22.99.  
MINI EGG TIMER. Jan. 82. £3.69  
SIREN MODULE. Jan. 82. less speaker. £3.21.  
MODEL TRAIN CHUFFER. Jan. 82. £7.73.  
SQUARE SIX. Dec. 81. £4.40.  
GUITAR ADAPTOR. Dec. 81. £3.52.  
REACTION METER. Dec. 81. £16.41.  
ELECTRONIC IGNITION. Nov. 81. £24.33.  
SIMPLE INFRA RED REMOTE CONTROL. Nov. 81. £15.99.  
PRESSURE MAT TRIGGER ALARM. Nov. 81. £5.88 less meta.  
EXPERIMENTER CRYSTAL SET. Nov. 81. Less aerial. £3.60.  
Headphones. £2.98 extra.  
CAPACITANCE METER. Oct. 81. £21.98.  
SUSTAIN UNIT. Oct. 81. £11.93.  
"POPULAR DESIGNS". Oct. 81.  
TAPE NOISE LIMITER. £4.28.  
HEADS AND TAILS GAME. £2.36.  
CONTINUITY TESTER. £3.70.  
PHOTO FLASH SLAVE. £3.24.  
FUZZ BOX. £6.82.  
OPTO ALARM. £4.34.  
SOIL MOISTURE UNIT. £3.43.  
ICE ALARM. £7.36.  
6-12V POWER SUPPLY. Sept. 81. £16.84  
CMOS CAR SECURITY ALARM. Sept. 81. £8.49.  
CMOS DIE. Sept. 81. £7.47.  
LED SANDGLASS. Aug. 81. £7.98.  
CMOS METRONOME. Aug. 81. £7.70.  
COMBINATION LOCK. July 81. Less case. £18.30.  
BURGLAR ALARM SYSTEM. June 81 less bell, loop & Mic's. £38.30.  
TAPE AUTO START. June 81. £11.98.  
LIGHTS REMINDER AND IGNITION LOCATOR E.E. May 81. £5.28.  
SOIL MOISTURE INDICATOR E.E. May 81. £3.83.  
GUITAR HEADPHONE AMPLIFIER E.E. May 81. £3.98.  
PHONE BELL REPEATER / BABY ALARM E.E. May 81. £5.29.  
INTERCOM. April 81. £20.78.  
SIMPLE TRANSISTOR & DIODE TESTERS. Mar. 81. Ohm meter version £1.98. Led version £2.56.  
MINI SIREN. Mar. 81. £7.52.  
LED DICE. Mar. 81. £7.89.  
LED FLASHER. Mar. 81. £4.01.  
MODULATED TONE DOORBELL. Mar. 81. £8.21.  
BENCH POWER SUPPLY. Mar. 81. £48.98.  
THREE CHANNEL STEREO MIXER. Feb. 81. £17.47.

- SIGNAL TRACER. Feb. 81. £7.64 less probe.  
Ni-Cd BATTERY CHARGER. Feb. 81. £12.72.  
ULTRASONIC INTRUDER DETECTOR. Jan. 81 less case. £49.98.  
2 NOTE DOOR CHIME. Dec. 80. £8.85.  
LIVE WIRE GAME. Dec. 80. £10.94.  
GUITAR PRACTICE AMPLIFIER. Nov. 80. £11.99 less case. Standard case £3.88. High quality case £8.33.  
SOUND TO LIGHT. Nov. 80. 3 channel. £19.95.  
TRANSISTOR TESTER. Nov. 80. £10.87 inc. test leads.  
AUDIO EFFECTS UNIT FOR WEIRD SOUNDS. Oct. 80. £12.28.  
BICYCLE ALARM. Oct. 80. £8.68 less mounting brackets.  
IRON HEAT CONTROL. Oct. 80. £5.48.  
TTL LOGIC PROBE. Sept. 80. £4.85.  
ZENER DIODE TESTER. June 80. £4.23.  
4 STATION RADIO. May 80. £15.33 less case.  
LIGHTS WARNING SYSTEM. May 80. £4.38.  
BATTERY VOLTAGE MONITOR. May 80. £4.63.  
CABLE & PIPE LOCATOR. Mar. 80. £3.85 less coil former.  
KITCHEN TIMER. Mar. 80. £13.70.  
STEREO HEADPHONE AMPLIFIER. Mar. 80. £18.97.  
MICRO MUSIC BOX. Feb. 80. £15.20. Grey Case £3.99 extra.  
SIMPLE SHORT WAVE RECEIVER. Feb. 80. £24.17. Headphones £2.98.  
SLIDE TAPE SYNCHRONISER. Feb. 80. £11.50.  
MORSE PRACTICE OSCILLATOR. Feb. 80. £4.32.  
SPRING LINE REVERB. UNIT. Jan. 80. £24.17.  
UNIBOARD BURGLAR ALARM. Dec. 79. £5.64.  
BABY ALARM. Nov. 79. £8.98.  
CHASER LIGHTS. Sept. 79. £21.87.  
SIMPLE TRANSISTOR TESTER. Sept. 79. £8.88.  
DARKROOM TIMER. July 79. £2.71.  
ELECTRONIC CANARY. June 79. £3.48.  
MICROCHIME DOORBELL. Feb. 79. £14.82.  
THYRISTOR TESTER. Feb. 79. £3.54.  
FUZE CHECKER. Oct. 78. £2.18.  
SOUND TO LIGHT. Sept. 78. £7.87.  
CAR BATTERY STATE INDICATOR. Sept. 78. Less case. £1.98.  
R.F. SIGNAL GENERATOR. Sept. 78. £24.98.  
IN SITU TRANSISTOR TESTER. June 78. £8.33.  
WEIRD SOUND EFFECTS GENERATOR. Mar. 78. £8.28.  
AUDIO VISUAL METRONOME. Jan. 78. £5.63.  
ELECTRONIC TOUCH SWITCH. Jan. 78. £2.56 less case.  
RAPID DIODE CHECK. Jan. 78. £2.57.  
PHONE/DOORBELL REPEATER. July 77. £8.98.  
ELECTRONIC DICE. Mar. 77. £5.31.

## SOLDERING/TOOLS/+

- ANTEX X5 SOLDERING IRON 25W £5.48.  
SOLDERING IRON STAND £2.40.  
SPARE BITS. Small standard, large, 85p each. For X5+X25.  
SOLDER. Hand, size 99p  
HOW TO SOLDER LEAFLET 12p  
DESOLDER BRAID 69p  
HEAT SINK TWEEZERS 29p  
DESOLDER PUMP £6.48  
SOLDER CARTON £1.84  
LOW COST CUTTERS £1.69  
LOW COST LONG NOSE PLIERS £1.68  
WIRE STRIPPERS & CUTTERS £2.89  
VERO SPOT FACE CUTTER £1.49.  
PIN INSERTION TOOL £1.98.  
VEROPINS. (pk of 100) 0-1" 52p.  
MULTIMETER TYPE 1 (1,000 opv). £6.66.  
MULTIMETER TYPE 2. 20,000 opv with transistor tester. Very good. £14.75.  
CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips. 99p.  
RESISTOR COLOUR CODE CALCULATOR. 21p.
- CONNECTING WIRE PACK. (5 x 5yd coils). 85p.  
CAST IRON VICE (Small). £2.88.  
SCREWDRIVER SET. £1.98.  
POCKET TOOL SET. £3.98.  
ILLUMINATED MAGNIFIERS. Small 2" dia (5 x mag) £1.14. Large 3" dia (4 x mag). £2.40.  
DENTISTS INSPECTION MIRROR. £2.85.  
JEWELLERS EYEGLASS. £1.50.  
HAND MAGNIFIER 3" £2.99.  
HELPING HANDS JIG. £8.30.  
EUROBREADBOARD. £6.20.  
VEROBLOC. £4.20.  
S. DEC. £3.98.  
BIMBOARD 1. £8.98.  
MIN. SPEAKERS. 8 ohm 87p, 64 ohm. 89p.  
PCB ETCHING KIT. £4.98.  
PLASTIC TWEEZERS. 69p.  
LETTERS/NUMBERS TRANSFERS. £2.48.  
SCREWS/NUTS/WASHERS—40peach. M2 pack £1.80. M3 £1.78. M4 £1.84.  
SOLDER TAGS. M3 33p/50. M4 54p/50. STICK ON FEET 23p/4.

## BOOKS (INCLUDES NEW TITLES)

- SEMICONDUCTOR DATA BOOK. Newnes. £5.90  
MICROPROCESSORS FOR HOBBYISTS. R. Coles £3.65  
PRACTICAL ELECTRONIC PROJECT BUILDING. Ainslie & Colwell £3.30  
CONSTRUCTOR'S PROJECT BOOKS  
ELECTRONIC GAME PROJECTS. Rayer £3.35  
ELECTRONIC PROJECTS FOR HOME SECURITY. Bishop £3.35  
ELECTRONIC PROJECTS IN AUDIO. Penfold £3.35  
ELECTRONIC PROJECTS IN MUSIC. Filnd £3.35  
ELECTRONIC PROJECTS IN PHOTOGRAPHY. Penfold £3.35  
ELECTRONIC PROJECTS IN THE CAR. George £3.35  
PROJECTS IN AMATEUR RADIO & SHORT WAVE LISTENING. Rayer... £3.35  
PROJECTS IN RADIO AND ELECTRONICS. Sinclair... £3.35  
ELECTRONIC PROJECTS IN HOBBIES. Rayer £3.35  
ELECTRONIC PROJECTS IN THE HOME. Bishop £3.35  
ELECTRONIC PROJECTS IN THE WORKSHOP. Penfold £3.35  
ELECTRONIC TEST EQUIPMENT PROJECTS. Ainslie £3.35  
MORE ELECTRONIC PROJECTS IN THE HOME. Filnd £3.35  
110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR Marston £3.35  
MODEL RAILWAY PROJECTS. Penfold £1.95  
SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS. Penfold £1.38  
BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS. Penfold £1.50  
ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING. Berry £1.35  
IC555 PROJECTS. Parr £1.98  
BASIC ELECTRONICS. A super book covering theory and practice. £7.98  
INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE. 320 pages. £1.75  
MICHAELS £2.95  
ELECTRONIC PROJECTS FOR CARS AND BOATS. Penfold £1.95  
SECOND BOOK OF CMOS IC PROJECTS. Penfold £1.50  
50 SIMPLE L.E.D. CIRCUITS: Book 2 £1.35  
ELECTRONIC MUSIC PROJECTS. Penfold £1.75  
ELECTRONIC HOUSEHOLD PROJECTS. Penfold £1.75  
ELECTRONIC GAMES. Penfold £1.25  
PROJECTS IN OPTO ELECTRONICS. Penfold £1.25  
52 PROJECTS USING IC 741. Redmer £1.25  
ELECTRONIC TIMER PROJECTS. Rayer £1.95  
POWER SUPPLY PROJECTS. Penfold £1.75  
REMOTE CONTROL PROJECTS. Bishop £1.95  
POPULAR ELECTRONIC CIRCUITS: Book 2 £2.35

### MAY 82 E.E. PROJECTS

- TWO TONE TRAIN HORN WITH REMOTE TRIGGER OPTION £10.53  
CAR L.E.D. VOLT METER less case £2.71  
LIGHTNING CHESS BUZZER £5.80

### ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board. Adventures with Microelectronics £2.55  
Component pack £29.64 less battery.

## ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.40. Component pack £17.98 less battery.

## MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST  
Price list included with orders or send us (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

## 1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order.

MORE E.E. KITS PLUS H.E. and E.T.I. PROJECT KITS IN THE PRICE LIST.

## TEACH IN 82

All top quality components as specified by Everyday Electronics. Our kit comes complete with FREE COMPONENT IDENTIFICATION SHEET. Follow this educational series and learn about electronics—Start Today.

LIST 1 and LIST 2 together £24.58. LIST 3 £5.98.

★ ★ ★ SPECIAL OFFER ★ ★ ★  
LISTS 1, 2 and 3 all bought together £28.95.

WOODEN CASE KIT also available £11.98—wood, formica, glue, screws etc. Cut to size.  
12 part series, reprints available of previously published parts. 45p each.

LISTS 1, 2, AND 3 ALL AVAILABLE NOW.  
ALSO WOODEN CASE KIT.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

## MAGENTA ELECTRONICS LTD.

£241, 135 HUNTER ST. BURTON-ON-TRENT, STAFFS., DE14 2ST. 0283 65435. MON.-FRI. 9-5. MAIL ORDER ONLY. ADD 45p P. & P. TO ALL ORDERS. Normal despatch by return of post. OFFICIAL ORDERS WELCOME. IRISH REPUBLIC & B.F.P.O. EUROPE: Deduct 10% from prices shown Payment, must be in Sterling. ACCESS and BARCLAYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST. SAE ALL ENQUIRIES.



# BI-PAK




**5T21 SCREWDRIVER SET**  
6 precision screwdrivers in hinged plastic case. Sizes - 0.8 1.4 2.2 4.2 9 and 3.8mm **£1.75**

**5T31 NUT DRIVER SET**  
5 precision nut drivers in hinged plastic case with turning rod. Sizes - 3 3.5 4 4.5 and 5mm **£1.75**

**5T41 TOOL SET**  
5 precision instruments in hinged plastic case. Crosspoint (Philips) screwdrivers - H 0 and H 1 Hex key wrenches - 1.5 2 and 2.5mm **£1.75**

**5T51 WRENCH SET**  
5 precision wrenches in hinged plastic case. Sizes - 4 4.5 5 5.5 and 6mm **£1.75**

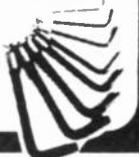BUY ALL FOUR SETS 5T21 5T51 and get **HEX KEY SET FREE**  
HEX KEY SET ON RING  
Sizes 1.5 2 2.5 3 4 5 5.5 and 6mm  
Made of hardened steel  
HX/1 **£1.25**



## BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m  
LCD 10 MEGOHM INPUT IMPEDANCE  
\* 3 1/2 digit \* 16 ranges plus hFE test facility for PNP and NPN transistors \* Auto zero auto polarity \* Single-handed pushbutton operation \* Over range indication \* 12.5mm (1/2 inch) large LCD readout \* Diode check \* Fast circuit protection \* Test leads battery and instructions included  
Max indication 1999 or - 1999  
Polarity indication Negative only  
Positive readings appear without + sign  
Input impedance 10 Megohms  
Zero adjust Automatic  
Sampling time 250 milliseconds  
Temperature range -5°C to 50°C  
Power Supply 1 x PP3 or equivalent 9V battery  
Consumption 20mW  
Size 155 x 88 x 31mm  
RANGES  
DC Voltage 0-200mV  
0-2-20-200-1000V Acc 0.8%  
AC Voltage 0-200-1000V  
Acc 1.2% DC Current 0-200uA  
0-2-20-200mA 0-10 A Acc 1.2%  
Resistance 0-2-20-200K ohms  
0-2 Megohms Acc 1%  
BI-PAK VERY LOWEST POSS PRICE  
**£35.00 each**



## MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a thickness of 1 1/2". The 2 1/2" jaws open to max of 1 1/2". Approx size 80 x 120 x 66mm  
Bi-Pak's Mini Vice at a Mini Price only

**£2.50**

ORDER NO. SX82



## The Third and Fourth Hand...



... you always need but have never got until now  
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2 diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**  
Without magnifier ORDER NO. T400 **£4.75**

## BI-PAK SOLDER-DESOLDER KIT

Kit comprises ORDER NO. SX80  
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit  
1 Quality Desoldering pump High Suction with automatic ejection Knurled anti-corrosive casing and teflon nozzle  
1.5 metres of De-soldering braid on plastic dispenser  
2 yds (1.83m) Resin Cored Solder on Card  
1 Heat Shunt tool Tweezer type  
Total Retail Value over **£12.00**  
OUR SPECIAL KIT PRICE **£8.05**



## BI-PAK PCB ETCHANT AND DRILL KIT


Complete PCB Kit comprises  
1 Expo Mini Drill 10 000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit  
1 Sheet PCB Transfers 210mm x 150mm  
1 Etch Resist Pen  
1 1/2 lb pack FERRIC CHLORIDE crystals  
3 sheets copper clad board  
2 sheets Fibreglass copper clad board  
Full instructions for making your own PCB boards  
Retail Value over **£15.00**  
OUR BI-PAK SPECIAL KIT PRICE **£9.75**  
ORDER NO. SX81


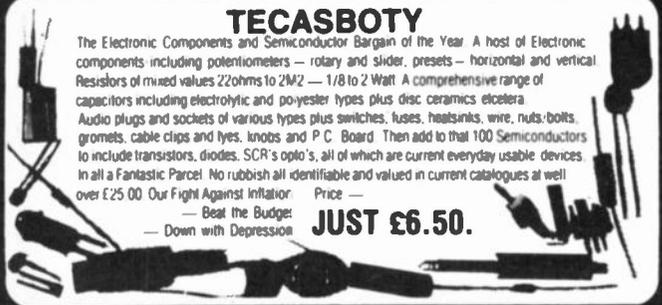
## TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers - rotary and slider, presets - horizontal and vertical Resistors of mixed values 22ohms to 2M2 - 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts, bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation Price -

— Beat the Budget.  
— Down with Depression  
**JUST £6.50.**



Send your orders to Dept. EE7,  
BI-PAK PO BOX 6 WARE HERTS.  
SHOP AT J BALDOCK'S  
WARE HERTS



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.  
Remember you must add VAT at 15% to your order. Total. Postage add 75p per Total order.

# WILMSLOW AUDIO

The firm for Speakers

Just **50p** will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits . . .

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS.  
GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

★ Lowest prices — Largest stocks ★  
★ Expert staff — Sound advice ★

★ Choose your DIY HiFi Speakers in the comfort of our listening lounge.  
(Customer operated demonstration facilities)

★ Ample parking ★

★ Access Visa American Express accepted ★



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



**METERS: 110 x 82 x 35mm**  
30µA, 50µA, 100µA. **£5.90.**  
Post 50p.

**METERS: 45 x 50 x 34mm**  
50µA, 100µA, 1mA, 5mA, 10mA, 25v, 1A, 2A, 5A 25V.  
**£2.90.** Post 30p.

**METERS: 60 x 47 x 33mm**  
50µA, 100µA, 1mA, 5mA, 10mA, 100mA, 1A, 2A, 25v, 50v, 50-0-50µA, 100-0-100µA. **£4.76.**  
VU meters. **£5.32.**  
Post on above meters 30p.

**Silicone grease 50g £1.32 Post 14p.**

**NI-CAD BATTERY CHARGER**  
Led indicators charge-test switch. For PP3, HP7, HP11 & HP2 size batteries.  
Price **£5.85** Post 94p.

**MULTI-METER**  
7N 360TR  
20,000 ohm/volt  
DC Volts: 0-1, 0-5, 2.5, 10-150—250-1,000v.  
AC Volts: 10-50, 250-1,000

**RESISTANCE RANGES**  
X1, X10, X1K, X10K  
**£14.10**  
P.&P. 87p



## TRANSFORMERS

**240v Primary**

3-0-3v	100mA	<b>82p</b>
6-0-6v	100mA	<b>87p</b>
6-0-6v	250mA	<b>£1.22</b>
12-0-12v	50mA	<b>92p</b>
12-0-12v	100mA	<b>£1.15</b>

Post on above transformers 48p.

9-0-9v	1A	<b>£1.80</b>
12-0-12v	1A	<b>£2.40</b>
15-0-15c	1A	<b>£2.60</b>
6-3v	1 1/2A	<b>£1.80</b>
6-0-6v	1 1/2A	<b>£2.10</b>

Post on above transformers 87p.

All above prices include V.A.T. Send 80p for new 1982 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

All goods despatched within 3 days from receipt of the order.

# M. DZIUBAS

158 Bradshawgate, Bolton  
Lancs. BL2 1BA

# LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Self-assembly simulated wood cabinet. £4.50 + £1.50 p+p.

Featured in April issue Practical Electronics, reprint 50p. Free with Kit.




## P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP ● TAPE COUNTER
- SWITCHABLE E.Q.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

INTRODUCTORY OFFER - ONLY  
**£32.95**  
+ £2.75 p&p.

## STEREO AMPLIFIER KIT

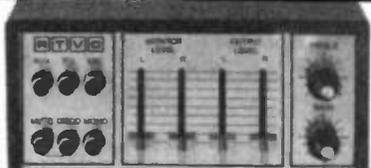

- Featuring latest SGS/ATES TOA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/2" x 3 1/2" (approx).
- 10+10 Stereo converts to a 20 watt Oisco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with kit.

**£16.50**  
+ £2.90 p&p.

**SPECIFICATIONS:** Suitable for 4 to 8 ohm speakers  
40Hz - 20KHz  
P.U. 150mV. Aux. 200mV.  
Mic. 1.5mV.  
Bass ±12db @ 60Hz  
Treble ±12db @ 10KHz  
0.1% typically @ 8 watts  
220 - 250 volts 50Hz.


**8" SPEAKER KIT** Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p, when purchased with amplifier. Available separately £6.75 & £1.70 p+p.

## 125W HIGH POWER AMP MODULE

KIT: **£10.50** BUILT: **£14.25**  
+ £1.15 p&p + £1.15 p&p.

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

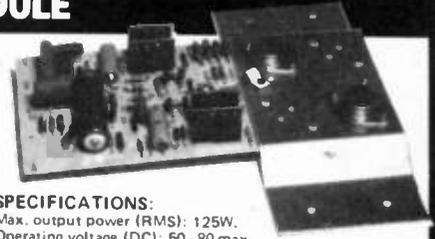
**ACCESSORIES:** Suitable mains power supply kit with transformer: £7.50 plus £3.15 p&p.  
Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



### SPECIFICATIONS:

Max. output power (RMS): 125W.  
Operating voltage (DC): 50 - 80 max.  
Loads: 4 - 16 ohms.  
Frequency response measured @ 100 watts: 25Hz - 20KHz.  
Sensitivity for 100 watts: 400mV @ 47K.  
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.  
Dimensions: 205 x 90 and 190 x 36 mm.

## HI-FI SPEAKERS AT BARGAIN PRICES

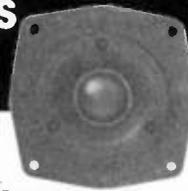

### GOODMANS TWEETERS

Bohm soft dome radiator tweeter (3 1/2" sq.) for use in up to 40W systems; with 2 element crossover.

£3.50 each (p&p £1) or £5.95 pair (p&p £2).

### 35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4" app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIF11JSM. Complete with U2M, 2 element crossover. Total impedance of system 4 ohms.



£7.95  
PER SET + £2.70 p&p.


## P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

**FEATURES:** VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

**£17.95**  
Plus £2.50 p&p.

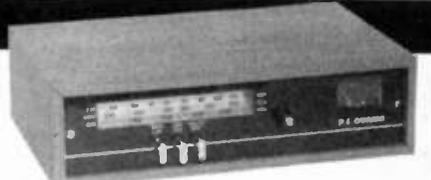
Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/2" x 8 1/2" x 3 1/4".  
£3.50 Plus £1.50 p&p.



### SPECIAL OFFER! TUNER KIT PLUS:

• Matching I.C. 10 watt per channel Power amp kit. + Mullard LP1183 built pre-amp, suitable for ceramic pick-up and aux. inputs. • Matching power supply kit with transformer. • Matching set of 4 slider £21.95 controls for bass, treble and volumes. + £3.80 P&P.
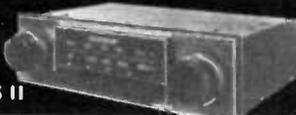
## PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II



### 2 WAVE BAND, MW - LW

- Easy to build. • 5 push button tuning. • Modern design. • 6 watt output. • Ready etched and punched PCB. • Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.) available as a complete kit. £2.50/pack + £1.50 p&p.

**£12.95**  
+ £2.00 p&p.


## BIRDAUDIO STEREO CAR RADIO BOOSTER



To boost your car radio or radio cassette to 15W r.m.s. per channel.

**£9.95** + £1.50 p&p.

## TV SOUND TUNER KIT

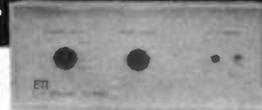

**£11.45**  
+ £1.50 p&p.

As featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case.

• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation. £1.95 + 75p p&p.

## MONO MIXER AMP



**£39.95**  
+ £3.70 p&p.

**50 WATT** Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux inputs. Size: 13 1/2" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

ALL MAIL TO:  
21A HIGH STREET, ACTON, W3 6NG.

Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope. All items subject to availability. Prices correct at 31/1/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch.

ALL PRICES INCLUDE VAT AT 15%.

ALL CALLERS TO: 323 Edgware Rd, London W2. Telephone: 01-723 8432. Open 9.30 - 5.30pm. Closed all day Thursday. RTVC Limited reserve the right to update their products without notice.



# Everyday ELECTRONICS

VOL. 11 NO. 7 JULY 1982

#### Editor

F. E. BENNETT

#### Assistant Editor

B. W. TERRELL B.Sc.

#### Production Editor

D. G. BARRINGTON

#### Technical Sub-Editor

G. P. HODGSON

#### Art Editor

R. F. PALMER

#### Assistant Art Editor

P. A. LOATES

#### Technical Illustrator

D. J. GOODING Tech. (CEI)

#### Secretary

JACQUELINE DOIDGE

#### Editorial Offices

KINGS REACH TOWER

STAMFORD STREET

LONDON SE1 9LS

Phone: 01-261 6873

#### Advertisement Manager

R. SMITH

Phone: 01-261 6671

#### Representative

R. WILLETT

Phone: 01-261 6865

#### Classified Supervisor

B. BLAKE

Phone: 01-261 5897

#### Make-Up and Copy Department

Phone: 01-261 6615

#### Advertisement Offices

KINGS REACH TOWER

STAMFORD STREET

LONDON SE1 9LS

## MAKING CONTACT

Anyone wanting to try their hand for the first time at electronic circuit construction but who happens to be deterred by the need to make soldered connections will find a very simple method for wiring up components illustrated in the *Two-Way Intercom* project this month. Component and inter-wiring connections are made via screw terminal blocks and the only tools required are commonplace implements found in every home: a small screwdriver and something with which to cut wire.

The finished project, which is based around two transistors, is a perfectly practical system permitting speech communication over a distance of up to 25 metres, using a two-wire interconnecting link between the two units. So while demonstrating that some electronic circuits can be constructed without recourse to soldering, the completed equipment can be put to use within different areas of a house, or between house and out-building.

This is just one example of the kind of simple electronic circuits that may be assembled using solderless techniques. Various other projects can be built this way and we expect to publish more from time to time.

For the benefit of those not familiar with these things, it should be explained that there is nothing new about solderless techniques. Time was when every electrical connection was made by terminal screw, but that was in those far off days of wireless set construction in the 'twenties.

It has to be admitted that this method of construction has its limitations and is not universally applicable, nor suitable to all kinds of electronic circuits or components. We do not offer it as a serious alternative to conventional methods for hard-wiring using soldered joints. The attractiveness of the solderless method is that—within its limitations—it makes circuit construction very easy and something that can be tackled by anyone unfamiliar with electronics since it calls for no special skills, materials, or tools. It can be employed with advantage to assemble simple basic circuits quickly, as required for demonstration or experimental purposes.

We hope that anyone who makes a start in electronics by building this Intercom will be excited and pleased with the results and thus stimulated to pursue this hobby further. This will necessitate, in due course, acquiring the ability to use a soldering iron. But there is nothing frightening about soldering and articles explaining this in step-by-step fashion appear frequently in our pages.



#### Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

#### Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

#### Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price 80p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.


#### Binders

Binders to hold one volume (12 issues) are available from the above address for £4.80 inclusive of postage and packing worldwide. Please state which Volume.

#### Subscriptions

Annual subscription for delivery direct to any address in the UK: £11.00. Overseas: £12.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, Kings Reach Tower, Stamford Street, London SE1 9LS.

# MODEL CAR Lap Counter & Judge

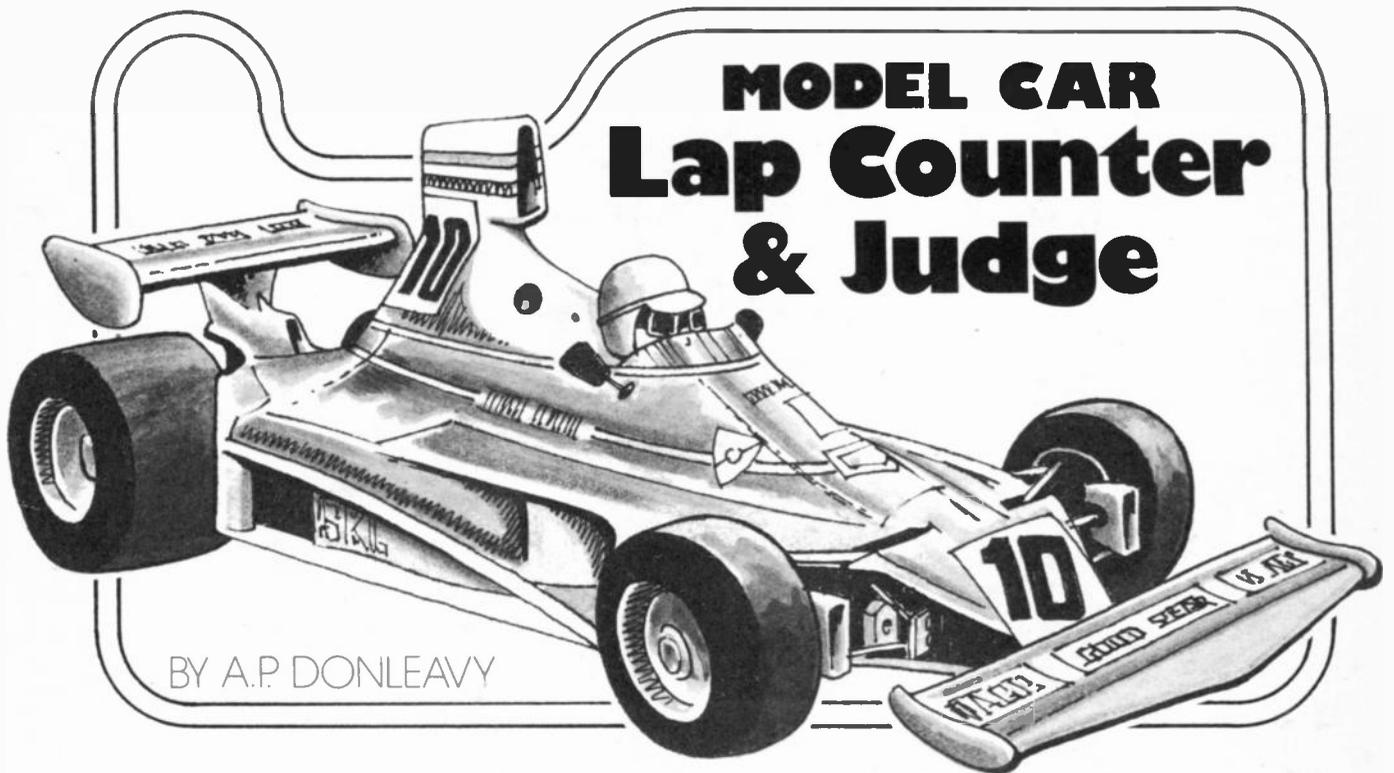

BY A.P. DONLEAVY

**D**ESCRIBED here, especially for the slot car racing enthusiast, is an electronic lap counter for a two lane racetrack. Each track has its own counter circuit, able to count either up or down, and in the count up mode there is also a win indicator for the first car to pass the 100 lap mark.

The cars are detected by two phototransistors buried in the track and as the car passes overhead, it momentarily interrupts the ambient light falling onto the light-sensitive base region of the phototransistor, thus creating a pulse.

## CIRCUIT OPERATION

The full circuit diagram is shown in Fig. 1. Each track has an identical counting circuit so only the first counter need be described.

Phototransistor TR1, mounted into the track, is the detector and under normal lighting conditions there is enough ambient light to hold the device on and the collector will be at nearly 0V due to volt drop across R1.

As the car interrupts the light, the current through TR1 drops and hence the collector voltage rises. This pulse is fed to pin 13 of IC1a, a CMOS NOR gate, which with IC1b, R2 and C1 forms a monostable multivibrator to provide a single clean pulse with a period of approximately 0.6 seconds. Once triggered, the monostable ignores any further voltage change at pin 13 for the duration of the timing period, thus eliminating any problems of jitter or multiple pulses from the detector and the car will have completely passed over it by the end of the 0.6 second period.

This pulse is connected to either pin 9 or 7 of IC2 via switch S1. IC2 is a 40110 CMOS decade up/down counter and display driver for a single seven segment display. With the input connected to pin 9, the counter will count up from 0 to 9, and down from 9 to 0 with the input on pin 7. This i.c. also has a latch facility but as this circuit does not use it, pin 6, the LATCH ENABLE input, is tied down to ground.

## UP OR DOWN

So IC1 counts up or down one digit each time the phototransistor "sees" a car and displays the result on X1a.

Resistors R5 and R6 prevent the unused input from floating, which would lead to random counting.

When the count on IC1 goes from 9 back to 0 (in the count up mode, a short negative going pulse emerges from pin 10, the CARRY output, and this is connected to the count up input, pin 9, of another 40110 i.c. IC3, driv-

ing the second (most significant) digit, thus permitting the count to go from 09 to 10. In the count down mode, this negative pulse emerges from pin 11, the BORROW output, when the count goes from 0 to 9, and is connected to the count down input pin 7, of IC3.

In this way, the decade counter i.c.s can be cascaded in series to provide as many digits as required, in this case, only two.


Both counter circuits can be reset to zero by pressing S2, which momentarily connects all the RESET inputs to the positive supply.

## WIN INDICATOR

The win indicator is based around IC6, a 4013 CMOS dual D-type flip-flop. Each flip-flop has a DATA and a CLOCK input and two outputs, Q and  $\bar{Q}$ . When a positive going pulse is applied to the CLOCK input, the logic state of the DATA input is transferred to the Q output, the  $\bar{Q}$  output automatically taking on the opposite state.

On receipt of a high level on the RESET inputs of both flip-flops in IC6 (pins 4 and 10), the Q outputs will be returned to logic 0 and the  $\bar{Q}$  outputs to logic 1. With IC6 wired as shown, that is the  $\bar{Q}$  of the first flip-flop connected to the DATA input of the second and the  $\bar{Q}$  of the second flip-flop connected to the DATA input of the first, both flip-flops are set ready for the  $\bar{Q}$  outputs to go high upon receiving a clock pulse.

Hence the first counter to reach 100 laps will send a pulse from the CARRY output (pin 10 of IC3 or IC5) to trigger the relevant flip-flop and turn

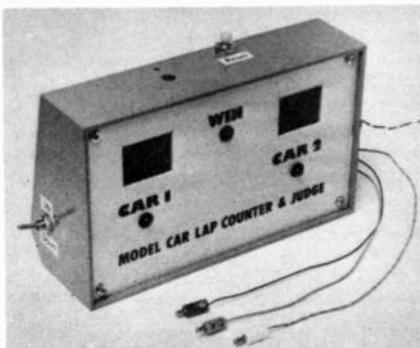

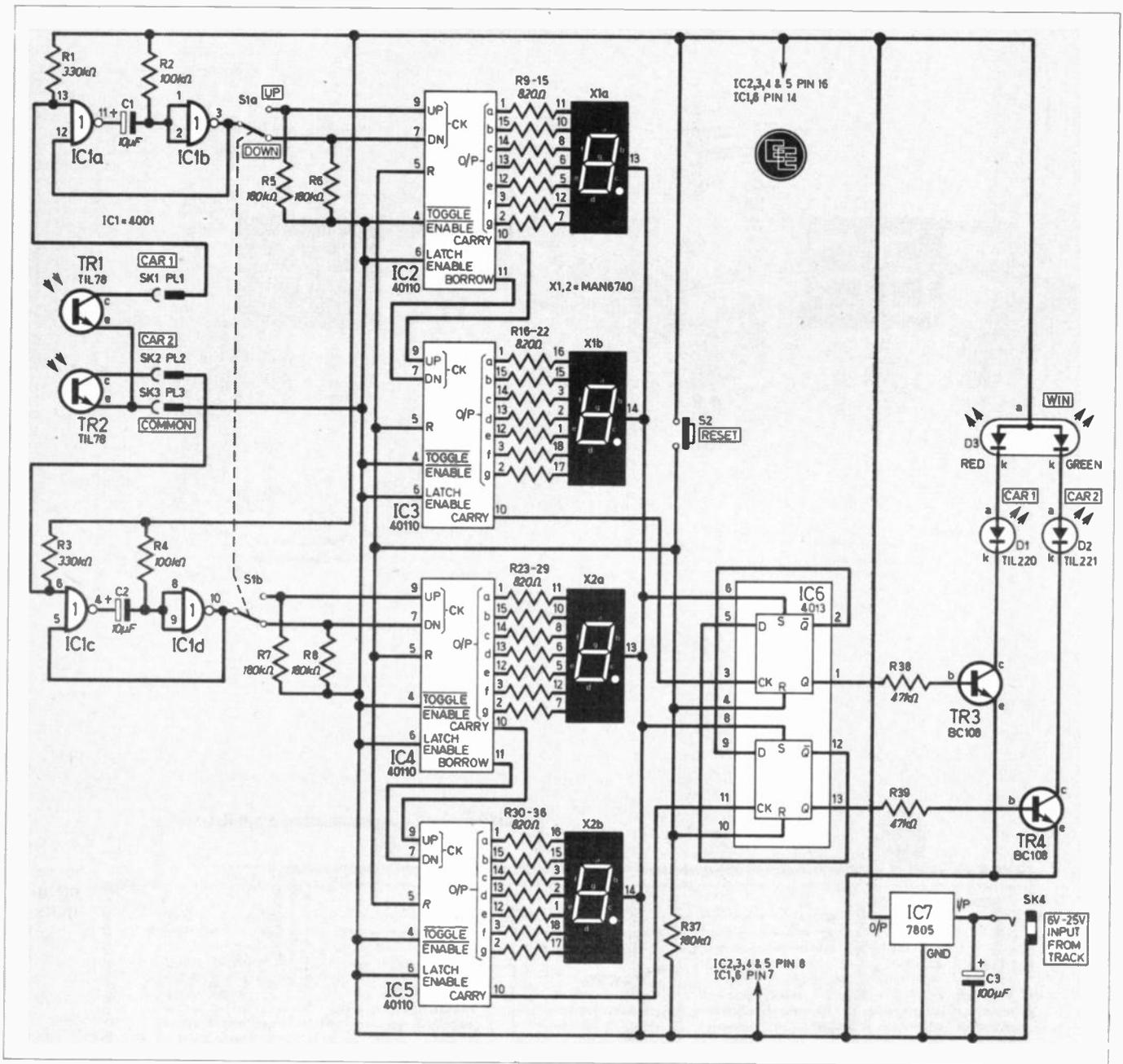


Fig. 1. Complete circuit diagram of the Model Car Lap Counter and Judge.

on the corresponding l.e.d., D1 or D2. The Q output of the winning flip-flop (and hence the DATA input of the losing flip-flop) will now be at logic 0 resulting in no change at the Q output of the losing flip-flop when the losing counter circuit also reaches 100.

### RESET

Thus only one l.e.d., the winner, will light and further pulses to either CLOCK input will not change the state of the outputs until the RESET button S2, has been pressed.

The win indicator can only be used in the count up mode, because the counters send their signal to the flip-flops at a count of 99 which would

occur after only one lap in the count down mode!

The power supply of the Lap Counter uses a five volt regulator, IC7, enabling any power source from 6 to 25V to be used without any modification to the circuitry. The author used a nine volt calculator adaptor but a battery or the power from the track itself could also be used. The power input is via a 2.5mm jack socket, the tip being positive.

### COMPONENTS

Resistors R5 to 8 and 37, the pull down resistors, are quoted as 180 kilohms but in fact are not critical and can be any value from 10 kilohms to one megohm.

The segment current limiting resistors, R9 to 36, were chosen to limit the total supply current to about 120mA, consistent with sufficient display brightness. If supply current is not restricted, then reducing the value of these resistors will give a brighter display. The specified regulator i.c. will supply 1A maximum.

Note that D3, the tri-colour l.e.d. is optional and can be omitted, the anodes of D1 and D2 must then be connected to the positive. The displays X1 and X2 can be any common cathode, two digit, seven segment display should the MAN6740 be difficult to obtain. However, in order to fit the p.c.b. the displays must be 18 pin d.i.l. packages on a 0.6 inch lead spacing.

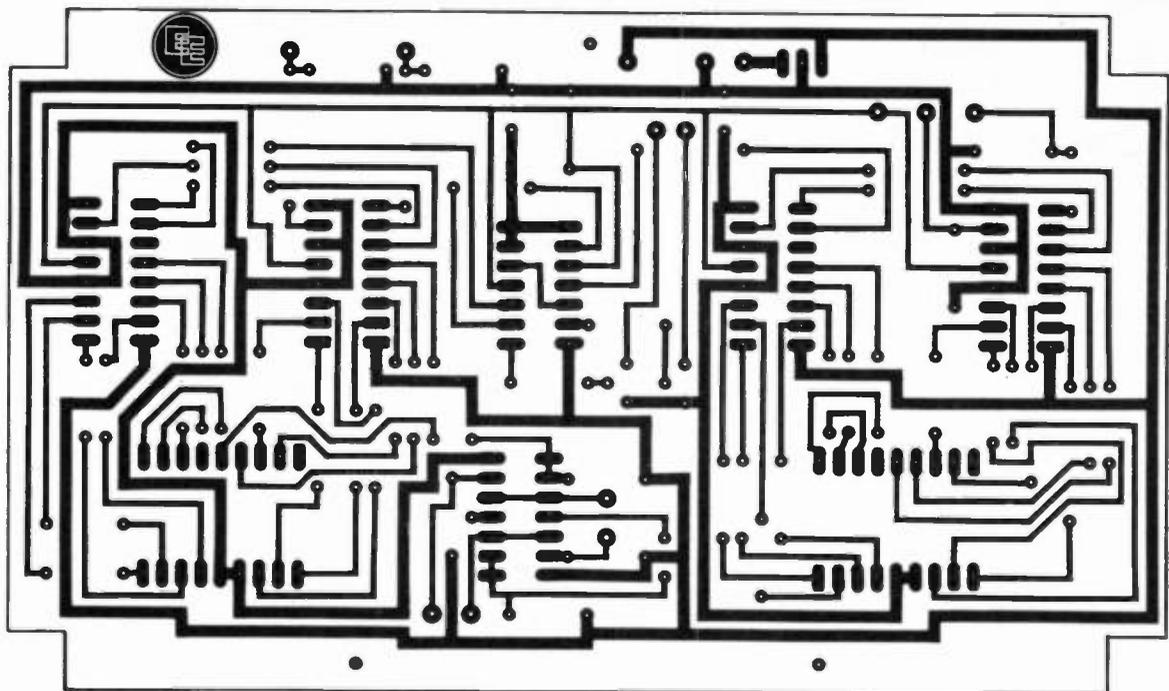
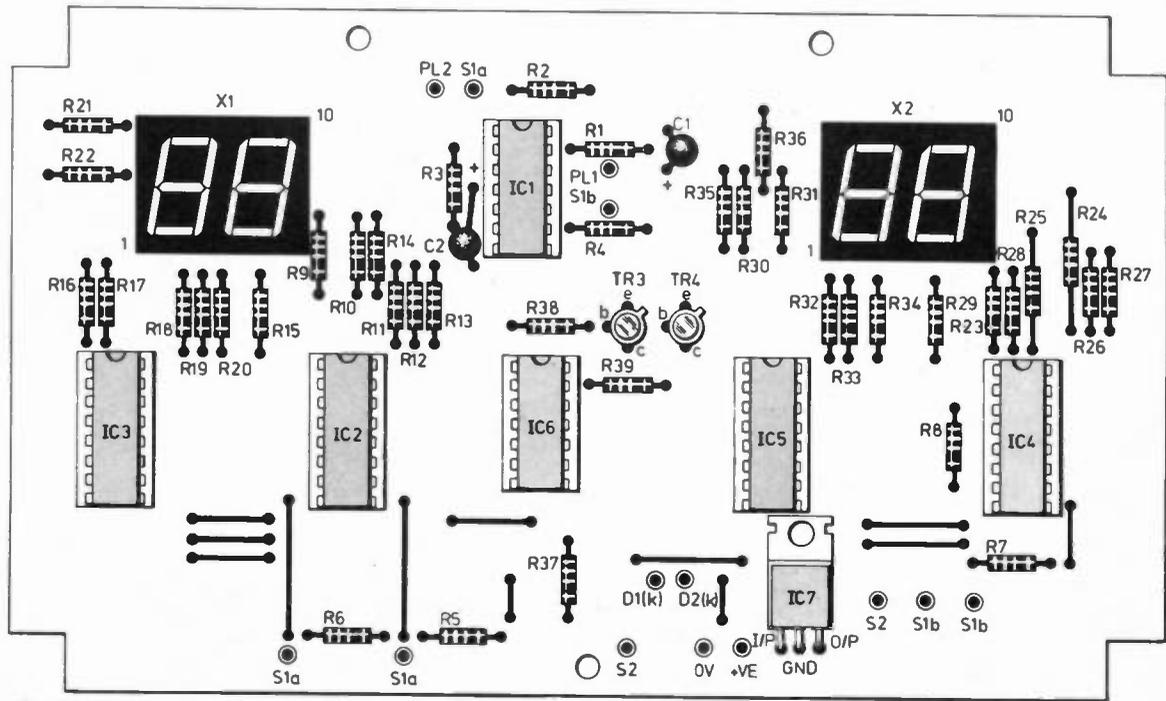


Fig. 2. Full size printed circuit board artwork and component layout for the Lap Counter and Judge.

# CONSTRUCTION starts here


## CIRCUIT BOARD

The circuit was built on a printed circuit board and the track pattern for this is shown, full size, in Fig. 2 along with the component layout on the top side. The board measures 152 x 88mm and has the corners cut as shown, to fit into the console case.

The layout is considered to be suitable for production with an etch resist pen but etch resistant rub-down transfers will probably give a better result.

When it comes to assembling the p.c.b. holders are recommended for all i.c.s and the displays are mounted into Soldercon strip connectors, although they could be soldered directly to the board without any damage.

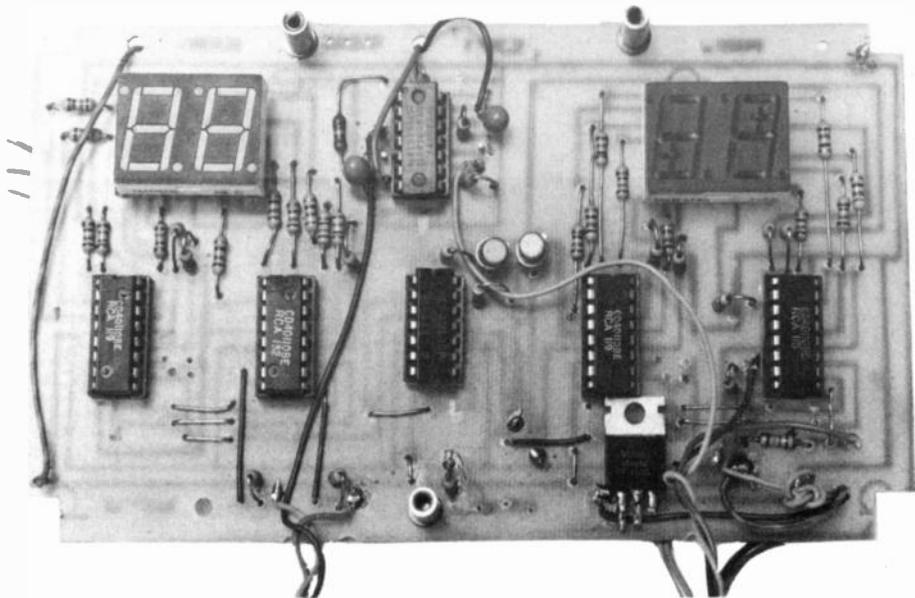All other components should be soldered into place, observing the



The assembled p.c.b. from the prototype.

polarity of the capacitor and the orientation of the transistors. Links are to be kept as tight as possible and sleeved if there is any risk of them shorting out on an adjacent component.

All flying leads to be terminated on the board with a Veropin.

## CONSOLE

The unit is housed in an inexpensive console type case with the p.c.b. assembly mounted beneath the aluminium lid on three 13mm long 6BA spacers.

When marking the positions of these mounting holes and the two rectangular display windows on the lid, the p.c.b. may be used as a template (prior to any components being soldered into the board). The mounting holes are 3mm diameter and each window measures 22 x 28mm.

Three additional holes, 6.4mm diameter, are needed for D1, D2 and D3 and the approximate positions of these are shown in the accompanying photographs. Care should be taken here to ensure that these l.e.d.s do not foul any components on the board.

The two switches and jack socket SK4 are mounted in convenient positions in the sidewalls of the case and the three leads to the phototransistors mounted into the racetrack all pass through another hole in the case and will be terminated with the banana plugs PL1, 2 and 3.

The red polarised filter has to be cut into two pieces and glued in position behind the two window cut-outs.

## FINAL ASSEMBLY

Insert l.e.d.s D1, 2 and 3 into the lid with the special mounting clips and solder to the corresponding flying leads from the p.c.b. as shown in Fig. 3. The board can now be mounted to the lid using the 6BA screws and spacers.

Solder the correct leads from the p.c.b. to the switches and jack socket, and the three leads to the phototransistors can now be threaded through the relevant hole and clamped tightly with a ratchet type cable tie

## COMPONENTS

### Resistors

R1, 3	330k $\Omega$ (2 off)
R2, 4	100k $\Omega$ (2 off)
R5-8, 37	180k $\Omega$ (5 off)
R9-36	820 $\Omega$ (28 off)
R38, 39	47k $\Omega$ (2 off)
All $\frac{1}{4}$ W carbon $\pm 5\%$	

### Capacitors

C1, 2	10 $\mu$ F 16V tantalum bead (2 off)
C3	100 $\mu$ F 40V elect

### Semiconductors

D1	TIL220 0.2 inch red l.e.d.
D2	TIL221 0.2 inch green l.e.d.
D3	Tri-colour l.e.d. common anode
TR1, 2	TIL78 silicon npn phototransistor (2 off)
TR3, 4	BC108 silicon npn (2 off)
IC1	4001B CMOS quad 2-input NOR gate
IC2-5	40110B CMOS decade counter/driver (4 off)
IC6	4013B CMOS dual D-type flip-flop
IC7	7805 5V, 1A voltage regulator, TO-220 case
X1, 2	MAN6740 2 digit, common cathode seven segment display (2 off)


### Miscellaneous

S1	d.p.d.t. miniature toggle switch
S2	Push-to-make, momentary action switch
SK1	2.5mm banana socket, red
SK2	2.5mm banana socket, green
SK3	2.5mm banana socket, white
SK4	2.5mm jack socket
PL1	2.5mm banana plug, red
PL2	2.5mm banana plug, green
PL3	2.5mm banana plug, white

Single sided glass fibre p.c.b. 152 x 90mm; console type case 160 x 95 x 60 (rear) x 40 (front) with aluminium lid; 16-pin i.c. holder (4 off); 14-pin i.c. holder (2 off); Soldercon strip i.c. holder, 36 way; 5mm l.e.d. mounting clip (3 off); polarised red filter, 105 x 35mm; 7/0.2 p.v.c. sleeved equipment wire; 6BA spacers, 13mm long (3 off); 6BA screws, 6mm long (6 off).

COMPONENTS  
approximate  
cost £25.00

See  
**Shop  
Talk**  
page 455

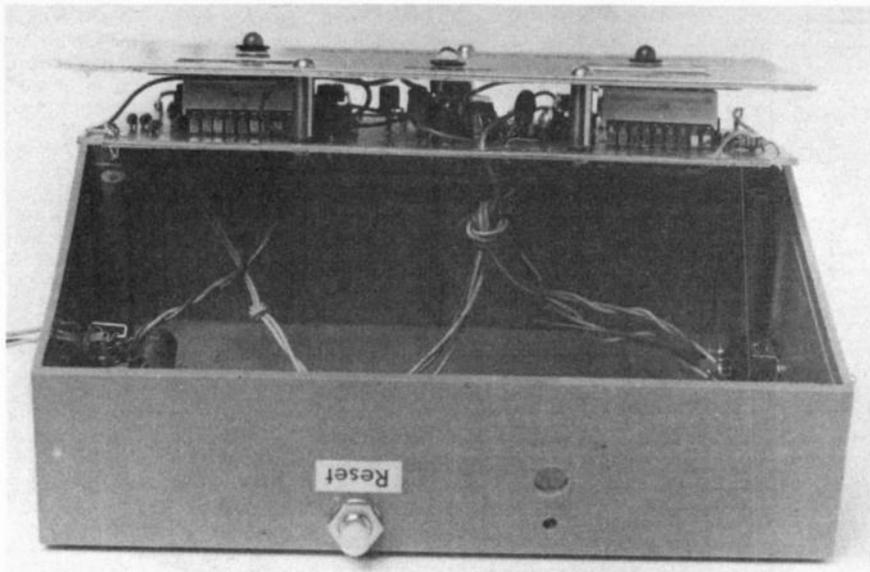

View inside the console showing the p.c.b. mounted beneath the lid.

to prevent them being pulled through. The banana plugs can now be added, taking care to get the colours right as the red plug (PL1) corresponds with the red l.e.d., (D1) win indicator.

Note that C3 is soldered directly to the terminals of jack socket SK4.

The lid can now be secured.

### PHOTOTRANSISTORS

To mount the phototransistors TR1 and TR2, drill holes in the track such that they will be a tight fit and secure with glue. It is necessary to choose the position of these devices such that the car will obscure the light from the cell when passing over it.

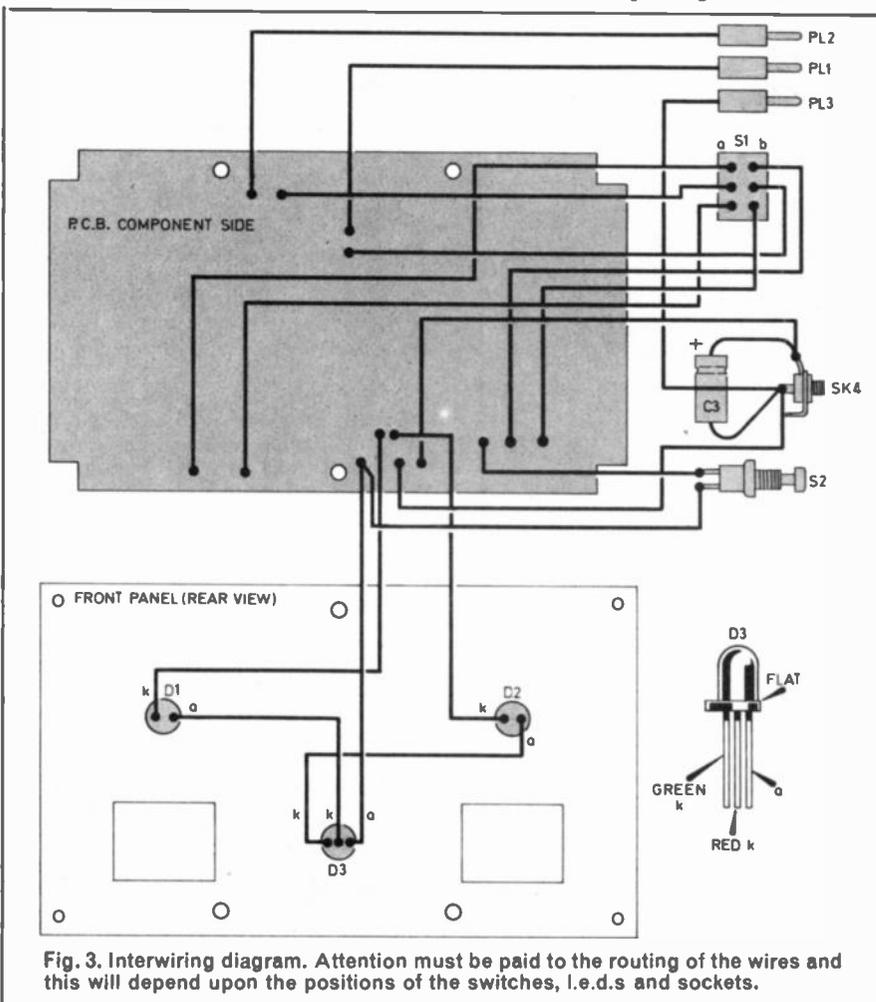


Fig. 3. Interwiring diagram. Attention must be paid to the routing of the wires and this will depend upon the positions of the switches, l.e.d.s and sockets.

The 2.5mm banana sockets are mounted on the edge of the track. Choose a straight piece of track for the cells and sockets otherwise a car skidding round a corner may hit them.

### TROUBLE SHOOTING

If the p.c.b. has been accurately reproduced then any malfunctions of the circuit will almost certainly be wiring errors or faulty components.

Should one or both of the counters not function then the fault may be due to reversed connections to the phototransistors. The functioning of the phototransistors can be checked by measuring the voltage at the collector with light falling on, and absent from, the light sensitive face. These should be 0.2 and 4.8V respectively.

The function of the monostable can also be checked by measuring the voltage at ICI pin 3. On interrupting the light to the photocell, the voltage at pin 3 should rise to approximately five volts for half a second and then fall back to zero.

Voltages at pins 10 and 11 of IC2 to IC4 should be five volts, if not then suspect a faulty i.c. Check also the pins tied to ground are in fact at zero volts and if not then there is probably a bad soldering connection.

If only one counter circuit is working, it is possible to transpose all the i.c.s from the faulty counter, one by one, to the good counter and thus isolating the malfunctioning i.c. when the fault itself is transferred. This highlights one of the many advantages of using i.c. holders.


### IN USE

In most situations, the ambient lighting will be sufficient to trigger the phototransistor. If difficulties arise, locate the track piece containing the detectors near to a light or window. If this proves to be impractical then a table lamp placed in the proximity of the track will give sufficient light for the sensors.

If the counters increment continuously, this indicates that the light level is on the threshold of being too low.

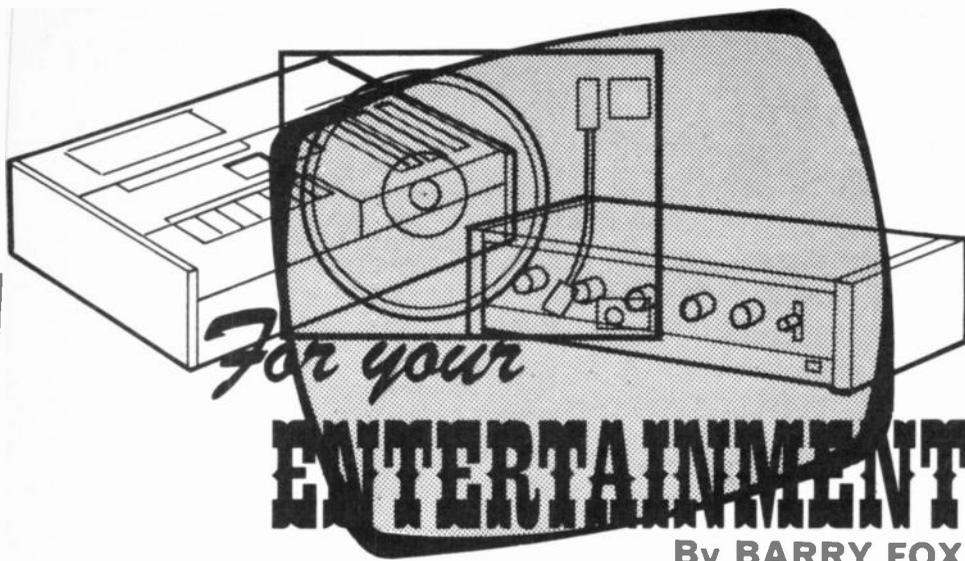Finally a shorter race, or even a handicap race can be arranged by putting the counter in the COUNT DOWN mode and passing your hand over each sensor until the required starting point is reached for each track. Then switch to the COUNT UP mode and start the race. □





## Cable Shock

Publication of our feature on optical fibre technology coincided not only with British Telecom's plans for more fibre 'phone links across the country, but also publication of an official report on the future of cable TV systems in Britain. These will rely, in part, on optical fibres. But note well those words "in part".

The cable TV report was prepared for the Prime Minister by the Information Technology Advisory Panel, set up in July 1981 "to ensure that Government policies and actions are securely based on a close appreciation of market needs and opportunities". The Panel was charged with keeping the Prime Minister and her colleagues up to date on "all aspects of information technology".

Essentially the ITAP report proposes that Britain should have a private enterprise cable TV system by the mid-80's. This would tie in with the proposed inauguration of a direct broadcasting satellite system to be run by United Satellites (the consortium of British Telecom, British Aerospace and GEC-Marconi). The panel proposes that Britain should be cabled with main trunk lines of optical fibres capable of carrying very wide bandwidth signals, and thus as many channels of video and digital data as are likely to prove necessary for the 1990's and even 21st century.

Unfortunately, the panel makes the potentially disastrous recommendation that these optical fibre links should not extend right into the home. Instead these will terminate at switching stations, probably at the end of each street, each handling fifty or one hundred homes.

These switching stations will receive all channels through the optical fibre link but connect with local homes through a coaxial link of greatly restricted bandwidth. According to the panel this will be adequate because "each subscriber (whether in a home or business) only needs simultaneous access to, at most, a few channels (so) there seems little need to provide all channels down the final links all the time".

This seems a terribly short sighted view point, especially bearing in mind the fact that the links won't be laid until the mid or late 80's. Also the panel is recommending that the cable system will be useful for business applications because it "enables information to be exchanged

between computers and word processors".

The inescapable conclusion is that the proposed coaxial links are likely to be inadequate even before they are laid!

## Short Sighted

The reasoning behind this short sighted proposal is even more disturbing. The panel compared the cost of laying optical fibre inter-active links into each home, with that of laying coaxial links.

The panel only asked British Telecom for an estimate on the cost of the optoelectronics necessary. This produced a minimum cost per home of between £1,500 and £1,700. The panel believes that it will only cost £200 or £300 to provide a coaxial link with the necessary command switching for the local sub-station.

Even if these estimates are correct (which seems unlikely) they are at today's prices. By the mid or late 80's when the system is being laid, opto-electronics will be commonplace and cheap.

In Japan it is already possible to buy a complete laser diode and photo receptor unit, the Taos made by Olympus, for between 40,000 and 50,000 yen, which is around £100. These units are still being made only in a small quantity, but the optics are formed as a single integrated unit. So the price will drop dramatically over the next few years.

By the mid 80's, when Britain is ready for cabling, they could cost only a few pounds each. What a pity the ITAP committee didn't talk to Olympus before publishing its report.

## Obsolete System

If the Prime Minister and Government go along with the panel's proposals, we could end up with an obsolete cable system based on obsolete coaxial technology, which actually costs more than a full bandwidth system based on optical fibre technology.

## Music For Pleasure

Music for Pleasure, the budget EMI record label, puts out some interesting re-issues. One does get the feeling, however, that there's a budget interest on the part of MFP. For instance, the wonderful André Previn, Shelly Manne, Leroy Vinegar jazz trio recording of songs from

*My Fair Lady* is a very welcome re-issue, even though it's clearly motivated by a more recent Previn recording on the EMI label which is plugged on the MFP sleeve.

A string of Previn trio recordings were made in the Contemporary Studio in Los Angeles between 1956 and 1958. Although most of these recordings were made before the RIAA standardisation on disc stereo (in March 1958) they were all taped in stereo, using AKG C12 condenser microphones, an Ampex recorder and Reeves Soundcraft tape. Roy DuNann was the engineer.

What a pity therefore that the MFP recording has been reissued with *Mono* stamped on the disc centre label and no mention on the sleeve of the fact that it is one of the earliest jazz stereo recordings. To confuse things further the mono disc is packed in a sleeve labelled Stereo. It is, by the way, cut in stereo.

## Live Performance

Another MFP re-issue is the Beach Boys *Live in London*. Here the sleeve note explains how in the days of *Good Vibrations* "many critics wondered aloud whether the group were capable of reproducing anything even vaguely resembling their recorded sound when making live in-person appearances".

Most of The Beach Boys recorded material was, of course, meticulously polished in the studio with re-mixing and over-dubs. "But," continues the sleeve "the group reached a level of polished stage performances . . . (and) this album, recorded at the peak of the group's prowess encapsulates the atmosphere of one of their live concerts".

Well, if my memory serves me well, the Beach Boys concert encapsulated on the MFP label was taped at the London Palladium on December 1, 1968. The group, fresh from recording in Californian studios, insisted on an 8-track system for their live concert taping in London.

Two 8-track recorders were rustled up, one dismantled from a fixed mount in Chappell's Studios, and the concert was duly multi-tracked. The tapes went back to California for re-mixing where all the sound of the London pit band had to be lost for Union reasons.

The group then spent so long on cleaning up their vocal and instrumental tracks that in the end the only untouched original material on the tape was a track of audience atmosphere and applause. The final result, which you can hear on the MFP record, is superb.

## Closed Shop

The biggest problem with buying an MFP record can be finding it. They are sold in shops like Woolworths whose assistants often know next to nothing about what's available. Other record shops have a rather snobbish attitude.

I asked at my local specialist record shop for the Classics for Pleasure re-issue of Stokowski's version of *Carmine Burana*, which is interesting both for Stokowski's treatment of the music and as an example of early stereo (it was recorded soon after RIAA standardisation). "We don't have it" they told me.

"Why? Because it's out of stock or you don't stock budget labels?" I asked. "Because it's not very good" they told me and returned to the more important job of talking amongst themselves.

The shop is now closed I note.



A COMPACT POCKET-SIZED CONSTANT PITCH OSCILLATOR FOR THE MUSICIAN. GENERATES NOTE A ABOVE MIDDLE C (440Hz) MAKING IT AN INVALUABLE TUNING AID FOR THE VIOLIN PLAYER AND OTHERS.

# ELECTRONIC PITCH PIPE

BY I. HICKMAN

FOR the accurate tuning of musical instruments, particularly the violin, some source of accurate pitch, usually the A above middle C, is required. Many homes have a piano, which solves the problem for the violinist at home, but when no piano is at hand (and the group of players does not include an oboeist) the usual solution is a "pitch pipe", or sometimes a tuning fork.

In these modern technological times it is easy to produce an electronic device to replace pitch pipes and tuning forks, and in fact the author has done just this for his violinist daughter. The electronic pitch pipe was built into a very small radio case, just large enough to include a 2in speaker, and fits easily into one of the pockets in her violin case.

Any small plastic box will do, though as the photographs show, if it is possible to obtain a suitable small radio case it looks more professional, making an unusual talking point at orchestral rehearsals!

## BATTERY POWER

The case shown is rather compact inside; the original circuitry (which was missing) was to have been powered from two 1.35V mercury cells. However, this voltage is too low to enable a simple audio oscillator with the necessary frequency stability to be designed, so a higher voltage battery was necessary. Because of its small size, an Ever Ready B154 15V battery was chosen. This is used in certain flash guns and is obtainable at any good photographic chemists store or camera shop.

However, the frequency of the tone produced by the electronic pitch pipe is independent of supply voltage down to just over six volts, so if a little more space is available in the box, the ubiquitous 9V PP3 can be used.


## CIRCUIT DESCRIPTION

Fig. 1 shows the circuit diagram of the electronic pitch pipe. IC1 is a 4011 CMOS quad two input NAND gate, with two of the gates (IC1a and b) being used as a squarewave oscillator,

Fig. 1. Pitch Pipe circuit diagram.

and a third (IC1c) as a buffer stage. The fourth is unused. Note, however, that the inputs of the unused gate (IC1d) should not be left floating, but connected as shown.

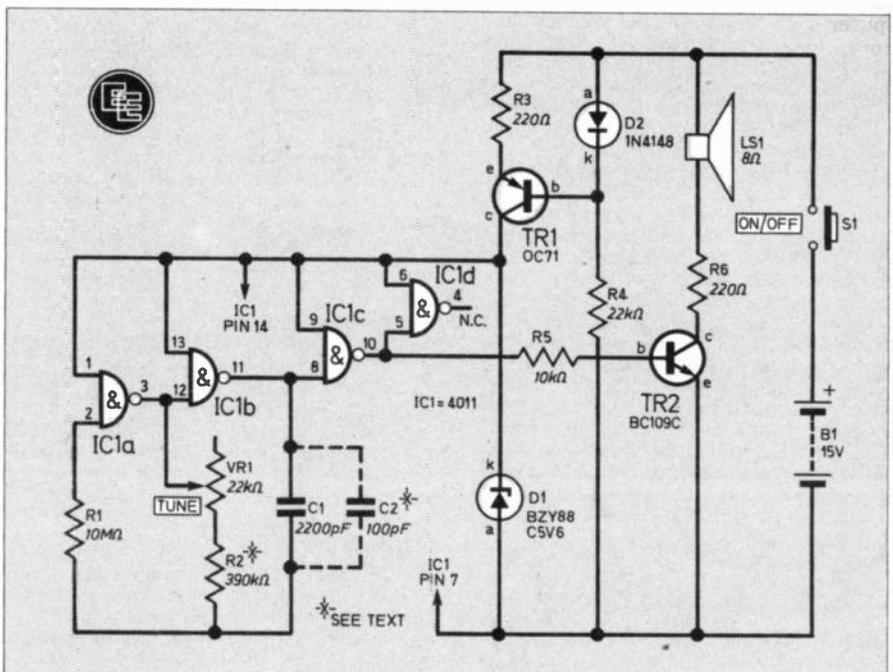To obtain a constant pitch regardless of the state of the battery, the supply to the oscillator is stabilised at 5.6V by means of zener diode D1, which is fed from a current source. The latter consists of TR1 and D2, and works by virtue of TR1 being a germanium transistor whilst D2 is a silicon diode; different types should not be substituted here.



The buffer stage, IC1c, drives the output transistor, TR2, the base current being limited by R5 and the collector current by R6. To provide maximum volume and to avoid loading the stabilised supply, the output stage is run directly from the battery. It might be thought that with R6, a 220 ohm resistor, in series with an 8 ohm speaker, nearly all the output would be dissipated in the resistor and that the output sound level from the speaker would be quite inadequate. However, the figure of 8 ohms refers to the resistance of the loudspeaker at d.c. and very low frequencies. At 440Hz (concert pitch A)

output power available does appear in the loudspeaker. The result is a very pleasant clear tone of more than adequate loudness, with no trace of "chirp" at switch-on.

The ON/OFF switch, S1, is a momentary action push-button, so there is no danger of the electronic pitch pipe being accidentally left on and running down the battery. With normal use, the life of the battery should be almost as long as its "shelf life", say 18 months or more.

### STABILITY

Of course an electronic pitch pipe must produce as accurate and stable a pitch as an ordinary pitch pipe if it is to be useful, so consequently the finished prototype was tested for consistency of pitch with variation of both battery voltage and ambient temperature.

From fifteen down to about six and a half volts, and over the maximum range of temperature that a violinist would care to play in, the pitch did not vary by more than a couple of cents or so. (A cent in this context is a frequency difference of one per cent of a semitone.) This is barely discernable, even if two notes, one cent apart are played simultaneously.

To obtain this excellent performance, good quality components should be used throughout, and for preference VR1 should be a cermet type, and R2 should be a high stability resistor. If you build the circuit and wish to temperature test it to check that the pitch doesn't change, make sure that it is heated or cooled evenly as a complete unit, blowing a hair



there is also the very substantial impedance due to the speaker's voice coil, so that a fair proportion of the limited

## COMPONENTS

See  
Shop  
Talk  
page 455

**Resistors**  
 R1 10MΩ  
 R2 390kΩ (see text)  
 R3, 6 220Ω (2 off)  
 R4 22kΩ  
 R5 10kΩ  
 all 1/4W carbon ±5%

**Capacitors**  
 C1 2200pF  
 C2 100pF (see text)

**Semiconductors**  
 D1 BZY88 C5V6 400mW, 5.6V Zener diode  
 D2 1N4148 silicon signal diode  
 TR1 OC71 germanium pnp  
 TR2 BC109C silicon npn  
 IC1 4011 CMOS quad 2 input NAND gate

**Miscellaneous**  
 VR1 22kΩ miniature vertical cermet preset  
 S1 push-to-make, momentary action  
 LS1 8 ohm miniature loudspeaker  
 B1 15V battery (Ever Ready type B154)  
 0.1 inch matrix stripboard, 21 strips by 21 holes; case to suit (approx 70 × 50 × 25mm); Veropins (5 off); 7/0.2 equipment wire, 14 pin d.i.l. holder.

**Guidance only**    **£5** excluding case  
**Approx. cost**

dryer at the circuit can heat some components more than others and is thus *not* representative of a normal change in ambient temperature.

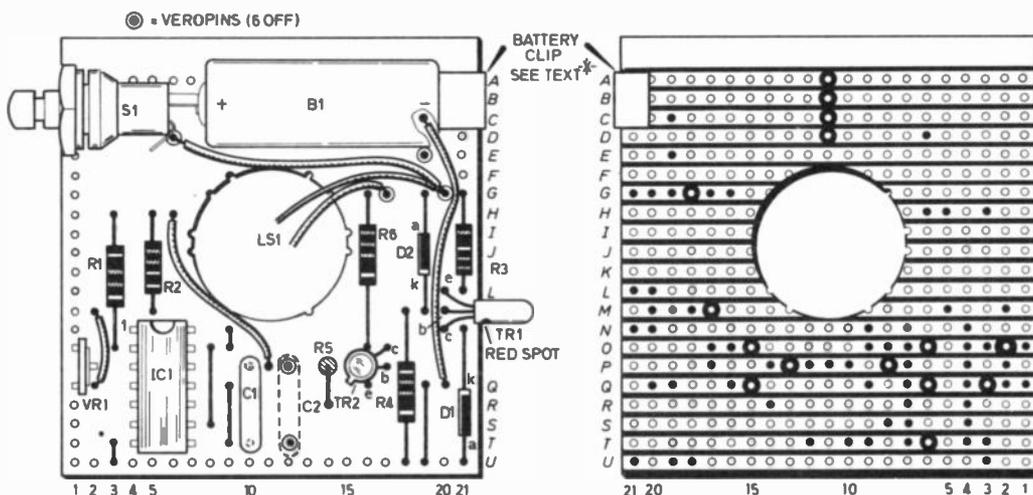


Fig. 2. Stripboard layout for the Pitch Pipe housed in the small transistor radio case shown in the photograph above. Note that this model employs the 15V battery (B1) and also has the speaker hole in the board. If a larger case is used, the layout may need to be modified accordingly to accommodate the larger PP3 battery and the new speaker position.

## CIRCUIT BOARD

The prototype circuit board was constructed on a piece of stripboard, 21 strips by 21 holes, with a hole, 22mm in diameter, to fit over the loud-speaker magnet. This hole is actually centred on a matrix hole, reference 111 (see Fig. 2), but this will largely depend upon the type and size of both speaker and case used by the constructor.

As discussed earlier, the case used on the prototype was a surplus stock miniature transistor radio enclosure of Russian origin, which regrettably, may be difficult to obtain. However, a similar radio case, more likely to have originated from the illustrious regions of Hong Kong, could easily be salvaged from a defunct tranny and modified to suit the project. This type of case is recommended as it not only readily accepts the miniature loud-speaker (more often than not it will have its own already!) but also houses a battery in a purpose-built compartment.

So bearing in mind that the layout shown in Fig. 2 is for a specific case and may require modification, assembly can commence. S1 and VR1 were positioned so as to line up with holes in the case and one of the terminals of S1 is actually used as the positive battery connection, the negative battery connection is formed from a strip of brass soldered to tracks A, B and C

on the board and then folded upwards to make a spring clip. This is only necessary if the smaller 15V battery is used.


S1 is then anchored down with a piece of solid wire, bent around it and soldered into the board. The other switch terminal is then bent away from the battery and soldered to a Veropin.

C2 should not be added at this stage, but two Veropins inserted into the positions shown to facilitate including this component should it be required when calibrating the pitch.
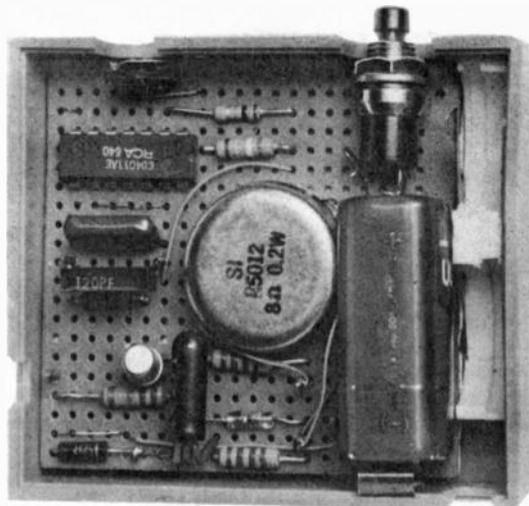
## CALIBRATION

To set the pitch to A above middle C (440Hz), VR1 is adjusted as necessary. If the pitch is still too high even with VR1 at maximum resistance, C2 should be added, about 100pF should suffice. If, however, the pitch is too low even with VR1 at minimum resistance, change R2 to 360 or 330 kilohms and proceed as above.

The pitch should be adjusted by sounding the electronic pitch pipe at the same time as a known accurate A, for example, a piano at concert pitch



Full size prototype of the Pitch Pipe.

or the tuning note on the oboe at the beginning of a broadcast concert.

If neither of these is available, a 440Hz tone is broadcast for a four minute period on the hour during BBC2 test card transmissions. It may be worth noting that the BBC2 test card goes out at 4pm until the first evening programme Monday to Friday and from 9am between programmes on a Saturday.

Finally, this project should be well within the capabilities of most constructors, and the finished article will be a treasured possession for any musician. ✧

# COUNTER INTELLIGENCE

By PAUL YOUNG

## Hot Recipe

I always make a point of answering every reader who is kind enough to write to me, but recently I had a letter from a lady, and although I replied to it, I am still not quite sure whether it was a leg-pull. She asked me if I had a microwave oven and a spectrometer.

It seems the good lady had taken three rather strange ingredients and cooked them in a microwave oven and she estimates that the resulting amalgam is copper gold and silver!! Would I check the results for her? If I remember rightly, when I worked under the sign of the three spheres, the usual test for gold was nitric acid.

I did explain to her that I am very anti microwave ovens, even more so, since a friend of mine pointed out that you might even be at risk if the chap next door has a leaky one and places it against the adjacent wall. The waves can pass right through the brick wall and damage you! All the same I wish her every success with her discovery, and if she is having me on, well I forgive her because she raised a smile, and that is quite a feat in these hard times.

## Good Publicity

I was once told that if you invented a better mousetrap, the world would beat a path to your door in order to buy it. I

regret to say, there is no truth in this statement at all. You might invent the finest mousetrap in the world and offer it at a very low price but unless you could back it with good publicity, you would still get no customers.

I was reminded of this the other day when I was asked if my Tabletop Workbench was still available. Although I abandoned it when my old friend Burt Malme died (he made all the wood work) it never really took off. Contrast this with the "Work Mate" which was a portable woodworkers bench, the man who dreamed this up made a fortune, because it was taken up by Black and Decker who were able to give it the necessary publicity.

I still think of the Tabletop Workbench as a viable proposition, but in order to keep down the cost, it needs to be turned out in one piece as a plastic moulding. This would need complicated tooling and today this would be extremely expensive.

## New Experience

I have always been keen to try new experiences, and when a friend of mine who runs a car hire firm, told me one weekend that two of his drivers had gone down with flu and could I help him out, I jumped at the chance.

Now for the interesting part. All the regular drivers are equipped with two-way radios. I had no such luxury, so my friend

said "you can use the portable", and handed me a small box measuring about eight inches by three by two and a half inches. It had a small rod projecting from one end about six inches by half an inch in diameter, which I took to be the aerial.

I kept my thoughts to myself, though I couldn't for the life of me see this tiny object working satisfactorily. However, after dropping a passenger I stood on the pavement and called up my base. Immediately back came the reply loud and clear. Surprise number one.

After my next trip the controller said, "You are not leaving your radio switched on!" I replied, "Surely it won't work inside the car being completely screened, including the aerial?" "Oh! yes it will" and it did! Surprise number two.


During a lull in the proceedings I decided to examine this little marvel more closely. I was curious to know where it was made. Although I had already decided it must be Japanese, the biggest surprise of all was number three. Clearly marked on the side in small letters were the words, *Made in Ripley, Derbyshire.*

Most of the drivers use a code partly derived from the old RAF jargon, such as "Roger out" and "My E.T.A. is 12.15". I fully expected it to crackle into life and a voice say, "Bandits, Angels One Five, Tally Ho!"

\* Enemy aircraft at fifteen thousand feet, attack!

# EE TEACH-IN 82

## PART 10 BY O.N. BISHOP

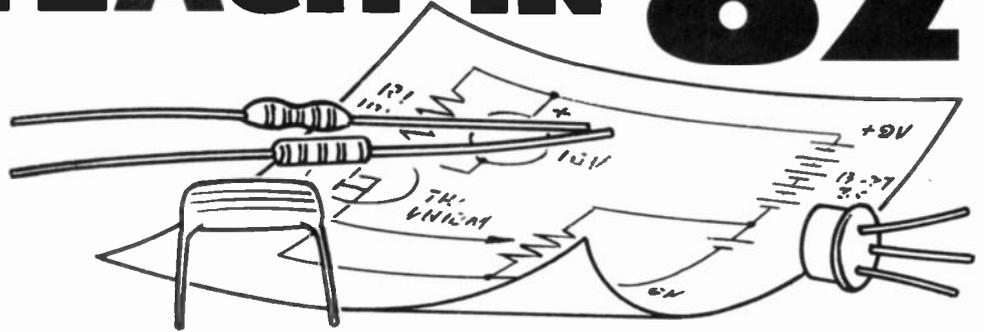

### BASIC ELECTRONIC THEORY WITH EXPERIMENTS OSCILLATORS

THE ASTABLE MODULE that forms part of *Minilab* is an example of the class of oscillators known as **relaxation oscillators**. You can think of them working by a gradual building up of tension followed by a sudden release, or relaxation. A capacitor is gradually charged up to a certain level. When that level is reached, a transistor or other device switches on and discharges the capacitor rapidly. The frequency of oscillation depends mainly on the time required to charge the capacitor.

#### UNIUNCTION TRANSISTOR OSCILLATOR

Another type of relaxation oscillator, is shown in Fig. 10.1. It uses a single active device, a **unijunction transistor (u.j.t.)** see Fig. 10.2a.

Current flows through VR3 and R23 gradually charging C8. The potential at the emitter gradually rises. When it is close to zero the junction is reverse-biased and only a small leakage current flows.

After a while the potential rises and the junction is forward biased. Current flows and holes are injected into the bar and these move toward base 1. This causes increased conductivity (=decreased resistance) in the lower part of the bar.

The effect of this is to lower the potential

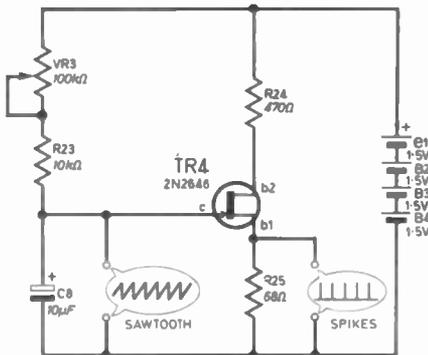


Fig. 10.1. Relaxation oscillator based on a unijunction transistor.

in that part of the bar (think of it as a potential divider, as in Fig. 10.2b, with R2 suddenly being made smaller). The junction becomes even more strongly forward-biased, causing greater emitter current, more holes and further drop in potential in the bar.

The result is a sudden burst of current, which almost instantly discharges the capacitor. When it is discharged, the process starts again.

We can obtain two kinds of waveform from this oscillator, a sawtooth at the emitter and a series of spikes at base 1. The frequency depends on the values of R and C (VR3 + R23 and C8).

#### EXPERIMENT 10.1 CMOS oscillator

It is even simpler to build a relaxation oscillator from CMOS logic gates, see Fig. 10.3. The two gates are wired as

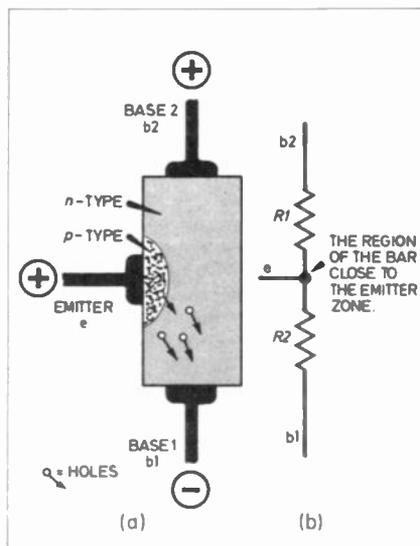


Fig. 10.2. (a) Construction of a unijunction transistor (b) equivalent circuit of a unijunction—it acts as a potential divider.

inverters (NOT gates), the only other components required being a capacitor and a resistor, C8 and R24.

If the output of IC3b suddenly goes high, the sudden increase in voltage is passed across C8, giving plate B a high potential. IC3a has a high input, so it has a low output. The low level at point X causes current to flow from B to X, through R24. When potential at B has fallen sufficiently, IC3a changes state. Its output becomes high, causing IC3b to change state and its output to become low.

Now plate B is pulled low, causing current to flow from X to B. This continues until the potential at B has risen sufficiently to switch IC3a back again. The switching back and forth continues indefinitely.

Resistor R23 is not essential for operation of the oscillator. Its effect is to make frequency less dependent on supply voltage. R23 should be at least twice the value of R24. Fig. 10.4 shows how to build this oscillator on *Minilab*. Note that a single i.c. can be the basis for two independent oscillators.

#### CRYSTAL OSCILLATORS

The frequency of relaxation oscillators is generally dependent on the time constant, RC. In practice, R and C vary with temperature, so frequency is temperature dependent. There is also the problem of obtaining components with exact values needed to produce a required frequency.

A much more precise control of frequency can be obtained by using a quartz crystal. A crystal is cut to vibrate mechanically at a precisely determined frequency. It is made to vibrate by applying an oscillating p.d. to it. As it vibrates, an oscillating e.m.f. is generated across it. It can therefore be connected into a circuit which supplies it with the energy to keep it vibrating and in which the e.m.f. from the crystal keeps the circuit oscillating at the required frequency.

Temperature stability is much better than with a simple RC circuit, yet crystals are cheap. Most digital watches base their timing on a crystal oscillator. Typically,

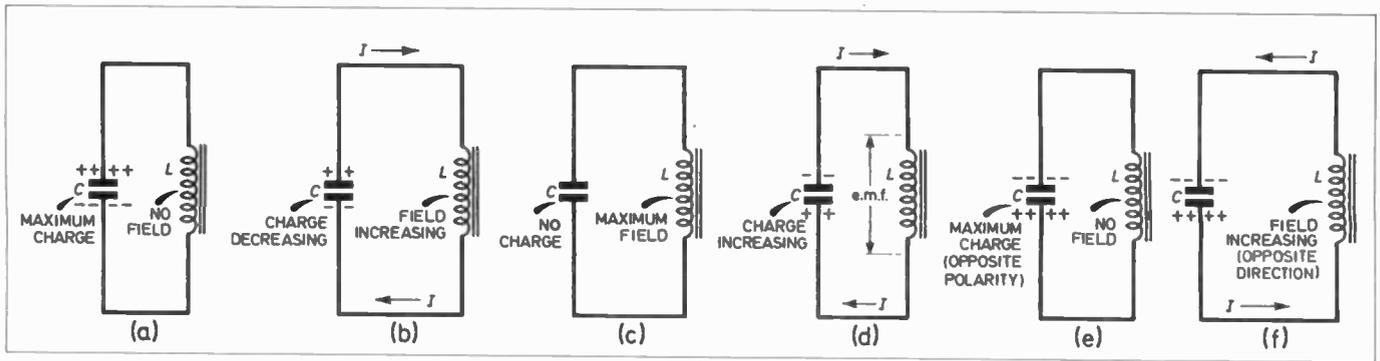


Fig. 10.5. An LC oscillator in various operational stages.

the crystal has a frequency of 32.768kHz. This is divided by  $2^{15}$ , using a 15-stage binary counter, to give a frequency of 1Hz.

### RESONANCE

A pendulum is an oscillator and, has long been used as such in timekeeping.

Left to swing, its amplitude of swing gradually decreases as it loses energy, mainly by creating currents in the air around it. Note that though the *amplitude* may decrease, the *frequency* remains unaltered.

In a pendulum clock, the mechanism keeps it swinging indefinitely by giving it

a small "kick" at each swing. The kicks must be provided at the right time, just as we must give a person on a swing a push at the right time if they are to be kept going. The supply of energy must be timed correctly—it must be in resonance with the natural period of swing of the pendulum.

Fig. 10.5 shows a circuit which oscillates. At (a) the charged capacitor *C* is discharging through the inductor *L*. At (c) it is discharged and the magnetic field of *L* is at its maximum. Now the current stops and the field collapses.

As explained last month, inductors oppose changes in magnetic field. An e.m.f. is induced to maintain the field. This causes a current to flow (d), recharging the capacitor, but with opposite polarity (e).

Energy has been transferred from the capacitor to the inductor and back to the capacitor again. Now the capacitor discharges again (f) and the cycle is repeated. This occurs at a frequency given by  $f = 1/2\pi LC$ .

In time, oscillations die away as electrical energy is converted to heat. But, just as with the pendulum, the frequency remains unchanged. If we replace the lost energy from outside, the circuit can oscillate indefinitely. This is the basis of the second main class of oscillator, the **harmonic oscillator**.

A pendulum swings with simple harmonic motion. If we could trace the motion of the bob on a sheet of steadily moving paper (Fig. 10.6) without stopping it swinging, we should obtain a sine curve.

## EXPERIMENT 10.1

Fig. 10.3. Relaxation oscillator based on CMOS gates.

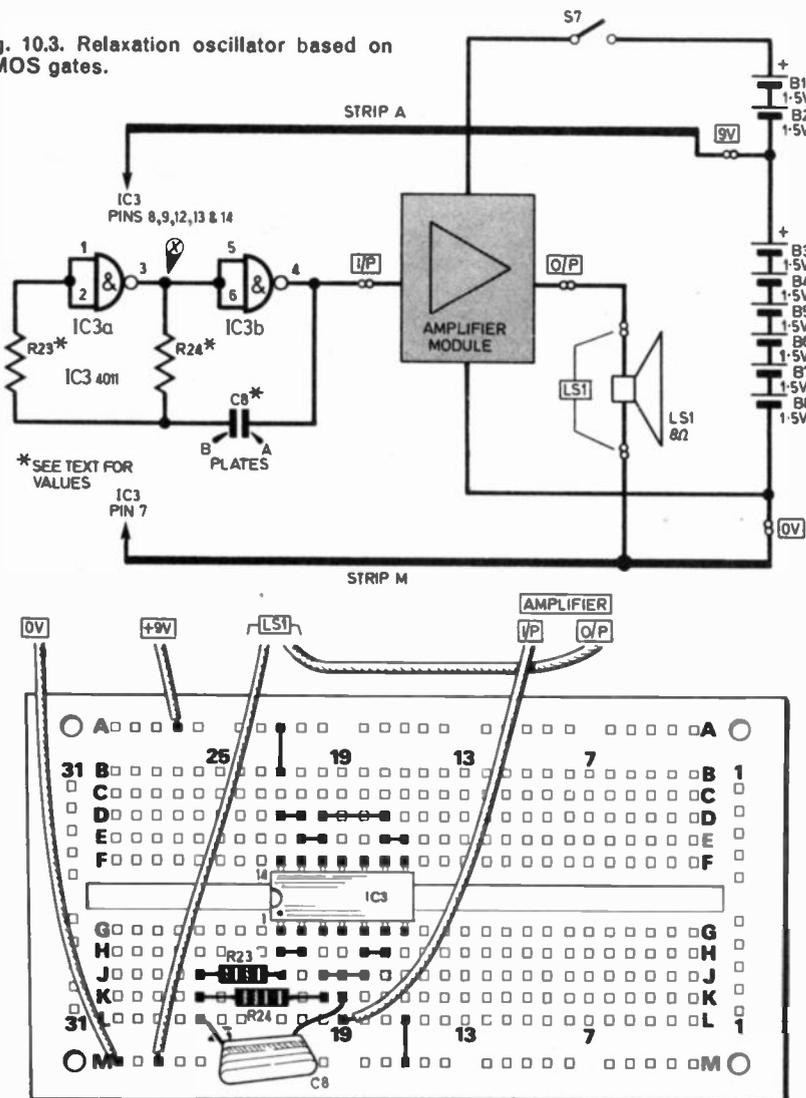


Fig. 10.4. The circuit of Fig. 10.3 wired up on the Verobloc.

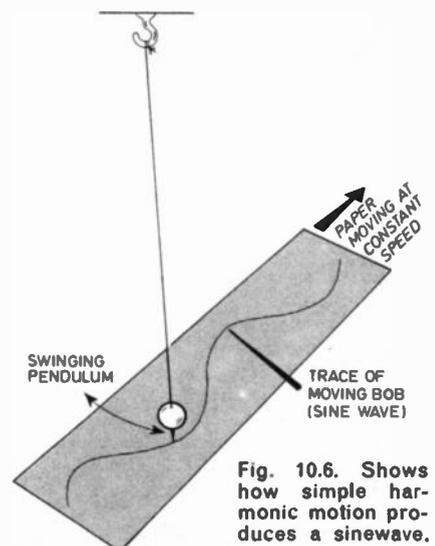


Fig. 10.6. Shows how simple harmonic motion produces a sine wave.

Similarly, if we measure the potential at any point in the LC circuit and plot it against time, we obtain a sine wave.

Harmonic oscillators are therefore very useful for making pure sine waves.

### LC OSCILLATOR

The Hartley Oscillator (Fig. 10.7) has an LC oscillator (C1, L1) in its collector circuit. The base potential is held very steady by C8. The LC circuit oscillates at its natural frequency and needs to be supplied with energy to maintain these oscillations.

The coil L1 is tapped a short distance from one end. The p.d. across this portion alternates in step with the oscillations. This alternating signal is fed back through the coupling capacitor C9 to the emitter of TR4. The signal alters the base-emitter p.d., and hence controls collector current.

Feedback is positive. As C1 is charging, decreasing current through L1 brings reduced potential at C9. This causes emitter potential to fall, increasing the base-emitter potential, so increasing collector

current. The p.d. across the oscillator is increased and additional charge is given to C1. This replaces energy being lost from the oscillator. Output is taken from this circuit by a second coil L2 wound on the same former.

### EXPERIMENT 10.2 Hartley Oscillator

Fig. 10.8 shows how to assemble the oscillator on *Minilab*.

To wind L1, first prepare a paper collar for the ferrite rod as you did for last month's radio circuit. Wind 20 close turns of 28 s.w.g. enamelled copper wire over the collar.

At this point scrape the enamel from 5mm of the wire and firmly twist the bare end of a short length of wire around this region. This is the "tap". Continue winding the coil to make 80 turns in all. The output coil L2 is not needed, for we can detect the output by other means.

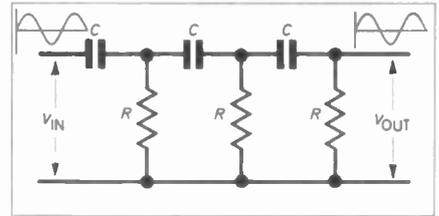


Fig. 10.9. A phase-shift network made up from three high pass filters connected in series.

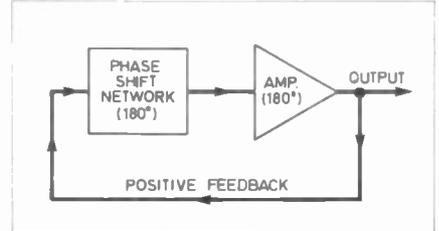


Fig. 10.10. Principle of a phase-shift oscillator.

Connect the battery. Set C1 to about the middle of its range. Now place a radio set beside the oscillator. Tune it to the medium waveband where no station is being received. You will hear a loud rushing sound which stops when you disconnect the battery from the oscillator.

Capacitance is only about 250pF and inductance is only a few millihenries, so the frequency of the oscillator is high.

The frequency of oscillation depends on the values of C1 and L1. The frequency of one oscillator built in this way was tested by winding L2 (20 turns) and connecting it to an oscilloscope. The frequency was 500kHz, which is well into the radio frequency band.

Naturally you cannot hear such a high frequency with the radio set, but it reacts with the radio circuits producing interference frequencies in the audible range. The radio set merely indicates that something is happening!

### COLPITT OSCILLATOR

The Colpitt Oscillator works in a manner very similar to the Hartley oscillator. Instead of a tap on the coil, there are two capacitors in series in the oscillating circuit. Feedback is taken from the junction between these. In effect, the capacitive side of the oscillator is being tapped.

Once again use is made of positive feedback to maintain the energy level in the oscillating circuit.

### PHASE SHIFT OSCILLATOR

Fig. 10.9 shows three high-pass filters in series. These constitute a high-pass filter with very sharp cut-off. Each filter causes some slight shift of phase between input and output signals.

For sine wave signals of one particular frequency the total phase shift is exactly 180 degrees. Input and output are exactly *out of phase*. The output has the same frequency as the input, but when  $V_{IN}$  is increasing  $V_{OUT}$  is decreasing, and the other way about.

Fig. 10.7. The circuit diagram of a Hartley oscillator.

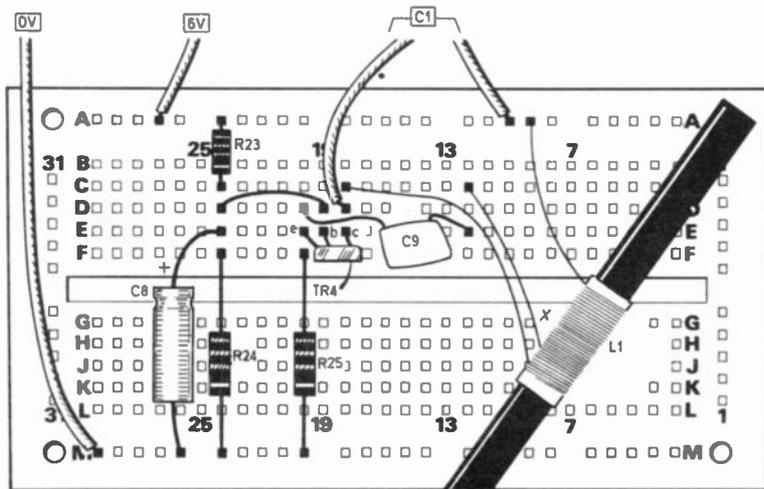
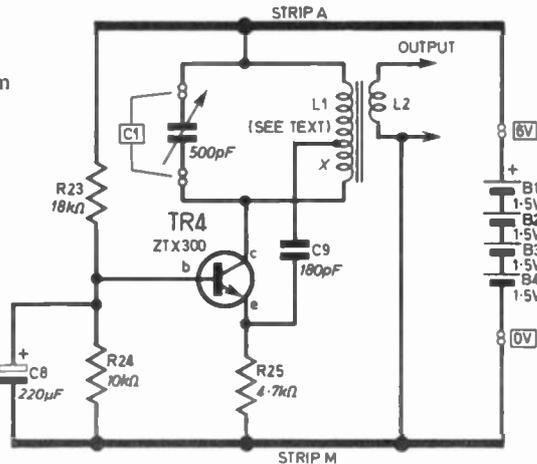


Fig. 10.8. The layout of the components on the Verobloc for the circuit of Fig. 10.7.

In Fig. 10.10 we see how this network is used in a phase-shift oscillator. Part of the output signal is fed back to the phase shift network. It passes through the network and enters the amplifier. This is an inverting amplifier, which shifts phase by another 180 degrees. Total phase shift of the loop is 180 degrees + 180 degrees = 360 degrees. In other words, the output signal is *in phase* with the signal originally fed back from the output.

Oscillations of precisely the right frequency produces positive feedback. The circuit steadily oscillates at that frequency.

An oscillator of this type was used last month to generate sinewaves for the experiments on filters. The amplifier was a Darlington pair, which gives 180 degrees phase shift.

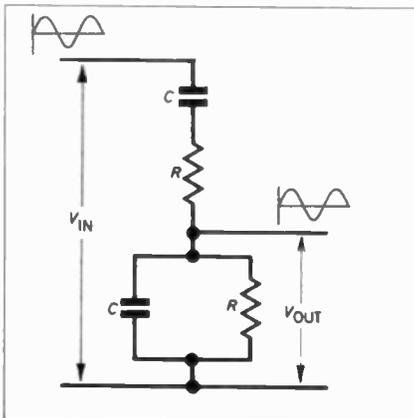


Fig. 10.11. A Wien bridge network.

### WEIN BRIDGE OSCILLATOR

The Wien Bridge Oscillator is based on a different design of filter than those discussed so far (Fig. 10.11). For a sine wave of the correct frequency, this network has zero phase shift. Input and output signals are exactly in phase. In addition,  $V_{OUT}$  is exactly one third of  $V_{IN}$ . To use this network in an oscillator, we need an amplifier with a gain of at least  $\times 3$ , and with zero phase shift.

Fig. 10.12 shows how an op amp may be used. Output from an op amp is always in phase with signals at the non-inverting input. The output from the network is fed to this input, giving positive feedback.

It is essential that the gain of the amplifier is carefully controlled. If it is more than  $\times 3$ , positive feedback causes it to oscillate with ever increasing amplitude until the output is swinging violently to +6V and -6V, giving a clipped waveform or even an almost square wave. If gain is less than  $\times 3$ , the oscillations gradually die out.

Gain is controlled by the negative feedback resistor VR3, which can be adjusted as required. Since gain is to be low, VR3 has a low value.

Gain is stabilised in an unusual way. VR3 and the filament of the lamp LPI form a potential divider between output and the 0V rail.

If output is tending to swing more widely than it should, this makes the average current through VR3 and LPI higher than normal. The filament is heated above its normal temperature and its resistance increases. An increased resistance in this section of the potential divider causes a rise of potential at the inverting input, resulting in a reduction in output level.

If output is lower than it should be, the reverse applies and output is increased.

### EXPERIMENT 10.3 Wien Bridge Oscillator

Fig. 10.13 shows how to set out the components. The output from IC3 has

enough amplitude, but by connecting a loudspeaker to it the operation of the oscillator is upset. For minimum effect on the oscillator we use an amplifier with very high input impedance. This is a good demonstration of the use of a source-follower amplifier.

This is similar in principle to the emitter follower amplifier described in Part 7 (Fig. 7.2). The source follower uses an f.e.t. and, as we are using a vmos f.e.t. (TR4), its input impedance is virtually infinite.

As with the emitter follower, gain is approximately unity (actually about 0.9) but, since the original signal already has sufficient amplitude, there is no need for further increase. The potential at the source follows the oscillations of the amplifier and

### EXPERIMENT 10.3


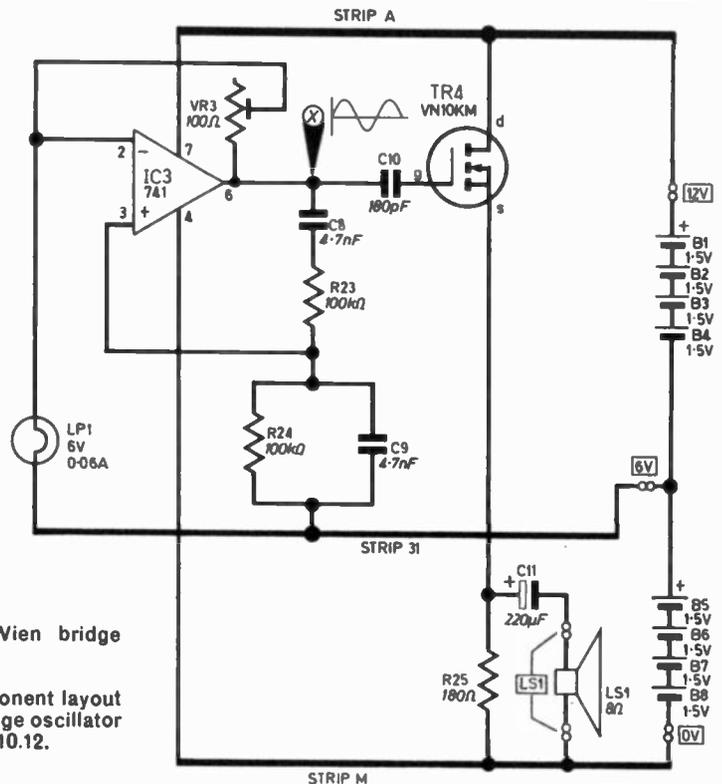


Fig. 10.12. A Wien bridge oscillator.

Fig. 10.13. Component layout for the Wien bridge oscillator experiment, Fig. 10.12.

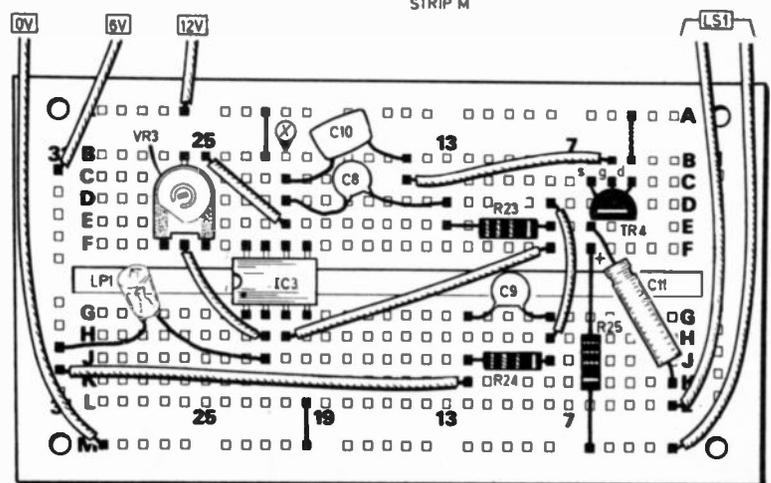

## QUESTION TIME

- 10.1. What type of oscillator is needed to produce a sine-wave?
- 10.2. What kinds of waveform can be obtained from a u.j.t. oscillator?
- 10.3. What is the advantage of a crystal oscillator?
- 10.4. Name a radio frequency oscillator?
- 10.5. How much is the gain of the amplifier in a Wein bridge oscillator?
- 10.6. What type of feedback is needed to keep a harmonic oscillator running?

is coupled to the loudspeaker circuit through C11.

For the reasons given in the previous section, VR3 must be carefully set. When the right position is found a loud note at about 340Hz will be heard. This has a much smoother sound than the harsh square waves we have heard before. It is a pure sine wave.

If  $C8 = C9 = C$  and  $R23 = R24 = R$ , the frequency  $f = 1/2\pi RC$ . Try other values for R23 and R24 (10k $\Omega$ , 1M $\Omega$ ) and for C8 and C9 (0.1 $\mu$ F). With some combinations,  $f$  is below audio frequency.

With 1M $\Omega$  and 0.1 $\mu$ F,  $f = 1.6$ Hz. To observe this, remove C11 and connect the voltmeter (10V f.s.d.) to the -6V rail and

## Answers to Part 9

- 9.1. At the start.
- 9.2. At the start.
- 9.3. The product of the resistance and the capacitance.
- 9.4. 0.33 seconds.
- 9.5. 37 per cent of 12V = 4.44V.
- 9.6. A quarter.
- 9.7. 1693 at 200Hz; 1.69 at 200MHz.
- 9.8. 106kHz.

to the source of TRI (sockets M6 (+ve) and E6 (-ve)). The needle oscillates steadily around 6V.

To be continued



By Dave Barrington

## Catalogues Received

We have just received the latest edition of the TK Electronics shortform catalogue.

This new 20-page edition contains over 100 new items and all components under the memories and microprocessor sections have been reduced in price. As well as popular components, the catalogue also carries goods that have sometimes proved difficult to locate, such as ultrasonic transducers and remote control devices.

Among the kits listed is an excellent selection of infra-red controllers for many applications, including a programmable receiver. Also available are a range of home lighting kits which includes a touch dimmer that can also be controlled remotely by an infra-red transmitter.

Now available from Verospeed is the fourteenth edition of the company's comprehensive components catalogue, featuring more than 300 new product lines. In total, it covers some 2500 products from over 50 suppliers.

New items in the latest edition include an ultra-miniature range of digital panel meters and a selection of dry-reed and mercury-wetted relays. Other products featured for the first time are a static-safe work station kit, range of analogue panel meters. Zeners and CMOS integrated

circuits from Motorola and a range of "flat-pack" cases.

Valid until the end of August, copies of the Verospeed components catalogue can be obtained from Verospeed, Dept EE, Stansted Road, Boyatt Wood, Eastleigh, Hants, SO5 4ZY.

If ever a title was a true reflection of its contents then the latest *Ambit International's* component catalogue "The World of Radio & Electronics" says it all.—Many's the time they have "saved our bacon" for those hard to locate devices.

This third edition contains 96 pages covering the whole gambit of components from coils to radio receivers and draughting aids to microprocessor development systems. Each page carries the goods price, less VAT, and is valid for the currency of the catalogue.

Available from newsagents or direct from *Ambit* for the sum of 70p, the catalogue contains three £1 redeemable vouchers. These are valid until July 31 and may be used with each order totalling £15, excluding VAT.

## Pastures New

London's loss is Glasgow's gain, with the announcement from Marshalls that they have closed their head office at Kingsgate House, London, and moved all their business transactions, mail order and industrial sales, to their Glasgow operation at 85 West Regent Street.

Running the business since her late husband died has been quite a task for Mrs June Marshall, especially so since she remarried. Therefore, unable to devote as much time in the business, Marshalls have disposed of their Bristol and London retail outlets to their respective managers.

In charge of the Glasgow operation is Gavin Briggs, nephew of the late Alex Marshall, and he will be pleased to hear from all Marshalls customers. Gavin informed us that he now considers that the Regent Street set-up holds the largest stock and widest range of electronic components and accessories in Scotland.

## CONSTRUCTIONAL PROJECTS

### Reflex Tester

Although the components list for the *Reflex Tester* calls for a miniature single-pole single-throw (s.p.s.t.) slide switch, the double-pole versions are more commonly stocked and can be used here.

However, the single-pole miniature type is certainly stocked by TK Electronics and also available through most Tandy stores.

The "Start" switch S3 used in the model was part of a non-latching 2-pole, 2 way switch block. Any 2-pole changeover momentary action push switch can be used.

### Model Car Lap Counter & Judge

The only source of supply we have been able to trace for the 40110 CMOS decade counter/driver used in the *Model Car Lap Counter & Judge* is Maplin and Watford Electronics.

The only stockist we have found for the specified 2-digit, common cathode, display is Maplin. Indeed, they list all the components for this project (except p.c.b.), including common anode tri-colour l.e.d.; stock no. YY61R.

### Brake Light Relay

The dry-reed switch used in the *Brake Light Relay* is a RS Components device. It is listed as type 6-RSR-A, stock number 338-147, and should be available from any RS supplier.

### Public Address System

The *Power Amplifier* output transformer T1 is the same as the mains transformer T2, except that it has a centre-tapped primary. Both transformers are obtainable from ILP Electronics Ltd., Dept EE, Graham Bell House, Roper Close, Canterbury, Kent. Quote the two type numbers given in the components list last month.

The meter ME1 is obtainable from Maplin Electronic Supplies.

### Two-way intercom

The terminal blocks used in the *Two-Way Intercom* should be 2A types with 8mm spacing between "ways". This is so that they may be placed directly on the template drawing.

### Electronic Pitch Pipe

The case used in our prototype for the *Electronic Pitch Pipe* was from an old discarded radio set.


The components are rather crowded in this size of case and we suggest that a larger one be used. This can be any plastics case with suitable dimensions.

### Comparator Voltmeter

When ordering components for the *Comparator Voltmeter* be sure to specify a wirewound type for the calibration control VR1. This component is stocked by most component suppliers and should not cause any problems.

# PUBLIC ADDRESS SYSTEM

**PART 3**  
**By E.A. Rule**

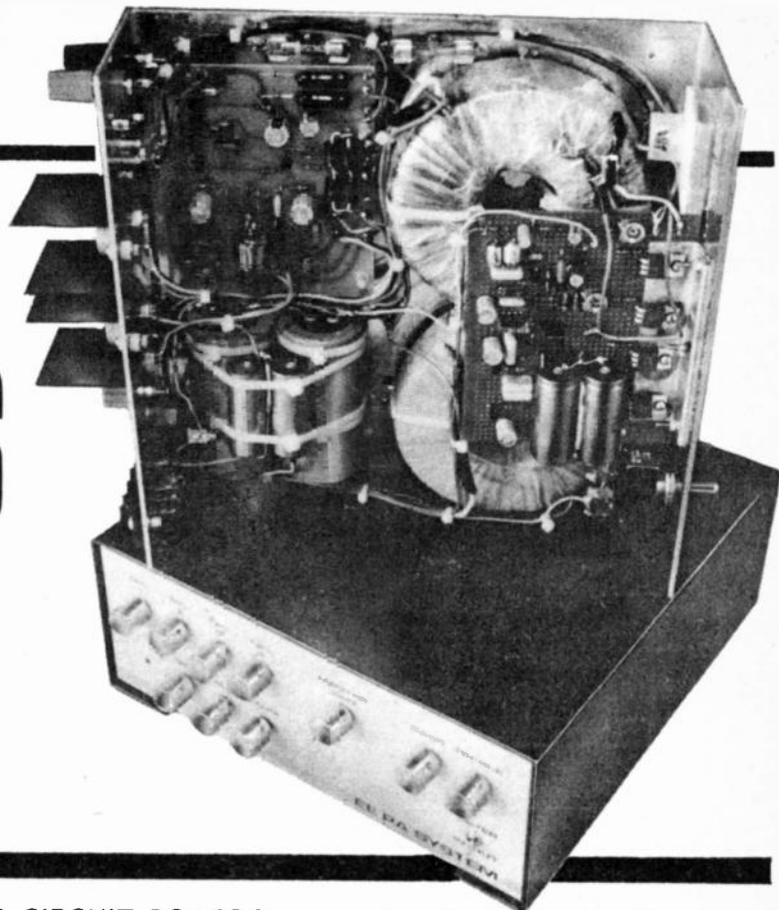

**T**HIS month's article deals with the construction of the power amplifier. The circuit diagram, technical description and components list for this unit were given in Part 2.

## METALWORK

The chassis is made in a similar fashion to the control unit chassis and the general remarks concerning the material to be used and the drilling and bending operations given in Part 2 should be referred to.

Drilling and bending details are given in Fig. 3.1.

As with the control unit, the cover for the power amplifier is made after the chassis has been completed, when the actual dimensions required can be ascertained by measuring the completed chassis. Refer to Fig. 2.4 for overall form of the case.

## HEAT SINKS AND BRACKET

The two heat sinks are made from aluminium as shown in Fig. 3-2. It is very important that the middle section which is for mounting the transistors is *completely* free from burrs and also *flat*. File the front and rear surfaces with a suitable flat file to ensure freedom from "bumps" or indentations.

When completed these heat sinks should be painted matt black.


The mounting bracket for the inverter Darlington transistors is shown in Fig. 3.3a and, again, the surfaces should be free from burrs and any "bumps".

## PRINTED CIRCUIT BOARDS

There are two printed circuit boards in the power amplifier unit: (1) the main (power amplifier) p.c.b. and (2) the inverter p.c.b.

The printed circuit track layouts are shown in Fig. 3.4 and Fig. 3.6 and the component layouts in Fig. 3.5 and Fig. 3.7, respectively.

Completed power amplifier viewed from rear. Note method of securing transformers and electrolytic capacitors with plastic cable ties.

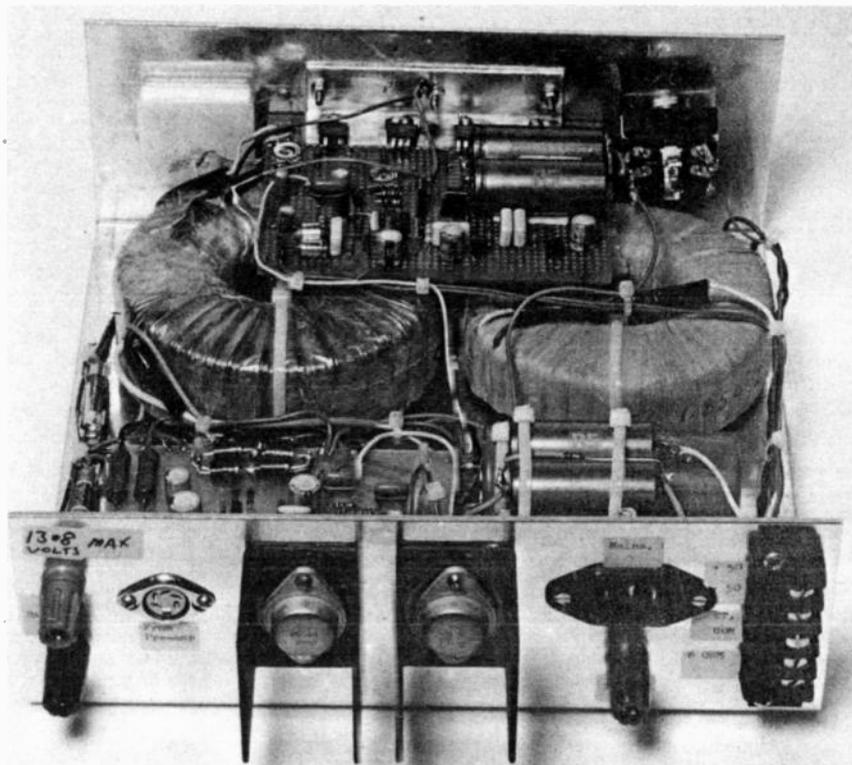



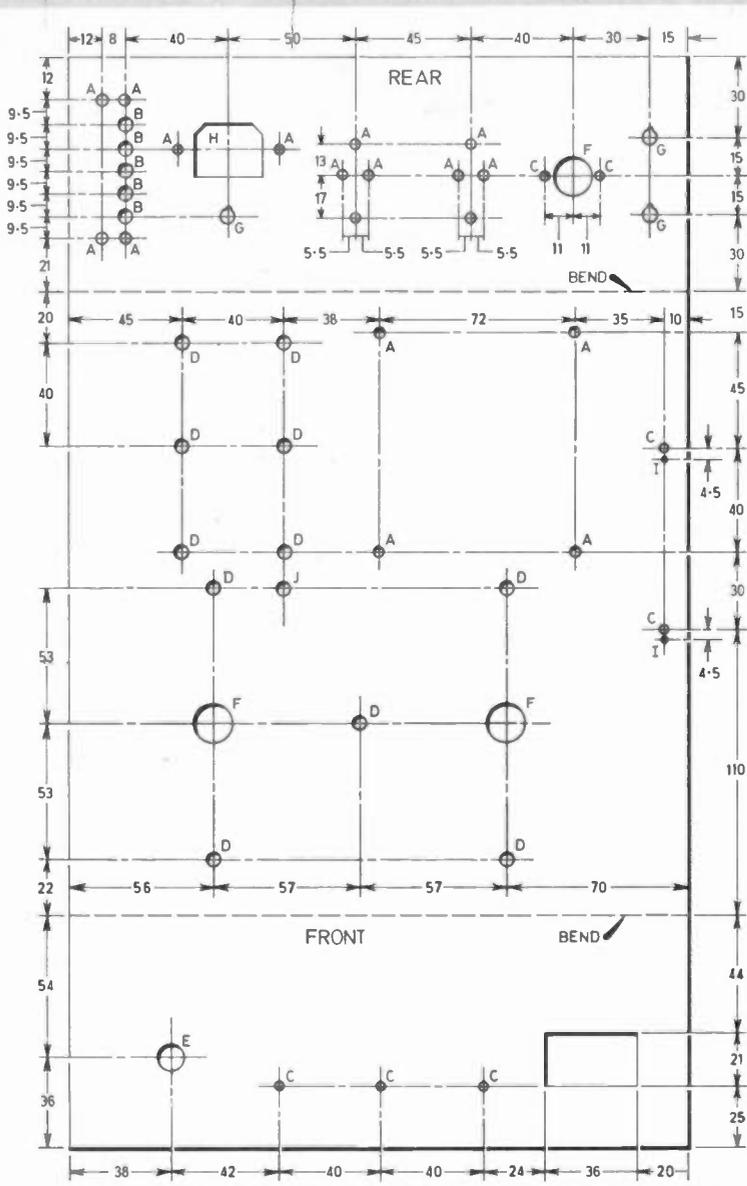
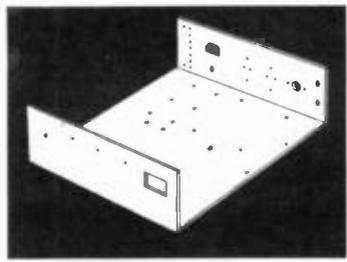


Fig. 3.1. Public Address System: Power Amplifier chassis drilling and bending details.

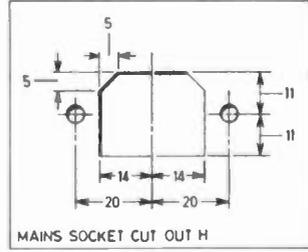

HOLE SIZES	
A = 4mm	F = 16mm
B = 7mm	G = 6.6mm
C = 3mm	I = 2mm
D = 6mm	J = 5mm
E = 11mm	

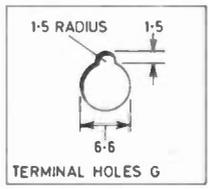

ALL DIMENSIONS IN mm

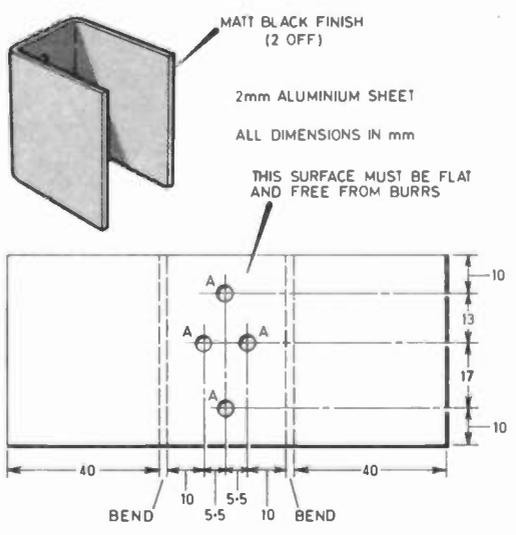


Fig. 3.2. Heat sink constructional details.

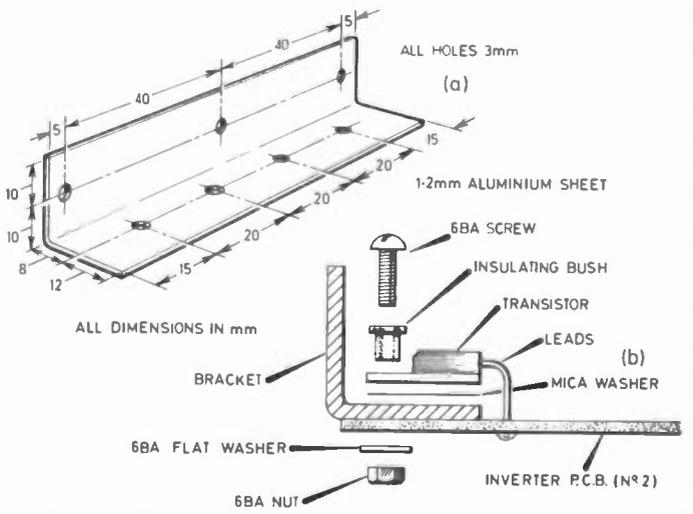


Fig. 3.3. Mounting bracket for inverter p.c.b. (a) constructional details (b) cross section showing method of mounting the Darlington transistors which also provides the means for securing bracket to board.

# MAIN AMPLIFIER BOARD (PCB1)

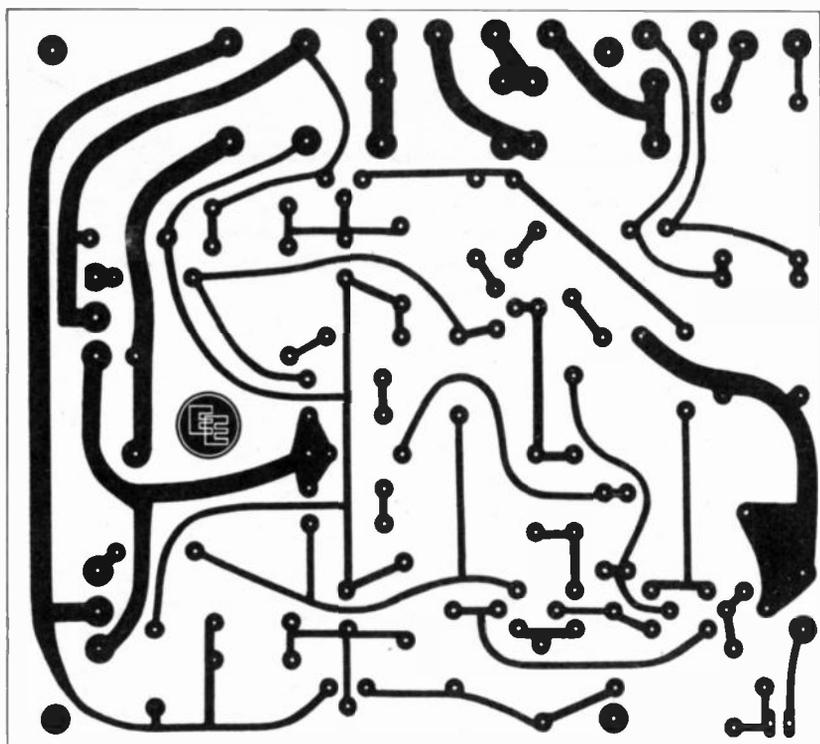


Fig. 3.4. Public Address System: Power Amplifier printed circuit board No. 1 (Main Board), actual size. **NOTE:** One side of C13 goes to terminal pin 14 (0V line), not to 12 (-42.5V line) as shown on circuit diagram.

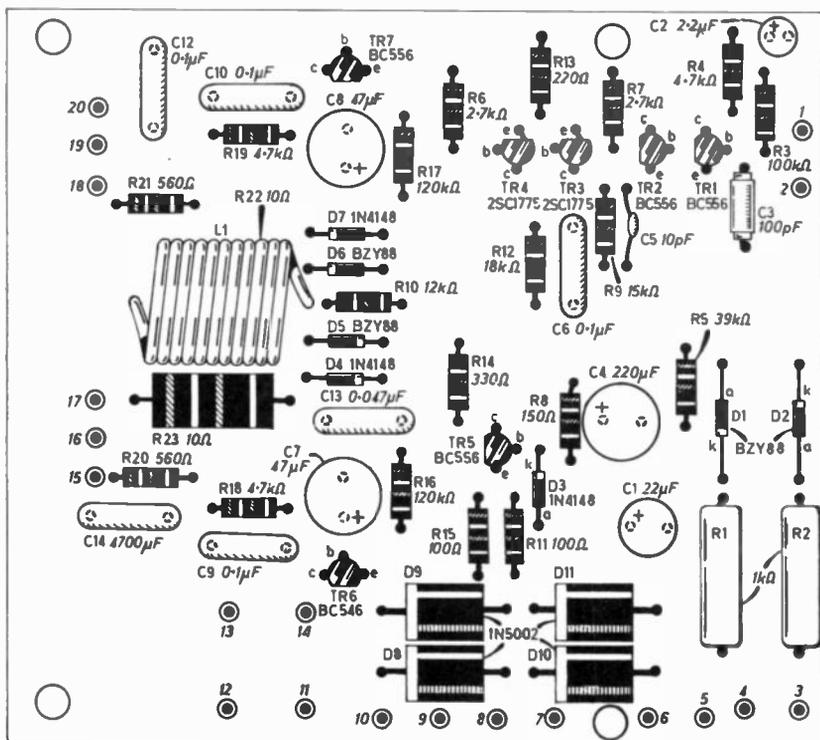


Fig. 3.5. Public Address System: Power Amplifier printed circuit board No. 1 (Main Board), topside with components in position.

## L1 COIL ASSEMBLY


Before assembling the power amplifier p.c.b., the coil assembly shown in Fig. 3.8 should be constructed; it consists of L1 and R22 shown on the circuit diagram.

The coil is wound with 30 turns of 18s.w.g. enamelled wire with three layers of windings. The first has 11 turns, the second has 10 and the third has 9. Between each layer is a layer of masking tape and this will help to keep the turns in place while winding. The internal diameter of the first layer is 8mm.

After winding, the 10 ohm 2 watt resistor is fitted inside and soldered as shown. The finished ends are then "pre-formed" to 22.5mm centres to fit the p.c.b. It will be necessary to scrape the enamel insulation from the 18s.w.g. wire before soldering.
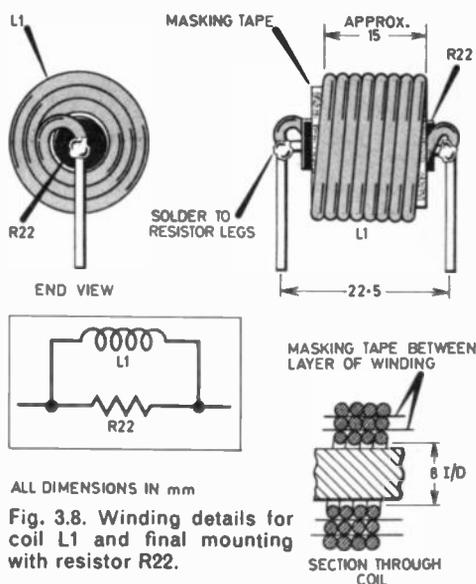
## P.C.B. ASSEMBLY

Assembly of the printed circuit boards should start with the terminal pins which are inserted from the track side of the p.c.b. and lightly



ALL DIMENSIONS IN mm

Fig. 3.8. Winding details for coil L1 and final mounting with resistor R22.

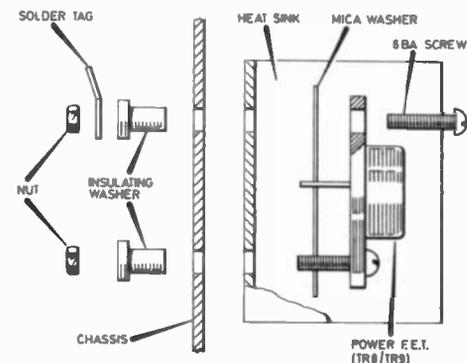


Fig. 3.10. Assembly of power f.e.t.s on to heat sinks.

hammered into place so that they are a firm fit but not overtight. The pins are then soldered into place. The p.c.b. should be supported from behind to avoid damage to the board.

After the pins are in place the suggested order of assembly is resistors, small capacitors, transistors, then electrolytics. In other words, the smaller components first, as this will enable the components to be inserted and the p.c.b. turned over onto a foam pad which will hold the components in place while they are soldered in.

Be very careful to mount all electrolytics and semiconductors the correct way round as indicated on the p.c.b. overlay; in particular watch the polarity of diodes and the position of pin 1 on the IC1. A socket may be used for the i.c. as this will be an aid to rapid servicing in the field in the event of failure.

A number of components may need to be pre-formed and details of these are given in Fig. 3.9. Pay special attention to the leads of transistors type 2SC1775e.

#### WINDING DATA FOR L1

Inside diameter	8mm
Length	15mm
Windings	3 layers of 11, 10 and 9 turns (30 total)
Outside diameter	18mm approx.
Wire	18 s.w.g. enamel covered copper
R22	10Ω 2W carbon resistor

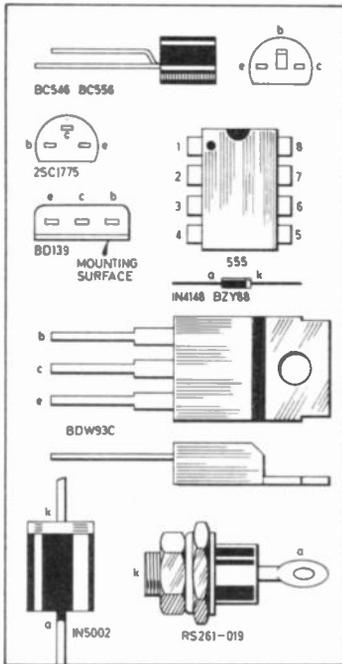


Fig. 3.9. Details of semiconductors used in power amplifier (for power f.e.t.s see Fig. 3.10).

## INVERTER BOARD (PCB2)


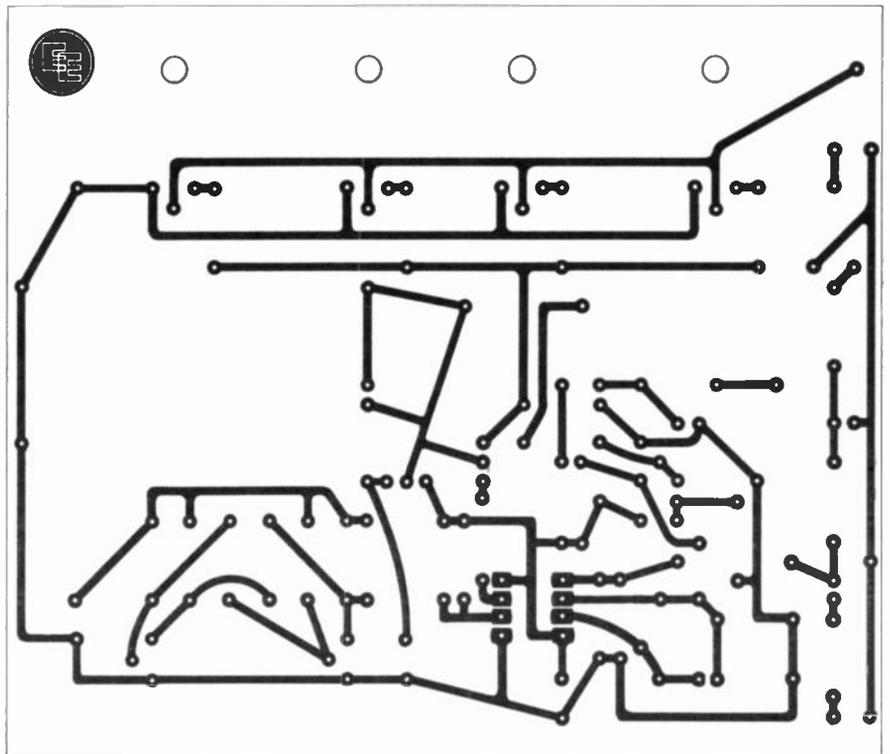


Fig. 3.6. Public Address System: Power Amplifier printed circuit board No. 2 (Inverter Board), actual size.

Fig. 3.7. Public Address System: Power Amplifier printed circuit board No. 2 (Inverter Board), topside with components in position.

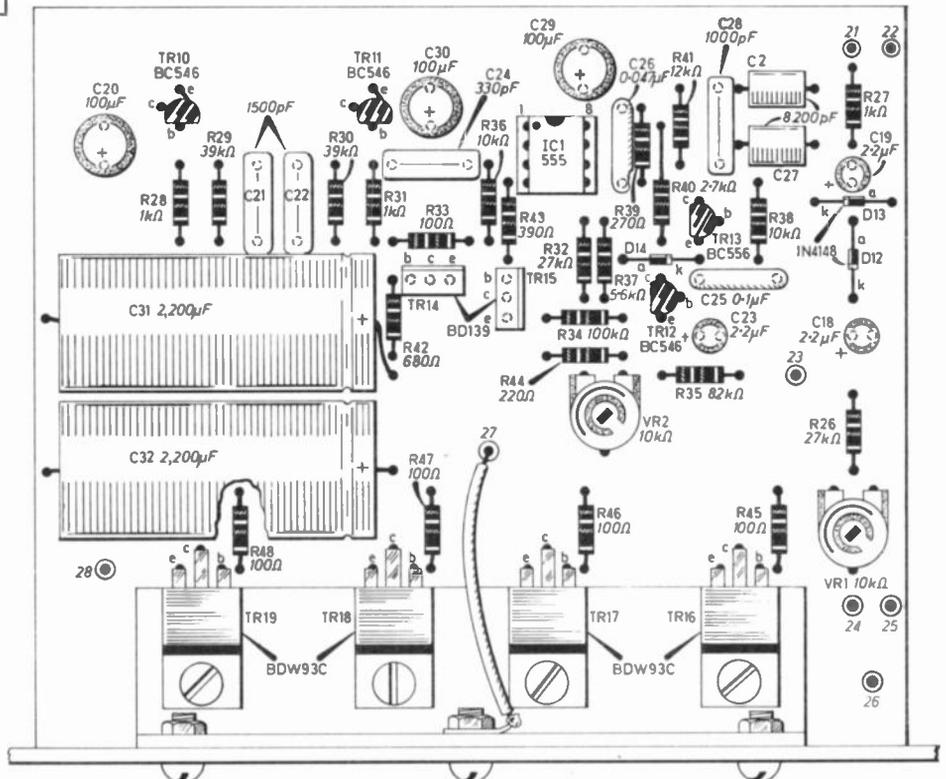


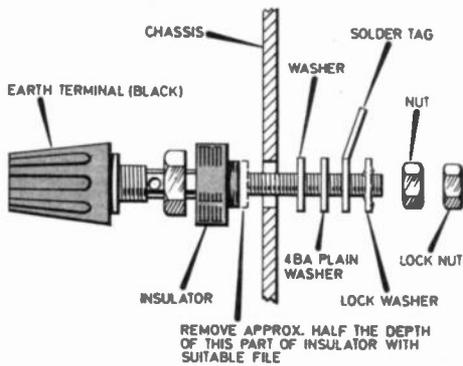


Fig. 3.11 Modification required to Earth terminal X1 (black).

Fig. 3.12 (right). Modified transformer T2. Two additional windings each of 24 turns are wound side by side (bifilar) over the normal transformer core as shown. See text.

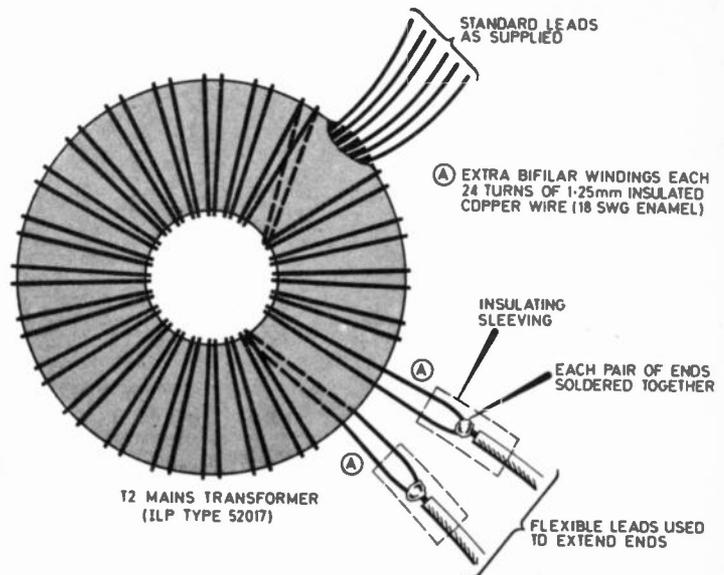

## GENERAL ASSEMBLY

Once the printed circuit boards have been assembled and carefully checked for good soldering and absence of solder "bridges" between tracks and components the general assembly can be started.

Fig. 3.10 shows how the power f.e.t.s are assembled onto the heat sinks. It is important that the insulating bushes used are the Hitachi type as these are longer than the more common types and will be long enough to come through both chassis and heat sink thickness; the more common shorter type will only come through the heat sink and may permit the screws to touch the metal chassis, causing a short circuit. This point may be checked out by an ohm meter.

The earth terminal is modified and assembled as shown in Fig. 3.11.

## MODIFIED MAINS TRANSFORMER

Two transformers are required if the full unit is being constructed: one for the line output and one for normal mains power supply. These are basically the same type of transformer: ILP type 5X017; which is the 160 VA type with a 30 volt plus 30 volt secondary. For the T1 line output order with a centre tapped 240 volt mains winding, ILP type 53017.

The transformer used for the power supply (T2) ILP type 52017 will need an extra winding if the battery powered version is being constructed.

This extra winding is wound by the constructor as is not difficult to do. Full details are shown in Fig 3.12.

Two windings are wound side by side (bifilar) each of 24 turns. These are wound with 18s.w.g. enamel insulated wire and the ends joined as shown. (The number of turns required is based on the ILP design and may not be suitable for other makes using a different turns/volt ratios).

The length of wire for each winding (before winding) is approximately 4 metres including ends. This should be measured off and any kinks removed before winding. The two windings should be wound evenly around the core as shown and care should be taken to avoid the wires "crossing over" each other.


After winding a layer of insulating tape should be wound over the winding to hold it in place and insulate it from contact with the chassis when mounted into position.

## FINAL WIRING

The final wiring layout is shown in Fig. 3.13. All wiring for the battery power supply and power f.e.t.s as well as the 8 ohm output should be done with at least 16/0.2mm (0.5mm<sup>2</sup>) conductors and preferably 32/0.2mm (1.00mm<sup>2</sup>) if possible. Currents as high as 12 amps can flow in these leads and the thicker wire will avoid voltage drop and power losses.

The remainder of the wiring can be carried out with 7/0.2mm p.v.c. covered equipment wire. These wires are available in many colours and different ones can be used as an aid to circuit identification.

Although the wiring layout is not critical in itself, the actual point of connections is, and these must be followed carefully.

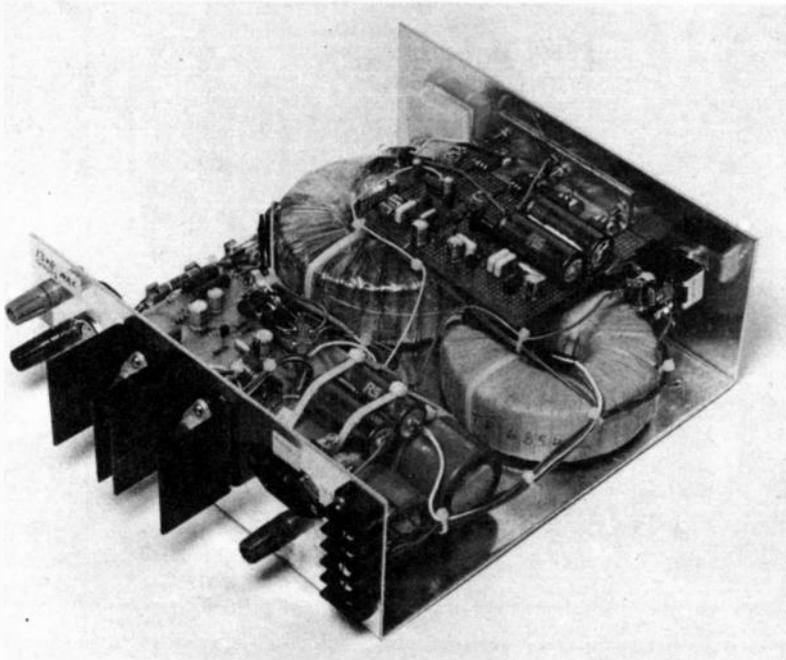



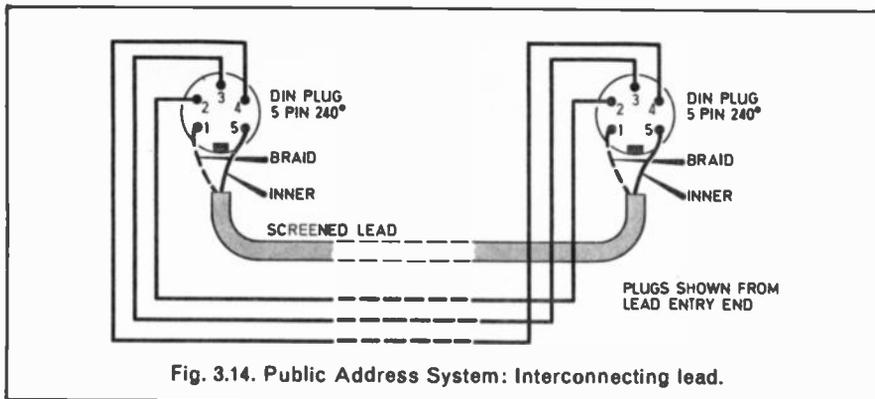


Fig. 3.14. Public Address System: Interconnecting lead.

Failure to follow as shown will result in increased background noise and/or distortion. This is particularly important with regard to the power supply circuits and the method shown for inter-connecting the two 4,700 $\mu$ F capacitors to the other parts of the circuit must repeat **MUST** be followed.

Do not be tempted to simply link (for example) terminal pins 3 to 7 to 12 to C15 thinking it will save wire and time, because it will greatly increase hum, noise, and distortion if you do.

With high power and sensitive inputs the actual method of wiring interconnections is vital to obtaining the full specification which the amplifier is capable.

The technical reason for making C15 the common point (in our example) is because the capacitor acts as the lowest impedance path to earth

for all signals flowing in the supply line. At the high peak currents involved in power amplifier and battery supply circuits it only takes a fraction of an ohm impedance common to two circuits to inject considerable amounts of unwanted signal into one of the circuits from the other one.

At the output from the bridge rectifier there would be a high ripple voltage and current present. Now, if the supply lead was taken direct from pin 12 to the early stages, the ripple voltage drop between C15 and pin 12 would be injected straight into these early stages. If we consider that the peak current could be several amps and the impedance of the wire 0.1 ohms we would in practice be injecting several hundreds of millivolts of ripple into the early stages power supply rail.

A similar thing happens with audio signals. By making C15 the actual common point, this unwanted signal is kept to the minimum possible.

### COMPONENT FIXING

The two transformers\* and the large electrolytics are held in position with large type plastic cable ties. Small type cable ties are used for holding cable runs. The RS types 543-428 and 547-717 respectively will be found suitable. C14 and C15 are held with additional ties once C16, C17 have been fitted.

Diode D15 will require its surplus stud cut off once mounted

The VU meter ME1 is held in position on the front panel with double sided Cellotape.

The two battery terminals are mounted in a similar way to the earth terminal (Fig. 3.11), but **WITHOUT** modification.

\*The ILP Ltd mounting kit is not used for the transformer fixing, although the foam washer is used between the transformer and chassis.

### INTERCONNECTING LEAD

An interconnecting lead is required between the two units to carry the power supply to the control unit and the audio signal to the power amplifier. The wiring details for this lead are shown in Fig. 3.14. As the output impedance of the control unit is

reasonably low the lead may be several metres long without loss of high audio frequencies, however in practice it is best to keep it as short as possible. Note that the DIN plugs are 5 pin 240 degree and **NOT** 180 degree types.

### ALTERNATIVE VERSIONS

There are a number of options which the reader may like to consider before starting to construct the amplifier.

1. It may be constructed with an additional socket (5-pin 240 degree DIN) on the power amplifier chassis. This will enable audio signals to be fed into extra slave amplifiers. To do this, move the existing socket higher by 20mm and also drill holes for a second socket with centres 20mm below the first. Wire the new bottom socket as before and link pins number 1 and 5 between the two sockets, (pin 1a to pin 1b; pin 5a to pin 5b). This will put an audio take-off on the top socket to drive another power amplifier. The d.c. power supply leads are **NOT** wired to the extra socket.

2. If Battery supply operation is not required, the mains transformer will not need the extra winding and only the VU meter section of the inverter p.c.b. need be assembled. The mains toggle switch can be changed for a standard two-position one and both live and neutral leads switch in the normal way. A standard 3 amp rated switch will be suitable. (Note that if battery power is intended the switch must be rated at 15 amps d.c.)

3. The line output transformer T1, C15, R24 can be omitted if 100 volt line operation is not intended. The output at 8 ohms impedance is not effected.

4. The fitting of an "ON" indicator to the power amplifier chassis. A suitable hole to take an extra l.e.d. can be drilled below the on/off switch and an l.e.d. wired with a resistor of 3.3 kilohms 2 watts rating in series, is fitted and wired between pin 11 (+50) and pin 14 (com). The current through the l.e.d. will be approximately 15 milliamps.

### SLAVE AMPLIFIERS

Additional amplifiers can be constructed when extra audio power is required. The main power amplifier construction is simply repeated with whatever options are needed. Each amplifier must drive separate load systems as they must not have their outputs commoned in any way. When used with battery supplies a separate battery should be used for each amplifier, if possible, to avoid earth loops in the power supply wiring.

To be concluded next month

### CONTROL UNIT—Part 2

Certain matters relating to the Assembly and Wiring (page 396) and Fig. 2.5 (page 398) need some further clarification.

1. Although the wiring layout is not critical in itself, the actual point of connections is, and these must in all cases be in accordance with the diagram Fig. 2.5.

2. Note that some screened leads do not have the braiding connected at both ends but only at one end and this is important. Where the two screened leads join behind the potentiometers the braiding must **NOT** be allowed to touch the chassis or rear metal case of the potentiometer. Note the way any earthing is carried out on input and power sockets and follow exactly.

The performance of the equipment may be impaired if these instructions are not adhered to.

**Everyday  
ELECTRONICS**

Presents

# Quizmaster

in the August issue

"Who was ready to answer first?" No doubt at all if this versatile machine is used during quiz competitions. A novel form of construction caters for various numbers of teams with various numbers of members.

## ROGER BLEEPER

An add-on unit for any citizen's band transceiver without the facility of an audio tone produced at the end of each transmission.


## TWO - TONE DOORBELL


A simple and effective unit for the front door. Has other uses wherever a distinctive audible alarm is needed.
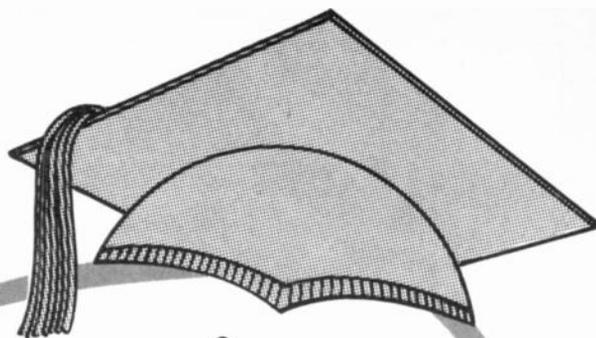
## Temperature Interface Unit for the Tandy TRS - 80 Microcomputer

Computes and displays on the screen of the TRS-80 Model I Microcomputer, the temperature of a remote sensor. Simply plugs into the expansion port of CPU console.

AUGUST 1982 ISSUE ON SALE FRIDAY, JULY 16



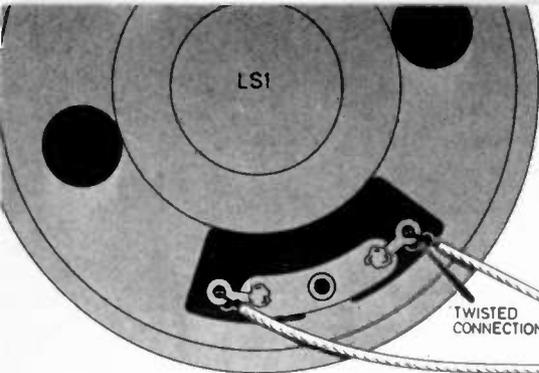

# two way

## USING THE EE SOLDERLESS TECH

**T**HIS article describes the construction of a simple two-way intercom that has been successfully operated at distances up to 25 metres between base and remote stations. It should also work effectively at double this distance but with reduced volume. It draws its power from a PP3 9V battery.

Other battery voltages may be used up to 16V, which allows operations from a car battery if required. A higher supply voltage leads to an increase in volume thereby extending its range capability.

### SIMPLE CONSTRUCTION

The project and its construction technique were developed following a request for a simple, easy to construct project for the novice which did not require any special skills or tools such as those associated with soldering. Also, component cost had to be low.

The choice of screw terminal blocks in the construction allows the unit to be assembled using only a few tools: a screwdriver, a means of stripping the insulation from a wire, and a wire cutter (scissors?). In fact there are screwdrivers available that have a wire stripper built into the handle which could also be used for cutting wire.



### COMPONENT IDENTIFICATION

The components are to be interconnected according to Fig. 1. First of all, identify each of the components. The values of the capacitors are printed clearly on the body of the component. Note that these have an indentation around the body at one end. This is the positive (+) terminal and must be connected as shown in Fig. 1.

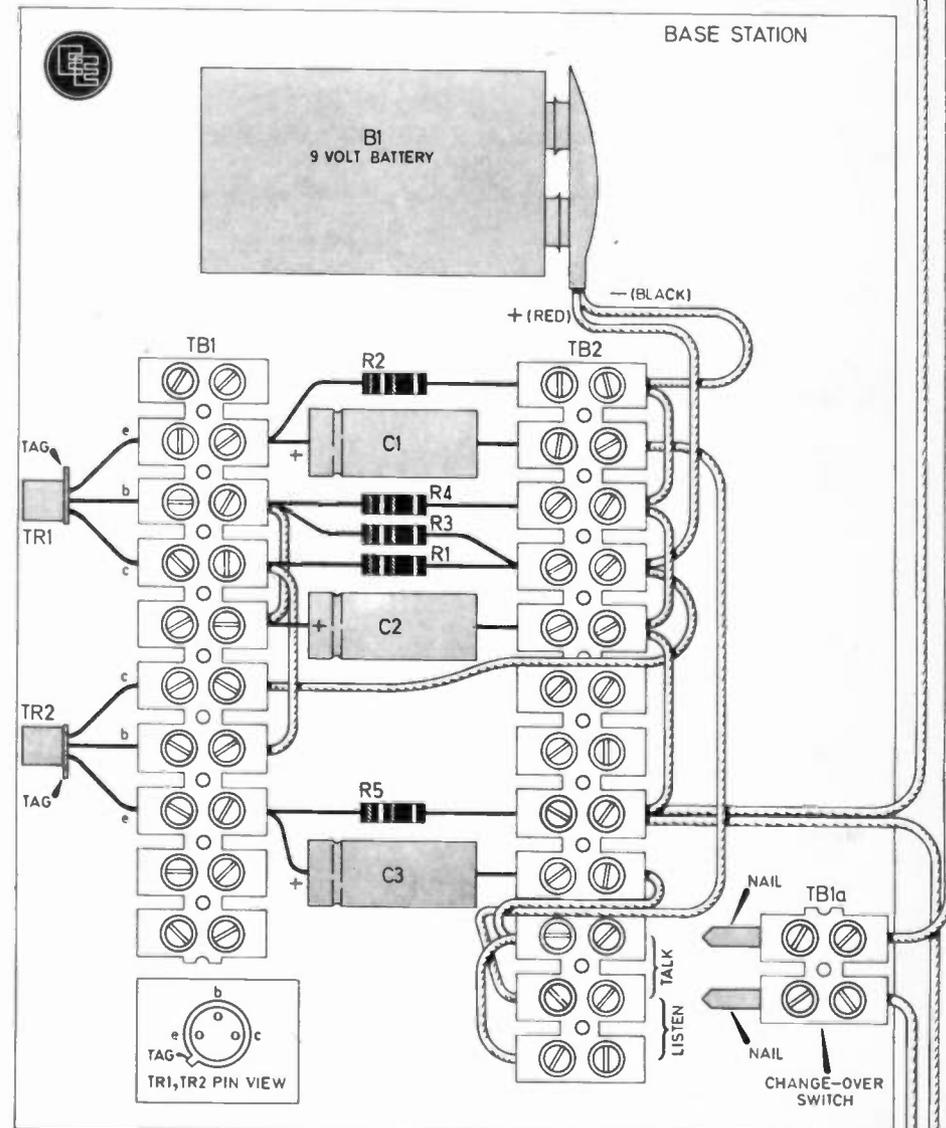


Fig. 1. Actual size layout and interconnection diagram of the Two Way Intercom. This may be used as a template.

The resistors have their values printed on the body in the form of a coloured-band code. For those not familiar with this coding system, refer to Fig. 2 for identification details. Resistors may be connected either way round.

### INTERCONNECTION TEMPLATE

The interconnection diagram, Fig. 1 is drawn actual size which allows it

to be used as a template during assembly. First of all, cut off the end two-ways from one of the blocks. This will be used later for constructing the changeover switch.

Place the now 10-way terminal block (TB1) over its position in Fig. 1, and then working from top to bottom, connect the components to TB1 by feeding the component lead(s) into the holes in the brass inserts in



## UNIQUE BY E.M. TERRELL

REF	VALUE	BAND 1	BAND 2	BAND 3	BAND 4
R1	27k $\Omega$	RED	VIOLET	ORANGE	GOLD OR SILVER
R2	2.2k $\Omega$	RED	RED	RED	
R3	150k $\Omega$	BROWN	GREEN	YELLOW	
R4	18k $\Omega$	BROWN	GREY	ORANGE	
R5	1k $\Omega$	BROWN	BLACK	RED	

Fig. 2. Colour code identification of the resistors R1 to R5.

### COMPONENTS

#### Resistors

R1 27k $\Omega$   
R2 2.2k $\Omega$   
R3 150k $\Omega$   
R4 18k $\Omega$   
R5 1k $\Omega$

All  $\frac{1}{4}$ W carbon  $\pm 5\%$  page 455

See  
**Shop  
Talk**

#### Capacitors

C1, C2, C3 47 $\mu$ F 16V elect. axial leads (3 off)

#### Semiconductors

TR1, TR2 BC109 silicon *n*p*n* (2 off)

#### Miscellaneous

B1 9V type PP3  
LS1 LS2 miniature 3 inch diameter moving coil speaker (2 off)  
TB1, TB2 2A 12-way screw terminal block (2 off)  
Equipment wire: stranded insulated 7/0.2mm, 50cm; battery clip with leads for PP3; 2A bell or speaker wire, length as required.

Approx. cost **£4.50** excluding battery  
Guidance only

the block and then tighten the appropriate screw to securely grip the component lead. When all components (not the transistors yet) have been fitted, trim the leads on the other sides of the components so that they are of approximately equal length.

Next form these leads so that they align with the appropriate positions on the other terminal block (TB2) and then manoeuvre this over the component leads and tighten the

screws as before. Check all connections before proceeding.

The next step is to connect all the linking wires between the various terminal block positions. Cut the wires to the correct length to comfortably span the positions they are to link, and then remove about 1cm of insulation from each end. Twist each end to form a solid core. Where more than one wire is connected to the same terminal block position, twist together both ends to form one before inserting in to the block. Tighten the screws onto the wires as before to securely grip them, see Fig. 3. Attach the battery clip leads to their positions.

### TRANSISTORS

The transistors may be fitted next, but pay particular attention to their orientation for they may be permanently damaged if connected otherwise. Refer to the inset in Fig. 1 which shows details of the BC109 lead-outs. Note that the emitter lead-out is closest to the body tab. Make sure also that none of the leads are touching or in contact with the case of the transistor, for this is internally connected to the collector(c).

Two 25mm long wire nails (with heads cut off) should next be fitted to the remaining terminal block. This arrangement will function as a d.p.d.t. switch and allow communications in both directions.

### CONNECTING SPEAKERS

It only remains for the speakers to be wired in before testing. Twin bell wire or speaker wire is ideal. Remove about 1cm of insulation from each of the eight ends, separating the twinning at each end for about 10cm. Twist all the ends as you did with the linking wires. Feed the appropriate bare wire ends through the eyelet connectors on each speaker and twist to form a closed hook tightened on the eyelet. Finally wire the remaining four ends of these wires to the terminal blocks (TB2 and TB1a).

In the prototype intercom, the base station assembly was glued to thick card with the battery held in place with Sellotape. Alternatively it may be housed in a plastics box, with or without its speaker.

\* Freetime, Thames Television, Friday, 4th June, 1982, 4.45pm.

Some form of enclosure must be used to house the speakers, for both best results and protection. The cardboard boxes in which the speakers were packed made quite effective enclosures once cut-outs were made.

### IN USE

Place TB1a in the TALK position on TB2. Connect the battery. A click will be heard in the remote station speaker. Get someone to speak into the base station speaker, and if you have carried out the assembly correctly, you will hear their message in your speaker when positioned fairly close to your ear.

Now move TB1a to the LISTEN position to allow the person at the base station to receive your message.

As there is only one-way communication at a time, the speaker should, when he/she has finished his/her immediate message sign off with the word "over". "Over and out" would mean the conversation has ended. The base station should normally be left in the LISTEN mode for incoming messages.


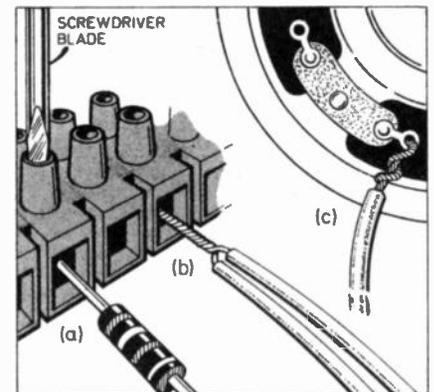


Fig. 3. Fixing component lead and two wire links to one block position (a) and (b); (c) shows wire connection to speaker eyelet.

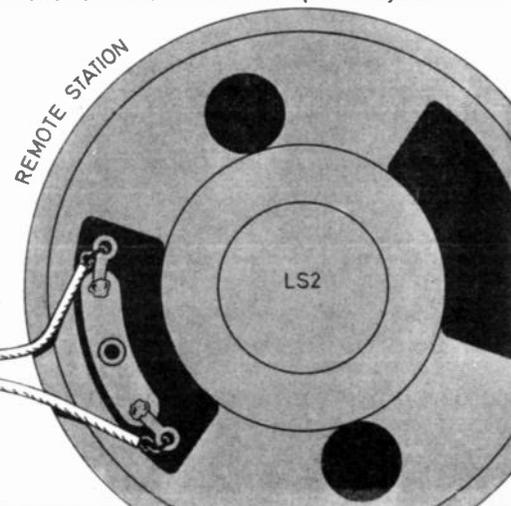

## CIRCUIT DESCRIPTION

The circuit diagram for the Intercom is shown in Fig. 4. The two speakers, LS1 and LS2 are used both in the normal loudspeaker mode, and in "reverse" as microphones according to their connection through the changeover "switch" arrangement.

When using a loudspeaker as a microphone, the pressure waves from the voice cause the speaker cone to vibrate in sympathy. Thus the coil connected to the cone moves in the field of the speaker magnet. This alternating motion causes an e.m.f. to be generated in the coil windings. The generated voltage follows the frequency and amplitude of the pressure waves reaching the cone. The amplitude however is very small, typically less than 1 millivolt.

## AMPLIFIER

Transistor TR1 is configured in a common-base mode which has very low input impedance and is capable of very high voltage amplification. To a first approximation the gain is given by the ratio of the value of R1 to the impedance of the microphone, that is  $27000/8=3300$  approx. (Loading of the second stage affects this figure).

The small a.c. signals developed in the "microphone" reach TR1 emitter via a.c. coupling capacitor C1 where they affect the base current flowing. The small base current variations cause much larger collector current variations (basic transistor action) resulting in a fairly large voltage change across R1. These voltage variations are available at the collector of TR1, the output of the voltage amplifier.

This voltage cannot be used directly to drive a loudspeaker as the

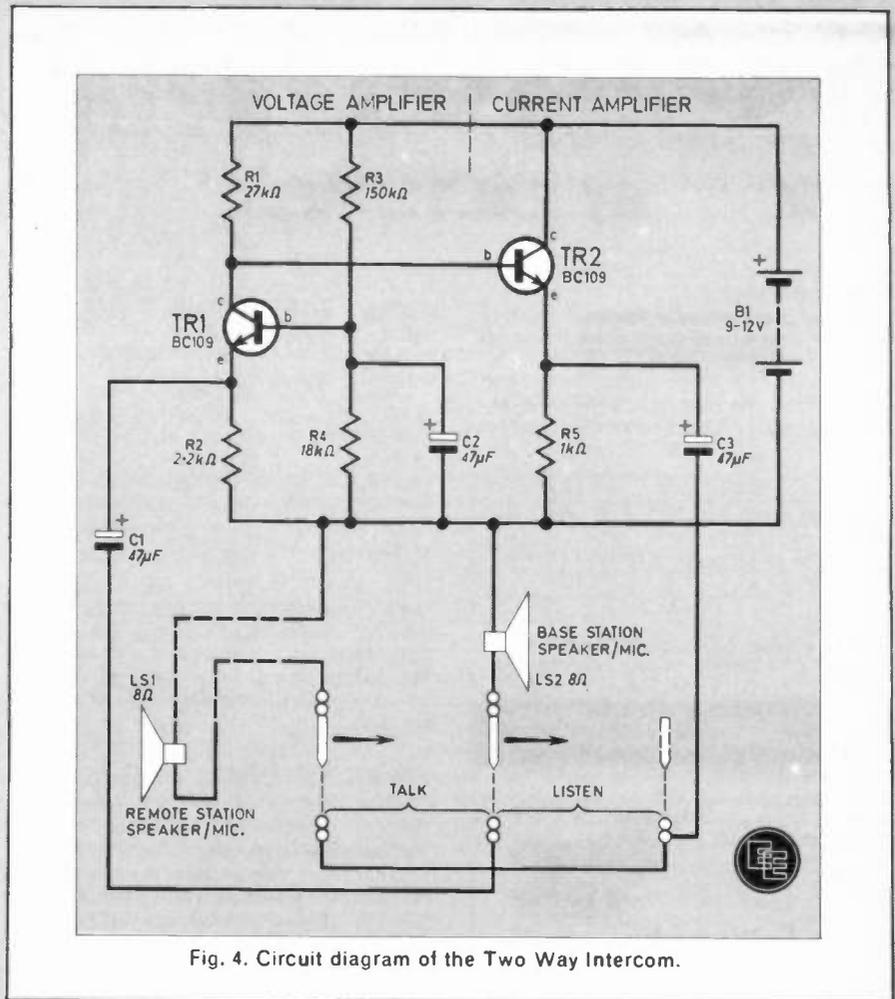


Fig. 4. Circuit diagram of the Two Way Intercom.

output impedance is high and consequently output current low. The function of TR2 (wired as an emitter follower) is to multiply this current by the gain factor of TR2 (typically 200) to produce a level suitable for

driving an 8 ohm loudspeaker. The voltage is slightly reduced by this stage of the circuit. The signal has thus received voltage and current amplification, the power being taken from the battery. □

## JACK PLUG & FAMILY...

BY DOUG BAKER



# RADIO WORLD

By Pat Hawker, G3VA

## Museum Pieces

During the past few years there has been increasing interest in "antique radio and television" and many of the domestic receivers of the 1920s, 1930s, 1940s and even 1950s are now being eagerly collected and restored. Surprisingly there is no really good permanent collection of such sets in any of the London museums.

A few years ago an excellent display of "wireless sets" covering 1922-1956 could be seen for some weeks at the Victoria & Albert Museum and attracted a large attendance. For this exhibition The British Vintage Wireless Society produced three wall-posters and a set of these on my office wall continues to arouse the interest of visitors. More recently this museum staged an excellent display of the original pen and ink drawings from early issues of the Radio Times.

The Science Museum brought together early television sets for its special "50 year" television exhibition in 1980—the Science Museum also has its permanent "Telecommunications" gallery though this provides more formal history and rather less nostalgia. For several years there has been talk of setting up a television museum at Alexandra Palace, and of course there are several "private" museums in the UK such as those run by Ron Ham and David Byrne.

## Texas Broadcast Museum

During a recent visit to the annual National Association of Broadcasters convention and exhibition in Dallas, Texas, I took the opportunity of visiting *The Texas Broadcast Museum* which claims to be the "world's largest broadcast museum". It emerged from the private collection of Bill Bragg (a video engineer at a Dallas television station) who as a youngster began collecting anything which involved broadcasting and gramophones; equipment, receivers, autographed photographs, magazines and literally almost any other broadcast memorabilia.

A few years ago, with his home overflowing with hundreds of items, the Bragg family "went public" and with a start-up fund of just \$25 moved their collection into shop premises in the main central area of Dallas—it has been growing ever since. Very far from being a formal history of broadcasting and the amateur radio bug, it really is the most fascinating "attic" of long discarded bits and pieces—with tapes and "78s" discs of famous American stars of yesteryear adding to the atmosphere.

## Collector's Items

A couple of bulky broadcast transmitters, 40 working Edison phonographs, listening booths, Edison's microscope, Bill Haley's guitar, Walter Cronkite's farewell microphone, old scripts, early wire and tape recorders, are all on display.

While set names, such as Atwater Kent, Paragon, Grebe, Philco "Cathedral", may be unfamiliar to British readers—they represent an important slice of the domestic history of our age.

I noted the 1940s Hallicrafters small-screen television receiver with a strong likeness to that firm's then current range of communications receivers. Similarly, I welcomed the opportunity to browse through a varied selection of old magazines and booklets including a description of amateur radio at the 1933 Chicago World's Fair.

The museum by no means adopts a rigid "hands off" policy and it seems to be run by the Bragg family on a very informal basis that adds to the attraction—not only to those who recall the days when the equipment was in many homes but also, I noted, to a party of school-children who seemed to be vastly enjoying the records of the Boswell Sisters, early Bing Crosbys and the big band era.

## American A.M.

When from time to time I have been in the USA I have always admired the extremely well-organized way in which their medium wave a.m. broadcasting works, at least from a technical point of view. In Europe we have been conditioned to accepting an appalling amount of co-channel interference, particularly during the hours of darkness when the ionosphere reflects back signals from stations several hundreds of miles away.

On many of the low power stations one now accepts that night time coverage, far from being greater after dark, is in reality only a small fraction of the daytime coverage. Some channels, occupied by very high power stations attempting to broadcast to other countries, are virtually only useful for a single station over the whole of Western Europe.

In the USA, once the chaos of the early days of broadcasting was overcome, the system has been well planned. Many a.m. stations are "daytime only" closing down as darkness falls to leave "clear channels" for others, and even these clear channel stations are limited to a maximum of 50kW.

## Directional Aerials

For many years, very good use has been made of highly directional aerial arrays using up to about a dozen masts, carefully designed to produce "nulls" of minimum radiation towards other stations using the same frequency. It is all a giant jig-saw pattern but it means that listeners in the cities, both during the day and night, can tune to many different stations, each coming through clearly enough to give reasonably good quality reception.

This year, at Dallas, I found a good deal of anxiety. Many of the a.m. broadcasters are worried that the present situation may

deteriorate rapidly due to the intention of Cuba to build many more a.m. stations, not using directional aerials, and with at least two 500kW transmitters. Calculations show that if the Cubans go ahead with their plans—they recently walked out of an international planning conference—a considerable number of American stations will lose between 90 to 99 per cent of their interference-free night time coverage.

To be fair to the Cubans, part of the problem has arisen from the intention of the Americans to broadcast on medium waves to Cuba. Up to now the radio propaganda "war" has been waged on short waves—including a period when the CIA operated an anti-Castro station on Swan Island in the Caribbean.

## A.M. Stereo

Another problem is facing the American a.m. broadcasters. Many of them are keen to introduce stereo on medium waves and for several years the FCC has been trying to decide which a.m. stereo system would be best. Now it has given up and ruled it must be left to the marketplace to decide.

There are still four aggressively-competing systems: Magnavox, Motorola, Harris and Kahn/Haseltine. Unfortunately the systems are not compatible and American anti-trust laws make it illegal for the broadcasters to agree among themselves on which system to use. So listeners may find their new a.m. stereo set can only be used on a few stations, or more likely it will delay the widespread use of any system unless it proves possible to design a universal decoder; difficult and very expensive.

Broadcasting in the States shows much rivalry between AM and FM stations and is based on 10kHz channel spacing. For these and other reasons it may be some considerable time before there is any move to start a.m. stereo in Europe.

"Faulty vertical hold, I'd say".



# Everyday News

## ROYAL AWARDS FOR THE

... FROM AIDS FOR INDUSTRY TO AIDS FOR THE DISABLED ...

Electronics figured prominently in this years 1982 Design Council Awards

For the first time a CHIP was given an award. LUCY, Mullard's teletext decoder chip was the happy recipient!

THE 1982 Design Council Awards were presented to 34 British companies by HRH The Duke of Edinburgh at a ceremony at the Barbican Centre, London.

The awards were given for a wide range of products. Among five motor awards there were two commendations for prototypes.

Engineering products and components award winners, eight and four awards respectively, came from the agricultural, aviation, robotics and micro-electronics fields. Four awards were made in the medical area for laboratory aids, surgery equipment and a mobility aid for handicapped children.

We regret that we are unable to mention all winners by name, but have selected a few to give some idea of the formidable task in winning one of these highly prestigious symbols of excellence.


### Lucy the Chip

It is fitting in 1982, designated Information Technology Year, that LUCY, a customised i.c. designed by Mullard for viewdata-type applications should win an award.

It has been designed specifically as part of a decoder used in TV terminals suitable for viewdata-type applications, where coded alphanumeric and graphic information is transmitted from a computer data base down the telephone line.

The function of the chip is to act as a general interface between various data sources and the microprocessor in the decoder. The circuit density of LUCY is so high that it combines the functions of the many conventional peripheral integrated circuits previously used in viewdata decoders. The result is a more compact, cheaper and more sophisticated decoders for viewdata systems.

The Homer 5 marine receiver.

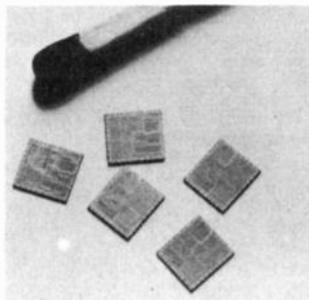

### Marine Call

Brookes & Gatehouse is the first marine electronics company to win two consecutive awards. This year the award has been given for the Homer 5 marine radio receiver.

The major advance in the design is that it is controlled by a microprocessor and has brought low cost sophisticated reception to a wide range of craft.



HRH The Duke of Edinburgh presenting an award to Ivor Cohen of Mullard for the company's LUCY chip (left), used in viewdata decoders.

### Mobile Aid


An award in the Medical Equipment section went to Malden Care for their Rally Special Go-Kart, a stylish vehicle for disabled children that provides them with a greater freedom of movement outdoors. The judging panel commended the obvious consideration that had been given to safety factors.

An electronic controller gives full directional and speed control from a joystick that can be mounted right or left of the driver. By gently pushing the stick halfway forwards, the

vehicle moves forward at half-speed; fully forward provides a speed of not more than 2.5mph.


The speed is controlled so that it will not increase on a downward slope. A key-switch at the back enables parents to immobilise the Go-Kart so that children, disabled or able-bodied, cannot go for unintended joy rides!

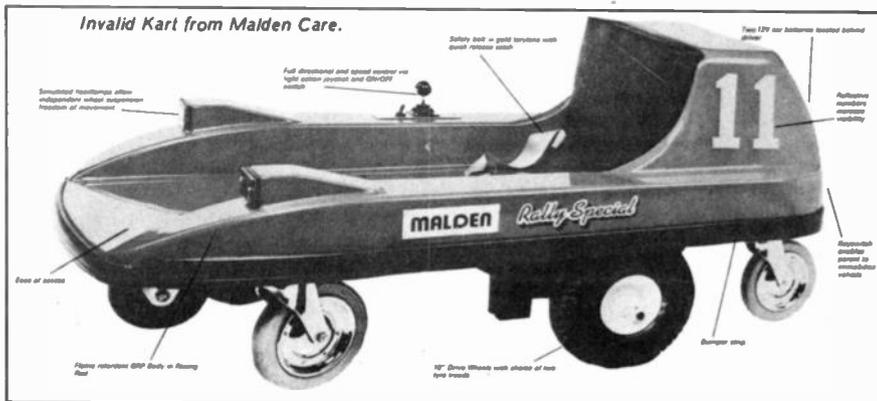Additional features for the Go-Kart include a detachable "bonnet" to protect legs, and a remote control for children who cannot drive the vehicle themselves.





# INNOVATORS

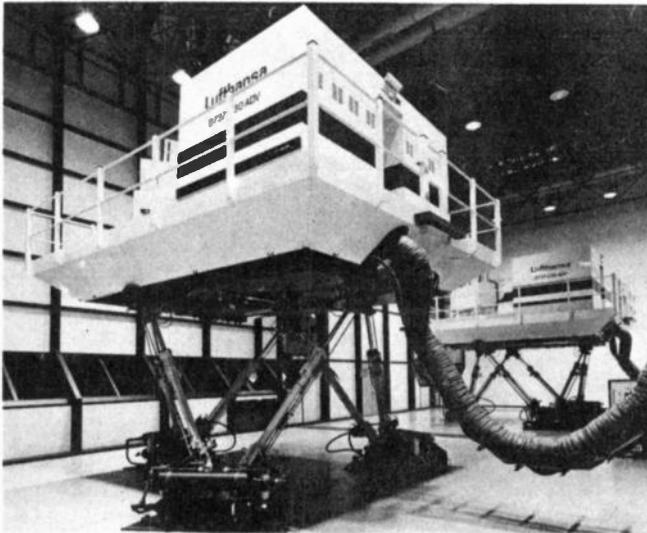

Advanced technology flight simulator from Rediffusion Simulation was an award winner in the engineering section.

## Flight Simulator

Two and a half tonnes of fuel is burned up every time a jumbo jet takes off. Increasing fuel prices, coupled with ever-tightening flight schedules means that fewer aircraft can be made available for essential crew-training.

A British company, Rediffusion Simulation Ltd from Crawley, has provided the answer to this world-wide problem, with the development of an advanced technology flight simulator for training crews in the most realistic conditions on the ground.

The main design criterion was to create a totally realistic training environment in terms of both the physical and performance characteristics of a particular aircraft. This has been achieved physically by fully reproducing the aircraft flight deck, making maximum use of original instruments, flying controls and furnishings.

Sensory cues of motion, control feel, vision and sound are provided through separate systems and co-ordinated by a central 32-bit computer programmed with flight data relating to each specific aircraft simulated.

## Robotics

In the area of robotics, the CompArm robot manufactured by Hall Automation is one of the leading examples designed to provide fully automatic spraying, previously carried out by operators in paint booths.

The arm is controlled by the HAL 90 computer control system with a solid-state, non-volatile memory with separate modules of 10 minutes capacity, and which can contain up to 63 separate spraying programmes.

## Computers

We leave readers to guess who took the computer award? But when last seen, not on the BBC, he had the full spectrum of expressions on his face and was using the code name ZX81.

## The Future

As this year's winners celebrate their success The Design Council begins its search for the 1983 Design Council Award winners and invites submissions for its five Awards categories—Engineering Products, Engineering Components, British Motor Industry, Medical Equipment and Consumer and Contract Goods, both decorative and durable.

## TELETEX

By international agreement the term Teletex is to be used for high-speed message transfer (electronic mail) in the UK and overseas networks.

Not to be confused with teletext, a term used to describe broadcast viewdata services such as Oracle and CEEFAX. UK Teletex starts on a pilot scale almost immediately with full implementation of domestic and international service by 1984.

A new industrial robot developed by Fujitsu is said to have such delicacy and accuracy of touch that it can be used to assemble small electronic components and watch parts.

World leader in semiconductor sales, Texas Instruments, is forecast to lose the championship in the coming year to challenger Motorola who has been Number Two for many years. Both companies have world sales of more than a billion dollars with TI currently leading at 1.3 billion against Motorola's 1.2 billion.

## ANALYSIS

### ZERO-ONE

Digital technology has become so dominant in recent years that many of us imagine it is not only fashionable but also something completely new. The fundamental idea is a binary system in which the basic operational component is a two-state device which can be either "on" or "off". In electronics, diodes or transistors can be used as switches in circuits whose signal paths always have one or other of two possible voltage levels or, in the terminology, logic level zero or logic level 1.

The principle of two-state signalling is nothing new. It was well-known to the ancients and has been practiced throughout recorded history. Perhaps the earliest examples were fire beacons recorded in the literature as early as 500 BC. Fire out, level zero. Fire lit, level 1.

An extended system of this type was used in 1588 between Plymouth and London to signal that the Spanish Armada had been sighted. The beacons were spaced some eight miles apart over 200 miles and it took 20 minutes for the message to reach the capital, the delay being the time it took to light each beacon in succession along the chain. But this was still very much faster than relays of riders on horseback.

The drawback of simple on-off signalling is its low information content of only one "bit". London was informed of the sighting but still knew nothing of the size of the Armada or its intention. It was also necessary to know in advance that beacon lit meant Armada sighted.

The electric telegraph was the big breakthrough in long-distance signalling, became faster, more private and independent of visibility. The two-state on/off principle was still used but the invention of a dot/dash, mark/space code by Samuel Morse (1791-1872) made it possible for alphanumeric messages of any complexity to be transmitted and received. The principle was as before but the information content was now virtually infinite.

By 1862 Britain had 15,000 miles of installed electric telegraph. The peripheral equipment was a Morse key for sending and headphones for receiving. Some sixty years ago those peripherals were updated to keyboard entry and printer read-out for commercial use.

The modern "digital revolution" is merely an extension of an old principle. The difference today is in sheer speed and handling capacity of very large quantities of logic states, in their marshalling, manipulation and storage. Zero and 1, the simplest of all signals, remains the operating principle of all digital computers, digitally controlled machines and processes.

Brian G. Peck



there is a poor electrical connection; at the socket on the towbar, for example.

### CIRCUIT OPERATION

The circuit diagram is shown in Fig. 1. When the brake pedal is pressed, the brake light switch closes as the car brake lights operate in the usual way. A small current also flows through R1 into the base of transistor TR1. This turns it "on" and as TR1 is directly coupled to TR2, as a Darlington pair, this is also turned "on".

TR2 is a power transistor capable of carrying the current needed for the trailer brake lights which are connected in its emitter circuit.

The collector current for TR1 and TR2 flows through a coil of wire (RLA/1) wound around the body of a miniature reed switch (RLA1). This will be operated by the magnetic field generated by the current flowing through the coil.

When construction is complete, the number of turns of wire on the coil will be adjusted so that the current for two lamps will be sufficient to operate the reed switch but the current for one will not. Thus, if one or both lamps fail or if there is a poor electrical connection, the reed switch contacts will fail to close.

### WARNING LIGHT

The reed switch contacts could be used to operate the warning light, LP1, directly but then this light would operate each time the brake pedal was pressed in normal operation. This is unsatisfactory; the warning light should stay off in normal use and only operate in cases of failure.

WHEN fitting a trailer or caravan to a car, one important point is often overlooked. This is to provide some assistance to the brake light circuit to relieve the load when the additional lights are operated.

The usual solution is to simply wire the caravan brake lights in parallel with those on the car, which will work but the switch will now pass *twice* the normal current and this can cause premature failure. Where the switch is of the type directly operated by the brake pedal, replacement is straightforward, but if it is of the pressure-operated type placed in the hydraulic brake line replacement is much more costly. This is because air will enter the system when the old unit is removed and "bleeding" will be necessary when the new switch is fitted.


Apart from it being illegal to drive a car with defective brake lights, such failure will endanger other road users.

The answer is to install a relay circuit which will operate the additional brake lights while imposing negligible load on the existing system and some commercial units employ a mechanical relay, but here we have used a power transistor to do the actual job of switching.

In designing this project, it was also thought worthwhile to add a special safety feature. This is an indicator light placed on the car dashboard which warns the driver that one or both trailer brake lights have failed.

As well as indicating "blown" bulbs, the warning light will also operate if

Fig. 1. Circuit diagram of the Brake Light Relay unit. Note that the inset diagram of the vehicle break light circuit is representative only and therefore omits certain details.

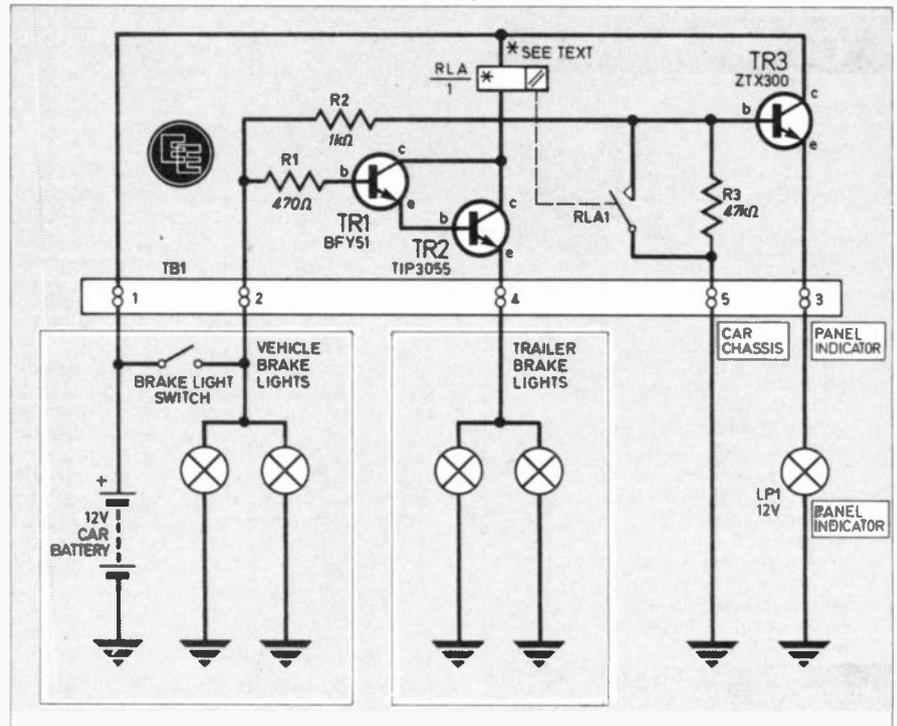

One method of achieving this would be to use a reed switch with *normally closed* contacts but these are uncommon. So as most reed switches have *normally open* contacts and are cheap and readily available, one of these was used along with TR3.

When the brake light switch is made, current also flows into the base of TR3 via R2, turning it "on". However, before there is time for LP1 (connected to the emitter of TR3) to light, the reed switch contacts close, earthing the base of TR3, turning it firmly "off".

## BRAKE LIGHT FAILURE

If a brake light fails, then the reed switch contacts will remain open since there will be insufficient current through RLA/1, and the warning light will operate. The purpose of R3 is to ensure that TR3 is "off" during the time when the brake pedal is not pressed.

From the foregoing it can be seen that the warning light will operate each time the brakes are operated whilst *not* towing a trailer, because, as far as the circuit is concerned, there is "failure" of the trailer brake lights. It is necessary to either disregard this or to fit a small switch on the dashboard to cancel the indicator when not towing. To preserve the safety feature it is, of course, necessary to remember to switch on again when towing.

## CONSTRUCTION

The prototype was built in a metal "throat lozenge" tin 85×65×22mm. This not only provides mechanical strength but also acts as a heat sink for TR2. For this reason a plastic box should not be used.

## COMPONENTS

### Resistors

R1 470Ω  
R2 1kΩ  
R3 47kΩ  
All 1/4W carbon ±5%

See  
**Shop  
Talk**

### Semiconductors

TR1 BFY51 *npn* silicon  
TR2 TIP3055 *npn* silicon  
TR3 ZTX300 *npn* silicon

page 455

### Miscellaneous

TB1 5A, 5 way terminal block  
LP1 12V panel mounting indicator  
RLA 6-RSR-A miniature reed switch, normally open contacts with six turns of 1/0.6mm wire (see text)  
0.1 inch pitch strip board, 13 holes by 16 strips; case to suit; grommet; transistor mounting kit; 4A auto type stranded wire; auto type spade connectors; auto type bullet connectors; board mounting hardware.

Approx. cost  
Guidance only **£5** excluding case

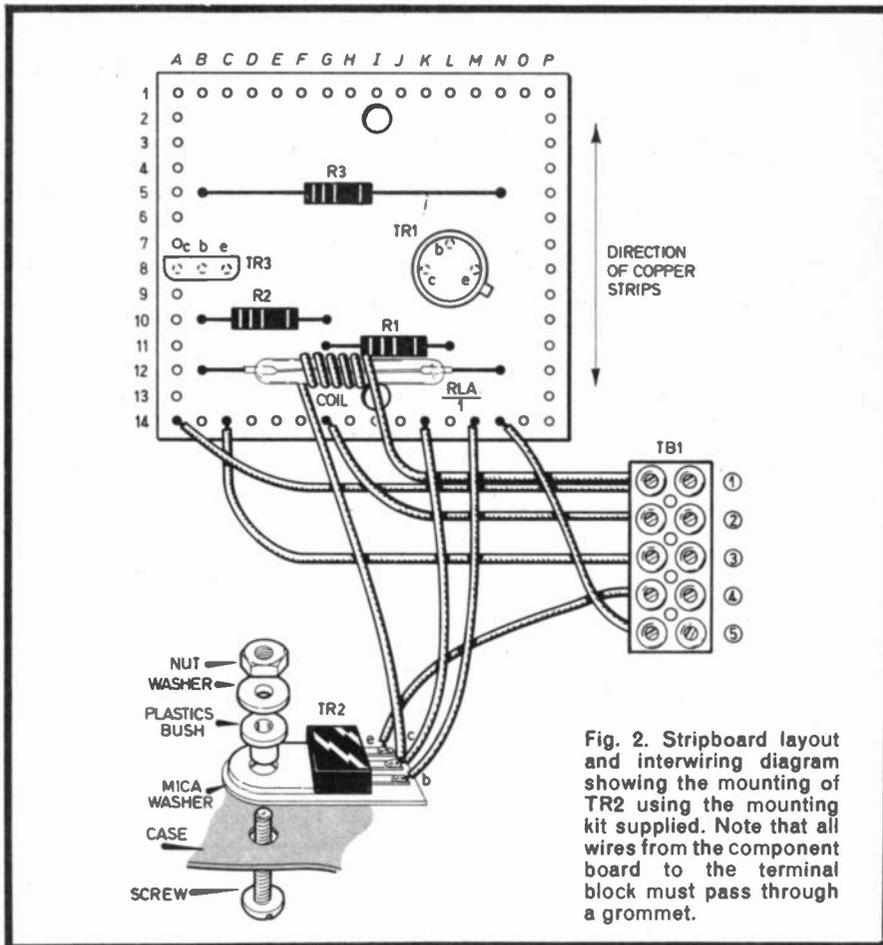


Fig. 2. Stripboard layout and interwiring diagram showing the mounting of TR2 using the mounting kit supplied. Note that all wires from the component board to the terminal block must pass through a grommet.

Most of the circuit is built on a piece of 0.1in pitch stripboard, 16 strips by 13 holes as shown in Fig. 2, with the exception of TR2 and the terminal block.

When fixing TR2 into the case, the mounting kit supplied must be used to electrically isolate it. The kit consists of a mica washer and a plastic bush and is assembled as shown in Fig. 2

## REED RELAY COIL

To begin with, the coil RLA/1 should consist of six turns of ordinary 1/0.6mm single core insulated equipment wire. This will be approximately right for the reed switch specified. There are differences between reed switches of the same type, so it is possible that some adjustment will be required later.

The circuit panel is secured inside the box using nuts, screws and stand-off insulators. These stand-offs may be made from two short pieces of plastic wall-plug. They are essential to ensure that the copper strips on the circuit panel do not touch the metal box and cause short circuits. Where wire connections pass through the box to the 5-way terminal block on top, a rubber grommet must be used.

## INSTALLATION

The finished unit may be mounted in the boot of the tow-car. It can, perhaps, be concealed behind a trim


panel but it is best to leave it free for the time being since final adjustments may be necessary.

Locate a fuse which is "live" only when the ignition is turned on with the aid of a 12V test lamp and run a length of wire from this fuse to TB1-1 on the unit. This wire *must* be of the stranded variety and be rated at 4A minimum. An automotive type connector must be used at the fuse end and if all available outlets from the fuse have been used, a "piggy-back" connector may be obtained from a car accessory shop to turn one outlet into two.


Wherever wire must pass through a metal panel in the car, a hole should be drilled and a rubber grommet fitted. Now run a wire from the indicator light LP1 on the dashboard to TB1-3 on the unit. This may be light-duty wire but must still be of the stranded automotive type.
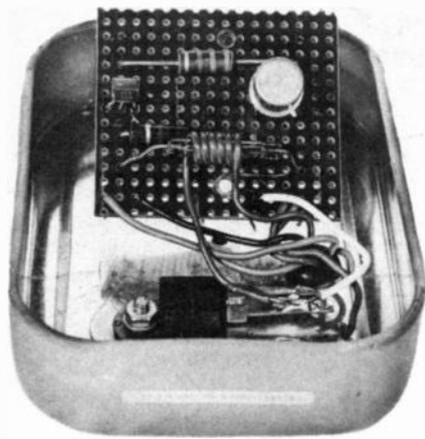
## BULLET CONNECTORS

Using a little detective work, locate the wire which leads from the existing car brake light system to the socket on the tow-bar. This wire should be broken at a convenient place and insulated "Bullet" connectors inserted to extend both free ends to the position of the unit. These connectors should allow the two ends to be joined together again so that "conventional" operation is once more possible in the event of the unit failing or, perhaps, when selling the car.



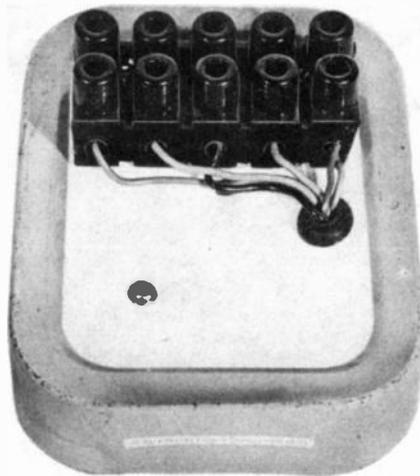View inside the finished prototype showing the circuit board and power transistor mounting.



The terminal block is mounted onto the base of the "lozenge" tin as shown.

The free wire leading to the existing brake lights should go to TB1-2 whilst that leading to the tow-bar socket should go to TB1-4 on the unit. Finally, TB1-5 on the unit should be connected to an earth point. One may already exist nearby or alternatively, a small hole may be drilled in the metal and an eyelet and self-tapping screw used. Ensure that the paint is scraped away from the area of contact.

### MOUNTING

An ideal way of securing the finished unit to the bodywork is by means of two self-tapping screws through the lid. In this way, the entire circuit may be "snapped" into position and removed just as easily.

The indicator light LP1 is mounted in the dashboard. One terminal is "earthed" and the other connected directly to TB1-3 or via the panel switch described earlier.

### FINAL TESTING

The circuit is now ready for final testing. The caravan plug should be connected to the car and the rear covers removed from the light clusters on the caravan. With the ignition switched on and the brake pedal operated, all four brake lights should operate and the panel light should remain off. If the panel light comes on when the lights are working, a few extra turns of wire should be added around the reed switch.

When one brake lamp is removed from the caravan the panel light LP1 should now signal a fault when the brake pedal is pressed. If LP1 stays off then there are too many turns of wire around the reed switch and a few should be removed. With both bulbs removed from the rear of the caravan, or with the caravan uncoupled, the indicator should again light.

When the correct number of turns have been found for RLA/1 it is advisable to "lock" them with a little adhesive. Check that everything works with the engine running.

All being well, the trim panel can be replaced and the unit left to do its job. As this circuit works along the lines of the old maxim that "prevention is better than cure", the extended life of the brake light switch is unlikely to be noticed. However, one day, when the dashboard indicator warns you of a failed bulb, you will bless the day you built this project! ☐

**DON'T FORGET TO PLACE A FIRM ORDER FOR**

**JOIN UP WITH LITESOLD**

Litesold's new 'L' Series soldering iron — now at a bargain price. Outstanding performance. Lightweight. Easy to maintain. Elements are enclosed in Stainless Steel shafts, insulated with mica and ceramic. Non-seize interchangeable bits, choose from 'copper' or 'long life'. A very special tool at a very special 'direct' price. Just £5.58 for iron fitted with 3.2mm copper bit. Just £2.40 for 3 spare copper bits (1.6; 2.4; 4.7). A mere £4.38 for professional spring stand! Or buy the lot for £11.12! and save 10%.

All prices inc. VAT P. & P.  
Please allow 14 days delivery.  
Write today. Send Cheque/P.O. to Litesold, 97-99 Gloucester Road, Croydon CR0 2DN or phone 01-689 0874 for Barclaycard/Access sales.

**LITESOLD**  
LIGHT SOLDERING DEVELOPMENTS LTD

**LIGHTNING**

**DO YOU NEED:- Electronic components, Tools, Test Equipment, Cases, Cabinets and Hardware etc. IN A HURRY? THEN YOU NEED:-**

**LIGHTNING Electronic Components.**

**WHY?**  
Because LIGHTNING Strikes out where others fail:-  
Express Despatch All Low Prices In Depth Stock  
All New Guaranteed Goods from Leading Manufacturers

With all that going for us, going to you can you really afford to be without a copy of our brand new exciting CATALOGUE?  
Many Prices Reduced — Many More Stock Lines  
Send for YOUR Copy Now, ONLY 70p Post Paid

**LIGHTNING ELECTRONIC COMPONENTS**  
84 Birchmoor Road, Birchmoor, Tamworth, Staffs. B78 1AB. (NOTE New Address)

**TITAN TRANSFORMERS AND COMPONENTS**  
**CENTRAL HALL CHAMBERS, GRIMSBY DN32 7EG**

**Mail Order only — Prices include 15% VAT**

**Inverters**—high quality frequency stable 12 volts DC. 240 AC/50Hz/100, 250 and 300 watt. 24 volts DC/240 AC/50Hz/500 watt.

**Voltage Stabilisers**—Coarse or fine regulation. High speed Null switching 170/260V/50Hz. 100VA to 5KVA plus other sizes.

**Adaptors**—Switchable 6-7-5-9V 300MA unregulated. 6-7-5-9V 250 MA regulated.


**Battery chargers**—2 volts & 6 volts, power supplies and a full range of transformers.

Send S.A.E. for details of product you are interested in.



Telephone Messages

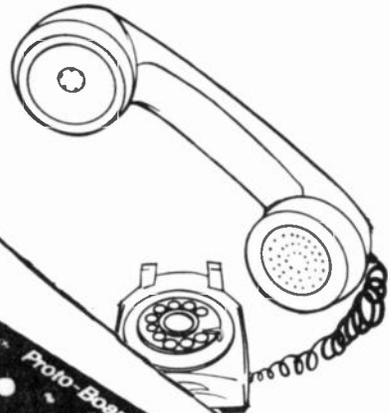**STILL  
SOLDERING ON?  
A MESSAGE FOR  
OLD SOLDERERS**



At last the message has come through, all you old solderers can throw away the soldering irons and the perforated circuit boards. NOW you can use PROTO-BOARDS from GSC. Despite daily break-throughs in components and packaging, designing and testing new circuit concepts is often a lot more manual work than creative work. No wonder if you are using old fashioned perforated boards and time-consuming soldering. With PROTO-BOARDS any component can be plugged in, tested, removed, and used again. Circuits can often be designed from component pinouts and the circuit diagram does not need to be drawn until after the circuit is working properly. PROTO-BOARD designing is very much like careful single-sided printed circuit design in terms of the effects of parasitics and in terms of operation at high frequency or low levels. Well planned grounds and judicious use of shielded cable can permit operation through VHF frequencies. So, you old solderers, stop soldering on! Send off for our FREE 40 page catalogue; we have a PROTO-BOARD to fit any size budget.

**PROTO BOARDS**

Models PB 203, PB 203A and PB 203AK offer a large breadboarding area and a built in regulated power supply housed in a rugged metal cabinet. Models PB6 to PB105 offer various breadboarding areas screw mounted onto sturdy back plates with non slip non scratch vinyl feet. Red and black binding posts are included: the red being electrically insulated from the back plate, the black being electrically connected for ground.

**PB 203**

Includes 5VDC 1 amp power supply, available at binding posts, two binding posts (V1 V2) remain uncommitted. The perfect board for TTL and other 5 volt logic designs.

**PB 203A**

Every development engineer should have one of these - includes 5VDC 1 amp power supply. Also includes separate 5.5 to 18 VDC and 5.5 to 18 VDC power supplies, each capable of supplying 500 mA at 15 VDC. Power supplies are factory preset to 15 VDC but can be independently adjusted.

**PB 203AK**

Identical to PB 203A but in kit form.

**PB 6**

A kit form breadboard with 4 binding posts, 630 contact points and includes non slip rubber feet.

**PB 100**

Another kit form breadboard with 760 contact points.

**PB 101**

A robust laboratory breadboard accepts up to 10 IC's. 940 contact points.

**PB 102**

A fully assembled breadboard with 1240 contact points.

**PB 103**

With 2250 contact points this board is perfect for prototyping and custom circuit applications.

**PB 104**

A total IC capacity of 32 with 3060 contact points makes this the ultimate electronics development engineers breadboard.

**PB 105**

The newest Proto-board: 4800 contact points, 48 IC capacity!

**24 HOUR SERVICE FROM GSC**

Call (0799) 21682 with your Access, American Express, Barclaycard number and your order will be put in the post immediately.

MODEL NO.	NO OF SOLDERLESS TIE POINTS	IC CAPACITY (114 µm DIP's)	UNIT PRICE	INC P&P 15% VAT	QTY REQUIRED
PB6	630	8	9.75	12.28	
PB100	760	10	12.50	15.52	
PB101	940	10	17.90	22.31	
PB102	1240	12	24.95	30.41	
PB103	2250	24	39.00	46.57	
PB104	3060	32	49.00	58.07	
PB105	4800	48	71.00	83.95	
PB203	2280	24	61.00	72.95	
PB203A	2250	24	89.00	104.65	
PB203AK	2250	24	71.00	83.95	

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE P.O. FOR £ \_\_\_\_\_

DEBIT MY CREDIT CARD NO \_\_\_\_\_

EXPIRY DATE \_\_\_\_\_

PLEASE SEND FREE CATALOGUE


TICK

GLOBAL SPECIALTIES CORPORATION Global Specialties Corporation (UK) Ltd.  
Dept 40  
Unit 1  
Shire Hill Industrial Estate  
SAFFRON WALDEN  
Essex  
CB11 3AQ

Goods despatched within 48 hrs.

Global Specialties Corporation, Shire Hill Industrial Estate,  
Saffron Walden, Essex, CB11 3AQ.

# A.C. MAINS EXPLAINED

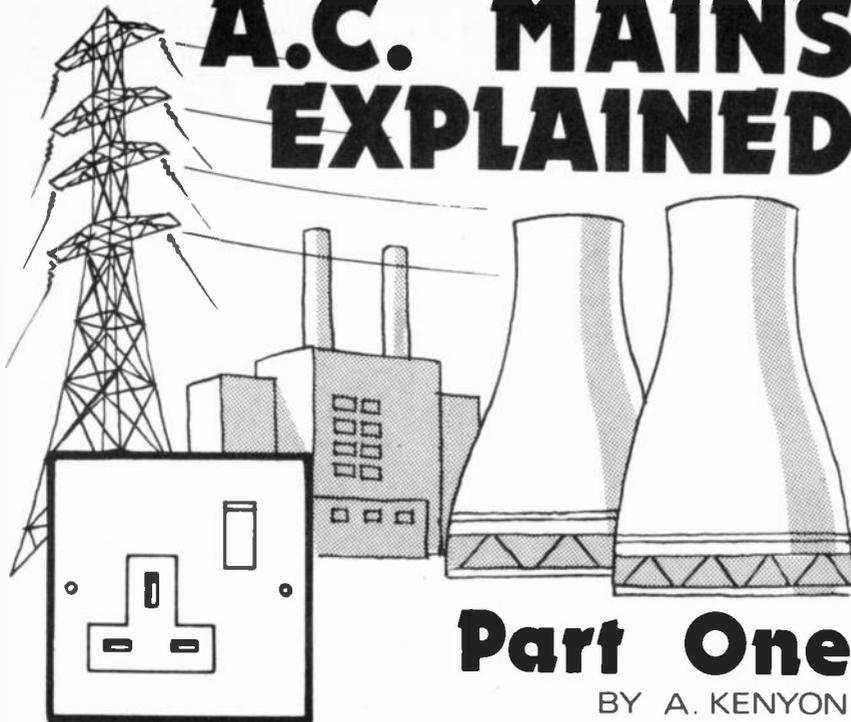

## Part One

BY A. KENYON

THE STANDARD method of transmitting and distributing electrical energy throughout the world is by Alternating Currents (a.c.), so called because the generated voltage is in the form of a sine wave and being a continuous wave, it has a frequency. The mains frequency used throughout the UK is 50 cycles per second or hertz (Hz) and in other countries is usually either 50 or 60Hz.

How therefore can the voltage of a sinusoidal wave which varies between zero and some peak value be classified? This can be achieved precisely because the a.c. voltage is *always* sinusoidal.

### DETERMINATION OF AN A.C. VOLTAGE

If a 12 volt, 24 watt lamp is first connected across a car battery and then across the output terminals of a suitable 12 volt transformer, it will be seen that the lamp lights with the same brilliance even though the

former voltage source is d.c. and the latter, a.c. So what are the characteristics of the sine wave which will give the same power output as a direct voltage? The easiest way to investigate this, is to compare each voltage on a Cathode Ray Oscilloscope (c.r.o.).

Set the time base frequency to measure 50Hz (5ms per division) and connect the battery to the c.r.o. input terminals noting the 12 volt calibration height (see Fig. 1.1a). Next observe the 12 volt a.c. waveform from the transformer output (with the lamp still across it) and note the detail of the voltage sine wave which is equivalent to the 12 volts d.c. (See Fig. 1.1b).

Upon examination it can be seen that this sine wave oscillates between a maximum of 16.97 volts positive and 16.97 volts negative in order to produce a voltage equivalent to 12 volts d.c. (The fact that the voltage goes negative during one

half cycle does not matter since reversing the lamp across the battery terminals gives the same brilliance).

The ratio of the peak a.c. voltage to the equivalent d.c., is equal to:

$$\frac{16.97}{12} = 1.414$$

and this is a constant for all sinusoidal waveforms.

It is also true that:

$$\frac{\text{peak voltage}}{1.414} = \text{equivalent d.c. voltage}$$

This equivalent is known as the r.m.s. value (Root Mean Square) of the a.c. voltage. All voltage referred to on an a.c. network are the voltages in terms of their r.m.s. value (their equivalent d.c. value).

For instance, the 240V single phase output from a domestic mains socket varies sinusoidally between plus and minus 339V (240V  $\times$  1.414) at a frequency of 50Hz.

### MEASUREMENT OF A.C. CURRENT

An inspection of Fig. 1.1b shows that at any instant, the a.c. voltage is either zero, positive or negative and if this voltage is applied to a resistance (for example, the filament of the 12V lamp) the resulting current ( $I$ ) will vary in accordance with Ohm's law,  $I = V/R$ .

It follows therefore that the current will also be a sine wave and its equivalent d.c. (r.m.s.) value will be:

$$I_{r.m.s.} = \frac{V_{r.m.s.}}{R}$$

From the power taken by the lamp we know that the current will be the power in watts divided by the voltage which equals  $24W \div 12V = 2A$ , and that this is the r.m.s. current. The peak current taken from the transformer will therefore be  $2 \times 1.414 = 2.828A$ .

As with the voltage, all currents referred to on an a.c. network are given in terms of their r.m.s. value. This is sometimes referred to as the "Virtual Value", that is the value of the a.c. waveform which is *virtually equivalent* to a d.c. voltage or current of the same value.

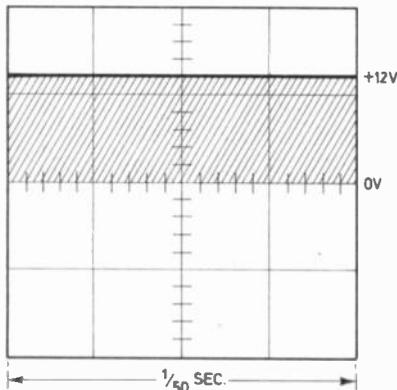


Fig. 1.1a. C.R.O. display for the 12 volts d.c.

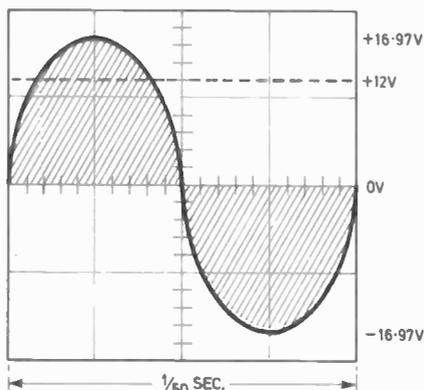


Fig. 1.1b. C.R.O. display for the 12 volts a.c.

### SINGLE PHASE AND THREE PHASE SUPPLY SYSTEMS

Generators of a.c. voltages are known as Alternators and the best way to understand the generation of a three phase system is to first examine how a single phase voltage is produced and to avoid confusion, a single conductor rotating in a magnetic field will be considered.

Referring to Fig. 1.2, the conductor (shown here looking "end on") is rotated in a uniform magnetic field created between the two poles of a permanent magnet.

If the conductor moves across the magnetic field in one direction as

shown (from point A to point C), a voltage is generated between the ends of the conductor. When the conductor moves back across the same magnetic field in the opposite direction (from point C back to point A), the polarity of the induced voltage is reversed. When the conductor moves parallel to the path of the magnetic field in either direction (at A or C), no voltage is generated in the conductor.

Three things now determine the amplitude of the generated voltage.

1. The speed at which the conductor moves across the magnetic field.
2. The strength of the magnetic field.
3. The length of the conductor.

Assume now the ends of the conductor to be connected to two slip rings (see Fig. 1.3) with carbon brushes connected to the input of an oscilloscope. The speed of rotation of the conductor is now set to fifty revolutions per second (3,000 r.p.m.) and the strength of the magnetic field adjusted to generate a peak voltage of 339·41V alternating from positive to negative between the slip rings. This is a standard 240V r.m.s. supply.

Now connect one slip ring to an Earth point; this will be the Neutral. This slip ring will always be at Earth potential while the other slip ring will alternate from 339V above earth potential to 339V below.

This slip ring is the Live terminal and the generated supply will be the same as the single phase 240V supply of Live and Neutral as supplied to domestic premises. Fig. 1.3 also shows how the output voltage sine wave that would appear on an oscilloscope, the frequency being 50Hz.

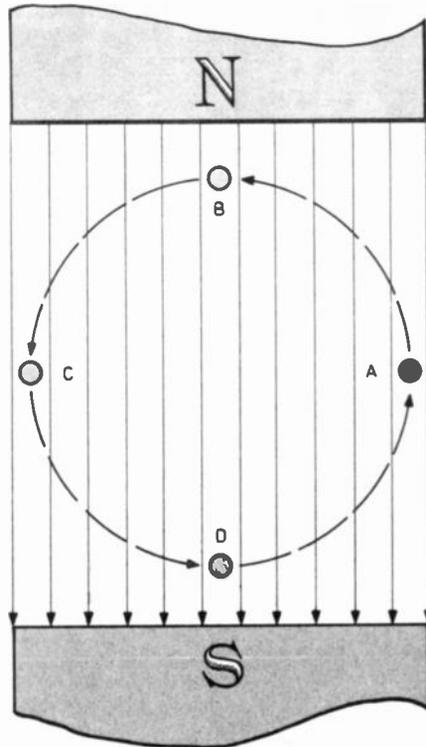


Fig. 1.2. Simple a.c. alternator. Magnetic field shown as parallel lines.

### THREE PHASE A.C. SUPPLIES

A Three Phase supply differs from the single phase system in that three voltages, each equal to the single phase supply, are simultaneously generated within the same magnetic field. (See Fig. 1.4).

This is similar to that shown in Fig. 1.3 but instead of having only one conductor rotating in the magnetic field, there are three, equally separated by 120 degrees. Each conductor will generate 240V at 50Hz as before but their respective peaks will occur

### QUESTION TIME

- 1.1. The single phase Line to Neutral voltage of a three phase system measures 115 volts. What is the three phase Line voltage?
- 1.2. A three phase transmission system is 33,000 volts. What is the peak voltage of any Line conductor to Earth?
- 1.3. Examine Fig. 1.3. Can you suggest any way in which the voltage could be increased two-fold whilst keeping the same magnetic field strength and the same frequency?

at 1/150 of a second intervals.

The three commoned ends of the slip rings are joined to one of the slip rings as shown. This slip ring will be permanently at Earth potential, and again called the Neutral while the three other slip rings will each have a separate 240Vr.m.s. voltages alternating above and below Earth potential. The resulting output waveforms are also shown in Fig. 1.4.

The voltage from any slip-ring to neutral is referred to as the single to neutral is referred to as the single phase voltage and the voltage across any two of the three live slip rings is referred to as the three phase Line voltage, that is, between rings one and two, two and three or one and three.

It can be shown that the Line voltage or the voltage between any two of the live slip rings on the three phase power system is  $\sqrt{3}$  times greater than the single phase Live to Neutral voltage. Now as  $\sqrt{3}$  (the square root of three) is approximately equal to 1.73, we can say that for a distribution system of 240V, the three phase voltage is  $240V \times 1.73 = 415V$ .

To be continued

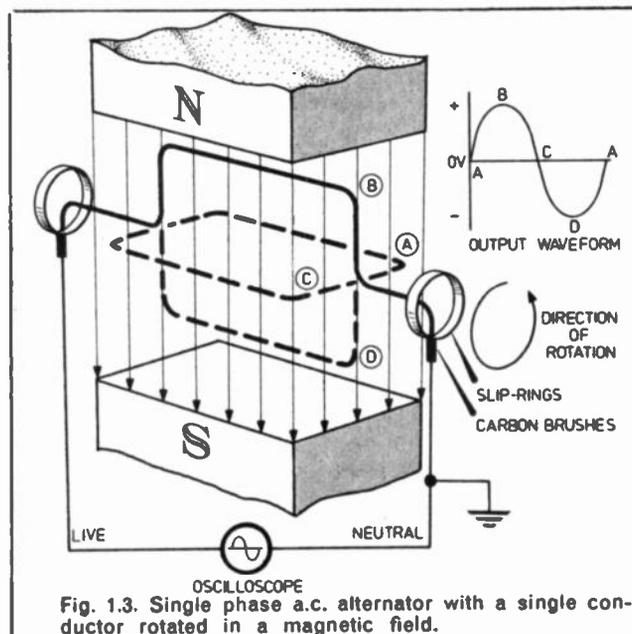


Fig. 1.3. Single phase a.c. alternator with a single conductor rotated in a magnetic field.

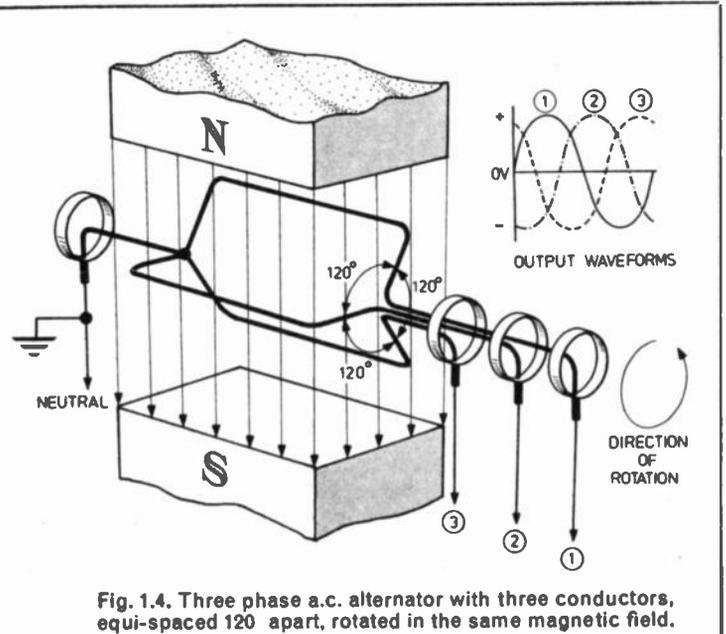


Fig. 1.4. Three phase a.c. alternator with three conductors, equi-spaced 120° apart, rotated in the same magnetic field.

# SQUARE one FOR BEGINNERS

**T**HIS month's subject deals with tools for the construction of electronics projects. Having the proper tools for the job certainly makes work a lot easier and will in general result in a better made project.

As with most things in life you get what you pay for—and tools are no exception. Quality tools cost more (obviously) but in the long term will be more cost effective than a number of lower grade (cheap?) tools.

## SOLDERING IRON

Virtually all projects involve soldering so a soldering iron is essential and should be at the top of your list. The majority of EE projects can be comfortably assembled with the aid of a 15 to 20W iron fitted with a 1.5mm diameter bit. A larger bit size could also be in stock for bigger jobs, for example, soldering to large tags on potentiometers, transformers and the like. An iron clad bit will last longer.

Choose a mains powered iron unless you have a specific reason for choosing a lower voltage type. The lower voltage types can be used with the mains via a suitable transformer which will provide isolation. Hooks are fitted to most irons for hanging purposes during use, but a stand is much better and safer.

## WIRE CUTTERS

Wire cutters are necessary for trimming component leads to the required length, either before or after soldering, and for cutting interconnecting wire to length. The latter may be cut using a pen-knife, but cutters are preferred. The two sections of the cutter can either be (a) lap-jointed, where the sections are laid one on the other and rivetted together to pivot at this point, (b) box-jointed, where the two sections are machined to inter-lock about a machined pivot. The latter will provide longer service.

Cutting edges can be obtained with and without a bevel, the latter providing a very close cut. Other variations are size, for light, medium and

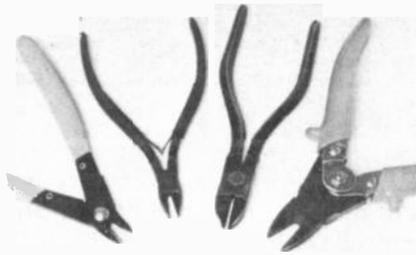


Fig. 1. A selection of wire cutters (these are also referred to as side cutters). The pair on the left are lap-jointed, the others all being the box-jointed type, the heavy duty pair in fact having two joints for extra leverage.

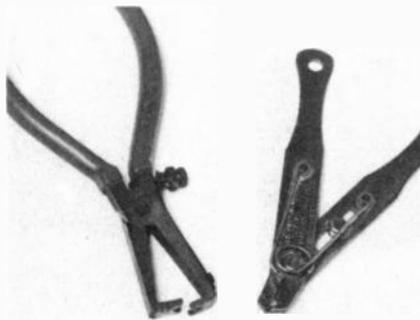


Fig. 2. Wire strippers. The pair on the left are of superior quality but as such, can be considerably more expensive. Both types are adjustable for different size wires.

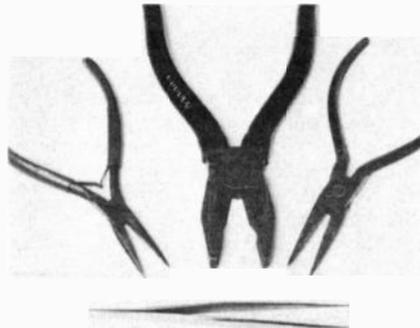


Fig. 3. A range of pliers with the electrician's pliers in the centre, flanked by two pairs of long-nosed pliers. A pair of fine tweezers are also shown.

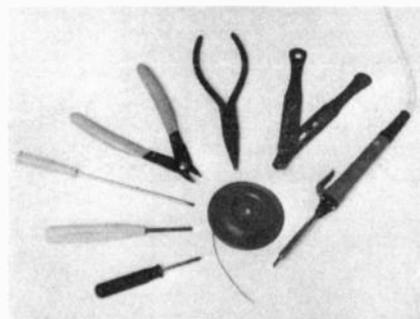


Fig. 4. The basic tool kit with, clockwise left to right, small cross-head screwdriver, spot-face cutter, small plain screwdriver, wirecutters, long-nosed pliers, wire strippers, mains soldering iron and in the centre, a reel of solder.

heavy duty use, and with and without spring loaded handles, see Fig. 1.

Lightweight sprung handle cutters without bevel have been found most useful in the workshop. Heavier cables could be cut with a pen-knife.

## WIRE STRIPPERS

Wire strippers are needed for removing the insulation from wire. Basically, there are two versions as shown in Fig. 2. Both shown are adjustable and spring loaded. The adjustment does allow the strippers to be also used as cutters.

There is quite a difference in the cost of these two versions and we have found that the cheaper type in (b) to still function well after several years of use. Cable strippers can also be bought, but their expense is not justified for hobbyist use.

## PLIERS

A selection of different pliers are seen in Fig. 3 and one or more different pairs will be regularly required during construction. The pair shown top centre in Fig. 3 are known as electrician's pliers which are also usually equipped with a centre cutter for heavy cables and wire, and a side-slot-cutter for heavy wire gauges. The jaws are serrated for gripping purposes, useful for holding nuts/bolts.

The smaller pairs of pliers are long-nose pliers. These will be useful for bending component leads and linking wires, as heatshunts, picking up and placing components on boards; tweezers are useful for the latter.

## SCREWDRIVERS

A small selection of screwdrivers are an essential part of any electronics toolkit. You can buy inexpensive screwdriver sets, conveniently packed in a plastics case with two or three different sized heads of different sizes which are satisfactory for the hobbyist.

The kits we have in mind are for general purpose use and also contain a pointed blade and a threaded blade, for making holes in wood.

## STRIPBOARD

Stripboard is rarely obtained in the size you require for a particular project and so has to be cut. A Junior hacksaw is ideal. A smooth file is required to clean up the edge and remove any jagged copper track ends that could possibly produce shorting bridges between the tracks.

To make breaks at positions along the tracks, a drill bit about 3mm diameter makes a clean cut but is a little difficult and soon tires the hand especially if there are a large number of breaks to be made. There is a tool called a "spotface cutter" made specially for this purpose and is recommended.



# makes soldering easy fast & reliable

## Ersin Multicore

Ersin Multicore, solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required. Comes in handy dispensers and tool box reels in two different alloys 40/60 tin/lead for general purpose electrical soldering and 60/40 tin/lead ideal for small components and fine wire soldering.



Size PC115 60/40 tin/lead  
£1.38 Handy pack 0.02mm dia



Size 3 40/60 tin/lead  
£4.37 Per reel 1.6mm dia  
Size 10 60/40 tin/lead  
£4.37 Per reel 0.71mm dia



Size 19A 60/40 tin/lead  
£1.15 Handy pack 1.22mm dia

## Multicore Savbit

Multicore Savbit, solder increases the life of your soldering bit by 10 times, for better soldering efficiency and economy. Comes in two handy dispensers and tool box reels.



Size 5 Savbit  
£1.15 Per pack 1.2mm dia



Size 12 Savbit  
£4.37 Per reel 1.2mm dia



Size SV130 Savbit  
£1.73 Per pack 0.048mm dia

## Multicore Alu-Sol

Multicore Alu-Sol, solder contains 4 cores of flux, suitable for most metals especially aluminium. Comes in handy dispensers on tool box reels.

Size AL150 Alu-Sol  
£2.07 Per pack 0.048mm dia



Size 4 Alu-Sol  
£7.82 Per reel 1.6mm dia



## Multicore Solder Wick

Multicore Solder Wick, absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds.

Size AB10 Solder Wick  
£1.43 Per pack



## Multicore Tip Klean

Multicore Tip Klean, soldering iron tip wiping pad. Replaces wet sponges.



Size 2 Tip Klean  
£0.92 Per pack

## Bib Wire strippers and cutters

Wire strippers and cutters, with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.



Size 9 Wire Strippers  
£2.69 Per pair

All prices inclusive of VAT. Available from most electrical and DIYs stores. If you have difficulty in obtaining any of these products send direct with 50p for postage and packing. For free colour brochure send S.A.E.

**Bib Audio/Video Products Limited**  
(Solder Division), Kelsey House,  
Wood Lane End, Hemel Hempstead,  
Hertfordshire, HP2 4RQ.  
Telephone: (0442) 61291  
Telex: 826437

# NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW


## STACKABLE LEDs

A new design of rectangular l.e.d. has recently been introduced by Zaerix Electronics enabling end or side stacking.

Available in red, yellow or green, the L-251 series couple the advantage of full area illumination with the facility of producing continuous unbroken lines in the end stackable direction, enabling a wide range of bar type displays to be generated.

Having a maximum power dissipation figure of 105mW, the l.e.d.s have a typical luminous intensity figures of up to 2.8mcd at 20mA.

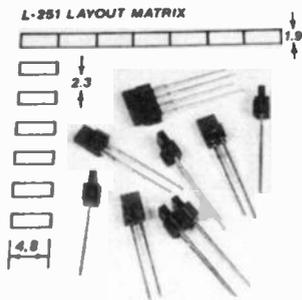Zaerix Electronics Ltd,  
Dept EE, Electron House,  
Cray Avenue, St Mary  
Cray Orpington, Kent  
BR5 3QJ.



## HIGH RESOLUTION

Owners of VHS and Beta format video machines will welcome the new video cassette tapes from the renowned Bib range of audio and video products.

This new top grade, high resolution tape, specially made for Bib in Japan, is claimed to provide the most realistic colour quality current technology can offer.

The E180(VHS) and L750 (Beta) Bib video cassettes should be available from most video shops and stores. The recommended retail price for the tapes is £9.98.

Bib Audio/Video Products Ltd, Dept EE,  
Kelsey House, Wood  
Lane End, Hemel Hempstead, Herts HP2 4QR.



## DIGITAL MULTIMETER

Introduced to meet the market demand for a portable digital multimeter for the "field" service engineer, Salford Electrical Instruments pocket meter incorporates two design features.

The input terminals are at the top, enabling the operator to probe the circuit under test whilst holding the instrument in one hand. The 3½ digit LCD display is at the base, and is sloped for easier reading.

The meter covers a resistance range of 0 to 20M $\Omega$ , with diode test facility, and a voltage range of 0 to 1kV (max) d.c. and 0 to 750V (max) a.c. Current range is 0 to 2A, both a.c. and d.c., which is protected by a 2A fuse. Short duration transient protection is included and will withstand 250V r.m.s. fed into any input, on



any range indefinitely.

The SEI D1000 Digital Multimeter is powered by a PP3 battery and comes complete with case and probes.

Salford Electrical Instruments Ltd, Dept EE,  
Barton Lane, Eccles,  
Manchester, M30 0HL.

## WORLD FIRST

For the princely sum of £2,500 plus VAT (someone must pay for development) you can own the world's first truly portable, flat-screen, liquid crystal display, digital storage oscilloscope. And it's British.

Claimed to be the first of its type in the world, the Scopex Voyager oscilloscope uses a flat-screen liquid crystal display in place of the conventional cathode ray tube. It has thus proved possible to have a portable, battery operated, digital storage scope with a front-to-back depth of less than 100mm and weighing only 2.5kg.

This unique instrument was the result of work undertaken by British Scientists at the Royal Signals and Radar Establishment, Malvern, Dr. Ian Shanks together with Paul Holland who were responsible for the method which is used in addressing 32,000 odd points which comprise the display.

Incorporated in the instrument is a function called "save memory" which maintains the information stored in a RAM device even when the instrument is switched off, enabling waveforms to be held for future reference. When switched on again the trace stored is shown as clearly as when first recorded. Comparison of signals sequentially coming from the same or different sources, and by use of the compare and store functions in the dual-trace mode, single and dual-trace storage over



the entire screen area is possible.

Another feature which comes out of the digital storage method employed is the ability to have a pre-trigger function. This effectively enables the user to look back in time to see what occurred before the event which triggered off the recording. This ability to look back can be made to give various amounts of pre-trigger information and is exceedingly useful in detecting random and occasional faults.

The digital storage system is controlled by six slide switches together with an indicator display which shows the mode of operation.

Other brief technical details are as follows. Vertical Systems — Bandwidth: d.c. coupled, d.c. to 150kHz at 8 samples per cycle; a.c. coupled, 3Hz to 150kHz at 8 samples per cycle. Sensitivity: 10mV/cm to 5V/cm in 9 calibrated ranges. Accuracy is claimed to be  $\pm 1.5$  per cent. Risettime: 800ns single trace; 1.6 $\mu$ s dual-trace or compare. Maximum input voltage: 250V (d.c. +pk a.c.). Input impedance:

1M $\Omega$   $\pm 3$  per cent and 22pF.

Horizontal system—Timebase sweep speeds: 20 $\mu$ s/cm to 50s/cm in 20 calibrated ranges. External input: 1.25MHz maximum, no lower limit; +4.75V  $\pm$  0.25V. Minimum pulse width 100ns. Accuracy is claimed to be 0.01 per cent internal; External; determined by external timebase source.

The trigger sensitivity internal: 2mV d.c.-150kHz; External: 100mV d.c.-150kHz. Sample rate is 1.25MHz. The flag display indicates aliasing, low battery, store saved, store, triggered and armed.

The internal battery supply consists of 6 nickel cadmium rechargeable cells which give upto 5 hours continuous use. The low battery indicator operates approximately 15 minutes before the display drive safety circuits finally cut out.


The Scopex Voyager with its low voltage display and operation enables it to be used in many semi-hazardous environments where oscilloscopes have been banned.

Scopex Instruments Ltd,  
Dept EE, Pixmore House,  
Pixmore Avenue, Letchworth, Herts SG6 1HZ.

**FREE** OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

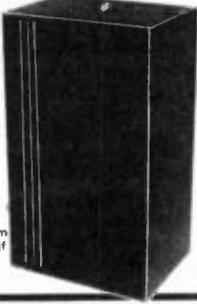**SUPER HI-FI SPEAKER CABINETS**

Made for an expensive Hi-Fi outfit — will suit any decor. Resonance free. Cut-outs for 6 1/2" woofer and 2 1/2" tweeter. The front material is Dacron. The completed unit is most pleasing. Supplied in pairs, price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.00 the pair.



**GOODMANS SPEAKERS**

6 1/2" 8 ohm 25 watt £4.50. 2 1/2" 8 ohm tweeter. £2.50. No extra for postage if ordered with cabinets. Xover £1.50.

**THIS MONTH'S SNIP**


**0 - 100 MICRO AMP PANEL METER**

Japanese made, flush mounting, size approximately 45mm x 50mm x 30mm deep. PRICE £2.95.




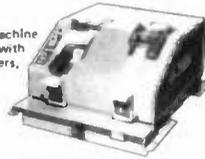**TAPE PUNCH & READER**

For controlling machine tools, etc, motorised 8 bit punch with matching tape reader. Ex-computers, believed in good working order, any not so would be exchanged. £17.50 pair. Post £4.00.



**3 CHANNEL SOUND TO LIGHT KIT**

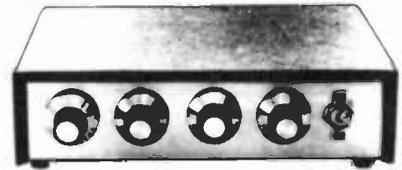

Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

**EXTRACTOR FAN**

Mains operated — ex-computer  
5" Woods extractor £5.75, Post £1.25.  
5" Plannair extractor £6.50, Post £1.25  
4" x 4" Muffin 115w. £4.50, Post 75p.  
4" x 4" Muffin 230v. £5.75, Post 75p.




**MILLIONS OF HOMES WILL BE BURGLED THIS SUMMER — SAY THE EXPERTS**

Don't let yours be one of them. Install our burglar alarm. Install our burglar alarm. Complete kit includes 6" external alarm bell, mains power unit, control box with key switch, 10 window/door switches, 100 yards of wire. With instructions £29.50.

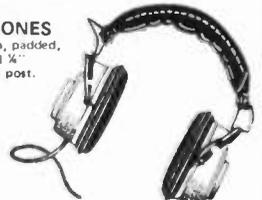**STEREO HEADPHONES**

Very good quality, 8 ohm, padded, terminating with standard 1/4" jack plug. £2.99 plus 60p post.



**TIME SWITCH BARGAIN**  
Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs **FOR ONLY £2.50.**

**POPULAR KITS**

**3 — 30v VARIABLE VOLTAGE POWER SUPPLY UNIT**

With 1 amp DC output, for use on the bench, students, inventors, service engineers, etc. Automatic short circuit and overload protection. In case with a volt meter on the front panel. Complete kit £13.80.

**MORSE TRAINER**

Complete kit for only £2.99.

**DRILL SPEED CONTROLLER**

Complete kit for £3.95.

**MAINS POWER SUPPLY**

Gives any voltage from 3V to 16V at up to 300mA. Complete kit less case £1.95. Case available at 90p.

**IONISER KIT**

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — complete mains operated kit, case included £11.95 plus £2.00 post.

**CAR STARTER/CHARGER KIT**

This kit has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on a shelf in the garage, whichever suits you best. Price: **ONLY £12.50 + £3.00 post.**

**8 POWERFUL BATTERY MOTORS**

For models, macanons, drills, remote control planes, boats, etc. £2.95.

**DELAY SWITCH**

Mains operated — delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps — second contact opens a few minutes after the 1st. £1.95.

**ZX81 OWNERS**

Make yourself a full size keyboard! Key switches complete with plain caps. 6 for £1.15.



**UNIVAC KEYBOARD BARGAIN**

50 keys together with 5 miniature toggle switches all mounted on a p.c.b. together with 12 i.c.'s many transistors and other parts. £13.50 + £2.00 post. This is far less than the value of the switches alone. Diagram of this keyboard is available separately for £1.



**AMAZING VALUE!**

**SOLENOID WITH PLUNGER**

Mains operated £1.99. 10 - 12 volts DC operated £1.50.

**STANDARD RELAYS**

3 changeover 10 amp contacts, single screw fixing, mains operated. £1.25. 12 volt operated £1.50. 6 volt model 99p. Other coil voltages — please enquire.

**ULTRA SMALL 12v RELAYS**

Single pole gold plated contacts. Tubular construction, 17mm long 10mm dia. Ideal for models. PCB or freemounting. £2.30 ea.


**MINIATURE PLUG IN RELAYS**

12v operated, 3 changeover. £2.45 base 45p.  
12v operated, 2 changeover. £1.87, base 35p.

**TINIEST MICROPHONE**

Not much bigger than a pea, 600 ohm condenser type. Ideal for bugging and similar applications. 50p each or 10 for £4.50

**LEVEL METER**

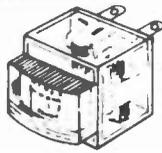

Size approximately 1 1/2" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200uA. 75p.

**RESISTORS**

Carbon film, 1/4 or 1/3 watt, standard leads, not pre-formed, all 5% values: 1p each 100's, 2p each 10, 5p each less than 10 per value. DR — INVENTOR'S PACK Containing 10 of each of 60 different values from 1 ohm to 10 meg-ohm, packed separately, £5.75.

**12 VOLT FLUORESCENT LIGHTING**

For camping — car repairing — emergency lighting from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical.

We offer an inverter for 21" 13 watt miniature fluorescent tube, **ONLY £3.45.** (tube not supplied).




**AMAZING VALUE!**

**ELECTRIC MOTORS!**

**MOTORS FOR ROBOTICS**

If it's a toy robot you are making then one of our eight battery motors (see centre column) may do. If it's a bigger one, however, then see below. If still not big enough then enquire, we have larger motors but these are usually mains driven.

**12v MOTOR BY SMITHS**

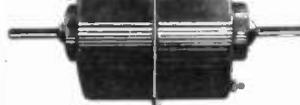

Made for use in cars, these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. These have a good length of 1/4" spindle — price £3.45. Ditto, but double ended £4.25.

**EXTRA POWERFUL 12v MOTOR**

Made to work battery lawnmower, this probably develops up to 1/2 h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. £6.90 + £1.50 post. [This is easily reversible with our reversible switch — Price £1.15].

**SPIT MOTORS**



These are powerful mains operated induction motors with gear box attached. The final shaft is a 1/2" rod with square hole, so you have alternative coupling methods — final speed is approx. 5 revs/min, price £5.50. — Similar motors with final speeds of 80, 100, 160 & 200 r.p.m. same price.

**REVERSIBLE MOTOR WITH CONTROL GEAR**

Made by the famous Framco Company this is a very robust motor, size approximately 7 1/2" long, 3 1/2" dia. 3/8" shaft. Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:  
- 1 Framco motor with gear box. - 1 manual reversing and on/off switch. - 1 push to start switch. - 1 x 100w auto transformer. - 2 limit stop switches. - 1 circuit diag. of connections. **£19.50 plus postage £2.50.**

**ROTARY WAFER SWITCHES**

5 amp silver plated contacts. 1/2" shaft. 1" dia. wafer.  
Single wafer types, 29p each, as follows:  
1 pole 12 way 2 pole 6 way 3 pole 4 way 4 pole 3 way 6 pole 2 way  
Two wafer type, 59p each, as follows:  
2 pole 12 way 4 pole 6 way 4 pole 6 way 12 pole 2 way 6 pole 2 way 8 pole 3 way  
3 wafer types 99p each, as follows:  
3 pole 12 way 6 pole 6 way 6 pole 6 way 12p 3 way 9 pole 4 way 6 pole 6 way 18p 2 way

**TRANSMITTER SURVEILLANCE**

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox — all electronic parts and circuit. £2.30. (not licencible in the U.K.)

**RADIO MIKE**

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 comp. kit. (not licencible in the U.K.)

**FM RECEIVER**

Made up and working, complete with scale and pointer needs only headphones, ideal for use with our surveillance transmitter or radio mike. £5.85. or kit of parts £3.95.

**SPECIAL OFFER!**

**Chance of a lifetime!**

We have to clear a big store. 100 tons of stock must go. 10 kilo parcel of unused parts. Minimum 1,000 items includes panel meters, timers, thermal trips, relays, switches, motors, drills, fuses and dies, tools, thermostats, coils, variable condensers, variable resistors, etc. etc. Individually these must cost in excess of £100.

**YOURS FOR ONLY £11.50 plus £3.00 post.**

**MINI-MULTI TESTER**

Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures:  
DC volts 10, 50, 250, 1000.  
AC volts 10, 50, 250, 1000.  
DC amps 0 — 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test leads and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

**FREE** Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

**J. BULL (Electrical) Ltd.**

(Dept. EE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3OU. **Established 50 YEARS**


MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £10, add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclaycard orders please Haywards Heath (0444) 454563. Bulk Orders: Write for quote. Delivery by return.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite


BRANDLEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM

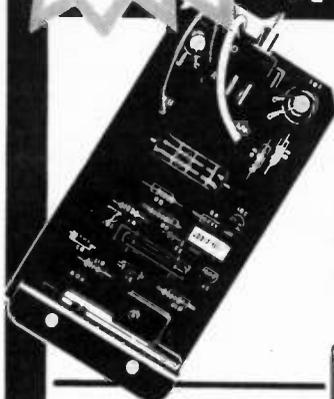
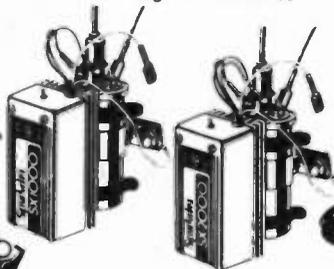
## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles






## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles
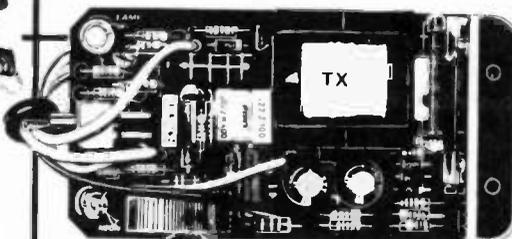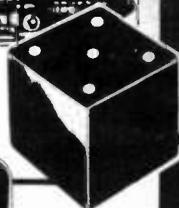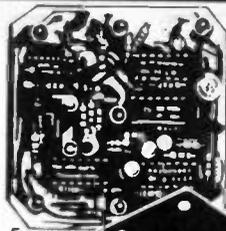
## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble





## TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble


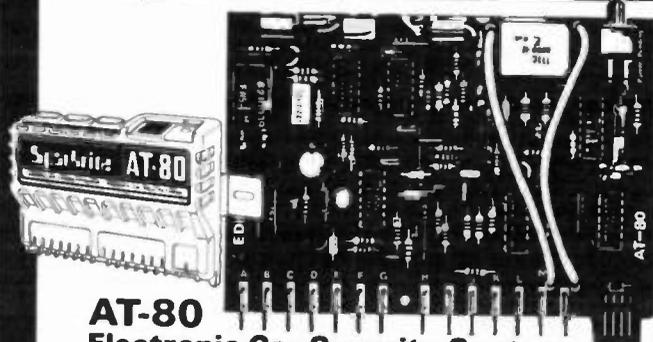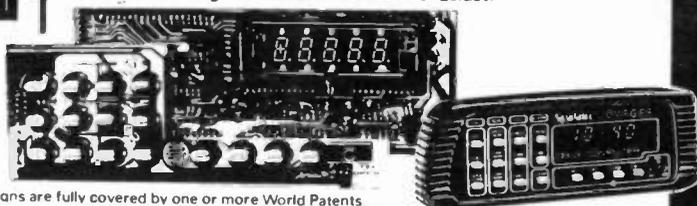
## VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble. A real challenge for the electronics enthusiast!



## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

All EDA SPARKRITE products and designs are fully covered by one or more World Patents

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

Please allow 28 days for delivery

NAME \_\_\_\_\_ EE 7 82  
ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF. \_\_\_\_\_

CHEQUE NO. \_\_\_\_\_  
24hr. Answerphone  
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD  
SEND ONLY SAE IF BROCHURE IS REQUIRED


	SELF ASSEM. KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

Everyday Electronics, July 1982

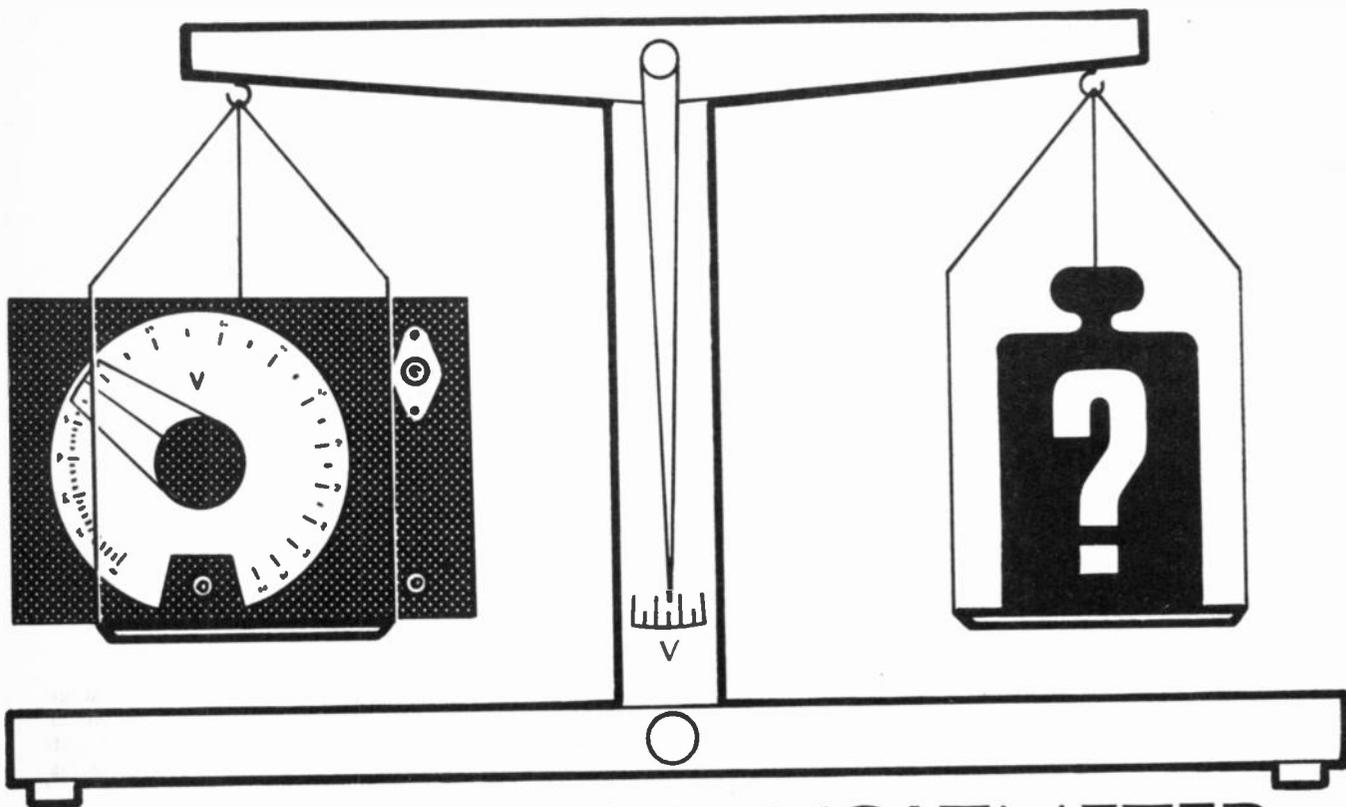

# COMPARATOR VOLTMETER

By N. P. Naughton

**M**ANY a precariously positioned multimeter has come to an expensive end in numerous garages and, indeed, workshops. The simple electronic voltmeter described here has no delicate meter movement to damage. It extends a technique widely used in the computerised testing of semiconductors.

An ordinary testmeter operates magnetically to indicate the value of an unknown voltage. But the same measurement can be made by comparing the unknown voltage with a known reference voltage. This reference voltage is varied by means of a

potentiometer until it coincides with the unknown voltage so when the test probe is applied to the unknown voltage, a pointer knob on the potentiometer is turned until an l.e.d. goes out to indicate coincidence. The voltage can then be read off from a calibrated scale. This is the principle of the comparator voltmeter.

Although this single range meter was originally meant for testing in fairly high current circuits, it has also been used for checking out low voltage circuits such as TTL. But the meter has a low input impedance and therefore loads a circuit somewhat more than a conventional type and the readings in such cases may be inaccurate. However, they will be accurate enough for most purposes.

## CIRCUIT DESCRIPTION

Three silicon *npn* transistors are employed in the complete circuit shown in Fig. 1. Zener diode D1, TR1 and R4 form an emitter follower voltage regulator which develops a stabilised voltage across potentiometer VR1 in such a way that any selected voltage at the slider is always negative with respect to point A. The probe input is always positive with respect to this point.


Whenever a negative voltage at VR1 slider coincides in value with a positive voltage at the probe, the voltage at point B will be equal to that at A. Transistor TR2 detects this "null" condition by turning on when it occurs. It does so because its base becomes 0.6 volts negative relative to its emitter when the null occurs. This voltage derives from an offset voltage developed across preset VR2 which acts as the SET ZERO control of the meter.

When TR2 turns on, TR3 turns off since TR2 collector voltage is now too low to allow TR3 to conduct. The NULL INDICATOR l.e.d., D2, therefore goes out when coincidence occurs.

## HALF WAVE

A single diode is used to provide half wave rectification of the 18 volts a.c. from the mains transformer, T1. This simplifies construction and assists Zener regulation by avoiding the voltage drop of two diodes which would happen with a full wave bridge. In fact, a small voltage drop does occur at VR1 slider when TR2 turns on, but since this discrepancy is constant throughout it is absorbed in calibration.

Electrolytic capacitor C1 provides smoothing and D3, a green l.e.d., provides POWER ON indication.

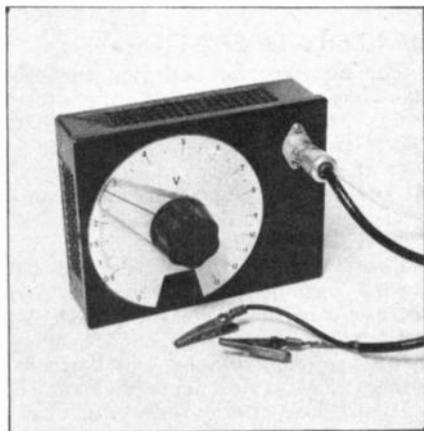

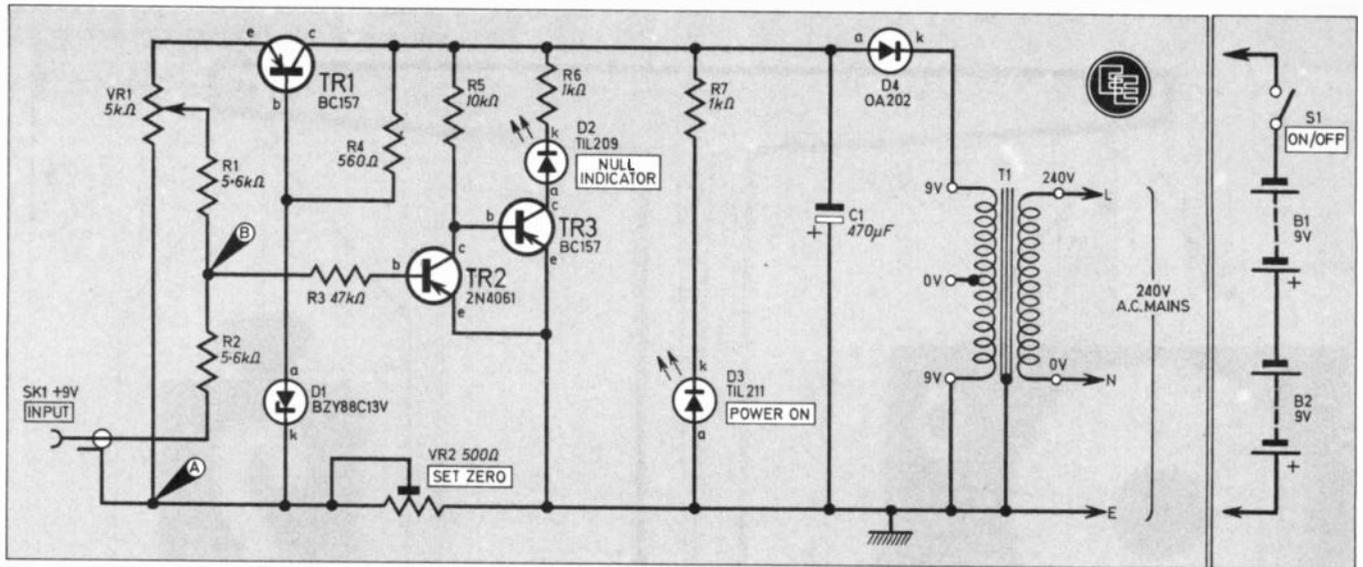


Fig. 1. Circuit diagram for the Comparator Voltmeter



## CIRCUIT BOARD

Most of the components are assembled on 0.1 inch matrix strip-board 28 holes by 17 strips and the layout is shown in Fig. 2. Ensure that the transistors, capacitor and diodes are correctly orientated before soldering and that foil breaks are made exactly as shown. Insert the resistors and links, made from component lead off-cuts, into the board and solder in position. VR2 should be accessible from the top.

Many constructors assemble strip-boards as instructed but have their own ideas regarding boxing and finish. However, for this particular project, the following points should be noted. It is strongly recommended that the box selected be a metal one, as this will act as a heat sink for the transformer which, in most cases, will be a miniature, warm running type. The case used in the prototype was an AB10 aluminium box 101×103×38mm, and finished with a black crackle paint. It is essential that the box be well ventilated so drill plenty of small holes in the sides, otherwise it will become something of an oven and the calibration may drift.

## FINAL ASSEMBLY

The circuit board is mounted in the base of the case on spacers as shown in Fig. 3. T1 is also secured to

the case alongside the board and on one of its mounting screws is placed a 3-way tag strip to accommodate the main input wires.

The mains cable enters through a grommet and is firmly held in place with a "P" clip. The EARTH wire (yellow/green) is soldered to the earth point on the tag strip, the live and neutral wires must be soldered to isolated tags.

The case lid holds VR1, l.e.d.s D2 and D3, and the probe socket, SK1 a u.h.f. coaxial connector, and these are mounted in the positions shown.

All interwiring is done with the p.v.c. sleeved 7/0.2 wire, Fig. 3.

A suitably drilled and scribed Perspex strip glued to the bottom of the knob makes an excellent pointer. If this is made 50mm long, effective scale length will be about 250mm.

## CALIBRATION

Before setting up the meter for the calibration procedure, a disc of paper no greater than 100mm in diameter must be temporarily stuck to the box lid, its centre on that of the potentiometer, VR1. It is on this that the calibration marks can be made with a sharp pencil. The suggested graduations are the zero point, 0.5 to 2V in 0.1V steps, up to 3V in 0.2V increments, from 3 to 10V in steps of half a volt and finally up to the maximum of 13V in 1V steps. Less than 0.5V was not thought to be necessary and, since the meter is not intended as a precision instrument, no more calibration marks are needed.

The zero control is best set with the test probe or clip floating. Simply turn VR1 to minimum and then carefully adjust SET ZERO potentiometer, VR2 until the NULL INDICATOR, D2, just lights up. The pointer now marks 0 volts.

A variable voltage source and an accurate conventional voltmeter are necessary for calibration. The variable source could be a pair of 9 volt batteries wired across a low resistance potentiometer, however, a variable power supply would be ideal.

With the calibration voltage source correctly connected to the probe, set the voltage to the first point, that is 0.5V, and rotate VR1 from the zero position in a clockwise direction. When l.e.d. D2 goes out, mark the position of the pointer on the scale with the sharp pencil. Return VR1 to the zero position and set the calibration voltage to the next value.

It will be noticed that when rotating VR1 back again the l.e.d. comes on again at a lower point on the scale. This Schmitt trigger effect is due to altered circuit conditions occurring the instant TR2 conducts.

The scale markings will be semi-logarithmic but the long scale length compensates for some crowding at the higher voltage end. The completed instrument should read from about 0.5 volts to just over 12 volts.

## BATTERY OPERATION

The high cost of batteries and the relatively low cost of miniature mains transformers make mains operation the obvious choice, however if battery operation is desired, T1 and D4 will be deleted, and in the interest of low power consumption remove D3 and R7.

Two 9 volt PP3 batteries will be needed and it will, of course, be necessary to fit an ON/OFF switch as indicated in Fig. 1. When the measured voltage differs significantly from a known reference, for example, a 1½ volt cell, the batteries will need to be replaced. □

# COMPARATOR VOLTMETER

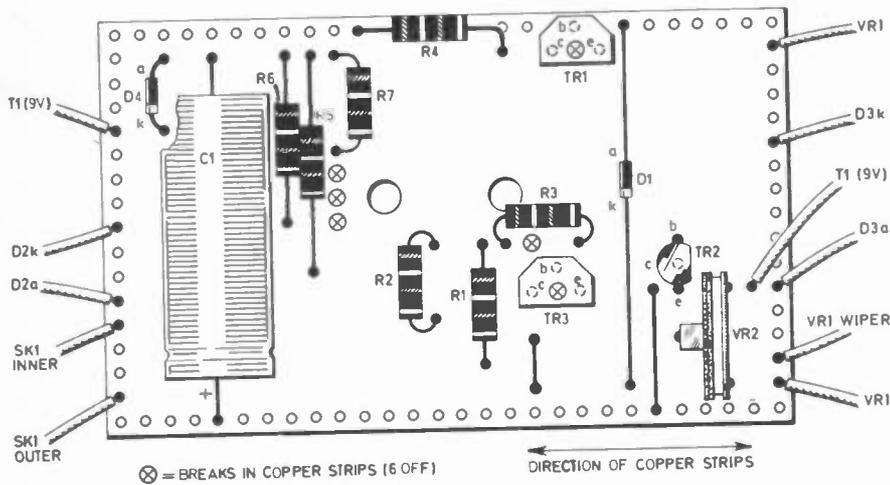


Fig. 2. Stripboard layout for the Comparator Voltmeter. Note the positions of the six track breaks.

## COMPONENTS

### Resistors

- R1, 2 5.6k $\Omega$  (2 off)
- R3 47k $\Omega$
- R4 560 $\Omega$
- R5 10k $\Omega$
- R6, 7 1k $\Omega$  (2 off)
- All  $\frac{1}{4}$ W carbon  $\pm 5\%$

See  
**Shop  
Talk**  
page 455

### Capacitors

- C1 470 $\mu$ F 25V electrolytic

### Semiconductors

- D1 BZY88 13V, 400mW Zener diode
- D2 TIL209 red l.e.d.
- D3 TIL211 green l.e.d.
- D4 OA202 general purpose silicon
- TR1, 3 BC157 silicon pnp (2 off)
- TR2 2N4061 silicon pnp

### Miscellaneous

- VR1 5k $\Omega$  lin w/w control potentiometer
  - VR2 500 $\Omega$  lin carbon vertical preset
  - T1 Miniature mains transformer, 9V-0-9V, 100mA secondary
  - SK1 Co-axial socket, surface mounting
  - PL1 Co-axial free plug
- Stripboard, 0.1 inch matrix, 17 strips by 28 holes; aluminium case 101 x 133 x 38mm (type AB10); 3-way tag strip with earth point; grommet; P-clip; l.e.d. mounting clips (2 off); control knob with long pointer; mains plug; crocodile clips (2 off); 7/0.2 equipment wire; mains lead (approx 2m); screened co-ax cable (approx 1m); mounting hardware for T1 and circuit board (M2.5 or 6BA).

Approx. cost **£8.70**  
Guidance only



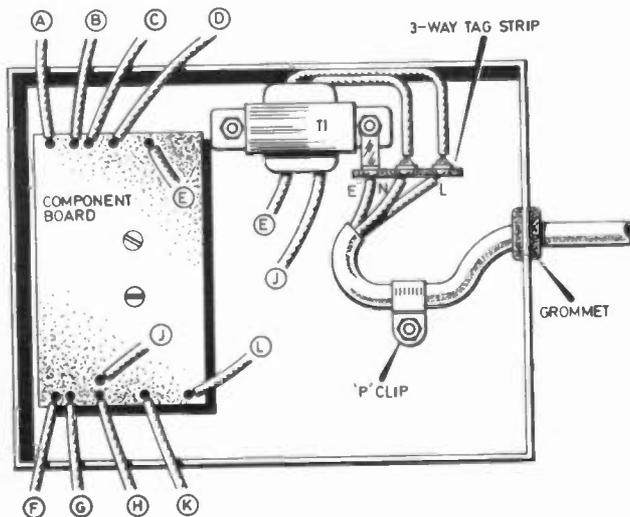
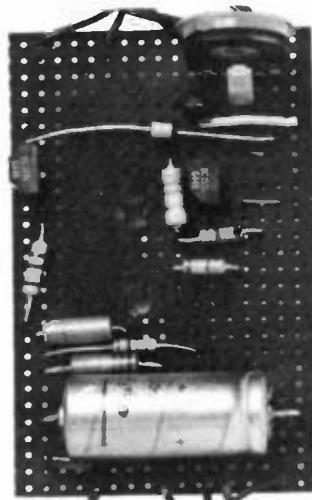


Fig. 3. Wiring diagram showing view inside case. Transformer and case must be earthed via the earth point on the tag strip.

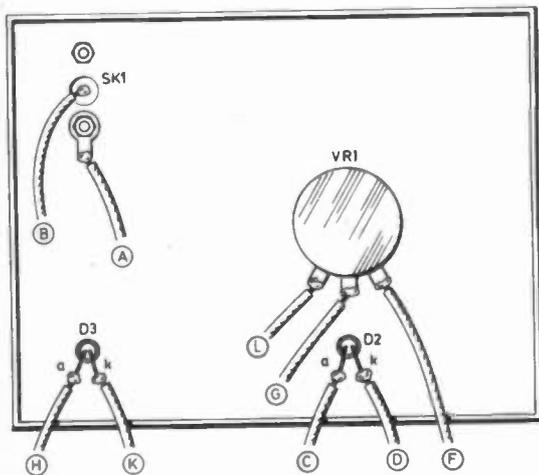

View inside the finished prototype unit. Note that the mains cable "p" clip is not shown, however it is important that it is included.

# REFLEX

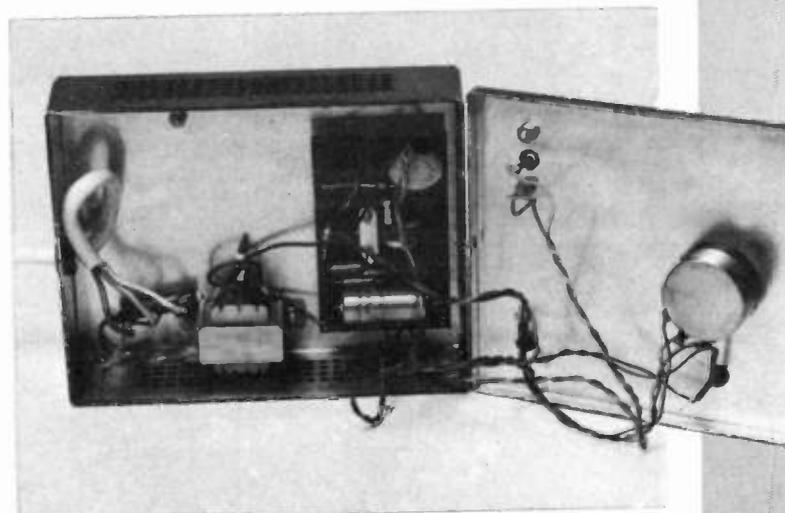

# TESTER

by D. J. EDWARDS

So you think you've got fast reactions? Would you really have been the fastest gun in the West? The speed at which people react to a stimulus is dependent on many factors. Age is one—as neurons die and nerve pathways deteriorate, the speed of impulse is delayed.

It is of course well known that alcohol affects reaction adversely.

Can you make up a composite definition of someone with good reactions? Will a tall person have slower reactions than a small person? Does it depend on fitness? All in all a reaction tester can be fun to have around.

## CIRCUIT DESCRIPTION

The circuit diagram is shown in

Fig. 1 and can be seen to be a good example of classic transistor action. It consists of two bistables (one for each contender) and the time variable "trigger" around TR5 and TR6 that gives the signal for the players to trip their respective switches.

Let us first look at the bistable around TR1 and TR2, bearing in mind its action is identical to the one comprising TR3 and TR4.

In the normal un-triggered state TR2 is off, therefore its collector is high and D1 is also off. The high voltage at TR2 collector is coupled to TR1 base via the potential divider of R2 and R3, keeping TR1 on. TR1 collector is therefore low and this is coupled back to the base of TR2 via R7 keeping TR2 off.


If a pulse is now applied to the base of TR2 by depressing S2, TR2 goes on. Its collector goes low, D1 lights up. The voltage at the junction of R2 and R3 is now insufficient to keep TR1 on, so its collector goes high. This is again fed back to TR2 base via R7, keeping TR2 on even if S2 was only operated for an instant. Because TR2 collector is now low there is insufficient current for the other player to trigger his bistable by pressing his switch, S1.

This description applies equally well for either bistable and ensures that the first player to hit his switch in response to the signal automatically cuts out his opponent.

Let us now turn our attention to the circuitry that initiates this action.

Initially C1 is uncharged and TR5 base is at 0V. TR5 is thus off, which

Fig. 1. Complete circuit diagram of the Reflex Tester.

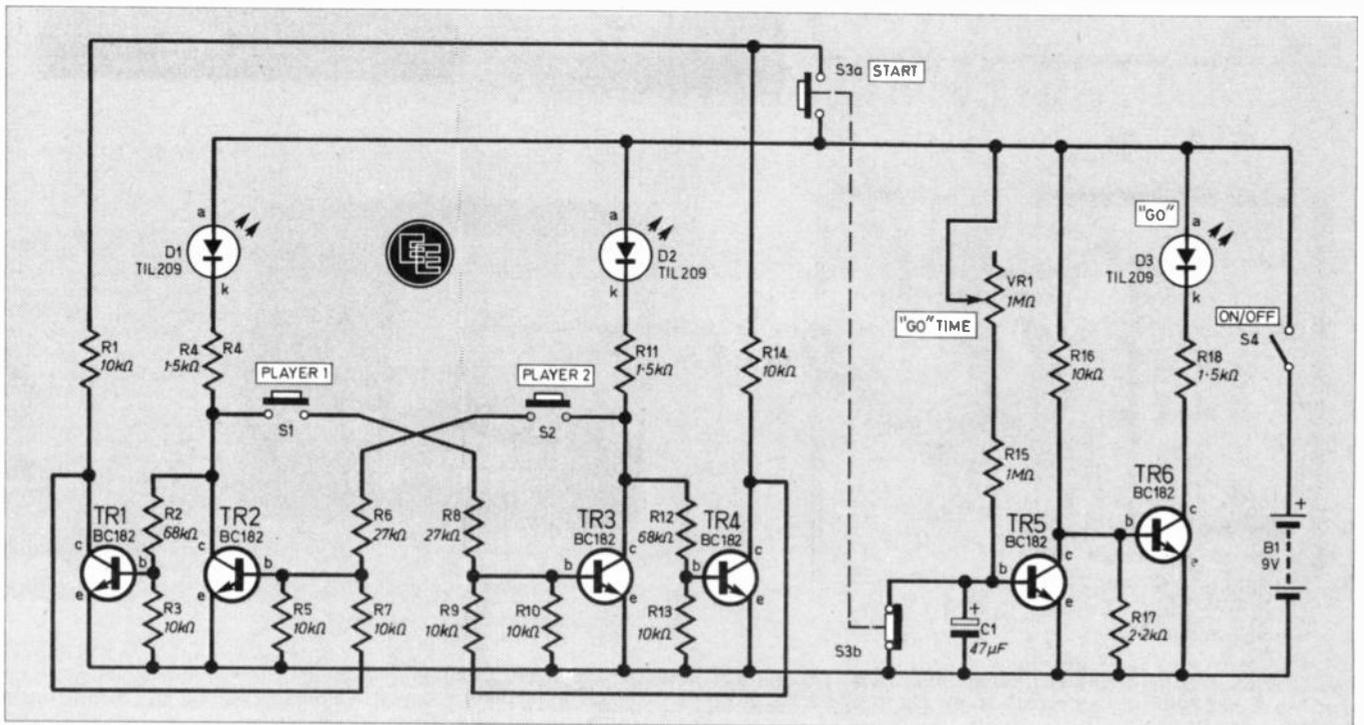

keeps TR6 on and D3 alight. As C1 slowly charges up via VR1 and R15, the voltage at TR5 base gradually rises. When it reaches approximately 0.6V TR5 switches on. TR5 collector goes low, TR6 goes off and D3 is extinguished. The time it takes for this process to be executed can be varied by VR1.

## BOARD ASSEMBLY

All the components with the exception of the switches, the l.e.d.s, and the potentiometer, are mounted on a piece of 0.1 inch matrix stripboard size 24 strips by 12 holes. The layout of the circuit board is shown in Fig. 2 together with details for the breaks to be made in the copper strips.

Leave the inclusion of the transistors until last. There are a number of flying leads which should be attached to the board at this stage. Notably the four leads to D1 and S2 should emerge from the copper side of the board that is to be soldered directly to their appropriate track positions without being passed through a hole on the board topside.

## CASE

There is not a great deal of room in the case specified, but there is sufficient if care is taken, and a compact, convenient unit is the result. The case used measured 120x66x40mm with internal slots for vertical board mounting hardware. This negates the need for mounting hardware.

Drilling details for the l.e.d.s and

switches are given in Fig. 3. The arrangement, however, is quite simple. D3 is situated in the centre of the panel with the on/off switch (S4) and reset button (S3) positioned either side. S1 and S2 are placed as near to their respective ends of the panel as possible.

The fixing centres of D1 and S2 are equidistant from the horizontal axis of the panel, as are D2 and S1. VR1 is mounted in the centre of a long side. The battery and the circuit board are placed either side of the centrally mounted switches and l.e.d.

## IN USE

When the unit is first switched on, all l.e.d.s should light. After a short period D3 will go out (the time this takes being dependent on the position of VR1) as C1 charges to 0.6V. If S3, the reset switch, is now briefly depressed D1 and D2 will be extinguished and D3 will light again. The unit is in the "play" state where the aim is to "hit" your switch first when D3 goes out.

VR1 is included in the circuit to add some unpredictability as to when D3 goes out, so that "veterans" cannot anticipate this. As such VR1 should have an unmarked knob and should preferably be twiddled between bouts by a third person.

Some people are also better on a short delay than a long one, and vice versa. But after saying this, remember that it's not to be taken too seriously and all results should be treated with a healthy amount of conjecture! ☺

# COMPONENTS

## Resistors

R1 10kΩ	R10 10kΩ
R2 68kΩ	R11 1.5kΩ
R3 10kΩ	R12 68kΩ
R4 1.5kΩ	R13 10kΩ
R5 10kΩ	R14 10kΩ
R6 27kΩ	R15 1MΩ
R7 10kΩ	R16 10kΩ
R8 27kΩ	R17 2.2kΩ
R9 10kΩ	R18 1.5kΩ

All ½W carbon ±5%

## Capacitor

C1 47µF 10V elect.

## Semiconductors

TR1-TR6 BC108 npn silicon (6 off)	See Shop Talk page 455
D1-D3 TIL220 0.2 inch red l.e.d. (3 off)	

## Miscellaneous

VR1 1MΩ linear carbon potentiometer
B1 9V type PP3
S1, S2 s.p.s.t. normally open momentary action push switch (2 off)
S3 d.p.d.t. momentary action push switch
S4 s.p.s.t. slide switch
Stripboard: 0.1 inch matrix size 24 strips by 12 holes; battery connector; plastic case, size 120 x 66 x 40mm (ABS 2004); control knob—no markings; fixing clips for l.e.d.s (3 sets).

Approx. cost £4.75  
Guidance only

See Shop Talk page 455

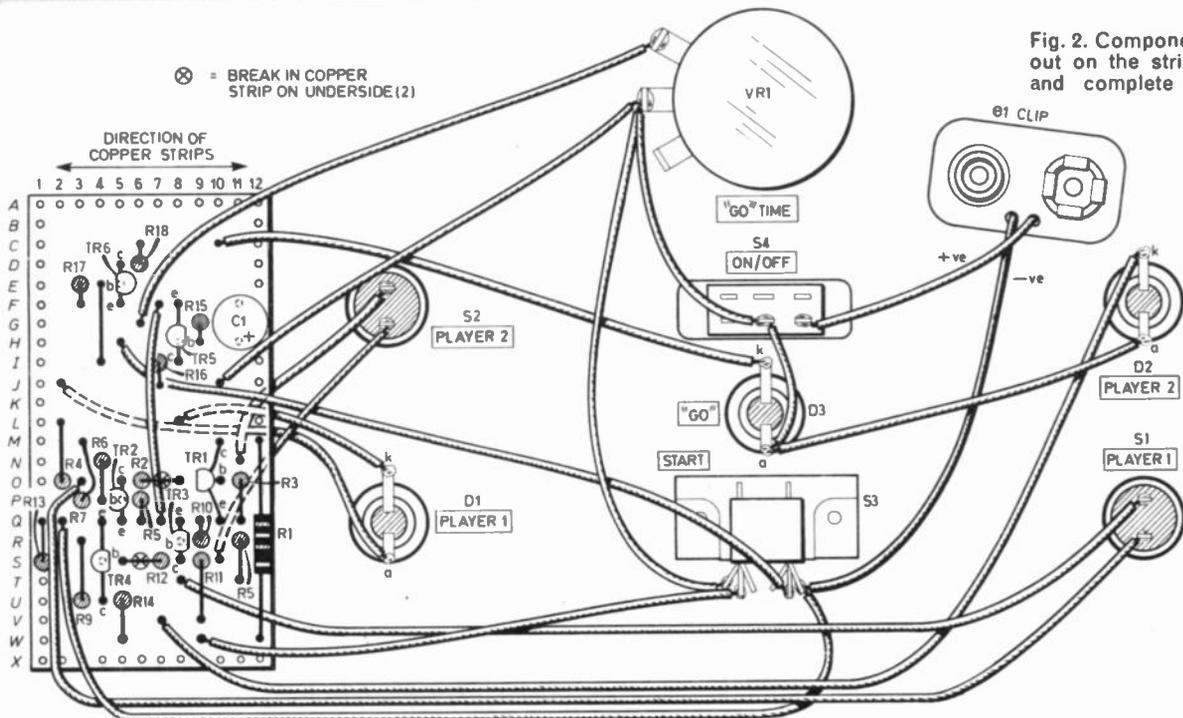


Fig. 2. Component layout on the stripboard and complete wiring.

# Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!


Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

## Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

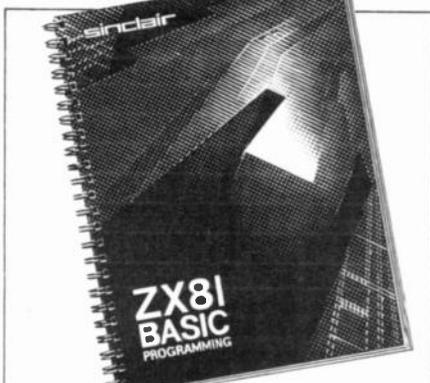And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



**New BASIC manual**

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs

## Kit: £49.<sup>95</sup>

### Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

### New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



## Built: £69.<sup>95</sup>

### Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 700 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



uter-



## Available now- the ZX Printer for only £59.<sup>95</sup>

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha- numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings – particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer – using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

## 16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software – the Business & Household management systems for example.

### How to order your ZX81

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST – use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (700 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	29.95	
	Sinclair ZX Printer.	27	59.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £ \_\_\_\_\_

\*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ \_\_\_\_\_

\*Please charge to my Access/Barclaycard/Trustcard account no. \_\_\_\_\_

\*Please delete/complete as applicable

Please print.

Name: Mr/Mrs/Miss \_\_\_\_\_

Address: \_\_\_\_\_

FREEPOST – no stamp needed. Offer applies to UK only.

EVE07

# sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: (0276) 66104 & 21282.


Everyday Electronics, July 1982

# CIRCUIT EXCHANGE

This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised.

Payment is made for all circuits published in this feature.

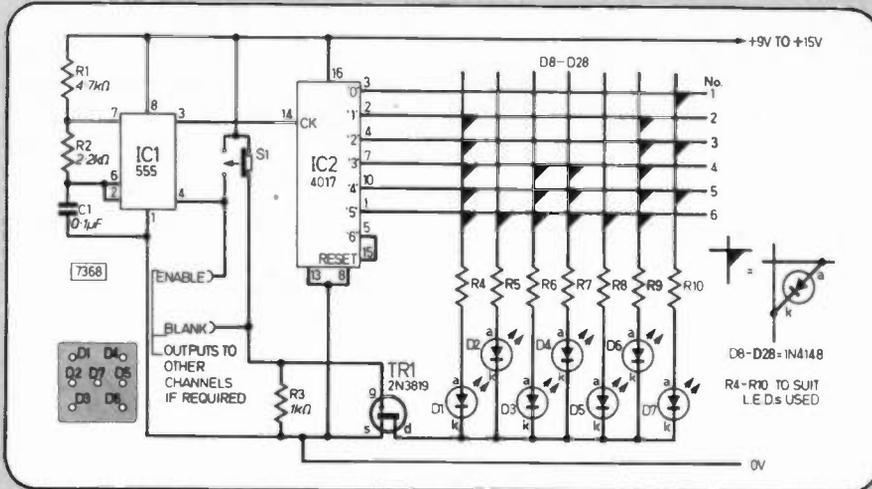Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.



## ELECTRONIC DIE

I enclose the circuit diagram of an Electronic Die which I have designed.

The display consists of seven l.e.d.s arranged in an "H" formation. These are connected to the outputs of IC2, a 4017 decade counter, via a diode matrix which ensures that only the l.e.d.s wanted are lit.


When S1 is pressed resistor R3 pulls the gate of TR1 negative, thus turning it off and blanking the display. It also enables the 555 oscillator IC1 which clocks IC2 at a fre-

quency of about 10kHz with the values shown.

When S1 is released it disables the oscillator and turns on TR1, allowing the display to light at a number dependant on which output of IC2 is high. Due to the high frequency used the output is virtually a random number. The diode matrix can be changed to suit the display wanted.

The circuit can be modified so that two or more die operate in "parallel", each having a different clock rate.

G. Foote,  
Woodford Green,  
Essex.

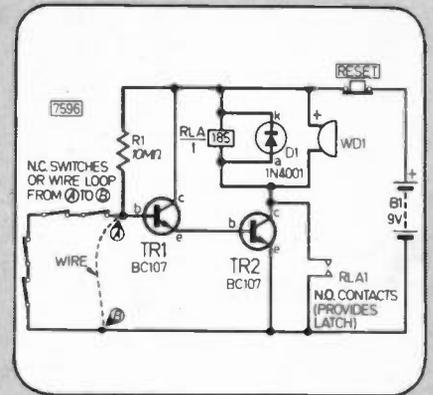


## BURGLAR ALARM

I enclose a circuit of an ultra-low quiescent current burglar alarm. I cannot read the current on my 500μA f.s.d. meter. The current, I estimate at 0.5μA. In use, my unit consumes 70mA, though it depends on the alarm device and RLA.

The alarm is designed for a closed loop alarm system; when the loop is broken the alarm sounds. This has obvious applications as a bike alarm; a wire being run through the spokes, which if broken or unplugged from unit sounds the alarm. Far cheaper than even the EE Bike Alarm.

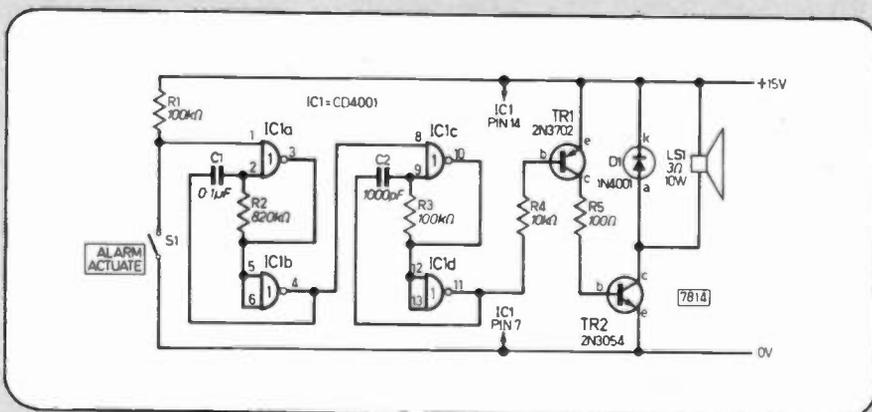Brian S. Craigie,  
Edinburgh,  
Scotland



## SIMPLE SOUND GENERATOR

I have just finished reading a book on simple sound generator circuits. I came to the conclusion that there was not an alarm generator that produced more than 2W output. I set about improving a design and have come up with this alarm which gives a full 10W from a 15V supply. It also has one other feature, the alarm is a pulsed tone alarm which is a more attractive sound than a normal tone generator.

P. Linforth,  
Solihull,  
W. Midlands

# Explore the Excellence of your ZX81

With MEMOTECH Add-Ons  
High Resolution Graphics



## Unique 3 month trade-in offer!

For your future needs, we'll allow you £10 against your purchase of our 64K model if:

- you return your 16K pack within 3 months of receipt;
- you supply evidence of purchase;
- your 16K model is received by us undamaged and unopened.\*

\*We reserve the right to reject, for discounting purposes, units which have been either opened or damaged in any way.

MEMOTECH  
ADD-ON  
£52.00  
plus  
VAT

- Fully programmable high resolution (192x248 pixels).
- Video page is both memory and bit mapped.
- Video page can be located anywhere in the RAM.
- The number of video pages is limited only by your RAM size (each page occupies about 6.5K RAM) and pages can overlap.
- Instant inverse video.
- Switching inverse video on and off gives flashing characters/numerals etc.
- Access to video page is similar to plot and unplot commands in BASIC.

- Video pages can be superimposed by software switching.

The pack comes in an elegant aluminium case, anodised black and styled to fit onto the back of the ZX81, allowing more add-ons (Memopak RAM, Sinclair printer, etc) to be connected without a further power supply. It contains a 2K EPROM monitor, holding a full range of graphics subroutines which can be called by the BASIC USR function or by machine code.

MEMOTECH  
ADD-ON  
£26.00  
plus  
VAT



## Memopak 16K Memory Extension

It is a fact that the ZX81 has revolutionised home computing and coupled with the new Memopak 16K it gives you a massive 16K of Directly Addressable RAM, which is neither switched nor paged. With the addition of the Memopak 16K your ZX81's enlarged memory capacity will enable it to execute longer and more sophisticated programs, and to hold an extended database.

The 16K and 64K Memopaks come in attractive custom-designed and engineered cases which fit snugly on to the back of the ZX81 giving firm, wobble-free connections.

MEMOTECH  
ADD-ON  
£68.70  
plus  
VAT



## Memopak 64K Memory Extension

The 64K Memopak is a pack which extends the memory of the ZX81 by a further 56K, and together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts BASIC commands such as 10 DIM A(9000).

### BREAKDOWN OF MEMORY AREAS

0-8K . . . Sinclair ROM 8-16K . . . This section of memory switches in or out in 4K blocks to leave space for memory mapping, holds its contents during cassette loads, allows communication between programmes, and can be used to run assembly language routines. 16-32K . . . This area can be used for BASIC programmes and assembly language routines. 32-64K . . . 32K of RAM memory for BASIC variables and large arrays. With the Memopak 64K extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

## Coming Soon...

MEMOPAK RAM  
HI-RES GRAPHICS  
CENTRONICS IF



A complete range of ZX81 plug-in peripherals  
Centronics Interface & Software Drivers  
Digitising Tablet RS232 Interface

We regret we are as yet unable to accept orders or enquiries concerning the above products, but we'll let you know as soon as they become available.

© R. Branton & G.A.C. Boyd 1982

Access Barclaycard Holders  
Please Tel. Oxford  
(0865) 722102  
(24 Hrs)

Please make  
cheques payable to  
MEMOTECH Ltd.

Please Debit my  
Access/Barclaycard  
account number

Please send me

16K RAM @ £26.00 + £3.90 VAT  
64K RAM @ £68.69 + £10.31 VAT  
HRG @ £52.00 + £7.80 VAT

Price No Total

£29.90		
£79.00		
£59.80		

Packaging & Postage @ £2.00 per unit

TOTAL ENC

\*Please delete whichever does not apply

SIGNATURE \_\_\_\_\_ DATE \_\_\_\_\_  
NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_  
TELEPHONE \_\_\_\_\_

We want to be sure you are satisfied with your Memopak - so we offer a 14-day money back Guarantee on all our products.  
Memotech Limited, 3 Collins Street, Oxford OX4 1XL, England Tel: Oxford (0865) 722102 Telex: 837220 Orchid G

# ENFIELD ELECTRONICS

## SPECIAL MONTHLY OFFER No. 1

Hand held Micro Cassette Tape Recorder. Compact and handy, this memory device records at two speeds providing up to one hour of recording. Comes complete with mini cassette, earphone and carrying pouch.



ONLY  
£20.70  
+ 50p p&p

## SPECIAL MONTHLY OFFER No. 2

Illustrated is one of a wide range of SWR meters in stock. Other examples are:—  
Model 171, only £16.95  
SWR/50A—just £12.95



ONLY  
£8.95  
+ 50p p&p

## BELOW IS JUST A SHORT LIST OF OUR TRANSISTORS, 74 SERIES & C MOS 4000 SERIES

TRANSISTORS				74 SERIES				C MOS 4000 SERIES					
AC107 27	BC137 32	BC212B 10	BCY71 15	BD233 45	7400 20	7480 80	7163 90	4000 22	4069 30	4000 22	4070 30	4000 22	4071 30
AC122 27	BC138 32	BC213 10	BCY72 15	BD234 45	7401 20	7481 175	7164 100	4001 20	4072 30	4001 20	4073 30	4002 22	4074 27
AC125 27	BC139 32	BC213A 10	BCY73 17	BD235 45	7402 20	7482 70	7166 100	4002 22	4075 27	4003 30	4076 25	4003 30	4077 25
AC128 27	BC140 32	BC213B 10	BD108 65	BD237 45	7403 20	7483 68	7167 400	4004 22	4078 30	4004 22	4079 30	4005 30	4079 30
AC127 27	BC141	BC213C 10	BD115 64	BD238 45	7404 20	7484 295	7170 195	4006 30	4080 30	4006 30	4081 30	4007 26	4082 30
AC128 27	BC142 32	BC214 10	BD118 62	BD239 45	7405 20	7485 95	7173 120	4008 36	4083 30	4008 36	4084 30	4009 36	4084 30
AC141 28	BC143 32	BC214B 10	BD121 80	BD240 55	7406 28	7486 28	7174 90	4010 36	4085 30	4010 36	4086 30	4011 24	4086 30
AC142 28	BC147 12	BC214C 10	BD123 240	BD240 55	7407 48	7489 195	7175 80	4012 28	4087 30	4012 28	4088 30	4013 40	4088 30
AC176 28	BC148 12	BC214L 10	BD131 45	BD240A55	7408 20	7490 36	7176 85	4011 24	4089 30	4011 24	4089 30	4012 28	4089 30
AC187 28	BC149 12	BC238B 30	BD132 45	BD241 55	7409 20	7491 75	7177 85	4012 28	4090 30	4012 28	4090 30	4013 40	4090 30
AC188 28	BC153 12	BC238B 30	BD133 45	BD437 47	7410 28	7492 30	7180 90	4013 40	4091 36	4013 40	4091 36	4014 40	4091 36
ACY18 70	BC154 12	BC251 12	BD135 45	BD439C 30	7411 25	7493 50	7181 200	4014 92	4092 36	4014 92	4092 36	4015 98	4092 36
ACY19 70	BC157 12	BC252 12	BD136 45	BD506 55	7412 22	7494 75	7182 200	4015 98	4093 36	4015 98	4093 36	4016 100	4093 36
ACY21 90	BC158 32	BC258B 30	BD137 55	BD519 47	7413 40	7495 65	7184 200	4016 100	4094 36	4016 100	4094 36	4017 100	4094 36
AD130 100	BC159 32	BC301 30	BD138 45	BD520 55	7414 80	7496 85	7185 200	4017 82	4095 36	4017 82	4095 36	4018 100	4095 36
AD143 95	BC161 32	BC303 30	BD139 45	BD589 100	7418 28	7497 80	7188 500	4018 87	4107 115	4018 87	4107 115	4019 61	4107 115
AD140 95	BC167B 32	BC307 30	BD140 45	BD648 100	7417 28	7100 310	7190 100	4019 61	4107 115	4019 61	4107 115	4020 96	4107 115
AD149 105	BC189 12	BC308 30	BD155 55	BD711 48	7420 20	7104 150	7191 100	4020 96	4108 83	4020 96	4108 83	4021 72	4108 83
AD161 50	BC189 12	BC309 10	BD175 75	BD712 48	7425 28	7105 150	7192 95	4021 72	4109 83	4021 72	4109 83	4022 82	4109 83
AD162 50	BC170 12	BC317 10	BD176 52	BF115 28	7426 30	7107 48	7193 100	4022 82	4110 83	4022 82	4110 83	4023 25	4110 83
AF106 50	BC171 12	BC327 10	BD177 87	BF117L 28	7427 25	7109 27	7194 90	4023 25	4111 83	4023 25	4111 83	4024 30	4111 83
AF114 65	BC172 12	BC328 10	BD178 68	BF119 100	7428 54	7110 25	7195 90	4024 30	4112 83	4024 30	4112 83	4025 23	4112 83
AF115 50	BC173 12	BC332 12	BD179 80	BF121 55	7430 20	7111 80	7196 95	4025 23	4113 83	4025 23	4113 83	4026 152	4113 83
AF116 65	BC174 12	BC337 12	BD180 80	BF123 60	7432 28	7116 170	7197 85	4026 152	4114 83	4026 152	4114 83	4027 50	4114 83
AF126 55	BC177 12	BC338 12	BD185 75	BF125 55	7433 36	7118 95	7198 145	4027 50	4115 83	4027 50	4115 83	4028 102	4115 83
AF127 50	BC178 12	BC348L 30	BD186 75	BF127 60	7437 30	7119 340	7199 145	4028 102	4116 83	4028 102	4116 83	4029 140 </td <td>4116 83</td>	4116 83
AF139 52	BC179 12	BC440 40	BD187 75	BF152 32	7438 30	7121 36	7221 200	4029 140	4117 83	4029 140	4117 83	4030 117	4117 83
BC107 12	BC181 12	BC461 30	BD188 75	BF154 15	7440 25	7122 46	7279 95	4030 117	4118 83	4030 117	4118 83	4031 97	4118 83
BC107B 12	BC182L 12	BC477 20	BD189 80	BF153 32	7441 60	7123 60	74284 95	4040 97	4119 83	4040 97	4119 83	4032 115	4119 83
BC107C 12	BC183 10	BC478 20	BD190 80	BF155 50	7442 60	7126 60	74285 95	4041 115	4120 83	4041 115	4120 83	4033 90	4120 83
BC108A 12	BC183A 10	BC479 20	BD195 90	BF156 40	7443 100	7135 50	74386 84	4042 80	4121 83	4042 80	4121 83	4034 90	4121 83
BC108B 12	BC183C 10	BC479 20	BD196 90	BF157 35	7444 100	7141 60	74390 375	4043 90	4122 83	4043 90	4122 83	4035 95	4122 83
BC108C 12	BC184 10	BC527 12	BD197 90	BF158 35	7445 90	7143 550	74393 195	4044 95	4123 83	4044 95	4123 83	4036 95	4123 83
BC109 12	BC184B 10	BC537 12	BD198 95	BF160 35	7447 65	7145 80	75107 120	4045 95	4124 83	4045 95	4124 83	4037 152	4124 83
BC109B 12	BC184C 10	BC547 12	BD200 95	BF162 32	7448 65	7147 125	75110 240	4046 152	4125 83	4046 152	4125 83	4038 112	4125 83
BC109C 12	BC184L 10	BC548 12	BD201 85	BF163 32	7450 25	7148 65	75140 180	4047 112	4126 83	4047 112	4126 83	4039 87	4126 83
BC113 18	BC186 12	BC550 12	BD202 85	BF165 30	7451 25	7150 120	75141 95	4048 80	4127 83	4048 80	4127 83	4040 80	4127 83
BC114 18	BC187 20	BC556 12	BD203 78	BF166 60	7453 50	7151 75	75150 200	4050 47	4128 83	4050 47	4128 83	4041 80	4128 83
BC115 18	BC204 20	BC557 12	BD204 90	BF167 60	7454 25	7153 65	75154 168	4051 80	4129 83	4051 80	4129 83	4042 85	4129 83
BC116 18	BC205 20	BC558 12	BD205 85	BF173 32	7460 25	7154 100	75182 150	4052 85	4130 83	4052 85	4130 83	4043 75	4130 83
BC117 18	BC207 20	BC559 12	BD206 85	BF177 35	7470 32	7155 80	75451 45	4053 75	4131 83	4053 75	4131 83	4044 150	4131 83
BC118 18	BC208 10	BCY30 110	BD207 95	BF178 32	7472 28	7156 80	75452 45	4054 150	4132 83	4054 150	4132 83	4045 135	4132 83
BC129 32	BC209 10	BCY31 120	BD208 95	BF179 32	7473 32	7157 70	75453 45	4055 135	4133 83	4055 135	4133 83	4046 145	4133 83
BC132 32	BC212 10	BCY32 120	BD222 45	BF180 35	7474 30	7180 90	75454 95	4056 145	4134 83	4056 145	4134 83	4047 80	4134 83
BC136 32	BC212A 10	BCY70 15	BD225 45	BF181 35	7475 44	7161 90	75459 110	4057 80	4135 83	4057 80	4135 83	4048 30	4135 83
			BD232 45	BF182 35	7476 35	7162 90	76003 220	4068 30	4136 83	4068 30	4136 83	4049 30	4136 83

WE ARE OPEN 9 AM - 6 PM MONDAY TO SATURDAY

Delivery within 14 days

208 Baker Street · Enfield · Middlesex · 01-366 1873



# ELECTROVALUE

A SPECIAL  
SUMMER  
PROMOTION

FREE VOUCHERS  
TO SAVE YOU UP TO

£2.10



Send for EV Catalogue 82 before Aug. 31 (80 pages A4 - 70p post paid) and we give you THREE 70p REFUND VOUCHERS FREE! Each is valid at any time for spending singly on any one C.W.O. order minimum list value £10 to quickly represent a useful saving for you. Send 70p now for your catalogue and 3 vouchers by return.

+ USUAL DISCOUNTS + FREE POSTAGE

### DISCOUNTS

9% on orders over £23 (inc. V.A.T.)  
18% on orders over £57.50 (inc. V.A.T.) on most catalogue items, but not on payments by credit cards.

### POSTAGE

Not charged on U.K. C.W.O. orders over £5.75 inc. V.A.T. If less, add 40p handling charge.

- \* SEMI-CONDUCTORS/ICs/OPTOs
- \* COMPUTERS/SOFTWARE
- \* CAPACITORS/RESISTANCES
- \* CONNECTORS/SWITCHES/KNOBS
- \* POTS/FERRITES
- \* BOOKS/BOXES/TOOLS

and more and more and more

ELECTROVALUE LTD. 2nd St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB.  
Telephone Egham (STD 0784; London 07) 33683; Telex 264475.  
Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA.  
Telephone 061 432 4045.

## SUMMERTIME SALE !! DEDUCT 20% OFF ALL ORDERS OVER £10

All prices include VAT—just add 50p post

### 1982/3 CATALOGUE

Bigger! Better! Buy one!!!

Only 75p inc. post—Look what you get!!

- Vouchers worth 80p
- 1st class reply paid envelope
- Wholesale list for bulk buyers
- Bargain List with hundreds of surplus lines
- Huge range of components
- Low, low prices

Sent free to schools, colleges etc.

### 'COMPUTER BATTLESHIPS'

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value: SN78477 sound IC; TMS1000 u-processor; batt clips, P's, C's etc. Size 180 x 140mm. Only £1.58. Instruction book and circuit 30p extra.

### 'STARBIRD'

Gives realistic engine sounds and flashing laser blasts—accelerating engine noise when module is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt clip (needs PP3). PCB size 130 x 60mm. Only £2.95.

### COMPONENT PACKS

K603 150 wirewound resistors from 1W to 12W, with a good range of values, £1.75.  
K514 100 silver mica caps from 5pF to a few thousand pF. Tolerances from 1% to 10% £2.00.  
K520 Switch pack—20 different, rocker, slide, rotary, toggle, push, micro, etc. Only £2.00.

### MIXED LED PACK

All new full spec by Micro, Fairchild, etc. Red, Yellow, Green, Amber, Clear, 3mm & 5mm. Pack of 50 assid £3.45; 250 £15.

### 1000 RESISTORS £2.50

We've just purchased another 5 million preformed resistors, and can make a similar offer to that made two years ago, at the same price!!! K523—1000 mixed ½ and ¼W 5% carbon film resistors, preformed for PCB mntg. Enormous range of preferred values. 1000 for £2.50; 5000 £16; 20k £38.

### COPPER CLAD BOARD

K522 All pieces too small for our etching kits. Mostly double sided fibreglass. 2500gm (approx. 110 sq in) for just £1.00.

### PANELS

Z521 Panel with 18236 (2N3442) on small heat sink, 2N2232 dual transistor, 2 BC108, diodes, caps, resistors, etc. 80p.  
Z527 Reed relay panel—contains 2 x 6V reeds, 6 x 25030 or 25330, 6 x 400V reeds x Rs, 80p.  
Z529 Pack of ex-computer panels containing 74 series ICs. Lots of different gates and complex logic. All ICs are marked with type no. or code for which an identification sheet is supplied. 20 ICs £1.00; 100 ICs £4.00.



# MASTER ELECTRONICS NOW!

## The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



New Job? New Career? New Hobby? Get into **Electronics** Now!

**FREE!**

COLOUR BROCHURE



Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

OTHER SUBJECTS \_\_\_\_\_

POST NOW TO:

BLOCK CAPS PLEASE


EE/7/826

**British National Radio & Electronics School** Reading, Berks. RG1 1BR.

# NICADS: UK'S LOWEST PRICES

AMBIT'S NEW CONCISE COMPONENT CATALOGUE IS OUT NOW -

**Price on the page**

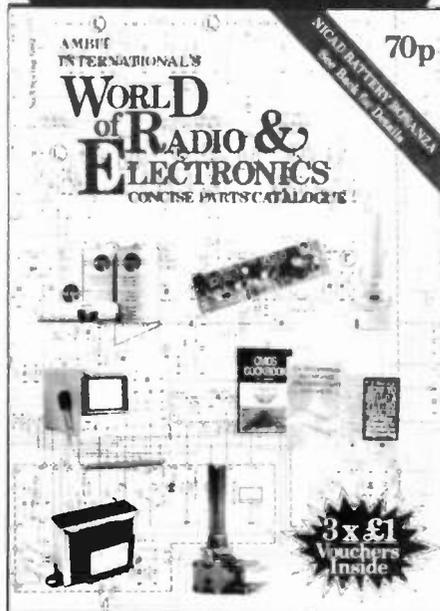

Ambit's new style catalogue continues to lead the market with low prices, new items, info, 3 x £1 discount vouchers. Here's a few examples of some super low prices:

- 78XX 1A 37p
- BC237/8/9 8p
- 3SK51 54p
- 10MHz XTALS £2
- 8 Pole 10.7MHz XTAL filters £14.50
- 2GHz coax relay 150W £10.95

+ all the usual stuff at rock bottom prices + Toko coils, crystal and ceramic filters, micrometals toroids, Fairite ferrites, Alps switches, OKI LSI, Piezo sounders, RF, IF Modules + Kits etc.

Available at your newsagent or direct, for 70p inc.



**RECHARGEABLE UP TO 400 TIMES PER CELL!**

CAPACITY	TYPE	1-9	10-49
500 mAh	AA	80	74
2200 mAh	C	2.35	1.99
1200 mAh	D	2.14	2.06
4000 mAh	D	3.05	2.85
110 mAh	PP3	3.70	3.50

Prices shown EXCLUDE VAT. Access/Barclaycard may be used with written or telephone orders, official MA details on application. E & EO.

**POSTAGE and PACKING**  
50p per order

Normal delivery 48 hours

**AMBIT international** TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG  
200 North Service Road, Brentwood, Essex

## CB EXTRA!

ADD-ON KITS FOR C.B. USERS

### SPEECH PROCESSOR

Dramatically improves the intelligibility of C.B. speech signals. This is the unit that so many C.B. owners are talking about on the air!

KIT CB-110 £13.98

### VOICE SCRAMBLER

For coding or decoding speech signals for greater transmission security.

KIT CB-117 £22.58

### FUNNY TALKER

Modified ring modulator for fascinating metallic quality to your voice when transmitting.

KIT CB-99 £13.32

### MUSICAL BLEEPER

Programme your own individual 8-note call sign. Push button operated for use when you want.

KIT CB-121 £16.41

### REVERB UNIT

Enhances the spacious quality of your transmitted voice. With control over depth and duration.

KIT CB-122 £15.85

Kits include printed circuit boards, U.K. P & P, 15% VAT, resistors, capacitors, semi-conductors, controls, switches, 4-pin CB plugs & sockets, wire, solder, metal case and assembly instructions. Batteries are not included (9v or 12v supply needed). All transmission units insert between microphone and rig without modification to either. For fuller details of these great popular add-on kits send a stamped addressed envelope for our Free catalogue. (Catalogue also includes many kits for musical and general projects.) For Export List send £1.00.

Prices correct at time of press, E. & O.E. subject to stock. Despatch usually 24 hours on all ex-stock items.

Terms: Mail Order C.W.O. or collection by appointment. Access, Barclay & Am-Express orders accepted. Tel: 01-302 6184.

## PHONOSONICS

DEPT EE27, 22 HIGH STREET, SIDCUP, KENT, DA14 6EH  
Founded 1972. A decade of design and delivery!

Talk, Update, Reaction,  
Fact, Opinion, Noise, News,  
Film, Print, Thrills, Chills,  
Right, Wrong,  
What Happens Next!

**NEW MUSICAL EXPRESS**

**THE WORD**  
Gets out every Thursday

# ELECTRONIC IGNITION

Makes a good car better



As a KIT or READY BUILT

**TOTAL ENERGY DISCHARGE** electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** — higher output voltage under all conditions.

**IMPROVED ECONOMY** — no loss of ignition performance between services.

**FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

## PLUS

**SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** — full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

## IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

## AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue and EVERYDAY ELECTRONICS December '81 Issue

**FITS ALL NEGATIVE EARTH VEHICLES**, 6 or 12 volt, with or without ballast

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS** Some older current impulse types (Smiths pre '74) require an adaptor — PRICE £2.95

**STANDARD CAR KIT** £ 14.85  
**Assembled and Tested** £ 24.95

**TWIN OUTPUT KIT** £ 22.95  
For MOTOR CYCLES and CARS with twin ignition systems  
**Assembled and Tested** £ 34.70

PLUS £1.00 U.K. P. & P. Prices include VAT.

## ELECTRONIZE DESIGN

Goods normally despatched within 7 days

Dept. C. Magnus Road, Wilnecote

Tamworth, B77 5BY

Phone (0827) 281000



# SPECIAL OFFERS

<b>TRANSISTORS</b> BC108A 7p BC171A 7p BC182L 7p BC183L 7p BC184L 7p BC212L 7p BC213L 7p BC214L 7p BC237B 7p BC307B 7p BC308 7p BC337 8p BC338 8p BC348B 8p BC351 8p BD243AX 43p — TIP3055 BU126 99p TIP32A 39p 2N2904 15p 2N3053 23p 2N3055 39p 2N3442 99p	<b>ZENER DIODES 400mW</b> 3V, 3V3, 3V9, 5V6, 6V8, 7V5, 15V, 30V and 33V All @ 4p each.	<b>ELECTROLYTIC CAPACITORS AXIAL</b> 2-2µF 63V (Mullard) 4p ea. 4-7µF 35V (Seatronic) 4p ea. 10µF 25V (Mullard) 5p ea. 33µF 100V (ITT) 7p ea. 17µF 16V (RDE) 5p ea. 100µF 16V (Erie) 6p ea. 220µF 10V (Erie) 7p ea. 220µF 16V (U Carbide) 9p ea. 220µF 40V (Mullard) 13p ea. 470µF 10V (ITT) 18p ea. 470µF 16V (Rubycon) 12p ea. 470µF 25V (Various) 75p ea.
<b>DIODES</b> IN4001 3p IN4002 35p IN4007 5p IN4140 19p IN4148 19p IN4383 49p BY133 8p	<b>TRANSFORMERS: 240V</b> <b>PRIMARY</b> 6-06v @ 100mA 85p ea. 9-0-9v @ 75mA 85p ea. 12-0-12v @ 50mA 85p ea. 56mm 8ohm Speak. 59p ea. Magnetic Earpiece 15p ea. Crystal Earpiece 49p ea. PPS Battery Clips 5p ea. B9A VALVE Holders 29p ea.	<b>ELECTROLYTIC CAPACITORS RADIAL</b> 4-7µF 50V PC (Rubycon) 4p ea. 4-7µF 100V PC (ITT) 5p ea. 100µF 40V PC (RDE) 8p ea. 330µF 6-3V (ITT) 8p ea. 470µF 10V PC (Plessey) 7p ea. 470µF 16V PC (Rubycon) 18p ea. PC = Short Leads for PCB.
<b>LEDs</b> TIL509 8p 3mm Clip 2p	<b>DIODES</b> DA47 uncodcd 4p ea. IN5401 uncodcd 5p ea. BZY88C15V Preformed— 3p ea.	<b>CERAMIC DISC CAPACITORS.</b> 4 7pF 500V 3p ea. 10pF 500V 3p ea. 120pF 500V 3p ea. 4700pF 50V 3p ea. 10n — 0.1µF 25V 3p ea. 47n — 0.47µF 25V 4p ea. 100n — 1µF 63V 8p ea.
<b>VEROBEXES PLASTIC</b> 202-21024B (Black) 45p ea. 202-21025K (White) 45p ea. 202-21026G (White) 69p ea.	<b>TRANSISTORS</b> 2N2904 15p 2N3053 23p	<b>RESISTORS Carbon Film Low Noise</b> ½ Watt 5% E12 Series. Range: 1R to 10M. @ 1p each. Except the above values are at 2 for 1p 1R8, 22R, 6K8, 120K, 680K, 1M2, 2M2 and 3M3.

ALL DEVICES BRAND NEW and GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. CAST/CHEQUE/POSTAL ORDERS WITH ORDER. PLEASE ADD 50p P & P. MAIL ORDER ONLY PLEASE.

## A. M. ELECTRONICS

TRADE/RETAIL SUPPLY OF ELECTRONIC COMPONENTS & EQUIPMENT

MAIL ORDER ONLY  
5 WILSON STREET, LEICESTER, LE2 0BB.

MAKE IT WITH BRADLEY

# Marshall's

OF LONDON

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS

Tel: 723-4242

**PROBABLY THE LARGEST STOCK OF ICs & TRANSISTORS IN THE SOUTH TRY US FIRST**

**LARGE RANGE OF ACCESSORIES**

Plugs  
Sockets  
Audio Connectors  
Veroboards  
IC Sockets  
Soldering equipment  
Screw drivers (BAHCO)  
Sifam Knobs etc.

**LARGE RANGE OF ICs**

Transistors  
Capacitors  
Diodes  
Triacs  
Thyristors  
Opto  
Resistors  
Potentiometers  
Fuses  
Bridges  
Please send S.A.E. for list.

**SPECIAL OFFER**

STEINAL MULTICHECK £7.50

+ VAT  
Normal price £10.26

**BUY WITH ACCESS**

BARCLAYCARD A/EXPRESS DINERS

Just phone we do the rest

**MAIL ORDER FASTER SERVICE**

PHONE 723-4242

**40 WAY RIBBON CABLE £2.20 metre**

Header plugs 14 way, 16 way, 40 way

**BAHCO TOOLS SIDE CUTTERS**

2132 £7.10

2112 £9.40

**END CUTTERS**

2211 £10.43

**PLIERS**

2411 £6.75

2415 £6.78

**ICE MULTIMETERS**

Microtest 80 £16.80

Supertest 680 R £32.00

Supertest 680E £24.50

**EXPERIMENTER BREADBOARD'S**

EXP 325 EXP 600

EXP 350 EXP 650

EXP 300 EXP 4B

**LOGIC PROBES**

LP1 £31.00

LP2 £18.00

**EXPERIMENTER KITS**

PB6 £9.20

PB100 £11.80

PLEASE REMEMBER To ADD 15% VAT

325 EGWARE ROAD LONDON W2 1BN

BARCLAYCARD • ACCESS • DINERS • A/EXPRESS



# CLASSIFIED

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.24 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury

notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## Veteran & Vintage

### "SOUNDS VINTAGE"

The only magazine for all vintage sound enthusiasts, packed with articles by top writers, covering gramophones, phonographs, 78s, wireless, news, history, reviews, etc.

Bi-monthly. Annual subscription £8.75 (airmail extra). Send 75p for sample copy. 28 Chestwood Close, Billericay, Essex

## Service Sheets

Any single service sheet £1/L.S.A.E. Thousands different Repair/Service Manuals/Sheets in stock. Repair data your named T.V. £6.50 (with circuits £8.50). S.A.E. Newsletter, Price Lists. Quotations.

**AUSEE, 76 CHURCHES,  
LARKHALL, LANARKSHIRE  
(0698 833334)**

**BELL'S TELEVISION SERVICE** for service sheets on Radio, TV etc. £1.25 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Rd. Harrogate, N. Yorkshire. Tel: 0423 55885.

## Courses

### SOUND ENGINEERS

If you're following a career in Sound Engineering or interested in learning all aspects of recording studios you should attend one of our weekend studio courses. Topics covered include:

- A. The basics of studio construction, wiring and materials used.
- B. Types of microphone uses, techniques, and limitations.
- C. Use of 2" 16 track machine, lining up, remotes, etc.
- D. Use of 24 Channel Desk and all controls.
- E. Effect equipment, ADT, reverb, Echo, etc.
- F. Ancilliary equipment.
- G. Mixing and Editing.

There are a maximum number of 8 students on each course and every one is tutored to their own level of knowledge with regard to their needs and interest. The cost is £98 for the weekend including hotel accommodation overnight. Details: please phone 01-580 4720 or 01-636 5308 during office hours.

## Receivers and Components

**AERIAL BOOSTERS** trebles incoming signal, price £7.00. SAE leaflets. **VELCO ELECTRONICS**, Ramsbottom, Lancashire BL0 9AG.

**TURN YOUR SURPLUS** capacitors, transistors etc., into cash. Contact **Coles Harding & Co.**, 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

**300 SMALL COMPONENTS**, transistors, diodes. £1.70 71bs assorted components £4.25 10lbs £5.75. Forty assorted 74 series ICs on panel £1.70. 500 capacitors £3.20. List 20p refundable. Post 60p. Optionable insurance 20p. **J. W. B. RADIO**, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

**BARGAIN PACKS!** New components, resistors, capacitors, semi-conductors, pots, etc. 1 pack £2.50 plus £1.00 p&p, 3 packs £7.50 (pack value £10 trade) p&p free. **JAY-SOUND**, Halliwell, 16 Hazeldene Close, Bury, Lancs BL9 9SA. Trade enquiries welcome.

**P.C. BOARD S.S.** 12in x 12in 3 for £2.00. glass fibre P.C board S.S. or D.S. 12in x 12in £1.00 each. Add 60p P&P any quantity. **COOPER**, 16 Lodge Road, Hockley, Birmingham B18 5PN.

### SCOOP PURCHASE — TELEPHONES

Black G.P.O. type for extension use. As new only £4.75 each, Carriage £1.75. 2 for £12.00 Carriage paid.

### HAVE YOU SEEN THE GREEN CAT?

1000s of new components, radio, electronic, audio at unbelievably low prices. Send 40p and receive list and FREE Record Speed Indicator. Try a JUMBO pack, transistors, caps, resistors, pots, switches, radio and electronic devices. Over £50 worth for £11 plus carriage £2.50.

**MYERS ELECTRONICS**, Dept E.E.2, 12/14 Harper Street, Leeds LS2 7EA. Tel: 452045. Callers Welcome.

## Wanted

**ARMY WIRELESS SETS** and instruction books on same. Hallicrafter receivers, and speakers. Will collect during my holidays in September. Please write to: **A. Huizer (PE1-DMN)**, Wilhelminasingel 16, 3135 JP Vlaardingen, Holland.

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for.....  
Insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)


NAME .....

ADDRESS .....

Send to: Classified Advertisement Manager

### EVERYDAY ELECTRONICS

Classified Advertisements Dept., Room 2612,  
King's Reach Tower, Stamford Street, London SE1 9LS  
Telephone 01-261 5942

#### Rate:

28p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 83886. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

7/82

## For Sale

**ZX81 16K RAM PSU Instructions Sinclair Tape Sinclair Assembled. Mint £50. HENDERSON, 21 Bridge Street, Aberdeen.**

**NEW BACK ISSUES OF "EVERYDAY ELECTRONICS". Available 85p each Post Free, cheque or uncrossed PO returned if not in stock. BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.**

**EVERYDAY ELECTRONICS, May 1976 to September 1979 complete. Offers: 5 Manor Road, Kingsthorpe, Northampton.**

## Miscellaneous

**TELETEXT ADD-ON ADAPTORS** convert your television for Oracle/Cefax. Also viewdata (Prestel) and teletext software. Access/Visa. Avon Office Services, FREEPOST, 82 Charlton Mead Drive, Bristol BS10 6BR. (0272) 502008 anytime.

**FOR PROFESSIONAL LOW COST Burglar Alarm DIY kits, contact: SECUTRONIC, Temple House, 43-48 New Street, Birmingham, B2 4LH. Tel: 021-643 4577.**

**PARAPHYSICS JOURNAL** (Russian translations): psychotronic generators, Kirlianography, gravity lasers, telekinesis. Details: SAE 4 x 9in, Paralab, Downton, Wilts.

## THE SCIENTIFIC WIRE COMPANY

PO Box 36, London E.4. 01 331 1588

### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
3 to 34	3.30	1.90	1.00	0.50
35 to 39	3.52	2.10	1.15	0.55
40 to 43	4.87	2.85	2.05	1.46
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

### SILVER PLATED COPPER WIRE

14 to 30	6.63	3.86	2.28	1.50
----------	------	------	------	------

### TINNEO COPPER WIRE

14 to 30	3.97	2.41	1.39	0.94
----------	------	------	------	------

10 x 10 mtr reels 3 amp PVC cable mixed colours \$ 80  
Prices include P & P vat. Orders under £2 add 20p.  
SAE for list of copper and resistance wire. Dealer enquiries welcome.

**FIBRE OPTIC GLASS LIGHT GUIDE.** 0.064" distal diameter, £1.50 metre 0.031", £1.00 metre. Minimum order £3.00. Nyewood Equipment, 91 Tilmore Gardens, Petersfield, Hampshire.

**DIGITAL WATCH REPLACEMENT PARTS.** Batteries, displays, backlights, etc. Also reports publications charts. SAE for full list. PROFORDS, Copners Drive, Holmer Green, Bucks HP15 6SGA.

**NEW ILLUSTRATED CATALOGUE** available 85p with two 25p vouchers. Griffiths Electronics (EE), 15 Windmill Gardens, Whixall, Whitchurch, Shropshire.

**ELECTRONIC GAMES.** Build your own microchip games from our detailed circuits. SAE for details. GHT Ltd, PO Box DR95, Dover, Kent, CT16 1UL.

## LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec.

This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Send cheque or P.O. to: Roden Products, Dep EE High March, Devon, Northants, NN11 4QE

**£4.70** plus 40p p.s.p. each

## BAKER £69 50 WATT AMPLIFIER

Post £2



Superior quality ideal for Hi-Fi systems. Discos and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available).

## BAKER 150 Watt AMPLIFIER 4 Inputs £89

Mono Slave 150W \$75. Stereo Slave \$125. post £2

## DRILL SPEED CONTROLLER LIGHT DIMMER KIT.

Easy to build kit. Controls up to 480 watts AC mains. \$3

## DELUXE MODEL Ready Built. 800 watts. \$5

## STEREO PRE-AMP KIT. All parts to build this pre-amp.

3 inputs for high, medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. \$2.95

## SOUND TO LIGHT CONTROL KIT MK II

Complete kit of parts, printed circuit, Mains transformer, 3 channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi. \$18

and all Disco Amplifiers. Cabinet extra \$4.50. Post 85p

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Base 75p each or 6 for £4 or 12 for £7.50.

## MAINS TRANSFORMERS Primary 240V A.C. POST

250-0-250V 70mA. 6 3V. 2A. £4.50 £2

250-0-250V 80mA. 6 3V 3 5A. 6 3V 1A. £5.00 £2

350-0-350V 250mA. 6 3V 6 Amp C.T. £12.00 £2

300-0-300V 120mA. 2 x 6 3V 2A C.T.: 5V 2A. £13.00 £2

220V 45mA. 6 3V 2A. £3.00 £1

Tapped outputs available

2 amp 3, 4, 5, 6, 8, 10, 12, 15, 18, 25 and 30V. £6.00 £2

1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2.00 £2

2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £1.50 £2

3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £1.50 £2

5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £1.60 £2

5-8-10-16V 1A. £2.50 80p 12-0-12V 2A. £3.50 £1

6V 1A. £2.00 £1 15-0-15V 2A. £3.75 £1

6-0-6V 1A. £3.50 £1 20V 1A. £3.00 £1

9V 250mA. £1.50 80p 20V 2A. £5.00 £1

9V 3A. £3.50 £1 20-0-20V 1A. £3.50 £1

9-0-9V 50mA. £1.50 80p 20-40-60V 1A. £4.00 £2

10-0-10V 2A. £3.00 £1 25-0-25V 2A. £4.50 £1

10-30-40V 2A. £3.50 £1 28V 1A Twice. £5.00 £2

12V 100mA. £1.50 80p 30V 1A. £3.50 £1

12V 750mA. £2.00 80p 30V 5A. £5.00 £2

12V 3A. £3.50 £1 32-0-32V 6A. £12.00 £2

12V 2A. £2.00 £1 35V 2A. £4.00 £1

TOROIDAL 30-0-30V 4 Amp +20-0-20V 1 Amp £10.00 £2

## CHARGER TRANSFORMERS RECTIFIERS

6-12V 3A. £4.00 £2 6-12V 2A. £1.00 80p

6-12V 4A. £6.50 £2 6-12V 4A. £2.00 80p

## R.C.S. LOUSPEAKER BARGAINS

3 ohm. 6 x 4in. 5in., 7 x 4in. £2.50. 8 x 5in. £2.00.

6in. £3.00. 8in. £2.50. 10in. £4.00. 8 ohm. 2in. £2.00.

3in. 5 x 3in. 5in. £2.50. 4in. £3.50. 10in. £5.00. 12in. £6.00.

16 ohm. 6 x 4in. 5in. £2.50. 8in. £3.50. 10 x 6in. £4.00.

25ohm. 3in. 35 ohm. 3in. £2.50. Many others in stock.

Samples: Speaker Covering Material 31p. stamps.

## R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 75p £3.95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.

## PP BATTERY ELIMINATOR. BRITISH MADE £4.50

Mains Transformer. Rectifier 9 volt 400mA. Post 75p

stabilised, with overload cutout. Plastic case size 5 x 5 1/2 x 2 1/2.

Suitable Radio/Cassettes. Fully isolated and Smoothed.

DELUXE Switched Model 3-6-7-9V 400mA. £7.50. post £1

## THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes and all sizes of tape reels.

A.C. mains 200/240V. £9.50 Post 95p

## HEAD DEMAGNETISER PROBE \$5.00.

A.C. ELECTRIC MOTORS POST 75p.

2 Pole, 240V, 0.2 Amp. Spindle—

1 43 x 0.212in. £1.75. 2 Pole,

240V, 0.15 Amp Double spindle—

1.75 x 0.16in. Each £1.2 Pole,

120V, .5 Amp Spindle—0.75 x

0.2in. Two in series — 240V. 50p

each. Brush Motor. From a Pool

Mixer 240V, .3 Amp High Speed

and Powerful Spindle—0.5 x

0.25in. £2.95. (good Selection.

B.S.R. Motors £4. Garrard Motors £5.

## ALUMINIUM CHASSIS 18 s.w.g. Undrilled, 4 sides, riveted

corners: 6 x 4 x 2 1/2in. £1.45; 8 x 6 x 2 1/2in. £1.80; 10 x 7 x 2 1/2in.

£1.80; 14 x 9 x 2 1/2in. £3.00; 16 x 6 x 2 1/2in. £2.90; 12 x 3 x 2 1/2in.

£1.30; 12 x 8 x 2 1/2in. £2.50; 16 x 10 x 2 1/2in. £3.20.

## ALL ALUMINIUM BRACKET 6 x 1 x 1 1/2in. £2.20.

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.50; 14 x 9in.

£1.45; 6 x 4in. 43p; 12 x 8in. £1.10; 10 x 7in. 96p; 8 x 6in. 72p.

14 x 3in. 72p; 12 x 5in. 72p; 16 x 10in. £1.68; 16 x 6in. £1.10;

ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.

4 x 2 1/2 x 2in. £1.00; 3 x 2 x 1in. 80p; 6 x 4 x 2in. £1.60; 8 x 6 x

3in. £2.50; 12 x 8 x 3in. £2.75; 6 x 4 x 3in. £1.80; 10 x 7 x 3in. £2.

## HIGH VOLTAGE ELECTROLYTICS 32 x 32/50V £0.50

8/450V ... 45p 50/450V ... 80p 32 x 32/800V £1.80

32/350V ... 45p 220/450V ... 80p 32 x 32 x 32/552V 75p

32/500V ... 75p 8 x 16/450V ... 75p 16 x 32 x 32/500V £3

## DE LUXE BSR HI-FI AUTOCHANGER

Stereo Ceramic Cartridge

Plays 12in., 10in., or 7in.

records Auto or Manual. A high

quality unit 240V A.C.

Above motor board 3 1/2in.

Below motor board 2 1/2in.

BBS Single Player P204 cueing device, Ceramic \$16 post \$2

or with ADC. QLM 30/3 Magnetic cartridge. \$20 post \$2

Garrard Single Player 780 8P metal turntable, £27 post £2

cueing device. Snake arm. Magnetic cartridge.

BBS P170 Single Player. 8 1/2in arm. 240V. A.C. £20 post £2

Ceramic cartridge. Cueing device. Auto stop.

B.S.R. P292. Belt drive, ceramic cartridge, £24 post £2

snake arm, cueing device. 240V.

B.S.R. Single Player. 12V D.C. motor, belt

drive, magnetic cartridge. £24 post £2

## Radio Component Specialists

337, WHITEHORSE ROAD, CROYDON, SURREY, U.K. TEL: 01-684 1665

Post 85p Minimum. Callers Welcome. Closed Wed. Same day despatch. Access-Barclay-Visa. Lists 31p.

## INDEX

## TO ADVERTISERS



Alcon	496
A.M. Electronics	493
Ambit	492
Bib Audio	477
Bi-Pak	439
BK Electronics	Cov. II, 436
B.N.R.E.S.	491
Bradly Marshalls	493
Bull J.	479
Cricklewood Electronics	434
Dziubas M.	439
E.D.A.	480
Electronize Design	493
Electrovalue	490
Enfield Electronics	490
Global Specialist	473
Greenweld	490
Heath-Kit	436
Intertext (ICS)	434
Lightning Components	472
Litesold	472
Magenta Electronics	438
Maplin Electronic Supplies Ltd.	Cov. IV
Memotech	489
Phononics	492
Radio Component Specialists	495
Radio TV Components	440
Rapid Electronics	437
Science of Cambridge	486, 487
Silica Shop	Cov. III
Titan Transformers	472
T.K. Electronics	434
Watford Electronics	435
Wilmslow Audio	436, 439





198 MOTT

# Make it with MAPLIN

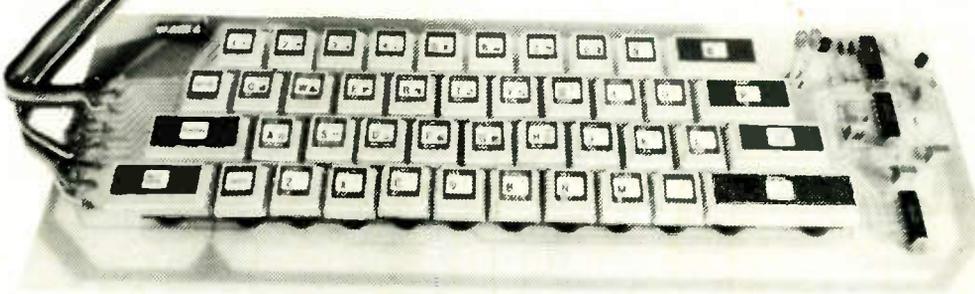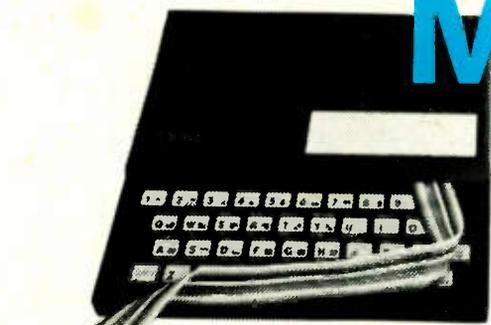

## KEYBOARD WITH ELECTRONICS FOR ZX81

- \* A full size, full travel 43-key keyboard that's simple to add to your ZX81 (no soldering in ZX81).
  - \* Complete with the electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections making entry far easier.
  - \* Powered from ZX81's own standard power supply - with special adaptor supplied.
  - \* Two-colour print for key caps.
  - \* Amazing low price.
- Full details in our projects book. Price 60p.  
Order As XA03D  
Complete kit for only £19.95 incl. VAT and carriage.  
Order As LW72P

## 25W STEREO MOSFET AMPLIFIER




- A superb new amplifier at a remarkably low price.
- \* Over 26W per channel into 8Ω at 1kHz both channels driven.
  - \* Frequency response 20Hz to 40kHz ± 1dB.
  - \* Low distortion, low noise and high reliability power-MOSFET output stage.
  - \* Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
  - \* Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in our projects book. Price 60p.  
Order As XA03D  
Complete kit for only £49.95 incl. VAT and carriage.  
Order As LW71N
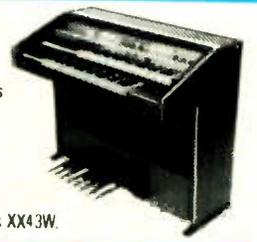
## MATINÉE ORGAN

Easy-to-build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50.  
Order As XH55K.



Complete kits available:  
Electronics - £299.95,  
Cabinet - £99.50 (carriage extra).  
Demo cassette price £1.99. Order As XX43W.

## HOME SECURITY SYSTEM



Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability. Full details in our projects book.  
Price 60p.  
Order As XA02C.

## MILES PER GALLON METER

Digital display shows you how economical your driving is as you go along.  
Complete kits available.  
Full details in our projects book.  
Price 60p.  
Order As XA02C.



## DIGITAL MULTI-TRAIN CONTROLLER

Control up to 14 trains individually on the same track with any four simultaneously! Low cost kits available. Full details in our projects book. Price 60p.  
Order As XA02C.



Don't miss out - get a copy of our catalogue now!  
Over 140,000 copies sold already!

On sale now in all branches of WHSMITH price £1.  
320 big pages packed with data and pictures of over 5,500 items.



### Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&pl). If I am not completely satisfied I may return the catalogue to you and have my money refunded.  
If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name \_\_\_\_\_

Address \_\_\_\_\_

Delivery within 14 days

EE/7/82

# MAPLIN ELECTRONIC SUPPLIES LTD.

All mail to:  
P.O. Box 3, Rayleigh, Essex SS6 8LR  
Tel: Sales (0702) 552911 General (0702) 554155

Shops at:  
159 King St., Hammersmith, London W6. Tel: 01-748 0926  
284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000  
Note: Shops closed Mondays