

EVERYDAY

NOVEMBER 1996

PRACTICAL

ELECTRONICS


<http://www.epemag.wimborne.co.uk>

£2.45

EPE ELYSIAN MIDI THEREMIN

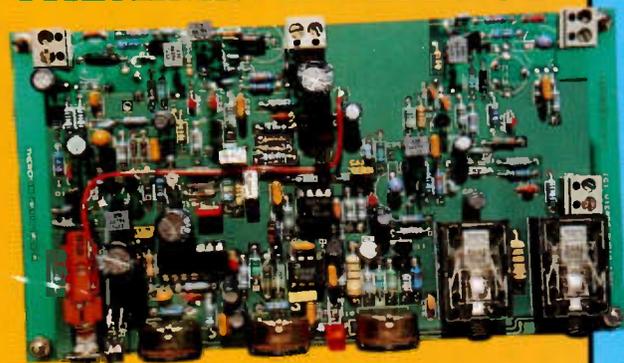Part 1 – A full specification
Theremin plus the

**WORLD'S FIRST MIDI
THEREMIN INTERFACE**



CENTRAL HEATING CONTROLLER

*Versatile microcontroller
based design*

SCRATCH FILTER

For everyone with old LPs

BUILD YOUR OWN PROJECTS

New, fully illustrated series

Plus **INGENUITY UNLIMITED**

NET WORK **CIRCUIT SURGERY**

FOX REPORT **INTERFACE** **NEW TECHNOLOGY UPDATE**



THE No. 1

**MAGAZINE FOR
ELECTRONICS TECHNOLOGY
& COMPUTER PROJECTS**



MOONSHINE BIBLE 270 page book covering the production of alcohol from potatoes, rice, grains etc. Drawings of simple home made stills right through to commercial systems. £15 ref MS1

NEW HIGH POWER MINI BUG With a range of 800 metres or more and up to 100 hours use from a PP3, this will be popular! Bug measures less than 1" square! £28 Ref LOT102.

SINCLAIR C6 MOTORS We have a new ones available without gearboxes at £50 ref LOT25

BUILD YOUR OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81

PC KEYBOARDS PS2 connector, top quality suitable for all 286/386/486 etc £10 ref PCKB, 10 for £65.

TRACKING TRANSMITTER range 1.5-5 miles, 5,000 hours on AA batteries, also transmits info on car direction and motion! Works with any FM radio. 1.5" square £65 ref LOT101

ELECTRIC DOOR LOCKS Complete lock with both Yale lock and 12v operated deadlock (keys included) £10 ref LOT99

GALLIUM ARSENIDE FISH EYE PHOTO DIODES Complete with suggested circuits for long range communications/switching £12 complete.

SURVEILLANCE TELESCOPE Superb Russian zoom telescope adjustable from 15x to 60x complete with metal tripod (impossible to use without this on the higher settings) 66mm lens, leather carrying case £149 ref BAR69

WIRELESS VIDEO BUG KIT Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP79. (probably not licensable!)

CCTV CAMERA MODULES 46X70X29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video IR sensitive. £79.95 ref EF137.

IR LAMP KIT Suitable for the above camera enables the camera to be used in total darkness! £5.99 ref EF138

REMOTE CONTROL AND DATA T01400 MODEM/VIEWDATA Complete system comprising 1200/75 modem, auto dialler, infra red remote keyboard, (could be adapted for PC use?) psu, UHF and RGB output, phone lead, RS232 output, composite output. Absolute bargain for parts alone! £9.95 ref BAR33.

9 WATT CHIEFTAN TANK LASERS

Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, full circuit diagrams, new price £50,000? us? £349. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. five or more units £299 ea £349 for one. Ref LOTA

TOWAY MIRROR KIT Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) Includes full instructions. £12 ref TW1.

NEW LOW PRICED COMPUTER/WORKSHOP/HI-FI RCB UNITS Complete protection from faulty equipment for everybody! Inline units fit in standard IEC lead (extends to 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £6.95 each ref LOT5. Or a pack of 10 at £49.90 ref LOT6. If you want a box of 100 you can have one for £250!

RADIO CONTROLLED CARS FROM £6 EACH!!!!

All returns from famous manufacturer, 3 types available, single channel (left, right, forwards, backwards) £6 ref LOT1. Two channel with more features £12 ref LOT2.

THOUSANDS AVAILABLE RING/FAX FOR DETAILS!

MAGNETIC CARD READERS (Swipes) £9.95 Cased with flyleads, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well? complete with control electronics PCB. Just £9.95 ref BAR31

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

PANORAMIC CAMERA OFFER Takes double width photographs using standard 35mm film. Use in horizontal or vertical mode. Complete with strap £7.99 ref BAR1

COIN OPERATED TIMER KIT Complete with coin slot mechanism, adjustable time delay, relay output, put a coin slot on anything you like! TV's, videos, fridges, drinks cupboards, HiFi, takes 50p's and £1 coins. DC operated, price just £7.99 ref BAR27.

ZENITH 900 X MAGNIFICATION MICROSCOPE Zoom, metal construction, built in light, shrimp farm, group viewing screen, lots of accessories, £29 ref ANAYLT.

AA NICAD PACK Pack of 4 tagged AA nicads £2.99 ref BAR34

PLASMA SCREENS 222x310mm, no data hence £4.99 ref BAR67

NIGHTSIGHTS Model TZ54 with infra red illuminator, views up to 75 metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty

LIQUID CRYSTAL DISPLAYS Bargain prices, 16 character 2 line, 99x24mm £2.99 ref SM1623A
20 character 2 line, 83x19mm £3.99 ref SM2020A
16 character 4 line, 62x25mm £5.99 ref SMC1640A

TAL-1 110MM NEWTONIAN REFLECTOR TELESCOPE Russian. Superb astronomical scope, everything you need for some

serious star gazing! up to 166x magnification. Send or fax for further

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST WOLVERHAMPTON TEL 01902 22039

details £249 ref TAL-1

CENTRAL POINT PC TOOLS Award winning software, 1,300 virus checker, memory optimiser, disc optimiser, file compression, low level formatting, backup scheduler, disk defragmenter, undelete, 4 calculators, Dbase, disc editor, over 40 viewers, remote computing, password protection, encryption, comprehensive manual supplied etc £25 ref lot 97 3.5" disks.

GOT AN EXPENSIVE BIKE? You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle cameras, supplied with two keys. SALE PRICE £7.99 REF SA32.

GOT AN EXPENSIVE ANYTHING? You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to anything from videos to caravans, provides a years protection from 1 PP3 battery, UK made. SALE PRICE £4.99 REF SA33.

DAMAGED ANSWER PHONES These are probably beyond repair so just £4.99 each BT response 200 machines. REF SA30.

COMPUTER DISC CLEAROUT We are left with a lot of software packs that need cleaning so we are selling at disc value only! 50 discs for £4, that's just 8p each! (our choice of discs) £4 ref EP66

IBM PS2 MODEL 160Z CASE AND POWER SUPPLY Complete with fan etc and 200 watt power supply. £9.95 ref EP67

DELL PC POWER SUPPLIES 145 watt, +5, -5, +12, -12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP55

1.44 DISC DRIVES Standard PC 3.5" drives but returns so they will need attention. SALE PRICE £4.99 ref EP68

1.2 DISC DRIVES Standard 5.25" drives but returns so they will need attention. SALE PRICE NOW ONLY £3.50 ref EP69

PP3 NICADS Unused but some storage marks. £4.99 ref EP52

DELL PC POWER SUPPLIES (Customer returns) Standard PC psu's complete with flyleads, case and fan. +12v, -12v, +5v, -5v. SALE PRICE £1.99 EACH worth if for the bits alone! ref DL1. TRADE PACK OF 20 £28.95 Ref DL2.

GASHOBS AND OVENS Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob. SALE PRICE £24.99 ref EP72. Basic small built in oven. SALE PRICE £79 ref EP73

RED EYE SECURITY PROTECTOR 1,000 watt outdoor PIR switch. SALE PRICE £6.99 ref EP57

ENERGY BANK KIT 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EF112.

PASTEL ACCOUNTS SOFTWARE, does everything for all sizes of businesses. Includes word processor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual, 90 days free technical support (01342-326009 try before you buy) Current retail price is £128. SALE PRICE £9.95 ref SA12. SAVE £120!!

COMPLETE PC 200 WATT UPS SYSTEM Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made. Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. LATEST FEW TO CLEAR AT £49 SAVE £30 ref LOT61

BIG BROTHER PSU Cased PSU, 6v 2A output, 2m op lead, 1.5m input lead, UK made. 220v. SALE PRICE £4.99 REF EP7



Check out our
WEB SITE

<http://www.pavillon.co.uk/bull-electrical>

RACAL MODEM BONANZA! 1 Racal MPS1223 1200/75m modem, telephone line, mains lead, manual and comms software, the cheapest way onto the net! all this for just £13 ref DEC13.

4.5mw LASER POINTER, BRAND NEW MODEL, NOW IN STOCK! supplied in fully built form (looks like a nice pen) complete with handy pocket clip (which also acts as the on/off switch.) About 60 metres range! Runs on 2 AAA batteries. Produces thin red beam ideal for levels, gun sights, experiments etc. Just £39.95 ref DEC49. TRADE PRICE £28 MIN 10 PIECES

BULL TENS UNIT Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 Ref TEN1

PC PAL VGA TO TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and swave. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

EMERGENCY LIGHTING UNIT Complete unit with 2 double

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3 P&P PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY/PHONE ORDERS

WELCOME (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500

FAX 01273 323077

E-mail bulk@pavillon.co.uk

bulb floodlights, built in charger and auto switch. Fully cased. 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11

YUASHA SEALED LEAD ACID BATTERIES Two sizes currently available this month. 12v 15AH at £18 ref LOT8 and 6v 10AH (suitable for emergency lights above) at just £6 ref LOT7.

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc. SALE PRICE JUST £4.99 REF SA28

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £8.99 REF SA25

MICRODRIVE STRIPPERS Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA26

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit. SALE PRICE JUST £4.99 REF SA27

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back anodised metal case. SALE PRICE £49 REF SA16B

PLUG IN ACORN PSU 19v AC 14w. £2.99 REF MAG3P10

13.8V 1.9A PSU cased with leads. Just £9.99 REF MAG10P3

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

PHONE CABLE AND COMPUTER COMMUNICATIONS PACK Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PC's over a long distance utilizing the serial ports. Complete kit £8.99. Ref comp1.

VIEWDATA SYSTEMS made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc. RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

AIR RIFLES .22 As used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets £4.50 ref EF80.

PLUG IN POWER SUPPLY SALE FROM £1.60 Plugs in to 13A socket with output lead, three types available. 9vdc 150mA £1.50 ref SA19, 9vdc 200mA £2.00 ref SA20, 6.5vdc 500mA £2 ref SA21.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, videorecorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12V DC op. Price is £25 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range up to 2km in open country. Units measure 22x25x155mm. Including cases and earpieces. 2xPP3 req'd. £30.00 pr. REF: MAG30

***FM TRANSMITTER KIT** housed in a standard working 13A adapter!! the bug runs directly off the mains so lasts forever! why pay £700? or price is £15 REF: EF62 (kit) Transmits to any FM radio.

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER COMPLETE WITH COIN SLOT MECHANISMS originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? SALE PRICE JUST £2.50 REF SA23

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £12.95 Ref EP82B extra pellets (500) £4.50 ref EF80.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30m for £12.99 ref MAG13P1

MIXED GOODIES BOX OF
MIXED COMPONENTS WEIGHING 2 KILOS
YOURS FOR JUST £6.99

4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R7

GYROSCOPES Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift or for educational use etc. £6 ref EP70

HYPOTHERMIA SPACE BLANKET 215x150cm aluminised foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirrors! £3.99 each ref O/L041.

LENSTATIC RANGER COMPASS Oil filled capsule, strong metal case, large luminous points, sight line with magnifying viewer. 50mm dia, 86gm. £10.99 ref O/K604

RECHARGE ORDINARY BATTERIES UP TO 10 TIMES! With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are charged, automatically rejects unsuitable cells, complete with mains adaptor. BS approved. Price is £21.95 ref EP31.

TALKING WATCH Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE! The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands. 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities. micro size just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3

3" DISCS As used on older Amstrad machines, Spectrum plus3's etc £3 each ref BAR400

STEREO MICROSCOPES BACK IN STOCK Russian, 200x complete with lenses, lights, filters etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee) full details in catalogue.

WE BUY SURPLUS STOCK

FOR CASH

BUYERS DIRECT LINE 0802 660377
FREE CATALOGUE

100 PAGE CATALOGUE NOW
AVAILABLE, 50P STAMP OR FREE
ON REQUEST WITH ORDER.

ISSN 0262 3617
PROJECTS ... THEORY ... NEWS ...
COMMENT ... POPULAR FEATURES ...






VOL. 25 No. 11 NOVEMBER '96

EVERYDAY

PRACTICAL

ELECTRONICS

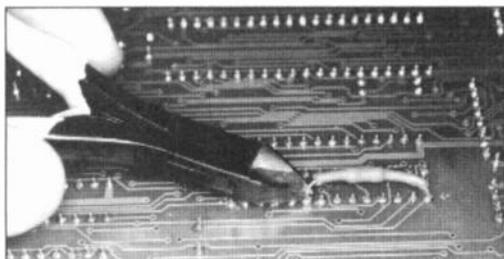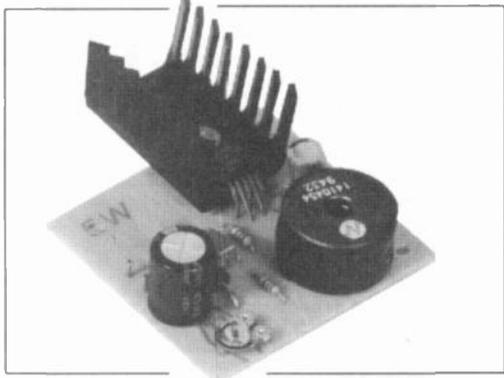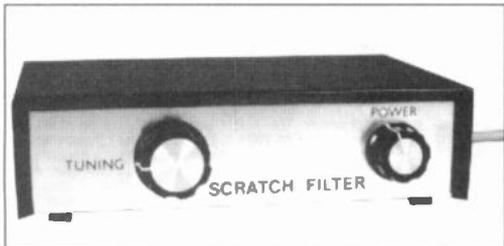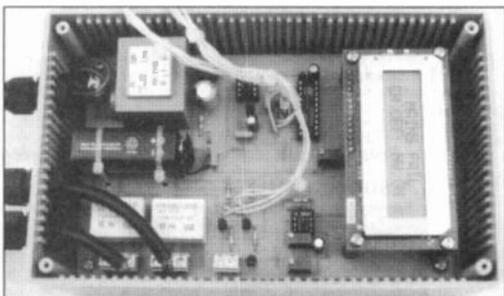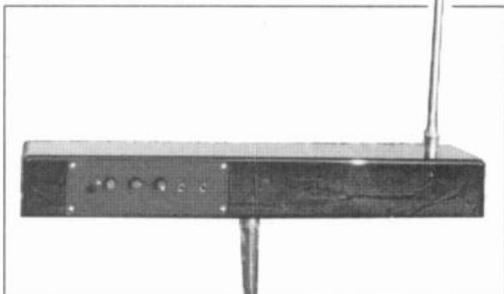The No. 1 Magazine for Electronics, Technology
and Computer Projects



© Wimborne Publishing Ltd 1996. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our December '96 issue will be published on Friday, 1 November 1996. See page 859 for details.
Everyday Practical Electronics, November 1996

Projects and Circuits

- D.C.-TO-D.C. CONVERTERS** by Robert Penfold 820
Choice of three low cost, low voltage, switch mode converters using custom i.c.s.
- CENTRAL HEATING CONTROLLER** by Richard Stone 831
Monitor your heating requirements with this microcontroller 7-day programmer
- INGENUITY UNLIMITED** hosted by Alan Winstanley 840
8-bit Binary-to-Decimal Converter; L.E.D. Quick Test; Model Railway Level Crossing Lights
- EPE ELYSIAN THEREMIN - 1** by Jake Rothman 844
Full spec. professional-grade instrument for the serious musicmaker
- INTERFACE** by Robert Penfold 856
PC-based Auto-Ranging Resistance Meter Interface
- TUNEABLE SCRATCH FILTER** by Robert Penfold 862
New life for old "vinyl" records

Series and Features

- NEW TECHNOLOGY UPDATE** by Ian Poole 842
Enhanced reliability is claimed for lead frame base modules
- BUILD YOUR OWN PROJECTS** by Alan Winstanley 852
Part 1: Initial guide lines, essential tools and equipment needed to get you started
- CIRCUIT SURGERY** by Alan Winstanley 873
Voltage Monitor problems, Flashing I.e.d.s, Hole Storage Noise plus a Challenge
- NET WORK - THE INTERNET PAGE** surfed by Alan Winstanley 876
Get SET for electronic security, on-site feedback and browser battles ahead

Regulars and Services

- EDITORIAL** 819
- FOX REPORT** by Barry Fox 826
Acrimonious Logic and Frank's confession
- INNOVATIONS** 829
Everyday news from the world of electronics
- BACK ISSUES** 858
Did you miss these?
- FAX ON DEMAND** 859
Need a recent *EPE* article today? Try our "instant" response service
- SHOPTALK** with David Barrington 860
Component buying for *EPE* projects
- ELECTRONICS VIDEOS** 868
Our range of educational videos
- DIRECT BOOK SERVICE** 870
A wide range of technical books available by mail order
- OHM SWEET OHM** by Max Fidling 874
A mysterious catcophony of sounds finds Max not knowing which way to turn next
- PRINTED CIRCUIT BOARD SERVICE** 875
PCBs for *EPE* projects. Plus *EPE* software
- ADVERTISERS INDEX** 880

Readers Services • Editorial and Advertisement Departments 819

809

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

LOW COST PC's -

SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run / Order as HIGRADE 286 **ONLY £129.00 (E)**

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£19.95
Wordperfect 6.0 for Dos - when 3 1/2" FDD option ordered	£22.50
NE2000 Ethernet (thick, thin or twisted) network card	£29.00

LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd user, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3 1/2" floppy disk drive. Fully tested and guaranteed. Fully expandable. Only **£399.00 (E)** Many other options available - call for details.

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" or 3 1/2" from only £18.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent RFE	£24.95(B)
3 1/2" Mitsubishi MF355C-L 1.4 Meg Laptops only	£25.95(B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg Non laptop	£18.95(B)
5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE	£18.95(B)
5 1/4" Teac FD-55F 0.3 U 720K 40/80 (for BBC's etc) RFE	£22.95(B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
Table top case with integral PSU for HH 5 1/4" Flopp or HD	£29.95(B)
8" Shugart 800/801 8" SS refurbished & tested	£195.00(E)
8" Shugart 810 8" SS HH Brand New	£195.00(E)
8" Shugart 851 8" double sided refurbished & tested	£250.00(E)
Mitsubishi M2894-63 8" double sided NEW	£275.00(E)
Mitsubishi M2896-63-02U 8" DS slimline NEW	£285.00(E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00(E)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only **£299.00** or 2 for **£525.00 (E)**

3 1/2" FUJI FK-309-26 20mb MFM I/F RFE	£59.95(C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE	£59.95(C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv) RFE	£69.00(C)
3 1/2" RODIME R030575 45mb SCSI I/F (Mac & Acorn)	£69.00(C)
3 1/2" WESTERN DIGITAL 950mb IDE I/F Brand New	£185.00(C)
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE	£49.95(C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Return	£69.95(C)
5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested	£69.95(C)
5 1/4" HP 9754B 850 Mb SCSI RFE tested	£89.00(C)
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00(C)
8" FUJITSU M3222K 160Mb SMD I/F RFE tested	£195.00(E)
Hard disc controllers for MFM, IDE, SCSI, RLL etc. from	£16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£36.95
TELEBOX STL as ST but fitted with integral speaker	£39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner	£69.95

For overseas PAL versions state 5.5 or 6 MHz sound specification. *For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Teleboxes is (B)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call for info / list.

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched landscape, test switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition. Tilt & Swivel Base. £4.75 Only **£119 (E)** Order as MITS-SVGA VGA cable for IBM PC included.

External cables for other types of computers CALL

As New - Used on film set for 1 week only!! 15" 0.28 SVGA 1024 x 768 res. colour monitors. Swivel & tilt etc. Full 90 day guarantee. **£145.00 (E)**

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" video monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed Dimensions: W14" x H12 3/4" x 15 1/2" D. Only **£95 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered. Only **£79.00 (D)**

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 11". Good used condition. Only **£125 (E)**

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

SPECIAL INTEREST ITEMS

MITS. FA3445ETKL 14" Industrial spec SVGA monitors 2Kw to 400 kw - 400 Hz 3 phase power sources - ex stock	£245
EPDA IBM 8230 Type 1, Token Ring base unit driver	£950
IBM 83F5501 Token Ring ICS 20 port job modules	£750
IBM MAU Token ring distribution panel 8228-23-5050N	£95
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE	£550
Trend DSA 274 Data Analyser with G703(ZM) 64 Vc	£6500
Marconi 6310 Programmable 2 to 22 GHz sweep generator	£6500
HP1650B Logic Analyser	£3750
HP3781A Pattern generator & HP3782A Error Detector	£POA
HP APOLLO RX700 system units	£950
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts	£1800
HP3081A Industrial workstation clc Barcode sweeper reader	£175
HP6264 Rack mount variable 0-20V @ 20A metered PSU	£175
HP54121A DC to 22 GHz 4 channel test set	£POA
HP7580A A1 8 pin HPGL high speed drum plotter	£1850
EG+G Brookdeal 950353C Precision lock in amp	£650
View Eng. Mod 1200 computerised inspection system	£POA
Ling Dynamics 2Kw programmable vibration test system	£POA
Computer controlled 1056 x 560 mm X Y table & controller	£1425
Keithley 590 CV capacitor / voltage analyser	£750
Recal ICR40 dual 40 channel voice recorder system	£3750
Fiskers 4K5VA 3 ph On Line UPS - New bats Dec 1995	£9500
ICI R5030UV34 Cleanline ultrasonic cleaning system	£POA
Mann Tally MT645 High speed line printer	£2200
Intel SBC 486/133SE Multibus 486 system. 8Mb Ram	£1200
Zeta 3220-05 A0 4 pen HPGL fast drum plotters	£1150
Nikon HFX-11 (Ephiphot) exposure control unit	£1450
Motorola VME Bus Boards & Components List. SAE / CALL	£POA
Trio 0-18 vdc linear, metered 30 amp bench PSU. New	£550
Fujitsu M3041D 600 LPM band printer	£1950
Fujitsu M3041D 600 LPM printer with network interface	£1250
Perkin Elmer 2998 Infrared spectrophotometer	£POA
VG Electronics 1035 TELETEXT Decoding Margin Meter	£3750
Andrews LARGE 3.1 m Satellite Dish & mount (For Voyager)	£950
Sekonic SD 150H 18 channel digital Hybrid card recorder	£1995
RAYLOR HOPSOR 1 Talky talk amplifier / recorder	£750
System Video 1152 PAL waveform monitor	£485
Test Lab - 2 mtr square quietised acoustic test cabinets	£300
Kenwood 9601 PAL Vectorscope - NEW	£650

Please call for further details on the above items



19" RACK CABINETS

Superb quality 6 foot 40U Virtually New, Ultra Smart Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels.	£335.00 (G)
OPT Rack 2 Rack, Less side panels	£225.00 (G)

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 1/2" W). Sold at LESS than a third of makers price!!

A superb buy at only **£195.00 (G)**

Over 1000 racks - 19" 22" & 24" wide 3 to 44 U high. Available from stock!! Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost!! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size!! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc. Imagine using your finger with 'Windows', instead of a mouse!! (A driver is indeed available!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: **£145.00 (B)** Full MICROTUCH software support pack and manuals for IBM compatible PC's £29.95 RFE - Tested

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. **£59.95(A1)** Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data. Order as: XT RAM UPG 256K. **£34.95** or 512K **£39.95 (A1)**

SIMM SPECIALS

1 MB x 9 SIMM 9 chip 120ns	Only £16.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns £19.50 or 70ns	£22.95 (A1)
1 MB x 9 SIMM 9 chip 80 ns £21.50 or 70ns	£23.75 (A1)
4 MB 70 ns 72 pin SIMM - with parity -	Only £95.00 (A1)
INTEL 486-DX33 CPU £55.00. Intel 486-DX66 CPU £69.00 (A1)	

FULL RANGE OF CO-PROCESSORS EX STOCK - CALL FOR LIST

FANS & BLOWERS

EPSON D0412 40x40x20 mm 12v DC	£7.95 10 / £55
PAPST Type 012 60x60x25 mm 12v DC	£8.95 10 / £75
MITSUBISHI MMF-D6012DL 60x60x25 mm 12v DC	£4.95 10 / £42
MITSUBISHI MMF-08C12DM 80x80x25 mm 12v DC	£5.25 10 / £49
MITSUBISHI MMF-09B12DM 92x92x25 mm 12v DC	£5.95 10 / £53
PANCAKE 12-3.5 92x92x18 mm 12v DC	£7.95 10 / £69
EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm specify 110 or 240 V. £6.95. 80 x 80 x 38 mm - specify 110 or 240 V. £5.95	
IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240V NEW	£79.95

Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

Issue 13 of Display News now available - send large SAE - PACKED with bargains!



ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept PE. 32 Bligg Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton, Heath &
Selhurst Park SR Rail Stations

NEW DISTEL ©
The Original
FREE On line Database
Info on 20,000 + stock items!
RETURNING SOON!

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)-£3.00, (A1)-£4.00, (B)-£5.50, (C)-£8.50, (D)-£12.00, (E)-£15.00, (F)-£18.00, (G)-CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996. E & O.E. 066

Transform your PC

into a digital oscilloscope, spectrum analyser, frequency meter, voltmeter, data logger .. for as little as £49.00

Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement instruments or as an advanced data logger.

Hardware and software are supplied together as a package - no more worries about incompatibility and no programming required.

Pico Technology specialises only in the development of PC based data acquisition instrumentation. We have the product range and experience to help solve your test and measurement problem.

Call for your guide on 'Virtual Instrumentation'. We are here to help you.



The ADC-10 supplied with PicoScope gives your computer a single channel of analog input.

ADC-10 £49
with PicoLog £59

Data Logging

Pico's range of PC based data logging products enable you to easily measure, display and record temperature, pressure and voltage signals.

TC-08 Thermocouple to PC Converter

- Supplied with PicoLog data logging software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs
- No power supply required.

TC-08 £199 TC-08 £224 with cal. Cert. complete with serial cable & adaptor. Thermocouple probes available.

Virtual Instrumentation

Pico's PC based oscilloscopes simply plug into the parallel port turning your PC into a fully featured oscilloscope, spectrum analyser and meter. Windows and DOS software supplied.

ADC-100 Dual Channel 12 bit resolution

The ADC-100 offers both a high sampling rate 100kHz and a high resolution. Flexible input ranges ($\pm 50\text{mV}$ to $\pm 20\text{V}$) make the unit ideal for audio, automotive and education use.

ADC-100 £199 ADC-100 with PicoLog £219

ADC-200 Digital Storage Oscilloscope

- 50 MSPS Dual Channel Digital Storage Scope
- 25 MHz Spectrum Analyser
- Windows or DOS environment
- $\pm 50\text{mV}$ to $\pm 20\text{V}$
- Multimeter
- 20 MSPS also available

ADC 200-20 £359.00
ADC 200-50 £499.00

Both units are supplied with cables, power supply and manuals.

Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK Tel: + 44 (0)1954 211716 Fax: + 44 (0)1954 211880 E-mail: post@picotech.co.uk Web site: <http://www.picotech.co.uk/>

Call for free demo disk and product range catalogue

Post & Packing UK £3.50, Export customers add £9 for carriage & insurance.


releasing PC potential

releasing PC potential

PICO Technology Limited



"extremely good value for money..."

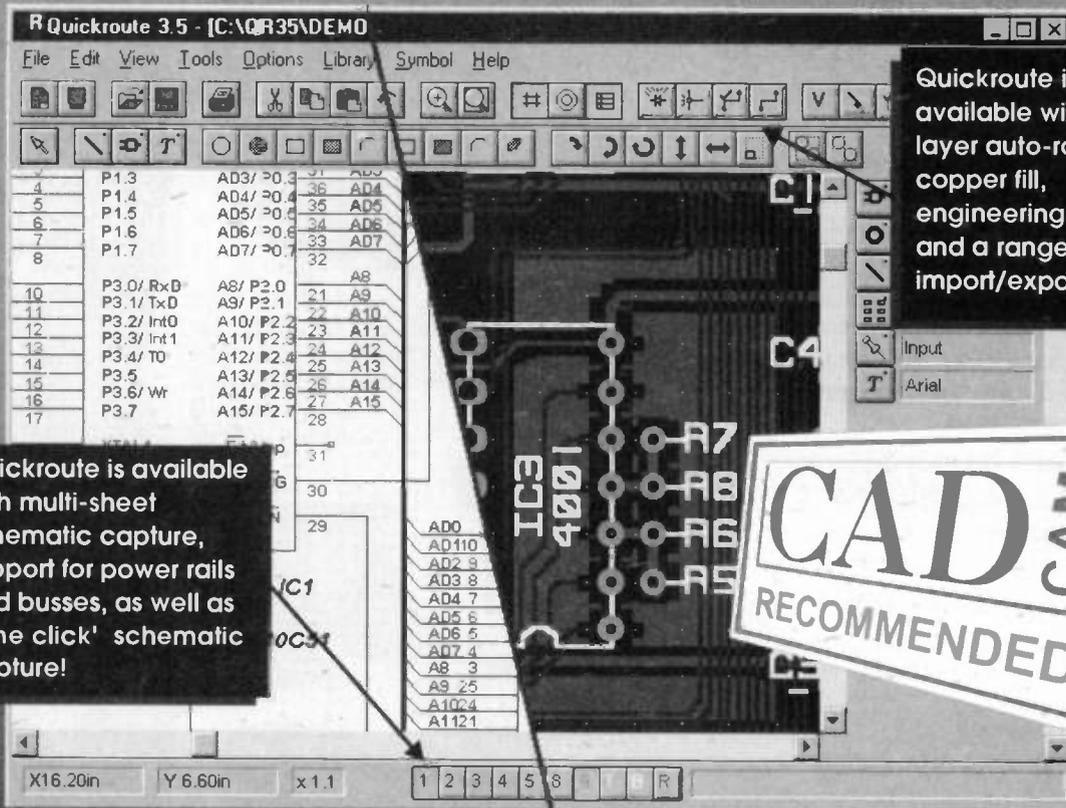

Quickroute is available with 1-8 layer auto-routing, copper fill, engineering change, and a range of import/export features.

Quickroute is available with multi-sheet schematic capture, support for power rails and busses, as well as 'one click' schematic capture!



..for such a comprehensive package"

Practical Wireless July 96

Quickroute 3.5 is a powerful, affordable and easy to use integrated schematic & PCB design system for windows. With its multiple button bars, 'tool tips' and parts-bin you will find that Quickroute helps you to work quickly and efficiently.

Whichever version of Quickroute you choose, you can be sure of getting value for money! Quickroute is available with multi-sheet schematic capture, 1-8 layer auto-routing, copper fill, engineering change, and a range of popular file import/export features allowing connection to simulators and other software packages (details on request). See the table for a selection of features.

Prices range from £68 to £399. Post and packing is £5 (UK), £8 (Europe), £12 (worldwide). VAT must be added to the total price.

**CAD/CAM Recommended March 95

	Personal	Designer	PRO	PRO+
PCB & Schematic Design	*	*	*	*
Schematic Capture	*	*	*	*
Design Rule Checking	*	*	*	*
Connectivity Checking		1	1	2
RouteASSIST (assisted routing)	*	*	*	*
Auto router		*	*	*
Export WMF & Tango		*	*	*
Export Gerber/NC-Drill		*	*	*
Extended Libraries		*	*	*
Tango & Gerber Import		*	*	*
Update PCB from schematic		*	*	*
DXF & SPICE Export		*	*	*
Copper Fill		*	*	*

1 Simple pass/fail 2 Advanced Check

NEW Now with RouteASSIST™



Tel/Fax 0161 449 7101

WWW: www.quickroute.co.uk EMail: info@quicksys.demon.co.uk

Quickroute Systems Ltd., 14 Ley Lane, Marple Bridge, Stockport, SK6 5DD, U.K.

DENMARK 45 33 25 0017 GERMANY 49 711 62 7740 NORWAY 22 16 7045 PORTUGAL 351 813 1975 8146230 SWEDEN 46 8 740 5500

Prices and specifications subject to change without notice. All trade marks are acknowledged & respected.

Phone Now
For More
Information

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

Genuine SUMA kits available only direct from Suma Designs. Beware inferior imitations!

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3V-12V operation. 500m range..... **£16.45**

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter. Just 17mm x 17mm including mic. 3V-12V operation. 1000m range..... **£13.45**

STX High-performance Room Transmitter

High performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm, including mic. 6V-12V operation, 1500m range. **£15.45**

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9V-12V operation. 3000m range..... **£16.45**

VXT Voice-Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range. **£19.45**

HVX400 Mains Powered Room Transmitter

Connects directly to 240V A.C. supply for long-term monitoring. Size 30mm x 35mm. 500m range..... **£19.45**

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range..... **£22.95**

SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range..... **£23.95**

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9V-12V operation..... **£22.95**

ATR2 Micro-Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line..... **£13.45**

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range..... **£15.95**

TLX 700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range..... **£13.45**

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range..... **£16.45**

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation..... **£22.95**

CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation..... **£30.95**

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation..... **£50.95**

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range..... **£40.95**

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range..... **£40.95**

QSLX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m..... **£35.95**

QRX 180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as pre-built and aligned module ready to connect on board so no difficulty setting up. Output to headphones. 60mm x 75mm. 9V operation..... **£60.95**

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send Sterling Bank Draft and add £5.00 per order for shipment. Credit card orders welcomed on 01827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

★★★ Specials ★★★

DLTX/DLTX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way d.i.l. switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits)..... **£50.95**
Individual Transmitter DLTX..... **£19.95**
Individual Receiver DLRX..... **£37.95**

MRX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle.

Size 27mm x 60mm. 9V operation. 250m range..... **£20.95**

**SUMA
DESIGNS**

**DEPT. EE
THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY, NEAR ATHERSTONE,
WARWICKSHIRE CV9 2LE**

VISITORS STRICTLY BY APPOINTMENT ONLY




**Tel/Fax:
01827 714476**

ELECTRONICS PRINCIPLES 3.0


For Windows 3.1, '95 or NT.

If you are looking for a means of improving your knowledge of electronics then this is the software for you.

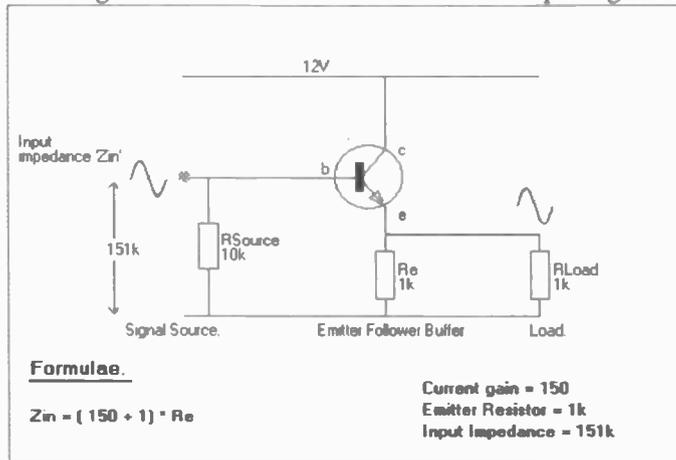Electronics Principles 3.0 now contains an extended range of fully interactive analogue and digital electronics topics, including the GCSE Electronics software in one package.



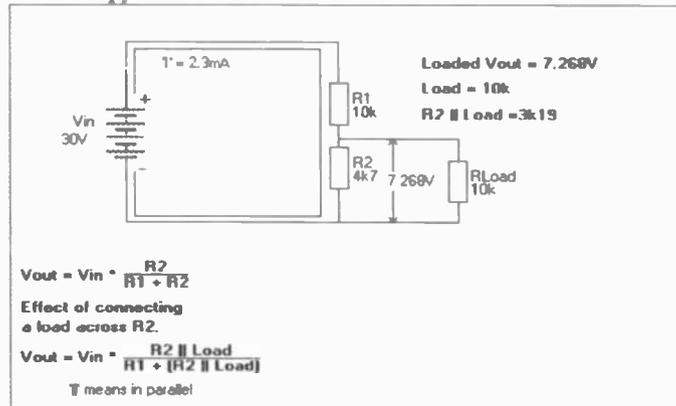
The software is completely self-contained, explanatory text and calculations are laid out in additional Windows, enabling you to see the effect of changing component values, one-at-a-time within the formulae. Graphics, text and calculations can be 'pasted', in colour into text documents for a hard copy reference.



Analogue topics, range from simple dc current flow through a conductor to complex number ac arithmetic, including bi-polar, FET transistors and Op-Amps. Digital investigation, from simple logic gates to binary arithmetic and number conversion using counters and shift registers.

Teaching Electronics & Mathematics? Our software is currently used in hundreds of UK and overseas schools & colleges to support GCSE, A level, BTEC, City & Guilds, Degree level foundation courses and a range of NVQ's and GNVQ's where students are required to have an understanding of electronics & mathematics principles.

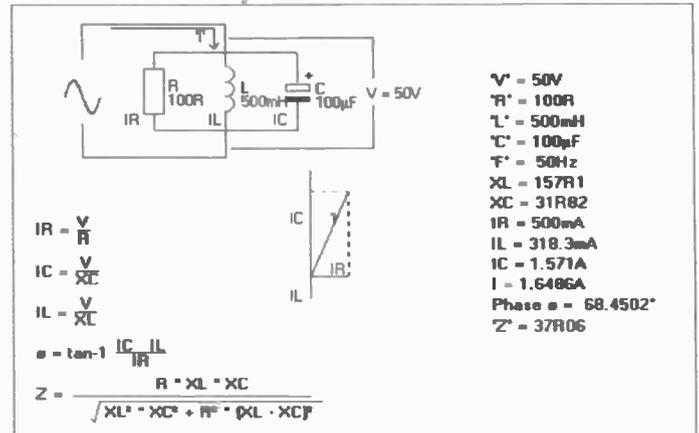'Copy to Clipboard' feature enables preparation of lecture overheads in colour, modify or expand the text to produce your own handouts or study notes.



Complete package still only **£49.95**

Also available as DOS version 2.1


ELECTRONICS TOOLBOX 3.0

A Windows version of the popular Toolbox Software.

Presents commonly used electronics formulae and routines in a way that makes calculations easy, thus encouraging experimentation in circuit design. Just select the topic, 'pop' in your values and find the result. **Only £19.95.**

MATHEMATICS PRINCIPLES 3.0

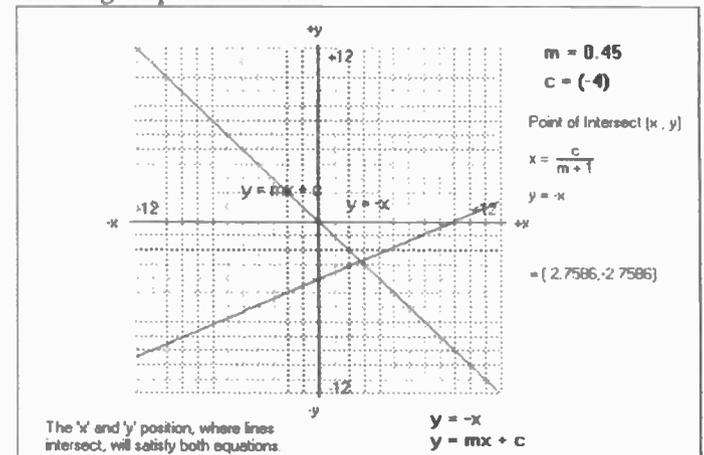An easy to use Windows package including GCSE course syllabus, enabling you to study or revise in what we believe is an interesting and enjoyable way. There are nearly two hundred mathematics topics with interactive, full colour graphics, enabling a "learning through doing" approach to encourage experimentation.



Mathematics topics, range from Number and Number Conversion, Using Numbers and Co-ordinates, Working with Fractions, Lines, Angles and Scaling, Shapes, Area and Volume, Circles, Area and Angles, Laws, Rules and Algebra, Powers, Indices, Linear Equations, Slope, Graphs and Trigonometry, Statistics, Vectors, Curves and Matrices. As used in many schools throughout the UK. **Only £49.95.**

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ. Tel/Fax: 01376 514008.

E-Mail Address, Sales@eptsoft.demon.co.uk Web pages <http://www.octacon.co.uk/ext/ept/software.htm>

For software only add £2 per order for UK post and packing. Make cheques payable to EPT Educational Software.

Switch. Visa and Mastercard orders accepted - please give card number and expiry date.


OVERSEAS ORDERS: Add £2.50 postage for countries in the EEC. Outside EEC add £3.50 for airmail postage.

PROTEUS

For DOS and Windows 3.1, 95 & NT

The Complete Electronics Design System - Now With RIP-UP & RETRY!

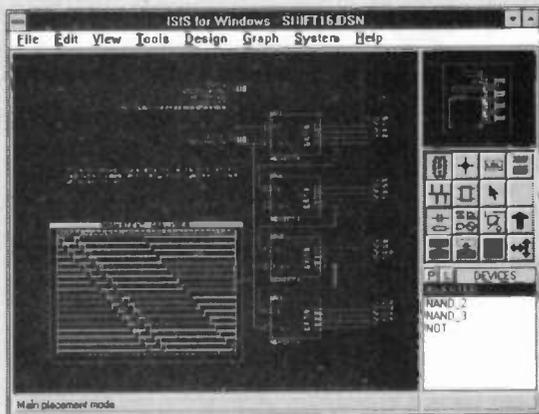NEW LOW PRICE OPTIONS AVAILABLE
Level 1 (500 pins) from £250
Level 2 (1000 pins) from £495
Level 3 (unlimited) from £995




Schematic Capture

- Easy to Use Graphical Interface under both DOS and Windows.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and



Simulation

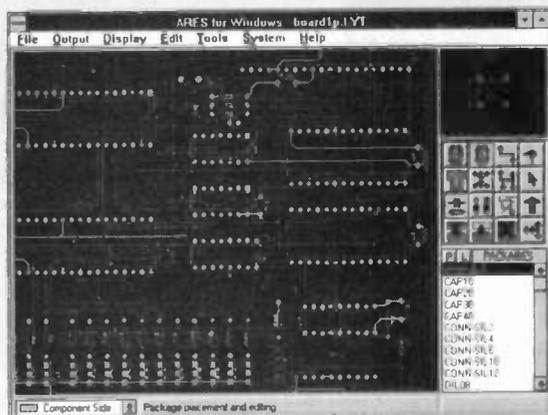- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



PCB Design

- 32 bit high resolution database.
- Multi-Layer and SMT support.
- Full DRC and Connectivity Checking.
- RIP-UP & RETRY Autorouter.
- Shape based gridless power planes.
- Output to printers, plotters, Postscript, Gerber, DXF and clipboard.
- Gerber and DXF Import capability.

labcenter
Electronics

Call now for your free demo disk
or ask about the full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857.
53-55 Main St, Grassington. BD23 5AA.

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

EMAIL: info@labcenter.co.uk
WWW: <http://www.labcenter.co.uk>



MAIL ORDER ONLY ● CALLERS BY APPOINTMENT

**EPE MICROCONTROLLER
PI. TREASURE HUNTER**

The latest MAGENTA DESIGN - highly stable & sensitive - with MC control of all timing functions and advanced pulse separation techniques.

- New circuit design 1994
- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



● Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847.....£63.95

DIGITAL LCD THERMOSTAT

A versatile thermostat using a thermistor probe and having an l.c.d. display. MIN/MAX memories, -10 to 110 degrees celsius, or can be set to read in Fahrenheit. Individually settable upper and lower switching temperatures allow close control, or alternatively allow a wide 'dead band' to be set which can result in substantial energy savings when used with domestic hot water systems. Ideal for greenhouse ventilation or heating control, aquaria, home brewing, etc. Mains powered, 10A SPCO relay output. Punched and printed case.

KIT 841.....£29.95

**PORTABLE ULTRASONIC
PEsT SCARER**

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56

**DIGITAL CAPACITANCE
METER**

A really professional looking project. Kit is supplied with a punched and printed front panel, case, p.c.b. and all components. Quartz controlled accuracy of 1%. Large clear 5 digit display and high speed operation. Ideal for beginners - as the µF, nF and pF ranges give clear unambiguous read out of marked and unmarked capacitors from a few pF up to thousands of µF.

KIT 493.....£39.95

ACOUSTIC PROBE

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches, and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers, and nosey parkers!

KIT 740.....£19.98

WINDICATOR

A novel wind speed indicator with LED read-out. Kit comes complete with sensor cups, and weatherproof sensing head. Mainspower unit £5.99 extra.


KIT 856.....£28.00

**BUCCANEER I.B.
METAL DETECTOR**

An Induction Balance (I.B.) detector with audible output. Providing good sensitivity and easy construction. COMPLETE KIT - INCLUDES ALL HARDWARE, HANDLE, SEARCH HEAD, PCB etc.

CIRCUIT REJECTS IRON WHILST PICKING UP GOLD, SILVER, COPPER etc. A SOLID RELIABLE DESIGN.

KIT 719.....£54.99

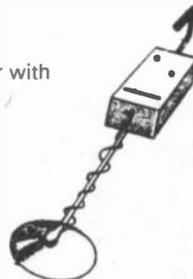

**1000V & 500V INSULATION
TESTER**

Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms. Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.


KIT 848.....£32.95



**MOSFET MkII VARIABLE BENCH
POWER SUPPLY 0-25V 2.5A.**

Based on our MkI design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.

KIT 845.....£64.95

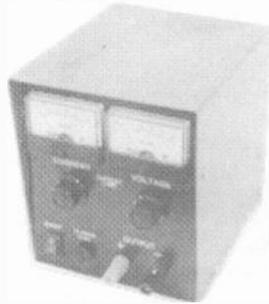

ULTRASONIC PEsT SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS

- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812.....£14.81



SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube + instructions for message loading.

KIT 849.....£16.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790.....£28.51

**MOSFET 25V 2.5A
POWER SUPPLY**

High performance design has made this one of our classic kits. Two panel meters indicate Volts and Amps. Variable from 0-25 Volts and current limit control from 0-2.5A. Rugged power MOSFET output stage. Toroidal mains transformer.

KIT 769.....£56.82

INSULATION TESTER

A reliable and neat electronic tester which checks insulation resistance of wiring and appliances etc., at 500 Volts. The unit is battery powered, simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. A very popular college project.

KIT 444.....£22.37

DIGITAL COMBINATION LOCK

Digital lock with 12 key keypad. Entering a four digit code operates a 250V 16A relay. A special anti-tamper circuit permits the relay board to be mounted remotely. Ideal car immobiliser, operates from 12V. Drilled case, brushed aluminium keypad.

KIT 840.....£19.86

**E.E. TREASURE HUNTER
PI. METAL DETECTOR
MKI**

Magenta's highly developed & acclaimed design. Quartz crystal controlled circuit MOSFET coil drive. D.C. coupled amplification. Full kit includes PCB, handle, case & search coil.

- KIT INC. HEADPHONES
- EFFICIENT CMOS DESIGN
- POWERFUL COIL DRIVE

- DETECTS FERROUS AND NON-FERROUS METAL - GOLD, SILVER, COPPER ETC.


- 190mm SEARCH COIL
- NO 'GROUND EFFECT'

KIT 815.....£45.95



DOLBY PRO-LOGIC DECODER

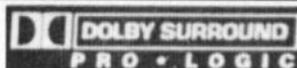Experience the delight of SURROUND SOUND in your own home. This project brings full Genuine PRO-LOGIC surround sound to you at a fantastic price. The circuit meets all 'Dolby' specifications, with "Stereo", "3-Stereo" and "Surround Sound" selections. Exactly as described in this booklet.



For minimum cost the "Short Form Kit" is ideal. This is complete except for the case and power transformer. It includes the switches, sockets, and pots, and is ideal for building into a custom set-up with pre-amp and power-amp modules, where power is available.



The alternative "Full Kit" gives the best value option. With a printed front panel, punched rear panel, power transformer and mains lead and black brushed aluminium knobs. This kit produces a complete stand-alone decoder that can be used with any audio.

Short Form KIT, Kit Ref: 858 £99.00

*DOLBY and the double D symbol are trademarks.

Kit with case and transformer, Kit Ref: 869 £124.99

DC Motor/Gearboxes

Our Popular and Versatile DC motor/Gearbox sets. Ideal for Models, Robots, Buggies etc. 1-5 to 4-5V Multi ratio gearbox gives wide range of speeds.

LARGE TYPE - MGL £6.95
SMALL - MGS - £4.77



Stepping Motors

MD38...Mini 48 step...£8.65
MD35...Std 48 step...£12.98
MD200...200 step...£16.80
MD24...Large 200 step...£22.95



SIMPLE PIC PROGRAMMER

INCREDIBLE LOW PRICE!

Kit 857 **£12.99**

INCLUDES 1-PIC16C84 CHIP SOFTWARE DISK, LEAD CONNECTOR, PROFESSIONAL PC BOARD & INSTRUCTIONS

Power Supply £3.99

EXTRA CHIPS:
PIC 16C84 £7.36

Based on the design in February '96 EPE Article Magenta have made a proper PCB and kit for this project. PCB has 'reset' switch, Program switch, 5V regulator and test L.E.D.s. There are also extra connection points for access to all A and B port pins.

PIC16C84 LCD DISPLAY DRIVER

INCLUDES 1-PIC16C84 WITH DEMO PROGRAM SOFTWARE DISK, PCB, INSTRUCTIONS AND 16 CHARACTER 2 LINE LCD DISPLAY

Kit 860 **£17.99**

Power Supply £3.99

FULL PROGRAM SOURCE CODE SUPPLIED - DEVELOP YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2 LINE x 16 character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers - Just waiting for your application!

★ Chip is pre-programmed with demo display ★

SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS™ SOFTWARE
- PIC16CXX AND 16C84
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED PIN SOCKETS FOR 18, 28, AND 40 PIN ICs.

NEW!

• SEND FOR DETAILED INFORMATION - A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply £3.99

PIC STEPPING MOTOR DRIVER

INCLUDES: PCB, PIC16C84 WITH DEMO PROGRAM, SOFTWARE DISK, INSTRUCTIONS AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED. ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS.

NEW!


Another NEW Magenta PIC project. Drives any 4 phase unipolar motor - up to 24V and 1 amp. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

PIC16C5x

- IN-CIRCUIT SIMULATOR
- POWERFUL ON-LINE MONITOR
- SINGLE STEP, DISPLAY REGISTERS, MEMORY, AND I/O, READ & PROGRAM
- SUPPORTS PIC16C54, 55, 56, & 57.
- FULL SOFTWARE & DATA SUPPLIED
- THE IDEAL SYSTEM FOR EDUCATIONAL USERS

DEVELOPMENT AND TRAINING SYSTEM

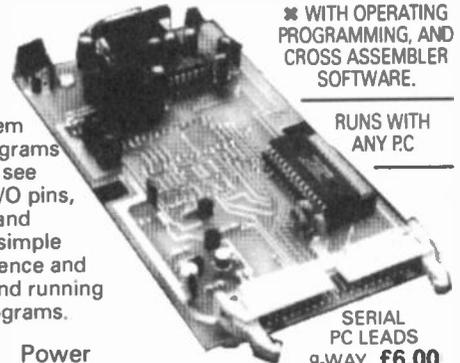The easiest way to get started with PIC Microchips. This system allows you to test programs one line at a time and see what happens to the I/O pins, the internal registers and memory. From these simple steps you gain experience and soon will be writing and running longer and longer programs.



✳ WITH OPERATING PROGRAMMING, AND CROSS ASSEMBLER SOFTWARE.

RUNS WITH ANY PC


Kit 853 **£99.00**

Power Supply £8.99

SERIAL PC LEADS
9-WAY **£6.00**
25-WAY **£7.00**

68000 DEVELOPMENT AND TRAINING SYSTEM

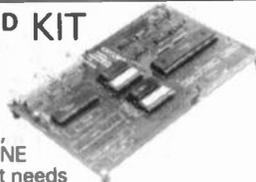Never before at this price! Our own 68000 board kit. Used all over the world in schools and universities. Double Eurocard PCB with RAM, ROM, and I/O. Full featured MONITOR and LINE BY LINE ASSEMBLER ON BOARD. Just needs power, and a serial link to your PC. Supplied with full data and applications course. Use to learn, or as a stand-alone computer board.



INCLUDES SOFTWARE

£55.00!

POWER SUPPLY +5V, +12V, -12V: £12.99 Kit Ref 601

NEW!

SUPER BAT DETECTOR

- 1 WATT OUTPUT
- BUILT IN SPEAKER
- COMPACT CASE
- 20-140kHz
- NEW DESIGN WITH NEW 40kHz MICROPHONE

A new circuit using a 'full bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.



KIT 861... **£24.99**


Mini-Lab & Micro Lab Electronics Teach-In 7

As featured in EPE and now published as Teach-In 7. All parts are supplied by Magenta. Teach-In 7 is £3.95 from us or EPE Full Mini Lab Kit - £119.95 - Power supply extra - £22.55 Full Micro Lab Kit - £155.95 Built Micro Lab - £189.95

MAGENTA

Tel: 01283 565435 Fax: 01283 546932

All prices include VAT.
Add £3.00 p&p.

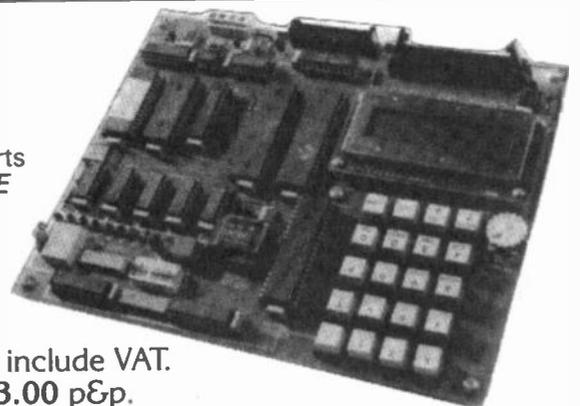

Tel (0191) 251 4363
 Fax (0191) 252 2296
ESR
 ELECTRONIC COMPONENTS
 Station Road, Cullercoats,
 Tyne & Wear
 NE30 4PQ
 U.K.

See Next / Last Months Ad. for
ELECTRONIC COMPONENTS

DIL Sockets

8 Pin DIL 0.3"	£0.07
14 Pin DIL 0.3"	£0.11
16 Pin DIL 0.3"	£0.15
18 Pin DIL 0.3"	£0.15
20 Pin DIL 0.3"	£0.16
24 Pin DIL 0.6"	£0.13
28 Pin DIL 0.6"	£0.22
40 Pin DIL 0.6"	£0.25

Turned Pin

8 Pin DIL 0.3"	£0.15
14 Pin DIL 0.3"	£0.27
16 Pin DIL 0.3"	£0.31
18 Pin DIL 0.3"	£0.35
20 Pin DIL 0.3"	£0.39
24 Pin DIL 0.6"	£0.46
28 Pin DIL 0.6"	£0.41
40 Pin DIL 0.6"	£0.78

SIL Header Strip

1 x 36 Way Straight	£0.38
2 x 36 Way Straight	£0.72
1 x 36 Way 90°	£0.55
2 x 36 Way 90°	£0.78
20 Way Socket Strip	£0.54

Transistor Sockets

T018-4 Base Socket	£0.24
T05 Base Socket	£0.24

IDC Cable Sockets

10 Way Socket	£0.23
14 Way Socket	£0.34
16 Way Socket	£0.31
20 Way Socket	£0.26
26 Way Socket	£0.30
34 Way Socket	£0.42
40 Way Socket	£0.66
50 Way Socket	£0.75

PCB Box Headers

10 Way Straight	£0.27
14 Way Straight	£0.36
16 Way Straight	£0.36
20 Way Straight	£0.41
26 Way Straight	£0.49
34 Way Straight	£0.52
40 Way Straight	£0.96
50 Way Straight	£0.96
10 Way 90°	£0.36
16 Way 90°	£0.47
20 Way 90°	£0.53
26 Way 90°	£0.58
34 Way 90°	£0.72
40 Way 90°	£0.83
50 Way 90°	£0.99

PCB Latch Headers

10 Way Straight	£0.50
16 Way Straight	£0.70
20 Way Straight	£0.78
26 Way Straight	£1.00
34 Way Straight	£0.86
40 Way Straight	£1.56
50 Way Straight	£1.29
10 Way 90°	£0.58
16 Way 90°	£0.78
20 Way 90°	£0.82
26 Way 90°	£1.06
34 Way 90°	£1.14
40 Way 90°	£1.64
50 Way 90°	£1.74

DIL Headers

14 Way DIL	£0.54
16 Way DIL	£0.59
24 Way DIL	£0.90
40 Way DIL	£1.02

Transistor Headers

10 Way Transistor	£0.49
14 Way Transistor	£0.47
16 Way Transistor	£0.47
20 Way Transistor	£0.54
26 Way Transistor	£0.62
34 Way Transistor	£0.67
40 Way Transistor	£0.90
50 Way Transistor	£1.02

D Type Connectors

Solder Bucket	£0.29
9 Way Male Plug	£0.30
9 Way Female Socket	£0.30
15 Way Male Plug	£0.39
15 Way Female Socket	£0.39
15 Way H.D. Plug	£0.49
15 Way H.D. Socket	£0.96
23 Way Male Plug	£0.49
23 Way Female Socket	£0.49
25 Way Male Plug	£0.48
25 Way Female Plug	£0.50
IDC Ribbon Mounting	
9 Way Male Plug	£1.20
9 Way Female Socket	£1.20
25 Way Male Plug	£1.26
25 Way Female Socket	£1.26

Right Angled PCB Mounting

9 Way Male Plug	£0.37
9 Way Female Socket	£0.35
25 Way Male Plug	£0.53
25 Way Female Socket	£0.51
Plastic D Covers	
9 Way Cover - Grey	£0.30
15 Way Cover - Grey	£0.33
23 Way Cover - Grey	£0.36
23 Way Cover - Black	£0.36
25 Way Cover - Grey	£0.36
25 Way D Cover - Black	£0.36
9 to 9 Cover / Case	£0.96
25 to 25 Cover / Case	£0.86
9 to 25 Cover / Case	£0.96

Audio Connectors

2.5mm Jack Plug	£0.21
2.5mm Line Socket	£0.16
3.5mm Chassis Socket	£0.09
3.5mm Mono Plug	£0.24
3.5mm Mono Line Skt	£0.30
3.5mm Mono Chassis Skt	£0.14
3.5mm Stereo Plug	£0.33
3.5mm Stereo Line Skt	£0.37
3.5mm Stereo Chassis Skt	£0.34
1/2" Mono Plug	£0.30
1/2" Mono Line Socket	£0.35
1/2" Mono Chassis Socket	£0.40
1/2" Stereo Plug	£0.40
1/2" Stereo Line Socket	£0.38
1/2" Stereo Chassis Skt	£0.44
DIN Series	
2 Pin Line Plug	£0.18
2 Pin Chassis Socket	£0.15
3 Pin Line Plug	£0.27
3 Pin Chassis Socket	£0.28
4 Pin Line Plug	£0.24
4 Pin Chassis Socket	£0.26
5 Pin Line Plug 180°	£0.26
5 Pin Chassis Skt 180°	£0.32
5 Pin Line Plug 240°	£0.24
5 Pin Chassis Skt 240°	£0.32
5 Pin Line Plug 360°	£0.24
5 Pin Chassis Skt 360°	£0.32
6 Pin Line Plug	£0.22
6 Pin Chassis Socket	£0.32
7 Pin Line Plug	£0.34
7 Pin Chassis Socket	£0.34
8 Pin Line Plug	£0.35
8 Pin Chassis Socket	£0.36

Phono Series

Red Line Plug	£0.20
Black Line Plug	£0.20
Yellow Line Plug	£0.20
White Line Plug	£0.20
Red Line Socket	£0.20
Black Line Socket	£0.20
Yellow Line Socket	£0.20
White Line Socket	£0.20
Red Chassis Socket	£0.20
Black Chassis Socket	£0.20
Gold Plated Plug - Red	£0.64
Gold Plated Plug - Black	£0.64

XLR Series - metal

3 Pin Line Plug	£1.36
3 Pin Line Socket	£1.64
3 Pin Chassis Plug	£1.36
3 Pin Chassis Socket	£1.70

RF Connectors

BNC Plug 50Ω Solder	£0.93
BNC Plug 50Ω Crimp	£0.56
BNC Plug 75Ω Solder	£0.96
BNC Plug 75Ω Crimp	£0.70
BNC Chassis Socket	£0.80
F Plug - Twist	£0.27
F Plug - Crimp	£0.30
TNC Plug Solder	£1.20
TNC Plug Crimp	£0.78
UHf Plug 5mm Cable	£0.72
UHf Plug 11mm Cable	£0.66
UHf Chassis Skt - Sqr	£0.45
UHf Chassis Skt - Rnd	£0.58

Terminals

All Available in - Red, Black, Green, Blue, White or Yellow	
2mm Solder Plugs	£0.18
2mm Chassis Sockets	£0.20
4mm Solder Plugs	£0.30
4mm Stackable Plugs	£0.40
4mm Chassis Sockets	£0.23
4mm Binding Posts	£0.54
33mm Crocodile Clips	£0.13

Power Connectors

DC Low Voltage	
DC Plug 7.0ID, 2.35OD	£0.46
DC Plug 1.3ID, 3.4OD	£0.32
DC Plug 1.7ID, 4.0OD	£0.46
DC Plug 1.7ID, 4.75OD	£0.46
DC Plug 2.1ID, 5.0OD	£0.24
DC Plug 2.5ID, 5.0OD	£0.24
DC Plug 3.1ID, 6.3OD	£0.46
DC Line Socket 2.1mm	£0.50
DC Line Socket 2.5mm	£0.50
DC Chassis Skt 2.1mm	£0.46
DC Chassis Skt 2.5mm	£0.46
IEC Mains 6A 250Vac	



3 Pin IEC Line Socket	£0.96
3 Pin IEC Line Plug	£1.83
3 Pin Chassis Socket	£0.56
3 Pin Chassis Plug	£0.72

8 Way Bulgin

8 Pin Line Plug P551	£3.93
8 Pin Chassis Skt P552	£1.25

Toggle Switches

Sub-Minature	
3A 125V 1A 250V	
5mm Ø Mounting Hole	
SPST 5 x 10mm	£0.58
SPDT 5 x 10mm	£0.60
SPDT C/OIF 5 x 10mm	£0.86
SPDT 9.2 x 10mm	£0.66
Miniature	
6A 125V 3A 250V	
6.2mm Ø Mounting Hole	
SPST 8 x 13mm	£0.66
SPDT 8 x 13mm	£0.60
SPDT C/OIF 8 x 13mm	£0.64
SPDT C/O Biased 2 way	£1.04
SPDT C/O Biased 1 way	£1.04
DPDT 12 x 13mm	£0.72
DPDT C/OIF 12 x 13mm	£0.76
DPDT C/O Biased 2 way	£1.28
DPDT C/O Biased 1 way	£1.28
Standard	
10A 250V Push on terminals	
11mm Ø Mounting Hole	
SPST 18 x 30mm	£1.14
SPDT 18 x 30mm	£1.28
SPDT C/OIF 18 x 30mm	£1.52
DPDT 21 x 30mm	£1.60
DPDT C/OIF 21 x 30mm	£1.78

Slide Switches

Miniature	
300mA 125V	
7 x 15mm Mounting Hole	
DPDT 7 x 23mm	£0.15
Standard	
5.5 x 12mm Mounting Hole	
DPDT 12.5 x 35mm	£0.24
DPDT C/O 12.5 x 35mm	£0.27

Rotary Switches

150mA 250V	
Make before Break 22mm Ø	
9.8mm Ø Mounting Hole	
1 Pole 12 Way	£0.84
2 Pole 6 Way	£0.84
3 Pole 4 Way	£0.84
4 Pole 3 Way	£0.84

Push Switches

Miniature Round	
250mA 125V 2K x 10mm	
7mm Ø Mounting Hole	
Non Latching Push to Make	
Black PTM	£0.25
Red PTM	£0.25
Yellow PTM	£0.25
Green PTM	£0.25
Blue PTM	£0.25
White PTM	£0.25
Non Latching Push to Break	
Black PTB	£0.25
Standard Square	

1A 250V	
39 x 15MM	
12mm Ø Mounting Hole	
Non Latching Push to Make	
Black PTM	£0.57
Red PTM	£0.57
Blue PTM	£0.57
White PTM	£0.57
Latching	
Black	£0.63
Red	£0.63
Blue	£0.63

Rocker Switches

Miniature	
6A 250V Solder Tags	
SPST 21 x 14 x 16mm	£0.63
DPDT 21 x 24 x 22mm	£0.96
Standard	
15A 250V Push on Tags	
SPST 30 x 11 x 22mm	£0.50
DPDT 30 x 25 x 22mm	£1.12
Illuminated	
15A 250V Push on Tags	
SPST 30x14mm Red	£0.84
DPDT 30x25mm Red	£1.40
DPDT 30x25mm Amber	£1.40
DPDT 30x25mm Green	£1.40

Relays

PCB Mounting	
1A 24Vdc DPDT 5V	£1.44
1A 24Vdc DPDT 12V	£1.44
3A 110V SPDT 6V	£0.58
3A 110V SPDT 12V	£0.58
5A 110V SPDT 6V	£0.72
5A 110V SPDT 12V	£0.72
5A 110V DPDT 6V	£0.93
5A 110V DPDT 12V	£0.93
5A 240V DPDT 6V	£1.76
5A 240V DPDT 12V	£1.76
10A 240V SPDT 6V	£1.25
10A 240V SPDT 12V	£1.44
10A 240V SPDT 24V	£1.44

Computer Accessories Adaptors

9M Gender Changer	£2.33
9F Gender Changer	£2.33
25M Gender Changer	£2.71
25F Gender Changer	£2.80
9 Male - 25 Female	£2.51
9 Female - 25 Male	£2.67
9M - 6 Mini Din Male	£2.55
9F - 6 Mini Din Female	£2.55
5M Din - 6F Mini Din	£3.02
5F Din - 6M Mini Din	£2.28
Testers / Patch Boxes	
Mini Tester 7 LEDs	£6.68
Check Tester 18 LEDs	£7.11
Enhanced LED Switches	£5.53
25D Jumper Box M-F	£2.90
25D Patch Box M-F	£7.32
Anti-Static Wrist Strap	£5.30
RS232 Surge Protector	£5.43
Mains Surge Protector	£11.99

Leads & Cables

1.5m Printer Lead	£3.40
5m Printer Lead	£9.38
10m Printer Lead	£12.38
Serial Printer 25M-9F	£4.20
Serial Printer 25M-25F	£4.45
Null Modem 9F-9F	£3.45
Null Modem 25F-25F	£3.63
Null Modem 9&25-9&25	£5.54
Modem Lead 25M-9F	£4.08
Modem Lead 25M-25F	£4.75
Interlink Lead 25F-9F	£6.50
Interlink Lead 25F-25F	£6.50
Interlink Lead 25M-25M	£6.50
Patch Lead 25M-25M	£4.66
Patch Lead 36M-36M	£5.90
Floppy Drive Cable A/B	£4.50
Hard Disk Cable 2xIDE	£2.90
Power Cable 3/2 x 3/2	£1.88
Power Cable 5/2 x 5/2	£2.24
Power Cable 5/2 x 3/2	£2.24
Power Cable 5/2 x 3/2 x 5/2	£2.24
Networking	
BNC T Piece FFF	£2.40
BNC T Piece MFF	£2.40
BNC Coupler F	£1.02
BNC Coupler M	£1.65
BNC Ratchet Crimper	£17.44
RJ45 IDC Plug	£0.39
Thinnet Cable per m	£0.48

Boxes & Cases

Many more sizes available	
75 x 56 x 25mm	£0.88
75 x 51 x 22mm	£0.88
111 x 57 x 22mm	£0.99
79 x 61 x 40mm	£1.47
100 x 76 x 41mm	£1.83
118 x 98 x 45mm	£1.83
150 x 100 x 60mm	£2.51
150 x 80 x 50mm	£2.36

General Purpose Plastic

100 x 50 x 31mm	£2.24
100 x 50 x 25mm	£2.98
112 x 62 x 31mm	£3.55
120 x 65 x 40mm	£4.02
150 x 80 x 50mm	£5.36
121 x 95 x 61mm	£5.99

Diecast Aluminium

133 x 70 x 37mm	£2.08
102 x 102 x 37mm	£1.94
102 x 70 x 37mm	£1.76
133 x 102 x 37mm	£2.19
102 x 63 x 50mm	£1.86
76 x 51 x 25mm	£1.34
152 x 102 x 50mm	£2.90
178	

EVERYDAY PRACTICAL ELECTRONICS

VOL. 25 No. 11 NOVEMBER '96

Editorial Offices:
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
ALLEN HOUSE, EAST BOROUGH, WIMBORNE
DORSET BH21 1PF
Phone: Wimborne (01202) 881749
Fax: (01202) 841692. Due to the cost we cannot reply to orders
or queries by Fax.
E-mail: editorial@epemag.wimborne.co.uk
Web Site: <http://www.epemag.wimborne.co.uk>
See notes on Readers' Enquiries below - we regret lengthy
technical enquiries cannot be answered over the telephone.
Advertisement Offices:
EVERYDAY PRACTICAL ELECTRONICS
ADVERTISEMENTS
HOLLAND WOOD HOUSE, CHURCH LANE
GREAT HOLLAND, ESSEX CO13 0JS
Phone/Fax: (01255) 850596

AMAZING

Amazing, isn't it, that an unusual musical instrument invented in the 1920s is still fascinating and is still exercising the inventiveness of design engineers. One would think that modern technology would easily be able to reproduce the physical and aural intricacies of a seventy year old instrument.

However, Jake Rothman's Theremin article looks briefly at the various designs and the methods used for overcoming the problems. It seems that valves were quite good in some circuits! Of course, they are still the only device used for high power transmitters, etc.

The *EPE Elysian Theremin*, plus its MIDI Interface, represent the top end of our constructional projects in terms of cost and complexity but, because these designs are unique, the circuitry interesting in its own right and we believe, as far as the MIDI Interface is concerned, also represent a world first, then we feel fully justified in providing in-depth details on these designs. They are not for the beginner to electronics construction but should not prove too difficult to build for those with a reasonable level of experience.

FIRST TIME

If you are a relative newcomer to the world of electronics we hope our new *Build Your Own Projects* series will help you take the first steps towards project construction. The series will also provide many hints and tips which will also be of interest to the more experienced reader. We believe it will be highly regarded by everyone involved in electronics.

HELP PLEASE

Finally, I hope you have discovered our Readership Survey question sheet tucked into this issue. Please help us to continue the development of *EPE* by letting us know of your interests, etc. There are also two £75 prizes to be won - see the Survey sheet for details.

Your answers will be *confidential* and only used to help us bring you the magazine you want. Your help would be appreciated.



SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £24. Overseas: £30 standard air service (£47.50 express airmail). Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subscriptions Dept., Allen House,

East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. Subscriptions start with the next available issue. We accept MasterCard or Visa. (For past issues see the *Back Issues* page).

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 post and packing (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). *Normally sent within seven days but please allow 28 days for delivery - more for overseas orders.*

Payment in £ sterling only please. Visa and MasterCard accepted, minimum credit card order £5. Send or phone your card number and card expiry date with your name, address etc.



Editor: MIKE KENWARD

Secretary: PAM BROWN

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Editorial: Wimborne (01202) 881749

Advertisement Manager:
PETER J. MEW, Frinton (01255) 850596

Advertisement Copy Controller:
DEREK NEW, Wimborne (01202) 882299

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope or a self-addressed envelope and international reply coupons. Due to the cost we cannot reply to queries by Fax.**

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that we cannot provide data, or answer queries, on projects that are more than five years old.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.


The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; overseas readers should check local laws.

D.C.-TO-D.C. CONVERTERS

ROBERT PENFOLD

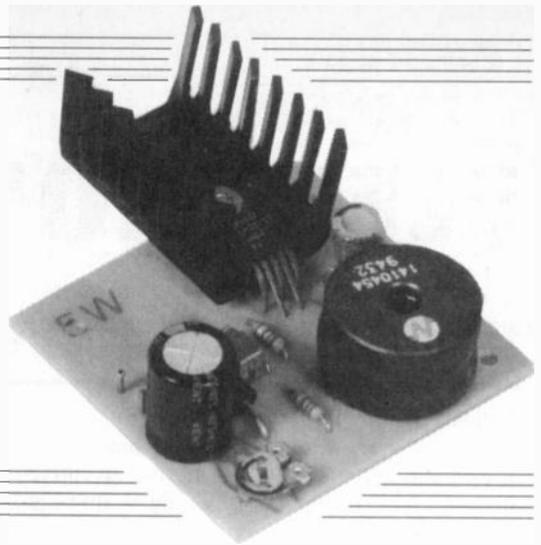

Using modern chips it is no longer difficult to build switch mode power supplies.

TRADITIONALLY, each supply voltage required for a circuit has been provided by what is essentially a separate supply circuit. Some components might be common to more than one supply circuit, such as a tapped mains transformer used to provide two or three output voltages, but there is generally limited scope for this type of thing unless suitable custom components can be produced. For the home constructor this is not usually a practical proposition.

Matters are rather different these days, with switch mode power supplies offering an alternative approach to multi-voltage supplies. There are numerous types of switch mode supply, but the type we are concerned with here are the d.c.-to-d.c. converters.

This kind of supply is a sort of d.c. equivalent to a transformer. Supply voltages can be stepped up or down with an efficiency that is often around 80 to 90 per cent.

CURRENT AFFAIRS

An ordinary series regulator can, of course, provide a voltage step-down, but not with good efficiency. For example, a 5V output is easily produced from a 15V input, but the input current will be slightly

higher than the output current. This results in less than a third of the input power reaching the output, and an efficiency of only about 30 per cent.

Using a switch mode step-down circuit, the input current can be much less than the output current, but, like a transformer, the input power is always more than the output power. With our 15V to 5V example the input current would be one third of the output current with a 100 per cent efficient circuit.

In practice, the input current would probably be closer to half the output current, but this obviously represents a reasonably efficient means of handling things, and a switch mode step-down circuit is far more efficient than a simple series regulator.

A switch mode supply can also provide a voltage step-up, which is something that is not possible using conventional supply circuitry. This begs the question, "is it better to use a low voltage main supply and a step-up circuit, or a high voltage main supply and a step-down circuit?"

The answer depends on the relative output currents of the two supplies. A step-up circuit would normally be used where a high current supply at a low voltage is

needed, plus a lower current supply at a higher voltage.

If the lower voltage supply must provide currents that are similar to, or less than, the currents supplied by the higher voltage supply, it is better to use a normal supply to provide the higher voltage, plus a step-down regulator to provide the lower output potential. In some cases the output currents will be such that either method will work perfectly well. If in doubt, it is probably best to opt for a the step-down approach.


With a step-up regulator, the input current will always be higher than the output current. If we invert our previous 15V to 5V example, a step-up from 5V to 15V is a three-fold increase in voltage. The input current must therefore be at least three times higher than output current, and in practice it would probably be closer to four times as much.

It is essential to bear this in mind when working out the maximum load current on the main supply circuit, particularly when using a large step-up. It is this relatively high input current that makes a voltage step-up generally inappropriate where a high output current is required.

POSITIVELY NEGATIVE

Switch mode power supplies can be used to generate a negative supply from a positive type. Circuits of this type are sometimes referred to as "inverters". In general, this approach is only used where fairly modest output currents are required. The efficiency of practical negative supply

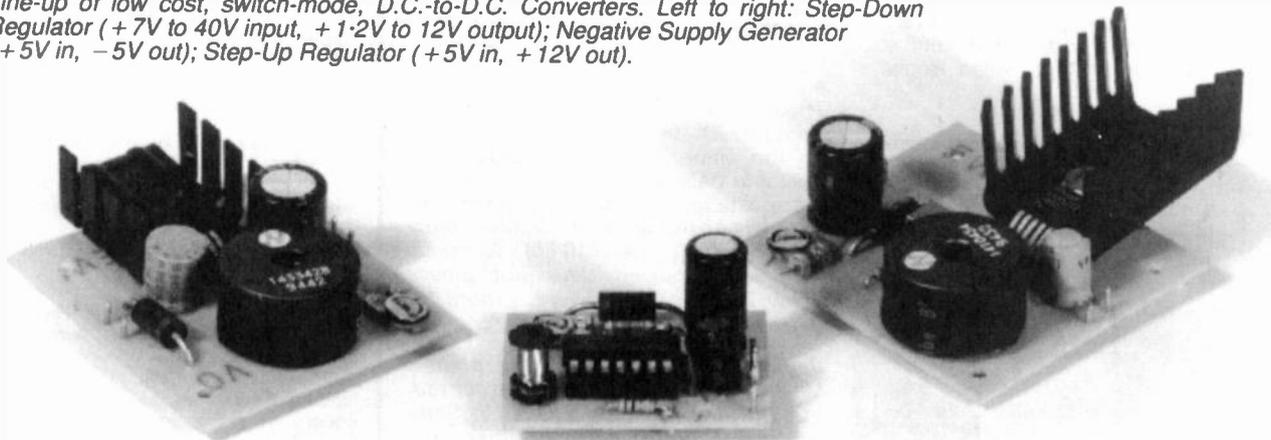Line-up of low cost, switch-mode, D.C.-to-D.C. Converters. Left to right: Step-Down Regulator (+7V to 40V input, +1.2V to 12V output); Negative Supply Generator (+5V in, -5V out); Step-Up Regulator (+5V in, +12V out).



generators tends to be rather less than that of step-up and step-down circuits. In fact it is often under 50 per cent.

This lack of efficiency is not of great importance if output powers of up to a Watt or two are involved, but it makes negative supply generators a less attractive proposition when higher powers are involved. It is not essential for this type of circuit to provide an output voltage that matches the input voltage. A voltage step-up or step-down can be provided as well.

Of course, switch mode circuits are not restricted to use in multi-voltage mains power supply units, and they have many uses in battery powered equipment. For example, a large 5V logic circuit could be powered from a 12V vehicle battery via a simple series regulator, but a step-down regulator could provide the same function with only about half the battery drain.

If it was necessary to power a 24V circuit from a 12V vehicle battery, a step-up regulator would probably be a more practical solution than using an additional battery to provide the boosted supply voltage. An inverter could be used in a project that required dual balanced supplies, so that one rather than two batteries would be needed.

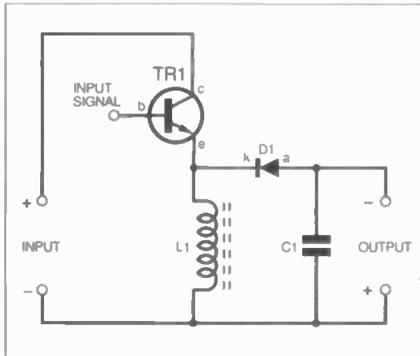


Fig. 1. Circuit diagram for an "inverter" output stage.

SWITCH MODES

All three types of switch mode regulator have an output stage that includes a rectifier, an inductor and a switching transistor. Each form of switch mode power supply uses these in a different configuration. In all three modes the switching transistor is pulsed at what is normally a high audio frequency (about 10 to 20kHz), but which can be a much higher frequency of about 100kHz.

Shown in Fig. 1 is the configuration used in a negative supply generator output stage. The switching transistor TR1 is used in the emitter follower mode, and its load is the inductor L1.

When TR1 is switched on, a current flows through L1 and a magnetic field builds up around it. The magnetic field rapidly collapses when TR1 switches off, and this produces a high reverse voltage across L1.

Due to the speed at which the field collapses, the voltage produced is quite high. In fact, it is likely to be more than ten times the input voltage, but it is at a relatively high impedance. It is this factor that enables a voltage step-up as well as an inversion to be provided.

Diode D1 enables the reverse voltage spikes across L1 to reach the smoothing


capacitor, C1, at the output of the circuit. It blocks any flow of current from C1 back to L1, which would otherwise interfere with the operation of L1 and TR1.

STEPPING-UP

The configuration for a step-up output stage is shown in Fig. 2. This is really just a slightly revamped version of the inverter configuration, with transistor TR1 operating as a common emitter switch that drives the inductor L1.

As before, a high reverse voltage is developed across L1 when TR1 switches off. This means that the top end of L1 is negative, and the bottom end is positive. This results in the voltage across L1 being added to the input voltage, and being fed to smoothing capacitor C1. Note that the polarity of diode D1 has been altered so that it enables this positive voltage to flow to the output, but blocks it from flowing back into TR1 when the transistor is switched on.

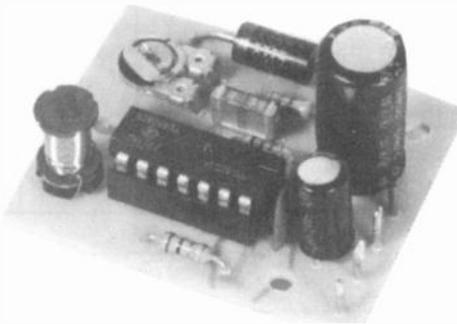Once again, the voltage developed across inductor L1 can be many times higher than the input voltage. This configuration can therefore provide a large voltage boost, and it is not restricted to voltage doubling.



Printed circuit board module for a negative supply or "inverter" generator.

STEPPING DOWN

The configuration for a step-down output stage is shown in Fig. 3. When transistor TR1 is switched on it subjects inductor L1 to a voltage that is virtually equal to the difference between the input and output voltages. Therefore, while TR1 is switched on, a steadily increasing current flows through L1 and into smoothing capacitor C1.

A charge is stored in L1 while TR1 is switched on, and this charge is released when TR1 switches off. The charge is released as the magnetic field around L1 collapses, giving a signal of the opposite polarity to the original signal. In other words, the left hand terminal of L1 is negative, and the right hand terminal is positive.

Diode D1 completes the circuit, and couples the signal from L1 to C1 and any load connected across the output.

The important point here is that the voltage dropped across L1 when TR1 is switched on is not wasted, but is held as a charge which is given up when TR1 is switched off. With an ordinary series regulator, the voltage drop from the input to the output is pure wastage, giving a relatively low level of efficiency. An input current only flows when TR1 is switched

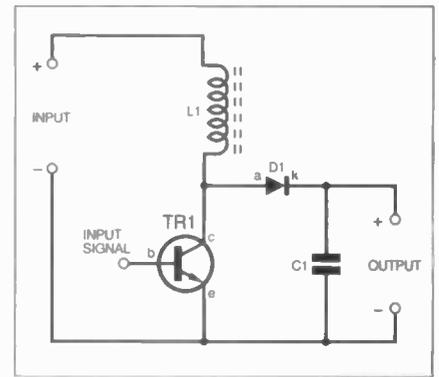


Fig. 2. Basic circuit configuration for a step-up output stage.

on, but a current flows into the output whether it is switched on or off. This factor gives a relatively low input current, and a sort of transformer effect.

A SWITCH IN TIME

There is a problem with a basic switch mode power supply in that the output voltage is not well defined. It is usually necessary to convert from one voltage to another with a fair degree of precision, rather than simply accepting whatever loaded output voltage the circuit happens to produce. It would obviously be possible to use a standard series regulator at the output of a switch mode power supply in order to provide a stable output at the required potential. However, this would greatly reduce the efficiency of the circuit, and is not the normal way that output regulation is tackled.

The more usual approach is to control the output voltage via the switching circuit. This is normally achieved using some form of pulse width modulator (p.w.m.) circuit. A conventional p.w.m. simply consists of a voltage comparator and a clock oscillator, as shown in Fig. 4.

It is essential to the operation of the circuit that the clock oscillator has a reasonably linear triangular output signal. The output of the comparator goes high when the input voltage is greater than the clock voltage, and low when the clock voltage is the higher of the two voltages.

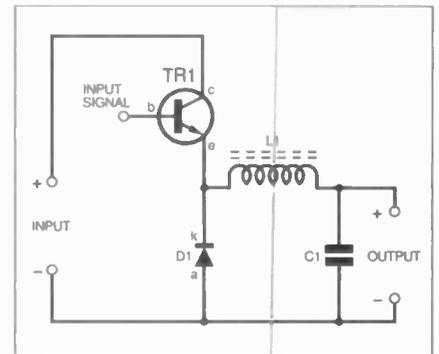


Fig. 3. Basic step-down output circuit.

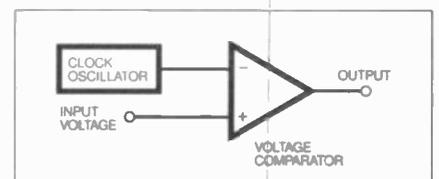


Fig. 4. A p.w.m. can consist of a clock oscillator and voltage comparator.

P.W.M. PROCESS

The waveform diagrams of Fig. 5 help to explain the way in which the pulse width modulation process operates. In each pair of waveforms the upper waveform is the clock signal plus the d.c. input voltage, and the lower waveform is the output from the comparator.

In Fig. 5a the input voltage is half way between the peak positive and negative levels of the clock signal. This gives a squarewave output having a 1-to-1 mark-space ratio. The average output voltage of the comparator is therefore equal to half the supply voltage.

The input voltage has been increased in Fig. 5b, resulting in the input voltage being higher than the clock voltage for the majority of the time. This gives longer output pulses from the comparator, and a higher average output voltage.

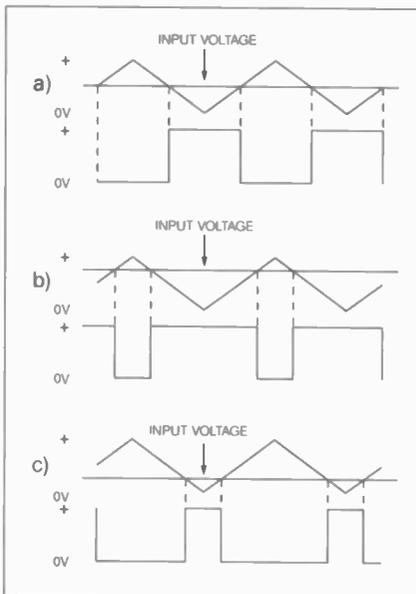


Fig. 5. Example p.w.m. waveforms.

In Fig. 5c the input voltage is quite low, resulting in the clock signal being at the higher voltage for the majority of the time. This gives brief output pulses from the comparator, and a low average output potential.

It should be apparent from this that the average output voltage from the modulator varies in sympathy with changes to the d.c. input level. A d.c. output voltage equal to the average output potential of the modulator can be obtained by feeding the pulsed output signal through a lowpass filter. With this type of modulator the output frequency is fixed, and the output voltage is altered by changing the pulse width of the output signal.

There is an alternative approach which uses a monostable to provide output pulses of fixed duration. The output voltage is controlled by altering the clock frequency. Infrequent triggering of the monostable gives output pulses that are few and far between, and a low average output voltage. Frequent triggering results in the output pulses being bunched close together, which gives a high average output voltage.

The point of controlling the output voltage using pulse width modulation is that it is very efficient. The series transistor that chops the output signal is either switched fully on or fully off. In either case it consumes very little power. There will be

some voltage drop through the transistor when it is switched on, but the voltage drop and resultant power wastage should be quite small. In most cases the regulator and switch mode output stage are combined, which further aids good efficiency.

SWITCH-MODE REGULATOR

In Fig. 6 is shown the simplified block diagram for a practical switch mode regulator. This has obvious similarities to a conventional series regulator, with a differential "error" amplifier, reference generator, and feedback from the output via a potential divider. The circuit is basically just an operational amplifier non-inverting mode amplifier circuit.

NEGATIVE SUPPLY GENERATOR

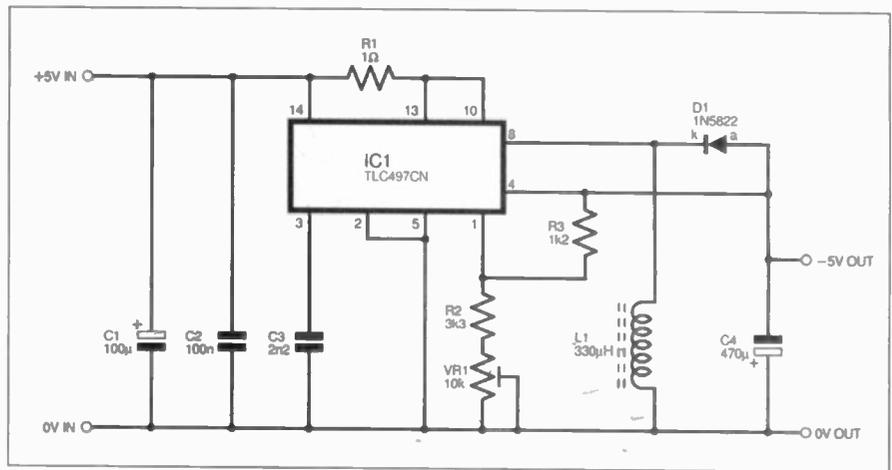


Fig. 7. Practical circuit diagram for a negative supply generator.

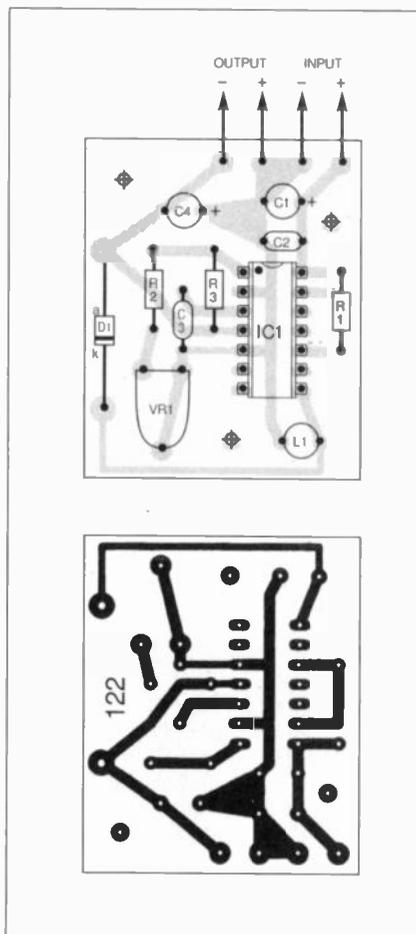


Fig. 8 (left). Inverter module component layout and full size foil master.

COMPONENTS

NEGATIVE SUPPLY GENERATOR

Resistors

R1 1Ω
R2 3k3
R3 1k2
All 0.25W 5% carbon film

See

TALK
Page

Potentiometer

VR1 10k min. preset, horiz

Capacitors

C1 100μ radial elect. 10V
C2 100n ceramic disc
C3 2n2 polyester
C4 470μ radial elect. 10V

Semiconductors

D1 1N5822 Schottky rectifier diode
IC1 TL497CN switch mode p.s.u.

Miscellaneous

L1 330μH inductor (see text)
Printed circuit board, available from the EPE PCB Service, code 122; 14-pin d.i.l. socket; single-sided solder pins; connecting wire; solder, etc.

Approx Cost
Guidance Only

£10

limiting and protection against excessive operating temperatures.

Although switch-mode power supplies offer neat solutions in many situations where awkward supply requirements must be met, they are not without one or two drawbacks. One problem is simply that the chips for use in switch-mode supplies are far more expensive than ordinary series regulator chips. Consequently, they provide neat but not necessarily cheap solutions.

Another point to bear in mind is that circuits of this type oscillate strongly at what is mostly a fairly high audio frequency. This makes them a poor choice for use with many audio circuits, radio circuits, sensitive test gear, or any circuit where stray pickup of the switching signal could be a problem.

PRACTICAL INVERTER

The TL497CN is not exactly the latest thing in switch-mode power supply chips, but it is very useful for applications that do not involve high output currents. In particular, it provides a cost effective means of providing a negative supply of up to about 150 milliamps. A circuit diagram for an Inverter based on this device is shown in Fig. 7.

The efficiency of the circuit is typically a little over 50 per cent with an input potential of 10V, but is significantly under 50 per cent with an input supply of 5V. This is not bad for a simple negative supply generator.

Capacitors C1 and C2 are simply supply decoupling components on the input supply. Resistor R1 is the series resistance in the current limiting circuit at the input to IC1. This is an essential safety feature since the circuit will often be fed from a high current supply that could almost instantly "fry" IC1 in the event of an overload on the device's output.

Capacitor C3 is the timing component in the oscillator section of the p.w.m. The TL497CN uses a fixed pulse width and a variable clock frequency to control the average output voltage.

Many switch-mode supply chips are either unsuitable for use in inverter circuits, or require the use of a discrete switching transistor and other components. The TL497CN works quite well in this mode if its substrate terminal (pin 4) is connected to the negative output rail. The only problem is that its internal diode cannot be used. Accordingly, discrete Schottky rectifier D1 is used instead.

The circuit will actually work using an ordinary rectifier such as a 1N4002, but the lower voltage drop and faster switching speed of a Schottky type result in significantly better efficiency. The circuit's output stage inductor is L1, and capacitor C4 provides output voltage smoothing.

The output voltage is determined by the feedback network which is comprised of preset VR1 plus resistors R2 and R3. The input and output voltages are nominally plus and minus 5V, but the circuit can handle input and output voltages of up to 12V. For input or output voltages of more than 10V, capacitors C1 and (or) C4 should have a voltage rating of 16V rather than the 10V specified in the components list.


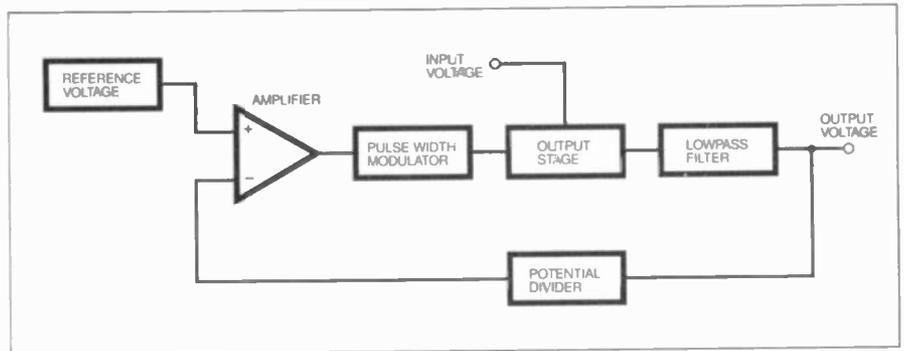


Fig. 6. Simplified block diagram for a switch-mode regulator.

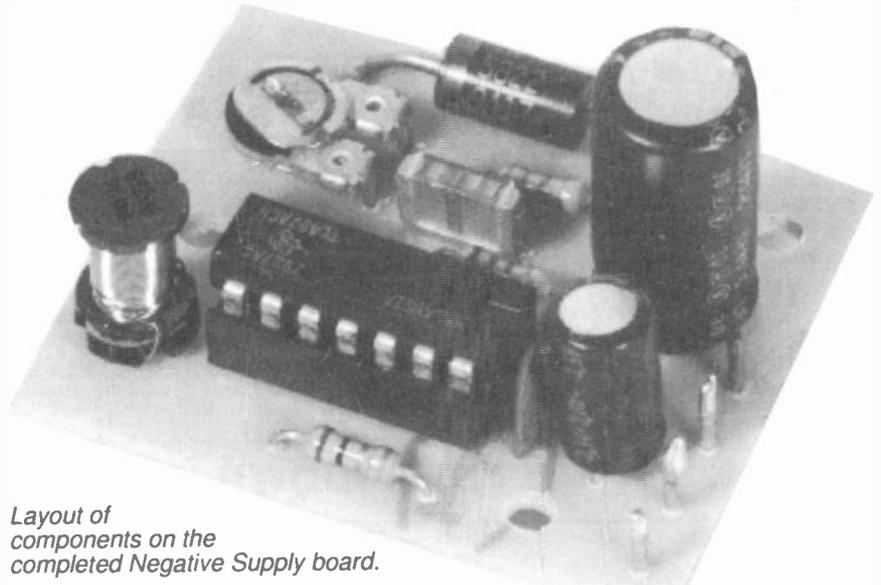

Layout of components on the completed Negative Supply board.

The input and output voltages do not have to be the same, and the circuit can provide a voltage step-up or a step-down. Just use the appropriate supply voltage of between 5V and 12V, and set VR1 for the required output voltage. Of course, the maximum output current is reduced if a voltage step-up is produced. For example, a maximum output current of about 50 milliamps is available with a step-up from +5V to -12V.

CIRCUIT BOARD


Printed circuit board details for the Inverter module are provided in Fig. 8. This board available from the *EPE PCB Service* code 122.

The only point worthy of note is that L1 must be an inductor that is intended for use in a switch mode power supply.

An ordinary r.f. choke will not work properly in this circuit. It must also be a miniature type having 5mm (0.2 inch) lead spacing if it is to fit onto the board properly. The RS type 228-523 is suitable.

STEP-DOWN CIRCUIT

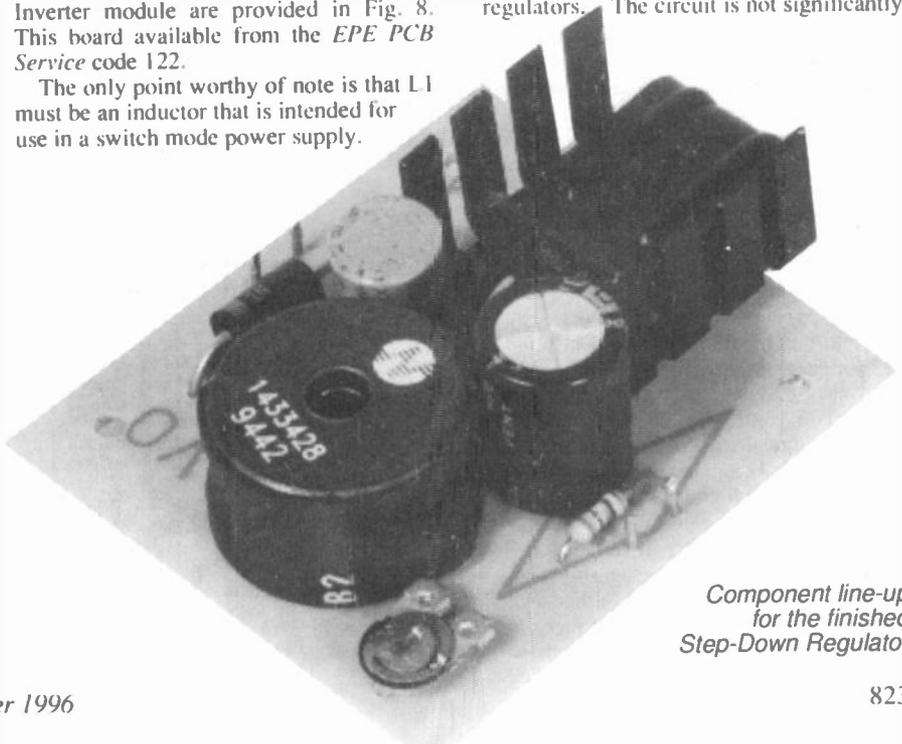A Step-Down Regulator circuit is shown in Fig. 9. It is based on a LM2575T-ADJ, which is a modern device that is intended to make switch-mode regulators almost as straightforward to use as ordinary series regulators. The circuit is not significantly



Component line-up for the finished Step-Down Regulator

more complex than one based on a conventional three or four terminal adjustable regulator.

Capacitor C1 provides supply decoupling at the input of IC1. Pin 5 is a TTL compatible input that is taken high in order to place IC1 in a low current standby mode. In most applications this serves no useful purpose, and pin 5 is connected to "earth" (0V) to hold IC1 in its normal operating mode. Diode D1, inductor L1 and capacitor C2 are a normal step-down mode output stage. Again, a Schottky rectifier is used for the diode, because its lower voltage drop and high operating speed provide much improved efficiency.

REGULATOR

There are several versions of the LM2575T. Some are fixed voltage devices which have a built-in potentiometer at pin 4. Pin 4 is simply connected to the output supply in order to obtain an output potential of 5V, 12V or 15V (depending on the particular version used).

The device used here has an "ADJ" suffix which indicates that it has an adjustable output voltage. Pin 4 connects to the inverting input of the internal error amplifier. This amplifier's non-inverting input is fed from a 1.2V reference source. A discrete potentiometer connected across the output and feeding into pin 4 therefore

enables the output voltage to be set at any realistic figure above 1.2V.

In this case the potentiometer is formed by VR1 in series with resistor R1. The adjustment range provided by VR1 is from 1.2V to a little over 16V. Higher output voltages can be accommodated by making R1 lower in value, but a circuit of this type is mainly used where there is a large voltage difference between the input and the output. Consequently, it is unlikely to be used with output voltages of more than about 16V.

The absolute maximum input voltage is 40V. The step-down circuit would normally be fed from the unregulated side of the main supply, rather than via the main regulator circuit. This avoids having the step-down circuit increase the loading on the main regulator. The only normal exception is where the unregulated supply might exceed the 40V limit for this step-down circuit. The same basic premise applies to the other regulator circuits, incidentally. The maximum output current for the LM2575T-ADJ is one amp.

CONSTRUCTION

The printed circuit board component layout and actual size foil track master for the step-down regulator module are shown in Fig. 10. This board is available from the *EPE PCB Service*, code 123.

As supplied, IC1 has straight leads. They must be carefully bent through right angles and into the appropriate staggered configuration in order to fit IC1 onto the board properly.

The inductor used in the L1 position must be a type intended for operation in switch mode power supplies, and it must also be capable of handling currents of up to 1A. Small radial inductors and r.f. chokes are not suitable. The Maplin 330 μ H "Bobbin Type Inductor" and the virtually identical RS 330 μ H "High Current Inductor Type A" were both found to work well in this circuit.

The RS version has long leadout wires. These must be trimmed short, and then the enamel insulation must be scraped away from the remaining leadouts so that the inductor can be fitted to the board in standard printed circuit mounting fashion.

The efficiency of the circuit is surprisingly high, and seems to be not far short of 90 per cent. With an input potential of 25V, the output set at 5V and a load current of 1A, the input current was only about 225 milliamps.

Due to this high efficiency there is very little power dissipated in the regulator chip. A small clip-on heatsink should be sufficient to ensure that IC1 does not overheat, and in most applications it will not be essential to use a heatsink at all.

STEP-DOWN REGULATOR

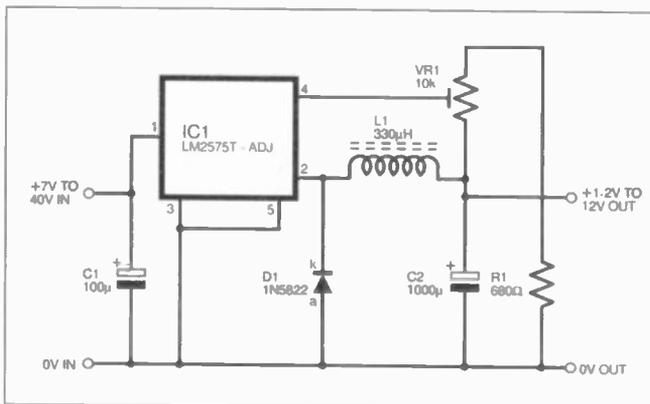


Fig. 9. Step-Down Regulator circuit diagram.

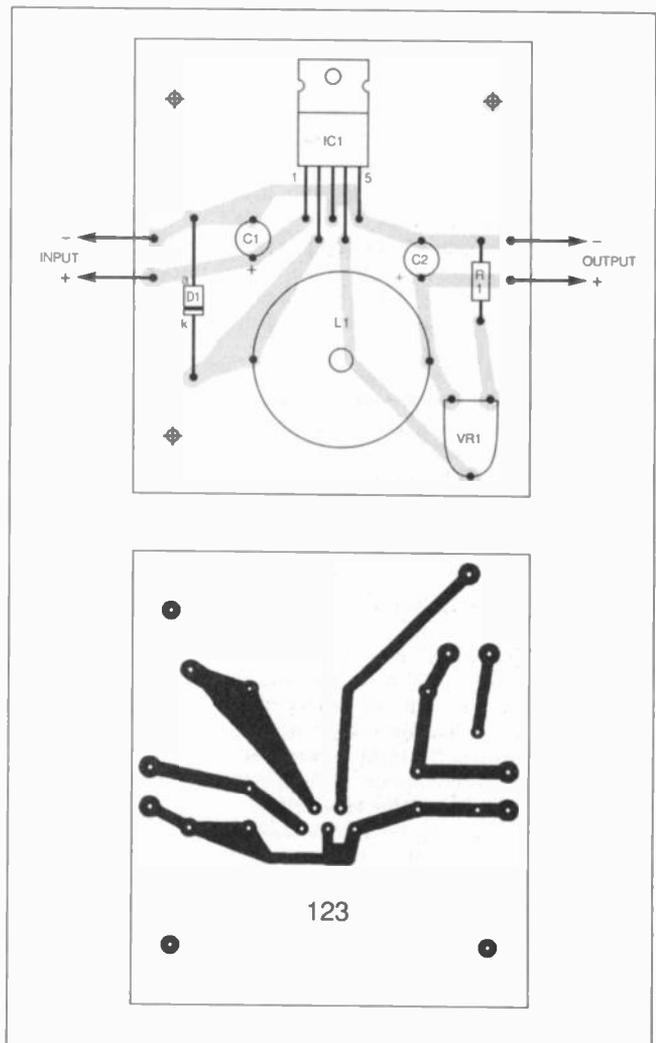


Fig. 10. P.C.B. component layout and foil master.

COMPONENTS

STEP-DOWN REGULATOR

Resistor

R1 680 Ω 0.25W 5% carbon film

Potentiometer

VR1 10k min. preset, horiz

Capacitors

C1 100 μ radial elect. 40V
C2 1000 μ radial elect. 16V

Semiconductors

D1 1N5822 Schottky rectifier diode
IC1 LM2575T-ADJ step-down regulator

Miscellaneous

L1 330 μ H inductor (see text)

Printed circuit board, available from the *EPE PCB Service*, code 123; clip-on TO220 heatsink; single-sided solder pins; connecting wire; solder, etc.

Approx Cost
Guidance Only

£15

STEP-UP REGULATOR

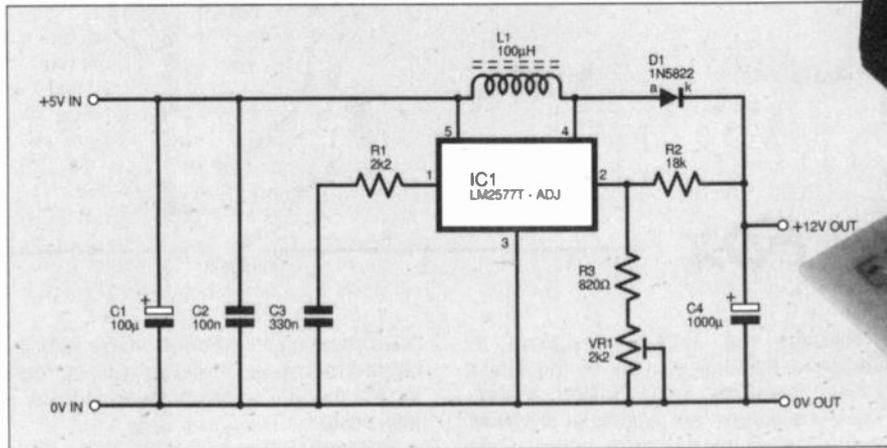


Fig. 11. Complete circuit diagram for the Step-Up Regulator.

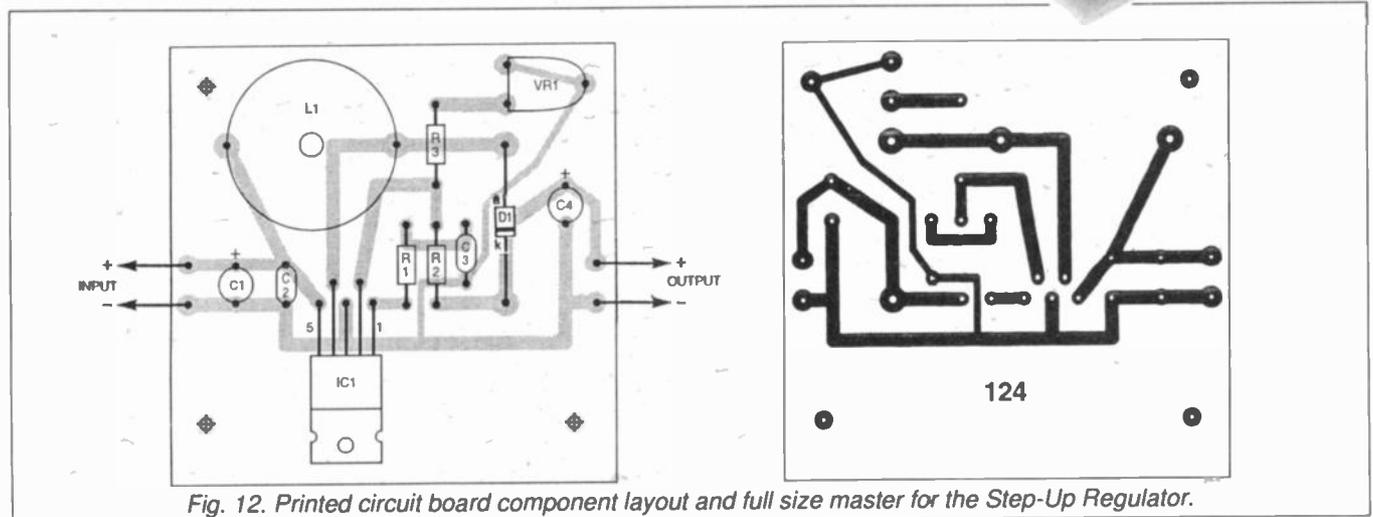
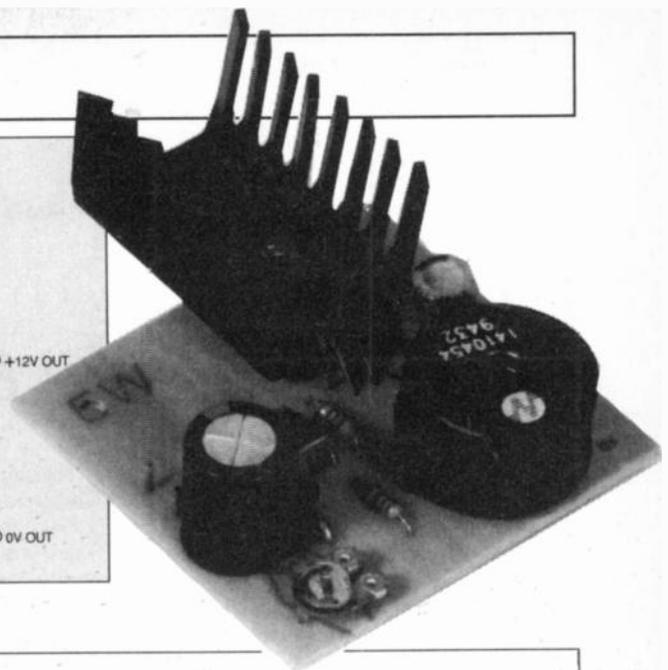


Fig. 12. Printed circuit board component layout and full size master for the Step-Up Regulator.

STEPPING UP

Refer to Fig. 11 for the circuit diagram of the Step-Up Regulator. This circuit is based on an LM2577T-ADJ, which is another chip designed to give a combination of high performance and stark simplicity.

It can provide output currents of up to 3A, and has both over-current and thermal protection circuits built-in. It requires a minimum input potential of 3.5V, and it shuts down automatically if the input voltage is inadequate. The maximum input voltage is 40V.

Capacitors C1 and C2 provide supply decoupling at the input, and C3 plus resistor R1 provide frequency compensation. Inductor L1, diode D1 and an internal switching transistor of IC1 form a standard step-up output stage, with output smoothing provided by capacitor C4. Resistors R2, R3 and preset VR1 form a potential divider that controls the output voltage.

IC1 has an internal 1.2V reference generator and the voltage at pin 2 is therefore stabilised at this figure. With the specified values in the potential divider circuit, the output voltage range is therefore around 9.5V to 25V.

CONSTRUCTION

The printed circuit board details for the Step-Up Regulator appear in Fig. 12. This board is available from the *EPE PCB Service*, code 124.

Inductor L1 can be either a Maplin 100µH "Bobbin Type Inductor", or an RS "High Current Radial Inductor Type A". In the case of the latter the leadouts must be pruned short and have the insulation scraped away before they are connected to the board.

Like the step-down regulator, this circuit achieves a high level of efficiency. The LM2577T has a specified efficiency of 80 per cent, but my tests suggest that a somewhat higher level of efficiency can be achieved. With a 5V to 15V step-up and 400mA drawn from the output, the measured input current was only a fraction over 1.4A. An input current of 1.44A would represent an efficiency of 80 per cent.

Due to this high efficiency, it is not necessary to fit IC1 with a large heatsink. Even when used at high output currents one of the larger bolt-on heatsinks should be perfectly adequate.

FINALLY

Switch mode power supplies have not been particularly popular with home constructors in the past. One probable reason for this is the relative complexity of many switch mode supply circuits. Also, suitable inductors and high speed rectifiers were difficult or impossible to obtain. Using modern devices it is possible to produce simple but efficient switch mode circuits using "off the shelf" components. □

COMPONENTS

STEP-UP REGULATOR

Resistors

R1	2k2
R2	18k
R3	820Ω
All 0.25W 5% carbon film	

Potentiometer

VR1	2k2 min. preset, horiz
-----	------------------------

Capacitors

C1	100µF radial elect. 10V
C2	100nF ceramic disc
C3	330nF polyester
C4	1000µF radial elect. 16V

Semiconductors

D1	1N5822 Schottky rectifier diode
IC1	LM2577T-ADJ step-up regulator

Miscellaneous

L1	100µH inductor (see text)
Printed circuit board, available from <i>EPE PCB Service</i> , code 124; bolt-on TO220 heatsink; single-sided solder pins; connecting wire; solder, etc.	

Approx Cost
Guidance Only

£17

See
**SHOP
TALK**
Page

REPORT

by Barry Fox



Acrimonious Logic

Technology runs on acronyms, snappy little words made up from the first letter of a string of jargon words. Without acronyms, articles would be twice as long. They are also a boon for bluffers who use them to disguise ignorance.

America's TV sets use the NTSC standard, after the "National Television System Committee" that wrote the specification. Many people who have seen North American TV pictures prefer *Never Twice the Same Colour*.

Digital telephone lines use ISDN. Wags say it stands for an *Innovation Subscribers Don't Need*, not the "Integrated Services Digital Network".

RAM is "Random Access Memory" in which users store data. ROM is "Read Only Memory", in which users cannot store data. But a PROM is a "Programmable ROM" which stores data.

An EPROM is an "Erasable PROM" from which the stored data is removed with ultraviolet light. An EEPROM is an "Electrically Erasable PROM" from which the stored data is removed by electricity, much like a RAM.

Rather more logically, WYSIWG describes modern software which lets you print out exactly what is on screen so that "What You See Is What You Get".

Rather less neatly, PITO, the "Police Information Technology Organisation", is now working with NSPIS, the "National Strategy for Police Information Systems", to give bobbies PSRCP, "Public Safety Radio Communication Project", walkie-talkies. Thanks to PITO and NSPIS, cops will also get NAFIS, the "National Automated Fingerprint Identification Service".

In case you are confused, PITO used to be HOSTG, the old "Home Office Science and Technology Group".

Tongue In Cheek

The good news is that some companies now have their tongues in their cheeks.

Apple recently proposed an SVS encryption system for DVD, the new Digital Video Disc. It works on the Something Very Simple principle.

Computer scanners and digital cameras are now usually labelled TWAIN-compatible. This means that TWAIN-compatible software can Acquire image data from the device. TWAIN is a Terminal Which Acquires Information. It really does stand for a Tool Without An Interesting Name.

Perhaps the TWAIN designers in California had visited one of the Napa Valley vineyards near Silicon Valley. There the guides talk proudly of the VBM in the corner of the wine cellar. Only those who ask are let into the trade secret that VBM stands for a "Very Big Machine".

The police, who breed acronyms like rabbits, may even be developing a sense of humour, too. Their catchy names come from the National Strategy for Police Information Systems, otherwise known as NSPIS.

In The Red

Some consumer electronics companies

Frank Confession

Dr Frank Carrubba, Executive Vice-President of Philips, visited the Philips Labs at Redhill in June, to mark fifty years of research in the UK.

He kicked off with a talk on the "Social Trend and Implications of Technology", and showed a video predicting a future full of videophones, video payphones, video cellphones and video answerphones. But do people really need, or want, callers to see whether they have shaved or made up?

The only real consumer use I could see was a kid going to a video payphone and saying "Is this the one you want Mum?" Presumably he was then arrested for shoplifting, having taken the thingy out of the shop to the phone before spending his mother's money.

Carrubba was gloriously frank when asked questions. He admitted that DCC (Digital Compact Cassette) had been a "great product" that failed. "We couldn't get the cost curve down", said Carrubba.

"We listened to the music industry when they said that people wanted to go on using tapes, but with CD quality, and that people would upgrade if the equipment was compatible. We spent a Helluva lot of money and time on making a compatible system with CD quality sound. But the music companies didn't move fast enough."

Now there is a question mark over DVD, the high density Digital Video Disc which Toshiba, Thomson and Panasonic have promised to launch this year.

have resorted to labelling VCRs with the big red message "If all else fails, try reading the manual". The computer industry is less polite.

Internet surfers will often encounter a list of FAQs, answers to the most "Frequently Asked Questions" on technical problems. Anyone who asks a question without bothering to read the FAQs, or looking at the maker's instruction book, can expect the snappy retort RTFM, Read The F***ing Manual.

Now that computer companies are cutting costs by providing no printed manuals, just On-Line help, idle enquirers can expect a new acronym. RTFOLP!

Industry observers believe there is no way it can be ready. So does Carrubba.

"DVD is tricky technology. The format is standardized, that's been put to bed. But now we are battling with the film and music industries. It's very difficult to protect copyright and their lawyers are screaming.

"People are saying they will launch this year. Don't believe it. There will not be a product this year. I'll tell you that. There are too many issues and problems still to be solved."

Sticky Digits

The DVD Consortium and the Hollywood movie studios are trying to agree on a digital encryption system that will stop people copying movie discs and will stop people playing movies discs in countries for which they are not intended (for example, movies are released in the USA ahead of Europe).

The encryption system must be tough enough to resist hackers but not so tough as to fall under an import/export ban because the US government then classifies it as munitions.

Personally, I am more interested in the robustness of the disc. With around seven times the packing density of an ordinary CD, it relies on accurate readout of very small pits.

Although publicists hold the discs aloft in sticky fingers, they never play those discs. The only discs played are very carefully handled, at the extreme edges, by engineers.

The general public has sticky fingers.

FREE 32
page full colour
Computer
Equipment
Catalogue

with the Winter 96/97
Cirkit Catalogue

STILL ONLY

£1.95

& 30p p+p



The Winter 96/97 Edition brings you:

- ▶ Even further additions to the Computer section extending our range of PC components and accessories at unbeatable prices.
- ▶ 100's of new products including; Books, Connectors, Entertainment, Test Equipment and Tools.
- ▶ New Speakers, Mixers and In-Car Amplifiers in the Entertainment section.
- ▶ £25 worth discount vouchers.
- ▶ 248 Page main Catalogue, plus 32 Page full Colour Computer Catalogue, incorporating 24 Sections with over 4000 Products from some of the Worlds Finest Manufacturers.
- ▶ Available at WH Smith, John Menzies and most large newsagents, or directly from Cirkit.
- ▶ **Get your copy today!**

WIN!
a **28,800**
Fax Modem



in our easy
to enter
competition

Cirkit


Cirkit Distribution Ltd

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ Tel: 01992 448899 · Fax: 01992 471314
Email: mailorder@cirkit.co.uk



Electronics Workbench[®] Version 4.1

NEW
WINDOWS 95/NT
32 BIT VERSION

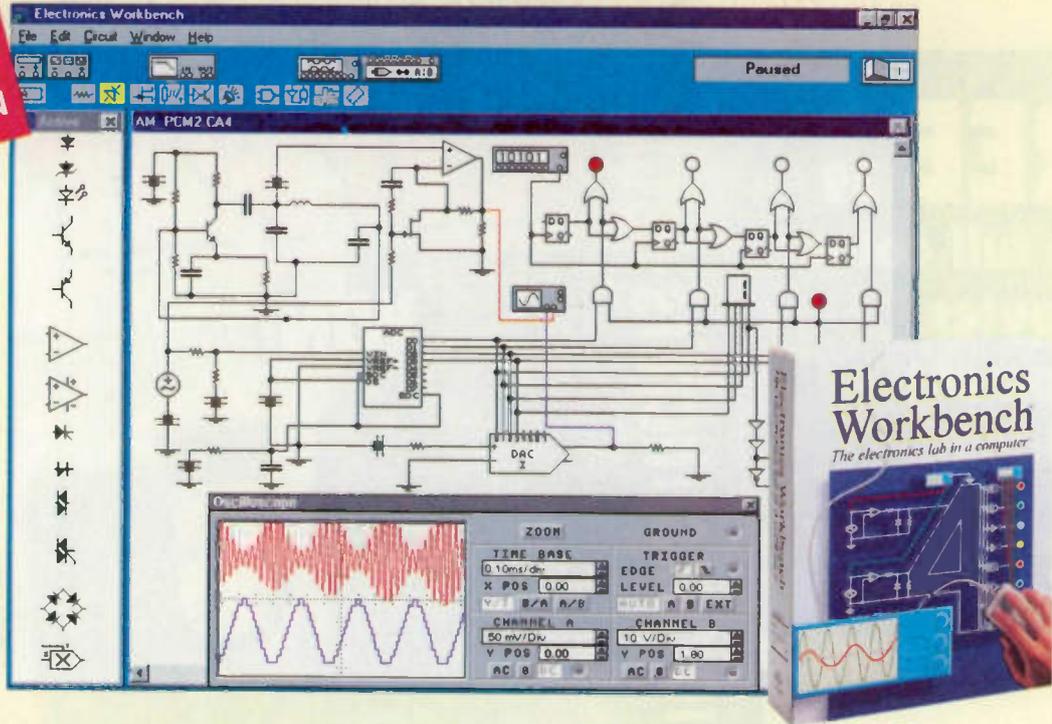

Design and Verify Circuits Faster

Join over 40,000 customers using *the* affordable mixed-signal simulator

Design faster with Electronics Workbench. Mix the analog and digital components and ICs in any combination. And with a click of the mouse, try 'what if' scenarios and fine tune your designs. The built-in SPICE simulator gives you real-world waveforms.

All without programming or netlist syntax errors.

And in minutes. Not hours or days.

You'll be up and running sooner. And create better designs faster with Electronics Workbench. We guarantee it!

RM **Robinson Marshall (Europe) Plc**

Nadella Building, Progress Close, Leofric Business Park, Coventry CV3 2TF
E-mail: sales@rme.co.uk. Fax: 44 (0) 1203 233210

Shipping charges UK £6.99 All prices are plus VAT.

All trade marks are the property of their respective owners.

Electronics Workbench is a trademark of Interactive Image Technologies Ltd., Toronto, Canada.

Electronics Workbench: £199

- Click & drag schematic capture
- Mixed analog/digital SPICE simulator
- Instant Bode plots and scrollable waveforms
- 50 analog components with 350 models
- 140 digital components and ICs in TTL and CMOS
- Windows 95/NT/3.1, DOS and Macintosh versions
- Free unlimited technical support
- 30-day money-back guarantee

Engineer's Pack: £399

- Electronics Workbench
- 2,450 models
- Import/Export SPICE netlists
- Export to PCB packages

To discover more about *the* affordable mixed-signal simulator, call us today at:

44-(0)-1203-233216

Fax: 44-(0)-1203-233210



Australia: 2519-9938 • Belgium: 2-884-7309 • Brazil: 11-453-5588 • Chile: 23260900 • Cyprus: 2631068 • Czech Republic: 42-482454 • Denmark: 35250109 • Finland: 0-897-9033 • France: 1-4909-0000 • Germany: 711627740 • Greece: 1-524-9981 • Hungary: 1-215-0082 • India: 11-544-1343
Indonesia: 21-670-0815 • Israel: 3-667-5613 • Italy: 11-437-5549 • Japan: 3-3382-3136 • Malaysia: 3-774-2189 • Mexico: 5-993-5260 • Netherlands: 18031-7666 • New Zealand: 9-267-1756 • Norway: 22-16-70-45 • Philippines: 973-27-0118 • Portugal: 1-81-86609
Singapore: 777-2303 • Slovenia: 61-317-830 • South Africa: 331-6-8309 • South Korea: 2-222-3431 • Spain: 1-383-8335 • Sri Lanka: 1-86-9970 • Sweden: 8-740-9500 • Taiwan: 886-2-366-0080 • Thailand: 662-398-6952 • UAE: 4-453-505 • UK: 203-23-3216



SWATCH WATCHES COME UP WITH A WINNER

— by Hazel Cavendish

ONE of the best electronically-inspired ideas of the year comes from Switzerland's Swatch watch company — a product which has already made billions internationally by marketing a timepiece of simple reliability and utility at a bargain price which has fitted admirably with today's casual dress codes. Now Swatch is moving upmarket into a more significant role.

The Company has an admirable philosophy of simplifying life for busy people, and it saw its chance by challenging the SMART card. Rightly reckoning that the public is heartily tired of carrying round a wallet or handbag stuffed with plastic cards, it has produced a Swatch Access wristwatch which not only tells you the time but contains a V4050 read-write EPROM chip capable of storing one kilobyte data, working at a low clock rate of 125kHz with a data length of 32 bits and a communication rate of 204kHz. This watch should save people a great deal of time and effort in the future, as the Company develops various applications.

SKI WATCH

Not unnaturally in a country which takes to the ski slopes for its recreation at the first heavy fall of snow in winter, the watch was first designed for the ski slopes, christened the Swatch Access Ski Watch and costed at only £28 in sterling.

Credit points are downloaded into the watch, and all the skier queuing at the ski lift needs to do is flash his watch at the gate. The transponder sends out signals constantly, while a sensor coil encircling the watch provides the antennae. Everything needed is integrated in the chip which is able to work without a microprocessor. Once up the mountain the skier can use his watch to obtain his hot chocolate and for any other facilities offered in the course of a day's ski-ing.

It is also possible to buy time related to points, so that an athlete could pay a set

sum for, say, five days, and the watch would be primed for those dates in which all ski trips (or other athletic events) were covered.

The ski watch has been an enormous success, and is used at 280 ski resorts and is registered in 13 countries including America and Canada as well as most of Europe.

Now the Swatch is being introduced for the tourist trade, and was trialled in Salzburg, Austria this autumn. The Ski Access watch is compatible with this use as the "Debit Value Solution" is contained in the EPROM chip. The potential for this new application is impressive.

Company spokesman Ruud Krabbe says, "This use of the Swatch watch is not only more comfortable for the tourist but it is actually far less expensive than operating a Smart card.

"A tourist arriving in Salzburg can now apply for an all-inclusive package in which his hotel, meal expenses in a wide range of the city's restaurants, tourist attractions such as visits to castles and including the Casino, will all be integrated.

"We do not load money on the watch; instead we load credit points for everything.

"We are also working on other more sophisticated chip solutions for the use of Credit Cards, which we recognise involves a need for more security."

MARIN CHIP

He explains that the reason his company has been able to offer the watch at such an economic price is because the large watch group to which Swatch belongs (which includes most of the famous

Swiss watch companies) has its own semi-conductor company, Electronic Marin, which specialises in low voltage and low power applications and produces chips for products as diverse as items for the motor industry and animal identification items for pigeons requiring small read-only chips fixed to their feet.

TRANSPORT

Mr Kabbe says another Swatch watch using a more powerful chip solution will soon be introduced for international transport fares. Watches can be used to pay fares on busses, metro systems and trains, similar to a system which has been in place in Hong Kong for some time, and negotiations to sell the system to two large Asian cities is in the pipeline and is expected to be announced shortly.

"In many parts of Asia people lack any sort of infrastructure and are prepared to jump directly on to new technology, giving them an advantage over older countries and fulfilling many needs," he said. "Such a process is very slow in America, because of their innumerable Labour regulations, and there is low penetration of our new technology in France because most of the ski regions are State owned and controlled by electricity companies, so we met some resistance there."

UK MARKET

His company is in final negotiation with a major British company at present, and is planning a marketing programme which will concentrate on the English market. Interest has already been shown by British amusement parks and it is expected that large department stores wishing to offer their customers 'loyalty bonuses' in the American manner may use the system to give people a convenient way to shop.

Swatch, which provided much of the timing at the Atlanta Olympics, is already in discussion with the Australian organisers of the next Olympics planned for Sydney, and hopes for a much larger role than they played in America, where they were hampered by the fact that their technology was not compatible with some of the established US systems.



DIG THAT PICTURE!

DIGITAL photographs that can be downloaded to your PC can be easily achieved with Sanyo's first digital camera, the VPC-G1 "Image PC". This compact camera uses a CCD sensor instead of film and stores pictures in its built-in memory.

The camera can then be coupled to a PC via the RS-232C serial port. Pictures can then be brought up on screen and even manipulated to be used in documents and other similar applications. Up to 32 images can be taken using normal resolution (320 x 240), or 16 in high resolution mode (640 x 480). Optional 2MB and 4MB memory expansions are available allowing up to 128 shots to be taken.

Retailing at £579.99, the VPC-G1 is designed to look and handle like a conventional film camera. It is supplied with "Chelsea" photo-enhancement software and is Microsoft Windows compatible.

For information ask your local camera dealer, or contact Sanyo UK Sales Ltd, Dept EPE, Sanyo House, Otterspool Way, Watford, Herts WD2 8JX.



NET CLEANING

SCIENCE and Technology Minister Ian Taylor recently challenged the Internet industry to co-operate to help parents and schools control children's access to undesirable material on the Internet.

He urged that software which can screen out unwanted and undesirable material should be made widely available. At the same time, he welcomed the inclusion of screening standards in the new version of Microsoft's Internet browser. The Platform for Internet Content Selection (PICS), can be implemented on any PC platform to allow Internet users and parents to be censorial.

Ian Taylor went on to say that "Government will face increasingly strong calls for legislation to regulate all aspects of the Internet, unless service providers are seen wholeheartedly to embrace responsible self-regulation."

Whilst most people will share his concerns about "undesirable" Net material, many will undoubtedly feel unease about Government intervention on the Net; such intervention by governments more aggressive than ours in the UK could suppress aspects of the "freedom of speech" which it is supposed that the Internet offers to the world-wide community.

BRIDGE TOO FAR?

INCREDULITY is likely to be the reaction of those who do not play Bridge to BT's announcement that it has introduced software which allows the game to be played via a computer/telephone link.

The software is part of BT's new interactive computer games network, Wireplay. BT is working with the English Bridge Union (EBU) to recruit members to test the system which will be fully launched in Spring 1997.

The uninitiated might be excused for thinking that Bridge is a game that requires socially interactive partnerships around the same table, not across the distances of remote telecoms. Cynics, however, could suggest that Bridge's reputation for breaking up relationships might decline if gameplay is not at close-quarters!

PATENTLY MORE INVENTIVE

IS it possible that in the UK we are becoming more inventive? The Patent Office has recently commented that "after many years of decline, the demands for patents appears to have stabilised. The increase in demand for registration of designs has continued and the demand for trade marks reached a further record level."

Let's hope that, contrary to past experience, we are also learning how to capitalise on our inventions to benefit the UK, not foreign businesses.

The Patent Office are at 25 Southampton Buildings, Chancery Lane, London WC2A 1AY.


PCB Designer

For Windows 3.1, '95 or NT



Runs on any PC running Windows 3.1, Windows 95 or Windows NT with a minimum 2MB RAM

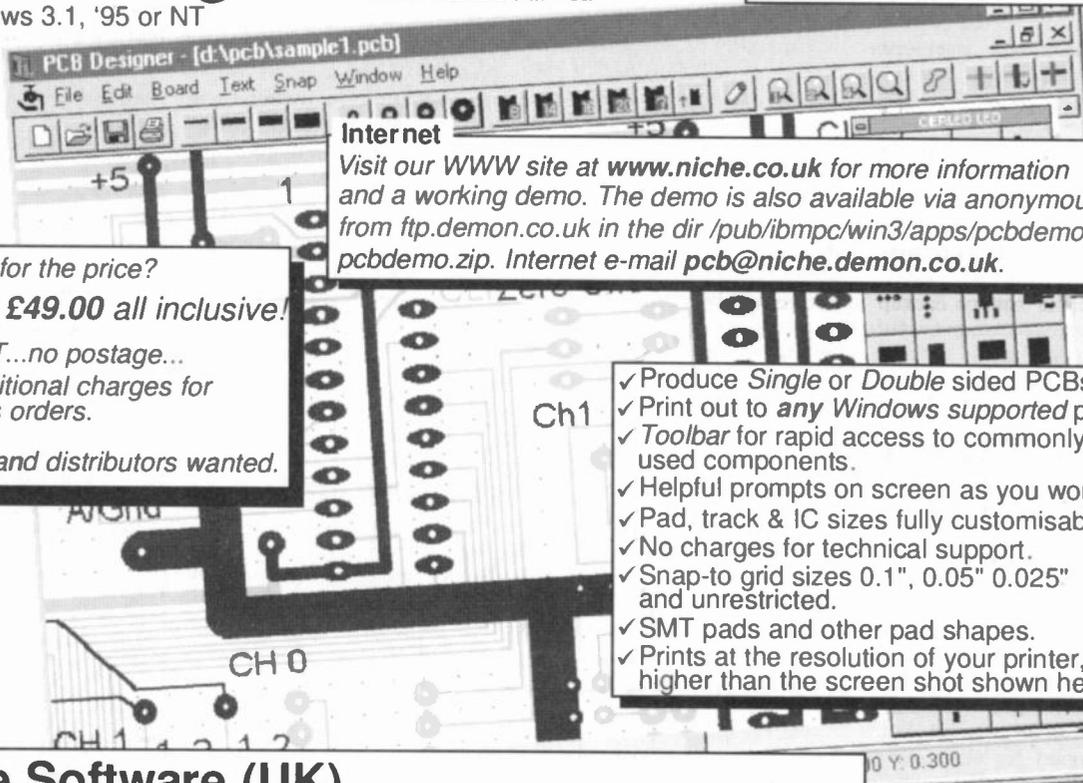Will work with any Windows supported printer and monitor



Internet

Visit our WWW site at www.niche.co.uk for more information and a working demo. The demo is also available via anonymous FTP from <ftp:demon.co.uk> in the dir /pub/ibmpc/win3/apps/pcbdemo/ as [pcbdemo.zip](#). Internet e-mail pcb@niche.demon.co.uk.

Looking for the price?

It's just **£49.00** all inclusive!

...no VAT...no postage...

...no additional charges for overseas orders.

Dealers and distributors wanted.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Prints at the resolution of your printer, much higher than the screen shot shown here.

Niche Software (UK)

12 Short Hedges Close, Northleach, Cheltenham, GL54 3PD Phone (01451) 860 737

Available in South Africa from JANCA Enterprises, PO Box 32131, 9317 Fichardtpark at R299,00

CENTRAL HEATING CONTROLLER

RICHARD STONE

Achieve the benefits of a sophisticated central heating system with this 7-day programmable controller.



THIS ARTICLE describes the design, construction and use of a microcontroller-based central heating controller similar in specification and performance to typical commercial units. The unit has been designed to be easy to use and reliable, and offers the following features:

- Independent switching of both central heating and domestic hot water
- Switching capacity of 5A at 240V a.c.
- Separate programs for each of seven days
- Once or twice per day switching cycles
- Thermostat capability using integral or external temperature sensor
- 2-line 16-character l.c.d. display
- Continuous display of temperature and time
- Rechargeable battery backup to protect program in event of mains failure
- Outputs configurable to be permanently on or off if required
- Indication by l.e.d. of relay operation

DESIGN OVERVIEW

A simplified block diagram of the Central Heating Controller is given in Fig. 1. The system is based around an 8051-series microcontroller (the Atmel AT89C2051). The microcontroller reads program instructions contained in its ROM (Read Only Memory) and then executes them to perform the functions of the Central Heating Controller in conjunction with a minimum of additional electronic circuitry.

User input is via four pushbutton switches which are continually scanned for a keypress by the microcontroller, which accordingly takes appropriate action as dictated by its control program.

Output to the user is via a 2-line 16-

character alphanumeric l.c.d. display module. The module is capable of displaying the full ASCII character set so user messages and prompts appear in plain English.

The unit monitors temperature by means of an analogue sensor whose output has to be converted to a digital format so that it can be processed by the microcontroller. This function is performed by means of an analogue-to-digital converter (ADC).

Relays are used to interface the

microcontroller outputs to the mains voltages which are required to be switched by the Control Unit.

The Central Heating Controller may be powered by either a mains derived supply or a standby battery. Under normal circumstances, the mains derived supply will be used but, in the event of mains failure being detected, the standby battery supply is switched in to ensure that the time and program information is not lost.

MICROCONTROLLER

The full circuit diagram of the Central Heating Controller is given in Fig. 2.

The Atmel AT89C2051 microcontroller is shown as IC3. This device is compatible with the industry-standard 8051 series of microcontrollers, although, as it is intended as a low cost device, some of the standard 8051 features are missing. The features included are as follows:

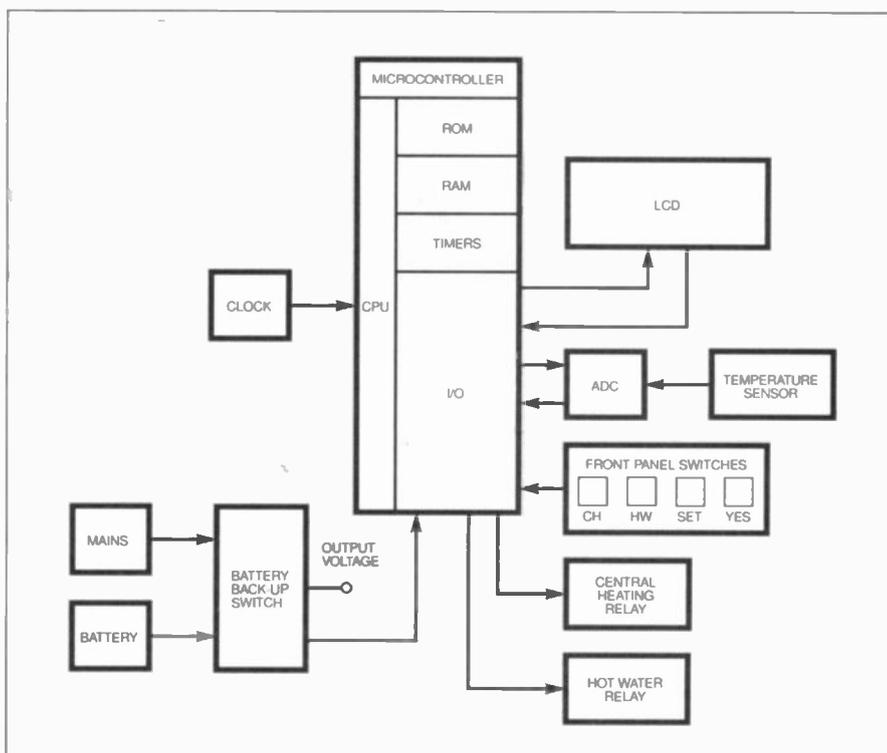


Fig. 1. Block diagram of the Central Heating Controller.



COMPONENTS

Resistors

R1	varistor, 275V a.c.
R2	330Ω
R3, R9	22k (2 off)
R4	3k3
R5, R7	
R6, R8	10k (4 off)

All 0-25W 5% carbon film except R1.

See
**SHOP
TALK**
Page

Potentiometers

VR1	20k multiturn preset
VR2, VR3	10k multiturn preset (2 off)

Capacitors

C1	470μ radial elect. 25V
C2	47n ceramic
C3, C7, C9	10μ radial elect. 16V (3 off)
C4, C8	100n ceramic (2 off)
C5, C6	33p ceramic (2 off)

Semiconductors

D1, D3, D4	1N4148 signal diode (3 off)
D2	LM335 temperature sensor diode
D5, D6	red l.e.d., 3mm (2 off)
REC1	W005 1.5A 50V bridge rectifier
TR1, TR2	BC546 <i>n</i> pn transistor (2 off)
IC1	ICL7673 battery backup switch
IC2	78L05 +5V regulator
IC3	AT89C2051 pre-programmed microcontroller (see text)
IC4	ADC0831 A-to-D converter

Miscellaneous

B1	9V NiCad battery, PP3 equivalent
FS1	200mA resettable fuse, p.c.b. mounting
RLA, RLB	12V relay, s.p.c.o. contacts rated 10A 240V a.c. (2 off)
S1 to S4	push-to-make switch, panel mounting (4 off)
T1	mains transformer, 12V secondary, 1-2VA
TB1, TB2	2-way terminal block (2 off)
TB3, TB4	3-way terminal block (2 off)
X1	6MHz crystal
X2	2-line 16-character l.c.d. display module

Printed circuit board, available from the *EPE PCB Service*, code 120; plastic case, 184mm × 115mm × 163mm; clear display bezel; 30mm p.c.b. mounting pillar (4 off); 15mm p.c.b. mounting pillar (4 off); PP3 battery clip; cable ties; l.e.d. mounting clip (2 off); cable grommets, clamping (3 off); 8-pin d.i.l. socket (2 off); 20-pin d.i.l. socket; connecting wire; solder, etc.

Approx Cost
Guidance Only

£65

A metal oxide varistor (R1) is connected across the mains supply, after the fuse, to afford the unit some protection from high voltage transients and spikes which are sometimes present on the mains supply. Under normal conditions, the varistor presents a very high impedance to the supply, but as soon as the supply voltage exceeds a predetermined level, e.g. due to a voltage transient, the device's impedance rapidly falls, which has the effect of clamping the transient voltage at a protective level. In this particular case the clamping level is 275V a.c.

The step-down transformer (T1) has two 6V secondary windings which are connected in series to give a 12V a.c. output. This is rectified by REC1 to give a full wave rectified d.c. output with a peak voltage of around 17V. This is smoothed by a large value electrolytic capacitor (C1) to give a steady d.c. output voltage.

BATTERY BACKUP

The battery backup feature is provided by a rechargeable NiCad battery (B1). This is a PP3 equivalent and is trickle charged via resistor R2 and diode D1. Resistor R2 sets the trickle charge current to approximately 10mA.

IC1 is an ICL7673 automatic battery backup switch integrated circuit which performs the switching function between the primary supply (mains derived) and the secondary supply (battery derived). IC1 determines which of the two input voltage sources is greatest and automatically switches this to its output at pin 1.

In normal operation, the primary voltage (around 12V to 16V) will be higher than the secondary voltage (around 9V) and so the primary supply will be switched through to the output pin. However, in the event of mains failure, then obviously the battery supply will be

highest and so this will be connected through to the output.

The switchover from one input source to the other occurs in less than 50μs, which means that the changeover is transparent to the rest of the circuitry.

The ICL7673 provides two open-drain transistor outputs (pins 3 and 5) to indicate which supply is currently connected. One of these, pin 3, is connected to the microprocessor's I/O line P3.4 which is configured as an input. This I/O line has an internal pull-up resistor to the microcontroller's supply voltage. When IC1 switches from primary to secondary supply, the voltage on this line will go from logic 1 (high) to logic 0 (low). The state of line P3.4 is read by the controlling program to detect if the mains has failed and take the appropriate action.

The voltage output from IC1 is fed to the regulator IC2, the output of which supplies the regulated +5V required to power the rest of the circuit. This output is decoupled by capacitors C3 and C4, although additional decoupling is used in various other parts of the circuit.

The 78L05 device used for IC2 has a maximum output current of 100mA, which is more than sufficient to power the entire Central Heating Controller circuit with the exception of the output relays. The latter are powered directly from the unregulated d.c. supply. This means that if the mains supply fails and the unit is running from the battery supply then the relays will be de-energised and both outputs will be off.

INPUT SWITCHES

There are four push-to-make switches, S1 to S4 (labelled CH, HW, SET and YES) which allow the user to programme and configure the unit for the desired mode of operation. These switches have one side connected to ground and the other to the

microcontroller's I/O lines P3.0 to P3.3 (pins 2, 3, 6 and 7) which are configured as inputs.

These I/O lines also have internal pull-up resistors to the supply voltage and hence operation of a switch will cause the corresponding I/O line to go from logic 1 to logic 0. The programmed software can therefore detect if a switch has been pressed and respond accordingly. The

problem of contact bounce, which is inherent to all mechanical switches, is taken care of by the software. This is done by performing successive reads of the input pins, separating each read by a delay which is greater than the expected contact bounce time (typically 10ms to 20ms).

DISPLAY MODULE

The system imparts information to the user via an Hitachi LM016XMBL l.c.d. display module (X2) which is capable of displaying two lines of 16 alphanumeric characters. This module consists of both the l.c.d. display itself and a driver and display controller chip (the HD44780) which provides the interface to the outside world.

In simple terms, the HD44780 appears as a series of byte-wide registers and memory locations which can be accessed as appropriate in order to display the required characters on the l.c.d. The HD44780 is normally accessed via a byte-wide data bus (lines D0 to D7) and three control inputs, Register Select (RS), Read/Write (\bar{R}/\bar{W}) and Enable (EN).

The EN input must be high in order to allow a data transfer to take place. The other two inputs, RS and \bar{R}/\bar{W} , are used to select the required register (either data or control) and to determine whether a read or write access is required.

The HD44780 also allows data transfer to take place as two consecutive 4-bit wide transfers using the upper four data bus lines (D4 to D7) and this is the approach used in this design in order to cut down on the number of I/O pins required.

Microcontroller I/O lines P1.4 to P1.7 are used as the data bus and connect to lines D4 to D7, respectively, of the HD44780. Lines P1.1, P1.2 and P1.3 are used as EN, \bar{R}/\bar{W} and RS, respectively. Line P1.1 requires an external pull-up resistor to the supply voltage and this is provided by R9.

Display contrast can be adjusted by means of preset potentiometer VR1, whose wiper sets the voltage applied to the module's control pin 3.

RELAY CONTROL

The Central Heating Controller has two switchable outputs which are intended to switch the central heating and the water heating on or off in accordance with how the unit is programmed. Both these outputs are electrically identical and so only the central heating output is described here.

A relay is used in order to meet the rated voltage and current requirements of the equipment to be switched. However, the output current drive available from the microcontroller's I/O lines is insufficient to directly power the coil of the specified relay (RLA). Consequently, the coil is driven by a transistor (TR1) operating as a simple switch.

When microcontroller I/O line P3.5 is set to output logic 1 the transistor is driven into saturation due to the current flowing into its base (b) via resistor R6. This effectively connects the relay coil to ground and hence the coil is energised and operates the contacts. Diode D3 protects the transistor against the inductive voltage generated across the coil at the moment that the transistor is switched off.

An l.c.d. (D5) is also controlled by TR1 and an appropriate current limiting resistor (R5) in order to give an external indication of the relay operation. The relay contacts are brought out to a terminal block (TB3) in order to allow easy connection to the external wiring.

The relays used are 12V types and operate directly off the unregulated supply available at the output of REC1. The reason for this was to reduce the amount of current required to be sourced via IC2. Using relays with 5V coils would have required an extra 100mA or so to be sourced via IC2, which would have necessitated using a larger regulator and also resulting in a lot of wasted energy dissipated as heat across the regulator. It would also impose an undue strain on the battery during a mains power failure.

TEMPERATURE SENSING

One of the features of the Central Heating Controller is the ability to measure and display temperature. In order to do this, some form of electronic temperature sensing device is required, the output of which is required to be in a format that can be interpreted by the microcontroller software.

The sensing device used in this design is the LM335 precision temperature sensor (D2) which basically operates as a two terminal Zener diode. When biased via a resistor from a suitable voltage source, this device has a breakdown voltage which is directly proportional to absolute temperature (i.e. temperature measured in degrees Kelvin). Therefore, at a temperature of 0° Celsius (273° Kelvin), the breakdown voltage of the device will be 2.73V, and at 25° Celsius, the breakdown voltage will be 2.98V.

Digital computing devices, such as a microcontroller, cannot directly interpret analogue voltages until they are converted into a digital format. This function is undertaken here by an ADC0831 analogue-to-digital converter, IC4. This device is capable of 8-bit resolution, which means that the analogue input voltage can be digitized into 256 (2⁸) discrete digital values.

The ADC0831 also features a differential amplifier input stage, which allows the analogue zero input voltage to be offset from ground, and an adjustable voltage reference input, which allows a smaller analogue voltage span to be encoded to the full eight bits of resolution. These features are very useful in this design due to the fact that, at the temperature range of interest, the output of the LM335 consists of a relatively small changing voltage superimposed on a large offset voltage.


TEMPERATURE RANGE

The temperature range chosen to be displayed is from -20°C to +43.75°C, corresponding to LM335 nominal output voltages of 2.53V to 3.1675V. In order to configure the ADC0831 to accept this input voltage range, all that is required is to set the appropriate voltage levels at the inverting amplifier and reference voltage inputs.

Adjustment is achieved by using preset potentiometers VR2 and VR3 connected between the supply voltage and ground. VR2 is adjusted to set the offset voltage at the inverting amplifier input (pin 2) to 2.53V. VR3 sets the input reference voltage and should be adjusted to give a voltage at this input (pin 3) of 0.6375V.

Using these settings of VR2 and VR3, the voltage resolution is 0.25V per digital unit, which is equivalent to 0.25°C, although the system software only deals with temperatures to the nearest integer value. Also, it should be noted that the output voltages quoted are for a "perfect" LM335 and a calibration process, detailed later, can be performed if the best possible accuracy is required.

The LM335 is connected to the non-inverting input of the ADC0831 and is biased from the +5V supply via resistor R4. Provision is made in the design to

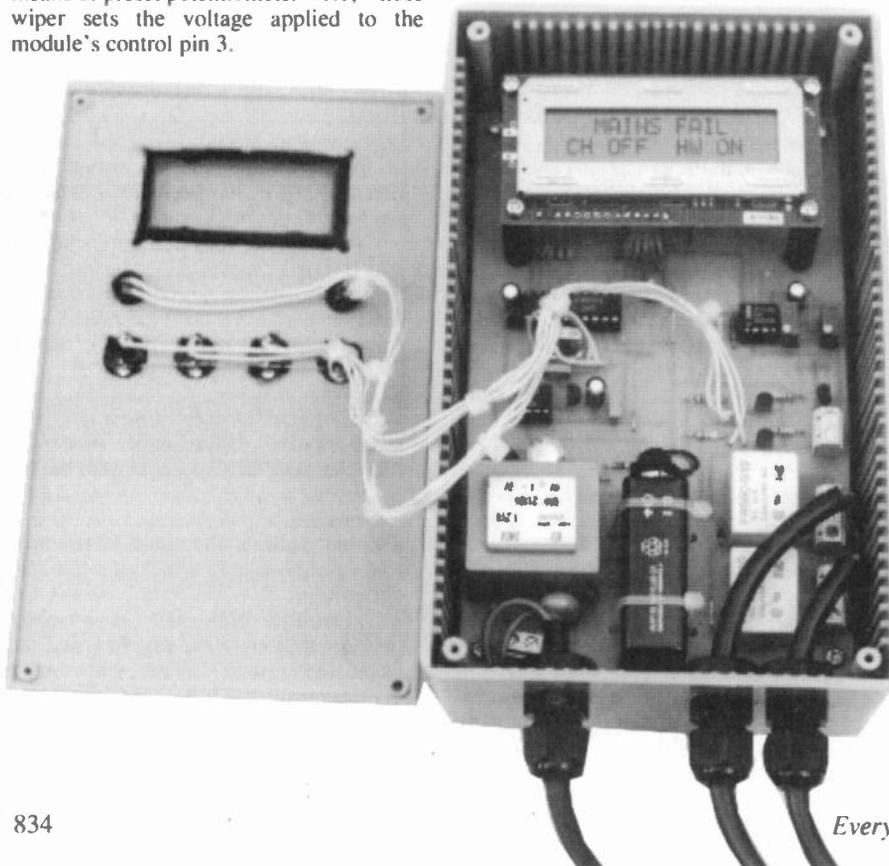

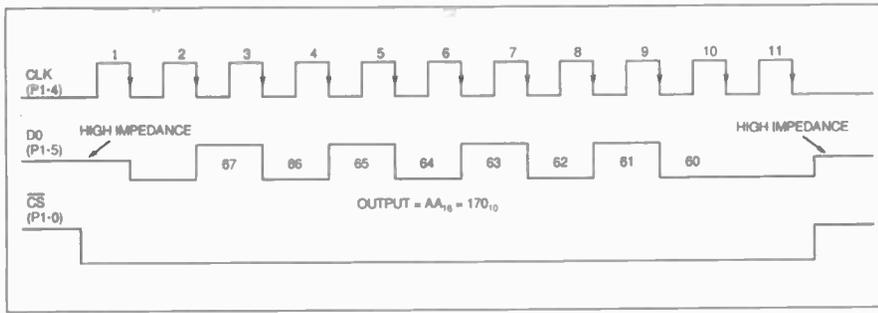


Fig. 3. Timing diagram for the ADC0831 ADC.

mount the LM335 either on the printed circuit board or remotely via connector TB2. Capacitor C9 provides a supply voltage decoupling function.

The ADC0831 features a 2-wire serial interface, comprising a clock input (CLK) and a data output (D0). An active low chip-select input (CS) is also provided. These pins are connected to microprocessor I/O lines P1.4, P1.5 and P1.0. It will be seen that I/O lines P1.4 and P1.5 are also connected to the l.c.d. display module.

This is allowable as the module's data bus takes on a high impedance state when its EN input is low, and the same can be said of the ADC0831's D0 output if its CS line is high. Therefore, as long as the software does not attempt to access both devices simultaneously, there will be no conflict.

Microcontroller I/O line P1.0 requires

an external pull-up resistor to the supply voltage and this is the function of R3.

In order to perform an analogue-to-digital conversion using the ADC0831, it is necessary to drive its CS line to a logic 0 level and then, while CS is low, generate a series of eleven clock pulses (high to low logic level transitions) at the CLK input. The conversion result is output, most significant bit first, via line D0 on the falling edge of clock pulses two to nine. After the eleventh clock pulse, the conversion is ended by bringing CS back to a high logic level.

This process can best be illustrated by reference to the timing diagram given in Fig. 3. The controlling software manipulates the relevant microcontroller I/O pins in such a way as to generate the necessary sequence of logic levels. The output data present on D0 is read by the

In addition to this continuous loop, another sequence of operations is being executed in the background on a periodic basis, the main function of which is to drive a software-based real time clock. Each operation is numbered and explained in greater detail in the following text.

MAIN PROGRAM LOOP

Operation 1 is the first sequence of instructions executed after a microcontroller reset, the main purpose being to initialise the program variables and the various sections of the microcontroller hardware. One of the functions undertaken here is to configure one of the microcontroller's internal timers to produce a periodic interrupt every 500 microseconds, which is used as an accurate timing signal for the real time clock (RTC).

After the initialisation sequence is complete, the software enters a continuous loop of operations.

Operation 2 is the first operation in this continuous loop and consists of a check upon the mains power supply status, which is determined by reading the state of line P3.4. If the mains supply is present, then the software jumps to Operation 3. However, if the state of line P3.4 indicates that the unit is being powered from the battery, then the software shows "MAINS FAIL" on the top line of the l.c.d. display and disregards any front panel switch operations until the mains power is restored.

It should be noted that the periodic timer-driven background functions continue to execute during this period so the time information is not lost, even though the time is no longer being displayed on the l.c.d. When it is determined that the mains power has been restored, the software begins the next operation.

Operation 3 is to check if the user has pressed a front panel switch. The software which reads and debounces front panel keypresses runs as a periodic background task. If it is determined that a keypress has occurred, a "flag" is set within the microcontroller RAM. This flag is read during Operation 3 and if it is determined that a keypress has occurred, then this keypress and any subsequent keypresses are processed appropriately within Operation 4. If no key has been pressed, then the software jumps to Operation 5.

Operation 4 processes the keypress which was detected in Operation 3 and, depending on subsequent keypresses, allows the user to set the operating mode of the unit or to program it with the current time, switching information and the thermostat trip point.

During this stage, the time and temperature are not displayed and the unit instead uses the l.c.d. display to prompt the user and allow switched entry of the required information. Once the user has finished entering the data, the software begins the next operation.

Operation 5 obtains the current time information from the real time clock and displays this on the l.c.d. The real time clock information is contained in the microcontroller RAM and the program simply reads this information, formats it, and then writes it to the appropriate area of the display. The software also flashes the

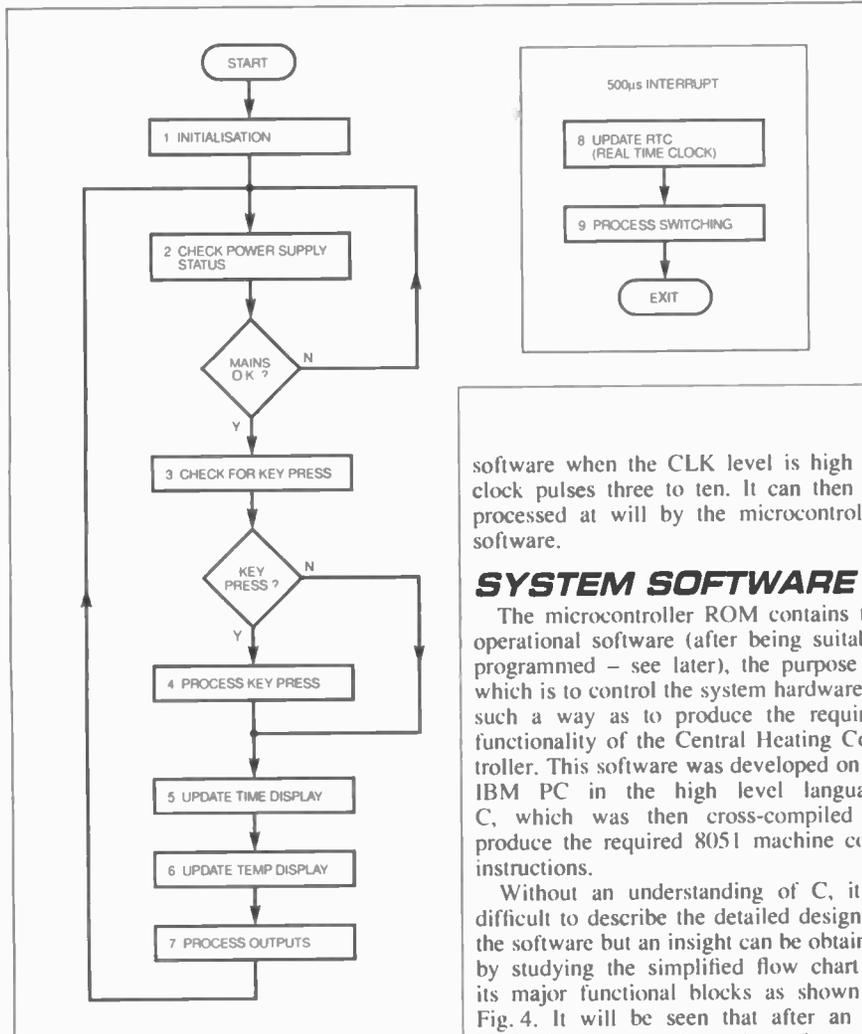


Fig. 4. Simplified flow chart of system software.

software when the CLK level is high on clock pulses three to ten. It can then be processed at will by the microcontroller software.

SYSTEM SOFTWARE

The microcontroller ROM contains the operational software (after being suitably programmed - see later), the purpose of which is to control the system hardware in such a way as to produce the required functionality of the Central Heating Controller. This software was developed on an IBM PC in the high level language C, which was then cross-compiled to produce the required 8051 machine code instructions.

Without an understanding of C, it is difficult to describe the detailed design of the software but an insight can be obtained by studying the simplified flow chart of its major functional blocks as shown in Fig. 4. It will be seen that after an initialisation process has taken place, the main body of the program is basically a continuous loop of repeated operations.


colon which separates hours and minutes at a 1Hz rate, to give a visual indication that the clock is operating.

During the period that this operation is accessing the real time clock information,

the periodic interrupt is disabled to ensure that the clock data does not change as it is being accessed, which could result in erroneous data being displayed on the l.c.d.

Operation 6 simply obtains the current

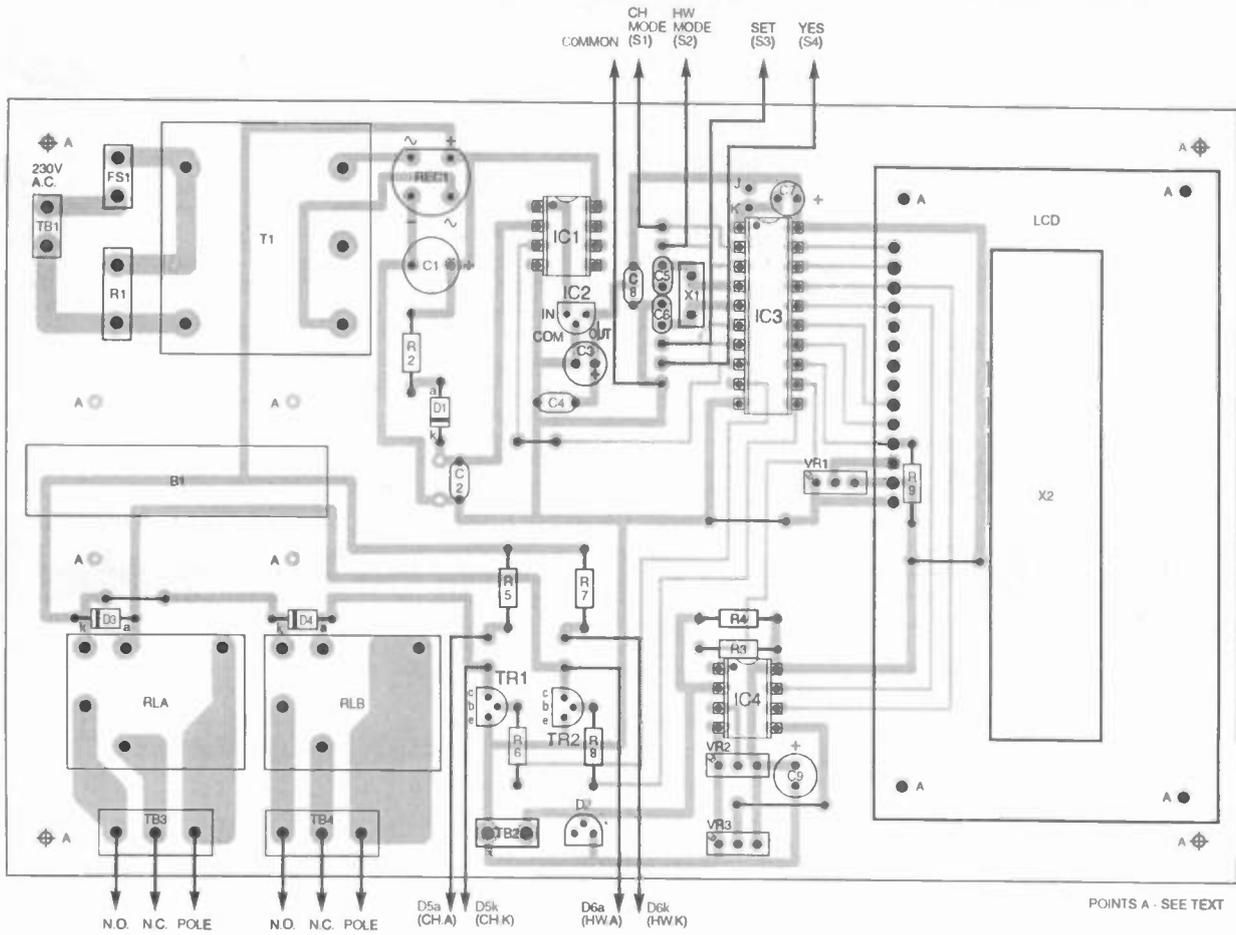temperature information by reading the analogue-to-digital converter. It converts this digital value to a degrees Celsius format and displays it on the l.c.d. This operation is only undertaken once every



POINTS A - SEE TEXT


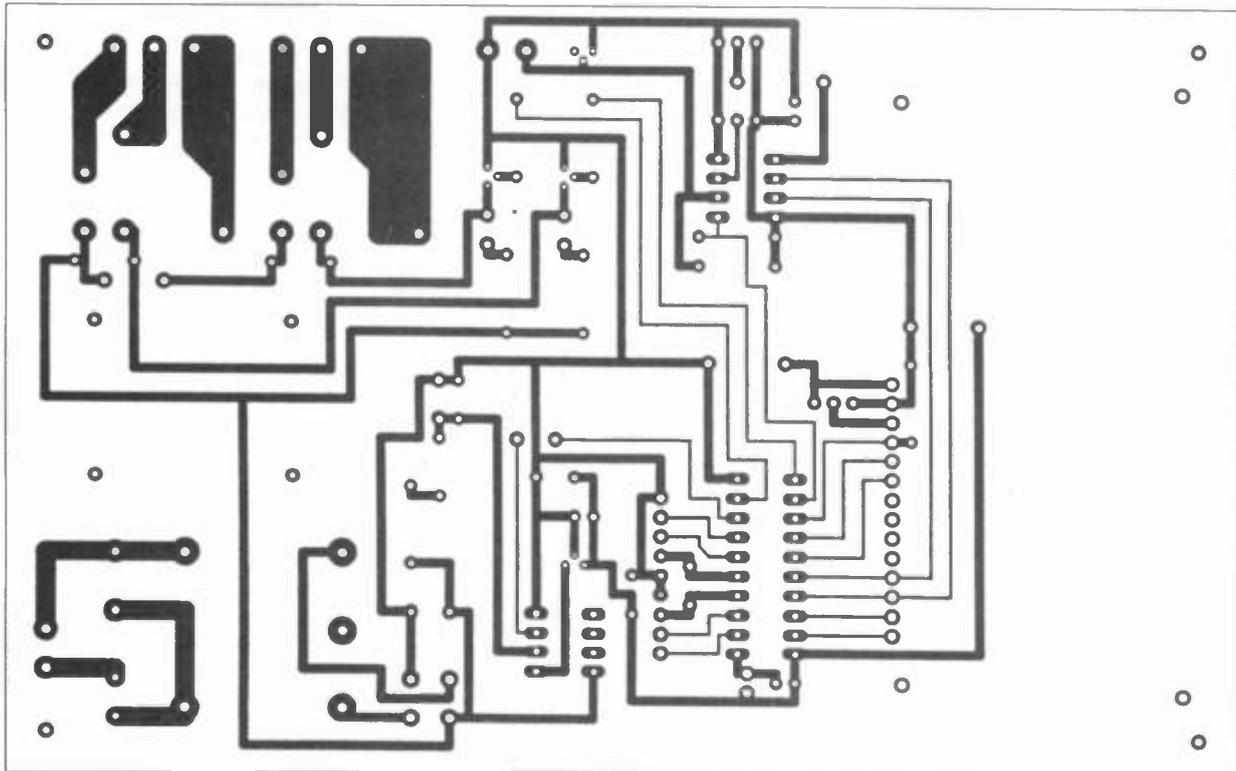


Fig. 5. Printed circuit board component layout and full size underside copper foil track master pattern.

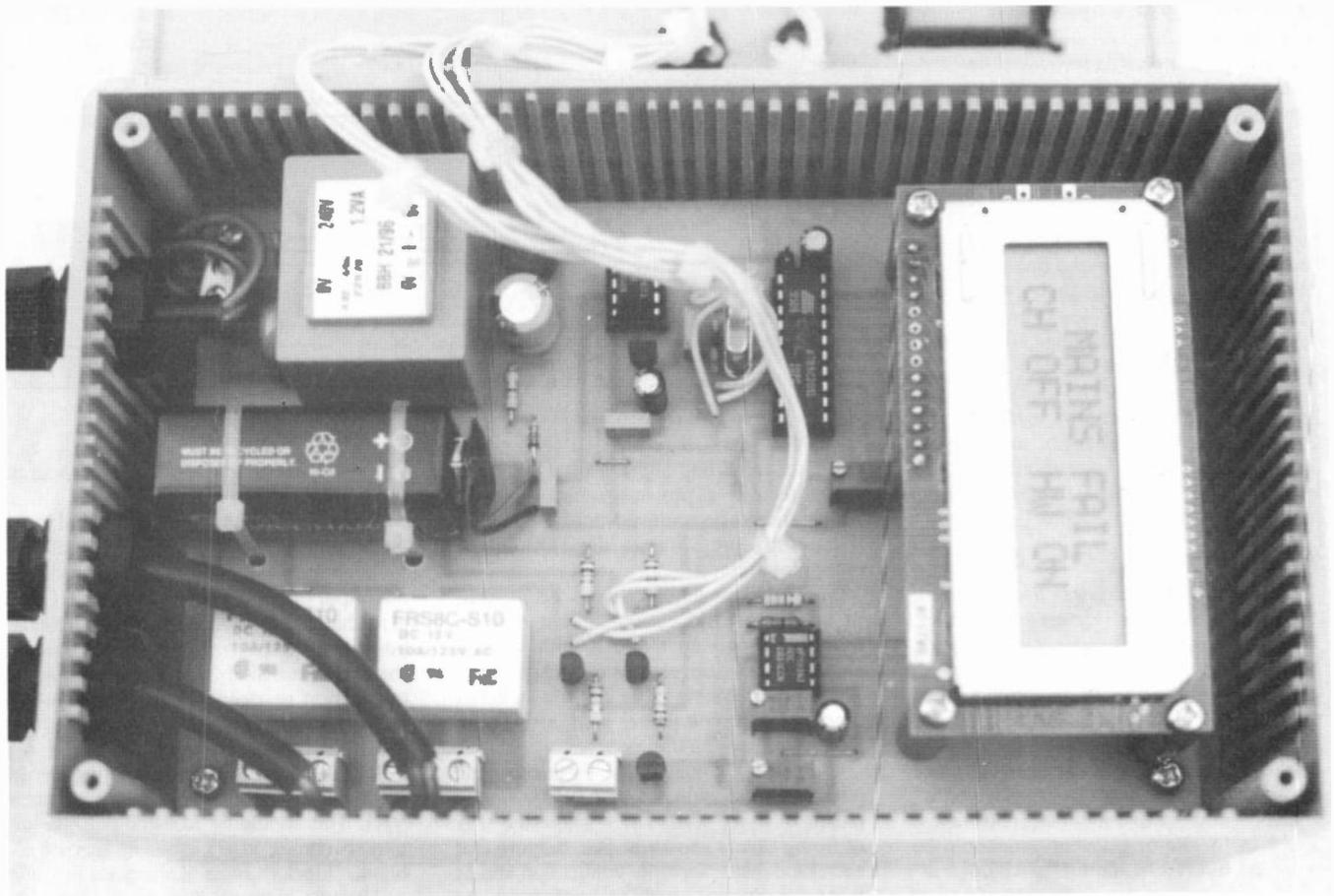

Even when the mains power is off, the battery keeps the controller functioning.

second, determined from the real time clock information, in order to prevent the display flickering as the temperature changes from one integer value to another.

Operation 7 determines whether the two relay outputs should be switched on or off, according to the data previously keyed into the program via the switches.

In the case of the central heating control (but not the hot water), the current temperature and the thermostat setting must also be taken into account. The software also incorporates a hysteresis mechanism on the Central Heating output to ensure that the output does not rapidly change on and off if the temperature is borderline between two integer values.

After Operation 7 has been completed, the program loops back to Operation 2 and the whole process repeats.

PERIODIC OPERATIONS

Operation 8 consists of implementing the software driven real time clock. This basically comprises a dividing chain which converts the 2.0kHz input frequency (equivalent to 500µs periodic interrupt) to days, hours, minutes and seconds.

The 2.0kHz frequency is derived from the microcontroller crystal via one of the hardware timers and therefore the real time clock has the potential to be very accurate. All of the real time clock data variables are stored in the microcontroller RAM and therefore can be easily accessed by other areas of the program.

Operation 9 is concerned with reading the state of the input switches, via lines P3.0 to P3.3, and determining if a valid keypress has occurred. This operation is

executed periodically every 20ms (determined from the real time clock) and uses this 20ms interval as a "debounce" period during switch closure and release. The software is coded in such a way that a key will not be acted upon until the key is released, and also to ignore rapid multiple keypresses.

CONSTRUCTION

The Central Heating Controller was designed to be a self-contained unit requiring only the addition of a suitable mains supply and appropriate wiring to the user's central heating system in order to operate.

All components, with the exception of the four front panel switches, S1 to S4, and the two l.e.d.s, D5 and D6, are mounted on a single printed circuit board (p.c.b.) which in turn is mounted in an ABS box. Details of this board are shown in Fig. 5. It is available from the *EPE PCB Service*, code 120.

The l.c.d. module is mounted on the p.c.b. using stand-off pillars to ensure that the display is at the correct height to be clearly visible through a bezel fitted in the lid of the box.

Connections to all components which are not directly mounted on the p.c.b. are made via flying leads. It should be noted that the p.c.b. assembly can be mounted into any suitable enclosure and that it is not necessary to use the specified box.

Assembly of components onto the p.c.b. is relatively straightforward, but it is recommended that the following sequence is adhered to:

First, before beginning assembly, the p.c.b. should be checked to ensure that all

the holes are drilled and clear. There are twelve holes on the board, marked "A" in Fig. 5, which are used for mounting pillars and to attach tie wraps to fasten the battery. These are only drilled as pilot holes in order to allow the constructor to drill them out to suit the actual mounting hardware used. On the prototype unit, they were all drilled out to 3mm diameter.

The four wire links should now be fitted using tinned copper wire of an appropriate gauge, or resistor cut-off leads. Resistors R2 to R9, and diodes D1, D3 and D4 can now be fitted. The diodes must be fitted the correct way round; the cathode (k) is usually indicated by a band on the component body.

The next stage is to fit the i.c. sockets, and it is strongly recommended that they *are* used. Capacitors C1 to C9 and crystal X1 can now be fitted. Ensure correct orientation of the electrolytic capacitors, C1, C3, C7 and C9.

Next fit the two transistors, TR1 and TR2, and the voltage regulator, IC2, again observing correct orientation in accordance with Fig. 5. If the temperature sensor, D4, is required to be internally mounted, it can also be fitted at this stage. With all these devices, it may be necessary to carefully preform (bend) the leads to suit the hole layout on the p.c.b.

All the remaining components should now be soldered to the p.c.b. The bridge rectifier, REC1, is the only other component whose polarity needs to be observed.

The l.c.d. display module is mounted on the p.c.b. using 30mm stand-off pillars and this should be fitted next. The mounting holes on the module are only 2.5mm in diameter and these may need opening out

slightly, depending on the type of mounting pillars used.

Electrical connection between the l.c.d. module and the p.c.b. is made by ribbon cable. This should be carefully cut to length and appropriately stripped and tinned before being connected.

The PP3 battery is fastened to the p.c.b. using nylon tie wraps. These should be fastened as tightly as possible so that the battery is firmly held on the board. Electrical connection may be made by soldering a PP3 battery connector lead direct to the p.c.b. However, at this stage, the battery should remain disconnected.

Switches S1 to S4 and l.e.d.s D5 and D6, which are mounted on the box lid, are connected back to the p.c.b. using flying leads. These connections, though, should be made after the respective components have been mounted in the box lid.

CONTROLLER CASE

An ABS plastic case was used to house the prototype Central Heating Controller. Any other similarly sized enclosure could be used instead. However, if a metal box is used, the box should be suitably earthed in order to minimise any electrical shock hazard.

The drilling details for the box will depend on the choice of display bezel, switches and l.e.d. mounting clips used. The area for the display cut-out should be removed by a combination of chain drilling and filing.

The lower portion of the box should have four holes drilled in it to secure the p.c.b. mounting pillars and should be countersunk if a flush finish is desired. If wall mounting of the unit is required, two "keyhole" slots should also be drilled and filed out.

You will also need to drill holes for the mains cable, switched outputs and external temperature sensor (if fitted). Appropriate glands or grommets should be used with all cable holes. On the prototype unit, an external temperature sensor was not fitted and all other cable entry/exit points were on the lower face of the box.

The box lid can be suitably labelled using rub down transfers or similar to indicate the function of the switches and l.e.d.s.

FINAL ASSEMBLY

Before the unit is assembled, it is necessary to fit the display bezel, the front panel switches and the l.e.d.s to the lid of the case. The display bezel is supplied with

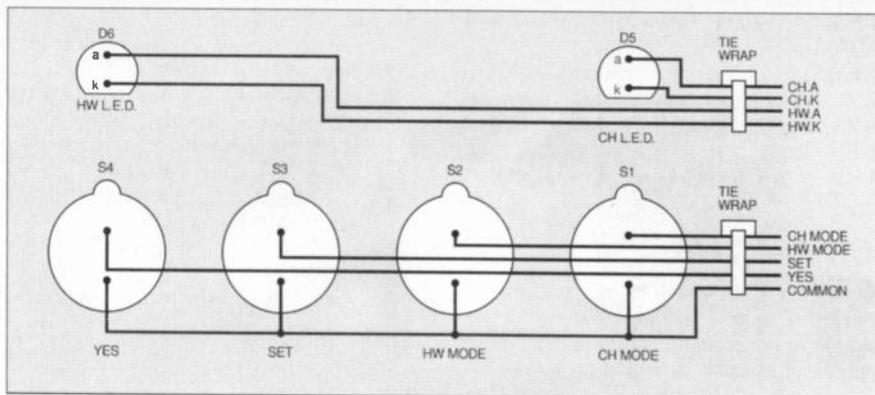
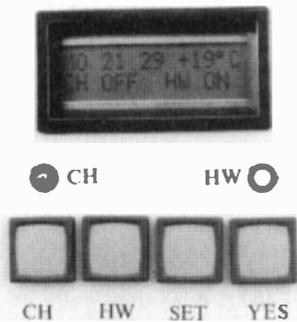


Fig. 6. Wiring connections to lid-mounted components.

the outer moulding and the filter separate. The filter has a protective film covering which should be removed before the filter is carefully pressed into the slots in the outer moulding.

The bezel assembly should be a push-fit in the case lid cut-out, but it may be found necessary to retain it with a small amount of plastic glue applied sparingly. The l.e.d. mounting clips and the switches used in the prototype are also push-fits in their respective mounting holes.

Electrical connections between the p.c.b. and the switches and l.e.d.s are by means of flying leads and a suggested way of doing this is shown in Fig. 6. Note that each l.e.d. has a separate connection and as these are polarity sensitive, care should be taken to ensure that the connections are made correctly.

When connecting up the flying leads, it is useful to allow sufficient length so that the box lid can be removed and laid to one side to allow access to the internal connections. Once the leads have been soldered up, nylon tie wraps should be used to neatly loom the individual cables together.

Once construction of the Central Heating Controller is complete, it is strongly recommended that you follow the advice concerning testing before applying power.

TESTING

When power is applied to the unit it should be borne in mind that several areas of the printed circuit board are at mains potential and therefore great care should be exercised. If you are in doubt about the mains electrical wiring, consult a qualified electrician.

The first test of the assembled p.c.b. should be a visual one to check for any soldering defects and for the correct orientation of polarised components. If all appears to be satisfactory, the battery can be connected and the unit carefully wired up to the mains supply. This should be done with all of the socketed i.c.s. removed as a precaution to avoid damage if there is a problem.

If the mains power supply circuitry is working correctly, then approximately 17V d.c. should be present across pins 8 and 4 of the socket for IC1. The precise voltage will depend on the transformer used and the load it is supplying. The battery voltage of approximately 9V d.c. should also be present across pins 2 and 4 of the same socket.

If all is in order, the unit should be powered down by removing the mains and battery supplies, after which IC1

can be inserted and both power sources re-applied.

A voltage of about 17V d.c. should now be present between pins 1 and 4 of IC1. Voltage regulator IC2 should be producing an output of 5V d.c. ($\pm 0.25V$ d.c.). Check also that 5V is present at all the relevant points on the p.c.b. If this is not the case then the most likely cause is a poor solder connection or open circuit on one of the p.c.b. tracks.

If all appears to be in order, the next task is to adjust the contrast setting on the l.c.d. display module by means of preset VR1. This should be adjusted until the display becomes just visible as a series of blank "blocks" in each character position.

The two output relays can be tested by temporarily "patching" a lead from pin 20 (5V) on the socket for IC3 to pins 9 and 11 in turn on the same socket. As the +5V is applied to each pin, the relevant relay should be heard to operate and the corresponding l.e.d. should illuminate.

This is about the extent of testing that can reasonably be performed so the next operation is to adjust presets VR2 and VR3 so that the analogue-to-digital converter (IC4) is correctly configured. This can either be done using the "default" settings described earlier in the text, or using the more accurate calibration procedure which is given in the following section.

The unit should now be powered down and the remaining integrated circuits (IC3 and IC4) inserted in their respective sockets.

Microcontroller IC3 should, of course, already be pre-programmed with the controlling software – see later.

Both power sources can now be re-applied and if all is well, the unit should display an initial time and temperature on the upper line of the l.c.d. and the status of the "CH" and "HW" outputs on the lower line.

TEMPERATURE CALIBRATION

As mentioned earlier, the nominal output of the LM335 temperature sensor is $10mV/K$, although this may differ slightly between devices. The only thing that can be guaranteed is that at a temperature of absolute zero ($-273^{\circ}C$) the output of the device will be 0V. (*Don't try to check this assertion! Ed.*) To compensate for slight differences, the settings of VR2 and VR3 can be optimised as follows:

- Measure the voltage at IC4 pin 2

- Note the ambient (room) temperature in °C
- LM335 output = measured voltage/ (measured temperature + 273)
- VR2 wiper setting (V) = LM335 output × 253
- VR3 wiper setting (V) = LM335 output × 63.75

USING THE CONTROLLER

The Central Heating Controller is simple to use in that each switched output only has four basic modes of operation:

- OFF Output off all the time
- ON Output on all the time
- T2 Output on for two periods each day
- T1 Output on for one period each day

The desired output mode is set by means of the CH and HW front panel switches. Pressing these will cycle through the available options with the user choice being displayed on the lower line of the I.c.d.

PROGRAMMING THE CONTROLLER

Before the Controller can be used, it is necessary to program the current day of the week and the current time into its memory. If the following preset switching times are not satisfactory, these may also be reprogrammed

- Central heating ON (Period 1) 06:30
- Central heating OFF (Period 1) 08:30
- Central heating ON (Period 2) 16:30
- Central heating OFF (Period 2) 21:30
- Hot water ON (Period 1) 06:30
- Hot water OFF (Period 1) 08:30
- Hot water ON (Period 2) 16:30
- Hot water OFF (Period 2) 21:30

It should be noted that when the unit is in T1 mode, i.e. one On period per day, the On time is given by the appropriate Period 1 On time and the Off time by the appropriate Period 2 Off time.

TIME SETTING

The current day and time is set as follows:

1. Press SET. The upper line of the display will go blank and the lower line will prompt you with "TIME ?"
2. Press YES. The upper line of the display will show the first two letters of the day of the week, e.g. "MO" for Monday
3. Increment the day to the correct setting by repeatedly pressing CH
4. Press SET to confirm the day setting. The upper line of the display will now also show the time in the form of "hh:mm" where "hh" is hours and "mm" is minutes
5. Increment the hours to the correct value by repeatedly pressing CH
6. Increment the minutes to the correct value by repeatedly pressing HW
7. Press SET to confirm these settings and return to the main display. Note that as SET is pressed, seconds are set to zero so the clock can be synchronised to an external time source if required.

SETTING FUNCTION TIMES

Setting the program function times follows a similar procedure:

1. Press SET. The upper line of the display will go blank and the lower line will prompt you with "TIME ?"
2. Press SET again. The lower line of the display will prompt with "PROG ?"
3. Press YES. The lower line of the display will show "MO" for Monday
4. Increment the day to the correct setting by repeatedly pressing CH
5. Press YES when the correct day for which you wish to set the program times is shown. The upper line of the display will show "CH 1 ON hh:mm", where "hh:mm" is the currently set time in hours and minutes
6. The time setting can be changed by means of CH and HW as described earlier, although it should be noted that the program times can only be incremented in 10 minute steps
7. Press SET when the correct time is showing. The display will now show "CH 1 OFF hh:mm". This time can also be altered as explained above
8. Step 7 can be repeated until all the program times have been programmed. After "HW 2 OFF" has been programmed, pressing SET will return you to step 4 with the next day showing, e.g. "TU"
9. You now have a choice of repeating steps 5 to 8 for the day shown, or returning to the main display by repeatedly pressing CH until Sunday (SU) has been and gone!

Note that it is not possible to "escape" from a sequence once you are in it, it must be completed, though this can be done by repeatedly pressing SET without having to change other settings.

Also, be aware that the unit does not have the capability to check if the times you have entered are valid times, and to avoid erroneous operation you should adhere to the following rules:

- All On and Off times should be programmed in a single 24 hour period i.e. between 00:00 and 23:59
- On times for a particular period should be before the corresponding Off time
- Period 1 Off times should occur before the Period 2 On time

THERMOSTAT SETTING

To set the thermostat temperature, follow this procedure:

1. Press SET. The upper line of the display will go blank and the lower line will prompt you with "TIME ?"
2. Press SET again. The lower line of the display will prompt with "PROG ?"
3. Press SET again. The lower line of the display will prompt with "TEMP ?"
4. Press YES. The upper line of the display will show "+xx°C", where "xx" is the currently set thermostat temperature in degrees Celsius.
5. The temperature setting can be changed by means of the CH key. It only counts upwards; to set a lower temperature than that shown, CH must be repeatedly pressed until the start of the cycle at -20°C appears following +43°C
6. When the desired temperature is displayed, press SET to return to the main display

If you do not require the thermostat facility on the Central Heating output, then setting the thermostat to the maximum (normally unattainable!) temperature of +43°C will to all intents and purposes achieve this.

INSTALLATION

Installation of the Central Heating Controller should be straightforward but will to a great degree depend on the nature of the rest of the central heating and domestic hot water system. It should be noted that if the central heating system does not allow heating to be on without hot water i.e. gravity fed, then care should be taken to ensure that the unit is programmed correctly to reflect this.

As an added precaution for mains powered solenoid valves, the CH output should be wired through the HW output as shown in Fig. 7. If there is any doubt at all about how the Central Heating Controller should be installed, then it is recommended that a qualified central heating engineer should be consulted.

As mentioned earlier, the temperature sensor, D2, can be remotely mounted and if this option is used then twisted cable should be used with a maximum cable length of five metres. The sensor can be insulated by using adhesive filled heat shrink tubing.

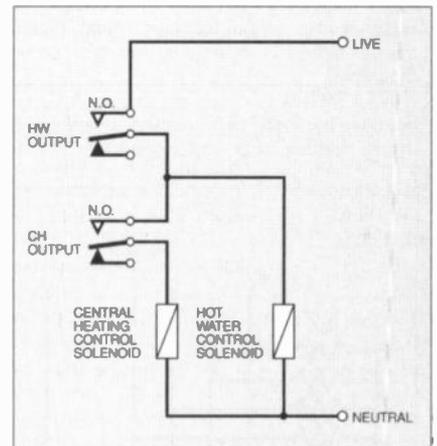


Fig. 7. Safety interlock wiring example.


SOFTWARE

Pre-programmed microcontrollers for this design are available direct from the author for £20 all inclusive, see *Shoptalk* page.

The software is also available on a 3.5 inch disk from the EPE Editorial office for £2.50 to cover admin costs (the software itself is free). This disk also includes software for other recent EPE projects - see *EPE PCB Service* page for details.

Alternatively, Internet users can download the software free from our ftp site: <ftp://ftp.epemag.wimborne.co.uk>. There are five files, totalling just under 20K bytes, held in the directory named "Heating" - you need all five.

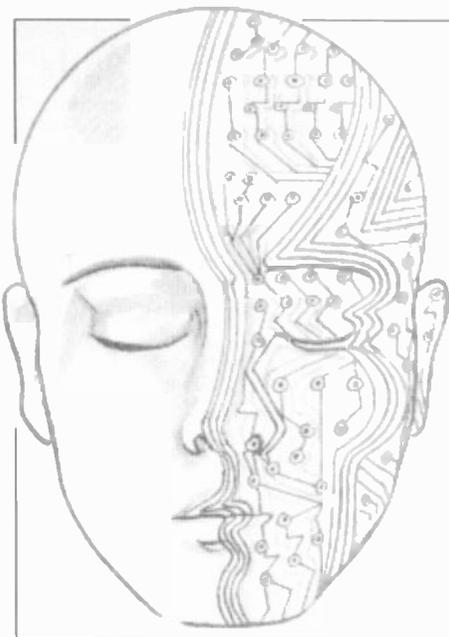Note that the software has been written in "C" and that in order to program the microcontroller, you need a programmer which is intended for use with the Atmel 89C2051 microcontroller (the PIC programmers recently published in *EPE* are not suitable).



Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit tips, not simply mechanical or electrical ideas. Ideas *must be the reader's own work* and **not have been submitted for publication elsewhere**. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should preferably be typed or word-processed, with a brief circuit description showing all relevant component values. Please draw all circuit schematics as clearly as possible.

Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. They could earn you some real cash!

8-bit Binary-to-Decimal Converter

— handy test project

THE design illustrated in Fig. 1 is one which I created to help me when testing a number of digital projects using 8-bit data buses. The decimal value of the eight input lines is displayed on three 7-segment displays. Whilst chips exist to perform this function for single displays, none include the possibility of displaying numbers greater than nine.

No EPROM is necessary in this design. It operates by using two counters synchronised to one another, one which generates an 8-bit

binary output and a second counter which drives the display. If the display is only updated when the binary counter is at the same value as the input, then the display will show the decimal value of the input.

IC4 is the binary counter and IC6 to IC8 form the display/counter section. IC5a and IC5b form the astable which clocks both counters at some 5kHz. The minimum display refresh rate is therefore 20 times per second. IC1 and IC2 are two 4-bit comparators, ganged to form an 8-bit comparator.

This compares the output of the binary counter IC4 with the binary input taken from the circuit under test. Resistors R1 to R8 pull down the input lines to prevent them floating when no input is connected.

When the comparator inputs are equal, pin 6 of IC2 goes high, triggering the monostable IC3ab which outputs a brief pulse. This latches the value of the display counters IC6 to IC8 to the display. When IC4 reaches a value of 256, the link between pins 11 and 12 resets the chip, and this resets the display counter also.

*Tom Baldwin,
Romsey, Hants.*

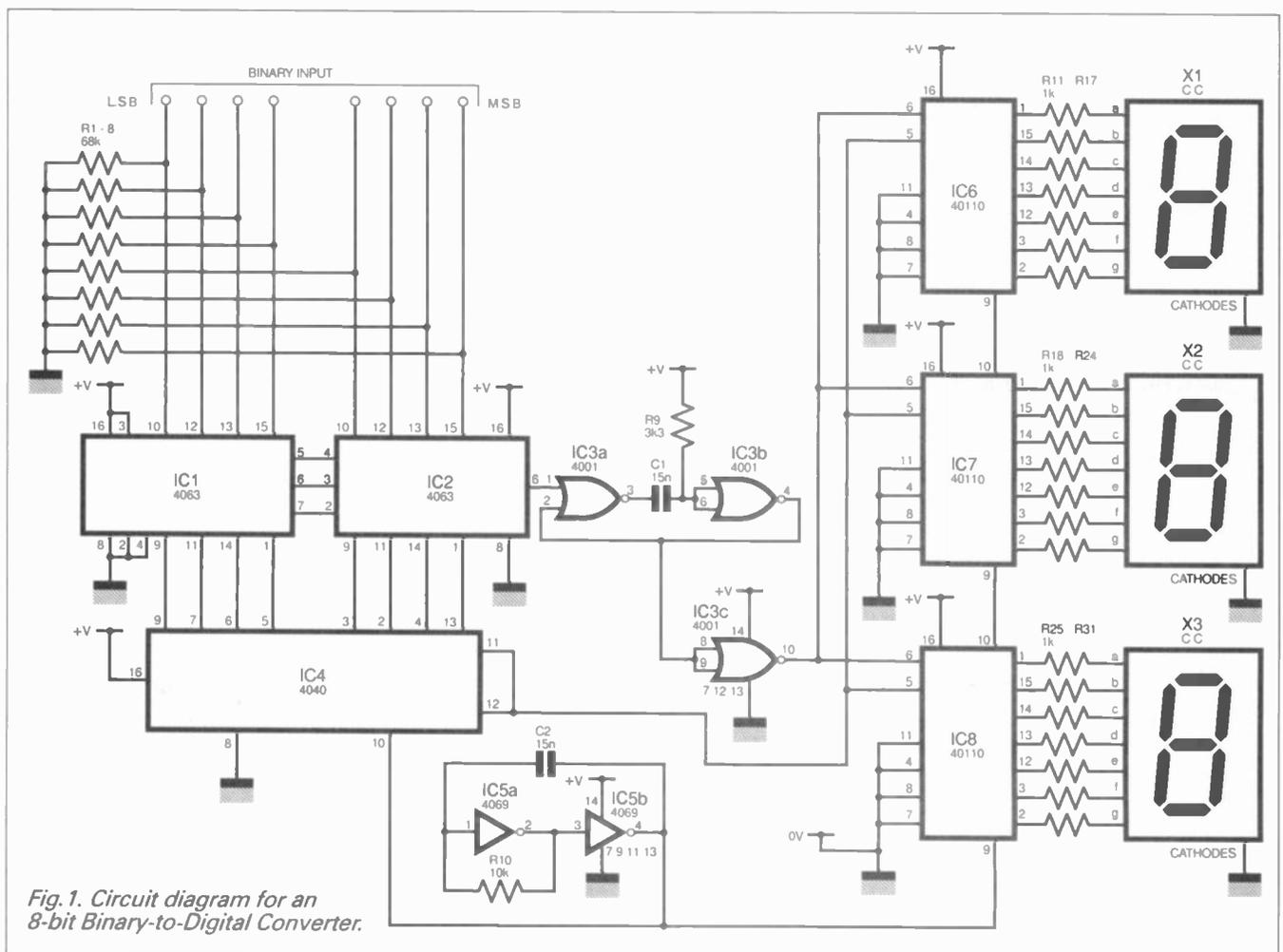


Fig. 1. Circuit diagram for an 8-bit Binary-to-Digital Converter.

L.E.D. Quick Test

— check in a flash

My idea for a handy unit to quickly check l.e.d.s. is shown in Fig.2. The circuit was intended as a simple one to enable it to be used at Radio Rallies for spot testing of bulk surplus l.e.d.s. A flashing l.e.d. is used (D1) with a 9V battery, and is connected to a coaxial socket.

By placing a test l.e.d. across the socket (anode to the inner conductor), both the flashing l.e.d. and the test l.e.d. will flash. No on-off switch is necessary.

Mark McGuinness,
Clondalkin, Dublin, Ireland.

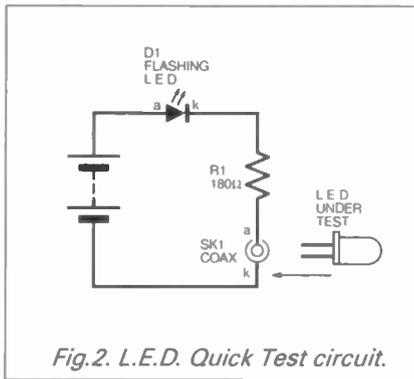


Fig.2. L.E.D. Quick Test circuit.

Model Railway Level Crossing Lights

THE small circuit of Fig. 3 is for use on model railway layouts and approximates the flashing light signals used at level crossings. It is operated by a reed switch (S1) embedded in the track, which is closed by a magnet on the underside of a passing train. This triggers the monostable timer IC1, which powers a Darlington transistor pair TR1 and TR2.

Diodes D1 and D2 (orange) illuminate and also TR3 and TR4, connected as an astable, cause the red l.e.d.s D3 to D6 to flash alternately for about six seconds, enough for the train to pass. One set of l.e.d.s is used on each side of the level crossing, for added realism. 3mm l.e.d.s are best for "00" scale.

Peter Gent (14),
Sutton, Surrey.

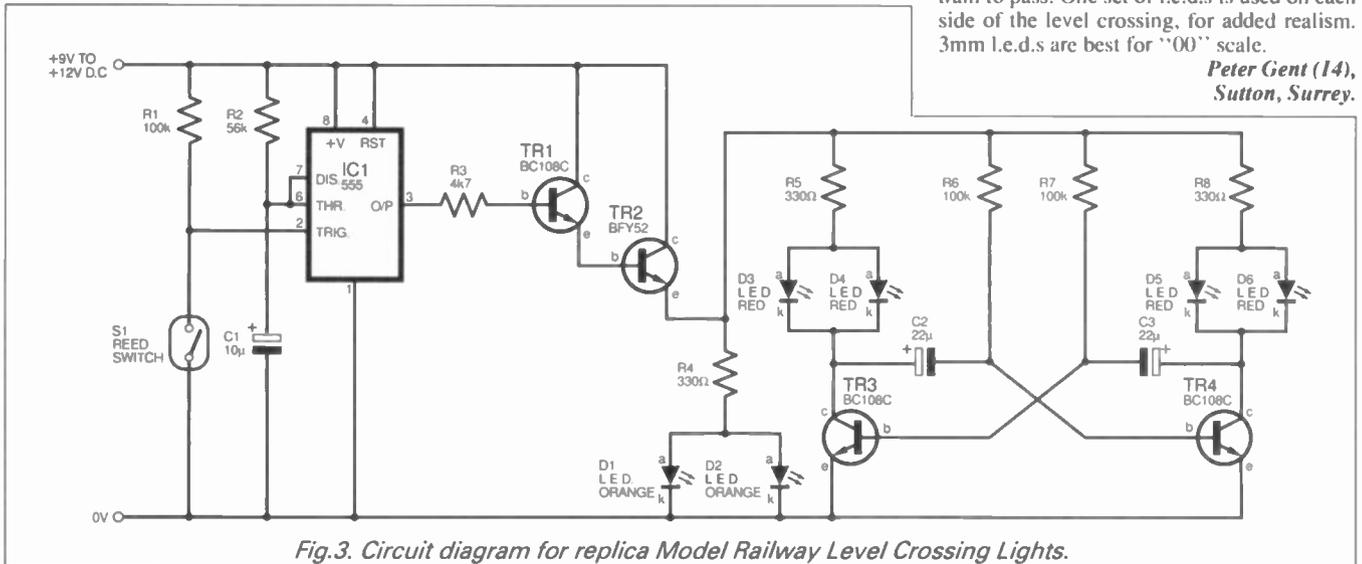


Fig.3. Circuit diagram for replica Model Railway Level Crossing Lights.



Longwave Audio

Jake Rothman

93 St Johns Road, Frome,
Somerset BA11 2BE.
Tel. 01373 451 818.

Supplier of Theremins and unusual audio/music items.

EPE & MIDI Interface Theremin Parts:-	
Complete Theremin	£645.00*
Fully built and tested circuit board with front panel	£210.00*
PCB	£22.00
Front panel	£12.00
Theremin Box with all fixings (assembled and ready for PCB and front panel)	£300.00*
Mk 1 Theremin Box (unfinished & not assembled)	£25.00*
Loudspeaker	£4.00
Coils - 100µ, 330µ, 1mH	56p
Trimmer caps	58p
Pots	75p
Knobs	35p
Mic stand attachment	£6.99*
Power supplies 15V	£15.00*
Hand-Forged aerial plus mount assy	£35.00*
Theremin Manual	£5.00
THEREMIN data pack	£19.99*
MIDI MCV1a complete	£599.99*
MCV1a PCBs	£40.00*
MCV1a Chip set (U1..U9)	£70.00
A-563H-12(DS1)	£2.10
MCV1a Chassis & Fixing kit (HW1)	£45.00
12V AC power supply for MCV1a	£15.00*
MIDI MCV1a Manual	£5.00
Mk 1 Theremin PCBs, ideal for experimenters	£5.99
Original Modern Electronics Manual article copy	£1.99
Perspex control panel for Mk1 and Mk2	£7.99
18V AC power supply	£5.00*
Aerial assy.	£15.00

Some assembled and tested boards available:-
EPE Pocket Theremin PCB £45.00
Mk1 Modem Electronics Manual Theremin PCB £85.00
MkII Theremin PCB £130.00*
Pocket "rubber duck" aerial £2.00

Audio Parts:- all less than a third of distributor prices!
Many unobtainable parts - here are a few examples.

Capacitors	
100µF 20V hermetic metal case	
tantalum	85p
10µF 50V STC tantalum bead	25p
22nF 63V 1% Philips polystyrene	25p
4n7 160V 1% Philips polystyrene	10p
220n 400V metal-cased polycarbonate ATMC	75p

Mil-spec pots, why use short-life sprayed carbon track pots?

4k7 cermet anti-log ideal mic.amp. gain control	£1.20
10k lin Allen Bradley EJ series, 1 million cycles life	£1.50
25k lin Bourns 81 series	£1.20
Alps motorised stereo pot, 50k LOG	£5.00
100k Balance control Zero centre-loss	£2.00
Calrostat sub min RV6 conductive plastic 50k LIN	£1.50
Elma 01 Gold plated 6-way stereo selector switches	£5.00
RA53 Theremistor for ultra low distortion AF oscillators	£3.00

Lots of unusual analogue parts at low cost available.

Please ask for specific lists:- tantalum caps, film caps, silver mica, pots, carbon composition resistors, germanium transistors, audio semiconductors, valves or switches.

Please allow up to 28 days for delivery. No VAT. P + P £2.50 on items marked* all other items free. Make cheques payable to J M Rothman.

TRANSMITTERS

NEW Fully comprehensive guide to building and using short/medium range radio transmitters and receivers. Includes detailed and practical information on all aspects of construction, from simple FM room transmitters to more sophisticated and powerful audio and data transmitters.

Manual includes:

- ▶ **AM, FM and UHF Transmitters** from micro power up to 3 Watts. Covers simple 'bugs' as well as circuits operating on 27MHz and 418MHz etc.
- ▶ **TRACKING AND SIGNALLING.** How to build micro circuits for finding animals, cars etc.
- ▶ **CRYSTAL CONTROLLED TRANSMITTERS.** High stability circuits.
- ▶ **RADIO PAGER AND RADIO CONTROL.** How to build coded radio keys, multi-channel remote controls, radio alarms etc.
- ▶ **RECEIVER CIRCUITS.** Wide range of receiver projects for building high security audio links and transceivers.
- ▶ **EXTENSIVE** assembly information. Includes sections on construction, testing, mics, aerials, coils and miniaturisation.

Over **100** detailed PCB, strip-board and point to point designs. Manual comes with **FREE** micro transmitter PCB.

(Some of the circuits included in the manual may not be used legally in the UK).



Make cheques/POs payable to
JCG ELECTRONICS

P.O. Box HP79, Woodhouse Street, Leeds, LS6 3XN.

Wide range of Audio/Radio kits available.
Send stamp for list. Mail order only.

£8.95
inc. p&p



New Technology Update

Reliability becomes one of the key words with the introduction of a special range of "lead frame base" modules – reports Ian Poole

CIRCUIT modules can be used in a number of niche applications. They are usually manufactured by placing surface mount components (s.m.d.s.) onto a substrate which is then encapsulated to provide protection. Often the packages are costly and cannot be repaired if they fail, although this is no different to an i.c.

One example of an area where modules are widely found is for crystal oscillators which are used in a wide variety of applications where accurate signals are needed. Often they are manufactured as small modules which can be sold separately and mounted directly onto boards. Another area is for d.c.-to-d.c. converters.

Whilst this approach enables items like these to be bought in by equipment manufacturers, they have two main drawbacks. These mainly arise because the techniques used in manufacturing do not lend themselves to automatic assembly. The first is cost, and the second is equally important, and is the reliability.

Reliability

Reliability is a particularly important factor in today's electronics industry. Fortunately, the quality of electrical goods is improving all the time. Television sets are a very good example. In the days of valve sets, it was not uncommon to have the repair man visit two or three times a year.

The introduction of semiconductors brought about an improvement, but even then a large number of repairs were required. After the Japanese manufacturers entered the market with very high quality goods, this forced other manufacturers to follow suit. Nowadays it is not uncommon to have a TV set work for ten years or more without the need for repair.

The reliability of a product is obviously dependent upon the workmanship whilst it is being built. However, it is far more dependent upon the design and methods used in production. Poor design may over stress a component which fails after a while. Alternatively, a poor production process will leave many latent faults in the equipment which may appear at any time.

It is for this reason that any new method used in manufacturing modules needed to be carefully designed and appraised before being introduced to the production line.

Lead frame base

In view of the problems with existing modules the Power Management group at National Semiconductor set up a study to investigate better methods of manufacturing modules.

Their aims were to produce a module which was in an i.c. package. It would need

to be possible to automate the manufacture of the package, and its cost would need to be comparable with that of an i.c.

The solution has been developed using a 24-pin dual in-line i.c. package, and it measures no more than 6mm above the board, making it ideal for a wide variety of applications. The inside consists of a "lead frame system" on which the components are mounted.

This does not have a substrate or insulating base material to act as a support for the lead frame. The plastic which is moulded around it gives the support. Areas where components are to be soldered are silver plated to give increased solderability.

the moulding process. The temperatures involved damaged many components and they could not be used.

To overcome this problem a number of special components were developed, and some existing ones were modified to cope with the very high temperatures. Coils particularly broke down under temperature with short circuit turns or the ferrites were damaged. A number of new techniques were used in the coil manufacture and this has cured the problem.

Capacitors now represent the major limitation to the technology. The physical size required for some capacitors means that they cannot be used. This limits the largest values which can be incorporated.

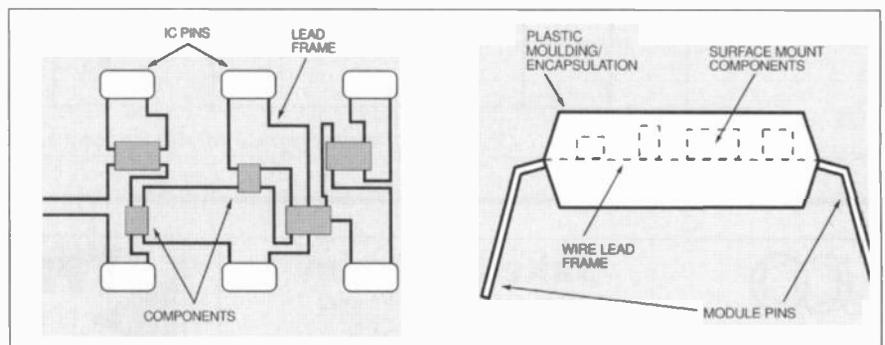


Fig. 1. Basic construction of a lead frame based module

One limitation of the system is that all the nodes must be brought out to the pins on the i.c. package because there are no mechanical supports for "internal islands". This limits the number of nodes in the circuit to only 24.

Nevertheless, this is quite sufficient for many small circuits and is unlikely to be a major limitation in the short term. At the moment even the full capacity of 24 nodes is not likely to be used. This is because the size of the internal components limits the complexity of the circuits which can be contained in the package.

Usually surface mount components are used. In the case of semiconductors the basic unpackaged die is used. The use of die instead of packaged semiconductors saves space in the module and also reduces costs if very large volumes are to be made.

Once the lead frame assembly has been assembled, it has plastic moulded around it. This gives the frame its strength and enables the required levels of reliability to be achieved.

Hurdles

One of the major problems encountered with the system was to find capacitors and inductors which could withstand

Current Usage

The new technique is being used for some d.c.-to-d.c. converters. In this manufacture yields of over 95 per cent have been achieved which is better than many i.c. processes.

Life testing has also been carried out and it has been calculated that the reliability of the modules will exceed expectations. Their reliability is now compared to that of an i.c. which is operating well within its limits.

Heat dissipation capacity is an important factor. Current experiments show that relatively high levels of power can be dissipated. There are two reasons for this. The first is that the components are distributed around the package and not in contact with one another. The second is that the lead frame provides a means by which the heat can be extracted from the package. As relatively wide tracks are used, heat conduction is good.

A further advantage is that the use of standard components has shown that many designs give improved performance with regard to electro-static discharge (e.s.d.). In view of the possibilities and the low costs involved, it is likely that many more of these products will be seen in the near future.



Is your PCB design package not quite as "professional" as you thought? Substantial trade-in discounts still available.

Board Capture

Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

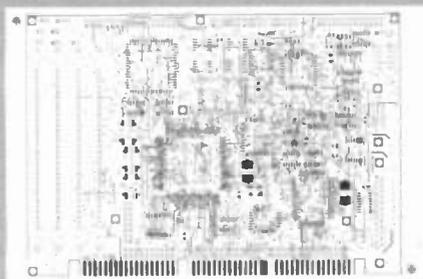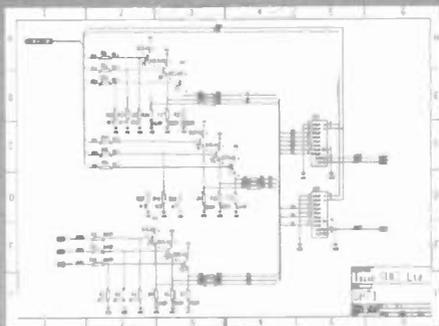

BoardMaker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1
- Full netlist support- BoardCapture, OrCad, Scherma, Tango CadStar
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with jack annotation
- Report generator- Database ASCII, BOM
- Thermal power plane support with full DRC

£395

Board Router


Gridless re-entrant autorouter

- Simultaneous multi-layer routing
- SMC and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

Output drivers - Included as standard

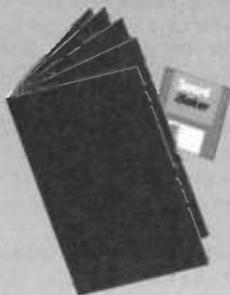- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Perplotters - HP, Grahtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)



All trademarks acknowledged

For further information contact
 Tsien (UK) Limited
 Aylesby House
 Nenny Road, Chatteris
 Cambridge, PE16 6JT
 Tel 01354 695959
 Fax 01354 695957
 E-mail Sales@tsien.demon.co.uk



tsien

EPE ELYSIAN THEREMIN WITH MIDI BOX

JAKE ROTHMAN

PART 1

From being the sensation of the 20s the Theremin is about to be the hit of the 90s!

Already in demand for "live performances" and for studio sound tracking.

FOLLOWING the soaring success of the simple, pocket sized, Theremin we are proud to present a "full-spec" design for the serious professional "musician" or studio user. As far as we can tell we believe the *EPE Elysian Theremin* is the first ever design with a MIDI Interface (details in January and February 1997 issues).

SIMPLE THEREMIN

In September last year *EPE* published a *Simple Theremin* design which became the world's first commercial pocket design (the Sept '95 issue is completely "sold out" so we can only offer a photostat copy of the article - see "Back Issues" page - Ed). Its low-cost gave many people a taste of the instrument for the first time.

However, to achieve the low retail price the pocket Theremin did not have a volume aerial. This meant that the volume had to be controlled by other means, such

as a foot pedal. The original RCA Theremins had a special loop which controlled the volume by hand capacitance, enabling the volume to be controlled by free-space hand movement as well as the pitch.

THEREMIN - THE LEGEND

Since the Theremin has received a lot of media attention recently, a whole mythology has been built up by non-technical people. Stories about Leon Theremin's abduction by the KGB and of inventing a colour television system in 1920s abound.

It is not *EPE's* job to elaborate on such conjecture, but to explain the technical details involved. Suffice it to say, it is the author's opinion that Theremin simply developed the well known radio phenomena of "hand capacitance" and the whistles that often accompanied it.

BASIC PRINCIPLES

The simplest Theremin consists of two radio frequency (r.f.) oscillators being mixed together, demodulated and then amplified as shown in Fig. 1.

Making the frequency of the oscillators higher increases the sensitivity although the tendency to instability increases. Aerial size also plays an important part since capacitance is proportional to area.

VOLUME CONTROL METHODS

The volume control has always been the most difficult aspect of Theremin design and virtually every commercial instrument has used a different approach. It is worth discussing briefly the circuits involved since they are all quite unique.

There have been basically five different methods used so far: damped oscillator; resonant plate; capacitive potential divider; dual-Theremin and finally phase control.

Damped Oscillator

This is the original method used in the RCA Theremin in the thirties. In this circuit the amplitude of a high frequency oscillator becomes damped or reduces as the hand approaches the aerial. This was then amplified to a few watts power to feed the heater of a directly heated triode valve. This enabled the brightness of the heater to vary with the oscillator output.

When the hand was near, the heater was almost cold, giving minimum volume. With the hand far away, full oscillator output was obtained giving full brightness, maximum electron emission and hence full volume. This valve circuit could be thought of as a crude form of voltage controlled amplifier or VCA for short.

One problem with this system was that there was a delay due to the thermal heating time of the filament and still today most Theremin parts are for slow sustained notes rather than percussive staccato

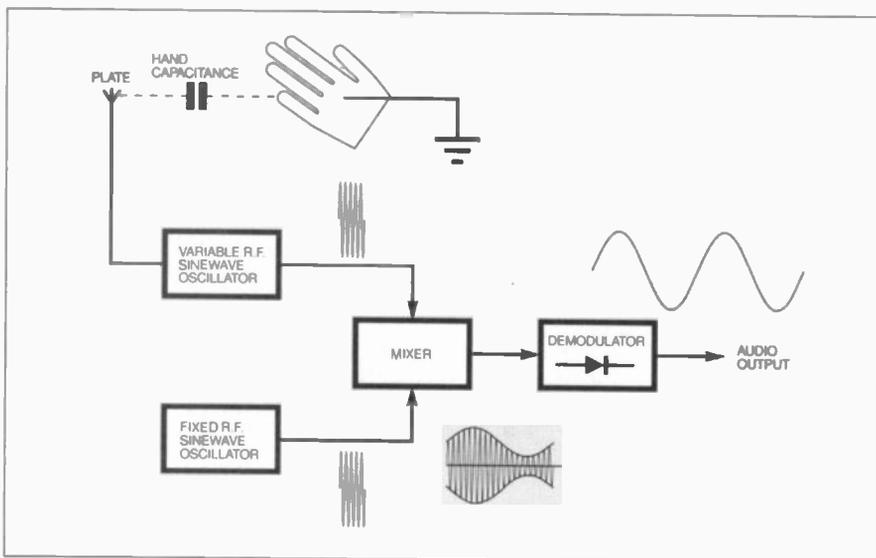


Fig. 1. Block diagram for a simple Theremin.

EVERYDAY
PRACTICAL
ELECTRONICS


READERSHIP SURVEY

We are determined that EPE will continue to be the leading UK publication in this market. To achieve this it is vital that we keep up-to-date with the interests and needs of our readership.

I would be grateful, therefore, if you would spare a few minutes to fill in and return (by FREEPOST) this questionnaire.

Every reply received before November 25th will be entered in a draw for one of two £75 prizes.

Many thanks for your help.

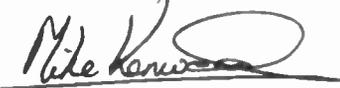
EDITOR



If you wish to enter the draw for one of two £75 prizes please print your name and address below. This information will not be disclosed to any third party.

Name.....

Address.....

.....

.....

The names of the prize winners will be published in the February '97 issue of EPE

P.S. The information you supply will be treated as strictly confidential and used only for the development of EPE.

PLEASE FILL IN THIS QUESTIONNAIRE AND SEND IT TO:

EPE, Wimborne Publishing Ltd
FREEPOST (SWB20080)
WIMBORNE
Dorset
BH21 1BR

No stamp is needed if posted in the UK

Section 1 - THE MAGAZINE

1. How did you first hear about *Everyday Practical Electronics*?

- Saw it in a newsagents
- Friend told me about it
- Saw it advertised
- Saw it at an exhibition / club

Other (please specify).....

2. How did you get this copy of *Everyday Practical Electronics*?

- Went to the shop especially to buy it
- Saw it in a shop and decided to buy it
- I have it on subscription Please go to Question 4.

- Newsagent saved it / delivered it for me
- A friend gave it to me

Other (please specify).....

3. Where do you usually buy your copy of *Everyday Practical Electronics*?

- W H Smith / John Menzies
- Other Large Newsagent Chains
(Martins, Forbuoys)
- Local Shop
- Rail/Tube Station Kiosk
- Supermarket

Other (please specify).....

4. How long have you been reading *Everyday Practical Electronics*?

- This is the first issue
- 3 to 6 mnths
- 6 mnths - 1 yr
- 1 to 2 yrs
- 2 to 3 yrs
- 3 years +

5. How many issues of *Everyday Practical Electronics* have you read in the last 12 months?

- 1 - 3 7 - 11
- 4 - 6 Every issue Please go to Question 7.

6. What made you buy this issue of *Everyday Practical Electronics*?

- I buy every issue
- The cover looked interesting
- Somebody else bought me the title
- A friend recommended it
- For a particular article/project
- To see the advertisements

Other (please specify).....

7. How many other people read your copy of *Everyday Practical Electronics*?

- No one else reads it
- 1 to 2
- 3 to 4

More than 4 (please specify).....

8. *Everyday Practical Electronics* is £2.45.

How do you rate it in terms of value for money?

- Very good value for money
- Fairly good value for money
- Poor value for money
- Very poor value for money

9. Have you ever had a problem finding *Everyday Practical Electronics* in a shop?

- Often
- Sometimes
- Never

10. Please indicate which of the following regular items you find of interest?

	Very interesting	Quite interesting	Not interesting
Teach-In/Theory Series and Features	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Ingenuity Unlimited	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Circuit Surgery	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Interface	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Techniques	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Net Work	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Innovations	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
New Technology Update	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Fox Report	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Ohm Sweet Ohm	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Advertisements	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

11. Please indicate which articles in this issue of *Everyday Practical Electronics* you found of interest?

	Very interesting	Quite interesting	Not interesting
Theremin	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Central Heating Controller	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Scratch Filter	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
DC to DC Converters	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Build Your Own Circuits	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

12. Which of the following types of projects are you interested in?

	Very interested	Quite interested	Not interested
Radio	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Computing	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Test Gear	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Alarms	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
PIC based/Microcontrollers	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Audio/Hi-Fi	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Musical	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Car	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Household	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Games/Toys	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Robots	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Metal Detecting	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Boating	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
RC Models	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
Photographic	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
TV/ Video	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Other (please state).....

13. Are there any particular projects which you would like to see featured? (Please specify)

.....

.....

14. On the whole, how would you describe the complexity of the projects in *Everyday Practical Electronics*?

- Too simple
- About right
- Too complex

15. How do you rate the cost of building *Everyday Practical Electronics* projects?

- Inexpensive
- Reasonably priced
- Slightly overpriced
- Far too expensive

16. How many purchases have you made by mail order from advertisers in the magazine in the last year?

- 1 - 3
- 4 - 6
- 6 or more
- None Please go to Question 18

17. How much have you spent on these products in the last year?

- £1 - £15 £51 - £75
- £16 - £30 £76 - £100
- £31 - £50 Over £100

18. How often do you buy each of the following electronics magazines?

Subscribe Regularly Occasionally Never

- | | | | | |
|----------------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| Electronics and Wireless World | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Electronics: The Maplin Magazine | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Electronics Today International | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Elektor Electronics | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Practical Wireless | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |

Other (please state).....

19. Do you read or look at any of the following daily newspapers regularly (at least 4 times per week), occasionally or never?

Regularly Occasionally Never

- | | | | |
|-----------------|--------------------------|--------------------------|--------------------------|
| Daily Express | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Daily Mail | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Daily Mirror | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| The Sun | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Daily Telegraph | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| The Guardian | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| The Independent | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| The Times | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| The Scotsman | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| Local Newspaper | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |

Other (please state).....

Section 2 - YOUR HOBBY

20. How much have you spent on electronics over the last year?

- | | | | |
|-----------|--------------------------|-------------|--------------------------|
| £0 - £20 | <input type="checkbox"/> | £81 - £100 | <input type="checkbox"/> |
| £21 - £40 | <input type="checkbox"/> | £101 - £150 | <input type="checkbox"/> |
| £41 - £60 | <input type="checkbox"/> | £151 - £200 | <input type="checkbox"/> |
| £61 - £80 | <input type="checkbox"/> | Over £200 | <input type="checkbox"/> |

21. Do you belong to any of the following groups / associations?

- RSGB
- IEEE
- BAEC

Any other electronics/computing club or association

(please specify).....

.....

22. On average, how many hours a week do you spend on electronics, in your spare time?

- 1 - 4 hours
- 5 - 8 hours
- 9 - 16 hours
- Over 17 hours

23. How long have you been involved in electronics?

- | | | | |
|----------------|--------------------------|---------------|--------------------------|
| 0 - 12 months | <input type="checkbox"/> | 4 - 6 years | <input type="checkbox"/> |
| 13 - 24 months | <input type="checkbox"/> | 7 - 10 years | <input type="checkbox"/> |
| 2 - 3 years | <input type="checkbox"/> | Over 10 years | <input type="checkbox"/> |

24. How would you describe your skill level?

- Beginner
- Intermediate
- Advanced
- Expert

25. Do you have access to a PC compatible computer?

- I own a computer but it is not PC compatible Please go to Q27
- Yes, I own a PC
- Yes, at work
- Yes, at school/college
- Yes, I use a friend's PC
- I do not have access to a computer Please go to Q27

26. Does the computer have a CD-ROM drive?

- Yes
- No

27. If you do not own a PC compatible computer do you intend to buy one?

- Yes, in the next year
- Yes, at sometime
- No

28. Do you have access to the Internet?

- Yes, through my computer
- Yes, at work
- Yes, at school/college
- Yes, through my friend's computer
- No

Section 3 - ABOUT YOU

This section allows us to look at who buys *Everyday Practical Electronics*. Please note that your answers are *strictly confidential* and will only be used for the purposes of developing *Everyday Practical Electronics*.

29. Are you:

Male Female

30. How old are you ?

Under 16	<input type="checkbox"/>	30 - 39	<input type="checkbox"/>
16 - 18	<input type="checkbox"/>	40 - 49	<input type="checkbox"/>
19 - 21	<input type="checkbox"/>	50 - 59	<input type="checkbox"/>
22 - 29	<input type="checkbox"/>	60 +	<input type="checkbox"/>

31. What is your marital status

Single
 Married
 Living with partner
 Separated / divorced
 Widowed

32. How many children do you have ?

none	<input type="checkbox"/>	3	<input type="checkbox"/>
1	<input type="checkbox"/>	4 or more	<input type="checkbox"/>
2	<input type="checkbox"/>		

33. Do you work ?

Full time	<input type="checkbox"/>	Self employed	<input type="checkbox"/>
Part time	<input type="checkbox"/>	Unemployed	<input type="checkbox"/>
Housewife	<input type="checkbox"/>	Retired	<input type="checkbox"/>
Student	<input type="checkbox"/>		

34. The following question on annual income helps us to complete the picture on the demographic composition of our readers. What is your total household income?

Under £2,500	<input type="checkbox"/>
£2,501 - £5,000	<input type="checkbox"/>
£5,001 - £7,500	<input type="checkbox"/>
£7,501 - £10,000	<input type="checkbox"/>
£10,001 - £15,000	<input type="checkbox"/>
£15,001 - £20,000	<input type="checkbox"/>
£20,001 - £30,000	<input type="checkbox"/>
Over £30,000	<input type="checkbox"/>

35. Where do you live? (See map)

North
 Yorkshire / Humberside
 East Midlands
 East Anglia
 South East (excluding London)
 Greater London
 South West
 West Midlands
 North West
 Wales
 Scotland
 Ireland

Overseas (please specify)

36. Do you have any electronics-related qualifications?

No qualifications
 GCSE
 A Level
 City & Guilds
 BTEC
 Degree

Other (please specify).....

37. How would you describe your present involvement in electronics?

It's my hobby
 I am a student trainee
 I am a technician/service engineer
 I am a professional engineer/designer

Other (please specify).....

38. In which of the following activities do you regularly participate?

Eating out	<input type="checkbox"/>	Computing	<input type="checkbox"/>
Walking	<input type="checkbox"/>	Surfing the Internet	<input type="checkbox"/>
Gardening	<input type="checkbox"/>	Fishing	<input type="checkbox"/>
Model making	<input type="checkbox"/>	Home decoration/DIY	<input type="checkbox"/>
Reading	<input type="checkbox"/>	Radio Controlled Models	<input type="checkbox"/>

Sport (please specify).....

The responses to all of these questions are strictly confidential and will not be disclosed to any third party, but will only be used to help us to design and produce a better magazine for you.

If you have any further comments or suggestions to make regarding *Everyday Practical Electronics*, please write them here:



effects (although the MIDI Box should change this). Another problem was that the volume control had a *negative* control characteristic, that is the volume reduced as the instrument was approached.

This was not considered a problem at the time, since the Theremin was used as an instrument for "classical" music in conjunction with an orchestra. In this situation, as anyone who has seen a conductor will know, a downward movement of the hand signifies a decrease in volume and an upward motion an increase.

However, since Theremins have now taken off in pop and general electronic music, a positive characteristic is expected where the volume increases as the hand is brought closer. It is possible to obtain this characteristic by rectifying the output of the damped oscillator and inverting before feeding into the VCA. For those interested, a valve VCA is shown in Fig. 2.

The damped oscillator system works particularly well with valves because the high supply voltages used ensure that a large amount of "headroom" is available. A suitable circuit is shown in Fig. 3 for those wishing to build a valve Theremin.

With solid-state devices this system is not so effective since it is difficult to ensure a wide dynamic range, although this is not a problem if dual-rails of at least plus and minus 12V are used. This system is used in the Moog circuits.

Resonant Plate

Another volume control method is to use an oscillator feeding a tuned circuit comprising an inductor and the hand/plate capacitance (see Fig. 4). This

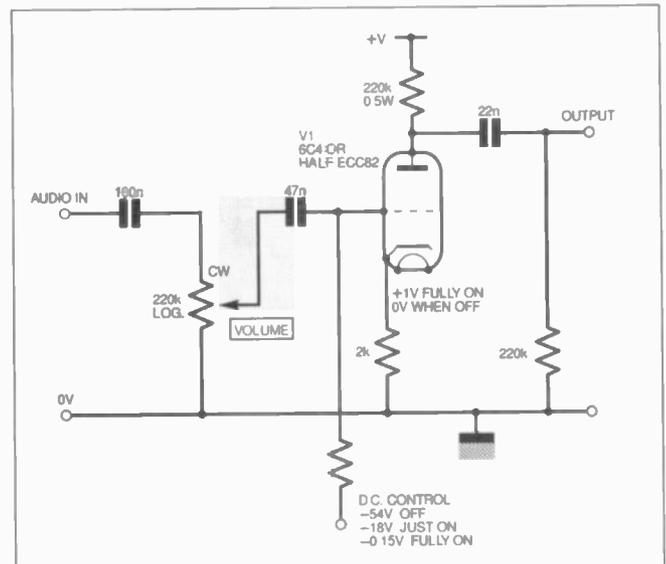
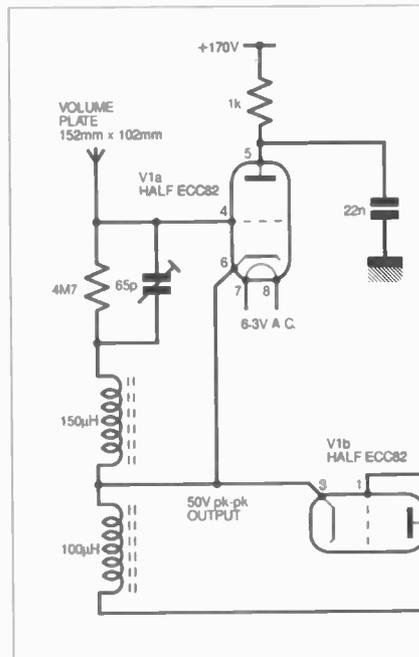


Fig. 2. Circuit for a valve voltage controlled amp. (VCA).

Fig. 3. Valve driven "damped oscillator" Theremin circuit.

system was used in the Theremin designed by the author for the *Modern Electronics Manual*.

This was the simplest circuit possible for a Theremin with a volume plate. However, as with all cheap and cheerful systems, the performance was compromised and the circuit only gave a range of a few inches and was quite abrupt and difficult to tune. This system was also used in the Babani circuit of the 1970s.

It is interesting to look at the developments of the next chart the commercial development of the original MEM first commercial Theremin called the Mk1 which was produced by Longwave Instruments.

Capacitive Potential Divider

The next stage in the development was to dispense with just rely on the capacitive potential divider effect, the

few circuits since these circuit into the UK's marketed and produced

the tuned circuit and principle of which

Features . . .

- * World First Midi compatible Theremin! Interfaces with Adam Fullerton's MIDI Box (Jan '97 issue - Order Your Copy - Now!)
- * Switched "volume direction" for Modern or Classical playing styles
- * Two "aerials" - Pitch and Volume
- * Varicap tuning for both aerials
- * All standard distributor components
- * Minimum inductor count
- * Continuous output for correct pitch monitoring
- * Headphone and speaker outputs
- * Industrial grade, plated-through-hole, p.c.b.
- * Uses standard, single-rail, wall-mounted, mains p.s.u.
- * For the advanced constructor (oscilloscope required)



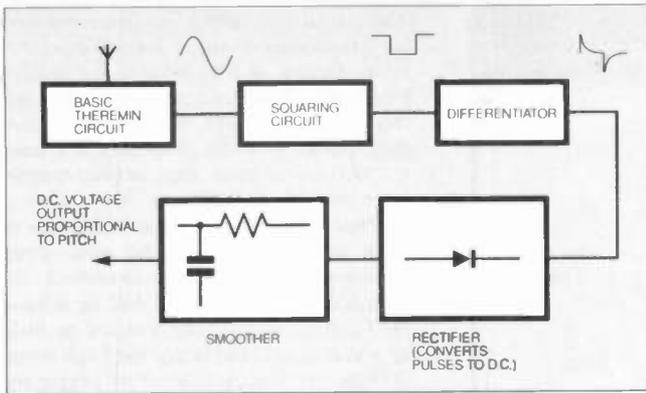


Fig. 7. Block schematic for a Theremin-to-voltage converter.

used on the highly regarded Tony Henk Theremins although these are still in the prototype stage and have not been "productionised" as yet.

FAKE SYSTEMS

All the preceding systems are true Theremin systems in that they respond to hand capacitance. A number of "fake" systems have appeared using infra-red, ultra-sound and microwaves which have the advantage of no interaction.

However, their wildly differing control laws make the instrument "feel" very different to a real Theremin.

OUTPUT WAVEFORM

The original Theremins generated a slightly asymmetric sinewave with a few per cent total harmonic distortion. Later models included special distortion circuits to increase the harmonics to emulate a Violin tone.

The use of a transconductance amplifier in single-rail mode generates the required

harmonics since it clips softly because it has no overall negative feedback. The asymmetries inherent in single-rail mode cause a slight bending of the waveform generating a few per cent of second harmonic distortion.

Below around 100Hz the waveform becomes more distorted due to the oscillators approaching lock and pulling on each other. Also, the filtering is less effective at low frequencies, this means that


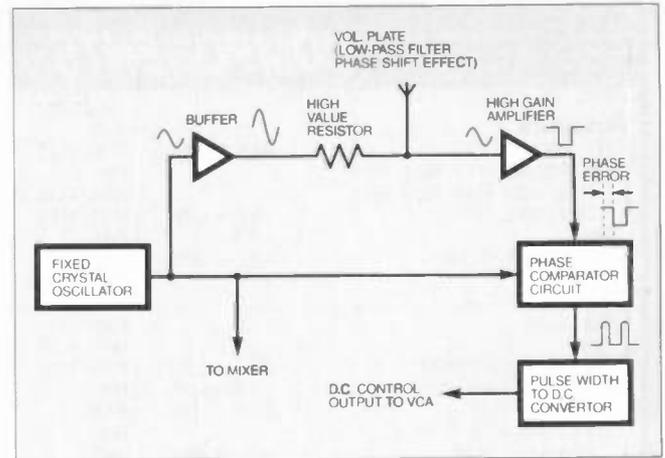


Fig. 8. Phase detector volume control system.

the Theremin sounds more "buzzy" at the low end as the waveform becomes more of a ramp. However, at higher audio frequencies the Theremin generates that characteristic smooth ethereal tone.

CIRCUIT DESCRIPTION

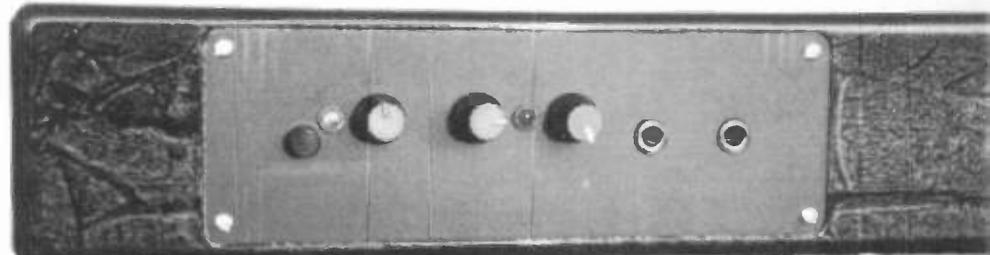The final block diagram of the whole EPE Elysian Theremin is shown in Fig. 9.



Front panel control layout.

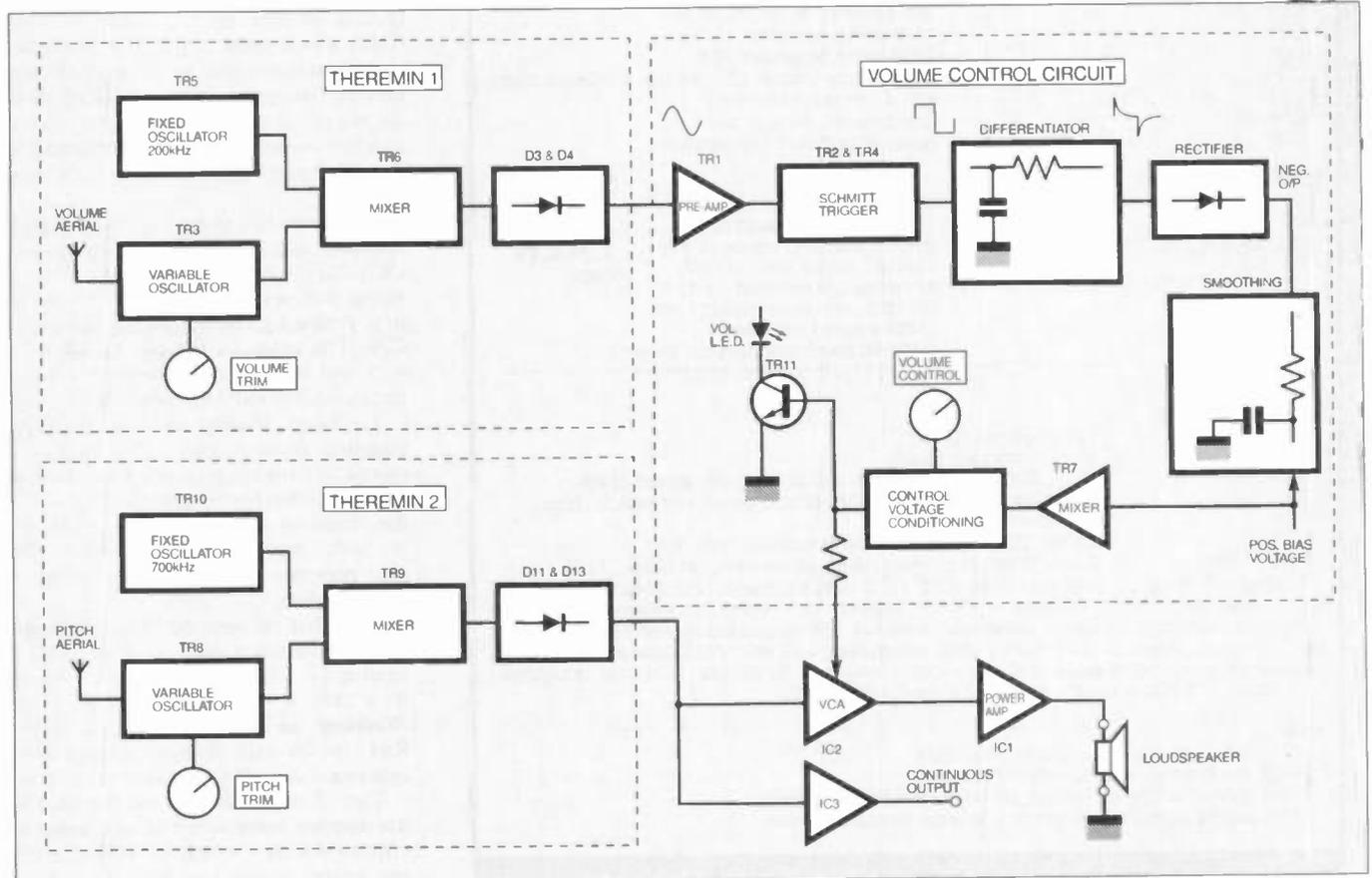


Fig. 9. Block diagram for the dual, Pitch and Volume, EPE Elysian Theremin.

COMPONENTS

Resistors

R1, R72	4k7 (2 off)	R23	2Ω
R2, R3, R9, R17, R24, R31, R38, R39, R49, R52, R56, R61, R64, R76	1k (14 off)	R25, R47	1M (2 off)
R4	680k	R26	330Ω
R5, R32, R70, R77	47k (4 off)	R34, R36, R60	470Ω
R6	18k	R35, R43	68k (2 off)
R7	2k7	R40	200k
R8	1k8	R41	22k (or 39k if network fitted)
R10	130Ω	R42, R71, R81	22k (3 off)
R11, R29, R69, R74	33k (4 off)	R45	100k
R12, R30, R68, R75	150k (4 off)	R46, R78	100Ω (2 off)
R13, R18, R37	1M5 (3 off)	R53, R67	470k (2 off)
R14, R16, R28, R33, R50, R51		R57	51k
R54, R63, R80	10k (9 off)	R58	680Ω 1W 5%
R15, R19, R44, R55, R66, R79	2k2 (6 off)	R59	3k
R20	560Ω	R62	3M3 5%
R21	15k	R65	8M2 5% (or 13k if network fitted)
R22, R27	1M (2 off)	R73	220k
		R82	10Ω 1W

All 0.6W 1% metal film, except where stated

Potentiometers

VR1, VR2, VR3	47k min. p.c.b. mounting rotary carbon, linear
VR4	5k min. cermet preset, horizontal

Capacitors

C1, C46	100p ceramic NPO (black band) 2% (2 off)
C2	100μ radial elect. 25V
C3	optional padder (see text)
C4, C16, (5mm only), C20, C22, C28, C33, C38, C39, C42, C44, C49, C50, C52, C58, C65, C69	100n ceramic -20% +80% (16 off)
C5, C10, C13, C26, C27, C43, C53, C55, C61, C62	10n ceramic 20% (10 off)
C6	22μ tantalum bead, 16V
C7	47μ radial elect. 25V
C8, C14, C18, C23, C29, C30, C35, C45, C66, C70, C71	1n ceramic, 5mm 10% (11 off)
C9, C15, C36, C37, C41, C47, C48, C60, C64	10μ radial elect. 35V (9 off)
C11, C24, C54, C59	330p 5mm ceramic N150 (orange) or polystyrene 2% (4 off)
C12, C67	27p ceramic NPO (black band) 2% (2 off)
C17	10n polyester
C19, C21, C40	470μ radial elect. 35V (3 off)
C25, C63	68p ceramic N330 2% (2 off)
C31	150n 5mm polyester 10%
C32	220n 5mm polyester 10%
C34	68n 5mm polyester 10% (or 15n if network fitted)
C51	4n7 5mm polyester 10%
C56, C57	82p ceramic 10% (2 off)
C68	optional padder (27p ceramic)

Semiconductors

D1	5mm blue diffused i.e.d.
D2, D6, D12	1N4001 rec. diode (3 off)
D3, D4, D5, D9, D11, D13	BAT25 Schottky diode (6 off)
D7, D8	1N4148 signal diode (2 off)
D10	5mm orange diffused i.e.d.
TR1 to TR11	BC182L npn transistor (11 off)
IC1	LM380 audio amplifier
IC2	CA3080 transconductance op.amp
IC3	TL081 j.f.e.t. op.amp (or similar)

See
**SHOP
TALK**
Page

Miscellaneous

L1, L2	1mH inductor (2 off)
L3, L4	330μH inductor (2 off)
JK1, JK2	SCJ-0639 switched, p.c.b. mounting, jack socket (2 off)
S1	pushbutton, p.c.b. mounting, dual changeover switch (Alps), with 8mm dia. button
LS1	8 ohm 102mm dia. 1.5W loudspeaker (see text)
TB1 to TB4	2-way 5mm, p.c.b. mounting, screw terminal block (2 off)

Printed circuit board available from *EPE PCB Service*, code 121; 25mm (1/2in.) MDF case, size 560mm x 126mm x 75mm; copper-clad board for volume plate, size 120mm x 42mm; pitch aerial assembly; external 15V regulated power supply; 2.1mm dia. (internal) power socket; front panel; plastic knob (3 off); microphone stand fixing; loudspeaker mounting plate and grille cloth; length of solid-core 1/0.6 red equipment wire, approx. 125mm length; connecting wire; solder etc.

Note

Circuit design copyright of J.M. Rothman.
PCB design copyright of Adam Fullerton.
This design is offered for one-off home construction only.
This article does not constitute a licence for manufacture.

The circuit diagram is split into two parts for convenience, the Pitch/VCA section being shown in Fig. 10 and the Volume Plate section given in Fig. 11. Note that the component designations follow their position on the printed circuit board (p.c.b.) rather than the circuit diagram since this aids assembly.

Since there are two basic Theremins for Pitch and Volume with the same circuit topology, these will be discussed first (component numbers used will be those of the Pitch oscillator). The Volume oscillator runs at around 200kHz and the Pitch around 700kHz, so a small amount of interference to MW/LW radios is to be expected if within a few feet of the Theremin.

The oscillators are a particularly interesting version of the Colpitts type. They cannot simply be defined as common base, emitter or collector as far as a.c. analysis is concerned, since it depends on what transistor connection node is taken to be reference 0V. In this case, they are drawn as "common emitter" circuits for convenience. The Colpitts configuration is preferred to others, such as the Hartley, since simple coils with no tapings are used.

The outputs of the oscillators are at quite a high level, in fact, slightly above the supply rail due to *Q* multiplication in the coils. The aerials are connected to the collector ends of the tank circuits (TR8/TR3) to provide the small frequency shift required. Capacitors (C66) are used to avoid the risk of an aerial short to ground burning out a coil and to limit the "splat" that occurs if the aerial is touched.

VARICAP CONTROL

Both Theremin sections can be trimmed to compensate for normal variations by panel mounted pots. These pots vary a reverse voltage across a rectifier diode (D12) which cause a variation in its junction capacitance and hence a small variation in frequency. Proper varicap diodes are *not* needed in this application since the required capacitance swing is so small and the standard 1N4001 rectifier diode is perfect.

The diode has to be a.c. coupled to the oscillator and this is achieved by capacitor C67. R.F. has to be prevented from entering the pot. wiring so r.f. decoupling is provided by resistor R77 and capacitor C70. The range of the pot. is limited by R25 and the range of adjustment can be increased if desired by reducing its value.

To avoid loading the oscillators and coupling them together, the outputs are mixed via high value resistors (R65 and R62) into the low impedance base (b) of the common emitter mixing stage. This is built around transistor TR9 which also provides a degree of buffering and amplification.

Note that the mix resistors (R65, R62) are of different values to ensure that the beating r.f. signal waveform does not drop to a zero level at any point to prevent distortion, as shown in Fig. 12. Resistor R64 sets the gain of this stage and can be reduced if desired to overdrive the VCA.

The r.f. signal is then a.c. coupled into the detector stage which is configured as a voltage doubler, which as well as providing extra output is also self clamping (since D13 provides a d.c. path to ground) allowing the input to be a.c. coupled.

Approx Cost
Guidance Only

£150 excluding case,
aerials and hardware


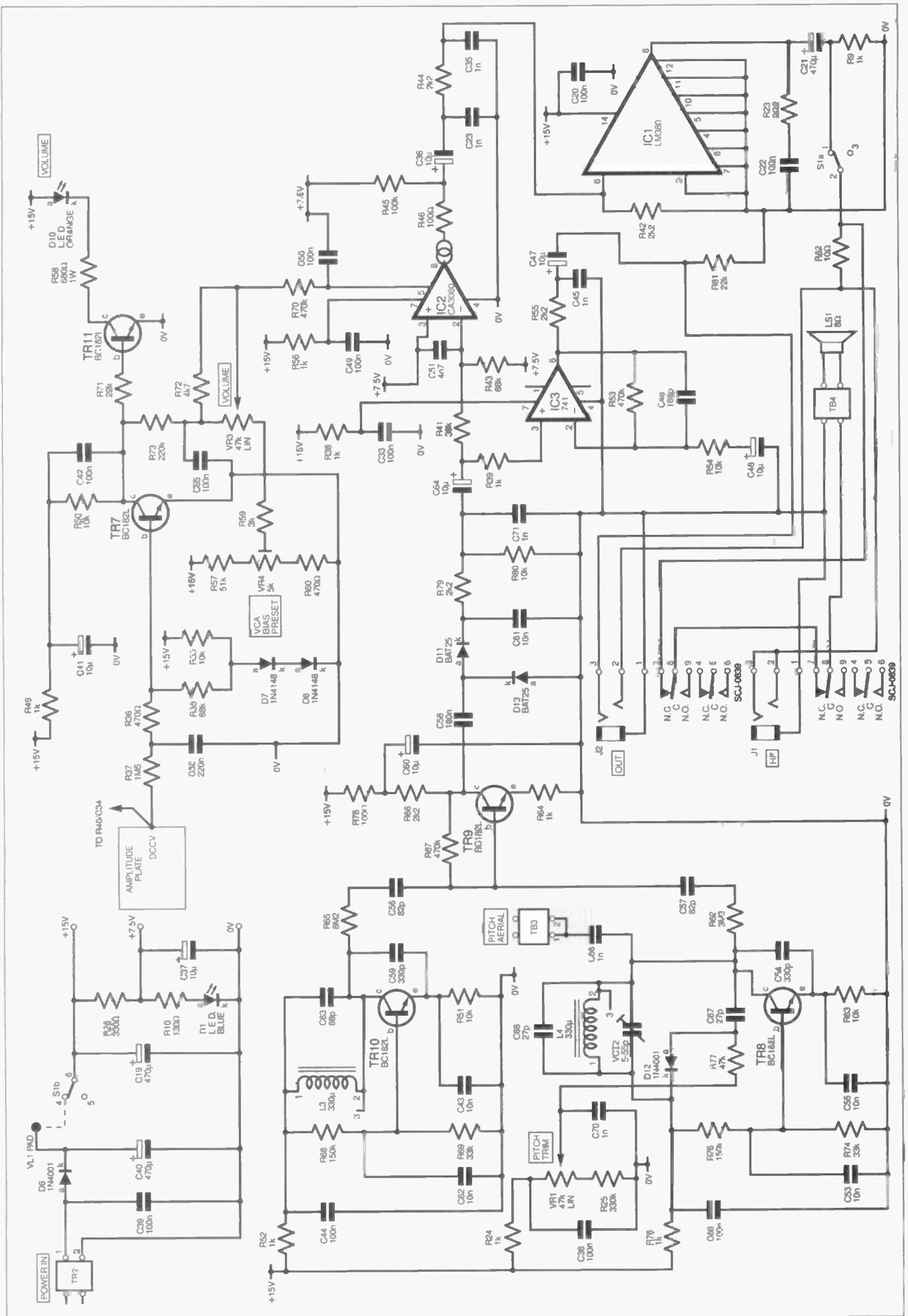


Fig. 10. Pitch section circuit diagram for the EPE Elysian Theremin. Note resistor R48 has been deleted (not used).

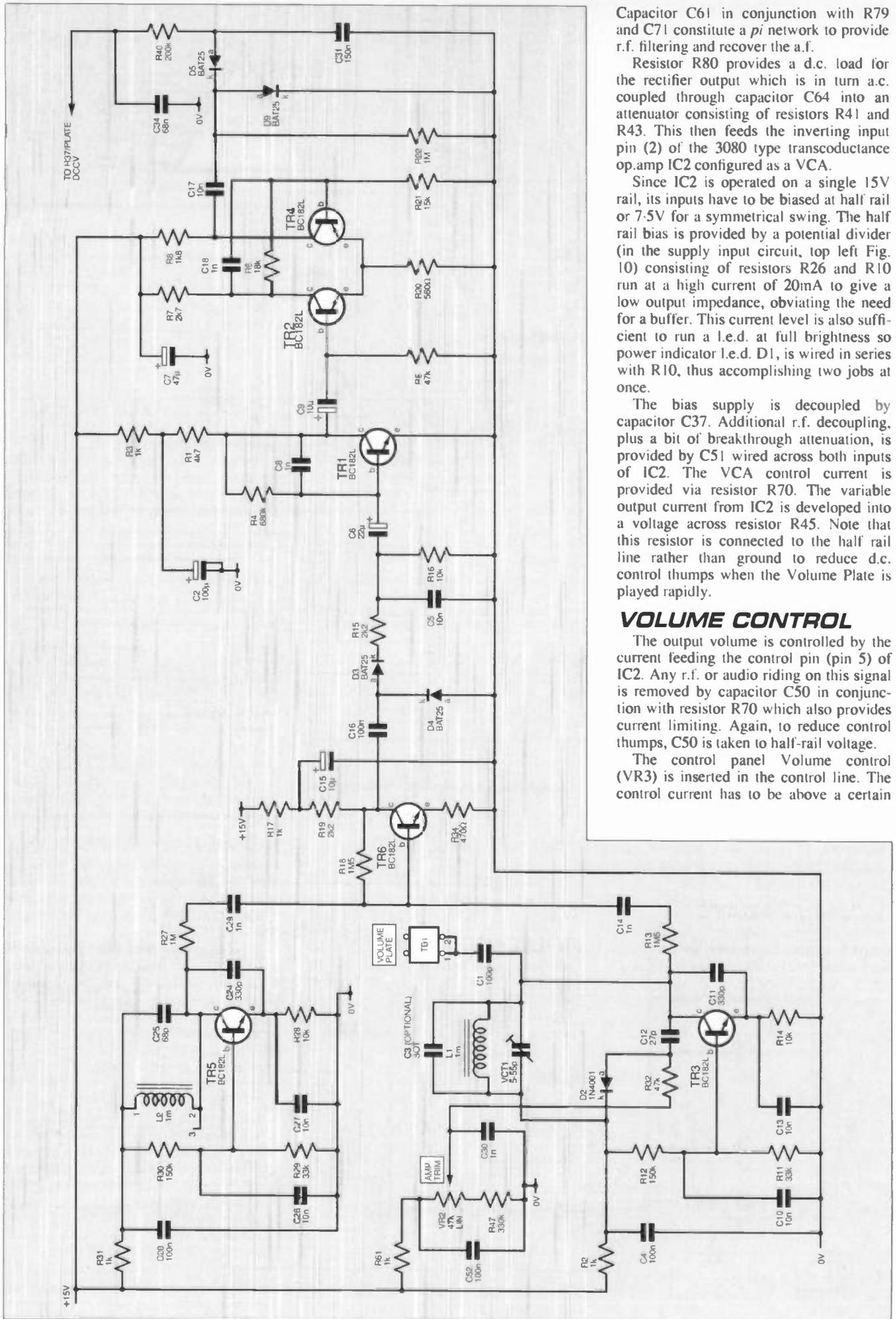

Capacitor C61 in conjunction with R79 and C71 constitute a π network to provide r.f. filtering and recover the a.f.

Resistor R80 provides a d.c. load for the rectifier output which is in turn a.c. coupled through capacitor C64 into an attenuator consisting of resistors R41 and R43. This then feeds the inverting input pin (2) of the 3080 type transconductance op.amp IC2 configured as a VCA.

Since IC2 is operated on a single 15V rail, its inputs have to be biased at half rail or 7.5V for a symmetrical swing. The half rail bias is provided by a potential divider (in the supply input circuit, top left Fig. 10) consisting of resistors R26 and R10 run at a high current of 20mA to give a low output impedance, obviating the need for a buffer. This current level is also sufficient to run a l.e.d. at full brightness so power indicator l.e.d. D1, is wired in series with R10, thus accomplishing two jobs at once.

The bias supply is decoupled by capacitor C37. Additional r.f. decoupling, plus a bit of breakthrough attenuation, is provided by C51 wired across both inputs of IC2. The VCA control current is provided via resistor R70. The variable output current from IC2 is developed into a voltage across resistor R45. Note that this resistor is connected to the half rail line rather than ground to reduce d.c. control thumps when the Volume Plate is played rapidly.

VOLUME CONTROL

The output volume is controlled by the current feeding the control pin (pin 5) of IC2. Any r.f. or audio riding on this signal is removed by capacitor C50 in conjunction with resistor R70 which also provides current limiting. Again, to reduce control thumps, C50 is taken to half-rail voltage.

The control panel Volume control (VR3) is inserted in the control line. The control current has to be above a certain

Fig. 11. Volume Plate circuit diagram for the EPE Elysian Theremin.

point before any audio output occurs and this is accounted for by a bias fed into the "earthy end" of the pot. The bias voltage required varies between different 3080 chips and preset VR4 is provided to accommodate this variation.

To obtain a good control law (or feel!) on the Volume pot, a law-faking bypass resistor (R27) is used. A visual indication of the control voltage is provided by l.e.d. D10, driven by transistor TR11. Note that the l.e.d. current limiting resistor R58 is rated at 1W so it runs cool.

Transistor TR7 provides the basis for conditioning the control voltage from the Volume control section. TR7's base-emitter junction is biased just into conduction by the 1.2V generated by diodes D7 and D8. This is fed into the base (b) of TR7 by R35 (whose value may have to be adjusted on some examples).

The control voltage generated by the Volume control circuitry is *negative* and this subtracts from the bias voltage. Thus, TR7 is off when the volume is high. Capacitor C42 is used to filter out any undesirable undulations in the control voltage along with C32 and R37 which provide further smoothing.

In practice there is a trade off in the speed of response and level of smoothing. Although, the smoothing is only a problem when the volume oscillators are just coming out of lock, beating at a very low frequency which may cause volume pulsing.


CONTINUOUS OUTPUT

A continuous output is obtained by feeding the detector output, from C64, directly into a non-inverting amplifier with a gain of 48 times, configured around IC3. Bias for this amplifier is provided from the same source as that for IC2.

Resistor R55 provides short circuit protection for the continuous output if a mono jack plug is inserted into socket JK2. Capacitor C45 provides yet more r.f. decoupling and many such capacitors are scattered around the circuit with every stage having its own RC network.

VOLUME PLATE

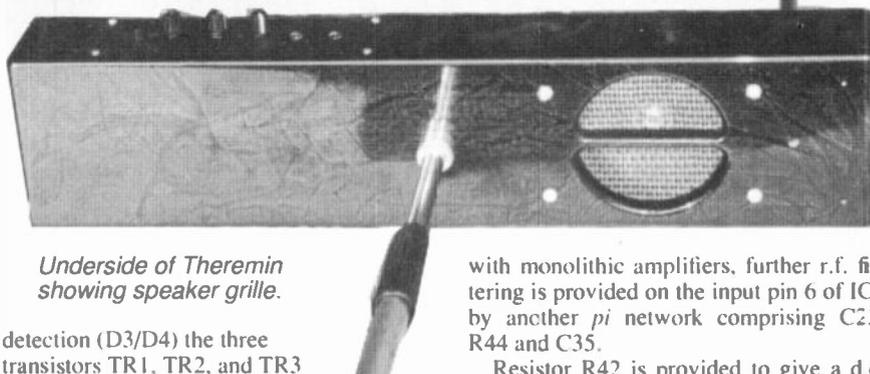The Theremin Volume Plate signal is derived in the same way as the Pitch section except that the mixing stage (Fig. 11) is set at a higher gain with lower value mix resistors (R13/R27) and emitter resistor (R34). Distortion is worse, but a sine wave is not required; indeed after



Underside of Theremin showing speaker grille.

detection (D3/D4) the three transistors TR1, TR2, and TR3 convert it into a square wave. Transistor TR1 is simply a common emitter amplifier giving enough output to drive the Schmitt trigger circuit designed around TR2 and TR4.

The square wave is then fed into a differentiator consisting of C17 and R22. The short duration pulses are then converted to d.c. by a voltage doubler circuit consisting of diodes D9 and D5. Smoothing of the resultant control voltage is provided by capacitors C31 and C34. The output voltage increases as the frequency of the Volume Theremin increases, and this provides the smooth incremental increase in volume.

This method alone would not provide the dynamic range required, so the null/lock point of the Theremin is used to provide the "fully off" part of the volume control characteristic. Note that if the varicap trim control VR2 is adjusted to the other side of the null point the volume direction is reversed. It is this mode that is used for "Classical" playing.

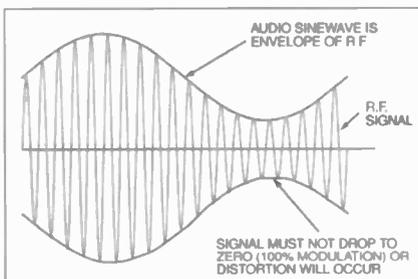


Fig. 12. Beat frequency waveform.

AUDIO SECTION

Power amplification is provided by the ubiquitous LM380 (IC1) providing about 2W into 8 ohms. It is also happy driving cables and headphones - see Fig. 10. Since instability is always a potential problem

with monolithic amplifiers, further r.f. filtering is provided on the input pin 6 of IC1 by another pi network comprising C23, R44 and C35.

Resistor R42 is provided to give a d.c. path to "ground", necessary with only the odd example of LM380 to help maintain the d.c. potential of the output (pin 8) at half rail. Capacitor C22 and resistor R23 constitute a Zobel network and provide a h.f. load for the amplifier where the inductance of the speaker voice coil comes into play.

OUTPUT SWITCHING

When either Headphones or an external lead is plugged into the Theremin, the internal speaker LS1 is muted by the switch contacts on the jack sockets JK1, JK2.

The output amplifier IC1 is protected against cable shorts by resistor R82, a 10 ohm 1W type, in series when feeding headphones or an external load. This resistor also ensures stability when driving long screened cables with high capacitance.

DE-THUMPING

An important aspect of audio/music electronic design is that of de-thumping. The Theremin circuit can emit an excruciating "death rattle" when turned off, this is simply avoided by using the extra switch section on the power switch to break the output when turned off.

This primitive de-thump protection does not work if the P.S.U. is yanked from its wall socket however! Switching clicks and jack connection thumps are reduced by pull-down resistors R9 and R81.

POWER SUPPLY

The power supply requirements for the EPE Elysian Theremin are modest, being a regulated 15V rail at a maximum of 300mA. This can be supplied via a simple 7815 + 15V regulator.

It is essential that the Theremin is "earthed" to avoid modulation hum. However, if the 0V rail is connected *directly* to mains Earth there is the possibility of "earth loops" occurring when it is connected to external equipment such as mixers.

Both these requirements can be satisfied if the 0V rail is connected to mains Earth via a capacitor and resistor in parallel. The capacitor provides a low impedance at r.f., while maintaining a high impedance at audio frequencies. The resistor provides the standard ground lift function to prevent earth loops. A suitable power supply circuit is shown in Fig. 13.

Although a diode (D6) is used on the input of the Theremin for reverse polarity protection and capacitors C40 and C39 provide plenty of smoothing, a.c. *must* not be fed into the unit since awful modulation hum will result.

Next Month: Construction and setting up the EPE Elysian Theremin.

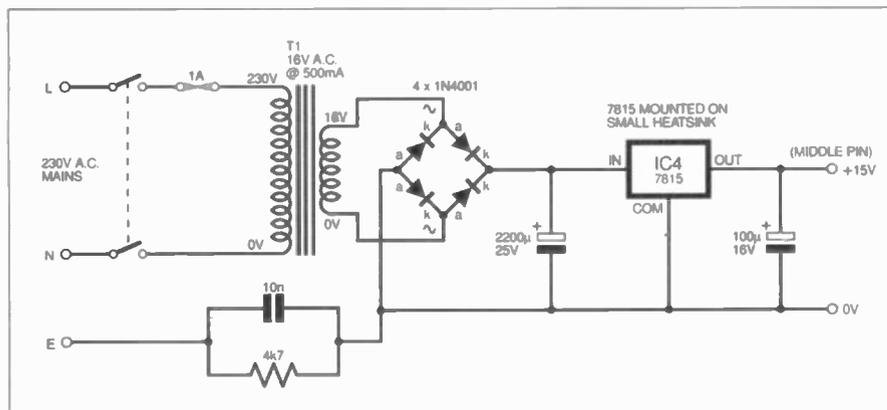


Fig. 13. Regulated power supply for the EPE Elysian Theremin.

BUILD YOUR OWN PROJECTS

Alan Winstanley

Part 1



IN THIS new series of articles which will be presented over the next few months, we shall be describing modern methods for constructing your electronic projects. This first part offers some initial tips for beginners and discusses essential tools and equipment needed to make a start.

Future parts will look at circuit board assembly, case and enclosure preparation, workshop tips and tricks – in fact, everything you need to know to get satisfying results when building your latest *EPE* project!

Alan is, of course, Surgeon-in-Chief at *Circuit Surgery*, and enjoys all aspects of electronics.

AS WITH any hobby or pastime, electronics offers many rewards, not least of which is the satisfaction derived from working with modern technology and applying it to fulfil a particular purpose.

There are several aspects to being an electronics enthusiast, and you can pick and choose whichever particular ones appeal to you most, depending on your needs: possibly you may wish to become proficient in circuit design, or perhaps concentrate on the constructional angle, or a bit of both.

You might simply have a passing interest in building pre-designed projects, keeping a keen eye on cost, and possibly *tweaking* them to meet your individual needs; after all, many readers seldom build projects exactly as described, but prefer to adapt them somewhere along the line!

RESOURCEFUL

Constructors sometimes need to be a bit resourceful, using parts from the *spares box* to keep the project rolling along. If you're fortunate enough to have a more generous budget, you might be able to afford more advanced test equipment, tools and other resources. Whatever your interest, though, electronics construction will involve you with modern electronic components, a field which is perhaps the most fast-moving of any technological field.

Many smaller parts cost literally "pennies" each and there has never been the requirement to keep up with the latest *cutting edge* electronic components to enjoy the hobby to the full, although we do indeed use some state-of-the-art devices, including the Arizona Microchip PIC microcontrollers.

Such products do not appeal to each and every reader, however, and happily many of our projects still use an assortment of highly effective *bread and butter* devices, some of which date back a couple of decades or so but are still as important today. At a time when components are smaller, cheaper and more powerful than they have ever been, electronics still has something to offer everybody, no matter what their skills or budget may be.



You do not need many tools to successfully undertake electronics, but the primary one you do need is a multimeter, of which a wide variety are available.

GO FOR IT!

There is nothing quite like the thrill of completing a project which you've built from raw materials with your own bare hands, and showing it off to your friends for the first time. Developing personal skills in technology, saving money by building it yourself, and customising something to meet your own precise requirements, are just some of the other benefits of being an electronics enthusiast.

This series of articles, *Build Your Own Projects*, will take you step-by-step through the methods of building electronic projects and prototypes from scratch, using modern electronic components, tools and equipment to prepare projects safely and efficiently.

Hopefully, by avoiding spoilt or wasted work which results in disappointment, there will be something in this series to appeal to everyone, whether a complete

novice looking for guidance and encouragement, or a more seasoned constructor who may be interested in a few hints or tips relating to modern-day assembly techniques.

Just like those coffee-table home decor books which inspire but don't dictate, *Build Your Own Projects* is not all *gospel* but may offer inspiration and pointers. Some things, though, will never change, so we'll start with some fundamental aspects behind electronics construction before moving onto real workshop techniques over the next few months.

LET'S GET WIRED

Firstly, if you're becoming involved in electronics for the first time, you'll soon become aware that some designs, although quite straightforward in nature, require the mains electrical supply to operate properly. Many other circuits use batteries

as their power source and it is these more modest types of project with which beginners ought really to consider starting.

Utilising the mains supply requires that your workmanship is of a satisfactory level and that certain precautions are followed, so that you endanger neither yourself nor the well-being of others who may handle the project routinely.

Hence, it's best to practise on the simpler constructional designs to begin with, and gradually acquire the skills needed to tackle more advanced work. *Everyday Practical Electronics* always screens projects carefully and publishes all the essential information you need to complete your prototype properly, and you should make a point of reading the author's notes thoroughly and following diagrams closely, cross-referring to the photographs as necessary.

Some constructional projects may involve more advanced skills, particularly soldering small components on densely populated boards, and these techniques are only ever acquired with practice. Rather like an author feeling comfy with a favourite pen (or keyboard, in my case!), you'll get the *feel* of a soldering iron and with practice you'll learn how to master the various tools and associated gear in order to produce results you can be really pleased with.

BUT DON'T OVERREACH

It would be regrettable if an enthusiast embarked upon a particularly ambitious project whilst lacking relevant experience or resources; this will invariably end in disappointment and may deter him or her from tackling other circuits. So, choose your projects with a little forethought, so that you can tackle the challenge of a new prototype without facing potential disappointment by being over-enthusiastic.


Incidentally, there will almost certainly come a time when you *have* built a project, yet you cannot quite manage to make it function fully, if at all. This can be a major source of disappointment amongst beginners and often damages their confidence. Fault-finding and troubleshooting are black arts which come with experience, and my own advice (easily said but harder to follow at the time) is to persevere and not be deterred, because there is often a very simple explanation for the fault.

Without question, fault-finding goes hand in hand with electronics, and it is all part of the electronics *experience* to resolve such problems: eventually, you will look back and laugh!

In any case, if you are struggling for whatever reason with an *EPE* project, you will find that most contributors are very willing to give you advice if you drop them a line via the Editorial address, explaining the symptoms fully, so help is never very far away.

WHERE TO BUY

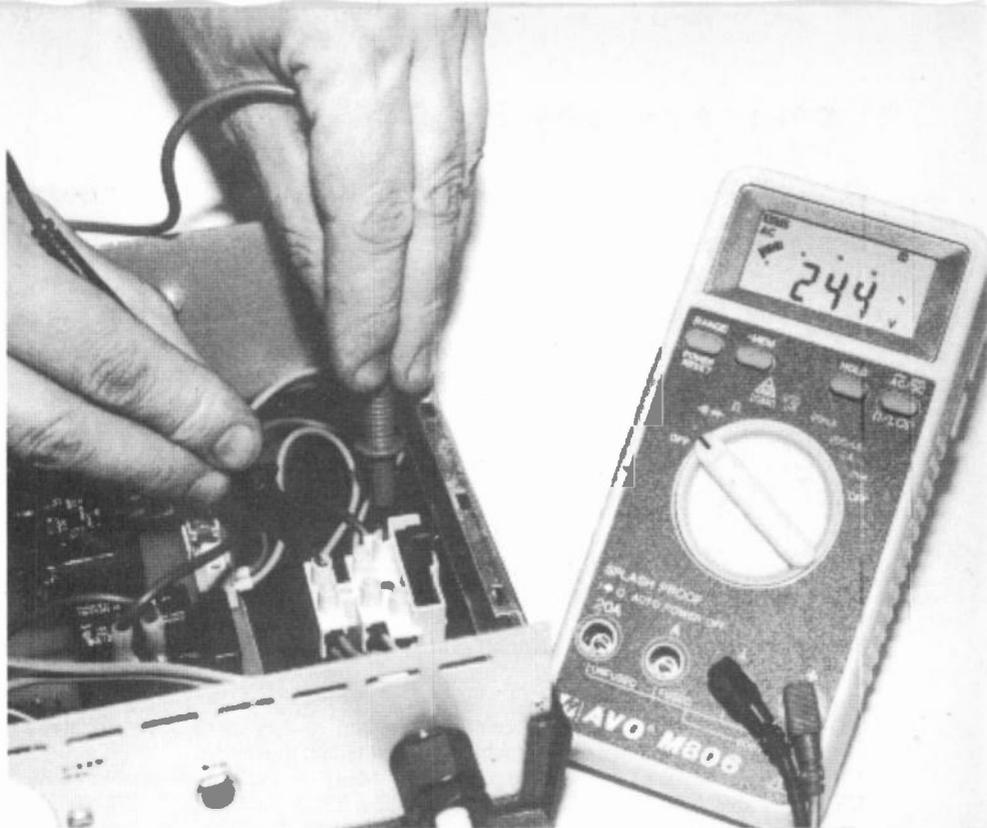Having considered the scope and nature of the project carefully, you will probably have priced it up and pencilled in an estimate of the likely constructional costs. With luck you may have at least some of the parts already to hand, but there will often be the need to buy in particular components.



Ensure that you have high quality meter probes so that high voltage readings can be safely made.

Every *EPE* project has a full Components List and we also make a deliberate point (often overlooked by readers, to our dismay) of publishing all component buying matters in our *Shoptalk* column. This should always be your first port of call before you pick up the phone or write out that order!

Because of the immense range of components now available, you shouldn't be surprised if often some unusual parts are called for, which may or may not be available from a local electronics retailer (possibly see *Yellow Pages* for names and addresses). A mail order source is usually suggested in *Shoptalk* for those out-of-the-ordinary parts, which means that they are only a phone call or letterbox away and are accessible by everybody!

Of course, we carry advertisements for many mail order specialists in our pages and you should make a point of acquiring at least *some* price lists and catalogues from advertisers. Indeed, mail-order components are a critical part of the electronics *scene* and it would be completely impossible for many readers to enjoy the hobby if it wasn't for mail-order suppliers making parts available conveniently by post.

MINIMISING COSTS

Bear in mind that there is little money made (except by the Post Office) in mailing out small, cheap components and therefore suppliers – even the largest ones – will commonly levy a handling charge for small orders. Mail order sources work hard for their money! You can cut your costs by planning ahead and grouping orders together to help reduce handling and postage charges.

If you can afford it, also think about *doubling-up* your order for some parts so that you can build up a modest stock of parts to keep on the shelf. Typically, I carry most small parts *in stock* but will send out by mail order for unusual or expensive components, or instrument cases

in particular. Other sources of parts include surplus boards, salvaging them with a soldering iron and stripping them down, something I enjoyed tremendously when I picked up an iron for the first time!


However, it is sometimes more trouble than it's worth trying to re-cycle certain parts from surplus boards, since they may be damaged by excessive heat, they do not always come away cleanly and many chips are cheap when new, anyway. It's fun though, and surplus equipment often yields valuable or unusual parts. You might consider re-cycling parts from discarded projects, too.

TEST EQUIPMENT AND TOOLS


It is possible to spend from a few tens, to many thousands of pounds on test equipment, but the first thing you are likely to require is a Multimeter to take test readings and measurements (voltage, current and resistance). You might follow on with more esoteric items of gear including mains power supplies (consider building your own), signal and function generators, oscilloscopes and so on, as your experience and confidence grows.

A multimeter is an essential item of measuring equipment and, briefly, they fall into two categories: analogue (moving coil) and digital. Analogue meters use a traditional-style moving coil meter movement but are falling out of favour in preference of their digital counterparts which are far more convenient to use.

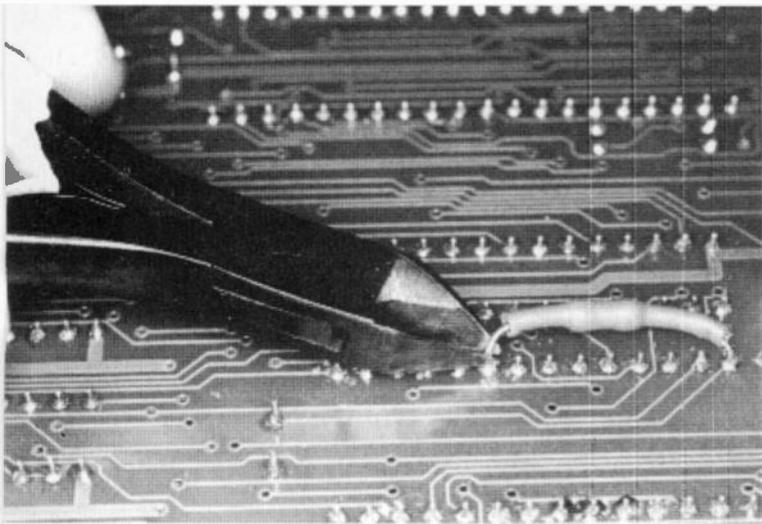A multimeter is not quite the *perfect* instrument you might think it is, because the meter itself possesses a certain resistance which can affect the circuit being tested. In the case of analogue meters in particular, this can easily result in false readings, because the meter's own movement will behave like a resistor, loading the circuit under test.



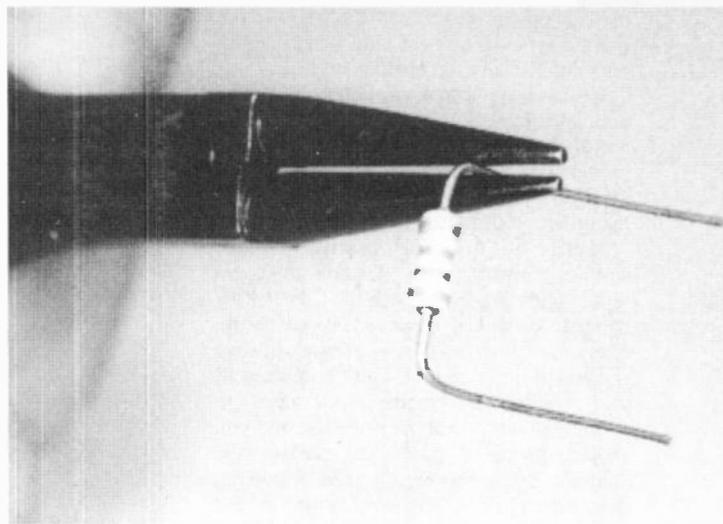There are many wires to be snipped during construction, so get a good pair of wire cutters.



Similarly, there are many things to be picked up, and neatly shaped, so decent pliers are a MUST as well.

Quite how much it loads the circuit is specified by a meter's sensitivity, which will be quoted in *ohms per volt* (o.p.v.). The higher this figure, the better its sensitivity (and accuracy) will be.

A typical modest moving-coil meter may have a sensitivity of, say, 2,000 ohms per volt, so if you set it to a 10V range, the meter behaves like a 20k Ω resistor. Put simply, if you were using it to measure the voltage across a 1M Ω resistor, for example, then you would be *shunting* that resistor to form a 19.6k Ω resistor, no less! (1M and 20k in parallel.)

Thus the meter has introduced an error into the circuit which may give you a false reading, but this also depends on other factors in the circuit under test. 20,000 o.p.v. is a good, general-purpose value to aim for with this type of instrument. The trick is to read voltages using the highest possible meter range, so as to avoid loading the circuit too much. Ideally, the resistance of your meter should be at least ten times that of the effective resistance under test.

Also check the other ranges offered on the meter, especially direct current (d.c.), which should ideally cope with, say, 2A or more. (I guarantee you will use it.) Resistance ranges will probably extend to 10M Ω or so, and the meter may or may not cater for alternating current (a.c.). Any extra features (e.g. transistor checking or continuity buzzers) are bonuses which may prove handy from time to time.

DIGITAL PRECISION

A digital multimeter (DMM) is the best way of obtaining accurate results; numerical displays are very convenient to read and many meters are *auto-ranging*, where they select the best range themselves – so there is no danger of trying to read 50V on a 5V range, or 2A on a 200mA range (though you'll find that not every meter auto-ranges on current).

Also, they should often be auto-polarising, so that they read a voltage regardless of which way round you have connected the positive and negative meter leads, which can be extremely useful at times. Some have a *hold* feature that acts like a memory and displays the latest value until you reset it.

Most importantly, they have a very high input impedance, typically 10M Ω or

higher, so they won't adversely affect the test circuit much.

Many models are available, some of them for a modest cost, and advertisers' catalogues should be consulted. You could buy a *starter* digital meter for as little as £20 and they may include other convenience functions such as a transistor or diode checker.

Small *pocket* moving coil meters costing under £10 should be treated virtually as a consumable item, or something you can have *kicking about* in the tool box which you're not afraid of damaging.

The photos show several types of meter, including a handy pen-type digital multimeter which I like to keep to hand for quick tests. Also, have a look at test leads and connectors, as you may be able to make your own additional leads using extra-flexible test lead wire with (usually) 4mm plugs and test clips.

You will find a variety of ready-made test gear available by mail order or from local electronics stores. However, you may prefer to build at least some of the gear yourself, based on a constructional project.

A mains-operated bench power supply, capable of providing, say, 0 to 25V at 0 to 1A or more, is a good next move, and will enable you to start prototyping circuits

and powering them economically, obviating the need for batteries.


More serious constructors will also think about purchasing an oscilloscope. We published a two-part series on the use of oscilloscopes in the June/July 1996 issues (see *Back Issues* page).

TOOLING UP


Unlike our contributor Max Fidling of *Ohm Sweet Ohm* infamy, whom it seems likes to collect colourful tools mainly to impress his chums (!), you can spend as much or as little as you like on hand tools and equipment. (*Max, are you going to stand for such abuse? Ed.*)

One rule passed down to me was that you should always buy the best tools you can possibly afford, consider them as investments and they will reward you with a lifetime of faithful service. There are enormous differences in the qualities of hand tools available, which are always reflected in their price.

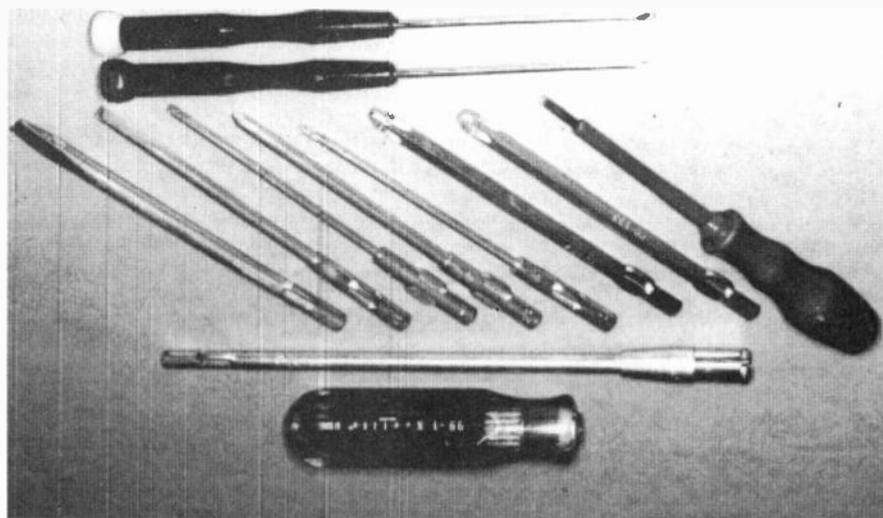
I've snapped the jaws of some Taiwanese wire cutters, and broken the handle or blunted many a cheap screwdriver; I would not reasonably expect a 49p screwdriver to be as strong or last as well as my favourite Xcelite 99 series driver set (the American firm



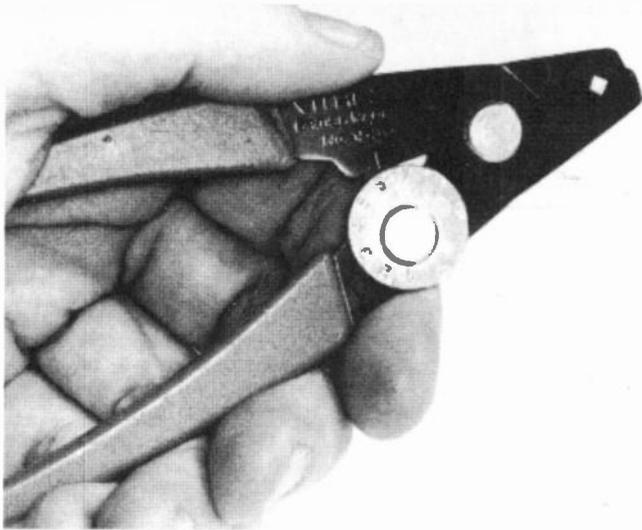When it comes to screwdrivers, the more the merrier, but you can economise by using the interchangeable blade type for some applications.



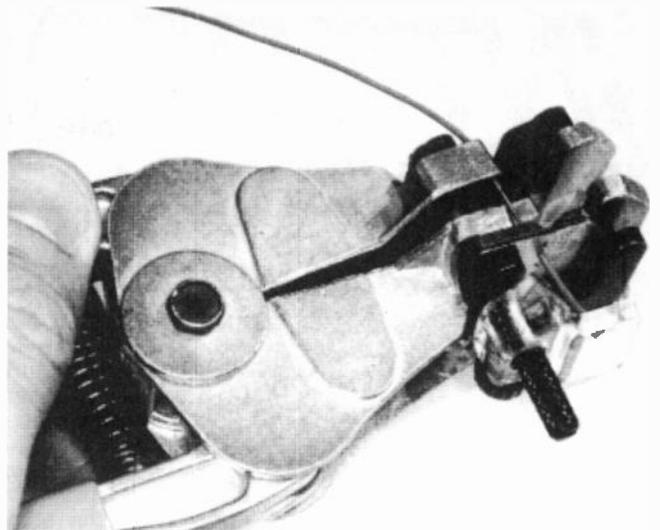Simple wire strippers are good for most simple tasks, like these dial-type ones from Vitrex.



But there are even more sophisticated wire strippers for the connoisseur, such as the Ideal Stripmaster.

Xcelite having invented the plastic-handled screwdriver, by the way). I would expect that some £30 Lindstrom wire cutters will almost last forever, unlike a cheap version at one-tenth the price, which you may have to throw away within a year or two. With hand tools more than anything else, you get what you pay for.

Ideally, cheap tools should serve as nothing more than to register your interest in electronics: upgrade when you can afford it, and you'll not regret it because quality tools make assembly a pleasure.

However, everybody obviously has to start somewhere and you may well choose to start with a modest set of tools, and build from there in the years ahead, depending on your budget and level of interest.

Personally, I used to buy the occasional tool on a need to buy basis along with mail-order components, and have built up a dazzling array over the years.

HAND TOOLS NEEDED

For hand tools, you should consider buying the following, at a minimum:

- *Long-nose, fine point pliers*, preferably with serrated jaws – useful for gripping wires securely to form them or solder them, and for holding small components.

You may see them listed as *radio pliers*. Look for PVC insulated handles (more for the comfort aspect). Spring-loaded jaws are available in some types, which are more convenient to use. *Box jointed* pliers have a precision-made joint for more accurate operation and alignment of the jaws.

- *Wire cutters* – ordinary *side cutters* are used for snipping wires to length. Again, PVC handles, and box jointed for more discerning users. They're normally designed for cutting copper wire with a high degree of precision, and are not suitable for cutting steel wire, for example – they'll be ruined.

- *Electrician's wire cutters* are heavy-duty snips having larger blades and a wider jaw, useful for cutting electrical cables and mains flex, etc. to length. Usually they are more crudely finished, giving a less precise cut than smaller versions for electronics/radio use.

Personal favourites in this area include Xcelite *Superior* and Lindstrom *Supreme* hand tools, but it's recognised that these are priced with the serious constructor and professional user in mind. Much more modest tools – but ideal for beginners or light use – are available which are made from pressed steel. Check your local DIY stores for some ideas, or refer to a mail-order catalogue.

More luxurious electronics hand tools (i.e., not necessarily essential, but very nice to have), include:

- *Round-nosed pliers* having circular jaws, for shaping wire ends into perfect loops or for bending wire leads accurately.

- *Flat-nose pliers* have smooth jaws for gripping wires, handling delicate components. Especially useful for straightening bent i.c. pins, etc.

- *Diagonal side cutters*, for snipping soldered joints on printed circuit boards, or for cutting small wires where access is restricted.

There are some weird and wonderful-looking hand tools available which make light work of stripping insulation from wire. I recommend the *Toggle* wire stripper as an indispensable aid when dealing with multi-core mains cable (or co-axial); this will guillotine 13A 3-core wire with surgical precision and then, with the twirl of a finger, slit the insulation using a rotating blade effect to produce perfect results. They are cheap to buy from most DIY shops.

For dealing with thin-gauge wires, you might opt for a simple wire-stripper with a dial-type setting (e.g. as manufactured by the British tool manufacturer Vitrex, see photo), which ensures that you cut the insulation without damaging the copper core.

A fearsome-looking but extremely impressive gadget for the more adventurous constructor is the famous *Ideal Stripmaster*, made in the USA, but with some imitators at one third the price which you might find quite acceptable. These grip the wire, cut the insulation at the desired point and then pull it off, all in one easy action (see photo). They are rather a luxury but speed up the sometimes tiresome chore of interwiring immensely. Again, such tools are readily available from various mail order houses, costing from £8 to £20 or so.

DRIVING HARD BARGAINS

Screwdrivers are another area where it's worth spending a few pounds building up a reasonable array of the most useful types. Again, price is everything and there are several options available. I favour owning a number of smaller-handled screwdrivers for precision work in fiddly places, and insulated shaft screwdrivers enable work to be carried out with no risk of accidentally touching *live parts*.

I am also a believer in using screwdriver sets which have only one handle and many interchangeable bits. This saves you having to store a range of bulky-handled screwdrivers, which is important if you want to save space in a toolbox. The larger handle also allows more leverage to be applied to larger screw fittings.

Some more expensive screwdriver ranges (Xcelite 99, for instance) have a complete range of extensions, ratchet handles, nutdrivers, Torx keys, hexagonal keys etc., available too, so one of these can become an indispensable item to which you may add various blades in the future.

Alternatively, C.K. produce an excellent magnetic ratchet screwdriver set which *freewheels* in one direction but drives in the other. It has no less than 32 bits plus 12 sockets. The magnet is built into the shaft, to hold the bits in place (also good for wiping floppy disks!) and it's retained in a handy storage box.

Many such tools are available from the larger electronics suppliers, but you'll see large ranges of hand tools at all the larger DIY superstores, too. Prices vary, so shop around, and don't forget to check out motorist's discount stores, as well.


You will find that rechargeable battery-powered screwdrivers have a place in electronics construction, but may need to be used with care at times, especially on plastic boxes or similar where it's possible to smash some fittings. We'll be describing these and other tools in forthcoming parts of *Build Your Own Projects*.

NEXT MONTH

In Part Two, next month, we'll be taking a look at soldering techniques, service aids, and circuit board assembly.

INTERFACE

Robert Penfold

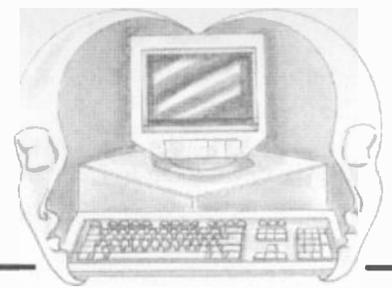

AUTO-RANGING RESISTANCE METER INTERFACE

LAST MONTH'S *Interface* article covered a simple PC-based Capacitance Meter. This month we continue in a similar vein, with a PC-based Auto-Ranging Resistance Meter.

The system has eight-bit resolution and full scale values of 2540 ohms, 25.4k, 254k, 2.45M, and 25.4M. The fact that the system has five ranges is not readily apparent to the user due to the auto-ranging. You simply connect up any resistor from a few tens of ohms to many megohms in value, and the value of the resistor is displayed on the screen of the monitor.

Constant Current

The block diagram of Fig. 1 helps to explain the basic principle used in the Resistance Meter Interface. The resistor under test is fed from a constant current generator, and the voltage developed across the resistor is then proportional to its value.

For example, suppose that a current of one milliamp (0.001 amps) is used. With a one kilohm test resistor the voltage developed across the resistor would be one volt ($1000 \text{ ohms} \times 0.001 \text{ amps} = \text{one volt}$). A resistance of two kilohms would give an output voltage of two volts ($2000 \text{ ohms} \times 0.001 \text{ amps} = \text{two volts}$), a resistance of three kilohms would give an output voltage of three volts, and so on.

In other words, the circuit operates as a simple resistance-to-voltage converter. The computer measures the output voltage via an analogue-to-digital converter and uses some basic mathematics to give an answer in ohms, kilohms, or megohms.

A very high input impedance buffer amplifier ensures that the converter draws no significant current from the constant current generator. This enables very low test currents to be used. In the actual interface the buffer amplifier is an integral part of the converter chip.

The interface actually has five switched currents, which provide it with the five measuring ranges. The constant current generator is under computer control via five outputs of the printer port, and the software selects the best range to use for a given resistance (i.e. the range that gives the highest in-range reading).

Meter Circuit

The full circuit diagram for the Auto-Ranging Resistance Meter Interface is shown in Fig. 2. The analogue-to-digital converter IC1 is a TLC5481P serial type.

This part of the circuit is essentially the same as the converter that was described in the November 1995 issue, and it utilizes the same method of connection to the host PC's printer port. Refer to the November 1995 issue of EPE if you require more information on the converter.

The converter differs from the original design only in that resistors R1 and R3 are used to set the full scale value of the converter at a little under 4V, whereas the original circuit had a full scale sensitivity of 5V. This is done to ensure that the resistance meter circuit can drive the converter to its full scale value.

The constant current generator actually consists of five generator circuits, with a different one being used for each range. If we consider the current source based on transistor TR2, this is basically just a conventional constant current generator having temperature stabilisation provided by diode D1.

Preset potentiometer VR1 enables the output current to be set at the correct

level of one milliamp. The emitter resistances in the other current sources are progressively higher, giving output currents of $100\mu\text{A}$, $10\mu\text{A}$, $1\mu\text{A}$, 100nA , and 10nA .

Transistor TR1 operates as a common emitter switch, and it is controlled by one

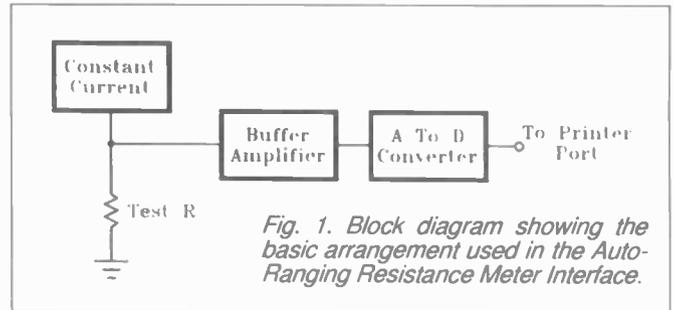


Fig. 1. Block diagram showing the basic arrangement used in the Auto-Ranging Resistance Meter Interface.

of the data outputs of the printer port. If the line controlling TR1 is set high, TR1 conducts and brings transistor TR2 into operation. With the line controlling TR1 set low, TR1 does not conduct, and TR2 is switched off. In use only one of the five lines controlling the current sources is set high at any one time, so that four of the sources are switched off, and one is brought into action.

The outputs of the constant current generators are connected in parallel. The output current from transistor TR10 is extremely low, which could give problems with minute leakage through TR2, TR4, TR6, and TR8 adding significantly to TR10's output current. No significant problems of this type were experienced with the prototype system, but accuracy on the 25.4M range might not be as good as on the other ranges.

Because very low test currents are used on the higher ranges, the circuit is vulnerable to stray pickup of electrical noise. This could result in unstable readings.

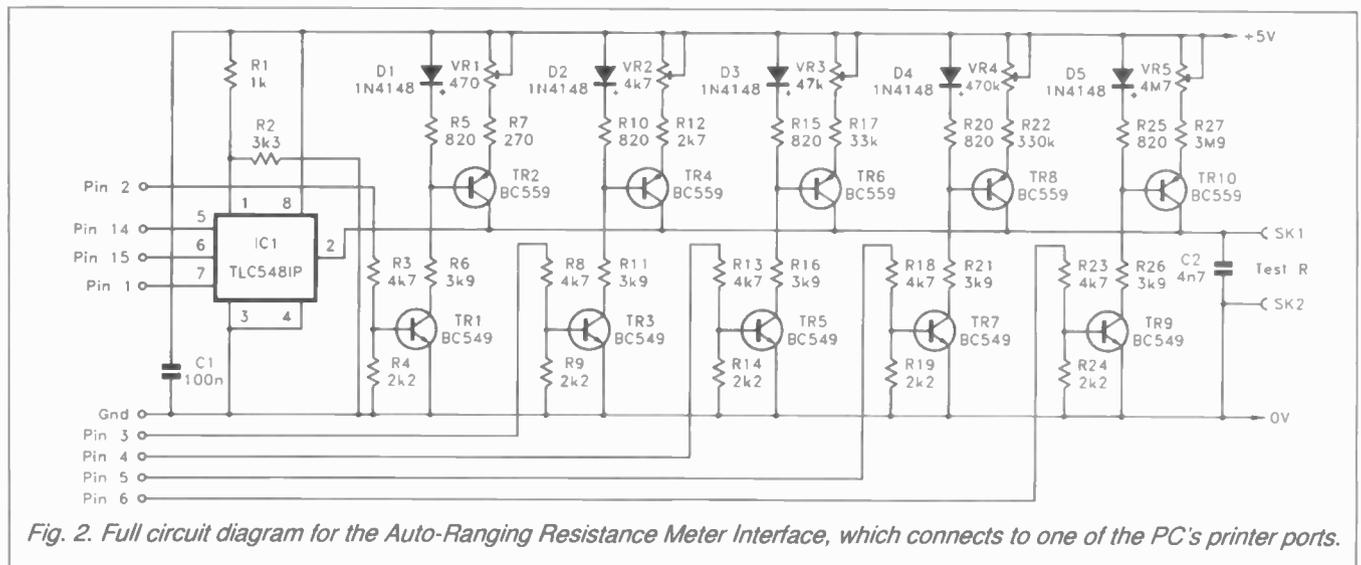


Fig. 2. Full circuit diagram for the Auto-Ranging Resistance Meter Interface, which connects to one of the PC's printer ports.

To minimise this problem the wiring to the "Test" sockets SK1 and SK2 must be kept as short as possible. Filter capacitor C2 should then be sufficient to keep the noise down to an insignificant level.

Software

The software for the Auto-Ranging Resistance Meter Interface is provided in Listing 1. The subroutine at line 310 is essentially the same as the routine provided in the November 1995 issue, and it simply reads the converter. The returned value is placed in variable "X." Double reads of the converter are used to ensure that the program always operates on fresh data.

The main program tries the unit on the lowest range, and if necessary works through to the highest range in an attempt to obtain an in-range reading. If an in-range reading is obtained, the program branches to the appropriate sub-program where the value in "X" is manipulated into the correct units and printed on screen.

For example, a value of 121 on the second range will be printed on screen as "12.1 kilohms", and not simply as "121." The program blanks the screen if no in-range reading is obtained, and then loops until an in-range reading is detected.

A delay is used each time the system is switched to a new range, to give the constant current generator circuit a chance to adjust to the change-over before a new reading is taken. The value of 10000 used at lines 40, 90, 140, 190, and 240 gives good results with a 75MHz Pentium PC, but a higher value

Listing 1: Auto-Ranging Resistance Meter Interface.

10 REM Resistance meter program	300 GOTO 30	590 X = X + Y
20 CLS	310 OUT &H37A,1	600 OUT &H37A,3
30 OUT &H378,1	320 OUT &H37A,3	610 OUT &H37A,2
40 FOR D = 1 TO 10000:NEXT	330 OUT &H37A,2	620 Y = INP(&H379) AND 8
50 GOSUB 310	340 X = INP(&H379) AND 8	630 Y = Y/4
60 GOSUB 310	350 X = X * 16	640 X = X + Y
70 IF X < 255 THEN GOTO 730	360 OUT &H37A,3	650 OUT &H37A,3
80 OUT &H378,2	370 OUT &H37A,2	660 OUT &H37A,2
90 FOR D = 1 TO 10000:NEXT	380 Y = INP(&H379) AND 8	670 Y = INP(&H379) AND 8
100 GOSUB 310	390 Y = Y * 8	680 Y = Y/8
110 GOSUB 310	400 X = X + Y	690 X = X + Y
120 IF X < 255 THEN GOTO 760	410 OUT &H37A,3	700 OUT &H37A,3
130 OUT &H378,4	420 OUT &H37A,2	710 OUT &H37A,1
140 FOR D = 1 TO 10000:NEXT	430 Y = INP(&H379) AND 8	720 RETURN
150 GOSUB 310	440 Y = Y * 4	730 LOCATE 10,30
160 GOSUB 310	450 X = X + Y	740 PRINT X * 10;"ohms "
170 IF X < 255 THEN GOTO 790	460 OUT &H37A,3	750 GOTO 30
180 OUT &H378,8	470 OUT &H37A,2	760 LOCATE 10,30
190 FOR D = 1 TO 10000:NEXT	480 Y = INP(&H379) AND 8	770 PRINT X / 10;"kilohms "
200 GOSUB 310	490 Y = Y * 2	780 GOTO 30
210 GOSUB 310	500 X = X + Y	790 LOCATE 10,30
220 IF X < 255 THEN GOTO 820	510 OUT &H37A,3	800 PRINT X;"kilohms "
230 OUT &H378,16	520 OUT &H37A,2	810 GOTO 30
240 FOR D = 1 TO 10000:NEXT	530 Y = INP(&H379) AND 8	820 LOCATE 10,30
250 GOSUB 310	540 X = X + Y	830 PRINT X / 100;"megohms "
260 GOSUB 310	550 OUT &H37A,3	840 GOTO 30
270 IF X < 255 THEN GOTO 850	560 OUT &H37A,2	850 LOCATE 10,30
280 LOCATE 10,30	570 Y = INP(&H379) AND 8	860 PRINT X / 10;"megohms "
290 PRINT " "	580 Y = Y/2	870 GOTO 30

might be needed for faster PCs. With very slow PCs each loop of the program might take an inordinately long time, and a lower value would then be appropriate.

Initially the five preset resistors should be set for about half maximum resistance. Close tolerance resistors having

values of 2k2, 22k, 220k, 2M2, and 10M are used to calibrate the interface. Connect the 2k2 resistor to SK1 and SK2 and adjust VR1 for a reading of 2k2, connect the 22k resistor instead and adjust VR2 for a reading of 22k, and so on, working through to the 10M resistor and a reading of 10M set via preset VR5.

PIC EEZE

PIC EEZE-V2

Program/read/verify 16C54/55/56/57/58/61/62/620/621/62263/64/71/73/74/84. Expansion port

Built and Tested Only £52.95


PIC EEZE-V3

As above but with In-Circuit Emulation Capability.

Built and Tested Only £72.95

Both systems have ZIF sockets unlike similar priced systems and operate via serial or parallel link to PC, all software provided. (V2 upgradeable to V3)

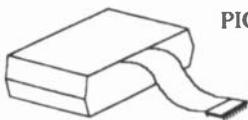Other PIC developments. Learning pack for beginners, demonstration pack, PIC basic (Tel/write for details)



True PIC based
Real
Time
In
Circuit
Emulation

TRICE™
PIC Real Time In-Circuit Emulation.

- Real time to 4MHz.
- Step/Skip/Animate/Run etc.
- Variable speed selection.
- Supports most 18/28 pin PIC's (Tel/write for further specs.)

Only £149.95

Test your code in a
'TRICE'

NEW

Lennard

Please add £2.00 P&P and
make cheques payable to
LENNARD RESEARCH

29 Lavender Gardens, Jesmond, Newcastle upon Tyne, NE2 3DD.
Telephone (0191) 281 8050.

FREE CATALOGUE

THINK COMPONENTS - THINK CRICKLEWOOD

- TELEVISION & VIDEO SPARES • RESISTORS & CAPACITORS • HI-FI GADGETS & SPEAKERS
- TRANSISTORS & I.C.'s • AUDIOPHILE CAPACITORS
- IN CAR AUDIO • COMPUTER BOARDS • TOOLS & TEST EQUIPMENT • PLUGS SOCKETS & LEADS



PLEASE SEND ME A COPY OF THE CRICKLEWOOD CATALOGUE.

Name.....

Address.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

PRICES HELD INTO 1996

Cricklewood Electronics Ltd, 40-42 Cricklewood Broadway,
London NW2 3ET. Tel: 0181-450 0995 Fax: 0181-208 1441

EVERYDAY

PRACTICAL

ELECTRONICS

BACK ISSUES

We can supply back issues of *EPE* by post, many issues from the past five years are available. An index for each year is also available – see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one article* (or *one part* of a series) can be purchased for the same price.

DID YOU MISS THESE?

MAY '95 Photostats Only (see below)

PROJECTS ● PIC-DATS-1 (PIC Development and Training System) ● R.F. Signal Generator – 1 ● MIDI Pedal ● Club Vote Totaliser ● Name of the Game-3, On Your Marks and Games Timer.
FEATURES ● Electronics from the Ground Up, Part 8 ● Las Vegas Show Report.

JUNE '95 Photostats Only (see below)

PROJECTS ● PIC-DATS-2 (PIC controlled 4-Channel Light Chaser) ● EPE HiFi Valve Amplifier – 1 ● R.F. Signal Generator – 2 ● AA to PP3 Converter ● Name of the Game – 4, Star-Struck!, Six-Shot Light Zapper, Wander Wands.
FEATURES ● Electronics from the Ground Up, Part 9 ● Smart Cards.

JULY '95

PROJECTS ● Windicator ● Curtain Winder ● Ramp Generator – 1 ● High Voltage Capacitor Reformer ● EPE HiFi Valve Amplifier – 2
FEATURES ● Bridge Rectification Enhanced ● Ingenuity Unlimited.



AUG '95

PROJECTS ● Solar Seeker ● Personal Practice Amplifier ● Infra-Red Remote Control Unit ● Versatile Microcontrolled 3-Digit Timer ● Ramp Generator – 2.
FEATURES ● Static ● Circuit Surgery.

SEPT '95 Photostats Only (see below)

PROJECTS ● Simple Theremin ● Low Range Ohmmeter Adaptor ● Comprehensive Security System ● Vandata ● Hum-Free Battery Eliminator.
FEATURES ● Cave Radio ● Ingenuity Unlimited.

OCT '95

PROJECTS ● Ginormous VU Meter ● Sound Switch ● Audio Sinewave Generator ● Treble Booster ● Infra-Red Controller/Alarm ● Capacitor Check ● Experimenter's Bargraph Test Board.
FEATURES ● Circuit Surgery ● Security Tagging ● Using Bargraph Displays.
FREE ● Multi-Project PCB with this issue.

NOV '95 Photostats Only (see below)

PROJECTS ● Digital Delay Line ● Video Enhancer ● 50Hz Field Meter ● Temperature Warning Alarm ● Current Tracer ● Distortion Effects Unit.
FEATURES ● Teach-In '96 Part 1 ● Developments in Radio Broadcasting Technology ● Turnpike for Windows Review ● Ingenuity Unlimited.

DEC '95 Photostats Only (see below)

PROJECTS ● Light Operated Switch ● Stereo "Cordless" Headphones ● EPE Met Office – 1 ● Modular Alarm System ● Audio Meter and Amplifier.
FEATURES ● Teach-In '96 Part 2 ● Circuit Surgery ● Index for Volume 24.

JAN '96

PROJECTS ● Printer Sharer ● Mains Signalling Unit ● Automatic Camera Panning System ● Audio Signal Generator ● EPE Met Office – 2.
FEATURES ● Teach-In '96 Part 3 ● Ingenuity Unlimited ● European Consumer Electronics Show ● Techniques – Actually Doing It ● Maths Plus Review ● Decibels and dBm Scale.

FEB '96 Photostats Only (see below)

PROJECTS ● Simple PIC16C84 Programmer ● Mains Signalling Unit – 2 ● PIC Electric Meter – 1 ● Vari-Speed Dice ● Analogue Frequency Meter.
FEATURES ● Teach-In '96 Part 4 ● Circuit Surgery ● Making Your Own P.C.B.s ● Techniques – Actually Doing It.



MARCH '96

PROJECTS ● Mind Machine Mk III Part 1 ● High Current Stabilized Power Supply ● Multi-Purpose Mini Amplifier ● Infra-Zapper ● PIC-Electric Meter – 2.
FEATURES ● Teach-In '96 Part 5 ● Ingenuity Unlimited ● Flight PAL Trainer Review.
FREE ● Headphones (UK copies only).

APRIL '96

PROJECTS ● Dolby Pro-Logic Decoder (Free Booklet) ● Bat-Band Converter ● Event Counter ● Mind Machine Mk III Part 2 – Programmer ● Hearing Tester.
FEATURES ● Teach-In '96 Part 6 ● Circuit Surgery ● Thermionic Valves Part 1.

MAY '96

PROJECTS ● Midi Analyser ● Mind Machine Mk III Part 3 – Tape Controller ● Versatile PIR Detector Alarm ● Countdown Timer ● Bat Band Converter B.F.O.
FEATURES ● Teach-In '96 Part 7 ● Ingenuity Unlimited ● Thermionic Valves Part 2 – The C.R.T.

URGENT?

NEED AN ARTICLE TODAY? TRY OUR FAX ON DEMAND SERVICE – see opposite for details

JUNE '96

PROJECTS ● Sarah's Light ● Ultra-Fast Frequency Generator and Counter Part 1 ● VU Display and Alarm ● Pulstar ● Home Telephone Link.
FEATURES ● Teach-In '96 Part 8 ● More Scope for Good Measurements Part 1 ● Circuit Surgery ● Miniscope Review.

JULY '96

PROJECTS ● Advanced NiCad Chargers ● Single-Station Radio 4 Tuner ● Games Compendium ● Twin-Beam Infra-Red Alarm ● Ultra-Fast Frequency Generator and Counter – 2.
FEATURES ● Teach-In '96 Part 9 ● More Scope for Good Measurements Part 2 ● Circuit Surgery ● The Internet ● Ingenuity Unlimited.

AUG '96

PROJECTS ● Component Analyser ● Garden Mole-Ester ● Mono "Cordless" Headphones ● Bike-Speedo ● Mobile Miser.
FEATURES ● Teach-In '96 Part 10 ● Circuit Surgery ● Ingenuity Unlimited ● Spies, Lies and Electronics ● EPT 3.0 Review.

SEPT '96

PROJECTS ● Analogue Delay and Flanger ● Simple Exposure Timer ● PIC-Tock Pendulum Clock ● Draught Detector ● Power Check.
FEATURES ● Circuit Surgery ● Ingenuity Unlimited ● Net Work – The Internet ● MAX038 Waveform Generator.

OCT '96

PROJECTS ● Video Fade-To-White ● Direct Conversion Topband and 80m Receiver ● Vehicle Alert ● 10MHz Function Generator.
FEATURES ● Introduction to Satellite Television ● Ingenuity Unlimited ● Circuit Surgery ● Net Work – The Internet.

BACK ISSUES ONLY £2.50 each inc. UK p&p.

Overseas prices £3.10 each surface mail, £4.10 each airmail.

We can also supply issues from earlier years: 1990 (except March), 1991 (except May, June, Aug., Sept. and Nov.), 1992 (except April and Dec.), 1993 (except Jan., Feb., March, April and May), 1994 (except April, May, June and Nov.), 1995 (except Jan., May, June, Sept., Nov. and Dec.). Please note we are not able to supply copies (or 'stats of articles) of *Practical Electronics* prior to the merger of the two magazines in November 1992.

Where we do not have an issue a photostat of any *one article* or *one part* of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOSTATS – INDEXES

- Send back issues dated
- Send photostats of (article title and issue date)
- Send copies of last five years indexes (£2.50 for five inc. p&p – Overseas £3.10 surface, £4.10 airmail)

Name

Address

I enclose cheque/PO./bank draft to the value of £.....

Please charge my Visa/Mastercard £.....

Card No. Card Expiry Date

Note: Minimum order for credit cards £5. Please supply name and address of cardholder if different from that shown above.

SEND TO: **Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.**

Tel: 01202 881749. Fax: 01202 841692. (Due to the high cost we cannot reply to queries or orders by Fax.)

E-mail: editorial@epemag.wimborne.co.uk

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

M11/96

FAX ON DEMAND EVERYDAY PRACTICAL ELECTRONICS ON FAX

WHY WAIT?

We Give You The Fax!
Projects and Series
From Past Issues of *EPE*
AVAILABLE INSTANTLY!
24 HOURS A DAY!

HAVE you ever wanted to get hold of a past project or part of a Teach-In series fast? *EPE ON FAX* is a service aimed at providing you with the article you need, on-demand, seven days a week, 365 days a year, 24 hours a day.

All the projects and major series from the the April '95 issue onwards have been stored on computer and linked to a sophisticated selection system that uses the latest voice and Fax technology. You can select the article you require from a menu and have it downloaded to any UK Fax machine on demand.

The service will be constantly updated with new material as each issue is published, thus providing a live, instantly available, resource.

HOW TO USE *EPE ON FAX*

- From your tone telephone or Fax machine call 0897 124 125, making sure that your handset is switched to "tone". You will then hear a series of messages, which will help to guide you through the system.
- For one of the available indexes, which contain the document numbers and the number of pages of each article, press "1" when prompted.
- To obtain a particular document, press "2" when prompted and, when requested, enter the document number you want from the keypad on your phone or Fax machine. The system will then confirm your selection.
- When you have selected the document that you require, you will then be prompted to enter the phone number of the Fax machine you want the article sent to, including the dialing code, finishing with the # key; the system will then confirm the phone number. Ring off when prompted and the Fax will automatically be sent to the given number.

HOW MUCH WILL IT COST?

EPE ON FAX service is a higher rate premium line phone service. Calls cost £1.50 a minute. First time use should cost no more than £3 per index or article. Subsequent use should only be £1.50 per article.

NOTE. Articles over six pages long are split in two, requiring two calls.

FURTHER INFORMATION

If you would like further information about how this project was put together, ring Starcomm Limited on (0113) 294 0600.

TRY IT NOW!
CALL 0897 124 125


Everyday Practical Electronics, November 1996

STEREO CASSETTE RECORDER

A complete, easy to build, design that can be used with most "surplus" cassette decks. An absorbing project produced by Robert Penfold as a result of many requests from readers.

VARI-COLOUR CHRISTMAS TREE LIGHTS

The electronically controlled Christmas tree lights featured in this article consist of a string of ten or twelve tri-colour light emitting diodes (l.e.d.s). A range of colourful effects can be produced, and standard flashing Christmas tree lights simply do not bear comparison to this system. The basic effect is for the lights to be cycled through red, green, yellow and off in a pseudo random fashion.

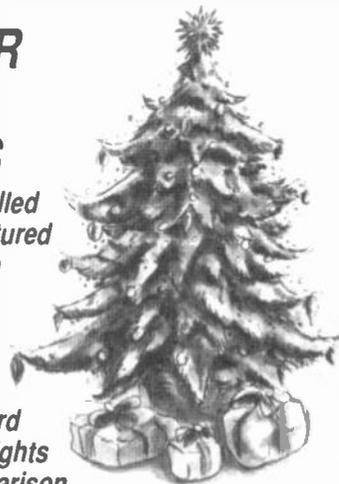

PIC D/A TACHOMETER

Most tachometers are either digital or analogue each with its advantages and disadvantages. The digital ones clearly indicate steady r.p.m. but are not good for indicating trends or where the rotation rate is not steady. On the other hand analogue types are excellent for displaying trends but the meter movements used in automobiles and motorcyles are heavily damped to give a slow response time, because there is a lot of vibration in these environments.

This design combines both digital and analogue displays in a compact, simple design based around a single chip microcontroller. The digital display is a two-digit seven segment type which will display the r.p.m. as multiples of 100 up to 9900 r.p.m. The analogue display consists of a baragraph with 17 elements. The length of the bar indicates the r.p.m. The resolution of the baragraph corresponds to 500 r.p.m. per l.e.d.

EVERYDAY

PRACTICAL

ELECTRONICS

**DECEMBER ISSUE ON SALE
FRIDAY, NOVEMBER 1**

SHOP



TALK

with David Barrington

D.C.-To-D.C. Converters

The main concern for those undertaking any of the *D.C.-To-D.C. Converter* modules is likely to be the sourcing of the "switch-mode" i.c.s. It is quite possible that they will not be available from local or usual mail order outlets.

The TL497CN chip called for in the *Negative Supply Generator* is not exactly the latest chip in switch-mode i.c.s, so it should be carried by quite a few of our component advertisers. However, if you do hit problems, it is currently listed by **Farnell Components (Tel:0113 263 6311)**, code TL497ACN. It is also listed by RS (code 126-6885) but not in *Electromail*, their mail order outlet.

The 330µH inductor coil must be a type that is intended for switch-mode power supplies. An ordinary r.f. choke will not work in this design. If it is to fit on the p.c.b. it should have 5mm lead spacing. The one in the model is an RS type and came from **Electromail (Tel:01536 204555)**, code 228-523.

Turning to the *Step-Down Regulator*, the circuit is based on the LM2575T-ADJ which is claimed to make switch-mode regulators as easy to use as ordinary series voltage regulators.

There are several versions of the LM2575T available and the device used here has an *ADJ* suffix added to its type number. This indicates that it has an adjustable output voltage and must be this type for this circuit. The one used in the module came from **Maplin (Tel:01702 554 161)**, code AD86T.

The inductor L1 must be a switch-mode type and be capable of handling currents up to 1A. It was found that the 330µH "Bobin Type", code AH23A, from the above company and the almost identical RS "High Cur-

rent" type-A version, *Electromail* code 228-438, both performed satisfactorily.

The LM2577T-ADJ needed for the *Step-Up Regulator* can provide output currents up to 3A, with built-in over-current and thermal protection, and was purchased from **Maplin**, code AD90X. It must be the "ADJ" device.

Once again, the 100µH inductor must be a high current type and can be either the RS High Current type-A (Code 228-416) or the Bobin Type, code AH21X, from **Maplin**. On the subject of inductors, its worth checking out the extensive range in the new *Cirkit* catalogue (see advertisement).

The Schottky diodes used in all three models also came from **Maplin**, code GX30H.

Central Heating Controller

With the choice of a pre-programmed microcontroller or source code disk for the *Central Heating Controller*, only a couple of problems could be encountered when searching for components.

If you wish to undertake your own programming, the AT89C2051 microcontroller is listed by RS and should be available through **Electromail (Tel:01536 204555)**, code 157-7567. The 16x2-line liquid crystal display module (code DK63T) and the 5A 240V a.c. single-pole changeover (s.p.c.o.) relays (code YX97F) came from **Maplin (Tel. 01702 554 161)**.

We can only find the 8-bit A/D Converter type ADC0831 listed by **Farnell Components (Tel:0113 263 6311)**, code ADC0831CCN. They also supplied the mains transformer (code 432-696), the pushbutton switches (code 150-247) and the clear display bezel (code 175-708).

A ready-programmed microcontroller is available directly from the designer, **Richard Stone** for the sum of £20 all inclusive.

(Overseas readers should add £2 to their order). All orders should be sent to: **Richard Stone, 2 Carmargue Fold, Bradford, BD2 1HB.** Make cheques payable to **Richard Stone.**

The software source code (8051 machine code) is obtainable on a 3.5in. disk from the Editorial Offices for the sum of £2.50 (Overseas: £3.10 surface; £4.10 airmail), see page 875. Alternatively, Internet users can download it free from our ftp site:

<ftp://ftp.epemag.wimborne.co.uk>

EPE Elysian Theremin

Some of the components needed to put together the *EPE Elysian Theremin* could be described as being marginally special items. Most of these are the "hardware" requirements.

As far as the "active" components go, items such as the diodes and i.c.s. should be stocked by most of our component advertisers. The switched jack sockets, SCJ-0639, are special commercial types used in sound studios and can be purchased from the author, **Jake Rothman**, who specialises in audio work. The nearest we have come to these are the **Maplin** "PCB sockets", with switch contacts.

The designer, **Jake Rothman**, has put together a range of kit options, including hardware, so that readers can select their own requirements. For further details write to him at: **93 St. Johns Road, Frome, Somerset, BA11 2BE.** Also see his advertisement on page 841.

Tuneable Scratch Filter

Only the 8-pin switched capacitor filter i.c. type LTC1063CN8 is likely to cause problems when hunting down parts for the *Tuneable Scratch Filter* project. This appears to be only available from **Electromail (Tel:01536 204 555)**, code 311-956.

Details for all this month's printed circuit boards can be found on page 875.

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX ★ 0131 667 2611

The supplier to use if you're looking for:-

★ A WIDE RANGE OF COMPONENTS AIMED AT THE HOBBYIST

★ COMPETITIVE VAT INCLUSIVE PRICES ★

★ MAIL ORDER - generally by RETURN OF POST ★

★ FRIENDLY SERVICE ★

1995/6 CATALOGUE NOW IN STOCK!
COST: £2.00. Includes vouchers to offset against future purchases.


OPEN: Monday-Thursday 9.15 - 6.00.

Friday 9.15-5.00

Saturday 9.30-5.00



BTEC
Certificated

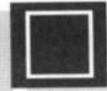

TUTOR
Supported

NATIONAL
COLLEGE OF
TECHNOLOGY

DISTANCE LEARNING COURSES

The National College of Technology offer a range of packaged learning short courses for study at home or in an industrial training environment which carry modular BTEC awards leading to a higher BTEC certificate. Study can commence at any time and at any level enabling you to create a study routine to fit around existing commitments. Courses on offer include:

Analogue Electronics
Digital Electronics
Fibre/Optoelectronics
Mechanics & Mechanisms
Programmable Logic Controllers
Electronic Testing & Fault Diagnosis

Tutor support and BTEC certification are available as options with no travelling or college attendance required. These very popular courses which are ideal for vocational training contain workbooks, audio cassette lecturettes, PCB's, instruments, tools, components and leads as necessary to support the theoretical and practical training. Whether you are a newcomer to electronics or have some experience and simply need an update or certification, there is probably a distance learning course ready for you. Write or telephone for details to:

National College of Technology
NCT Ltd., PO Box 11
Wendover, Bucks
Tel: (01296) 624270

RADIO DATA MODULES SYSTEMS & ACCESSORIES

UK, E.E.C, Scandinavia, Eastern Europe, North & South America, Middle East, South Africa, New Zealand, Far East or Australia. Wherever you are, we have a module on the right frequency for you!

F.M Transmitter & Receiver Starter Kits

- Construct quality F.M remote controls, data links, wire-free alarms *
 - * Range up to 200M with dipole, 5KM with RX Yagi *
- Available on UK 418MHz to MPT1340. Export 433.92MHz, 403Hz. *
- SILRX - Receiver includes, audio, digital data, carrier detect o/p *
- RXM - as SILRX + signal strength RSSI, tamper and jamming det *
- Kit Prices inclusive of VAT and UK 1st Class Postage: *
- TXM-418-A + SIL-418-A + Data/Application Sheets: Only £29.95 *
- TXM-418-A + RXM-418-A + Data/Application Sheets: Only £34.95 *
- Decoder Board for RXM or SIL c/w HT-12-D: Only £15.00 *



TXM-418-A/F Transmitter



SILRX-418-A/F Receiver



RXM-418-A Receiver

NEW! High Data Rate (-F) 20,000 bps, 3V Version:

- Same o/p Power but twice as fast as the - A version, up to 20,000 bps *
- Drives directly from PIC port, reducing component count & size *
- TXM-418-F + SILRX-418-F + Manual: Only £29.95 *

TXR-4XX-DTR100 Data Transceiver: Starter Kit £299.95



- 458MHz MPT1329 for UK Operation *
- 433.92MHz for European I-ETS-300-220 *
- 472MHz for Australia and NZ *
- 462 - 465MHz for North America *
- Up to 500M range with Internal Antenna *
- Up to 5KM range with External Dipole *

Prices 1 + £179.95 10 + £149.95 100 + £115.00

- UK, 173MHz to MPT1344 & MPT1328 Licence Exempt *
- Australia and South Africa Licence Exempt
- F.M Operation: With 1mW, 10mW or 20mW Versions
- Range up to 1 to 5 Km line-of-site *
- Low Cost or High Performance versions *
- Transmitters, Receivers and Transceivers
- Starter Kits From £59.00 to £199.00 *

PCB mounting or D-Type Interfaced Options

100mW Spread Spectrum Transceiver

Operates on the globally accepted 2.45GHz band. Complete with antenna diversity switch and RS485 serial interface. With a data rate of between 250K bps to 1M bps we challenge you to find a faster and more secure wire free solution!

Starter kit: comprising 2 of TXR-2450-100M transceivers and 2 2.45GHz dipole antenna. Save nearly 20% on MLP at only : 799.95 per pair. Export Only!!

Probably the smallest wire-free modem in the World exclusively from Radio-Tech. The Cyphernet 1M and 10M represent the latest in SMT RF technology and offer the user a low cost off-the shelf solution to their communications needs. Windows 3.11 and 95 compatible, equally at home in the PC networking environment the unit may be used for EPOS, bar-code, Telemetry and Telecommand applications. Price start from 79.95 each. Optional interface cables 7.95. + VAT for 9-pin D-Type Version.

- Only 40 x 60 x 15mm *
- Up to 19200 bps Half Duplex *
- ESD protected RS232 Port *
- Carrier detect output *
- User EEPROM *

SECURITY

ULTRASONIC MOVEMENT DETECTOR
Xtal controlled oscillator, detector circuits & edge mounted transducers on one PCB just 75x40mm. Detection range 4-7m. Adjustable sensitivity LED indicator Outputs to drive external relay/circuits. 9V DC operation. 3049-KT. £14.95



MINI CCTV CAMERA



FEATURES

- Compact & light camera PCB module 54Wx38L x30mmH. 33 grams
- Low power consumption 12V DC, 150mA
- Low light requirement 0.1Lux (IR LED on)
- High quality, high resolution CCIR image 512x562 pixels
- Video output 1Vp-p/75Ω
- Lens 3.6mm, F1.8
- Field of view 74°H x 55°V
- Maintenance free
- Built-in electronically controlled auto-iris
- Internal synchronisation

Latest high quality IR-sensitive monochrome camera module for Video Intercom CCTV, Surveillance etc. Simply plug into smart or video. Six on-board IR LED's. Less than half the size of a cigarette pack!

ASSEMBLED UNIT: 30A7-AS £89.95

X-FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. N.B. Minimum order charge for reports and plans is £5.00 PLUS normal P.&P

SUPER-EAR LISTENING DEVICE Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. R002 £3.50

TELEPHONE BUG PLANS Build your own micro-beetle telephone bug. Suitable for any phone. Transmits over 250 metres - more with good receiver. Made from easy to obtain, cheap components. R008 £2.50

LOCKER - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. R008 £3.50

RADIO & TV JOKER Complete plans for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities!! DISCRETION REQUIRED. R017 £3.50

INFINITY TRANSMITTER PLANS Complete plans for building the famous infinity transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for home/office security! R019 £3.50

THE ETHER BOX CALL INTERCEPTOR PLANS Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! R025 £3.00

GENERAL KITS

3 DIGIT LED COUNTER 2 board basic event counter. Main board has 3 digit counter circuit. 2nd board has Count & Reset switches & debounce circuit. Cascaded with other boards to provide more digits. Box & battery holder provided. 9V battery 78x50x25mm. 3001-KT £14.95

OP-AMP FUNCTION GENERATOR Quad Op-Amp connected as oscillator & wave shapers to generate audio range wave-forms. Oscillator generates Square Wave from 6Hz to 6kHz. Other amps produce Triangle & pseudo Sine outputs. Solder pad outputs. 9V powered. 47x40x22mm. 3023-KT £4.95

LOGIC PROBE Original, modern design tests both CMOS & TTL circuits as well as detecting fast pulses. Gives visual & audio indication of logic states found. Operates from front or rear test. It's operation is fully explained. 3024-KT £7.95

ROULETTE LED A great introduction to gambling... er electronics! Watch the 'ball' spin round the roulette wheel, slow down & drop into slot. Uses 10 LED's, CMOS decade counter & Op-Amp to teach Voltage Controlled Oscillator (VCO) principles. 9V powered. Educational & fun! 3008-KT £10.95

PELTIER JUNCTION HEAT PUMP Boil or freeze water instantly! Use for regulated cooling of temperature sensitive components and much more. 3066-KT £21.95

9V XENON TUBE FLASHER This powerful high voltage xenon flasher runs off a simple 9V battery. A transformer is used to step up the 9V supply voltage to the high voltage to flash the 25mm long tube. Flash between 0.25 to 2 second intervals. £11.95

LM383 AMPLIFIER MODULE Proven, popular building block for use in any audio project where general amplification required. Power output dependent on supply voltage & load resistance. Typical ratings: Over 10W for 16V supply & 2W speaker; 1W for 9V supply & 8Ω speaker. 3047-KT £3.95

plus AUDIO • EDUCATIONAL • LASER • SECURITY • TEST GEAR • BOOKS & more

Our high quality project kits are supplied with all components, fibre glass PCB's & comprehensive instructions. FREE CATALOGUE with order or send 2 x 1st Class stamps (refundable) for details of over 100 kits & publications. Mail order only. Please ADD £2.00 P. & P. (Europe £3, Rest of World £5) & make cheques/PO's payable to Quasar Electronics. Goods normally despatch within 5 working days. Please allow 28 days for delivery. Prices include VAT at 7.5%. For safety send cash by recorded delivery.

Quasar Electronics Unit 14 S.Jinningdale BISHOP'S STORTFORD Herts CM23 2PA
E-mail 101364 3510 @compuserve.com
Website: http://ourworld.compuserve.com/homepages/QuasarElectronics

Established 1990



COMBINATION LOCK Versatile electronic lock comprising main circuit & separate 9 key touch-pad for remote opening of lock. 120VAC/10A relay supplied. 9-12V 3029-KT £9.95

LIGHT ALARM Protect your valuables with the practical, clever little circuit. Alarm sounds if even the smallest amount of light falls on the circuit. Place in cash box etc. 3008-KT £4.95

THE SCREAMER! Painful alarm siren gives out a massive 110db of ear piercing noise. Box supplied has two 35mm piezo elements already built into their own resonant cavity. PCB fits inside box to give a neat, compact unit. Use as part of an alarm circuit or just for the fun of it! 6-9V operation. 3015-KT £5.95

SURVEILLANCE

High performance surveillance kits. Room transmitters supplied with sensitive electret microphones & battery holders/clips. All transmitters can be received on an ordinary VHF FM radio.

MTX - Miniature 3V Transmitter
Easy to build & guaranteed to transmit 500 metres (over 1000m possible with higher voltage & better aerial). 3-9V operation. Only 45x18mm. 3007-KT £4.95

MRTX - Miniature 9V Room Transmitter
Our best selling 'bug'. Super sensitive, high power - 1000m range (Up to 2 miles with 18V supply & better aerial). 9V operation. 45x19mm. 3018-KT £5.95

HPTX - High Power Room Transmitter
High performance, 2 stage transmitter gives greater stability & high quality reception. 1000m range with 9V battery. 6-12V operation. On/off switch. Size 70x15mm. 3032-KT £6.95

VTX - Voice Activated Transmitter
Powerful 2 stage voice activated transmitter. Only operates when sounds are detected. 1km range. Low standby current - conserves battery power. Adjustable sensitivity & turn-off delay. Only 63x38mm. 3028-KT £6.95

TRI - Telephone Recording Interface
Connect between phone line & cassette recorder. Automatic-ally switches on tape when phone is used. Records all conversations. Powered from line. 48x32mm. 3033-KT £6.95

TRVB - Tape Recorder Vox Switch
Very sensitive, voice activated switch - automatically turns on cassette recorder when sounds are detected. Adjustable sensitivity & turn-off delay. 115x18mm inc. case. 3013-KT £7.50

MTTX - Miniature Telephone Transmitter
Attaches anywhere to phone line. Transmits only when phone is used! Uses phone line as aerial & power source. 500m range. 45x15mm. 3016-KT £5.50

Two Station /Hard Wired Bug
Each unit has its own speaker, microphone & amplifier (LM3886). Turn into a hard wired bug by using 4 stand ribbon cable supplied to send power from the receiving unit to the remote 'bug' unit. 9V. 3021-KT £12.95

Telephone Amplifier Kit
Pick-up coil & sensitive amplifier let you hear conversations without even holding the phone! Can be used for surveillance purposes. 3055-KT £8.95

LED SEQUENCE/RANDOM FLASHER, 5 ultra bright red LED's flash in sequence or random. Ideal for model railways. On/off switch. COB PCB 15x8mm (spare provided). 3V powered. 3052-KT £4.95

LEO DICE The classic electronic project that never loses its popularity. Combines a great game with an easy introduction to electronics & simple circuit analysis. 7 LED's emulate a real dice face. The dice rolls, slows down, stops on a number at random. Uses a 555 timer & counter IC. Box included. 9V operation. 3003-KT £8.95

STAIRWAY TO HEAVEN GAME The game of skill tests your hand-eye co-ordination. If you press the switch each time the green part of the bi-polar LED lights you climb higher up the stairway - but miss & you start again! Introduces you to several basic electronic circuits. Box provided. 9V operation. 78x50x19mm. Rolle Harms Not included! 3006-KT £8.95

DC MOTOR SPEED CONTROLLER
Control the speed of any common DC motor rated up to 100V (5A). Operates on 5-15V. Uses NE566 IC to pulse-width modulate a TIP122 high current, switching power transistor. In this way torque of the motor is not lowered. Box mounted. 3067-KT £19.95


SWITCHING POWER SUPPLY Replace expensive 9V batteries with cost-efficient 1.5V cells. IC based circuit acts as a step-up switching power supply. Selectable 1.5 or 3V DC outputs. Gives a fixed output of 9V (a 18mA from a 1.5V 'AA' cell). Solder pads for input/output. 1 cell & 2 cell 'AA' holders & jumper switches supplied. 40x16x12mm. 3035-KT £4.95

SINGLE CHIP AM RADIO Complete mini sized AM radio on a PCB. Tuned Radio Frequency front-end. AM Radio IC & 2 stages of audio amplification. All components supplied inc. prewound coil & speaker. 32x102mm. 3063-KT £9.95

TRAIN SOUNDS 4 selectable sounds - Whistle, Blowing, Level Crossing Bell, Chugging & 'Clickety-Click'. 2.5-5V. Supplied with all components inc. speaker. 16 x 29mm COB PCB, switches & 2 x 'AA' battery holders. SGI £4.95

TUNEABLE SCRATCH FILTER

ROBERT PENFOLD

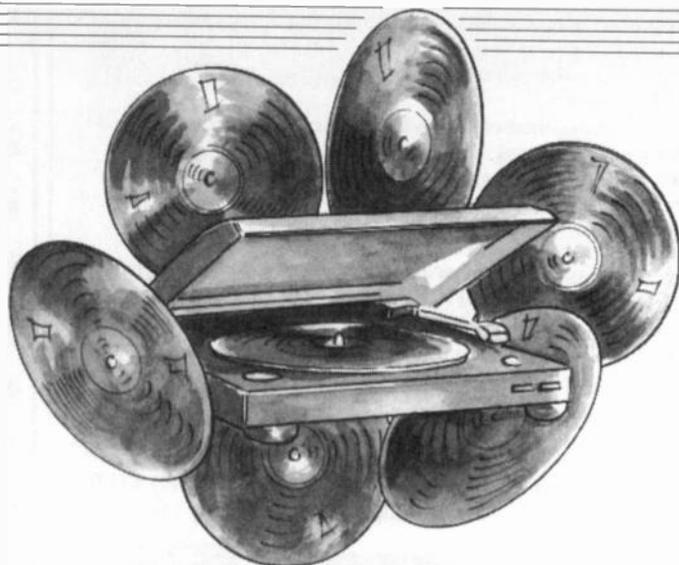

Bring your treasured "golden oldies" up to scratch and give your ageing "vinyls" a new spin!

VINYL records are no longer in large scale commercial production, having been supplanted by compact discs (CDs), but many people still have large collections of ageing LPs.

Much of the programme matter on these LPs has been made available on compact discs, but there is still a fair percentage of material which has yet to be released on CD. Even where your favourite "golden oldies" are available in digital form, buying everything in your collection again could prove to be prohibitively expensive!

UP TO SCRATCH

Although LPs are obsolete, it seems likely that they will still be in widespread use for many years to come. Record players and record decks are certainly still available and selling in large numbers.

This leaves the problem of extracting reasonably high fidelity from increasingly worn records. Using high quality playing equipment and record cleaning devices will minimise wear, but there seems to be an inevitable increase in "surface" noise over the years.

The standard way of dealing with this background "crackling" sound is to use a scratch filter to process the signal from the record deck. A filter of this type is just a simple lowpass type which has a cut-off frequency that is usually at about 5kHz to 7kHz.

Surface noise is produced by tiny imperfections in the groove walls, or by minute particles of dust in the grooves. The small size of the imperfections and dust particles results in them producing very brief "click" sounds. The frequency content in these sounds is predominantly at high audio frequencies at around 5kHz to 20kHz.

Because surface noise is largely at high frequencies, attenuating these frequencies

produces a large amount of noise reduction. It also produces some loss of fidelity, because some of the main signal is also attenuated. This gives a less "bright" sound, but where the surface noise has become quite severe, the reduction in noise easily outweighs the general loss of treble.

ROLL-OFF RATE

There seems to be no generally accepted optimum attenuation rate for a scratch filter. Backing off an ordinary treble tone control will give a reduction in surface noise, but the attenuation rate of 6dB per octave means that the improvement is limited, and there is some attenuation of signals at lower frequencies.

A roll-off rate of 12dB or 18dB per octave is generally considered to give better results, and true "brickwall" filtering having an attenuation rate of about 100dB per octave is sometimes used. However, for most tastes such sharp filtering sounds rather too obvious, and unmusical.

The cut-off frequency of most scratch filters is fixed, and has to be a compromise figure. If a record is suffering from a moderate amount of surface noise a relatively high cut-off frequency of about 8kHz or 9kHz will probably provide the best results.

For a record that is in rather poor condition a much lower cut-off frequency is usually needed in order to effectively reduce the surface noise. A cut-off frequency as low as 3kHz to 4kHz might be needed.

The Tuneable Scratch Filter described here provides an attenuation rate of 30dB per octave, which is high enough to ensure a high degree of noise reduction while leaving the music as little affected as possible. The roll-off rate is not so high as to make the filtering over-obvious and intrusive.

Using switched capacitor filters makes it possible to vary the filter's cut-off frequency over a useful frequency range. The -6dB point can be varied from under 3kHz to around 9kHz to 10kHz. The cut-off frequency can therefore be varied to suit the surface noise present on each record. This factor, together with the relatively high attenuation rate of the filtering, enables excellent results to be obtained with practically any record.

SWITCHED CAPACITORS

Conventional active filter configurations can easily provide attenuation rates of around 30dB per octave, but it is impractical to have a high attenuation rate and a variable cut-off frequency. An attenuation rate of 30dB per octave would require a five-gang potentiometer, or a 10-gang type for a stereo filter.

Switched capacitor filters are a more practical proposition, as they permit high attenuation rates to be obtained, and the



cut-off frequency is controlled via a clock signal. In order to vary the cut-off frequency, it is merely necessary to vary the clock frequency.

A basic switched capacitor filter is quite similar to a conventional CR filter. Fig. 1a shows the circuit for a single stage CR lowpass filter.

With a low frequency input signal the charge on capacitor C1 can accurately track the input voltage, giving no significant losses through the circuit. At higher frequencies the current flow in and out of C1 must be higher in order to maintain an output signal at virtually the same level as the input signal.

Resistor R1 limits the amount of current that can flow, and above a certain frequency it begins to keep the current flow below the level at which the output level can be sustained. Taking the input frequency above this frequency produces increasing losses through the circuit, with an ultimate attenuation rate of 6dB per octave. In other words, each doubling of the input frequency causes the losses through the circuit to double.

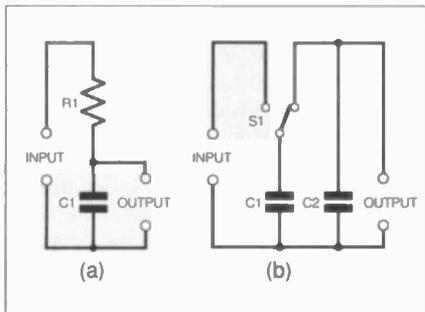


Fig. 1(a). A normal CR filter and (b) the switched capacitor equivalent.

ALL PUMPED-UP

The switched capacitor equivalent to a CR lowpass filter is shown in Fig. 1b. The resistor is replaced by a switch and a capacitor (C1 and S1). In a practical circuit the switch is an electronic type controlled by a clock oscillator. Capacitor C2 is the equivalent of C1 in the CR filter.

The basic action of the circuit (Fig. 1b) is for C1 to be connected to the input where it charges to the input potential, and then to C2 where it modifies the charge on C2. In practice, switch S1 is operated continuously, and at a frequency that is typically between about 20kHz and 1MHz.

With a static input voltage, capacitor C2 is soon charged to a potential that is virtually equal to the input voltage. Capacitor C1 repeatedly charges from the input signal, and discharges into C2, rapidly "pumping-up" the potential on C2 to a level that is virtually the same as that on C1.

If the input voltage increases, the same action will again boost the charge on C2 to a level that is practically the same as the input voltage. A reduction in the input voltage results in C1 being charged from C2, and discharged to some extent into the signal source. The charge on C2 therefore falls to a level that is virtually the same as the input voltage.

This circuit can couple the input signal through to the output with minimal losses, but only if the "electronic" switch S1 is operated at a frequency that is much higher

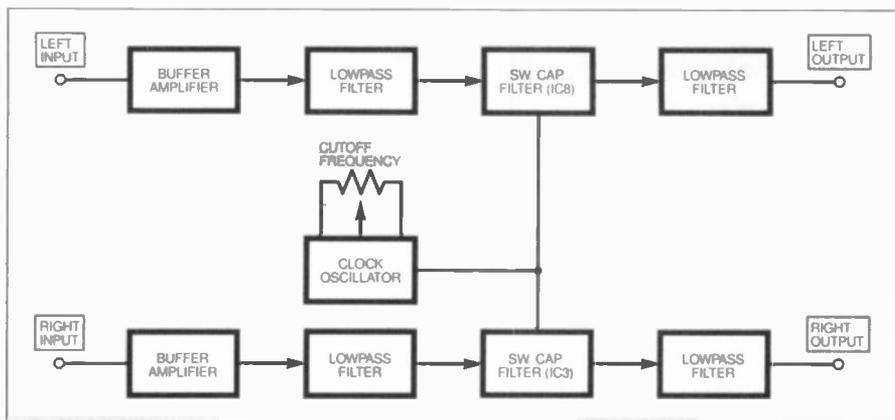


Fig. 2. Block diagram for the Tuneable Scratch Filter.

than the input frequency. This is due to the fact that C1 is made much lower in value than C2.

It therefore takes several charge transfers for the output voltage to respond to a sudden voltage change at the input. Like the resistor in the CR filter, the switch and capacitor can only provide a limited current flow into and out of the filter capacitor, and a 6dB per octave lowpass filter action is obtained above a certain frequency.

The cut-off frequency of a switched capacitor filter is controlled by the clock frequency, and by the relative values of C1 and R1. Practical switched capacitor filters are mostly designed to have a cut-off frequency that is a fiftieth or a hundredth of the clock frequency.

SYSTEM OPERATION

The block diagram of Fig. 2 shows the general arrangement used in this Tuneable Scratch Filter. The two stereo channels are identical.

A buffer amplifier at the input provides a suitably low drive impedance for the next stage, which is an ordinary CR active lowpass filter. This has a cut-off frequency that is well towards the upper limit of the audio range, and it does not significantly aid the scratch filtering. Its purpose is to ensure that no high frequency signals enter the switched capacitor filter, where they could react with the clock signal to produce heterodyne tones.

Practical switched capacitor filters invariably seem to have more than one stage, and the device used in this circuit is a five stage type. It has a frequency response which closely approximates that of a "Butterworth" lowpass filter. The clock oscillator is common to both channels, and the filter's cut-off frequency is one hundredth of the clock frequency ($\pm 0.5\%$).

Another lowpass filter is used at the output of the unit. The degree of clock breakthrough at the output of the switched capacitor filter is very low at only about 50 μ V r.m.s., which, on its own, is insufficient to merit any output filtering.

However, the output waveform is a stepped type, rather like the digitised audio output from a digital-to-analogue converter. The high frequency content on the output from the switched capacitor filter will not necessarily cause any problems, but it is as well to severely attenuate it in order to ensure that it cannot cause any difficulties.

COMPONENTS

Resistors

R1, R2, R13, R14 100k (4 off)
R3, R4, R5, R8,
R9, R10, R15,
R16, R17, R20,
R21, R22 5k6 (12 off)
R6, R7, R18, R19 3k9 (4 off)
R11 4k7
R12 1k5
All 0.25W 5% carbon film

Potentiometer

VR1 4k7 rotary carbon, lin

See

TALK Page

Capacitors

C1, C12,
C23, C24 100n ceramic (4 off)
C2, C13 470n polyester (2 off)
C3, C7,
C14, C18 3n3 polyester (4 off)
C4, C8,
C15, C19 4n7 polyester (4 off)
C5, C9,
C16, C20 330p polystyrene (4 off)
C6, C17 4 μ 7 radial elec. 50V (2 off)
C10, C21 10 μ radial elec. 25V (2 off)
C11 180p polystyrene
C22 1000 μ radial elec. 25V
C25 100 μ radial elec. 25V

Semiconductors

D1, D2 1N4002 100V 1A rectifier diode (2 off)
IC1, IC2,
IC4, IC6,
IC7, IC9 LF351N bifet op.amp (6 off)
IC3, IC8 LTC1063CN8 switched cap. filter (2 off)
IC5 4046BE CMOS phase-locked loop
IC10 μ A78L12 12V 100mA regulator

Miscellaneous

SK1 to SK4 phono socket, chassis mounting (4 off)
T1 230V mains transformer, with twin 12V 250mA secondaries (or 12V-0V-12V 250mA secondary)
FS1 250mA 20mm quickblow fuse
S1 rotary mains switch, d.p.s.t.
Metal instrument case, size about 203mm x 127mm x 51mm; printed circuit board, available from the EPE PCB Service, code 115; 8-pin d.i.l. holder (8 off); 16-pin d.i.l. holder; control knob (2 off); pair of 20mm fuse-clips; M3 or 6BA fixings; mains lead and plug; multistrand connecting wire; solder pins, solder, etc.

Approx Cost Guidance Only

£45

excluding case

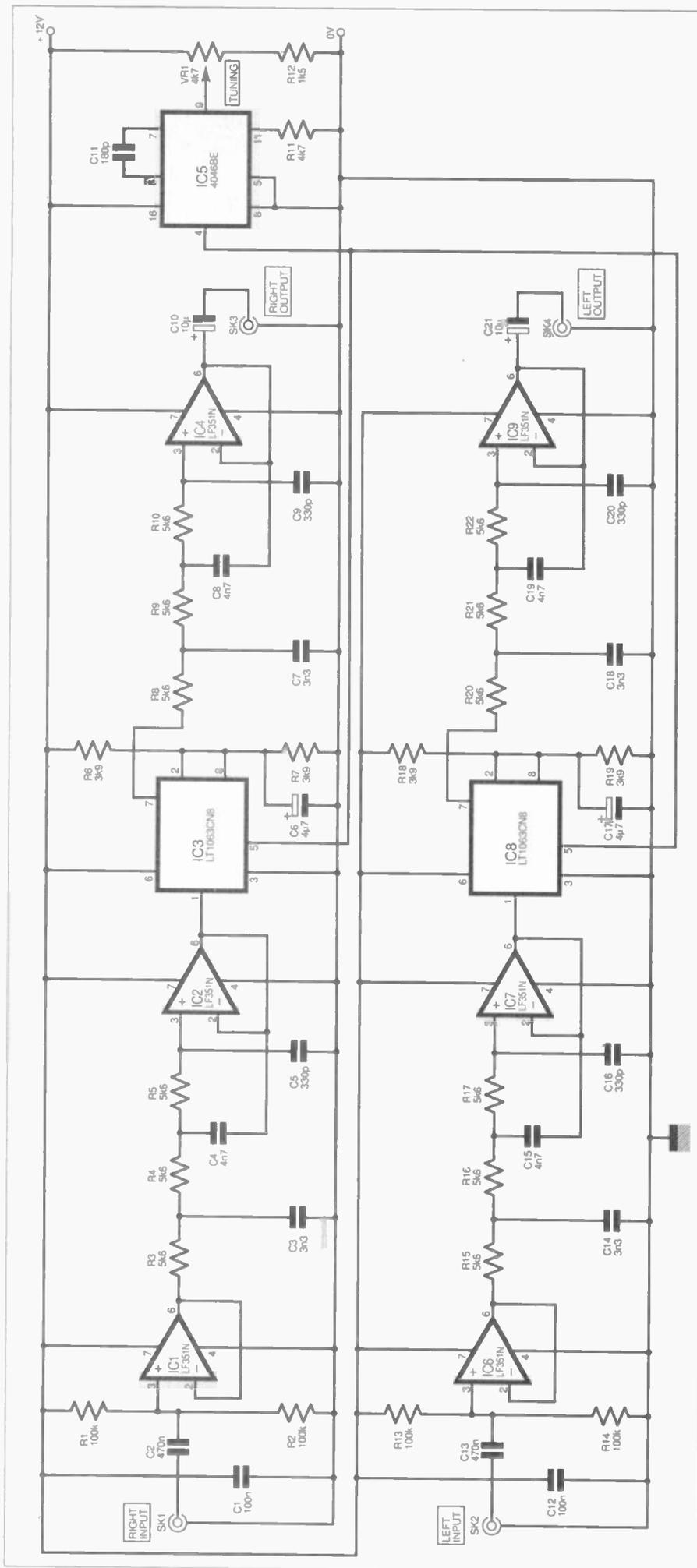


Fig. 3. Main circuit diagram for the Tuneable Scratch Filter.

CIRCUIT DESCRIPTION

The main "active" circuit diagram for the Tuneable Scratch Filter is given in Fig. 3. As the two stereo channels are identical we will only consider operation of the right hand channel. IC1 is used as the input buffer amplifier, and its input impedance is set at 50 kilohms (50k) by bias resistors R1 and R2. It drives a conventional third order (18dB per octave) lowpass filter, formed around IC2, which has a cut-off frequency of about 16kHz.

An LTC1063CN8 switched capacitor filter is used for IC3. Some switched capacitor integrated circuits are state variable filters which can be used in a variety of modes. The LTC1063CN8, without the use of some additional active circuitry, can only operate as a lowpass filter. This limitation is clearly of no importance in this context, where it is a lowpass filter that is needed.

A minimal number of discrete components are required. Apart from the input and output filters and the clock generator, only resistors R6, R7, and electrolytic capacitor C6 are required. These provide a half supply voltage bias to ground (0V) and output voltage adjustment terminals (pins 2 and 8 respectively).

The LTC1063CN8 is primarily designed for use with dual balanced supplies, but it works well when used with a single supply and a bias circuit to effectively provide the central 0V "ground supply." The output voltage adjustment terminal is only needed in d.c. circuits where it enables an output offset voltage to be introduced, or an unwanted offset to be trimmed out. It serves no useful purpose here, and is simply biased to the mid-supply voltage.

Direct coupling is used at the input and output of IC3. In fact the circuit is direct coupled throughout, apart from the input and output coupling capacitors. IC4 is used as the buffer amplifier in the output filter, which is identical to the input filter.

CLOCKING-OUT

The LTC1063CN8 has a built-in clock oscillator that only requires a discrete timing resistor and capacitor. However, the integral clock oscillator is only designed for operation up to about 500kHz. With a maximum cut-off frequency at about 9kHz to 10kHz, and the clock frequency 100 times higher than the cut-off frequency, this application requires a maximum clock frequency of almost 1MHz.

An external clock circuit is therefore used, and it is based on IC5. The latter is a CMOS "micropower" phase-locked loop, but in this circuit only its voltage controlled oscillator (v.c.o.) is used, and no connections are made to the other stages of the device. Capacitor C11 and resistor R11 are the timing components.

Control potentiometer VR1 and resistor R12 provide a variable voltage to the control input of IC5, and VR1 enables the output frequency to be varied from under 300kHz to around 950kHz. The output signal of IC5 is a squarewave signal at normal CMOS levels, which gives good results with the LTC1063CN8.

The approximate frequency response of the Tuneable Scratch Filter, with VR1 set for a -6dB point at 5kHz, is shown in Fig. 4. The Butterworth type response gives minimal losses immediately below


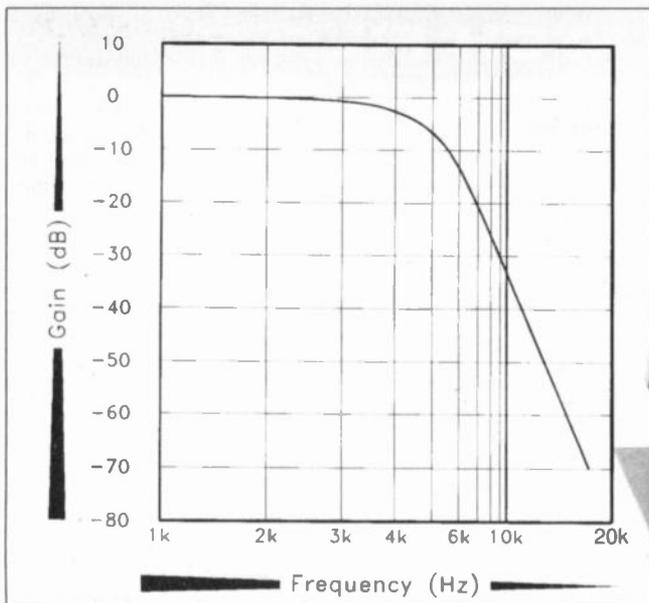


Fig. 4. Approximate frequency response of the Scratch Filter, with VR1 set for a -6dB point at 5kHz .

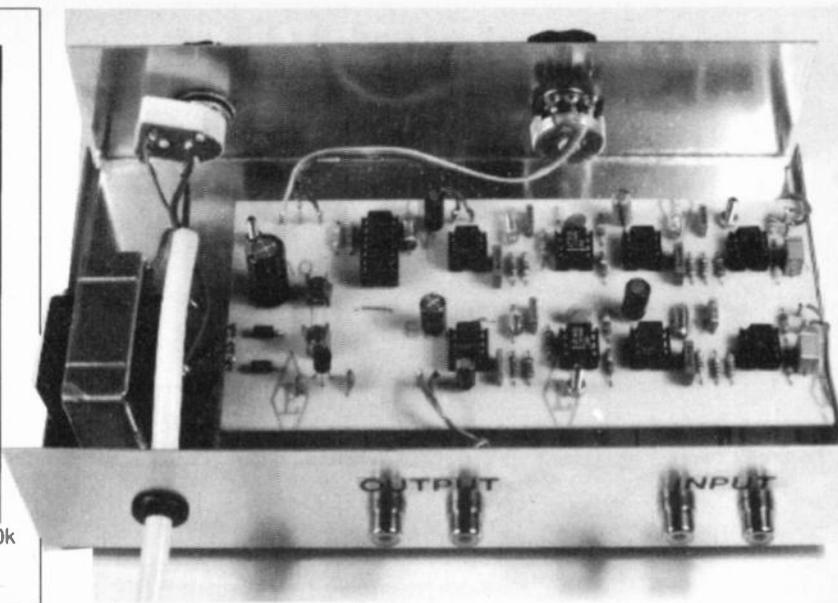

Completed unit showing wiring to the Mains on/off switch and tuning control VR1.

the cut-off frequency, and a rapid introduction of the full roll-off rate. Together with the fairly high attenuation rate of 30dB per octave, this gives excellent results.

POWER SUPPLY

A well smoothed and reasonably stable 12V supply is required. The current consumption of the circuit should be no more than about 60mA , and is typically only about 40mA or so. It is possible to use a fairly high capacity battery as the power source, such as eight HP7 size cells in a holder, but a mains power supply circuit is the more practical choice.

A recommended circuit diagram for the mains power supply appears in Fig. 5. This is a conventional design using full-wave push-pull rectification (T1 and D1/D2) and a small 12V voltage regulator IC10 to stabilise the output voltage and provide electronic smoothing.

On the face of it, a transformer having a current rating of 100mA is adequate for this circuit, but in practice the loaded input voltage to IC10 might be inadequate. A 12V transformer having a 200mA or 250mA current rating provides a more than adequate input voltage to IC10, and a 15V type having a current rating of about 100mA to 166mA is also suitable.

BYPASS SWITCHING

The Tuneable Scratch Filter is designed to handle a high level signal of up to about 2V r.m.s., and it will provide insignificant

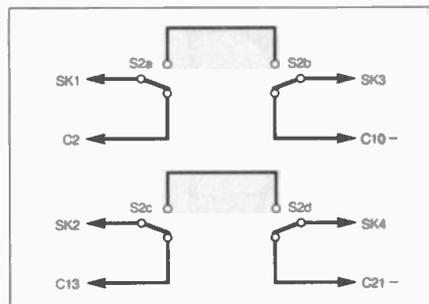


Fig. 6. Built-in bypass switching can be provided by a four-pole changeover switch.

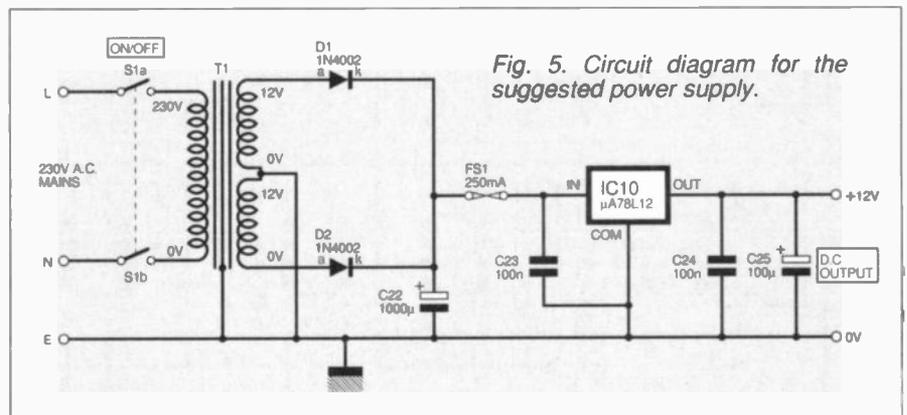



Fig. 5. Circuit diagram for the suggested power supply.

noise and distortion levels when used with a reasonably high signal level. The signal-to-noise ratio will be very poor indeed if it is used between a magnetic cartridge and the preamplifier.

Ideally, the unit should be fitted between the RIAA preamplifier and power amplifier. If you are using a separate preamplifier and power amplifier there should obviously be no difficulty in doing this, and many combined pre/power amplifiers have provision for using external signal processors. Even if there is no facility for external signal processing, in most cases there is a tape monitoring facility that can be pressed into service for this purpose.

In either case, the amplifier's built-in switching should provide a means of bypassing the filter when it is not needed. If the filter is connected between separate pre- and power amplifiers it might be necessary to provide it with built-in bypass switching. This requires a four-pole changeover switch connected in the manner shown in Fig. 6.

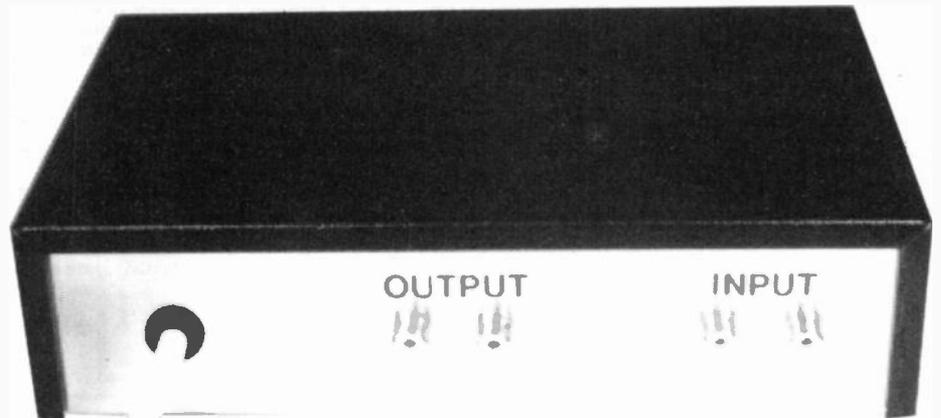Another way of using the unit is to provide it with an integral RIAA preamplifier (see Oct. and Nov. 93 issues for a suitable design), and connect its output to the "Aux" input of the amplifier, or any other spare high level input. The built-in bypass switching will also be needed if this method is utilized.



The input and output phono sockets on the rear panel.

TUNEABLE SCRATCH FILTER


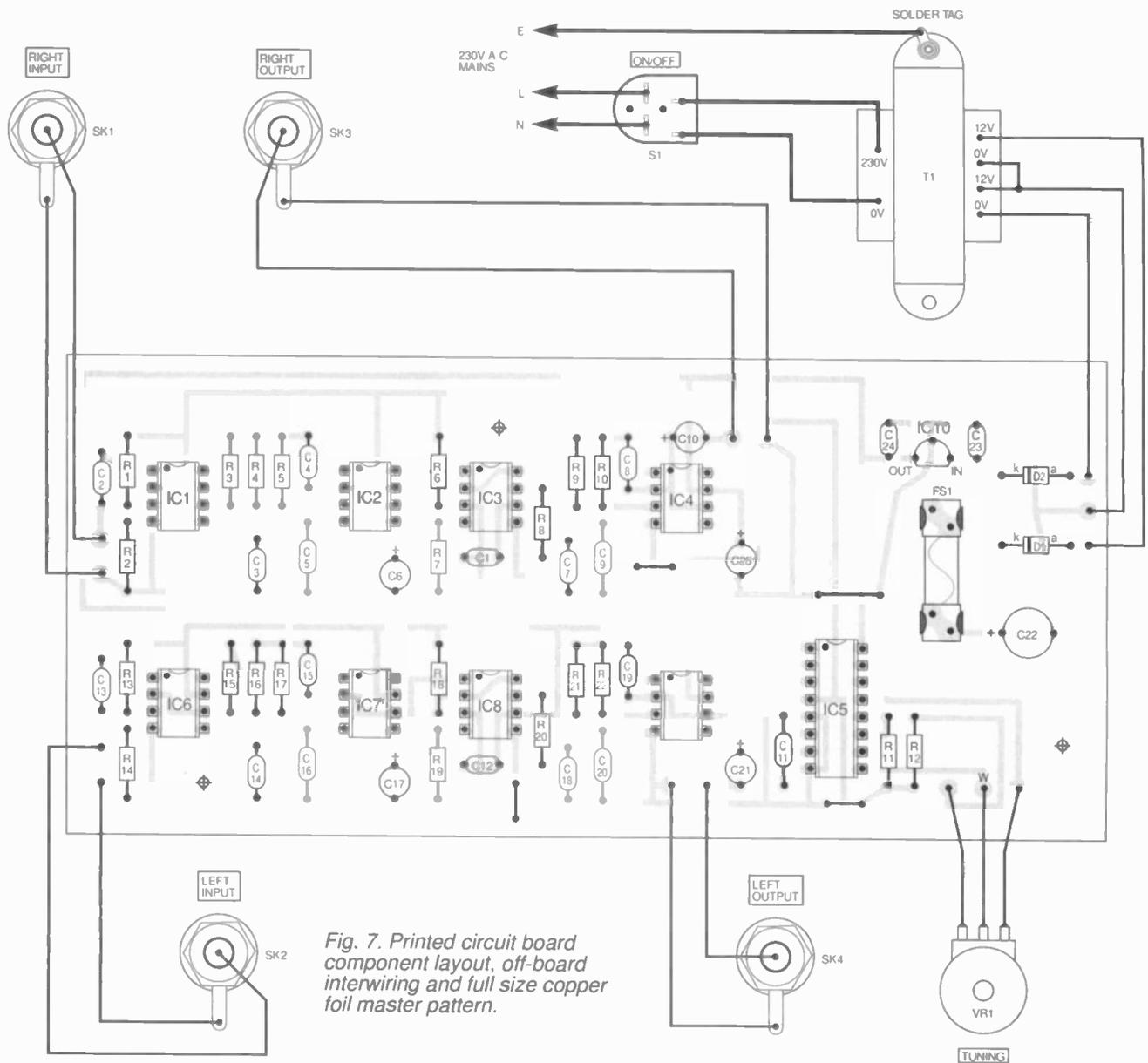


Fig. 7. Printed circuit board component layout, off-board interwiring and full size copper foil master pattern.

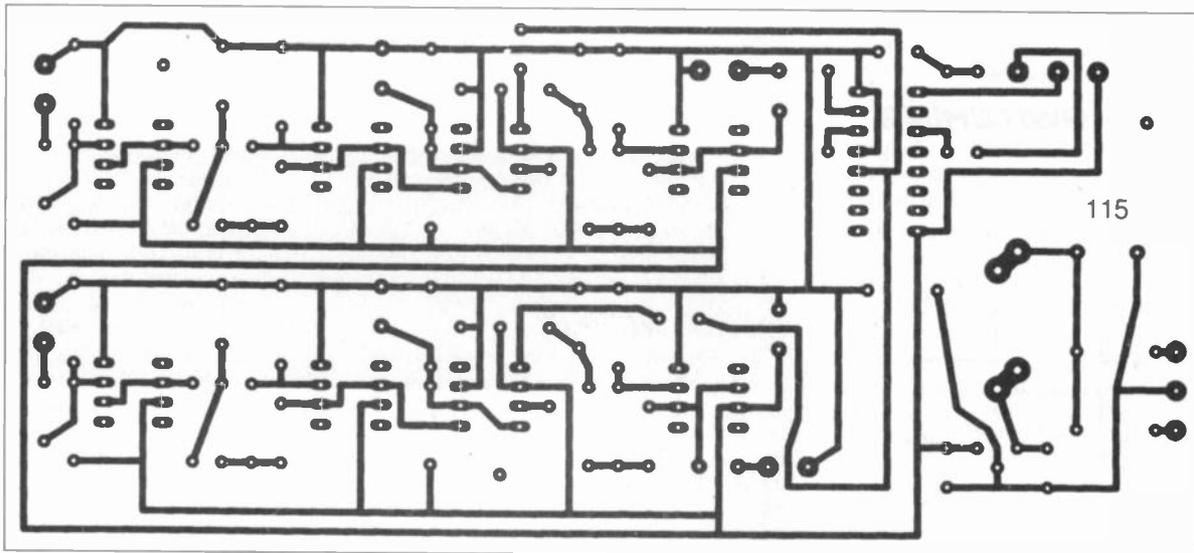

CONSTRUCTION

The topside component layout and actual size copper foil pattern for the Tuneable Scratch Filter printed circuit board (p.c.b.) are shown in Fig. 7. This board is available from the *EPE PCB Service*, code 115.

The 4046BE and LTC1063CN8 are CMOS devices that are static-sensitive. The LTC1063CN8 is also a relatively expensive component. Therefore, the normal anti-static handling precautions must be scrupulously adhered to when dealing with IC3 and IC8. It is advisable to use holders for all the d.i.l. integrated circuits, but they should *definitely* be used for IC3, IC5 and IC8.

Do not fit the i.c.s into their holders until the board and hard wiring have been completed. Until then they should be left in their anti-static packaging, which in the case of IC3 and IC8 will probably be a conductive plastic holder.

When "plugging" the i.c.s into their holders try to handle them no more than is absolutely necessary and, as far as possible, avoid touching the pins. It is obviously important to keep well away from sources of static electricity (televisions, computer monitors, carpets that are prone to generating static discharges, etc.) when fitting the three MOS integrated circuits.

Start construction of the board by fitting single-sided solder pins at the positions where connections to the controls, sockets, etc. will eventually be made. Then fit the integrated circuit holders, the resistors, the capacitors, and the four link-wires. The latter are quite short and can be made from trimmings from the resistor leadouts.

The polyester capacitors should be p.c.b. mounting types having 7.5mm (0.3 in.) lead spacing. It could be difficult to fit other types onto the board properly.

For the same reason the electrolytic capacitors must be miniature p.c.b. mounting components. Be careful to fit them with the right polarity, *especially* C22. This component could literally explode if it is fitted the wrong way round.


Fuse FS1 is mounted on the circuit board via a pair of fuse-clips. To finish the board add voltage regulator IC10 and the two rectifier diodes D1 and D2, being careful to fit the rectifiers with the correct polarity.

The integrated circuits (apart from IC3, IC5 and IC8) can now be fitted into their holders. Once again, be careful to fit these components the right way round.

CASE

Ready-made hi-fi style cases do not seem to be available any more, so a *metal* instrument case is probably the best choice unless you are prepared to take the do-it-yourself approach. As this project is mains powered it is *important* that the case is largely of *metal construction*, and that it is reliably "earthed" to the mains Earth lead. The case must have a screw fitting lid, not a clip-on/clip-off type that would provide easy access to the dangerous mains wiring.

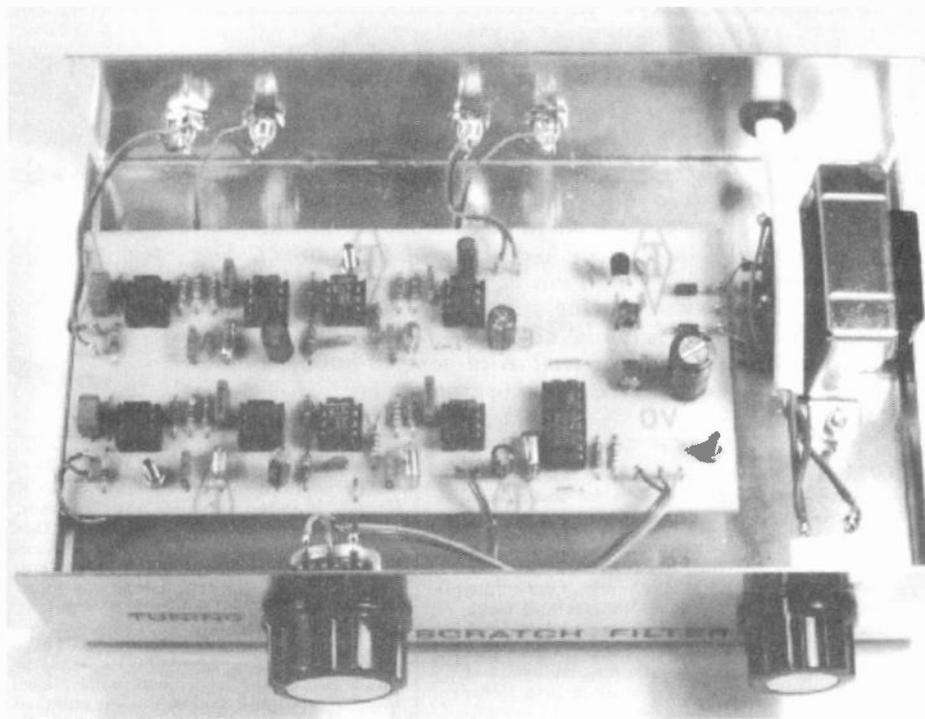The input (SK1/SK2) and output (SK3/SK4) sockets are mounted on the rear panel of the case, with output sockets at roughly the middle of the panel, and the input sockets well towards the left end (as



Completed Scratch Filter showing positioning of p.c.b. and the mains transformer. Use a "strain-relief" type grommet for the mains lead entry.

viewed from the front). Phono sockets are used on the prototype, and these are now by far the most common form of connector on hi-fi equipment. Obviously a different type of connector can be used if it will be a better match for the rest of your hi-fi system.

A hole for the mains lead is made at a position well towards the right end of the rear panel. This hole must be fitted with a grommet to protect the mains cable. Switch S1 is mounted on the front panel, roughly opposite the entrance hole for the mains lead.

Mains transformer T1 is mounted on the base panel of the case, as far to the right as possible. Using the specified case it must be mounted towards the rear of the case so that it does not obstruct one of the fixing screws for the outer casing.

A solder tag is fitted on one of T1's mounting bolts, and this provides a chassis connecting point for the mains Earth lead. Potentiometer VR1 can be mounted anywhere on the large expanse of otherwise unused front panel.

There is just about sufficient space for the component p.c.b. on the base panel of the case to the left of T1. It is mounted using 6BA or metric M3 screws, with spacers being used to hold the board about 12mm clear of the metal base panel. This relatively large stand-off is needed to ensure that the board is kept clear of the second fixing screw for the outer casing.

INTERWIRING

The hard wiring from the printed circuit board to the case-mounted components is also shown in Fig. 7. It is not essential to use screened lead to make the connections from the p.c.b. to VR1 and the sockets, but try to keep this wiring reasonably short. Make sure that the mains earth (E) lead is connected to the solder tag on T1 by way of a strong soldered joint. If the quality of this joint is in any doubt, clean away all the solder and try again.

In Fig. 7, T1 is shown as a type having twin secondary windings, which is the type that most retailers now offer. The two secondary windings are connected in *series* to give what is effectively a centre tapped secondary. If a genuine 12V-0V-12V type is used, the 0V terminal simply connects to the centre pad, and the 12 volt terminals connect to the outer copper pads allocated for the mains transformer.

Switch S1 is a rotary mains switch on the prototype, but it is in order to use any form of double-pole mains switch here. The tag arrangement for other types of switch is almost certain to be different to that shown. If in doubt, check the switch with a continuity tester to determine the correct method of connection.

As this is a mains powered project it is essential to thoroughly check all the wiring before switching on the unit and testing it. Pay particular attention to the wiring around T1 and S1.

IN USE

The Tuneable Scratch Filter is connected to the hi-fi system using ordinary twin-screened phono leads.

The effect of the unit will be very obvious if it is functioning correctly. With front panel control VR1 set for maximum cut-off frequency there is only a small amount of high frequency loss, but with it fully backed-off the loss of high frequency response is massive, and obvious on any programme material.

For most records, results are best with VR1 at a "middle" to "high" setting, but it is really a matter of experimenting a little to find the setting that gives what are judged to be the best results.

Note that a filter of this type is not effective against large scratches. These contain strong signals at relatively low frequencies, which makes it impossible to counteract them using simple filtering. A Scratch Blanker, which works on a totally different principle, is the only effective way of counteracting large scratches.

VIDEOS ON ELECTRONICS

A range of videos designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They have proved particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc.



BASICS

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

VT201 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more.


Order Code VT201

VT202 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits.

Order Code VT202

VT203 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained.

Order Code VT203

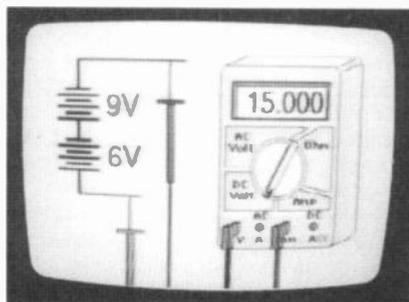

VT204 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply.

Order Code VT204

VT205 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc.

Order Code VT205

VT206 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits.

Order Code VT206

£34.95 each
inc. VAT & postage

Order 8 or more get one extra FREE
Order 16 get two extra FREE

VCR MAINTENANCE

VT102 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output.

Order Code VT102

VT103 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path.

Order Code VT103

DIGITAL

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

VT301 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation.

Order Code VT301

VT302 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc.

Order Code VT302

VT303 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc.

Order Code VT303

VT304 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits.

Order Code VT304

VT305 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices.

Order Code VT305

VT306 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work.

Order Code VT306


RADIO

VT401 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system.

Order Code VT401

VT402 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver.

Order Code VT402

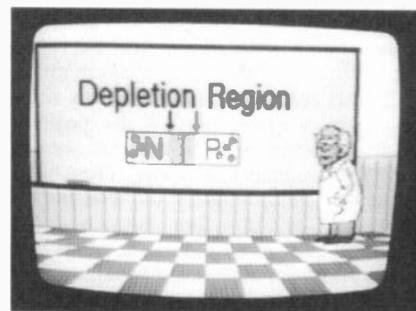

VT403 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding.

Order Code VT403


MISCELLANEOUS

VT501 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers.

Order Code VT501

VT502 57 minutes. Laser Technology A basic introduction covering some of the common uses of laser devices, plus the operation of the Ruby Rod laser, HeNe laser, CO₂ gas laser and semiconductor laser devices. Also covers the basics of CD and bar code scanning.

Order Code VT502

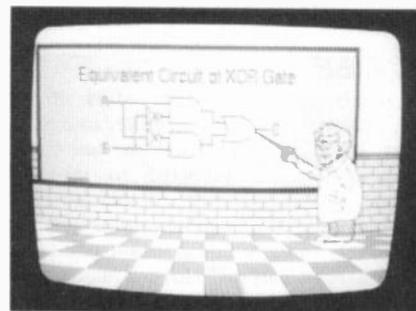

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier. (All videos are to the UK PAL standard on VHS tapes)

ORDERING: Price includes postage to anywhere in the world.

OVERSEAS ORDERS: We use the VAT portion of the price to pay for airmail postage and packing, wherever you live in the world. Just send £34.95 per tape. All payments in £ sterling only (send cheque or money order drawn on a UK bank).

Visa and Mastercard orders accepted - please give card number, card expiry date and cardholder's address if different from the delivery address.

Orders are normally sent within seven days but please allow a maximum of 28 days - longer for overseas orders.

Send your order to: Direct Book Service, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW (Mail Order Only)

Direct Book Service is a division of Wimborne Publishing Ltd.,
Tel: 01202 881749. Fax: 01202 841692

E-mail: editorial@epemag.wimborne.co.uk

£1 BARGAIN PACKS

- List 5

If you would like to receive the other four £1 lists and a lot of other lists, request these when you order or send SAE.

TEST PRODS FOR MULTIMETERS with 4mm sockets. Good length very flexible lead. Ref: D86.
8 OHM PM SPEAKERS, size 8" x 4", pack of two. These may be lightly rusty and that is why they are so cheap but are electrically OK. Ref: D102.
PAXOLIN PANELS, size 6" x 6", approximately 1/16" thick, pack of two. Ref: D103.
13A SOCKET, virtually unbreakable, ideal for trailing lead. Ref: D95.
PIEZO BUZZER with electronic sounder circuit. 3V to 9V D.C. operated. Ref: D76.
DITTO but without internal electronics, pack of two. Ref: D75.
LUMINOUS ROCKER SWITCH, approximately 30mm sq, pack of two. Ref: D64.
ROTARY SWITCH, 9-pole 6-way, small size and 1/4" spindle, pack of two. Ref: D54.
FERRITE RODS, 7" with coils for Long and Medium waves, pack of two. Ref: D52.
DITTO but without the coils, pack of three. Ref: D52.
SLIDE SWITCHES, SPDT, pack of 20. Ref: D50.
MAINS DP ROTARY SWITCH with 1/4" control spindle, pack of five. Ref: D49.
ELECTROLYTIC CAP, 800µF at 6-4V, pack of 20. Ref: D48.
ELECTROLYTIC CAP, 1000µF + 1000µF 12V, pack of 10. Ref: D47.
MINI RELAY with 5V coil, size only 26mm x 19mm x 1mm, has two sets of changeover contacts. Ref: D42.
MAINS SUPPRESSOR CAPS 0.1µF 250V A.C., pack of 10. Ref: 1050.
TELESCOPIC AERIAL, chrome plated, extendable and folds over for improved F.M. reception. Ref: 1051.
MES LAMP HOLDERS, slide on to 1/4" tag, pack of 10. Ref: 1054.
PAXOLIN TUBING, 1/4" internal diameter, pack of two, 12" lengths. Ref: 1056.
ULTRA THIN DRILLS, 0.4mm, pack of 10. Ref: 1042.
20A TOGGLE SWITCHES, centre off, part spring controlled, will stay on when pushed up but will spring back when pushed down, pack of two. Ref: 1043.
HALL EFFECT DEVICES, mounted on small heatsink, pack of two. Ref: 1022.
12V POLARISED RELAY, two changeover contacts. Ref: 1032.
PAXOLIN PANEL, 12" x 12" 1/16" thick. Ref: 1033.
MINI POTTED TRANSFORMER, only 1.5VA 15V-0V-15V or 30V. Ref: 964.
PRE-SET POTS, one megohm, pack of five. Ref: 998.
WHITE PROJECT BOX with rocker switch in top left-hand side, size 78mm x 115mm x 35mm, unpainted. Ref: 1006.
6V SOLENOID, good strong pull but quite small, pack of two. Ref: 1012.
FIGURE-8 MAINS FLEX, also makes good speaker lead, 15m. Ref: 1014.
HIGH CURRENT RELAY, 24V A.C. or 12V D.C., three changeover contacts. Ref: 1016.
LOUDSPEAKER, 8 Ohm 5W, 3-7" round. Ref: 962.
NEON PILOT LIGHTS, oblong for front panel mounting, with internal resistor for normal mains operation, pack of four. Ref: 970.
3.5MM JACK PLUGS, pack of 10. Ref: 975.
WANDER PLUGS, pack of 10. Ref: 986.
PSU, mains operated, two outputs, one 9.5V at 550mA and the other 15V at 150mA. Ref: 988.
ANOTHER PSU, mains operated, output 15V A.C. at 320mA. Ref: 989.
PHOTOCELLS, silicon chip type, pack of four. Ref: 939.
LOUDSPEAKER, 5" 4 Ohm 5W rating. Ref: 946.
230V ROD ELEMENTS, 750W terminal-ended, 10" long, pack of two. Ref: 943.
LOUDSPEAKER, 7" x 5" 4 Ohm 5W. Ref: 949.
LOUDSPEAKER, 4" circular 6 Ohm 3W, pack of 2. Ref: 951.
FERRITE POT CORES, 30mm x 15mm x 25mm, matching pair. Ref: 901.
PAXOLIN PANEL, 8 1/2" x 3 1/2" with electrolytics 250µF and 100µF. Ref: 905.
CAR SOCKET PLUG with P.C.B. compartment. Ref: 917.
FOUR-CORE FLEX suitable for telephone extensions, 10m. Ref: 918.
VERO OFF-CUTS, approximately 30 square inches of useful sizes. Ref: 927.
PROJECT CASE, 95mm x 66mm x 23mm with removable lid, held by four screws, pack of two. Ref: 876.
SOLENOIDS, 12V to 24V, will push or pull, pack of two. Ref: 877.
2M MAINS LEAD, 3-core with instrument plug moulded on. Ref: 879.
TELESCOPIC AERIAL, chrome plated, extendable, pack of two. Ref: 884.
MICROPHONE, dynamic with normal body for hand holding. Ref: 885.
CROCODILE CLIPS, superior quality flex, can be attached without soldering, five each red and black. Ref: 886.
BATTERY CONNECTOR FOR PP3, superior quality, pack of four. Ref: 887.
LIGHTWEIGHT STEREO HEADPHONES. Ref: 898.
PRESETS, 470 Ohm and 220 kilohm, mounted on single panel, pack of 10. Ref: 849.
THERMOSTAT for ovens with 1/4" spindle to take control knob. Ref: 857.
12V-0V-12V 10W ** VINS TRANSFORMER. Ref: 811.
18V-0V-18V 10W MAINS TRANSFORMER. Ref: 813.
AIR-SPACED TRIMMER CAPS, 2pF to 20pF, pack of two. Ref: 818.
AMPLIFIER, 9V or 12V operated Mullard 1153. Ref: 823.
2 CIRCUIT MICROSWITCHES, icon, pack of 4. Ref: 825.
LARGE SIZE MICROSWITCHES (20mm x 6mm x 10mm) changeover contacts, pack of two. Ref: 826.
MAINS VOLTAGE PUSH SWITCH with white dolly, through panel mounting by hexagonal nut. Ref: 829.
POINTER KNOB for spindle which is just under 1/4", like most thermostats. pack of four. Ref: 833.

TOROIDAL MAINS TRANSFORMERS



All with 220/240V primary winding. 0-6V + 0-6V at 50VA would give you 6V at 8A or 12V at 4A, price **£5**, Order Ref: 5PG1.
 0-30V + 0-30V at 120VA would give you 30V at 4A or 60V at 2A, price **£8**, Order Ref: 8PG2. 0-110V + 0-110V at 120VA would give you 110V at just over 8A or 220V at 1/2A, price **£8**, Order Ref: 8PG3. 0-35V + 0-35V at 150VA would give you 35V at 4A or 70V at 2A. Price **£8**. Oder Ref: 8PG9. 0-35V + 0-35V at 220VA would give you 35V at 6 1/2A or 70V at 3 1/4A, price **£9**, Order Ref: 9PG4. 0-110V + 0-110V at 220VA would give you 110V at 2A or 220V at 1A, price **£10**, Order Ref: 10PG5. 0-45V + 0-45V at 500VA would give you 45V at 11A or 90V at 5 1/2A, price **£20**, Order Ref: 20PG7. 0-110 + 0-110V at 500VA would give you 110V at 5A or 220V at nearly 3A, price **£25**, Order Ref: 25PG7.

REMOTE CONTROL

REMOTE CONTROL from as far as 100ft is what the Shepherd RCA100 unit is capable of. It comes packaged and with instructions for use as a vehicle security system. This has a 20W siren which would shriek directly the car is tampered with but the special feature is that this system can be switched on and switched off up to 100 feet away giving you good control. You can get well away from it before you switch it on and similarly when you want to get into the car yourself you can switch it off.

Other uses If instead of the 20W horn speaker you use a relay, you could use this remote control to operate other devices.

In the packet you have full instructions, 2 keychain remote units, the main module with wire harness to connect to an aerial (could be a car aerial), a lamp (could be one of the parking lights) and a fan, the 20W power unit and last but not least, the shock sensor, once disturbed will sound off the siren. Price for the complete unit is **£30**, Order Ref: 30P14.

SMART HIGH QUALITY ELECTRONIC KITS

All kits are complete with PCB and other components in a blister pack. Smart catalogue, this gives full details and circuit diagrams of each kit, price is **£1**, deductible if you order kits to the value of **£20**.

CAT. No.	DESCRIPTION	PRICE £	CAT. No.	DESCRIPTION	PRICE £
1002	VU Meter, with l.e.d. display	4.60	1062	5V 0-5A Stabilized Supply for TTL	2.30
1003	5W Electronic Siren	2.53	1063	12V 2A Power Supply	2.30
1004	Light Switch	3.22	1064	+ 12V 0-5A Stabilized Supply	3.22
1005	Touch Switch	2.87	1067	Stereo VU Meter, with l.e.d.s	9.20
1007	Stabilized Power Supply: 3V to 30V at 2-5A	6.90	1068	18V 0-5A Stabilized Power Supply	2.53
1008	SF Function Generator	6.90	1069	Fluorescent Tube Unit from 12V d.c.	2.99
1010	5-input Stereo Mixer, with monitor output	19.31	1070	HiFi Pre-amplifier	7.47
1011	Motorbike Alarm	3.20	1071	4-input Selector	6.90
1012	Reverberation Unit	5.52	1074	Drill Speed Controller	2.76
1016	Loudspeaker Protection Unit	3.22	1077	100W HiFi Amplifier	12.50
1023	Dynamic head preamp	2.50	1080	Liquid Level Sensor - Rain Alarm	2.30
1024	Microphone preamp	2.20	1082	Car Voltmeter, with l.e.d.s	7.36
1025	7W HiFi Power Amplifier	2.53	1083	Video Signal Amplifier	2.76
1026	Running Lights	4.60	1084	TV Line Amplifier	1.84
1027	NiCad Battery Charger	3.91	1085	DC Converter, 12V to 6V or 7-5V or 9V	2.53
1029	4 sound electronic siren	3.00	1086	Music to light for your car	4.60
1030	Light Dimmer	2.53	1087	Thyristor/Triac Tester	2.76
1032	Stereo Tone Control	4.14	1088	Kitt Scanner	10.12
1035	Space Sound Effects	2.30	1089	LED Flasher/555 Tester	1.61
1038	AM/FM Aerial Amplifier	1.61	1090	Stress Meter	3.22
1039	Stereo VU Meter	4.60	1093	Windscreen Wiper Controller	3.68
1040	10W HiFi Power Amplifier	2.76	1094	Home Alarm System	12.42
1041	25W HiFi Power Amplifier	4.60	1098	Digital Thermometer, with l.c.d. display	11.50
1042	AF Generator, 250Hz-16kHz	1.70	1100	2 x 18W Integrated Amplifier	18.39
1043	Loudness Stereo Unit	3.22	1103	LED Power Meter	1.84
1047	Sound Switch	5.29	1106	Thermometer with l.e.d.s	6.90
1048	Electronic Thermostat	3.68	1107	Electronics to help win the pools	3.68
1050	3-input HiFi Stereo Pre-amplifier	12.42	1109	40W HiFi Amplifier	7.36
1051	Touch Dimmer, with memory	4.60	1112	Loudspeaker protection, with delay	4.60
1052	3-input Mono Mixer	6.21	1113	2 x 18W Power Amplifier	5.98
1053	Electronic Metronome	3.22	1115	Courtesy Light Delay	2.07
1054	4-input Instrument Mixer	2.76	1118	Time Switch with triac 0-10mins	4.14
1056	8V-20V 8A Stabilized Power Supply	12.42	1123	Morse Code Generator	1.84
1057	Cassette Head Pre-amplifier	3.22	1124	Electronic Bell	2.76
1058	Electronic Car Ignition	7.82	1125	Telephone Lock	3.68
1059	Telephone Amplifier	4.60	1126	Microphone Pre-amplifier	4.60
1060	+ 40V 8A Power Supply	8.28	1127	Microphone Tone Control	4.60
			1128a	Power Flasher 12V d.c.	2.53
			1130	Telephone Bug Detector	3.20
			1133	Stereo Sound-to-Light	5.26

YOU SAVE £40



THE JAP MADE 12V 15AH SEALED LEAD ACID BATTERY from regular suppliers costs £50, you can have one from us for only £10 including VAT if you collect or £12.50 if we have to send. Being sealed it can be used in any position and is maintenance free. All in tip top condition and fully guaranteed, Order Ref: 12.5P2. Or if you want a smaller one we have 12V 2.3AH, regular price £14, yours for only £5, Order Ref: 5P258.

Prices include VAT and carriage if order over £25 otherwise add £3. Send cash, uncrossed postal orders, cheque or quote credit card number.

J & N FACTORS

Pilgrim Works (Dept. E.E.)
 Stairbridge Lane, Bolney,
 Sussex RH17 5PA

Telephone: 01444 881965
 (Also fax but phone first)

DIRECT BOOK SERVICE

INTRODUCING MICROPROCESSORS

Mike Tooley B.A. (published by *Everyday Practical Electronics*)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

Sections cover Microcomputer Systems, Microprocessors, Memories, Input/Output, Interfacing and Programming. There are various practical assignments and eight Data Pages covering popular microprocessors.

And excellent introduction to the subject even for those who do not wish to take the City and Guilds assessment. 80 pages **Order code TI-88/89** £2.45

ELECTRONICS TEACH-IN No. 6

DESIGN YOUR OWN CIRCUITS

(published by *Everyday Practical Electronics*)

Mike Tooley B.A.

This book is designed for the beginner and experienced reader alike, and aims to dispel some of the mystique associated with the design of electronic circuits. It shows how even the relative newcomer to electronics can, with the right approach, design and realise quite complex circuits.

Fourteen individual p.c.b. modules are described which, with various detailed modifications, should allow anyone to design and construct a very wide range of different projects. Nine "hands-on" complete DIY projects have also been included so readers can follow the thinking behind design, assembly, construction, testing and evaluation, together with suggested "mods" to meet individual needs.

The subjects covered in each chapter of the book are: Introduction and Power Supplies; Small Signal Amplifiers; Power Amplifiers; Oscillators; Logic Circuits; Timers; Radio; Power Control; Optoelectronics.

The nine complete constructional projects are: Versatile Bench Power Supply; Simple Intercom; Bench Amplifier/Signal Tracer; Waveform Generator; Electronic Die; Pulse Generator; Radio Receiver; Disco Lights Controller; Optical Communications Link. 136 pages **Order code TI6** £3.45

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book page.

FOR ANOTHER SELECTION OF BOOKS SEE NEXT MONTH'S ISSUE.

Note our UK postage costs just £1.50 no matter how many books you order!

TEACH-IN No. 7. plus FREE SOFTWARE ANALOGUE AND DIGITAL ELECTRONICS COURSE

(published by *Everyday Practical Electronics*)

Alan Winstanley and Keith Dye B.Eng(Tech)AMIEE

This highly acclaimed *EPE Teach-In series*, which included the construction and use of the *Mini Lab* and *Micro Lab* test and development units, has been put together in book form. Additionally, EPT Educational Software have developed a GCSE Electronics software program to complement the course and a FREE DISK covering the first two parts of the course is included with the book.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The *Mini Lab* and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and

interesting way: you will both see and hear the electron in action! The *Micro Lab* microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.

160 pages

Order code TI7

£3.95

ELECTRONIC PROJECTS BOOK 1

(published by *Everyday Practical Electronics* in association with *Magenta Electronics*)

Contains twenty projects from previous issues of *EE* each backed with a kit of components. The projects are: Seashell Sea Synthesizer, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three-Channel Sound to Light, BBC 16K sideways RAM, Simple Short Wave Radio, Insulation Tester, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser, Ioniser, Bat Detector, Acoustic Probe, Meinstester and Fuse Finder, Light Rider - (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator. 128 pages **Order code EP1** £2.45



PROJECT CONSTRUCTION

TEST EQUIPMENT CONSTRUCTION

R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:-

AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe.

The designs are suitable for both newcomers and more experienced hobbyists.

104 pages

Order code BP248

£3.99

A BEGINNER'S GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold

The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronic theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor.

166 pages

Order code BP285

£3.95

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books, and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.

80 pages

Order code BP121

£2.50

AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

The purpose of this book is to provide the reader with a wide range of preamplifier and power amplifier designs that will, it is hoped, cover most normal requirements.

The preamplifier circuits include low noise microphone and RIAA types, a tape head preamplifier, a guitar preamplifier and various tone controls. The power amplifier designs range from low power battery operation to 100W MOSFET types and also include a 12 volt bridge amplifier capable of giving up to 15W output.

All the circuits are relatively easy to construct using the p.c.b. or stripboard designs given. Where necessary any setting-up procedures are described, but in most cases no setting-up or test gear is required in order to successfully complete the project.

100 pages

Temporarily out of print

DESIGN YOUR OWN CIRCUITS

See ELECTRONICS TEACH-IN No. 6 above left.

RADIO / TV / VIDEO

ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS

R. A. Penfold

This book provides a number of practical designs for video accessories that will help you get the best results from your camcorder and VCR. All the projects use inexpensive components that are readily available, and they are easy to construct. Full construction details are provided, including stripboard layouts and wiring diagrams. Where appropriate, simple setting up procedures are described in detail; no test equipment is needed.

The projects covered in this book include: Four channel audio mixer, Four channel stereo mixer, Dynamic noise limiter (DNL), Automatic audio fader, Video faders, Video wipers, Video crispener, Mains power supply unit.

109 pages

Order code BP356

£4.95

SETTING UP AN AMATEUR RADIO STATION

I. D. Poole

The aim of this book is to give guidance on the decisions which have to be made when setting up any amateur radio or short wave listening station. Often the experience which is needed is learned by one's mistakes, however, this can be expensive. To help overcome this, guidance is given on many aspects of setting up and running an efficient station. It then proceeds to the steps that need to be taken in gaining a full transmitting licence.

Topics covered include: The equipment that is needed; Setting up the shack; Which aeriels to use; Methods of construction; Preparing for the licence.

An essential addition to the library of all those taking their first steps in amateur radio. 86 pages **Order code BP300** £3.95

EXPERIMENTAL ANTENNA TOPICS

H. C. Wright

Although nearly a century has passed since Marconi's first demonstration of radio communication, there is still research and experiment to be carried out in the field of antenna design and behaviour.

The aim of the experimenter will be to make a measurement or confirm a principle, and this can be done with relatively fragile, short-life apparatus. Because of this, devices described in this book make liberal use of cardboard, cooking foil, plastic bottles, cat food tins, etc. These materials are, in general, cheap to obtain and easily worked with simple tools, encouraging the trial-and-error philosophy which leads to innovation and discovery.

Although primarily a practical book with text closely supported by diagrams, some formulae which can be used by straightforward substitution and some simple graphs have also been included.

72 pages

Order code BP278

£3.50

25 SIMPLE INDOOR AND WINDOW AERIALS

E. M. Noll

Many people live in flats and apartments or other types of accommodation where outdoor aeriels are prohibited, or a lack of garden space etc. prevents aeriels from being erected. This does not mean you have to forgo shortwave listening, for even a 20-foot length of wire stretched out along the skirting board of a room can produce acceptable results. However, with some additional effort and experimentation one may well be able to improve performance further.

This concise book tells the story, and shows the reader how to construct and use 25 indoor and window aeriels that the author has proven to be sure performers.

Much information is also given on shortwave bands, aerial directivity, time zones, dimensions etc. 50 pages **Order code BP136** £1.75

CIRCUITS AND DESIGN

PRACTICAL ELECTRONIC CONTROL PROJECTS

Owen Bishop

Explains electronic control theory in simple, non-mathematical terms and is illustrated by 30 practical designs suitable for the student or hobbyist to build. Shows how to use sensors as input to the control system, and how to provide output to lamps, heaters, solenoids, relays and motors.

Computer based control is explained by practical examples that can be run on a PC. For stand-alone systems, the projects use microcontrollers, such as the inexpensive and easy-to-use Stamp BASIC microcontroller. These projects are chosen to introduce and demonstrate as many aspects as possible of the programming language and techniques.

198 pages

Order code BP377

£5.99

COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages

Order code 160

£3.95

PRACTICAL ELECTRONICS HANDBOOK - Fourth Edition. Ian Sinclair

Contains all of the everyday information that anyone working in electronics will need.

It provides a practical and comprehensive collection of circuits, rules of thumb and design data for professional engineers, students and enthusiasts, and therefore enough background to allow the understanding and development of a range of basic circuits.

Contents: Passive components, Active discrete components, Discrete component circuits, Sensing components, Linear I.C.s, Digital I.C.s, Microprocessors and microprocessor systems, Transferring digital data, Digital-analogue conversions, Computer aids in electronics, Hardware components and practical work, Standard metric wire table, Bibliography, The HEX scale, Index.

440 pages

Order code NE21

£12.99

AUDIO IC CIRCUITS MANUAL

R. M. Marston

A vast range of audio and audio-associated i.c.s are readily available for use by amateur and professional design engineers and technicians. This manual is a guide to the most popular and useful of these devices, with over 240 diagrams. It deals with i.c.s such as low frequency linear amplifiers, dual pre-amplifiers, audio power amplifiers, charge coupled device delay lines, bar-graph display drivers, and power supply regulators, and shows how to use these devices in circuits ranging from simple signal conditioners and filters to complex graphic equalizers, stereo amplifier systems, and echo/reverb delay lines etc.

168 pages

Order code NE13

£13.95

50 CIRCUITS USING GERMANIUM, SILICON AND ZENER DIODES

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most simple and inexpensive of components - the diode. Includes the use of germanium and silicon signal diodes, silicon rectifier diodes and Zener diodes, etc.

64 pages

Order code BP36

£1.95

A BEGINNERS GUIDE TO CMOS DIGITAL ICs

R. A. Penfold

Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.


The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and other logic "building blocks"; CMOS logic i.c. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

The emphasis is on a practical treatment of the subject, and all the circuits are based on "real" CMOS devices. A number of the circuits demonstrate the use of CMOS logic i.c.s in practical applications.

119 pages

Order code BP333

£4.95

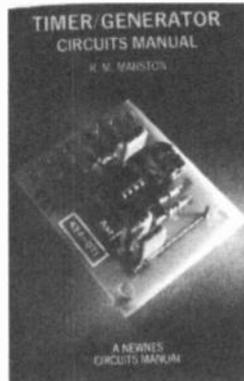

TIMER/GENERATOR CIRCUITS MANUAL

R. M. Marston

This manual is concerned mainly with waveform generator techniques and circuits. Waveform generators are used somewhere or other in most types of electronic equipment, and thus form one of the most widely used classes of circuit. They may be designed to produce outputs with sine, square, triangle, ramp, pulse, staircase, or a variety of other forms. The generators may produce modulated or unmodulated outputs, and the

outputs may be of single or multiple form.

Waveform generator circuits may be built using transistors, op.amps, standard digital i.c.s, or dedicated waveform or "function" generator i.c.s.

The manual is divided into eleven chapters, and presents over 300 practical circuits, diagrams and tables. The subjects covered include: Basic principles; Sine wave generators; Square wave generators; Pulse generator circuits; "Timer i.c." generator circuits; Triangle and sawtooth generators; Multi-waveform generation; Waveform synthesizer i.c.s; Special waveform generators; Phaselocked loop circuits; Miscellaneous "555" circuits.

267 pages

Order code NE18

£13.95

OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston

A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the i.c.s and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages

Order code NE14

£13.95

OPERATIONAL AMPLIFIER USER'S HANDBOOK

R. A. Penfold

The first part of this book covers standard operational amplifier based "building blocks" (integrator, precision rectifier, function generator, amplifiers, etc), and considers the ways in which modern devices can be used to give superior performance in each one. The second part describes a number of practical circuits that exploit modern operational amplifiers, such as high slew-rate, ultra low noise, and low input offset devices. The projects include: Low noise tape preamplifier, low noise RIAA preamplifier, audio power amplifiers, d.c. power controllers, opto-isolator audio link, audio millivolt meter, temperature monitor, low distortion audio signal generator, simple video fader, and many more.

120 pages

Order code BP335

£4.95

AUDIO AND MUSIC

INTRODUCTION TO DIGITAL AUDIO

(Second Edition)

Ian Sinclair

Digital recording methods have existed for many years and have become familiar to the professional recording engineer, but the compact disc (CD) was the first device to bring audio methods into the home. The next step is the appearance of digital audio tape (DAT) equipment.

All this development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages

Order code PC102

£7.95

Along with the electric guitar, sections are also included relating to acoustic instruments. The function of specialised piezoelectric pickups is explained and there are detailed instructions on how to make your own contact and bridge transducers. The projects range from simple preamps and tone boosters, to complete active controls and equaliser units.

92 pages

Order code BP358

£4.95

AUDIO

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Analysis of the sound wave and an explanation of acoustic quantities prepare the way. These are followed by a study of the mechanism of hearing and examination of the various sounds we hear. A look at room acoustics with a subsequent chapter on microphones and loudspeakers then sets the scene for the main chapter on audio systems - amplifiers, oscillators, disc and magnetic recording and electronic music.

320 pages

Temporarily out of print

MIDI SURVIVAL GUIDE

Vic Lennard

Whether you're a beginner or a seasoned pro, the MIDI Survival Guide shows you the way. No maths, no MIDI theory, just practical advice on starting up, setting up and ending up with a working MIDI system.

Over 40 cabling diagrams. Connect synths, sound modules, sequencers, drum machines and multitracks. How to budget and buy secondhand. Using switch, thru and merge boxes. Transfer songs between different sequencers. Get the best out of General MIDI. Understand MIDI implementation charts. No MIDI theory.

104 pages

Order code PC111

£6.95

PRACTICAL ELECTRONIC MUSICAL EFFECTS UNITS

R. A. Penfold

This book provides practical circuits for a number of electronic musical effects units. All can be built at relatively low cost, and use standard, readily available components. The projects covered include: Waa-Waa Units; Distortion Units; Phaser; Guitar Envelope Shaper; Compressor; Tremolo Unit; Metal Effects Unit; Bass and Treble Boosters; Graphic Equaliser; Parametric Equaliser. The projects cover a range of complexities, but most are well within the capabilities of the average electronics hobbyist. None of them require the use of test equipment and several are suitable for near beginners.

102 pages

Order code BP368

£4.95

LOUDSPEAKERS FOR MUSICIANS

Vivan Capel

This book contains all that a working musician needs to know about loudspeakers; the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, when and where to use wadding, and when not to, what fittings are available, finishing, how to ensure they travel well, how to connect multi-speaker arrays and much more.

Ten practical enclosure designs with plans and comments are given in the last chapter, but by the time you've read that far you should be able to design your own!

164 pages

Order code BP297

£3.95

DIRECT BOOK SERVICE ORDERING DETAILS

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Our postage price is the same no matter how many books you order, just add £1.50 to your total order for postage and packing (overseas readers add £3 for countries in the EEC, or add £6 for all countries outside the EEC, surface mail postage) and send a PO, cheque, international money order (£ sterling only) made payable to Direct Book Service or credit card details (including card expiry date), Visa or Mastercard - minimum credit card order is £5 - quoting your name and address, the order code and quantities required to DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET BH21 1RW (mail order only).

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.


For a further selection of books see next month's issue.

DIRECT BOOK SERVICE IS A DIVISION OF WIMBORNE PUBLISHING LTD.

Tel 01202 881749 Fax 01202 841692

E-mail:editorial@epemag.wimborne.co.uk

LEARN ALL ABOUT ELECTRONICS

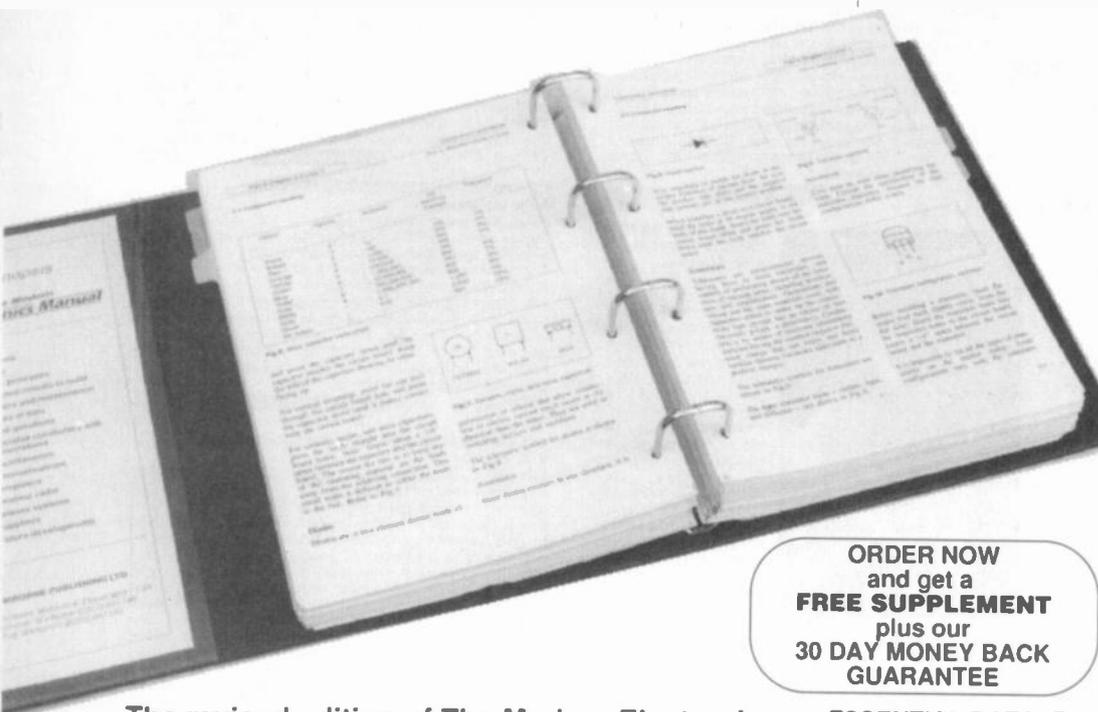

The essential reference work

- Easy-to-use format
- Clear and simple layout
- Comprehensive subject range
- Regular Supplements
- Sturdy ring-binder
- Projects to build
- Components checklists
- Extensive data tables
- Detailed supply information
- Ready-to-transfer PCBs
- Detailed assembly instructions
- Professionally written

ORDER NOW and get a **FREE SUPPLEMENT** plus our **30 DAY MONEY BACK GUARANTEE**

The revised edition of **The Modern Electronics Base Manual** contains practical, easy-to-follow information on the following subjects:

BASIC PRINCIPLES: Symbols, components and their characteristics, active and passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, analogue electronics, physics for electronics.

CIRCUITS TO BUILD: From basic principles to circuit-building, The Modern Electronics Manual and its Supplements describe how to assemble radios, loudspeakers, amplifiers, car projects, computer interfaces, measuring instruments, workshop equipment, security systems, etc.

Guarantee

Our 30 day money back guarantee gives you complete peace of mind. If you are not entirely happy with the Manual, for whatever reason, simply return it to us in good condition within 30 days and we will make a full refund of your payment - no small print and no questions asked.

(Overseas buyers do have to pay the postage charge)

ESSENTIAL DATA: Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors.

The Manual also has an extensive Glossary, and covers **Safety, Specialist Vocabulary with Abbreviations and Suppliers.** The most comprehensive reference work ever produced at a price you can afford, the revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the essential information you need.

OVER 1,000 A4 loose leaf pages in a sturdy ring binder all for just £39.95 plus £5.50 post and packing. Regular Supplements continuously extend the Manual with new material, each Supplement contains approximately 160 pages of information. These are sent about five times a year and cost £23.50 plus £2.50 p&p. You can of course return any Supplement (within 10 days) or cancel the Supplements at any time.

Wimborne Publishing Ltd., Dept. Y11
Allen House, East Borough,
Wimborne,
Dorset BH21 1PF
Tel: 01202 881749 Fax: 01202 841692

PLEASE send me **THE MODERN ELECTRONICS MANUAL** plus a **FREE SUPPLEMENT.**

I enclose payment of **£45.45**. I shall also receive the appropriate supplements several times a year. These are billed separately and can be discontinued at any time. Should I decide not to keep the Manual I will return it to you within 30 days for a full refund.

ORDER FORM

Simply complete and return the order form with your payment to the following address:
**Wimborne Publishing Ltd, Dept. Y11
Allen House, East Borough, Wimborne,
Dorset BH21 1PF**

FULL NAME
(PLEASE PRINT)

ADDRESS.....

..... POSTCODE

SIGNATURE.....

I enclose cheque/PO payable to Wimborne Publishing Ltd.

Please charge my Visa/Mastercard/Access

Card No. Card Ex. Date

OVERSEAS ORDERS: All overseas orders must be prepaid and are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the Manual return it within a month for a refund of the purchase price (you do have to pay the overseas postage). SEND **£39.95 PLUS THE POSTAGE SHOWN BELOW:**

EIRE, SCOTTISH HIGHLANDS and UK ISLANDS	£11
EUROPE (E.E.C. Countries)	AIR MAIL ONLY £20
EUROPE (non E.E.C.)	SURFACE MAIL £20, AIR MAIL £26
U.S.A. & CANADA	SURFACE MAIL £25, AIR MAIL £32
FAR EAST & AUSTRALIA	SURFACE MAIL £31, AIR MAIL £33
REST OF WORLD	SURFACE MAIL £25, AIR MAIL £44


Note surface mail can take over 10 weeks to some parts of the world. Each manual weighs about 4kg including the free supplement when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.

ec24

CIRCUIT SURGERY

ALAN WINSTANLEY

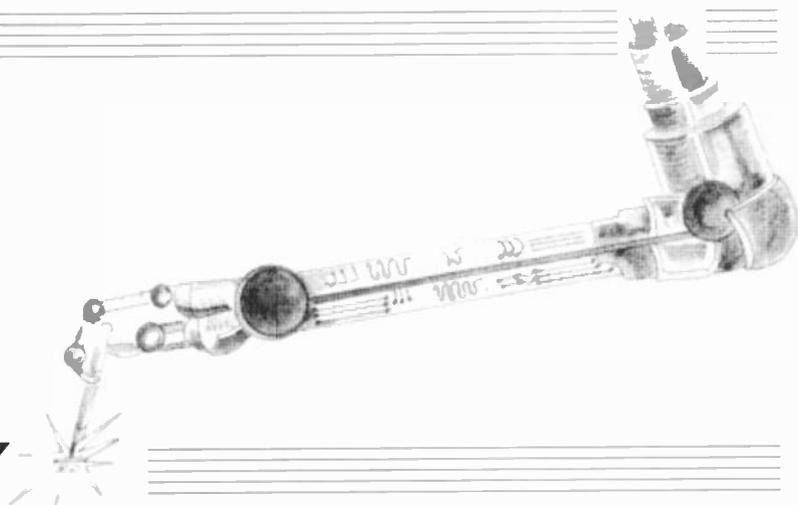

This month our resident surgeon investigates a faulty project, flashing l.e.d.s, hole storage noise and some useful battery tips.

Too Hot

WE sometimes receive calls for help from constructors who might be experiencing problems with constructional projects. Extensive care is taken to ensure that all published information is accurate, and it is extremely rare for errors to creep into a project article. We try to help as much as possible though we don't guarantee that we can assist with projects over five years old: parts become obsolete, suppliers disappear, and technology moves on, making it occasionally not at all worthwhile trying to diagnose the ills of such a project.

Simpler projects using discrete components generally have a good lifespan, though. If things go wrong, and the project doesn't quite operate as expected, there is often a very simple reason for the failure and – most importantly – I'm keen to stress that things *do* go wrong from time to time, as part and parcel of electronic construction, but you shouldn't let this deter you.

Fault-finding and troubleshooting are all part of the deal when you become involved in electronics. For instance, *M. Neill* of Formby High School, Liverpool asks:

I would be grateful for your help in solving a problem with the Vehicle Voltage Monitor project (February 1991 issue). When I use the circuit, both transistors and both resistors get extremely hot! I changed the resistors for higher power versions and I changed TR1 and TR2 for TIP31A and TIP32A power types, too. I made the circuit with a p.c.b. instead of the suggested stripboard – I hope you can help find a solution.

The circuit in question is shown in Fig. 1. In my experience, transistors are easily the main source of problems in circuits such as this. It's easy to connect them incorrectly by identifying the leads wrongly, or even by accidentally inserting the wrong device altogether.

In the *Voltage Monitor* circuit, the two transistors are simply driving or shunting light-emitting diodes. If the l.e.d.s were shorted out, for example, the fact that each transistor has a 220 ohm resistor in its load says that the maximum current which

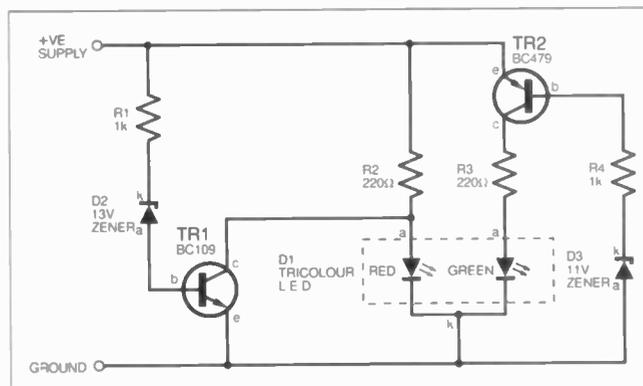


Fig. 1. Circuit of the Voltage Monitor project from Feb. '91.

could flow through each transistor as collector current would be $(12/220) = 50\text{mA}$. Note that it's not necessary to be accurate, we're only looking for clues as to what to expect in this circuit, so that we can check things further.

This means that the resistors would be dissipating, say, 0.6 watts (12×0.05) or so, and indeed the designer specified 0.6W resistors in the published parts list, so I would expect the resistors to become quite warm to the touch. It could be that you're using ordinary 0.25W resistors instead, which will become hot in use.

It's a bit odd, though, if the transistors become hot, and there should definitely be no need to change them for the power transistors mentioned. How do I know? By doing a few rule of thumb calculations, you can glean a few more clues as to what's going on: the transistors, in use, are acting as switches. This means that when they are switched hard on (saturated), there is only a small voltage drop between their emitter and collector terminals. Now, the power dissipated by a transistor is calculated by multiplying this voltage drop by the current flowing through it. The result is a power dissipation, in watts.

In this circuit, only a rough calculation is needed to tell you that there's something wrong somewhere. Take the case of the *pnp* transistor TR1. If TR1 is switched on, then the green l.e.d. will be glowing and TR2 will be saturated. I would expect (rule of thumb time) to see no more than perhaps 0.2V to 0.4V or so across the

transistor's collector/emitter. With 50mA flowing through the l.e.d., this means that the transistor will dissipate no more than $0.4\text{V} \times 50\text{mA} = 0.02\text{W}$ or 20mW.

A TIP31A power transistor is good for no less than 40 watts! So it would be reasonable, Mr. Neill, to expect that neither transistor became at all warm because they dissipate so little. Weighing it up, I would only guess that the transistors have been incorrectly connected, especially if you departed from the published design and built the project on a home-made p.c. board.

In general terms, if readers do have cause to contact us concerning a problem with a project, please write to us providing as much relevant information as you can, including test readings where possible. We will do our best to help you get up and running – and, best of all, the service is free!

Flashy!

A quick note from *Mark McGuinness* of Clondalkin, Ireland concerning the use of flashing l.e.d.s. Mark says:

I've found that a flashing l.e.d., of the type containing an internal flasher i.c., can be used to pulse other non-flashing, standard l.e.d.s. connected in series. Small relays can also be pulsed on and off when connected in series with the flashing l.e.d.

Just to illustrate the point, this month's *Ingenuity Unlimited* features a simple project which Mark designed to test light emitting diodes.

Hole Storage Noise

If you ever see capacitors surrounding a bridge rectifier, you might wonder what they're for. It's to combat hole storage noise which may be generated by the semiconductor junctions. **Mr. B.J. Taylor** confirms the score:

In June 96 Circuit Surgery (Page 477) you mentioned rectifier diode noise. You were correct that the effect is called hole storage noise but this doesn't get mentioned much these days. I have known the effect give problems on FM tuners where it appeared as modulation buzz. But it seems very rare to encounter it these days, probably because of the routine use of voltage regulators, and their ability to eliminate nearly all noise on the supply. I had a noise problem with a couple of 15W valve amplifiers which was only eventually eliminated by wiring 10nF 800V a.c. capacitors across the rectifiers.

I'm seeing more of this form of filtering, typically 10 to 220nF capacitors placed in parallel with each rectifier diode. In some commercial equipment I've also seen a 220nF polyester capacitor placed across a transformer secondary, also to combat noise.

Challenge

Finally this month, from a regular reader – and we chat on the Internet from time to time – thanks to **Mr. Walter Gray** who presents us all with a challenge! Walter writes:-

Here's a simple 9V (PP3-style) Ni-Cad Discharger: three green l.e.d.s. in series with a 68 ohm resistor for current limiting. Safe if left overnight because the final discharge rate is only about 50 microamps or less!

And a simple PP3 battery tester – a 180 ohm and an 82 ohm resistor in series, with

a red l.e.d. connected across the 82 ohms. Draws 40mA from a fresh battery – useful!

I have built both of these on the back of 9V battery snaps and encapsulated them with hot glue. Perhaps you should start a "How many parts can you get onto a battery snap competition!"

See you next month for a further round-up of readers' questions and comments.

At your service

Circuit Surgery is your page. If you have any questions to ask or comments to make, please write to Alan Winstanley, *Circuit Surgery*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset, BH21 1PF. E-mail alan@epemag.demon.co.uk

We cannot guarantee an individual reply nor undertake to answer questions on commercial equipment but we do try to help wherever possible.

Ohm Sweet Ohm

Max Fidling

Mystique

Each and every year the Boss decides our holiday destination and gives me my marching orders. It's a pretty simple arrangement, really – all I have to do is drive and pay for everything!

One slight handicap exists, though, in the form of our faithful old caravan. Since there's hardly any free-standing area left at *Fidling Acres*, the caravan is stored at a nearby farm, for a nominal yearly rent, and one of my chores involves checking out the old *Vin Blanc* every now and then, and doing the honours with repairs.

Not being one to spend money if I can at least avoid it, I'd worked the previous weekend rummaging through the shack looking for some heavy duty wire and crimp connectors, of the sort used on vehicle's electrical systems. Car electrics are something which have a mystique all of their own, and ever since I installed a pair of foglights which only came on with the indicators, the Boss looked upon my motoring maintenance with a wary eye. Most unfair, given my reputation as a member of the electronics elite!

Anyway, I cycled over to the farm and was greeted by the sight of my caravan, having survived another over-wintering in the company of an old combine harvester, and shored up on wooden blocks looking somewhat sorry for itself. A couple of hours work fitting the wheels back on (always useful things to have on caravans – they make the car go faster), sprucing up with a bucket of water from the farm tap, and *Vin Blanc* was soon feeling happier, I sensed, as I whistled a tune and scrubbed away at the polycarbonate windows with a sponge till they glistened.

Back to the crimp connectors and the wire. The previous camping holiday had had added excitement in that the indicators mounted on the rear of the caravan, didn't always work properly. Maybe it was a bad earth or something.

It was possible to give an approximate idea of one's intentions to following motorists, by carefully juggling a combination of the brakes, indicator and headlamp switch – though this did nothing to help any hapless motorists following me but it made life in the car more interesting, as the Boss tended to get nervous if ever the indicators flashed left but I turned right instead or vice versa.

Plundered

So for our next adventure holiday to a nearby caravan site (ten miles away, quicker by bike), I'd designed a way of monitoring the indicators of the caravan so that I would know when they were actually working (if at all). I'd plundered the idea from a magazine project, my usual source of inspiration for my madcap ideas, and had eventually arrived at a contraption which needed plumbing into the indicator wiring.

It would buzz in the car when the caravan's indicators sprang into life. Apparently similar things are needed by law anyway, a point lost on yours truly in these halcyon days of holiday making.

The scheme was to tap into the caravan's indicators somehow, and run the cable back to the new bleeper project which I'd fitted in the boot. After ferreting around in the caravan for some considerable time, removing furniture and fittings which never quite go back the same way, I'd fitted the wiring in the rather dingy-smelling caravan, and I left the windows open to let some fresh air in as I cycled back home to the shack, dinner and the cat.

The day quickly arrived when, fully loaded with suitcases, holiday gear and cat food, the Boss, myself and Piddles the cat boarded this spectacle and headed down the road at 40 miles an hour in search of the caravan site. The moggie hates travelling, but I'd long ago abandoned the idea of using a travel basket since he made the



most insufferable noise whenever I put him in it! Hence he was on the back seat on the tartan rug, when we came upon the first roundabout (a fine feat of British road engineering if ever there was one). The indicators were duly switched on as I aimed for the third exit, and the buzzer beeped in the boot like a good un. Even the Boss seemed happy so far!

Catcophony

The caravan lurched as we turned off en route for the holiday camp – the trouble was, although I cancelled the indicators, the buzzer kept buzzing! I twiddled the indicator stalk to and fro but it made no difference!

I could see a tailback of about a dozen cars behind me, and there was nowhere to pull in! *Trouble!* Piddles ears pricked up at the sound of this angry buzzing noise (either that or he was about to be car sick) and he started wailing too!

Desperately, I clicked all the lighting switches, fan, radio – you name it – but still the buzzer kept beeping! What a commotion! Believe me, readers, you haven't lived till you've driven ten miles at forty m.p.h. towing a caravan, with a beeping buzzer, a tailback of traffic, an irate Boss and a wailing cat being ill in the back. Thank heavens for tartan rugs!

PCB SERVICE

Printed circuit boards for certain EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749; Fax 01202 841692 (NOTE, we cannot reply to orders or queries by Fax); E-mail: editorial@epemag.wimborne.co.uk**. Cheques should be crossed and made payable to *Everyday Practical Electronics (Payment in £ sterling only)*.

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required – see the Back Issues page for details.

Please check price and availability in the latest issue.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Multi-Purpose Thermostat MAR'95	931	£6.30
Multi-Project PCB	932	£3.00
Sound-Activated Switch		
Audio Amplifier		
Light Beam Communicator (2 boards required)		
Multi-Project PCB APR'95	932	£3.00
Light-Activated Switch		
Switch On/Off Timer		
Continuity Tester		
Auto Battery Charger	934	£5.36
National Lottery Predictor	935	£5.34
R.F. Signal Generator - R.F./Mod. MAY'95	936	£6.48
Coil & Power Supply (pair)	937a/b	£6.10
MIDI Pedal	938	£7.78
Club Vote Totaliser	939	£6.05
PIC-DATS Development System (double-sided p.t.h.)	940	£9.90
EPE HiFi Valve Amplifier – Phase splitter JUNE'95	941	£6.71
PIC-DATS 4 -channel Light Chaser	942	£7.90
HV Capacitor Reformer JULY'95	943	£5.60
Ramp Generator		
Logic Board (double-sided p.t.h.) & Analogue board (pair)	944/5	£32.00
Automatic Curtain Winder	946	£6.75
Windicator	947	£4.10
Microcontrolled 3-Digit Timer AUG'95	933	£6.61
IR Remote Control – Transmitter	948	£5.76
Receiver	949	£6.14
Personal Practice Amplifier	950	£6.09
Low-Range Ohmmeter Adaptor SEPT'95	926	£5.55
Simple Theremin	952	£6.68
Vandata		
Boot Control Unit	953	£10.52
Display Unit	954	£6.61
Sound Switch OCT'95	915	£6.55
Multiple Project PCB	932	£3.00
Audio Sinewave Generator		
Treble Booster		
Infra-Red Controller/Alarm (2 boards required)		
Capacitor Check	955	£5.76
Ginormous VU Meter	956	£9.31
Multiple Project PCB NOV'95	932	£3.00
Video Enhancer – Current Tracer – Distortion Effects Unit		
Digital Delay Line	958	£8.04
50Hz Field Meter	959	£8.32
Temperature Warning Alarm (Teach-In '96)	960	£6.15
Stereo "Cordless" Headphones DEC'95		
Transmitter	961	£8.04
Receiver	962	£7.66
EPE Met Office – Sensor/Rainfall/Vane	963/965	£11.33
Spiral transparency free with above p.c.b.		
Light-Operated Switch	966	£6.37
Modular Alarm System (Teach-In '96)	967a/b	£7.12
Audio Meter and Amplifier	968	£5.99
EPE Met Office – Computer Interface (double-sided) JAN'96	964	£7.69
Audio Signal Generator	969	£6.58
Mains Signalling Unit, Transmitter and Receiver	970/971 (pr)	£9.09
Automatic Camera Panning (Teach-In '96)	972	£6.63
Printer Sharer	973	£9.93
Analogue Frequency Meter FEB'96	957	£6.70
Vari-Speed Dice (Teach-In '96)	974	£5.69
Mains Signalling Unit – 2		
12V Capacitive PSU	975	£6.07
PIC-Electric Meter – Sensor/PSU – Control/Display	977/978 (pr)	£9.90
Multi-Purpose Mini Amplifier MAR'96	976	£6.12
PIC-Electric – Sensor/PSU – Control/Display	977/978 (pr)	£9.90
High Current Stabilised Power Supply	979	£6.62
Mind Machine Mk III – Sound and Lights	980	£7.39
Infra-Zapper Transmitter/Receiver (Teach-In '96)	981/982 (pr)	£8.01

PROJECT TITLE	Order Code	Cost
Mind Machine Mk III – Programmer APRIL'96	983	£7.36
Bat Band Converter/B.F.O.	984a/b	£5.80
Hearing Tester	985	£6.87
Event Counter (Teach-In '96)	986	£8.39
B.F.O. and Bat Band Converter MAY'96	984a/b	£5.80
Versatile PIR Detector Alarm	988	£6.76
Mind machine Mk III – Tape Controller	989	£6.70
Midi Analyser	992	£6.74
Countdown Timer (Teach-In '96)	993	£9.44
Sarah's Light JUNE'96	996	£7.17
Home Telephone Link	997 (pr)	£10.72
PulStar	998	£6.60
VU Display and Alarm	999	£7.02
Ultra-Fast Frequency Generator JULY'96		
and Counter – Oscillator/L.C.D. Driver	994/995 (pr)	£12.72
Timed NiCad Charger	100	£6.99
Single-Station Radio 4 Tuner	101	£7.02
Twin-Beam Infra-Red Alarm – Transmitter/Receiver	102/103 (pr)	£10.50
Games Compendium	104	£6.09
Mono "Cordless" Headphones AUG'96		
– Transmitter/Receiver	990/991 (pr)	£10.16
Component Analyser (double sided p.t.h.)	105	£12.18
Garden Mole-Ester	106	£6.07
Mobile Miser	107	£6.36
Bike Speedo	108	£6.61
PIC-Tock Pendulum Clock SEPT'96	109	£6.31
Power Check	110	£6.42
Analogue Delay/Flanger	111	£7.95
Draught Detector	112	£6.22
Simple Exposure Timer	113	£6.63
Video Fade-to-White OCT'96	114	£6.98
Direct Conversion 80m Receiver	116	£7.52
Vehicle Alert	117	£6.55
10MHz Function Generator		
– Main Board	118	£7.33
– PSU	119	£5.39
Tuneable Scratch Filter NOV'96	115	£7.83
Central Heating Controller	120	£7.85
EPE Elysian Theremin	121	£22.00
D.C. to D.C. Converters		
– Negative Supply Generator	122	£5.96
– Step-Down Regulator	123	£6.01
– Step-Up Regulator	124	£6.12

EPE SOFTWARE

Software programs for the following EPE projects (PIC-microcontrolled except for Met Office and Central Heating Controller) are available altogether on a single 3.5 inch PC-compatible disk, or as needed, via our Internet site: Met Office (Dec '95) – GWBasic; Simple PIC16C84 Programmer (Feb '96); PIC-Electric Meter (Feb '96); PulStar (June '96); Games Compendium (July '96); PIC-Tock Pendulum Clock (Sept '96); PIC Disassembler (unpublished); Central Heating Controller (Nov '96) – 8051 machine code.

The disk (order as "PIC-Disk") is available from the *EPE PCB Service* at £2.50 (UK) to cover our admin costs (the software itself is free). Overseas £3.10 surface mail, £4.10 airmail.

Alternatively, the software files can be downloaded free from our Internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>

EPE PRINTED CIRCUIT BOARD SERVICE


Order Code	Project	Quantity	Price																				
.....																				
Name.....																							
Address.....																							
.....																							
I enclose payment of £..... (cheque/PO in £ sterling only) to:																							
																							
Everyday Practical Electronics																							
Access (MasterCard) or Visa No.																							
Minimum order for credit cards £5																							
<table border="1" style="width: 100%; height: 20px;"> <tr> <td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td> </tr> </table>																							
Signature..... Card Exp. Date.....																							
Please supply name and address of cardholder if different from the address shown																							



SURFING THE INTERNET

NET WORK

ALAN WINSTANLEY

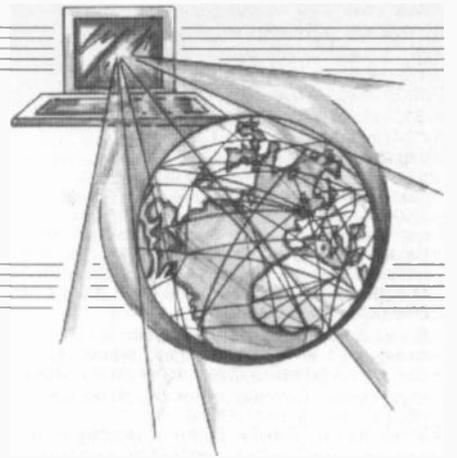

WE hope you will take the time to visit the *EPE* World Wide Web site, the URL of which is <http://www.epemag.wimborne.co.uk> – the first electronics magazine in the UK to open a WWW page. Having been active on the Internet for two years, you can expect us to lead the way once again by adding new online services to our WWW pages in due course, telling you everything you need to know about us (we hope) and adding a further dimension to help you enjoy *Everyday Practical Electronics* even more! Also remember our FTP site which holds PIC files and more, at <ftp://ftp.epemag.wimborne.co.uk>

Secure Transactions

This month *Net Work* highlights a few projects which are destined for our WWW site. In particular, we're working on implementing Secure Electronic Transactions (SET) via the Web. Several readers have enquired about the facility of ordering on-line, though it's a complex matter which is causing a few global headaches at the moment.

We're not alone in this respect as security issues are involved, since the object is to offer a facility for web site readers to place an order safely on-line quoting credit card numbers, via security encryption systems which are being implemented on our server. A useful fill-in form will be available on screen, and readers will be able to select back issues, or take out a subscription, type in their details and the order will be processed swiftly and securely.

If you're interested in SET then look at <http://www.visa.com> – and <http://www.mastercard.com> – for the current specs. (Remember that all the URL's in this column are also made on the on-line version of *Net Work*, so all you need to do is browse, point and click – no need to type in those clumsy addresses! Furthermore, you can easily access the URL's from previous issues since these will be archived on the same *Net Work* page.)

You might often stumble across what are called – mailto: forms on the World Wide Web, where you fill in a selection of dialogue boxes, click radio buttons and generally make a selection from an on-screen page. The simplest implementation of this function simply sends the result of your input as a straight E-mail message to <whoever>@<wherever>. The problem is that this doesn't work with *Microsoft Internet Explorer* (MSIE) or, say, *AIR Mosaic* browsers, but it does work with *Netscape Navigator*.

Even though *Netscape* currently commands some 85 per cent of the global browser market, having some 38 million users, the safest and most reliable route from our point of view is to use a *cgi* (Common Gateway Interface) script which resides on our server and absorbs your input to the on-screen form. Regardless of what type of browser you use, this script or mini program will ensure that your instructions are received here safely and intact by the server, ready for processing by the *EPE* staff. Coupled with our ultimate aim of Secure Electronic Transactions, this will add a whole new dimension to the services we offer our readers.

On-site Feedback

Also on the web site, we're adding readers' feedback to the site by publishing an on-line version of Readout called *Dear EPE*, a selection of readers letters (both E-mail and snail mail). This fits in perfectly with our view that the WWW site should be an adjunct to the printed magazine, but will never replace it.

The *Printed Circuit Board Service*, suppliers' advertisements, the *Direct Book Service*, and – most importantly – our comprehensive *Back Issues Service* – will all eventually find their way onto the web site too. Such ambitious projects take time, though, but you can expect the site to develop nicely over the

coming months. The HTML is written in-house and we hope you'll let us know the kind of things you'd like to see there. After all, it's your web site too!

Browser Battles

The web world is in for a stormy battle over the next twelve months. *Netscape Navigator*, being the most popular web browser on the planet, is set to meet an intense challenge from Microsoft who want the world to adopt their *Internet Explorer* (MSIE) browser instead. The latter is found in Windows 95 and is now being adopted by Demon Internet Services Ltd. as well as the likes of CompuServe, AOL and Netcom as their browser.

At the time of writing, events at Demon are quite interesting. Demon, the UK's largest ISP purchased the Internet access software company Turnpike (<http://www.turnpike.com>) some time ago, whose product has been reviewed in this magazine several times. Turnpike includes a licensed copy of *Netscape Navigator 1.22*, which is adequate for those who only access the web occasionally and don't mind missing out a few features (animated graphics, frames etc.) but most enthusiasts upgrade to *Netscape 2.0* or *3.0*.

Turnpike V3.0 (32-bit) in beta phase was promised to include *Netscape Navigator 3.0* as the new browser. In a sharp and embarrassing about-turn, Turnpike have suddenly shelved plans to ship *Navigator* and will instead be offering *Microsoft Internet Explorer 3.0* as their preferred browser, to the intense annoyance of an audience of expectant Turnpike users who fear they're being fobbed off with less than the real thing. Not surprisingly, Demon Internet have been chosen by Microsoft to serve out *Explorer* from their FTP site, in the UK. The impression is one of Turnpike having their own ideas, but Demon calling the shots.

At the end of the day, you pay your money (MSIE is free) and take your choice. In general, you can look forward to a chaotic scene of new releases, add-ons, and leap-frog moves as Microsoft attempts to gain the upper hand over *Netscape* to dominate the global browser market. One inside source guesses that *Explorer* will indeed displace *Navigator* within two years, leaving the latter confined to the fringes, e.g. Macintosh users. On future releases of the Windows GUI, there will also be a move towards browser-style screens away from the familiar *desktops* you see on PCs today. If you thought that the push for Windows 95 was tough enough, you've seen nothing yet!

New Links

Just time for some of the links I've spotted which may be of interest to electronics enthusiasts. Users of Hexfets (International Rectifier's name for their MOSFETs) will find a lot of information on them on the IR web pages at <http://www.irf.com>. Look for **tech info/design tips/application notes**. Probably the best and most comprehensive list of web sites for semiconductor manufacturers can always be found at <http://www.scruznet.com/~gcraeger/hello5.htm>. This is generously maintained by Gray Creager, a Xicor applications engineer. CE Standards Engineers might check the Standards FAQ at http://world.std.com/~techbook/standards_faq.html. Tandy (known as Radio Shack in the USA) have a site that contains some useful data on their products, at <http://www.tandy.com>. A provider of electronics kits, DIY Electronics' can be found on <http://www.hk.super.net/~diykit>.

Join me for more *Net Work* next month. See you soon on our web pages!

DC TO DC CONVERTERS

DRM58 input 10-40vdc output 5v 8A £15
 DRM128 input 17-40vdc output 12v 8A £50
 DRM158 input 20-40vdc output 15v 8A £50
 DRM248 input 29-40vdc output 24v 8A £40
 DRS123 input 17-40vdc output 12v 3A £20
 DRS153 input 20-40vdc output 15v 3A £20
 DRS243 input 29-40vdc output 24v 3A £15

SOLID STATE RELAYS

CMP-DC-200P 3-32vdc operation, 0-200vdc 1A £2.50
 SMT2000/3 3-24vdc operation, 28-280vac 3A £4.50
 SMT2000/4 3-24vdc operation, 28-280vac 4A £5.00
 ZRA6025F 28-280vac operation, 28-280vac 25A £7.00

200 WATT INVERTERS Nicely cased units 12v input 240v output 150watt continuous, 200 max. £49 ref LOT62

6.8MW HELIUM NEON LASERS New units, £65 ref LOT33
COINSLIT TOKENS You may have a use for these? mixed bag of 100 tokens £10 ref LOT20

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £65/set. Ref F/KP1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £45/set Ref F/TKE1.

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set. Ref F/EH2.

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means- cause it to levitate. £10/set Ref F/GRA1.

WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, "Plasma in a jar", St Elmo's fire, Corona, excellent science project or conversation piece. £5/set Ref F/BTC1/LG5

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/set Ref F/CVL1.

VOICE SCRAMBLER PLANS Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £65/set Ref F/V59

PULSED TV JOKER PLANS Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound works on FM too! DISCRETION ADVISED. £85/set Ref F/JT5.

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £85/set Ref F/BHT1.

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc. £125/set Ref F/LC7.

MYSTERY ANTI GRAVITY DEVICE PLANS Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £65/set Ref F/ANT1K.

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £65/set Ref F/ULB1.

ULTRA HIGH GAIN AMP/STETHOSCOPIC MIKE/SOUND AND VIBRATION DETECTOR PLANS Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £65/set Ref F/HGA7.

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £65/set Ref F/DOG2.

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £125/set Ref F/LLIST1.

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 Ref F/LLS1.

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £65/set Ref F/PSP4.

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL 01902 22039

Interference. Detects low, high and UHF frequencies. £55/set Ref F/BD1.

ELECTROMAGNETIC GUN PLANS Projects a metal object a considerable distance- requires adult supervision. £5 ref F/EM2.

ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £55/set Ref F/EM1.

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £85/set Ref F/PM5.

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 Ref F/A-TVM7/TCL4.

INFINITY TRANSMITTERS The ultimate 'bug' fits to any phone or line, undetectable, listen to the conversations in the room from anywhere in the world! 24 hours a day 7 days a week! just call the number and press a button on the mini controller (supplied) and you can hear everything! Monitor conversations for as long as you choose £249 each, complete with leads and mini controller! Ref LOT9. Undetectable with normal RF detectors, fitted in seconds, no batteries required, lasts forever!

SWITCHED MODE PSU'S 244 watt, +5 32A, +12 6A, -5 0 2A, -12 0 2A. There is also an optional 3.3v 25A rail available. 120/240v I/P. Cased, 175x90x145mm. IEC Inlet Suitable for PC use (6/d/drive connectors 1 mboard). £10 ref PSU1.

VIDEO PROCESSOR UNITS/76v 10AH BATT/12V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2 x 6v 10AH sealed lead acid batts, pcb's and a 8A7 12v toroidal transformer (mains in). Condition not known, may have one or two broken knobs due to poor storage. £17 50 ref VP2.

RETRO NIGHT SIGHT Recognition of a standing man at 300m in 1/4 moonlight, hermetically sealed, runs on 2 AA batteries, 80mm F1.5 lens, 20mw Infrared laser included. £325 ref RETRON.

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 Mhz but easily changed to cover 63-130 Mhz. Works with a common 9v (PP3) battery. 0.2W RF. £7 Ref 1001.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 Ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £12 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob your self but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM. Built in 5 watt amplifier, inc speaker. £15 ref 1013.

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200w power handling, microphone included. £14 Ref 1014.

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3 RF stages, microphone and audio preamp included. £20 Ref 1028.

STROBE LIGHT KIT Adjustable from 1-60 Hz (a lot faster than conventional strobes). Mains operated. £16 Ref 1037.

COMBINATION LOCK KIT 9key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £10 ref 1114.

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £6 ref 1130.

ROBOT VOICE KIT Interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! 12vdc £9 ref 1131.

TELEPHONE BUG KIT Small bug powered by the 'phone line, starts transmitting as soon as the phone is picked up! £8 Ref 1135.

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction controls supplied with 12 LEDs (you can fit tracs instead to make kit mains, not supplied) 9-12vdc £17 ref 1026.

12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2a transformer also required. £8 ref 1069.

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recorders etc. adjustable sensitivity. £8 ref 1073.



Check out our
WEB SITE

<http://www.pavilion.co.uk/bull-electrical>

PREAMP MIXER KIT 3 input mono mixer, sep bass and treble controls plus individual level controls, 18vdc, input sens 100mA. £15 ref 1052.

*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.

BN3 5QT. (ESTABLISHED 50 YEARS).
 MAIL ORDER TERMS: CASH, PO OR CHEQUE
 WITH ORDER PLUS £3 P&P PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY/PHONE ORDERS WELCOME (ACCESS, VISA, SWITCH, AMERICAN EXPRESS).

TEL: 01273 203500
 FAX 01273 323077
 E-mail bull@pavilion.co.uk

SOUND EFFECTS GENERATOR KIT Produces sounds ranging from bird chips to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045.

15 WATT FM TRANSMITTER (BUILT) 4 stage high power, preamp required 12-18vdc, can use ground plane, yaqi or open dipole. £69 ref 1021.

HUMIDITY METER KIT Builds into a precision LCD humidity meter, 9lc design, pcb, lcd display and all components included. £29

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1, 640k, serial port, hard drive with min 100k free. £24.99

FM CORELESS MICROPHONE This unit is an FM broadcasting station in miniature. 3 transistor transmitter with electret condenser mic+fetamp design results in maximum sensitivity and broad frequency response. 90-105mhz, 50-1500hz, 500 foot range in open country! PP3 battery required. £15.00 ref 15P42A.

MAGNETIC MARBLES They have been around for a number of years but still give rise to curiosity and amazement. A pack of 12 is just £3.99 ref G/R20.

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £39.99 ref NIK39.

Miniature adjustable timers, 4 pole o/o output 3A 240v, HY1230S, 12VDC adjustable from 0-30 secs. £4.99

HY1260M, 12VDC adjustable from 0-60 mins. £4.99

HY2405S, 240v adjustable from 0-5 secs. £4.99

HY24060m, 240v adjustable from 0-60 mins. £6.99

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9.

9v DC POWER SUPPLY Standard plug in type 150ma 9v DC with lead and DC power plug. price for two is £2.99 ref AUG3P4.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors, 1 mother board connector, 150watt, 12v fan, iec inlet and on/off switch. £12 Ref EF6.

VENUS FLY TRAP KIT Grow your own carnivorous plant with this simple kit. £3 ref EF34.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13. Ideal for experimenters! 30m for £12.99 ref MAG13P1.

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together believed to cause rain! £3 a pair REF EF29.

3' by 1' AMORPHOUS SOLAR PANELS 14.5v 700mA 10 watts, aluminium frame, screw terminals. £44.95 ref MAG45.

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needles! good to experiment with. £7 ref 7P30.

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £7 ref 7P36.

FLYING PARROTS Easily assembled kit that builds a parrot that actually flaps its wings and flies! 50 m range. £6 ref EF2.

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 miles per hour! Range of over 200 metres! £7.99 ref R/9.

BALLOON MANUFACTURING KIT British made, small blob blows into 4 large, longlasting balloons, hours of fun! £3.99 ref G/E/99R.

9-0-9V 4A TRANSFORMERS chassis mount. £7 ref LOT19A.

2.5 KILOWATT INVERTERS, Packed with batteries etc but as they weigh about 100kg CALLERS ONLY! £120.

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb for just £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref LOT17.

CLEARANCE SECTION, MINIMUM ORDER £15, NO TECHNICAL DETAILS AVAILABLE, NO RETURNS, TRADE WELCOME.

2000 RESISTORS ON A REEL (SAME VALUE) 99P REF BAR340
 AT LEAST 200 CAPACITORS (SAME VALUE) 99P REF BAR342
 INFRA RED REMOTE CONTROLS JUST 99P REF BAR333
 CIRCUIT BREAKERS, OUR CHOICE TO CLEAR 99P REF BAR335
 MICROWAVE CONTROL PANELS TO CLEAR £2 REF BAR 329
 2 TUBES OF CHIPS (2 TYPES OUR CHOICE) 90P REF BAR305
 LOTTERY PREDICTOR MACHINE!! JUST £1.50 REF BAR313
 HELLA/ROVER ELECTRIC H/LAMP LEVELLER £2 REF BAR311
 INCLINER C5 16" TYRES TO CLEAR AT JUST 75P REF BAR318
 LARGE MAINS MOTORS (NEW) TO CLEAR AT 75P REF BAR310
 MODEMS ETC FOR STRIPPING £2.50 EACH REF BAR324
 110V LARGE MOTORS (NEW) TO CLEAR AT 50P REF BAR332
 MODULATOR UNITS UNKNOWN SPEC JUST 50P REF BAR323
 GX4000 GAMES COSLES JUST £4 REF BAR320
 SMART CASED MEMORY STORAGE DEVICE, LOADS OF BITS INSIDE, PCB, MOTOR, CASE ETC. BUMPER PACK OF 5 COMPLETE UNITS TO CLEAR AT £2.50 (FOR 5) REF BAR 330.
 2 CORE MAINS CABLE 2M LENGTHS PACK OF 4 £1 REF BAR337
 PC USER/BASIC MANUALS, LOADS OF INFO. £1 REF BAR304
 PCB STRIPPERS TO CLEAR AT 2 FOR 99P REF BAR341
 3 M 3 CORE MAINS CABLE AND 13A PLUG. 60P REF BAR325

WE BUY SURPLUS STOCK

FOR CASH
 BUYERS DIRECT LINE 0802 660377

FREE CATALOGUE
 100 PAGE CATALOGUE NOW
 AVAILABLE, 45P STAMPS.

EVERYDAY

CLASSIFIED

PRACTICAL

ELECTRONICS

Everyday Practical Electronics reaches nearly twice as many UK readers as any other independent monthly hobby electronics magazine, our audited sales figures prove it. We have been the leading independent monthly magazine in this market for the last eleven years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Holland Wood House, Church Lane, Great Holland, Essex CO13 0JS. Phone/Fax (01255) 850596.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY
Up to 38 volts d.c. at 6 amps continuous, 10 amps peak, fully variable from 1 to 38 volts. Twin Voltage and Current meters  **£96 inc. VAT** for easy read-out, 240 volt a.c. carriage £6 input. Fully smoothed, size 14½ x 11 x 4½ inches.

RADIO COMPONENT SPECIALISTS
337 WHITEHORSE ROAD, CROYDON SURREY, CR0 2HS. Tel: 0181-684 1665

Lots of transformers, high volt caps, valves, speakers, in stock. Phone or send your wants list for quote.

 **FM TRANSMITTERS**

Full range of transmitter Kits from under £10. Wide range Mono, Stereo and Surveillance. Also professional FM broadcasting transmitters. 18 Victoria St., Queensbury, BRADFORD, BD13 1AR Tel 01274 816200 Email veronica@legend.co.uk

Miscellaneous

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poynings Drive, Hove, Sussex BN3 8GR, or phone Brighton 883871.

THE ELECTRONICS BOOK AND COMPONENT LISTING

A regular listing of hundreds of secondhand electronics books and magazines from 1940-1995 for the hobbyist, student and engineer. Includes numerous electronics reference books and surplus electronic components and hardware at bargain prices. Send six first class stamps for listing.

Dept E. Chevet Supplies Ltd., 157 Dickson Rd., Blackpool FY1 2EU
Tel: 01253 751858 Fax: 01253 302979

THE BRITISH AMATEUR ELECTRONICS CLUB

exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.

For membership details, write to the Secretary:

Mr. J. F. Davies, 70 Ash Road, Cuddington, Northwich, Cheshire CW8 2PB.

Space donated by Everyday Practical Electronics

G.C.S.E. ELECTRONICS KITS, at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 70 Oxford Road, Clacton, CO15 3TE.

VALVE ENTHUSIASTS: Capacitors and other parts in stock. For free advice/lists please ring, Geoff Davies (Radio). Tel: 01788 574774.

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and Production. Artwork raised from magazines or draft designs at low cost. PCBs also designed from schematics. Production assembly also undertaken. For details send to P. Agar, 36 Woodcot Avenue, Belfast, BT5 5JA or phone 01232 473533 (7 days).

BTEC ELECTRONICS TECHNICIAN TRAINING

GNVQ ADVANCED ENGINEERING (ELECTRONIC) - PART-TIME
HND ELECTRONICS - FULL-TIME
B.Eng FOUNDATION - FULL-TIME

Next course commences Monday 6th January 1997
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 PENYWERN ROAD EARLS COURT, LONDON SW5 9SU
TEL: 0171-373 8721

This 3cm space in *Everyday Practical Electronics* will ONLY cost you **£24 + VAT**

PCB SCHEMATIC AND ARTWORK LAYOUT, customised product design, surface-mount component sourcing and much more. Prices from £15.00. Contact ULTRA-TECH. Tel/Fax: 0181 472 8213, Mobile: 0850 973555.

FREE ELECTRONIC SAMPLES + 12 audio projects. S.A.E. K.I.A., 1 Regent Road, Ilkley, Look stereo amplifiers 30 + 30 Watt + preamp. + controls, T.B. & V. tested + directions. £10.

WANTED, AY-3-8910, three channel plus two ports, soundchip. Ring Andy 0181 9483540.

SAVE OVER £5 - SUBSCRIBE NOW!

EVERYDAY PRACTICAL ELECTRONICS

SUBSCRIPTION ORDER FORM

Annual subscription rates (1996/7): UK £24.00.

Overseas £30.00 standard air service, £47.50 express airmail.

To:
Everyday Practical Electronics,
Allen House, East Borough,
Wimborne,
Dorset BH21 1PF
Tel: 01202 881749
Fax: 01202 841692

E-mail: editorial@epemag.wimborne.co.uk

Name

Address

.....

.....

.....

I enclose payment of £.....

(cheque/PO in £ sterling only, payable to Everyday Practical Electronics). Alternatively send Mastercard or Visa number and card expiry date.

Signature

Please supply name and address of cardholder if different from the subscription address shown above. Subscriptions can only start with the next available issue. For back numbers see the Back Issues page.

M11/96

N. R. BARDWELL LTD (EPE)

200	Signal diodes 1N4148	£1.00	25	5mm red l.e.d.s.	£1.00
75	Rectifier Diodes 1N4001	£1.00	25	3mm red l.e.d.s.	£1.00
50	Rectifier Diodes 1N4007	£1.00	25	Assld. high brightness l.e.d.s.	£1.00
10	W04 Bridge Rectifiers	£1.00	50	Axial l.e.d.s. (Diode package)	£1.00
5	NE555 Timer I.C.s	£1.00	12	Assld. 7-segment displays	£1.00
50	Assld. Zener Diodes	£1.00	2	ORP12 light dependant resistors	£1.00
20	BC182L Transistors	£1.00	30	Assld. IF transformers	£1.00
30	BC212L Transistors	£1.00	48	Assld. coil formers	£1.00
30	BC213L Transistors	£1.00	50	Assld. RF chokes (inductors)	£1.00
30	BC214C Transistors	£1.00	30	Assld. connectors edge.d.i.l. sil etc.	£1.00
30	BC237 Transistors	£1.00	30	Assld. d.i.l. sockets up to 40 pin	£1.00
20	BC328 Transistors	£1.00	200	Assld. disc ceramic capacitors	£1.00
20	BC337 Transistors	£1.00	80	Assld. capacitors 1nF to 1µF	£1.00
30	BC478 Transistors	£1.00	80	Assld. electrolytic capacitors	£1.00
30	BC546 Transistors	£1.00	10	4P3W MBB min. rotary switches	£1.00
30	BC547 Transistors	£1.00	20	Min. SP/CO slide switches	£1.00
30	BC548 Transistors	£1.00	20	1" glass reed switches	£1.00
30	BC549 Transistors	£1.00	200	4N7 mini axial capacitors	£1.00
25	BC557 Transistors	£1.00	24	24 pin d.i.l. wire wrap i.c. skts	£1.00
30	BC558 Transistors	£1.00	1	12V motorised volume control 50K	£1.00
30	BC559 Transistors	£1.00	50	Grommets 6.3mm id, 9.5mm od	£1.00
25	BC640 Transistors	£1.00	100	of 1/4W 5% resistors any one value, E24, range 1R to 10M	£0.45
20	MPSA42 Transistors	£1.00	Prices include VAT, postage £1.25. 30p stamp for Lists		
20	MPSA92 Transistors	£1.00	288 Abbeydale Road, Sheffield S7 1FL		
20	2N3904 Transistors	£1.00	Phone (0114) 2552886 Fax (0114) 2500689		
5	78L12 12V 100mA Pos Regulators	£1.00			
10	79M08 8V 500mA Neg Regulators	£1.00			

SERVICE MANUALS & Technical Books

Available for most equipment, any make, age or model.
Technical Book and Manual Compilations now on CD-ROM
Return the coupon for your FREE catalogue



MAURITRON TECHNICAL SERVICE (EPE)

8 Cherry Tree Road, Chinnor, Oxon, OX9 4QY

Tel:- 01844-351694. Fax:- 01844 352554.

Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps, or £4.11 for the complete Service Manuals Index on PC Disc plus catalogue.

NAME _____

ADDRESS _____

POSTCODE _____

Photocopy this coupon if you do not wish to cut the magazine

VISA



Cooke International

SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS, GENERATORS, OSCILLOSCOPES, POWER METERS, ETC. ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME
SEND FOR LISTS OF EQUIPMENT & MANUALS

ALL PRICES EXCLUDE VAT AND CARRIAGE

DISCOUNT FOR BULK ORDERS

SHIPPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM-5PM


Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis,
West Sussex, PO22 0EB, U.K.

Tel (+ 44) 01243 545111/2 Fax (+ 44) 01243 542457

EQUIPMENT & ACCESSORIES PURCHASED

HIGH QUALITY LOW COST C.C.T.V. CAMERA

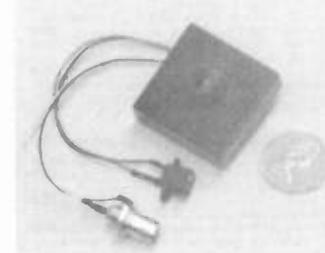VERY LOW LIGHT LEVEL.
ALTO ELECTRONIC SHUTTER.
COMPOSITE VIDEO OUT VIA BNC PLUG.
SMALL, DISCRETE SIZE.
CAN BE USED WITH PC DIGITISER.



This super quality CCD camera can be connected into your existing TV or video using the AV channel and can be used for discrete surveillance or observing your property externally using a suitable weatherproof housing. Can accommodate lighting levels ranging from daylight to street lighting using its built in electronic shutter. Excellent when using with an infra red source. Built in wide angle fixed focus lens the camera has a resolution of 380 TVL. Can be housed inside an empty floodlight case. (extra).

Special offer price of only: £79.95 Plus VAT (P&P £3.50)

For full range of CCTV products send SAE to:
Direct CCTV Ltd., Dept. PE27., Direct House, Florence Street,
Middlesbrough TS2 1DR.

TECHNICAL INFORMATION SERVICES

76 Church St, Larkhall, Lanarks, ML9 1HE
Tel: 01698 883334/884585 Fax: 01698 884825

PHONE NOW FOR YOUR FREE QUOTE

We have the World's Largest Collection of

SERVICE MANUALS

Why not join Europe's fastest growing
"Information Library Service"

Buy ANY Service Manual for £10.00 and return any

manual no longer needed for a £5.00 credit

CALL/WRITE NOW FOR FURTHER DETAILS

Initial joining fee of £70 : Thereafter £20 Yearly

Join Now: Get your first Manual FREE!

3lb mixed component pack	£4.95
Jumbo component pack	£10
250 off mixed capacitors	£4.95
250 off i.c. sockets	£3.95
1000 off mixed ceramic caps	£7.50
20 off mixed crystals/filters	£4.95
25 off mixed relays	£3.50
100 off phono plugs	£2.95*
10 off mixed displays	£3.75*
50 off d.i.l. switches	£3.75*
30 off mixed heatsinks	£3.75*
30 off mixed switches	£3.75*
Brand new 360k 5 1/4" floppy drive	£4.50
5 1/4" to 3 1/2" floppy drive converter leads	£1.50*
1.2MB 5 1/4" floppy drive	£10
200MB 3 1/2" E.S.D.I. hard drive	£28
12V d.c. 200 r.p.m. geared motor	£1.50 each, 10 for £12
220V 1500 r.p.m. geared motor	£6 each, 10 for £50
7V-12V d.c. motor, 4/6000 r.p.m.	£4 each, 10 for £30
700mA-1450mA	£4 each, 10 for £30
12V d.c. motor, 13,000 r.p.m.	£1 each, 10 for £8
180mA	£1 each, 10 for £8

6V d.c. motor, 1,200 r.p.m. 600mA	£1 each, 10 for £8
9V d.c. motor, 13,000 r.p.m. 460mA	£1 each, 10 for £8
10-5V d.c. motor, 9,000 r.p.m., 220mA	£1 each, 10 for £8
S.M. P.S.U., mains input, +5-2V 6A, +24V 0.5A, +24V 5-5A outputs	£6 each

QUANTITY DISCOUNTS AVAILABLE PLEASE RING.

We also buy all forms of electronic components, p.s.u.s, disk drives etc. Lists to below address.

ALL PRICES INCLUDE V.A.T.
PLEASE ADD £2.00 p&p EXCEPT ITEMS MARKED * WHICH ARE 50P.

SAE FOR BULK BUYING LIST PAYMENT WITH ORDER TO:

Dept EE, COMELEC,
14 Constable Road,
St. Ives, Huntingdon,
Cambs PE17 6EQ

Tel/Fax: 01480 300819

THE CR SUPPLY CO

RESISTORS
1/4 Watt Mixed metal/carbon film resistors
5% E12 series 10 ohms to 1 Megohm.....2p
1 ohm to 10 Megohm.....1p
100 off per value - 85p even hundreds
per value totalling 1000.....£7.50
1/4 Watt Metal film resistors 5% E12 series
10 ohm to 1 Meg - 1 1/2p 1% E24 series.....2p
1/4 Watt Mixed metal/carbon film resistors
5% E24 series 1 ohm to 10 Megohm.....2 1/2p
1 Watt Mixed metal/carbon film 5%
E12 series 4R7 to 10 Megohms.....5p
NEW Resistor development kits, 1/4 Watt Cr/Film
5x78 different values from 1 ohm to 10 Meg-
ohm, comes in storage drawer with printed
colour code on outside. ideal for laboratories,
education, service depts., repairers and
hobbyists, etc.....£6.95

CAPACITORS
Radial Aluminium Electrolytics (mid Volts).
1/63, 2/263, 4/7100, 10/25, 10/63 - 6p;
100/16, 100/25 - 8p; 100/63 - 13p; 22/16,
22/25, 22/50, 33/16, 47/16, 47/35, 47/50 - 7p;
220/16 - 9p; 220/25, 220/50 - 11p; 470/16,
470/25 - 13p; 1000/25 - 23p; 2200/25 - 42p;
4700/25 - 74p

Miniature Polyester, 250V working vertical
mounting (mid). 01, .015, .022, .047, .068 -
5p; 0.1 - 6p; 0.12, 0.15, 0.22 - 7p; 0.47 - 9p;
0.68 - 10p; 1.0 - 13p

Mylar (polyester) 100V working E12 series
vertical mounting (p). 1000 to 8200 - 4p;
0.01 to 0.068 - 5p; 0.1 - 6p; 0.12, 0.15, 0.22 -
7p; 0.47/50V - 9p

Submin Ceramic Plate, 100V working E12
series vertical mountings (p). 2%, 1.8 to 47 -
4p; 2%, 55 to 330 - 5p; 1%, 390-4700p - 6p
Polystyrene .63V working E12 series, long
axial wires (p). 10 to 820 - 5p; 1000 to 10,000 -
6p; 12,000 - 8p

Subminiature, Tantulum Bead electrolytics
(mid Volts). 0.1, 0.22, 0.47, 1.0, 2.2, 3.3
@35V, 4.7/16, 10/6, 6.8/35 - 13p; 4.7/25,
6.8/16, 10/16 - 15p; 15/16, 22/6, 33/10 - 21p;
10/25 - 22p; 10/35, 22/16 - 28p; 47/10 - 29p;
47/16 - 65p; 47/20 - 72p; 47/35 - 76p; 100/3 -
78p; 100/6, 220/6 - 81p

TRANSISTORS
BC107/8/9 - 18p; BC547/8/9 - 7p; BC557/8/9 - 8p;
BC182, 182L, BC183, 183L, BC184, 184L,
BC212, 212L - 10p; BC327, 337, 337L - 8p;
BC727, 737 - 12p; BD135/8/7/8/9 - 27p;
BCY70 - 28p; BFY50/51/52 - 32p; BFX88 -
38p; 2N3055 - 55p; TIP31, 32 - 40p; TIP41, 42 -
40p; BU208A - £1.50, BF195, 197 - 12p

20mm fuses
100mA to 5A. Q/blow - 8p; A/surge - 14p.
Holders, chassis, mounting - 8p

WE HOLD PACKS OF COMPONENTS FOR THIS MONTH'S EPE PROJECTS - RING FOR PRICES

CMOS
4001B - 23p; 4011B - 25p; 4017B - 45p;
4069UB unbuffered - 25p

D.I.L. HOLDERS
8-pin - 9p; 14, 16, 18-pin - 15p; 24-pin - 19p;
28-pin - 22p; 40-pin - 31p

VOLTAGE REGULATORS
1A +ve or -ve 5V, 8V, 12V, 15V, 18V & 24V -
61p; 100mA +ve 5V, 8V, 12V, 15V - 38p

DIODES (PIV/amps)
75/150mA 1N4148 - 2p; 800/1A 1N4006 - 5p;
400/3A 1N5404 - 14p; 115/50mA OA91 - 18p;
100/1A 1N4002 - 4p; 1000/1A 1N4007 - 5p;
60/1.5A S1M1 - 7p; 100/1A bridge - 28p; 400/1A
1N4004 - 4p; 1250/1A BY 127 - 14p; 30/150mA
OA47 gold bonded - 24p

Zener diodes E24 series 3V3 to 33V 400mW - 6p;
1 watt - 12p

L.E.D.'s
3mm, and 5mm. Red, Green, Yellow - 14p; Grom-
mets to suit 3mm - 2p, 5mm - 3p; 5mm Tricolour
& Bicolour - 22p; Red flashing L.E.D.'s require
9V-12V supply only, 5mm - 70p

BATTERIES
AA/NP7 NiCad rechargeable cells - £1.78 each.
With PCB mounting pins 600mA, £2.28p AA/NP7
zinc/carbon batteries in packs of 4 - £1.10 per pack
Watch batteries, diam x thickness in mm 7.9x3.6,
11.6x3, 11.6x4.2, 11.6 x 5.4 - 55p each
Battery snaps for PP3 - 8p; for PP9 - 16p

ELECTRIC MOTORS
1.5V to 3V with bracket, 18x25mm shaft diam 2mm
- £1.24p; high torque 30x23mm - £1.45p; 3V to
6V, 25x21mm diam - £1.20p

MISCELLANEOUS
Mains indicator neons with 220k resistor.....14p
High speed PCB drill bits 0.8, 1.0, 1.3, 1.5, 2.0mm
- 47p; 12V mini drill, 3 jaw chuck - £14.75

Helping-hands 6 ball joints and 2 croc clips
to hold awkward jobs, cast-iron base.....£4.50
Glass reed switches with single pole make
contacts - 11p; Magnets - 28p

0.1" Stripboard 2 1/2" x 9" rows 25 holes - 26p.
3" x 2 1/2" 24 rows 37 holes - 80p

Jack plugs 2.5 & 3.5mm - 16p; Sockets Panel Mtg,
2.5 & 3.5mm - 11p

Earpieces 2.5 & 3.5mm, dynamic - 29p;
3.5mm crystal - £1.60

Multi-core solder, 22SWG - 11p/yard,
18SWG - 21p/yard

Air Purifier and Ioniser complete with mains adap-
tor and car lead made by Smiths Industries. £12.50
21-pin Scart to 21-pin Scart lead, 1.2m all pins
connected - £3.95p; PCB Scart sockets - 92p

Satellite cable 75 ohm semi air spaced 6.5mm,
OD black or white - 36p/yard.
741 Op Amp - 24p; 555 Timer - 25p; 555L Low
Power - 30p; 556 Dual Timer - 40p; 556L Low
Power - 74p; 558 Dual Op. Amp. - 22p

SAE for lists. P&P £1.00. 100% V.A.T.

44 Chapelfield Way, Rotherham,
South Yorkshire S61 2TL.

Tel/Fax: 0114 2468049

NEW MINI CAMERA and SPECIAL OFFERS
NEW - Mini Waterproof TV Camera, 40 x 40 x 15mm, requires 10V to 16V at 120mA with composite video output (lo lead into a Video or a TV with a SCART plug). It has a high resolution of 450 TV lines vertical and 300 TV lines horizontal, electronic auto iris for nearly dark (1:1Lux) to bright sunlight operation and a pinhole lens with a 92 degree field of view, it focuses down to a few cm. It is fitted with a 3-wire lead (12V in, gnd and video out). £93.57 + VAT = £108.95 or 10 + £89.32 + VAT = £104.86.

High quality Stepping Motor Kits (all including stepping motors) Comstep independent control of two stepping motors by PC (via the Parallel Port) with two motors and software. Kit £87.00, Built £98.00
 Software support and 4 digital inputs kit £27.00
Power Interface: 4A kit £36.00, 8A kit £46.00.
Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit. £23.00
Hand Held Transistor Analyser. It tells you which lead is the base, the collector and emitter and if it is APN or PNP or faulty. £33.45. Spare 6V battery £1.20.
 LEDs 3mm or 5mm Red or Green 7p each, Yellow 11p each.
 Cable Ties 1p each, £3.95 per 1000, £49.50 per 10,000.

RECHARGEABLE BATTERIES
 AA (HP7) 500mAh £0.90
 AA 700mAh £1.75
 C 2Ah with solder tags £3.60
 D 4Ah with solder tags £4.85
 1/2AA with solder tags £1.55
 AAA (HP16) 180mAh £1.75
 AA 500mAh with solder tags £1.56
 C (HP11) 1/2Ah £2.20
 D (HP2) 1/2Ah £2.60
 PFG 8.4V 110mAh £4.94 each, £3.95 100 +
 Sub C with solder tags £2.50
 1/3 AA with tags (Philips CTV) £1.86
 Standard Charger, charges 4 AA cells in 5 hours or 4 Cs or Ds in 12 to 14 hours, plus 1xPP3 (1, 2, 3 or 4 cells may be charged at a time) £5.95
High Power Charger, as above but charges the Cs and Ds in 5 hours. AAs, Cs and Ds must be charged in lots or tins. £10.95
Nickel Metal Hydride AA cells, high capacity with no memory. If charged at 100mA and discharged at 250mA or less 1100mAh capacity (lower capacity for high discharge rates) £3.75

SPECIAL OFFERS - PLEASE CHECK FOR AVAILABILITY
 Stick of 4, 42mm x 16mm NiCad batteries, 171mm x 16mm dia, with red and black leads, 4.6V. £3.95
 Five button cell, 6V 280mAh battery with wires (Varia 5 x 2500K) £2.45
 Shaded-pole motor, 240V a.c. 5mm x 20mm shaft, 80mm x 60mm x 55mm, excluding the shaft. £4.95
 115V a.c. 80V d.c. motor, 4mm x 22mm shaft, 50mm dia x 60mm long body (excluding the shaft) it has a replaceable thermal fuse and brushes. £4.94 each, £3.95 100 +
 7-Segment, common anode, i.e.d. display, 12mm. £4.5p
 LM337K, TO3 case, Variable regulator, £1.95, 100 + £1.44
 GaAs F.E.T. low leakage current 58873 £12.95 each, £9.95 10 +, £7.95 100 +
 BS2290 p-channel MOSFET 45p
 BC558 transistor £3.95 per 100
 BC547A transistor 20 for £1.00
 74LS05 Hex inverter £10.00 per 100
 Used 6748 Microcontroller £3.50
 LS952 UHF Limiting amplifier, LC 16 surface mounting package with data sheet. £1.95
 DC-DC Converter, Reliability model V12PS, 12V in, 5V 200mA out, 300V input-to-output isolation, with data £4.95 each or pack of 10 £38.50

Hour Counter used 7 digit 240V a.c. 50Hz £1.45
 GWERTY keyboard, 56-key, good quality £6.00
 switches, new £6.00
 Alps AB2903-C large stepping motor 14V 7.5° step, 27 ohm, 68mm dia. body, 6.3mm shaft. £8.95 or £200 for a box of 30
 Polyester capacitors, box type, 22.5mm lead pitch 0.5µF 250V d.c. 18p each, 14p 100 +, 9p 1000 + 1µF 250V d.c. 20p each, 15p 100 +, 10p 1000 + 1µF 50V bipolar electrolytic axial leads, 15p each, 7.5p 1000 +
 0.22µF 250V polyester axial leads, 15p each, 100 + 7.5p each
 Polypropylene 1µF 400V d.c. (Wima MKP10) 27 5mm pitch, 25mm x 29mm x 17mm case, 75p each, 60p 100 +
 Philips 123 series solid aluminum axial leads, 33µF 10V and 2.2µF 40V 40p each, 25p 100 +
 Philips 108 series, long life, 30p each, 15p 1000 +
 22µF 63V axial 30p each, 15p 1000 +
 Multilayer AVX ceramic capacitors, all 5mm pitch, 100V 100pF, 150pF, 220pF, 10,000pF (10n) 10p each, 5p 100 +, 3.3p 1000 +
 500pF compression trimmer capacitor 60p
 40µF 370V a.c. motor start capacitor (dielectric type containing no p.c.b.s.) £3.95 or £49.50 for 10
 Solid carbon resistors, very low inductance, ideal for i.c. circuits, 27 ohm 2W, 68 ohm 2W 25p each, 15p each 100 +
 We have a range of 0.25W, 0.5W, 1W and 2W solid carbon resistors - please send SAE for list
 P.C. 400W PSU (Intel part 201035-001) with standard motherboard and five disk drive connectors, fan and mains input/output connectors on back and switch on the side (top for tower case) dims, 212mm x 149mm x 149mm excluding switch, £28.00 each, £138.00 for 6
 MX180 Digital Multimeter 17 ranges, 1000V d.c. 750V a.c. 240Vohm 200mA transistor Hi 9V and 1.5V battery test £9.95
 AMD 27256-3 EPROMs £2.00 each, £1.25 100 +
 DIP switch 3PCO 12-pin (ERG SDC-3-023) 60p each, 40p 100 +
 Disk Drive Boxes for a 5.25 disk drive, with room for a power supply, light-grey plastic 67mm x 268mm x 247mm £7.95 or £49.50 for 10
 Handheld Ultrasonic Remote Control £3.95
 CV2488 Gas Relay 30mm x 10mm dia. with 3-wire terminals, will also work as a neon light. 20p each, or £7.50 per 100
 Verbatim R5000H Streamer tape commonly used on nc machines and printing presses etc. It looks like a normal cassette with a slot cut out of the top £4.95 each, £3.75 100 +
 Heatsink Compound Tube 95p
 HV3-2405-E5 5V-24V 50mA Regulator i.c. 18V-24V a.c. input, 8-pin DIL package, £3.49 each, 100 + £2.25
 LM555 timer i.c., 16p, 8-pin DIL socket, 6p
 All products advertised are new and unused unless otherwise stated.
 Wide range of CMOS TTL 74HC74F Linear. Transistors kits, rechargeable batteries, capacitors, tools etc. always in stock.
 Please add £1.95 towards P&P. VAT included in all prices

JPG ELECTRONICS
 276-278 Chatsworth Road
 Chesterfield S40 2BH
 Access/Visa Orders:
 Tel: (01246) 211202 Fax: (01246) 550959
 Callers welcome 9.30am to 5.30pm
 Monday to Saturday

Millions of quality components at lowest ever prices!
 Plus anything from bankruptcy - theft recovery - frustrated orders - over production etc.
NO VAT to add on.
 Send 45p stamped self addressed label or envelope for clearance lists.
Brian J Reed
6 Queensmead Avenue, East Ewell
Epsom, Surrey KT17 3EQ
Tel: 0181-393 9055 Mail order UK only.
 Lists are updated and only 40 are sent out every 2 weeks. This normally ensures that orders can be fulfilled where only a few thousand of an item is available. (Payment is returned if sold out. I do not deal in credit notes). This will sometimes entail a delay of up to eight weeks - but the prices will be worth the wait!

ADVERTISERS INDEX

N. R. BARDWELL.....879
 B.K. ELECTRONICSCover (iii)
 BRIAN J. REED.....880
 BULL ELECTRICALCover (ii)/877
 CIRKIT DISTRIBUTION.....827
 COMPELEC.....879
 COOKE INTERNATIONAL.....879
 CRICKLEWOOD ELECTRONICS.....857
 CR SUPPLY CO.....879
 DIRECT CCTV.....879
 DISPLAY ELECTRONICS.....810
 EPT EDUCATIONAL SOFTWARE.....814
 ESR ELECTRONIC COMPONENTS.....818
 INFOTECH & STREE.....879
 JAKE ROTHMAN.....841
 JCG ELECTRONICS.....841
 J&N FACTORS.....869
 JPG ELECTRONICS.....880
 LABCENTER ELECTRONICS.....815
 LENNARD RESEARCH.....857
 MAGENTA ELECTRONICS.....816/817
 MAPLIN ELECTRONICS.....Cover (iv)
 MAURITRON.....879
 MODERN ELECTRONICS MANUAL.....872
 NATIONAL COLLEGE OF TECHNOLOGY.....860
 NICHE SOFTWARE.....830
 OMNI ELECTRONICS.....860
 PICO TECHNOLOGY.....811
 QUASAR ELECTRONICS.....861
 QUICKROUTE SYSTEMS.....812
 RADIO-TECH.....861
 ROBINSON MARSHALL (EUROPE).....828
 SHERWOOD ELECTRONICS.....880
 SUMA DESIGNS.....813
 TSIEN (UK).....843

ADVERTISEMENT MANAGER: PETER J. MEW
ADVERTISEMENT OFFICES:
 EVERYDAY PRACTICAL ELECTRONICS,
 ADVERTISEMENTS,
 HOLLAND WOOD HOUSE, CHURCH LANE,
 GREAT HOLLAND, ESSEX CO13 0JS.
 Phone/Fax: (01255) 850596
 For Editorial address and phone numbers see page 819.

SHERWOOD ELECTRONICS
FREE COMPONENTS
 Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red Leds	SP118 2 x Cmos 4047
SP2 12 x 5mm Green Leds	SP119 4 x Cmos 4072
SP3 12 x 5mm Yellow Leds	SP124 20 x Assorted ceramic disc caps.
SP6 15 x 3mm Red Leds	SP125 10 x 1000/16V radial elect caps.
SP7 12 x 3mm Green Leds	SP130 100 x Mixed 0.5W C.F. resistors
SP8 10 x 3mm Yellow Leds	SP131 2 x TL071 Op.amps
SP10 100 x 1N4148 diodes	SP135 6 x Min. slide switches
SP11 30 x 1N4001 diodes	SP137 4 x W005 1.5A rectifiers
SP12 30 x 1N4002 diodes	SP138 20 x 2.2/50V rad. elect. caps.
SP13 20 x Assorted radial elect. caps.	SP142 2 x Cmos 4017
SP18 20 x BC182 transistors	SP144 3 x TIP31A transistors
SP19 20 x BC183 transistors	SP145 6 x ZTX300 transistors
SP20 20 x BC184 transistors	SP147 5 x Stripboard 9 strips/25 holes
SP21 20 x BC212 transistors	SP151 4 x 8mm Red Leds
SP22 20 x BC214 transistors	SP152 4 x 8mm Green Leds
SP23 20 x BC549 transistors	SP153 4 x 8mm Yellow Leds
SP24 4 x Cmos 4001	SP156 3 x Stripboard, 14 strips/27 holes
SP25 4 x 555 timers	SP160 10 x 2N3904 transistors
SP26 4 x 741 Op.amps	SP161 10 x 2N3906 transistors
SP28 4 x Cmos 4011	SP162 10 x 100K hor. trimpots
SP29 4 x Cmos 4013	SP165 2 x LF351 Op.amps
SP33 4 x Cmos 4081	SP167 6 x BC107 transistors
SP36 25 x 10/25V radial elect caps	SP168 6 x BC108 transistors
SP37 15 x 100/35V radial elect caps	SP173 10 x 220/25V rad. elect. caps
SP39 10 x 470/16V radial elect caps	SP175 20 x 1/63V radial elect caps
SP41 20 x Mixed transistors	SP182 20 x 4.7/50V radial elect caps
SP42 200 x Mixed 0.25W C.F. resistors	SP183 20 x BC547 transistors
SP47 5 x Min. pushbutton switches	SP187 15 x BC239 transistors
SP48 12 x Assorted axial elect. caps.	SP192 3 x Cmos 4066
SP102 20 x 8-pin DIL sockets	SP193 20 x BC213 transistors
SP103 15 x 14-pin DIL sockets	SP194 10 x OA90 diodes
SP104 15 x 16-pin DIL sockets	SP195 3 x 10mm Yellow Leds
SP105 5 x 74LS00	
SP106 5 x 74LS02	
SP112 4 x Cmos 4093	
SP115 3 x 10mm Red Leds	
SP116 3 x 10mm Green Leds	
SP117 15 x BC556 transistors	

RESISTOR PACKS - C.Film
 RP3 5 each value - total 365 0.25W £2.40
 RP7 10 each value - total 730 0.25W £3.75
 RP10 1000 popular values 0.25W £6.00
 RP4 10 5 each value-total 365 0.5W £3.40
 RP8 10 each value-total 730 0.5W £6.00

Catalogue £1 inc. P&P or FREE with first order.
P&P £1.25 per order. NO VAT.
 Orders to:
Sherwood Electronics,
7 Williamson St., Mansfield,
Notts. NG19 6TD.

Published on approximately the first Friday of each month by Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Printed in England by Wiltshire (Bristol) Printers Ltd., Bristol, BS20 9XP. Distributed by Seymour, Windsor House, 1270 London Road, Norbury, London SW16 4DH. Subscriptions INLAND £24 and OVERSEAS £30 (£47.50 airmail) payable to "Everyday Practical Electronics", Subs Dept, Allen House, East Borough, Wimborne, Dorset BH21 1PF. EVERYDAY PRACTICAL ELECTRONICS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" xH3 1/2" (2U)xD11"
MXF400 W19" xH5 1/4" (3U)xD12"
MXF600 W19" xH5 1/4" (3U)xD13"
MXF900 W19" xH5 1/4" (3U)xD14"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH



OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency. Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover it is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

- TYPE 'A' (KSN1036A)** 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
- TYPE 'B' (KSN1005A)** 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
- TYPE 'C' (KSN1016A)** 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
- TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
- TYPE 'E' (KSN1038A)** 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
- LEVEL CONTROL** Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.



IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.



POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

ibi FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
ibi FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR
OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair

IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99 400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS

Features:
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm. PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm. PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm. PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm. PRICE £132.85 + £5.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm. PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC

- ALL EMINENCE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO.** PRICE £32.71 + £2.00 P&P
 - RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.**
 - 8" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID.** PRICE £33.74 + £2.50 P&P
 - RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.**
 - 10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID.** PRICE £43.47 + £2.50 P&P
 - RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.**
 - 12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR.** PRICE £35.64 + £3.50 P&P
 - RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.**
 - 12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR.** PRICE £36.67 + £3.50 P&P
 - RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB.**
 - 12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID.** PRICE £46.71 + £3.50 P&P
 - RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB.**
 - 12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC.** PRICE £70.19 + £3.50 P&P
 - RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.**
 - 15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR.** PRICE £50.72 + £4.00 P&P
 - RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB.**
 - 15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR.** PRICE £73.34 + £4.00 P&P
 - RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.**

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

- ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohms)**
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 8" 50Watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR.** PRICE £88.90 + £2.00 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.**
 - 10" 50Watt EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR.** PRICE £13.65 + £2.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.**
 - 10" 100Watt EB10-100 BASS, HI-FI, STUDIO.** PRICE £30.39 + £3.50 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.**
 - 12" 100Watt EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO.** PRICE £42.12 + £3.50 P&P
 - RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.**
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 5 1/2" 60Watt EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC.** PRICE £9.99 + £1.50 P&P
 - RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.**
 - 6 1/2" 60Watt EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC.** PRICE £10.99 + 1.50 P&P
 - RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.**
 - 8" 50Watt EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC.** PRICE £12.99 + £1.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB.**
 - 10" 60Watt EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC.** PRICE £16.49 + £2.00 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.**

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz. VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES. SIZE 38 x 123mm. SUPPLY 12V @ 0.5AMP PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz. VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m. SIZE 56 x 46mm. SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P

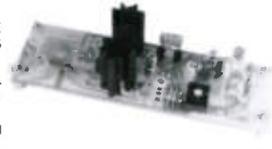


PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA, ESSEX, S92 6TR. Tel.: 0702 - 527572 Fax.: 0702 - 420243



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



NEW!

The **MPLIN** **MPS** MAPLIN PROFESSIONAL

Catalogue

is now available

**Over 17,000
technical products
for industry,
education and
the enthusiast**

**New! Free delivery
on all orders***

MPLIN **MPS**

MAPLIN PROFESSIONAL

01702 554000

MPS
MAPLIN PROFESSIONAL



**THE COMPLETE
CATALOGUE FOR
ELECTRONICS**

1996/7

September '96-
February '97



**NEW
FREE DELIVERY***

BRITAIN'S BEST-SELLING ELECTRONICS CATALOGUE

**Call in for your copy at WH SMITH, John Menzies and
Maplin stores nationwide, or order direct by mail-order
on 01702 554000 - Only £3.45 (plus 50p packaging)
PLEASE QUOTE REF. MA010 WHEN ORDERING.**

If you live outside the U.K. send £8.45 or 21 IRCs for Airmail in Europe or Surface mail outside Europe;
£16.00 or 37 IRCs for Airmail outside Europe to Maplin MPS, P.O. Box 777, Rayleigh, Essex, England SS6 8LU.

* on orders over £30.00 (inclusive of VAT). Free delivery on ALL orders for Business Account customers.

See us on the Web at <http://www.maplin.co.uk>