

MODERN WIRELESS



December.

1/6

Vol. III. No. 7. Edited by JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E. December, 1924.

Special XMAS number



THE ARMSTRONG SUPER-HETERODYNE. *By Edwin H. Armstrong.*
MAKING A 4-VALVE T.A.T. RECEIVER. *By John Scott-Taggart, F.Inst.P., A.M.I.E.E.*
A REINARTZ RECEIVER FOR PLUG-IN COILS. *By Percy W. Harris.*
A 2-VALVE POWER AMPLIFIER. *By John Underdown.*
A LOOSE-COUPLED SINGLE-VALVE SET. *By J. W. Barber.*
A HOME 3-VALVE RECEIVER. *By E. Redpath.*
A NEW DESIGN OF CRYSTAL SET. *By Stanley G. Rattes, M.I.R.E.*
LATEST CONTINENTAL BROADCASTING TABLES. *By Captain L. F. Plugge, B.Sc., F.R.Ae.S., F.R.Met.S.*
RECEPTION ON THE ULTRA SHORT WAVES. *By A. D. Cowper, M.Sc.*


THE CROWNING SUCCESS
OF THE RECORD-BREAKER

GRAND
XMAS No.
READY Dec. 15

NO INCREASE IN PRICE.

275,000 COPIES OF NO. 2 SOLD!

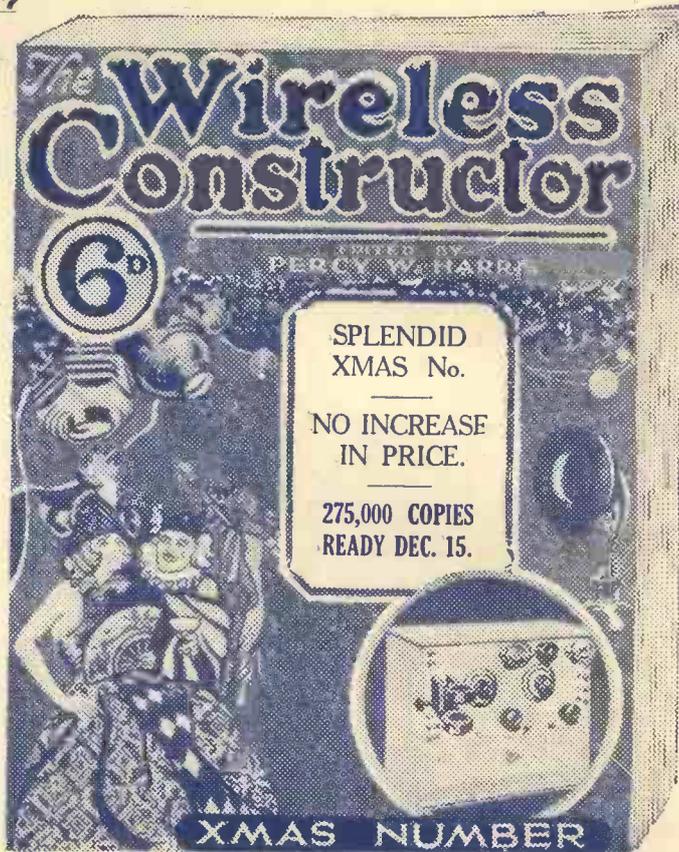Probably 300,000 of No. 3 will be printed.



THE GREAT 6d. MONTHLY

The Contents are even more pleasing and up-to-date than the splendidly illustrated cover which you will see on every Bookstall on December 15. Its 96 pages will help greatly to increase your pleasure during the festive season.

Young and old, beginners or experienced Wireless enthusiasts, will be surprised that a 6d. Monthly Magazine, constructional and instructional, yet simple to read, can contain so much of interest and value while giving pleasure and education combined.

A Set of outstanding merit in this issue is
THE "TWIN-VALVE" RECEIVER.

By JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.
Has received five B.B.C. Stations on a Loud-Speaker at Bedford!
A FREE BLUE PRINT of this Set is included in every copy.

The **Wireless
Constructor**

Obtainable from all Bookstalls, Newsagents and Booksellers,
or 8s. 6d. per annum, post free.

**RADIO PRESS, Ltd., Bush House, Strand,
LONDON, W.C.2.**

A small selection from the —

CONTENTS.

THE "TWIN-VALVE" RECEIVER.
By JOHN SCOTT-TAGGART, F.Inst.P.,
A.M.I.E.E.
A splendid Loud-Speaker Receiver for
the Local Station.

**A SIX-VALVE NEUTRODYNE RE-
CEIVER WITH THREE STAGES OF
HIGH FREQUENCY.**
Full Constructional Details.
By PERCY W. HARRIS.


A FOOLPROOF CRYSTAL RECEIVER.
By PERCY W. HARRIS.

**A LOUD-SPEAKER AMPLIFIER FOR
YOUR CRYSTAL SET.**
By E. REDPATH.

Hundreds of Practical Hints and Tips
for the Beginner and Experienced alike.

FREE BLUE PRINT
With every copy.

H. Armstrong

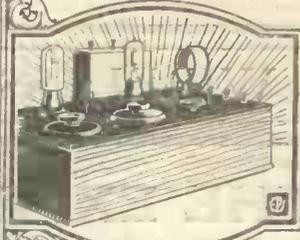

Contents

The Super-Heterodyne	735
BY EDWIN H. ARMSTRONG	
The T.A.T. Four-Valve Receiver	740
BY JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.	
In Passing	748
A New Reinartz Receiver	748
BY PERCY W. HARRIS	
Reception on the Ultra-Short Waves	754
BY A. D. COWPER, M.Sc.	
The Home Three-Valve Receiver	760
BY E. REDPATH	
American Broadcasting Stations	770
A Long-Distance Single-Valve Receiver	772
BY JOHN W. BARBER	
Marconi's Wireless Beam	781
BY LT.-COL. CHETWODE CRAWLEY, M.I.E.E.	
A Two-Valve Power Amplifier	786
BY JOHN UNDERDOWN	
How the Advent of Radio and Broadcasting has Changed our Christmas	797
BY D. J. S. HARTT, B.Sc.	
A Low-Loss Crystal Set	802
BY STANLEY G. RATTEE, M.I.R.E.	
Regular Programmes from Continental Broadcasting Stations	813
BY CAPTAIN L. F. PLUGGE, B.Sc., F.R.Ae.S., F.R.Met.S.	
Some Two-Valve Reflex Circuits	821
BY JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.	
Tested by Curves	845
Trouble Corner	166

Editor:
JOHN SCOTT-TAGGART,
F.Inst.P.

Assistant Editor:
PERCY W. HARRIS.

Staff Editors:
E. H. CHAPMAN,
M.A., D.Sc.
A. D. COWPER, M.Sc.
G. P. KENDALL, B.Sc.
R. W. HALLOWS, M.A.
S. G. RATTEE, M.I.R.E.

Scientific Adviser:
Prof. G. W. O. Howe,
D.Sc., M.I.E.E.
Advisory Editors:
Prof. R. WHIDDINGTON,
M.A., D.Sc.
Prof. C. L. FORTESQUE,
M.A., M.I.E.E.
Advertisement Managers:
BARCLAYS
ADVERTISING LTD.,
Eush House, Strand, W.C.2
Tel.—City 9911.

RADIO PRESS, LTD.,
"Publishers of "Wireless Weekly," and "The
Wireless Constructor,"
Bush House, Strand, W.C.2.
Telephone.—City 9911.

All correspondence relating to contributions is to be addressed to the Editor of "Modern Wireless."

Nothing contained herein is to be regarded as permission or encouragement to infringe any patent rights."

*Put the World
on your Dial.*




"I would like to congratulate you on the wonderful valves which you manufacture. They are the only distortionless and perfectly made valves on the market, and they are all and more than you claim for them.

"I was testing my one-valve set between 1 and 2 o'clock in the morning, using a MYERS Valve when I was surprised to hear telephony which I discovered to be KDKA, viz., Pittsburgh.

"There is one more thing I wish to say. It is this: Good luck to MYERS Valves, THE ONLY PERFECT RADIO VACUUM TUBE WHICH DOES ALL THAT ITS MAKERS CLAIM FOR IT."

Myers Practically
Unbreakable
Valves

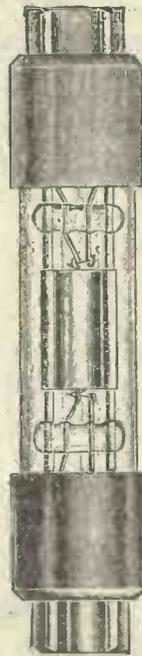It is the experience of well-known Amateurs that the MYERS is the only Valve which can be made to oscillate on 40 metres—Veb. Sab.



The valve's the thing. Long distance reception with the minimum of equipment—that's your aim. Get to earth as soon as you can—but fit suitable valves—MYERS.

There is no set about the success of the MYERS in Trans-Atlantic short wave work—undoubtedly the most critical and difficult side of wireless reception. Receivers fitted with ordinary valves suffer from short-distance paralysis due to their high internal capacity.

MYERS are low internal capacity valves. Their design brings the grid and anode leads out at opposite ends—a method of construction which gives you "Radio on Wings."

If you would span Continents, fit MYERS—they give you distance and POWER.

MYERS are obtainable from all dealers, or from the following distributors:

LONDON—The Dull Emitter Valve Co., 83, Pelham St., South Kensington, S.W. 7 (Kensington 3331).

MANCHESTER—R. Davis & Sons, Wireless Depot, Bilberry St.

LIVERPOOL—Apex Electrical Supply Co., 59, Old Hall St.

GLASGOW—Milligan's Wireless Co., 50, Sauchiehall St.

YORKSHIRE—H. Wadsworth Sellers, Standard Buildings, Leeds.

SOUTHERN COUNTIES—D.E.D.A., 4, Tenn's Road, Hove.

Universal, 12/6
4 volts .6 amp.
Dry Battery, 21/-
2 1/2 volts .25 amp.

Advertisement of Cunningham and Morrison, Wireless House, Victoria Street, S.W.1.

Barclays 413.

In replying to Advertisers, please use Order Form enclosed.

WIRELESS FROM A TO Z!

THE EXPERIMENTER'S DREAM COMES TRUE.

POLAR BLOK

SYSTEM OF SET CONSTRUCTION

You want to build a wireless set. How are you going to do it?

Buy separate parts and mount them on a sheet of ebonite and put up with its amateur appearance?

This method cramps expansion, and becomes more expensive with each mistake and with each change of circuit.

Or are you going to buy all the components mounted on small panels which by means of an easy method of assembly can be built easily and rapidly to form the larger panel of the complete set?




By this method costs are low and wastage is eliminated. If the set has annoying limitations, rebuild it to suit your amended requirements, whether they be calculated to affect range, selectivity, purity, or a combination of any of these features.

This is the Polar Blok method.

Your set never becomes obsolete. Wireless developments are followed step by step with ease and certainty. Its appearance is unexcelled. In performance it is reliable, robust and extremely pleasing.

Polar Blok has withstood the severe test of Polar Exploration and emerged with flying colours on a recent Polar Expedition. It is used on ships, where only the very best is possible. It carries the Polar Guarantee. You cannot do better than use it yourself.

BUILD EVERY CIRCUIT WITH POLAR BLOK

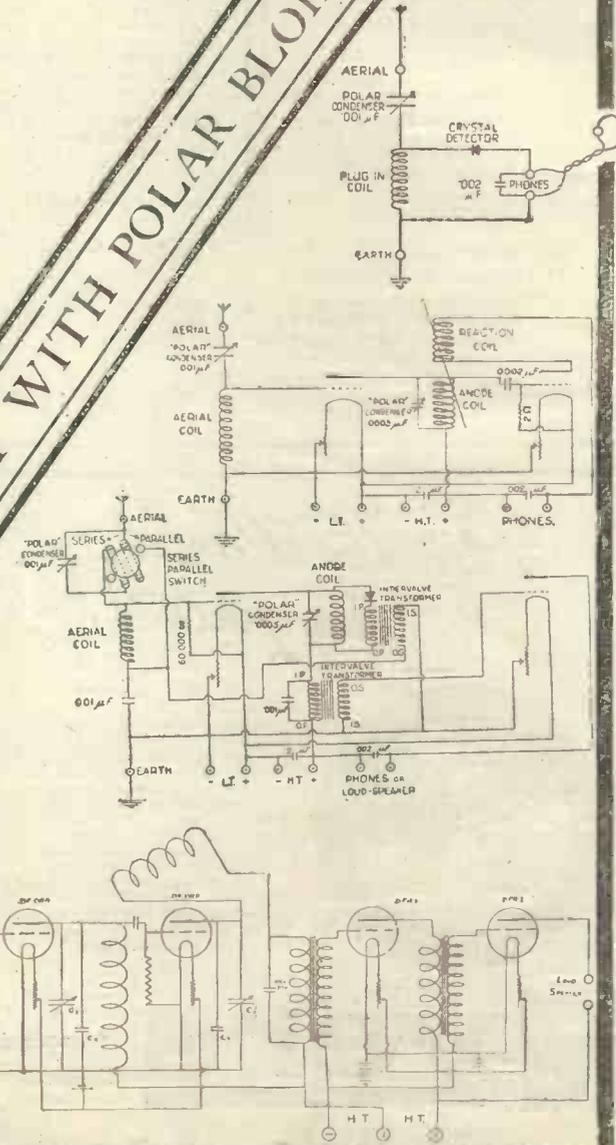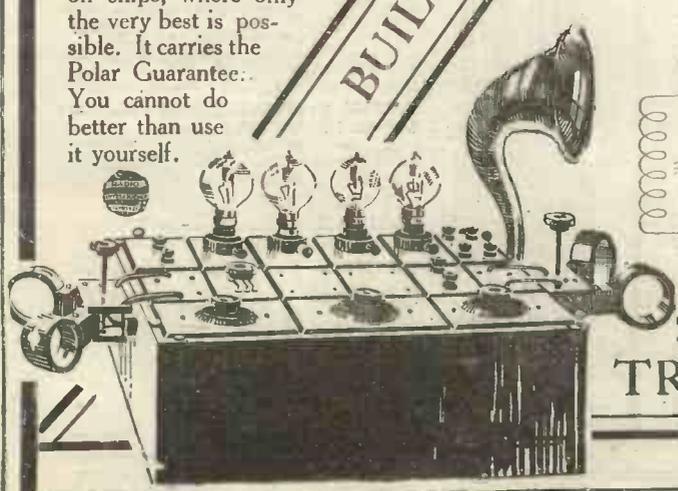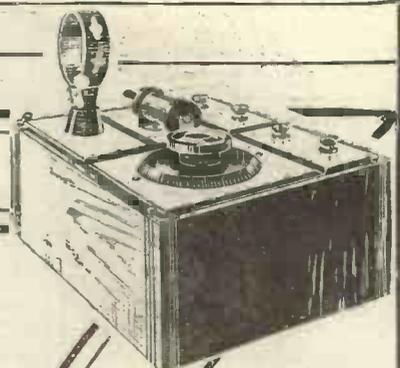

TRY THEM ALL IN TURN

RADIO COMMUNICATION CO., LTD., 34-35, Norfolk Street, Strand, W.C.2.



Major E. H. Armstrong.

THE SUPER-HETERODYNE.

Its origin, development and some recent improvements.

By Edwin H. ARMSTRONG.

We have much pleasure in giving from the pen of the well-known inventor himself an account of his work.



Mr. Harry Houck.

THE purpose of this paper is to describe the development of the super-heterodyne receiver from a wartime invention, primarily intended for the exceedingly important radio telegraphic direction-finding service in the Signal Corps of the American Expeditionary Force, into a type of household broadcasting receiver which, with our present vision, appears likely to become standard.

The invention of the super-heterodyne dates back to the early part of 1918. The full technical details of this system were made public in the autumn of 1919. Since that time it has been widely used in experimental work and is responsible for many of the recent accomplishments in long-distance reception from broadcasting stations. While the superiority of its performance over all other forms of receivers was unquestioned, very many difficulties rendered it unsuitable for use by the general public and confined it to the hands of engineers and skilled amateurs. Years of concentrated effort from many different sources have pro-

duced improvements in vacuum tubes, in transformer construction, and in the circuits of the super-heterodyne itself, with the result that at the beginning of the present month there has been made available for the general public a super-heterodyne receiver which meets the requirements of household use.


A Problem.

It is a peculiar circumstance that this invention was a direct outgrowth to meet a very important problem confronting the American Expeditionary Force. This problem was the reception of extremely weak spark signals of frequencies varying from about 500,000 cycles to 3,000,000 cycles, with an absolute minimum of adjustments to enable rapid change of wavelength. The technical difficulties of this problem are now so well known that it is not necessary to consider them. Round in England and Latour in France, by some of the most brilliant technical radio work of the war, succeeded in producing radio frequency amplifiers covering the band from 500,000 to 1,000,000 cycles and though covering a much-

more limited band, amplifiers operating on 2,000,000 cycles had been constructed. These results had been accomplished by the use of vacuum tubes and transformers of a minimum capacity. As this apparatus was used in the highly important intelligence services, all information was carefully guarded. When the United States entered the war, the facts that it was necessary to produce sensitive receivers for short wavelengths and that valve capacity would prove the bar to a straightforward solution of the problem were not known in that country. As a result, no attention was paid to the capacity in the type of valve which was adopted, and while the valve met the requirements of the lower frequencies admirably, it was impossible to use it effectively for the frequencies of importance in the direction-finding service.

The Solution.

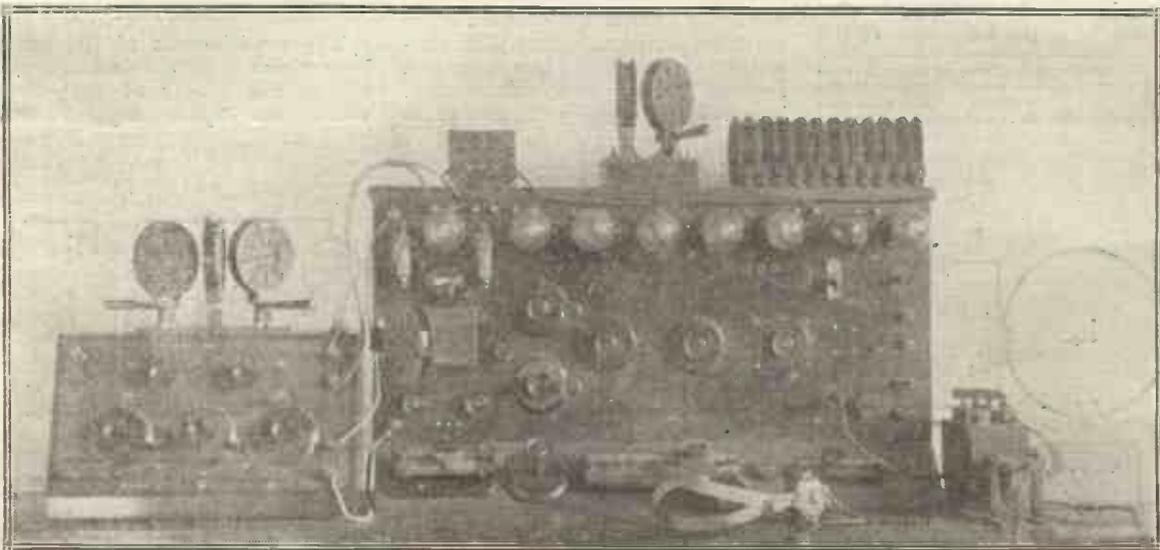During the early part of 1918, through the courtesy and energy of General Ferrié and his staff, the American Expeditionary Force was supplied with apparatus of French




This interesting 10-valve supersonic heterodyne receiver was designed by Mr. Kenneth Alford.

manufacture. It was quite apparent, however, that this source of supply could not be a permanent one, and a solution of the problem became essential. During the early part of 1917, I had made a careful study of the heterodyne phenomena and their effect on the efficiency of amplification. With this work freshly in mind, the idea occurred to me to solve the problem by selecting some frequency which could be handled by the valves available, building an effective amplifier for that frequency, and then transforming the incoming high-frequency to this readily amplifiable value by some converting means which had no low limit; preferably the heterodyne and rectification. The principles and advantages of this method were explained in a paper presented before this Institute (1) and are now so well known that no further explanation is required here.

Experimental Work.

After much experimental work, an eight-valve set was constructed consisting of a rectifier valve, a separate heterodyne oscillator, three intermediate frequency amplifiers a second rectifier or detector and two audio-frequency stages. The intermediate frequency stages were coupled by tuned air-core transformers set for a frequency of about 100,000 cycles, with an adjustment for controlling the regeneration. The amplification of voltage measured at the input of the second detector with the amplifier just below the oscillating point, was about equivalent to a radio frequency amplification of 500. It gave satisfactory results except that the inclusion of a reaction control on the intermediate frequency amplifier made skilled handling necessary, as the adjustment of the frequency of the

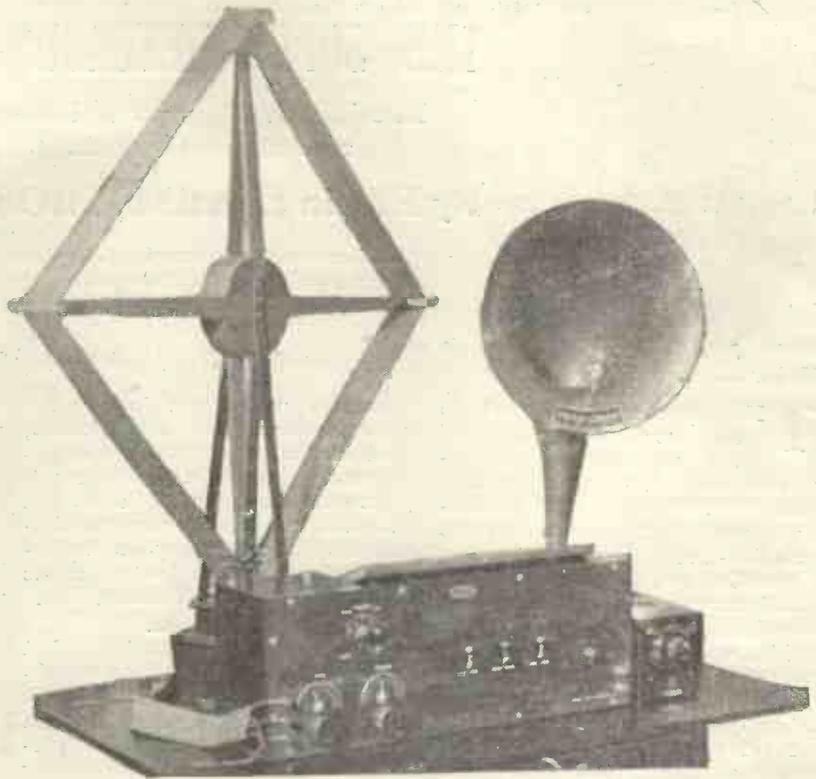(1) This amplification is based on the ratio of the voltage applied to the second detector to the voltage at the frame terminals. The intermediate frequency amplification is unknown.



The Western Electric Co.'s 7-valve super-heterodyne set uses Weeco valves.

oscillator changed the plate current of the detector valve and this, in turn, varied the resistance which that valve introduced into the amplifier system and upset the reaction adjustment.

Performance.

The Armistice ended development at this point, but in the autumn of 1919, for the purpose of determining the results obtainable by pushing the super-heterodyne method of reception to the limit, a resistance-coupled intermediate frequency amplifier consisting of five high- μ (amplification factor) valves was constructed. The voltage amplification of these

five stages was probably between 5,000- and 10,000-fold. While greater amplification could have been obtained, the sensitiveness of a set composed of a two-valve frequency converter, a five-valve intermediate frequency amplifier, a detector, and one stage of audio, was such that on a three-foot (one-metre) frame, the sole criterion of reception was simply whether the signal was stronger than the atmospheric disturbances.

Sensitivity.

The sensitiveness of the super-heterodyne was demonstrated during the winter of 1919-1920, when the spark signals from

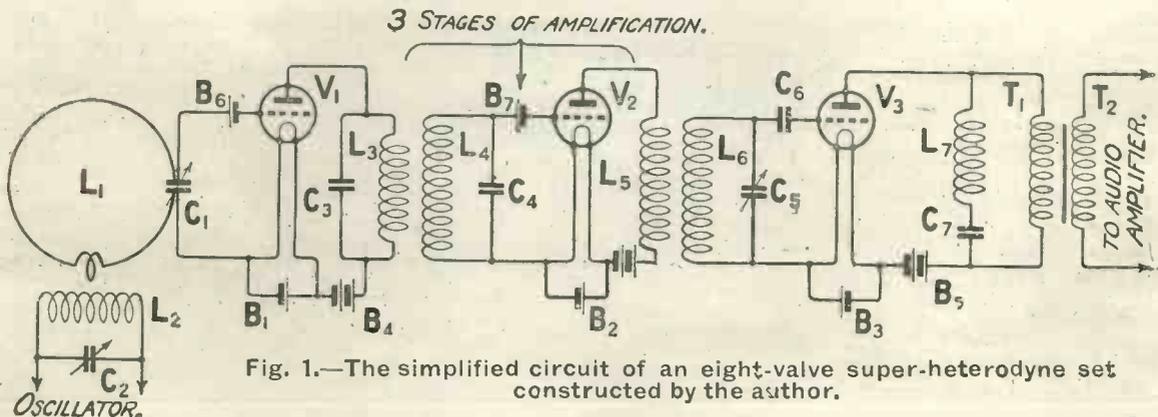


Fig. 1.—The simplified circuit of an eight-valve super-heterodyne set constructed by the author.

amateur stations on the West coast and telephone signals from destroyers in Southern waters were received in the vicinity of New York on a three-foot (one-metre) frame. Probably the most striking demonstration of the capabilities of the method occurred in December, 1920, when Paul F. Godley, at Ardrrossan, Scotland, received the signals of a large number of amateur stations located in the

dyne offered the ideal solution. This solution lay in the construction of an intermediate frequency amplifier which would amplify a given frequency and a band 5,000 cycles above and below it and which would cut off sharply on either side of this desired band. The adjustments necessary to accomplish this could all be made by skilled men, and the only operations left for the user would be the

to 30,000 cycles, a second detector valve, and two-stages of audio frequency amplification. UV-201 valves were used. To prevent the intermediate frequency amplifier from oscillating, each stage was shielded separately. The use of a radio frequency stage ahead of the first detector possesses a number of advantages, but the chief one is in eliminating the reaction between the frame circuit and the oscillator circuit.

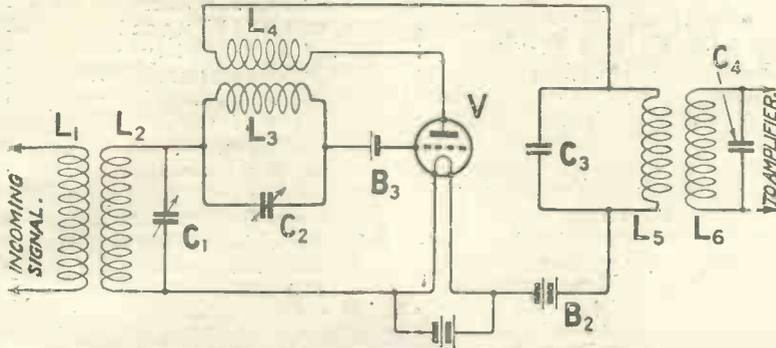


Fig. 2.—Houck's arrangement whereby one valve functions as the self-rectifier and the self-heterodyne oscillator.

United States, many of them being spark stations. The super-heterodyne used by Godley consisted of a regenerative valve for the rectifier, a separate oscillator, four stages of resistance-coupled intermediate frequency amplification, a second rectifier, and two stages of L. F. While it is difficult to state definitely the actual voltage amplification obtained, it appears to have been between 3,000- and 5,000-fold.

Simple Tuning.

With the coming of the broadcasting art, and with the great increase in the number of stations and the consequent interference, the super-heterodyne began to take on a new importance—an importance which was based not on its superior sensitiveness nor on its selectivity, but on the great promise which the method offered in simplicity of operation. It was, and still is, the standard practice to furnish the public with receivers equipped with a variety of tuning adjustments for the purpose of amplifying the desired band of radio frequencies and excluding all others. As a matter of fact, many more adjustments than are on receivers should be used—more than could be placed in the hands of the average user. It would obviously be of the greatest importance if in some way these tuning adjustments could be made in the laboratory by skilled engineers and sealed, leaving some relatively simple adjustment for the hands of the operator. The super-hetero-

two adjustments necessary to change the incoming frequency down to the band of the amplifier—adjustments which are not dependent on each other, which are of extreme simplicity, and which can be made equally well by the novice or the engineer. To determine just what could be accomplished along these lines, the writer, working in conjunction with Mr. Harry Houck, constructed during the spring of 1922 a set designed for the maximum usable sensitiveness and selectivity.

Arrangement Used.

The arrangement used consisted of one radio frequency stage (non-tuned transformer) a rectifier valve, and oscillator valve (used as a separate heterodyne), a three-stage iron-core transformer-coupled intermediate frequency amplifier designed to cover a band of 20,000

Coupling Effects.

Experience with the original type had shown that when an oscillator of ordinary power was used, it was necessary to couple it rather closely with the frame circuit in order to insure a sufficiently strong heterodyne current. This close coupling affected the tuning of both circuits, an adjustment of one changing the setting of the other. To avoid this trouble and to produce a system wherein a station could always be tuned in on exactly the same settings, a single stage of radio frequency amplification (non-tuned transformer) was used, and the oscillator was coupled to this transformer. This arrangement eliminated the reaction, reduced the radiation to a minimum and, in addition, removed the damping of the first rectifier from the loop circuit and improved its selectivity.

High Selectivity.

The results obtained with this set were about as expected. On a three-foot (one metre) frame, the factor determining the reception of a station was solely whether the signal strength was above the level of the atmospherics. The selectivity was such that stations which had never been heard before on account of blanketing by local stations, were received without a trace of interference. While the

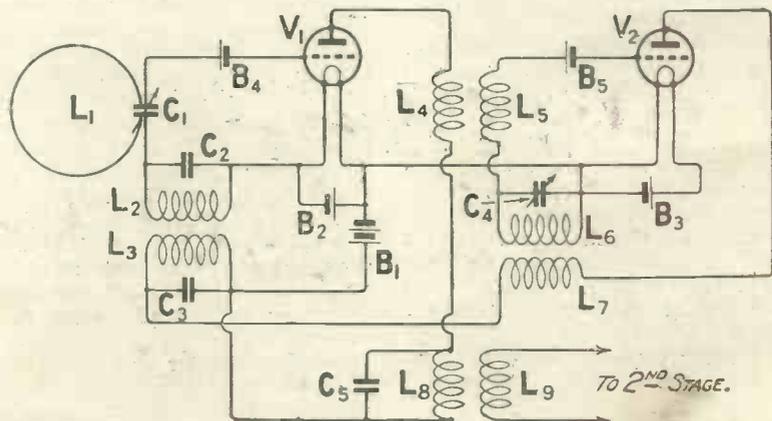


Fig. 3.—The radio-frequency amplifiers here act in a dual capacity.

performance of the set was much superior to any other receiver, it was apparent that the cost of construction and maintenance was prohibitive. The single item of a ten-ampere filament current will give some idea of the size of the storage battery and auxiliary apparatus required.

With the coming of the low filament consumption, or dry battery type of valve, the possibilities of producing a super-heterodyne for household use were tremendously improved. A set was remodelled for the WD-11 valve, and its sensitiveness was brought to about the same value as obtained with the bright-emitter valves. This was a long step forward, but still the cost was prohibitive.

Eliminating Valves.

It has been apparent ever since the question of the application of the super-heterodyne to broadcasting had been considered; that there were too many valves performing a single function which were quite capable of performing a double one. The most outstanding case is that of the separate heterodyne oscillator. In view of our knowledge of the self-heterodyne, it appears quite obvious to perform the first rectification by means of a self-heterodyne oscillator and thereby save a valve. As a matter of fact, this was one of the very first things tried in France, but, except for very short wavelengths, it was never very successful when a high intermediate frequency was necessary. The reason was this: If a single tuned oscillating circuit was used, the mis-tuning to produce the proper beat caused a loss of signal strength which offset the gain of a valve. If two tuned circuits were used on the oscillator, one tuned to the signalling frequency and the other arranged to oscillate at the heterodyne frequency, then on account of the relatively small percentage difference in frequency a change in the tuning of one circuit changed the tuning of the other. The solution of this problem was made by Houck, who proposed an arrangement so simple and so effective that it completely solved the problem. Houck proposed to connect two tuned circuits to the oscillator, a simple circuit tuned to the frequency of the incoming signal and a regenerative circuit adjusted to oscillate at such a frequency that the second harmonic of this frequency beating with the incoming frequency produced the desired intermediate frequency. The general arrangement is illustrated by Fig. 2.

Circuit Diagram.

In the diagrammatic illustration, circuit L_2C_1 is tuned to the incoming signal, circuit L_3C_2 is tuned to one-half the incoming frequency plus or minus one-half the intermediate frequency, and the circuits L_3C_3 and L_6C_4 are both tuned to the intermediate frequency. The operation of the system is in line with ordinary self-heterodyne action. By reason of the asymmetrical action of the valve, there are created in the circuits a variety of harmonics. The second harmonic combines to produce beats with the incoming signals of the desired intermediate frequency, the valve rectifies them to produce the desired intermediate frequency and, through L_3C_3 and L_6C_4 , the new frequency is supplied to the amplifier. On account of the fact that circuits L_2C_1 and L_3C_2 are tuned to frequencies differing by approximately 100 per cent., a change

rectified by the second valve, producing a current of the intermediate frequency which is applied to the grid of the first valve, amplified therein, and passed on to the second stage of the intermediate amplifier. A more practical method of carrying out this idea is illustrated in Fig. 4. In this arrangement, a secondary of the first intermediate frequency transformer is connected to the grid of the first valve and in parallel with the frame circuit. Otherwise, the arrangements of Figs. 3 and 4 are identical. The parallel type of circuit arrangement eliminates a variety of reactions which would give rise to oscillations of various frequencies and in addition, prevents the reception of long wave signals by the intermediate frequency amplifier. When this development had been completed, improvements in the design of the intermediate frequency



An Interesting supersonic heterodyne receiver.

in the tuning of one has no appreciable effect on the tuning of the other. This arrangement solved the oscillator problem and, in addition, practically eliminated radiation.

The next step in the reduction of the number of valves was to make the radio frequency amplifier perform the function of amplifying intermediate frequency as well. This can be done with none of the difficulties inherent in audio frequency amplification, as the very small amplitudes of voltage handled by the first valve preclude the possibility of the grid becoming positive with respect to the filament. The general arrangement of circuits for carrying this out is illustrated by Fig. 3. In this arrangement the signals received by the frame are amplified at radio frequency by the first valve and applied to the grid of a second harmonic oscillator by means of an untuned radio frequency transformer. The combined signalling and heterodyning currents are then

transformers made it possible to obtain with two stages all the amplification which could be used.

Overloading.

On account of the high amplification, signals from local stations overload the second rectifier and introduce distortion. Control of the amount of intermediate frequency amplification is essential. While there are numerous methods equally effective, the simplest one appears to be the control by means of the filament temperature of the second intermediate frequency amplifier.

The features just described were all incorporated in the receiver. The set measured 18 in. by 10 in. by 10 in. (45.6 by 25.4 by 25.4 cm.) and was completely self-contained—the batteries, frame aerial, and speaker mechanism being enclosed in the box. The results were highly satisfactory, and loud-speaker signals (at night) in the vicinity of New York were obtained from

stations in Chicago and Atlanta. It demonstrated that not only could a household receiver of the super-heterodyne type be built, but that the first practical solution of the portable set was at hand.

A Commercial Form

In this form, the capabilities of the set were brought to the attention of the Westinghouse Electric and Manufacturing Company and the Radio Corporation of America a little over a year ago. Its possibilities were instantly visualised by Mr. David Sarnoff, who immediately took steps to concentrate the resources of the research laboratories of the Radio Corporation of America, the Westinghouse Electric and Manufacturing Company, and the General Electric Company on this new development.

and ease of operation of the set may be gathered from an incident during the Transatlantic broadcasting tests of November and December, 1923.

2 LO Received

On December 1, two ladies, neither having any technical radio knowledge, received loud-speaker signals from station 2LO, London, England. This was accomplished at Merrimac, Massachusetts, and probably constitutes a record for the first reception from Europe with a portable receiver. With the same set and a three-foot (one metre) frame, loud-speaker signals from broadcast stations on the Pacific Coast were received in the vicinity of New York on an average of three or four times a week. The factor determining reception was simply whether the signal strength

Interference Abroad.

To the Editor of MODERN WIRELESS.

SIR,—You may be interested in the following notes re atmospheric interference abroad. As is only to be expected, atmospherics abroad are vastly different from those at home. Doubtless the great ionisation of the atmosphere in the tropics is in no small measure responsible. The disturbances are at times of a degree undreamt of by the majority of listeners-in. As a case in point, I had once to communicate with a certain coast station in the Dutch East Indies. The coast operator was using a multi-valve receiver. I was at the time only seven miles distant from him, and was endeavouring to get a code message through. Although I was using a Marconi 1½ K.W. transmitter, on full power, he was utterly unable to read me! Those of your readers who live near the coast will know that a Marconi transmitter can make itself heard under most conditions. Considering that my aerial was 250 feet long, and 60 feet above the wireless room, it says something for the power of those "X's." I had eventually to close down altogether, as lightning was continually striking the aerial. Such conditions are quite common in the tropics.

On the other hand, excellent ranges are sometimes obtained. It is no uncommon thing for a ship's crystal receiver to pick up FL time signals at over 3,000 miles. As regards interference on long waves, tropical conditions vary considerably. Sometimes interference is more marked on long waves, sometimes it is less. No hard and fast rule can be laid down. It is probably on account of atmospherics that there is so little broadcasting outside of Europe and U.S.A.

Hoping these few remarks may, in some degree, illustrate conditions abroad,—Yours truly,

J. ROBINSON.

P.S.—I am a regular reader of your excellent journal, from which I receive much information useful to me. I wish you every success. S.S. Arabestan, Colombo.

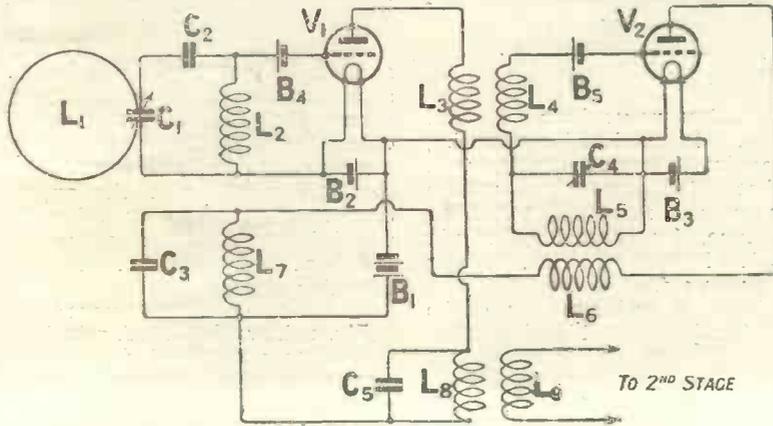


Fig. 4.—A more practical arrangement of Fig. 5.

From that point on it passed into a new phase—that of placing an invention in a commercial form.

The Final Set

In the limited time available, this was a most extraordinarily difficult proposition, and credit for its accomplishment is due to the untiring efforts on the part of the engineers of the above organisations. Many improvements and some radically new ideas of designs have been introduced, but it is the privilege of those responsible for them to present these. In the final development, an additional stage of audio frequency amplification was added in order to insure operation within steel buildings, particularly those within the city limits where signals are relatively very weak compared to suburban locations. This makes a six-valve set, but six valves can be readily operated on dry batteries and the increase in sensitiveness is well worth the extra valve. Some idea of the sensitiveness


was above the level of the atmospheric disturbances.

The type of super-heterodyne described is now available to the public in the two forms. Each of these sets incorporates the arrangements herein described. Their sensitiveness is such that, with a two-foot (61-cm.) frame and an unshielded location, the atmospheric disturbances are the criterion of reception. Here we reach a milestone in the development of broadcast receivers, for no increase in the distance of reception can now be obtained by increase in the sensitiveness of the receiver. Unless the power of transmitting stations is increased we are about at the limit of the distance which can be covered. Future improvement of this receiver will lie along the line of selectivity and simplifying the construction.

The above article is reproduced from the Proceedings of the Institute of Radio Engineers, Vol. 12, No. 4, October 1924. In considering the theoretical diagram given, it should be understood that these are shown in the conventional American fashion.

"EARLY WIRELESS HISTORY."

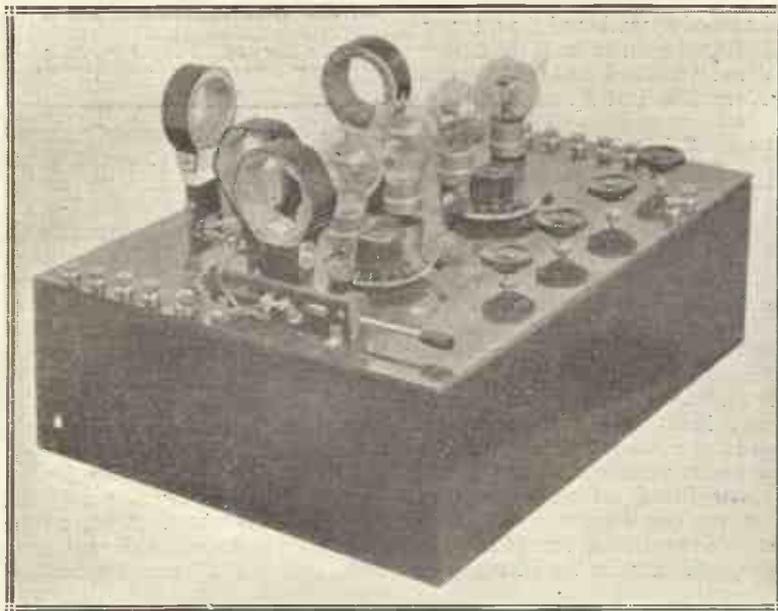In this article, which appeared in October MODERN WIRELESS, Mr. Hinks has asked us to point out that he is not an M.I.E.E., but a member of the Junior Institute of Engineers.



With coils in position the set presents a handsome appearance.

Introductory

IN the last issue of MODERN WIRELESS I went into the whole theory of the T.A.T. principle as a solution of the multi-stage high-frequency system.

For the benefit of new readers it may be as well to summarise the various points in the article. It was explained that the great trouble in multi-stage high-frequency amplifiers was the fact that one or more of the valves contained both a tuned grid and a tuned anode circuit, and that under these conditions self-oscillation of that valve was extremely likely, owing chiefly to capacity coupling, not only inside the valve itself but due to the capacity effect between condensers, leads, coils, etc. Intervalve transformers do not overcome this trouble even when the secondaries of the transformers are tuned, because a transformer, especially if the coupling is tight, acts in very much the same way as a tuned anode circuit when the secondary winding is tuned, and the tendency to oscillate increases as the coupling is tightened. This coupling between the primary and secondary of the high-frequency transformer helps considerably towards stability, but on the other hand, if this coupling is too loose, there will be an excessive loss in signal strength, owing to a falling off of the energy transfer from primary to secondary.

Perfect Stability

I obtained perfectly stable high-frequency amplification covering a multitude of stages by a method which, simple as it may seem, has

nevertheless never been proposed before. It consists in separating tuned circuits by an aperiodic circuit so that grid and anode circuits of the same valve are not both tuned. I can tune, for example, the grid circuit of the first valve, making the anode circuit of the first valve aperiodic, a resistance or choke coil forming the high-frequency part of the anode circuit of the valve. The high-frequency potentials across this choke coil or resistance are then communicated to a second valve in the anode circuit of which is a tuned anode circuit; the next valve acts as a detector, or if it acts as a high-frequency amplifier, then the anode circuit of this third valve will have a choke coil or a resistance. The next valve, if a further stage of H.F. amplification is desired, would have a tuned circuit.

The T.A.T. Four-Valve Receiver

Designed by

JOHN SCOTT-TAGGART,

F.Inst.P., A.M.I.E.E.

By doing this we have the T.A.T. system, the letters indicating tuned, aperiodic, tuned, this implying, of course, that the tuned and aperiodic circuits alternate so that in the case of no single valve are both the grid circuit and the anode circuit tuned; one or other is tuned, but both of them are never tuned at the same time to the incoming signal.

A 3-Valve Arrangement

Fig. 1 shows the T.A.T. principle applied to a three-valve set using two stages of high-frequency amplification and reaction, but no low-frequency amplification. It will be seen that the first valve V_1 acts as a high-frequency amplifier, the coupling being provided by the choke coil Z , which, for wavelengths over 1,000 metres, e.g., when receiving 5XX the high power station, may be replaced by a resistance R_6 of, say, 100,000 ohms resistance. The high-frequency potentials established across the choke


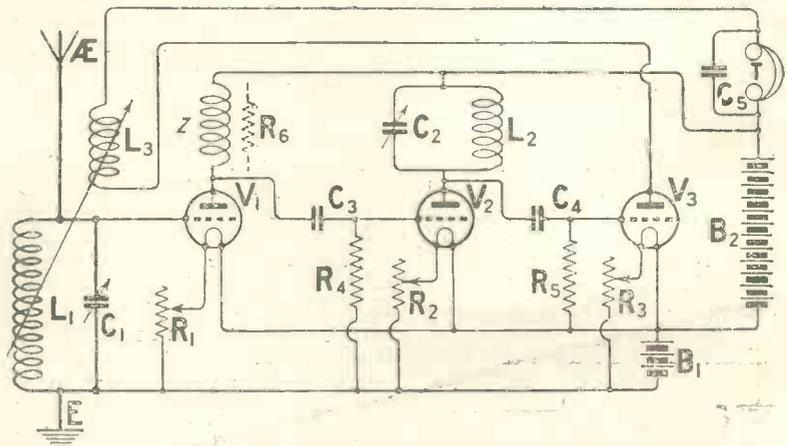


Fig. 1.—A three-valve T.A.T. circuit with two H.F. stages.

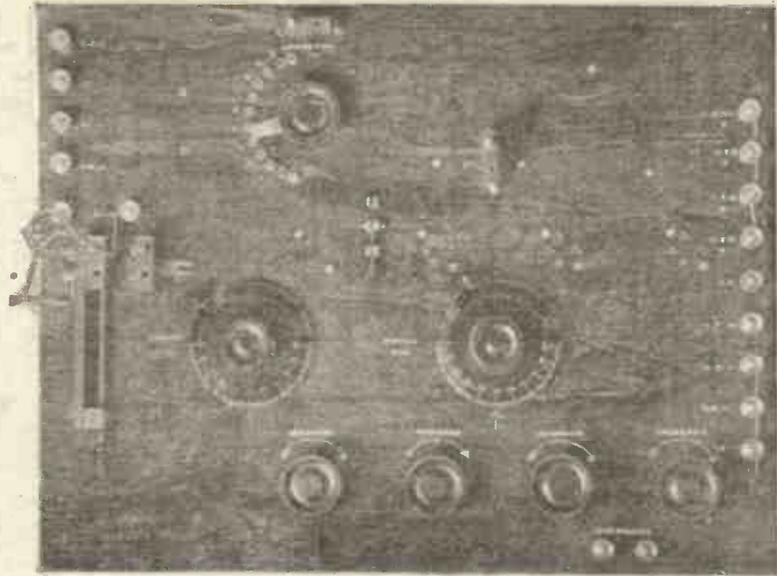Full
 constructional
 details of a
 very distinctive
 2 H.F.
 Receiver.



From the photograph the disposition of the components is clearly seen.

Z or the resistance R_6 , as the case may be, are communicated to the grid of the second valve V_2 which is the second high-frequency amplifier. In the anode circuit of this amplifier we have the circuit $L_2 C_2$ tuned to the incoming signal, and the potentials across this circuit are now communicated to the grid of the valve V_3 , which acts as a detector. In the anode circuit of this valve we have, not only the telephones T, but also the reaction coil L_3 which is coupled to the aerial inductance L_1 , thereby introducing a reaction effect, not only into the aerial circuit but also into the tuned circuit $L_2 C_2$.

The 4-Valve Circuit

The four-valve T.A.T. receiver which I have designed and described in what follows, works on a similar circuit, the general scheme being similar to that of Fig. 2 which shows the use of a variable choke coil L_3 . It will be seen that

Fig. 2 is, in general, similar to Fig. 1, but that a stage of low-frequency amplification is added so that a loud-speaker may be used.

Choke Coil Sizes

It will be noted in Fig. 2 that the choke coil L_3 is shown variable; obviously a different size choke coil will be required for a different range of wavelengths. For example, whereas for short waves a small choke coil will be found quite satisfactory, for receiving long wave stations a much larger choke coil will be necessary.

Another factor which enters into the question is that there is always a rough adjustment where the best transfer of energy will be obtained. To speak about an aperiodic choke coil is, of course, not altogether accurate, because there is always a certain amount of "tuning" in a

choke coil, but nevertheless, in the apparatus about to be described, and in the system generally, a very fair approximation to aperiodicity is obtainable with the result that great stability is obtained combined with ease of adjustment.

The Aperiodic Stage

I explained in the original article that the aperiodic stage of high-frequency amplification does not give as good signal strength as the tuned stage, although I would like to qualify this statement in regard to the longer wavelengths. On 5XX I find that a resistance substituted in place of L_3 , thus producing the circuit shown in Fig. 3, will give nearly as good results as if a choke coil of 300 turns is employed. In this case there is no question that the two valves are giving a full measure of high-frequency amplification, and this combined with perfect stability.

It was made perfectly clear in the original article that the T.A.T. system is not merely adding one method of high-frequency amplification after a different method. Others, of course, have combined different methods, but the method of sandwiching described in the article for stabilising multi-stage H.F. receivers is as novel as it is effective.

It will be clear to those who read the original article that the peculiar advantages of the T.A.T. system become more and more pronounced as additional stages of high-frequency amplification are used. I am only proposing in this article to describe a four-valve receiver using two stages of H.F., a detector

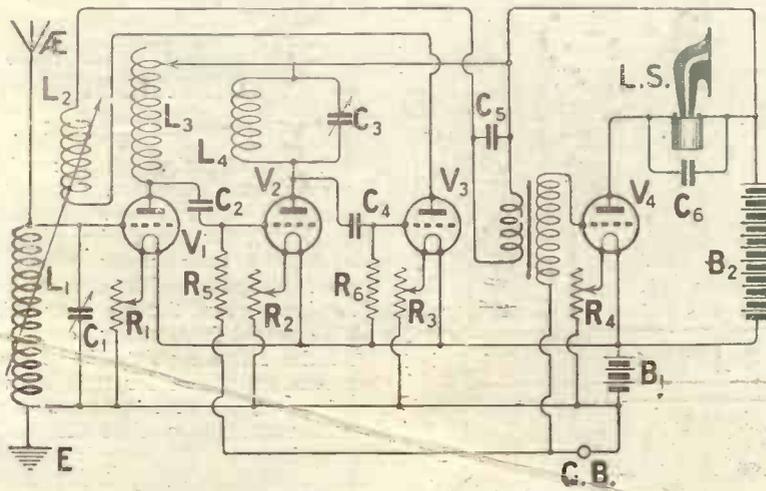


Fig. 2.—The general theoretical circuit of the receiver.

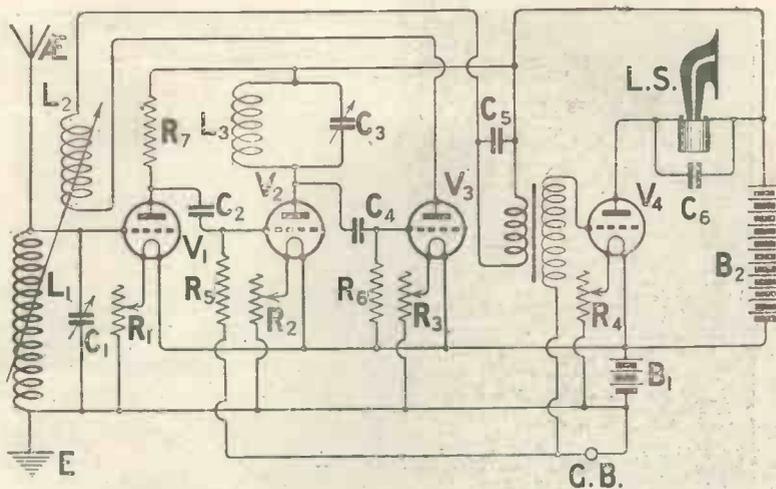


Fig. 3.—On the higher waves the choke coil may be replaced by a resistance.

valve and one L.F. valve. This forms an excellent combination for working a loud-speaker, and if the receiver is suitably placed, several, or all, the main B.B.C. stations, as well as many foreign stations, should be heard on a loud-speaker. For a Continental or an experimenter in a foreign country desiring to receive 5XX, the set should prove ideal. Our very many readers on the Continent and in Denmark, Norway and Sweden will probably take even more interest in the set than British experimenters, whether they propose to receive 5XX or the 300 to 500 metre stations, because in their case range is a vital matter and two stages of H.F. amplification are really necessary for good working.

In order to test the set effectively at a suitable distance from 2LO,

I took the set to Bedford, which is approximately 50 miles from London, in order principally to test the signal strength from 2LO on small and average aerials. Even though only one stage of low-frequency amplification is used (two L.F. stages are used on most loud-speaker sets) it was mere child's play to receive 2LO on almost any kind of an aerial at this distance, an anode voltage of 78 volts being employed.

Two Controls

It will be seen that there are only two controls, the condensers C_2 and C_4 and, of course, the reaction. The variable choke L_3 was not in the least critical. As a matter of fact, I made this choke of resistance wire, namely 40 gauge silk-covered Eureka, wound on a tube mounted under the panel. This

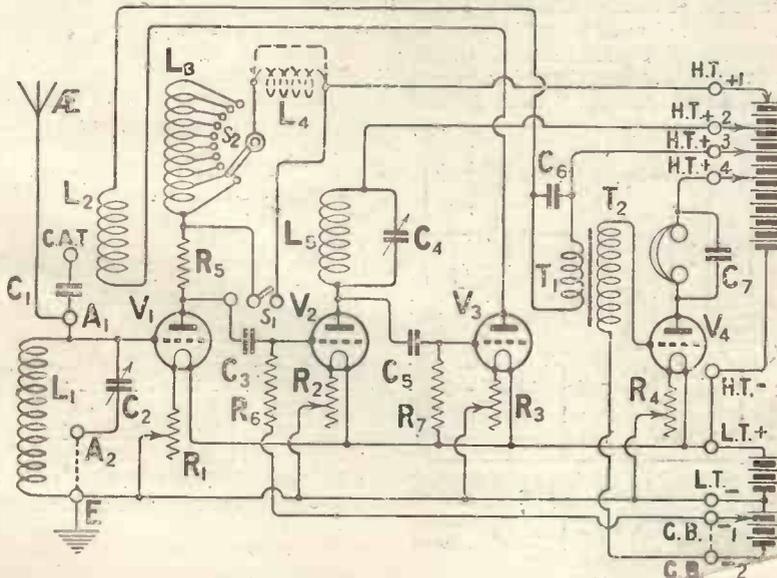


Fig. 4.—Shows the practical circuit used in the receiver described.

particular choke, to save time, was the same one used by Mr. G. P. Kendall in his Radio Press Envelope No. 3, which describes a very effective set in which, as many of our readers know, the coupling between the first and second valve is entirely by means of a choke coil, no tuned anode circuit being employed in the set. The tapped choke coil method of coupling used in Mr. Kendall's set, and also used commercially by, I believe, Burndepts Limited, in some of their receivers, has many points in its favour in connection with simplicity of operation, and when used in combination with tuned circuits, as in the T.A.T. receiver, not only is excellent amplification given but perfect stability is obtained, although, as I have indicated above and in my preceding article, the simplicity of choke coupling is accompanied by some small loss as compared to an efficient tuned anode circuit.

The Secret of Success


In an ordinary single H.F. valve receiver the use of a choke coupling is usually a compromise, but in the T.A.T. circuits it is the secret of the success of the whole receiver. In all cases I prefer to follow a choke coupling by a tuned anode coupling, so that when using a T.A.T. receiver it is desirable to use either two, four, six or eight stages of high-frequency amplification, rather than three, five or seven.

The choke, or resistance, is used to connect together tuned circuits, so that obviously it is desirable to end up with a tuned circuit or, put another way, it is desirable to get the maximum number of tuned circuits with the minimum number of aperiodic circuits, and this occurs with an even number of high-frequency amplifying valves.

CONSTRUCTIONAL DETAILS.

Components Required

In constructing this receiver care should be taken as to the quality of the components employed, for one faulty piece of apparatus may easily result in poor reception with the finished receiver, even though everything else were functioning correctly. In the following list of the components required for building the set, manufacturers' names have been included so that the reader may have no difficulty in copying the receiver in every detail should he so desire.

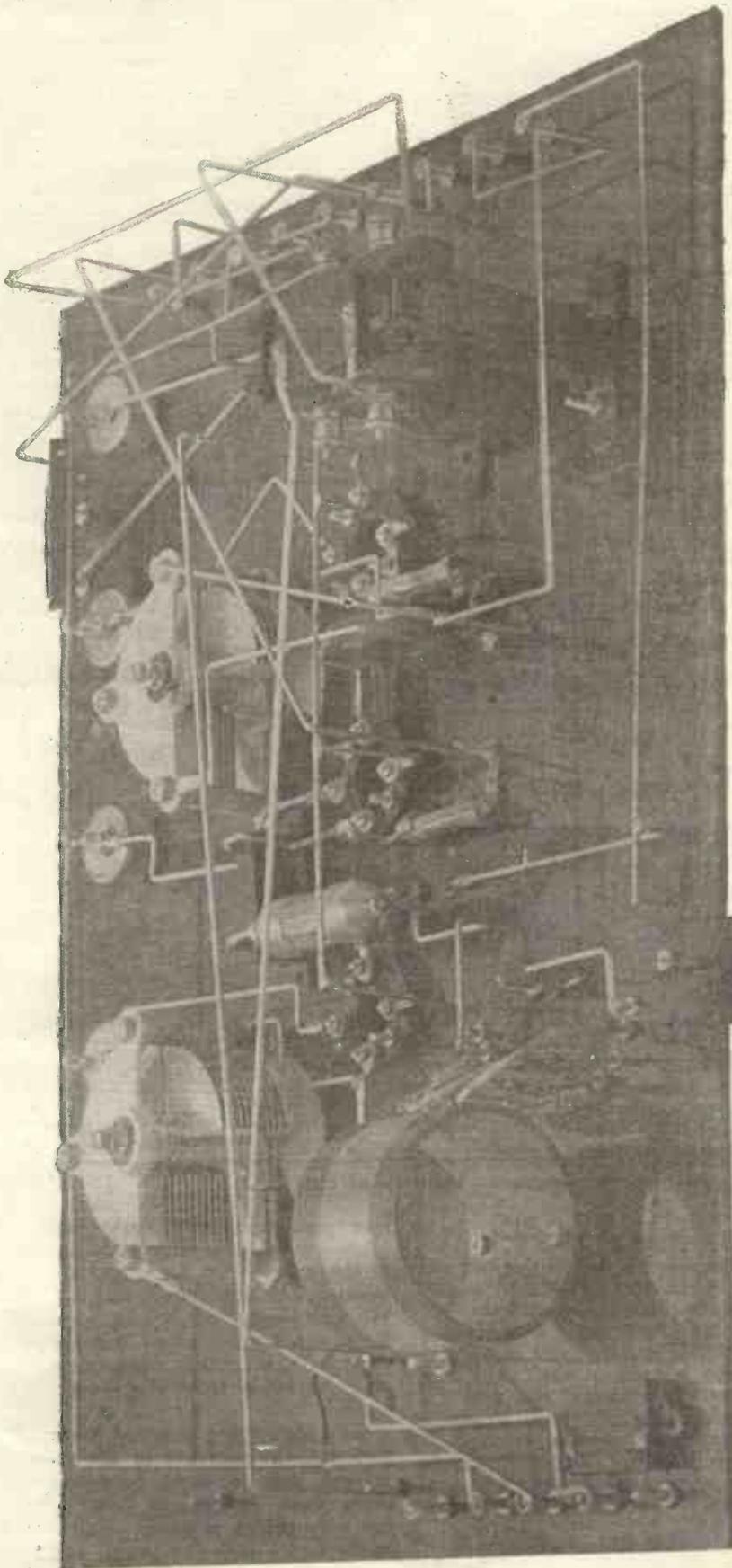

The wiring is clearly seen here.

Ebonite panel, 18 in. by 14 in. by 3-16 in. (Radion A., American Hard Rubber Co.).

Cabinet of suitable size for above panel.

2-coil holder. (Beard and Fitch.)

1 0.0005 μ F variable condenser with vernier. ("Utility," Wilkins and Wright.)

1 0.0003 μ F variable condenser with vernier. ("Utility," Wilkins and Wright.)

1 L.F. inter-valve transformer. (Radio Instruments, Ltd.)

4 valve holders. (H.T.C. Electrical Co., type C.)

4 filament rheostats. (Wates Bros., "Microstats.")

1 0.0001 μ F fixed condenser. (Dubilier.)

2 0.0003 μ F fixed condensers. (Dubilier.)

1 0.001 μ F fixed condenser. (Dubilier.)

1 0.002 μ F fixed condenser. (Dubilier.)

2 2-megohm gridleaks with clips. (Dubilier.)

1 100,000 ohm resistance. (Dubilier.)

2 fixed coil sockets. (Burne-Jones and Co., Ltd.)

1 single pole, double throw, knife switch for panel mounting.

1 nickel-plated switcharm, 10 nickel-plated contact studs and 2 switch stops. (K. Raymond.)

1 tapped reactance coil. (Burne-Jones and Co., Ltd.)

17 W.O. type terminals. (K. Raymond.)

Short length of rubber tubing.

Quantity of square section tinned copper for wiring.

Short length of rubber-covered flexible wire.

About 2 dozen 6 B.A. screws and nuts.

1 packet of Radio Press panel transfers.

Panel Drilling

A number of firms now sell ebonite of guaranteed quality, and though it may be possible to purchase cheaper ebonite which is not guaranteed, this proceeding is not advised, for the troubles arising from the use of cheap semi-conducting ebonite are numerous and not always easily traced.

Having purchased, then, a piece of guaranteed ebonite of the correct size, drilling may be commenced. The drilling diagram is given in Fig. 5, and with its aid all the necessary holes may be drilled save for a few whose positions should be found when all the components are to hand.

Mounting the Components

This is easily accomplished with the aid of the photographs and the drilling and wiring diagrams, to which reference should be made.

The following components are not mounted until wiring is in

progress, for reasons which will shortly become obvious:—

The five fixed condensers.

The gridleak shown in the centre of the panel.

The 100,000 ohm resistance.

Six B.A. screws are used for fixing the valve holders in position, and also for securing the two gridleak clips marked X in the wiring diagram, Fig. 6. Another clip, it will be seen, is secured to a filament terminal of V₃.

The same size screws hold in

leads, adequate support being obtained in this manner. The gridleak clip Y is soldered to the wire which goes to the grid socket of V₂, and thence to the condenser C₃.

A novel method of mounting the 100,000 ohm anode resistance has been adopted. Two pieces of stiff wire have been adapted for the purpose, the ends being bent into small circles into which the ends of the resistance fit. These wires are shown in dotted lines, being underneath the resistance.

enable the reader to construct the coil himself should he so wish. A piece of ebonite tube is required, 2½ in. in diameter and 2 ins. long, and also 1 oz. of No. 40 resistance wire, single silk-covered. The wiring is commenced ½ in. from one end of the tube, and 50 turns wound on. At this point a tapping is taken, after which 10 turns are wound and another tapping made. After this 60 turns more are wound, a tapping being taken at every 10 turns. We have

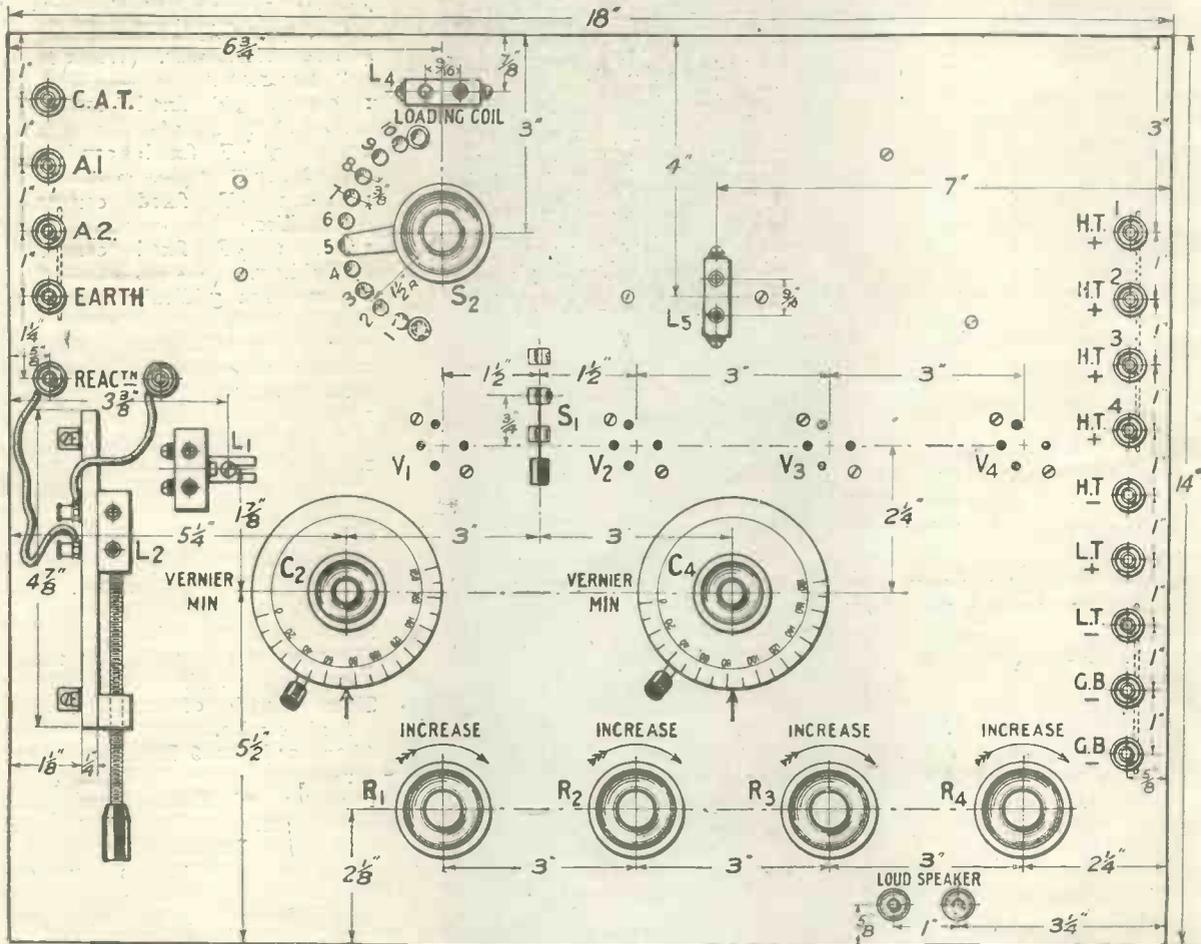


Fig. 5.—Front of panel drilling diagram. Blue Print No. 79A.

position the reactance coil — the method being seen in the photographs.

Wiring Up

The complete wiring diagram is given in Fig. 6, which should enable the whole of the wiring to be carried out without any difficulty whatever. Reference to back-of-panel photographs will be found helpful, and is a guide to spacing the various connections.

Comments upon the method of securing the fixed condensers, gridleaks and anode resistance may be welcome. The condensers are merely soldered to their respective

The Reactance Coil

The construction of this coil will prove difficult for most readers, and it is consequently advised that the coil be purchased ready made from the manufacturer mentioned in the component list. The firm primarily intended the coil for constructors of Mr. G. P. Kendall's "Simplicity" 3-valve receiver, in which a similar tapped reactance coil is employed, and this fact should be mentioned when ordering.

Coil Construction

The following directions will

now wound on 120 turns and taken 8 tappings (excluding the end of the wire). 30 turns are now wound, this completing the coil. We now have eight tappings and the two ends of the coil, constituting 10 points to which connections must be made from the contact studs.


Care should be exercised when soldering the tappings of the reactance coil to their respective studs, both to prevent breaking the wire (which is easily possible owing to its very fine gauge) and to ensure that the connections are

made correctly. Upon consulting Fig. 6 it will be seen that 50 turns are included between stud 1 and stud 2, and 30 turns between stud 9 and stud 10. Ten turns are included between each pair of consecutive studs from stud 2 to stud 9.

It is not essential to cover the tappings with rubber tubing as in the present case, but by so doing, the risk of short-circuiting is eliminated.

Two flexible rubber-covered leads will be seen in Fig. 6, soldered to the leads from A₁ and E; these pass through holes in the panel, and are connected on the other side to the fixed aerial coil socket as in Fig. 5. Other leads (stiff wire) may be seen passing through the panel at L₄ and L₅, and these are also connected on the other side of the panel to fixed coil sockets.

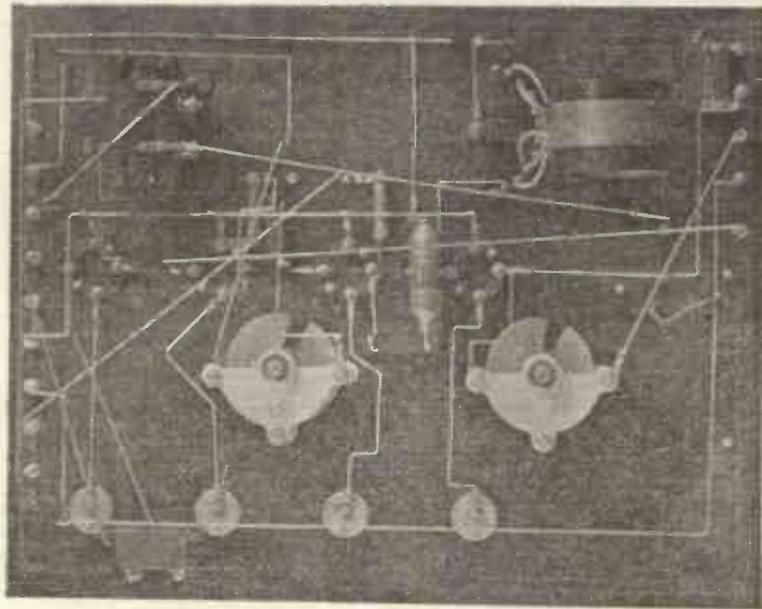The wiring of the receiver is completed upon connecting the two terminals marked reaction in Fig. 5 to the terminals on the moving coil socket by means of flexible leads.



A helpful plan view of the wiring.

The Cabinet

As will be gathered from the photographs, an ordinary square box has been used in the present

instance. Since the cabinet does not affect the working of the receiver, the constructor may please himself as to the type of cabinet chosen.

Results obtained with the Set

The four-valve T.A.T. receiver, as stated above, was tested at Bedford, the various results being (continued on page 834)

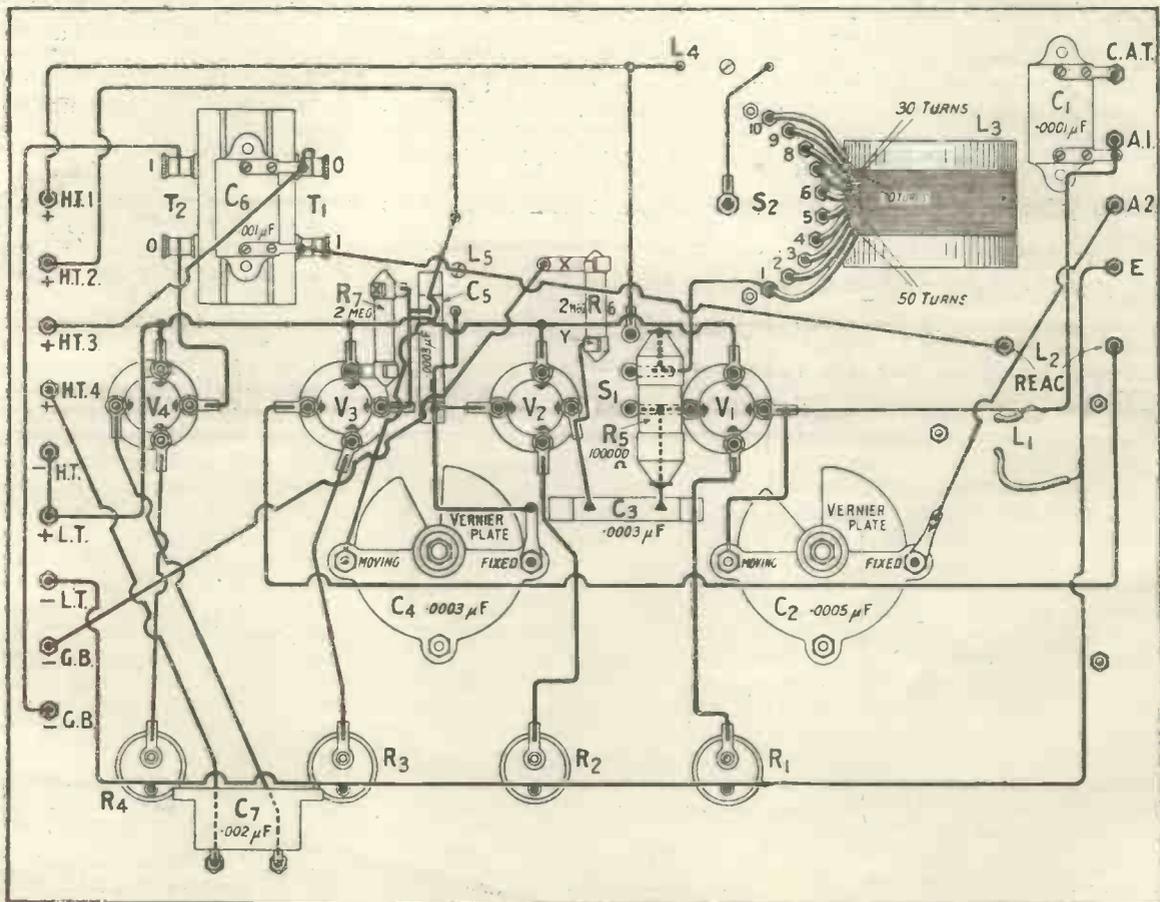


Fig. 6.—Wiring is a simple matter using this diagram. Blue print No. 79B.



I HAVE seen it stated by authorities for whom I have the utmost respect, especially as I am myself one of them, that there is no component in a wireless set over which the purchaser is more likely to be done to a turn than the simple, harmless-looking variable condenser. Even the fixed variety can administer a shrewd bite to the unwary buyer, for the gentle Hun has put upon the market a brand of grid condenser upon which he himself marks in large figures $0003 \mu F$, whereas its actual capacity may be anything you like or even nothing at all. However it is not of the fixed condenser that I would speak to you just now. I want to give you careful and detailed instructions for purchasing variable condensers, so that when next you visit a wireless shop you may foil any base deceiver behind the counter who tries to palm off a priceless dud upon you as the finest thing of its kind ever turned out. Let me say at once that you must fling aside all base notions of economy. Few variable condensers at ninepence apiece are really good articles. And even for double that sum I once bought one whose fixed plates could be moved in all directions, whilst the moving plates remained firmly fixed. This strikes me as a most ingenious and novel arrangement, but I must say that it worked very inefficiently. I mention this little incident just to show you what can happen if you are not thoroughly on your guard.

Why Condenser ?

Before I give you full instructions for sallying forth to purchase your component I think that I had better answer the question with which I am sure you are bursting. You want to know why it is called a condenser. Attend carefully and I will tell you. Many years ago there lived at Leyden an old scientist whose name is a household

word, though for the moment it escapes me. Being something of a jester in his lighter moments he one day took an empty jam pot from the store cupboard and covered both sides of it with tin foil. Inside it he placed a rod with a brass ball at its upper end. The next morning, during his lecture, he had his eye upon a student whom for want of a better name I will call Heinrich Sauerkraut. This lad, though not really a bad fellow, had the reprehensible habit of ragging his professors, and most particularly the Professor of electricity. The latter watched his antics for some time without appearing to notice that anything was happening and then said sweetly, "I will now show you another little experiment. Heinrich Sauerkraut, will you kindly hand me that jam pot." Not knowing that the aforesaid pot had spent some time in contact with the business



ends of a Wimshurst machine, or whatever they had of the kind in those days, young Sauerkraut obeyed with alacrity. He placed his right hand upon the brass ball and his left upon the outer tin foil. The Professor continued to smile whilst the student, after a leap into the air, sat down violently upon the floor and expressed himself in fluent and forcible Dutch. When he had

recovered his composure he shouted to the class, "Don't you ever touch one of those things. They are full of condensed electricity." That is how the condenser got its name, though between you and me and the bedpost it does not do much in the way of condensing. For this reason I strongly advise the novice not to say to the man behind the counter, "Are you quite sure that this condenser condenses properly?" To do so is to betray a lamentable ignorance of modern electrical theory.

The Outfit


Before setting out for the wireless shop you must first of all assemble the outfit which it is necessary to take with you in order to make quite sure that your purchase is up to snuff. For this you will need a high-tension battery, a pair of telephones, a milliammeter, a megger, a micrometer, and a life preserver. The last is to be used only if the salesman shows signs of losing his patience and begins to turn nasty. The best way of conveying these things with you is to obtain a soap box from the grocer and a pair of ex-perambulator wheels from the rag and bone shop. With the aid of the box, the runnells (as John Henry would call them) and a little ingenuity, you can make a neat and handy cart which will be invaluable to you not only when purchasing condensers, but also when going in search of other components of various kinds. When the ordinary man, unprovided with testing gear, enters a wireless shop, the salesman is frequently quite off-hand with him; but I make bold to say that when you go in with your outfit you will attract immediate attention. This is as it should be. There is nothing like making a good impression from the first, as the schoolboy remarked when he took at one bite a generous half of the apple held out to him by a trusting friend.

Creating Atmosphere

Success is largely a manner of letting people in the shop see right away that you are somebody. An excellent way of doing this is to advance to the most intelligent-looking salesman and say to him: "Good-morning. I want a condenser. By the way, I am Smith." "Oh, yes, certainly, sir," he will reply, "certainly, Mr. Smith." The man will endeavour to look as though you had said Marconi, but this will be rather a failure on his part. "I see," you proceed, "that you do not know my name. I presume that you don't read the wireless papers." The man will then assure you that your name is thoroughly familiar to him and that everyone, of course, knows the story of your achievements. It is probably just as well that they do not . . . but we will not become personal. You will now find that even though there are twenty other people in the shop clamouring for attention, the whole staff is engaged in looking after your needs. If you listen carefully you will hear the other customers whispering to one another in an awed kind of way, "I say, that's Smith." So far so good. In explaining how to create atmosphere I have really given away the secret of the famous Smelman Course which teaches you in six postal lessons how to develop your personality.

Getting On With It

But you must not stop here. It is essential that even greater diffidence shall be shown you. Throw out a few airy sentences such as: "As I was saying to my friend Hercy Parris . . ."; or "When I was showing Bendall how to wind coils . . ." This sort of thing goes splendidly. When the first variable condenser is shown to you give it one scathing look and place it as far away as possible on the counter. "My good man" you

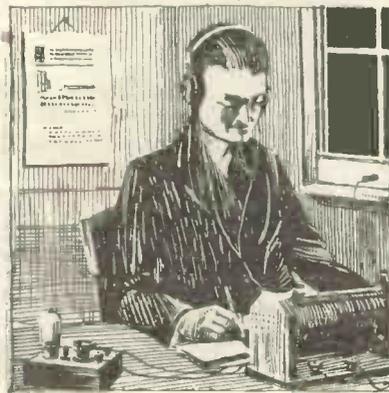

say, "you surely don't think that I would ever dream of buying a thing of that kind. It is quite all right, of course, for beginners, but I am afraid that it would hardly suit me." Things will now begin to get busy. The manager will appear from his office at the back, and, brushing aside the concourse of salesmen, will assure you with a low bow that it gives him the greatest possible pleasure to serve personally such a distinguished expert as yourself.

Testing

When he has produced something which looks rather less vile than those which he has previously shown you, you say: "Ah yes, now this looks something like the kind of thing I want. I will just test it out." Be very careful over this. First of all twiddle out the moving plates and place your thumb nail under the top one. Give it a good tweak. It will probably bend upwards at right angles. Do not apologise. Just lay it on the counter with a sad little shake of the head and say: "Dear me, dear me, rather weak in the plates, I fear." If you had not impressed upon everyone that you were Smith (a name which they have never heard, though they all think that they ought to have heard it), the father and mother of a row would now ensue; but, as it is, you are warmly thanked for pointing out the shortcomings of a defective component. Another condenser is produced. You don the telephones, wire up the high-tension battery and proceed to twiddle the knob, saying meanwhile: "Tut, tut. Just what I thought." Again you return the condenser as quite useless. Perspiring freely at every pore, the manager dashes off to the stock-room, whence he returns laden with condensers of the most expensive kind. For your megger you have two sets of leads. The first contains one wire which, though it looks all right, is really shorted to the other. You twiddle the handle. The pointer remains at zero. You explain that a shorted condenser can hardly be expected to produce the best results. Another is offered you. You substitute the other set of leads, obtaining an infinity reading. "That," you say, "is rather better." Further tests of all kinds follow, after which you inquire the price of the selected article. In a loud voice the manager reads the price off the ticket and then whispers that as you are Smith he will give you a fat discount. You simply say haughtily that you came to buy one con-



denser and not to purchase the shop. Then repacking your barrow you move off, leaving consternation in your wake.

A Pleasant Afternoon

You next visit in turn a number of wireless shops, playing much the same game in each. The crowd of admirers which you found in the first shop will probably follow you round, and if you are in luck some of them will precede you, spreading the news of your imminent arrival. You will thus find the way already prepared for you and the subsequent proceedings will be easy. By the end of the afternoon you will have reduced every shop in the neighbourhood to a metaphorical pulp, and you will also have spotted the one condenser that you really want to have. To obtain this at a reasonable price is a perfectly simple matter. Apply all your tests several times and finish up by saying that though the plates are buckled, the insulation is hopeless and the spacing between plates is all anyhow, you can of course put it right in a few hours in your own workshop. Though you do not care as a rule about buying an imperfect article, you are willing to purchase this condenser even in its present ghastly state provided that the price is reasonable. If you have made yourself sufficiently objectionable they will probably give it you; but anyhow it will be yours for a trifling sum. Before you go home you will almost certainly be buttonholed by the reporter of the local paper, who will demand an interview. Give it him. Express your opinions freely upon the quality of components, the future of wireless, the broadcast programmes and the Postmaster-General. Reporters are always thirsting for copy and there is no reason why this one should not get it if he wants it.

THE LISTENER-IN.

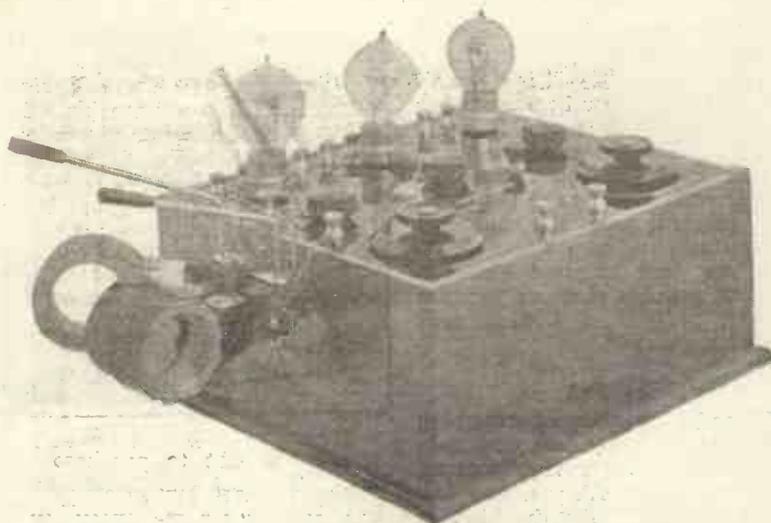


Fig. 1.—Outwardly the set resembles a conventional three-valve set.

A New Reinartz Receiver

By PERCY W. HARRIS,

Assistant Editor.

A QUESTION often put to me and extremely difficult to answer is: "Which is the best three-valve circuit to make up?" It seems a simple kind of question—one to which any experienced man ought to be able to reply—but actually no satisfactory direct reply can be given. So much depends upon the tastes, circumstances, and limitations of the would-be builder. Does he desire to stretch out into the great distances, being content with only moderate signals in the telephones? Is he prepared to sacrifice something in range to obtain volume from a near-by station? Is his problem one of interference, and will he be thankful to sacrifice some strength in order to eliminate signals from near-by shipping? Is simplicity of handling one of the vital requirements? These are but a few of the questions which must be put before any answer can be given.

Reinartz Tuners

I have lost count of the number of receivers I have designed in the last two or three years, but one which has always interested me, and which, strangely enough, has not achieved the popularity its merits deserve, is the Reinartz. John L. Reinartz, the young American originator of this circuit, is one of the most prolific producers of tuner designs in the United States. In the spring number of MODERN WIRELESS (March, 1924) I wrote a fairly comprehensive article giving many modifications of the original Reinartz circuit, and also published a complete design for a three-valve Reinartz receiver, consisting of a detector followed by two stages of note-

magnification. In this receiver, as in all other Reinartz designs previously published, it was necessary to wind a special coil, and this, of course, has limited the wavelength range. I have been experimenting lately to find a suitable way in which to use standard plug-in coils in the Reinartz, and I am pleased to say that the design in the present article has proved thoroughly satisfactory for all the wavelength ranges in which telephony and broadcasting are comprised. The two great virtues of the Reinartz circuit, high selectivity and simplicity of reaction, are both present in full force in this receiver. Indeed, reaction control is particularly easy here owing to an arrangement which I shall describe later. Whilst not quite as sensitive for distance as the best circuits containing one stage of high frequency

magnification, it is yet quite sensitive enough on a good outside aerial to hear all the broadcasting stations when conditions are favourable. When tested recently on two different aerials, it succeeded in giving Aberdeen on the loud-speaker at what may be termed "small room strength" quite easily.

Theoretical Circuit

The theoretical circuit which is given in Fig. 5 differs only slightly from that of the last design published, in that a radio frequency choke coil is included between the plate of the detector valve and the primary of the low frequency transformer. This choke is not always necessary, and often, particularly with the latest type of intervalve transformers with very low self-capacity, it can be dispensed with. I have included it because I think its presence will ensure that practically every make of

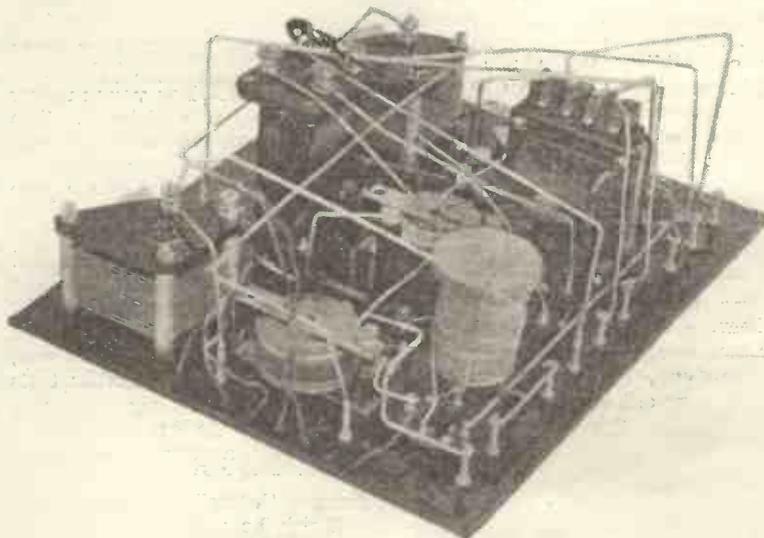


Fig. 2.—Compact construction is a salient feature.

In this instrument the disadvantages of the older types of Reinartz Receiver are removed.

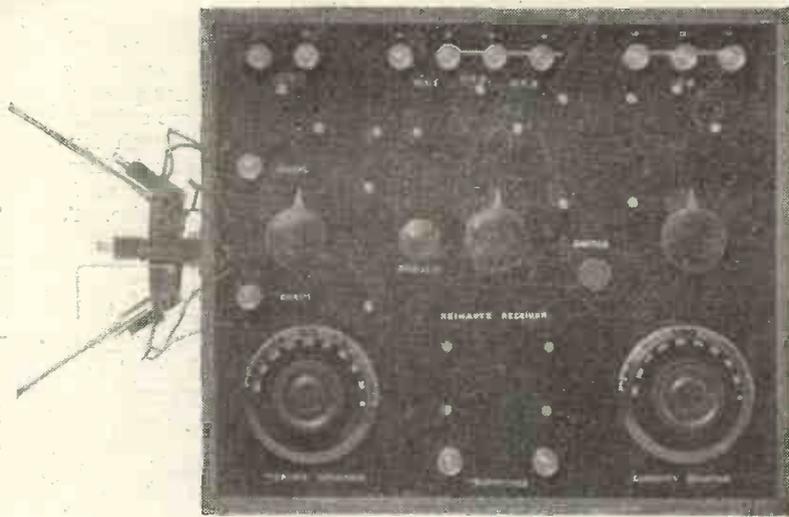


Fig. 3.—Separate high tension terminals are provided for each valve.

low frequency transformer will give good results, and I advise its inclusion in all cases.

Semi-Aperiodic Aerials

All Reinartz receivers have a semi-aperiodic aerial system, the aerial coil being both conductively and inductively connected to the grid coil as shown. In the original Reinartz receiver the aerial coil was tapped in single turns and the grid coil in two or three places. The plate coil was also tapped. Later it was found that if the grid coil was suitably wound with thick wire it was possible to dispense with the plate coil; this I have confirmed myself. The presence of a plate coil, however, makes reaction control easier, and, when used as I am about to show, gives a simplification of reaction control which is most desirable.

The aerial coil and the grid coil

in the present receiver are two plug-in coils in a three-coil holder, the third socket of this holder being used for the reaction coil. It will be seen that connections are made between the aerial and grid coils, and in practice they are kept closely coupled all the time. The plate coil, which is in the furthestmost moving socket, has its position determined by some preliminary experiments, and once the best position for the particular valve and the wavelength range has been found, it is left so adjusted and reaction control carried out entirely on the reaction condenser.

Reaction Control

Reaction in the Reinartz receiver is carried out by combination of the electrostatic and electro-mag-

netic methods, and it is essential that the high frequency current takes the path through the reaction coil and reaction condenser rather than through the self-capacity of the transformer windings, or the capacity of a shunt condenser. This is why we must omit the usual poor condenser across the primary of the transformer, and to make sure that the self-capacity of the transformer windings is itself not permitted to by-pass these high frequency currents, a radio frequency choke consisting of about 300 turns of No. 36 double silk covered wire on a former about 1 1/2 in. diameter is used.

There are no special arrangements in the note-magnifying stages save that, as just mentioned, it is essential to omit the usual shunting condenser across the primary of the first transformer. A push-pull switch is incorporated in the receiver so that the second note-magnifying stage can be cut out when reception in the telephones only is desired. Filament resistances can be fitted for either bright or dull emitters. In the present instrument special dull emitter resistances have been fitted, as it was desired to use this particular instrument with dull emitter valves only.

Components Required

The components in this receiver should be of good quality, but apart from this they can be of any of the numerous makes now available. As usual, I strongly recommend the use of square law condensers for tuning. In the case of the reaction condenser, however, there is no special point in having

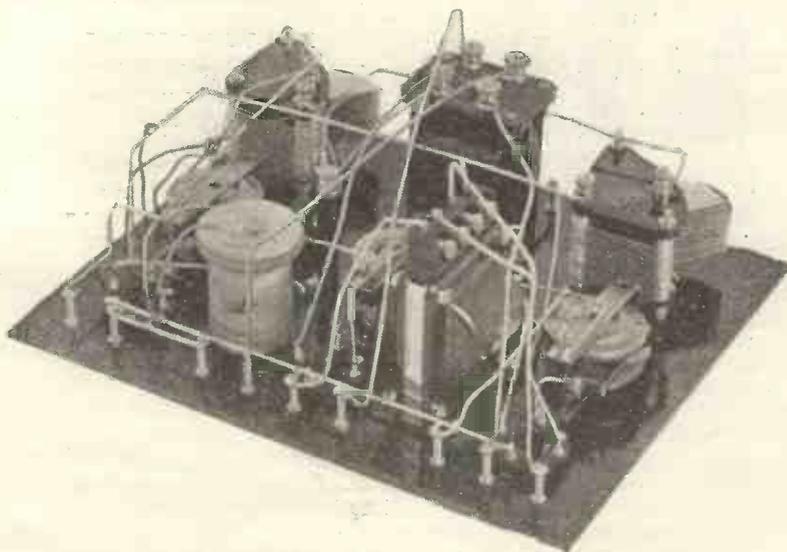


Fig. 4.—The panel viewed from another angle.

this of the square law pattern, seeing that it is not used for tuning; but, on the other hand, it is quite as convenient to use the square law type here, and so I have fitted it. We need, then—

One ebonite panel 12 in. by 10 in. by $\frac{1}{8}$ in. or $\frac{1}{4}$ in. (Use one of the guaranteed makes here. In the instrument illustrated I have used a Bowyer-Lowe panel.)

A suitable cabinet. (This can be of the flat or the vertical type, according to taste.)

Two variable condensers, one at least square law. (Jackson Bros. were used here.)

Thirteen terminals.

One three-coil holder. (Magnum.)
Two inter-valve transformers of good make. (I have used one Ferranti and one Igranic.)

One fixed condenser, .0003 mfd.
One variable grid leak, $\frac{1}{2}$ -5 megohms. (Bretwood.)

Three filament resistances to suit the valves it is desired to use. (I have used Igranic dull emitter resistances.)

One three-point push-pull switch. (Lissen, Ltd.)

One wooden bobbin on which the choke coil is wound. (I have used an ordinary spool on which wire had been wound. Any piece of wood roughly an inch and a half in diameter and about two inches long will do.)

Suitable valves.

Coils for wavelength range desired. (See note at end of article.)

Batteries and telephones.

The panel should be laid out carefully from the designs given, and departure from the general arrangement is not recommended, as it is essential on this receiver to avoid certain interaction effects which might not be quite so harmful in others. Different makes of transformer, condensers, etc., vary slightly in the space they occupy, and the parts should be laid out first of all before drilling the panel to see that all components fit into the places given

The Choke Coil

The choke coil should be made from No. 36 double silk (or double cotton) covered wire (even enamelled wire will do, but the double silk is best). This coil is not critical in its dimensions, and can be made up of 300 turns (approximating to a single layer, but it does not matter if the turns are slightly "scrambled") on a bobbin of about 1 $\frac{1}{2}$ in. diameter. After the ends have been secured the coil can be wound round with empire tape or some such substance

to protect it from mechanical injury. Ample length should be left at each end for subsequent connections. I should mention in passing that where the wires go from the coil to other portions of the apparatus they are safeguarded by being passed through lengths of insulating tubing, otherwise wiring is done with the ordinary square section tinned wire. After

three valves in circuit, and when it is pulled out we have two. When only two-valves are used the third filament resistance should be turned to the off position.

Owing to lack of room it is not found possible to mount the three-coil holder on the panel itself. It is therefore attached to the side of the box. Six holes in the left side of the panel (looking from the

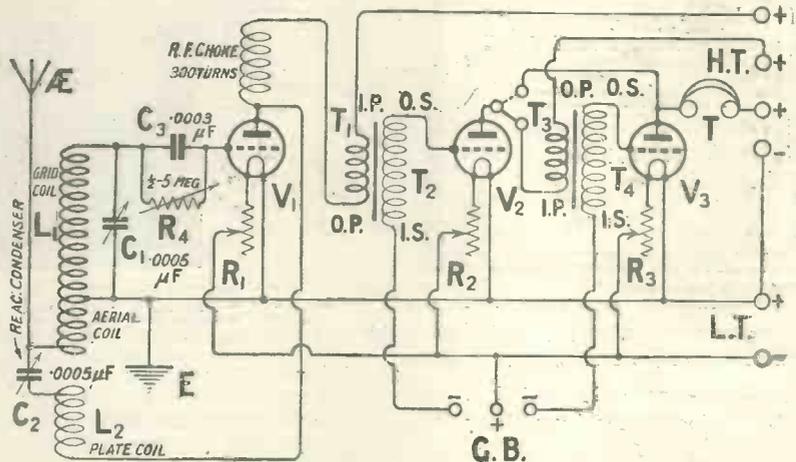


Fig. 5.—The theoretical circuit.

the coil is wound it is a simple matter to secure it to the panel by two wood screws.

The Push-Pull Switch

The push-pull switch has three soldering lugs attached to it. An examination of the switch will show that one of these lugs is connected to a screw which makes contact with the central rod. The other two lugs are connected to

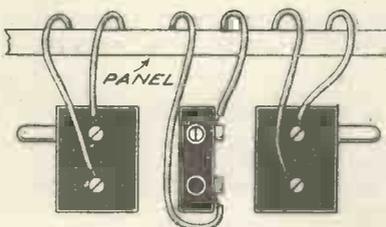


Fig. 6.—How to join up the sockets.

metal fingers. When the switch is pushed inwards the centre spindle makes contact through a grooved ring with one of the blades, and when the switch is pulled out the other blade is substituted. Thus the switch acts as a single pole throw-over switch. The switching arrangement adopted in this instrument is to connect the plate of the second valve either to the primary of the intervalve transformer or to the telephones. In this way, when the switch is pushed in we have

top) are made for flexible leads from the interior of the instrument. These flexible leads are pushed through the holes and left free when the panel is secured in place, and are subsequently joined to the three-coil holder by the special securing screws. Note particularly that the exact order of connections of the flexible leads to the coil holder must be followed, the leads going alternately to the top and bottom of the plugs. The first wire can go either to the top or the bottom of the first plug so long as the alternate order is followed.

New Wiring Method

This month we have introduced for the first time a new method of depicting the wires in our wiring diagrams. In previous diagrams the crossing of one wire over another has been shown by a small semi-circle, so that the reader may know which wires cross over and which are soldered. Whilst this method is free from confusion in one respect, it has the disadvantage that in sets where there are many wires the constant looping confuses the eye and gives rather a false idea of the complication of the wiring. The new method consists in showing the wires between points as a straight line just as they appear on the set, the cross-over points not being indicated by any semi-circles. So

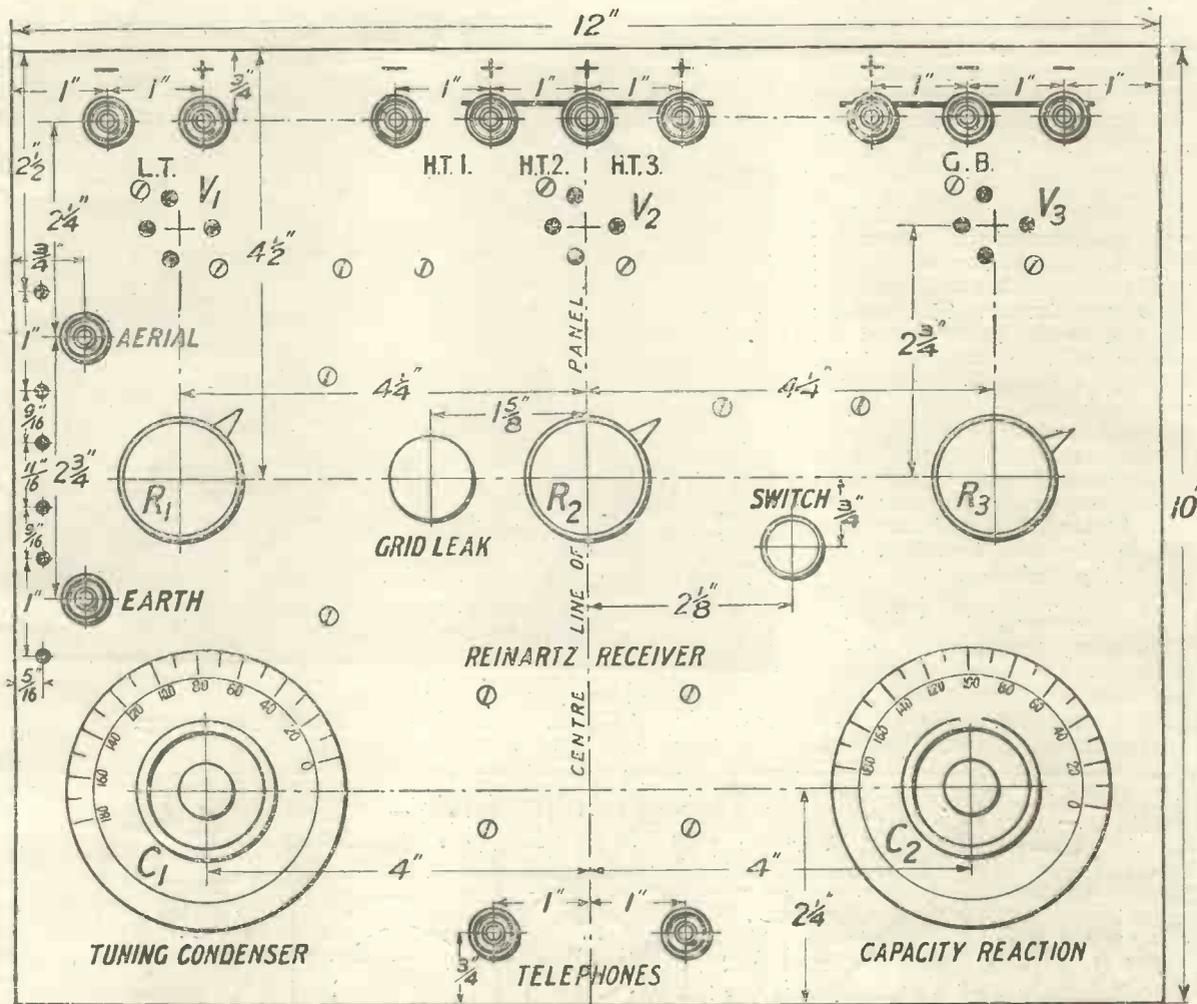


Fig. 7.—Drilling diagram of the top of the panel. Blueprint No. 75A.

that the reader may have no doubt as to which points are soldered, these connections (other than on terminals where a soldered connection is obvious) are shown by small black squares. The wiring diagram therefore is a more faithful reproduction of the actual wiring, and I think will be clearer. We should greatly appreciate readers' opinions on this matter—whether they like the new or the old method, and which of the two they consider the clearer.

It will be noticed that in the present instrument provision is made, not only for grid bias, but for separate high tension for each valve. In this way it is possible to use a power valve in the last socket, a good arrangement when signals from the local station are very strong and the ordinary valves cannot handle them. Until the reader is used to manipulating this receiver it is just as well to connect the three high tension positives together and to short circuit the grid bias terminals. When he has

become accustomed to the instrument, he can find the best high tension voltage for each valve and the best grid bias.

Testing the Receiver

As soon as the wiring is completed valves may be inserted and the batteries connected for preliminary test. The best results with this receiver will be obtained with the aerial coil best suited to your own aerial, but as a preliminary trial I would suggest a 25 coil (or its equivalent in other methods of indication) in the aerial socket, a 50 in the grid circuit socket and a 50 or a 75 in the plate socket. Before turning on the current set the reaction coil at right angles to the grid coil and the reaction condenser at zero. The aerial coil should be placed as close as possible against the grid coil. Now turn on the current and, leaving the coils as stated, tune on the aerial tuning condenser. You will soon pick up your local station, although you may easily miss it in

rapidly turning the tuning dial. As soon as you have found the station, turn the reaction condenser half way round and see whether the set oscillates. It will probably not do so. Now very slowly approach the plate coil to the grid coil until, with the condenser still at the half-way point, the set just oscillates. Now leave the coil in this position and turn the condenser back towards zero until the set ceases to oscillate. You will now find that reaction control can be carried out entirely by the reaction condenser, and you will obtain a very smooth control without "backlash." A further slight adjustment of the tuning condenser will be needed. Considerable variations of the tuning condenser will make it necessary to alter the reaction setting, but it will be found possible to obtain a good measure of reaction over the whole range of the tuning condenser without any further alteration.

You will soon get used to handling this receiver, and once

you have found the best position for your coils in the three-coil holder you need not touch this again. On the longer wave broadcasting stations try inserting a 75 for the grid coil.

Selectivity

If you have a set of special short wave coils, one of which is smaller than the 25, put the smallest coil in the aerial socket and again try some experiments. The smaller the coil in the aerial socket the greater will be the selectivity, although a point will be reached when you lose signal strength in gaining this selectivity. In general, I have found a 25 coil quite useful. For longer wavelength ranges it is wise to have coils in which the grid coil is twice the size of the aerial coil, and the reaction coil about the same size as (or one size larger than) the grid coil. The size of the grid coil can be found by referring to the MODERN WIRELESS Coil Table, using the same size as the table gives for an anode coil. Thus Radiola and Chelmsford will need a No. 230.

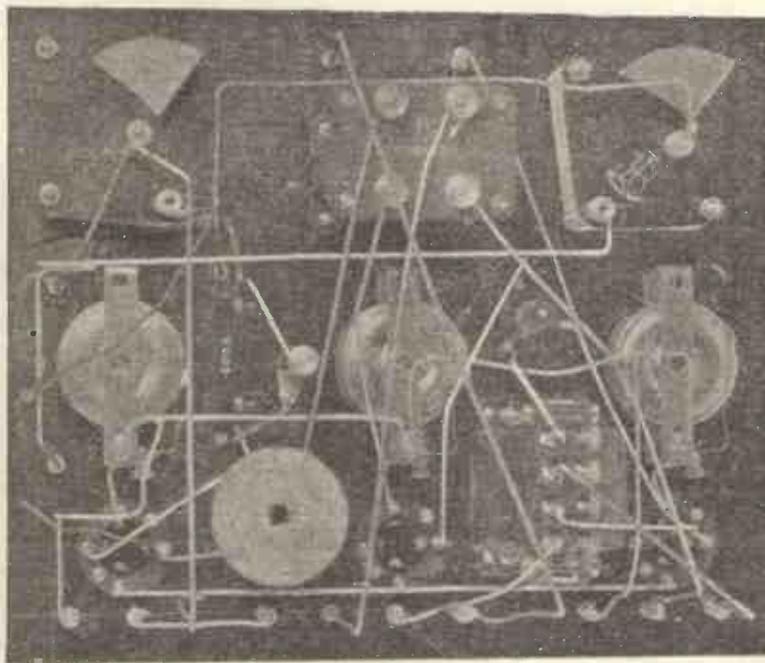


Fig. 8.—Plan photograph of the wiring.

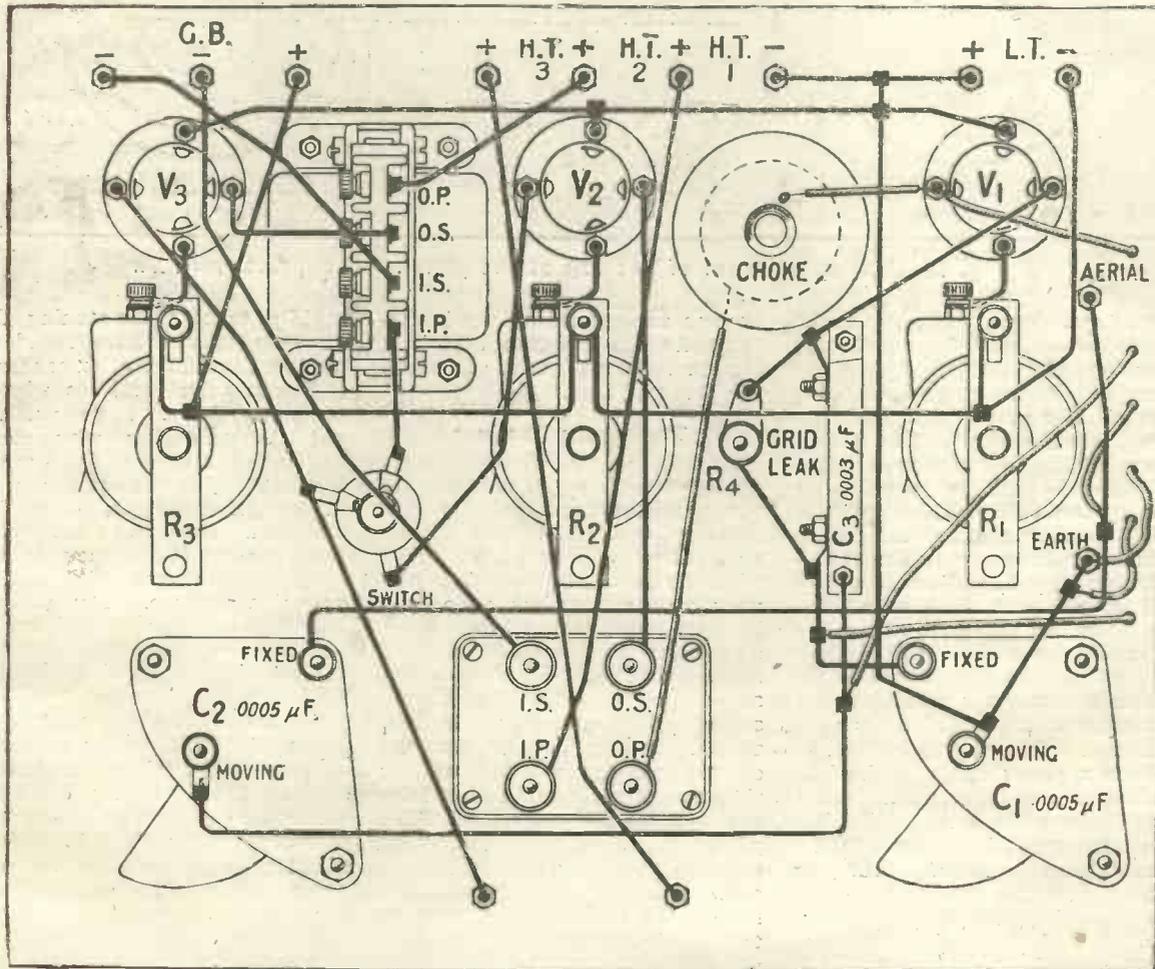


Fig. 9.—Practical wiring diagram. Blueprint No. 75B. Note the new method of showing wiring. Joints are indicated by small squares. Where no square is shown, the wires cross without touching.

THE GLASGOW STATION

Test Report

During the very full test I gave this instrument on completion it was found to give adequate loud-speaker strength for the average room on a very small indoor aerial seven miles from 2I.O. On a good outdoor aerial Aberdeen was received at small room loud-speaker strength, and three other stations similarly. In the telephones all the British stations were heard, with the exception of a few of the relay stations, which do not come in well, although some difficulty was found in picking up one or two of the main stations. The fact that all stations can be received in favourable circumstances should not be taken to mean that I recommend the set for long distance work, but for anybody who desires a highly selective receiver to work a loud-speaker from a near-by station the present Reinartz system will be found hard to beat.

Continental Stations


Of the Continental stations Ecole Supérieure and several Germans were heard at excellent telephone strength, whilst Radiola was quite satisfactory on a loud-speaker in a small room. As an extra test the instrument was lent to other members of the Radio Press Editorial Staff, and their reports coincide with that just given.

Aerial Reaction

As this set is arranged to give reaction on the aerial the usual precautions must be taken to prevent radiation. In practice this is quite a safe receiver, as control of the reaction is most gradual and the set does not "flop" into oscillation as do many sets in which the ordinary magnetic reaction is used.

American Broadcasting


Reports on this set will be, as usual, welcomed, particularly from those readers who use the set to work a loud-speaker with an indoor aerial. As we are now at the time of the year when reception of American broadcasting stations is most favourable, I may say that the present receiver is quite suitable for this work when conditions are good, and, indeed, one member of the staff picked up an American broadcasting station on the first night he tried the instrument. Critical adjustment is, of course, needed, and for those who are particularly desirous of picking up American broadcasting I would recommend a design using one or more stages of high frequency.

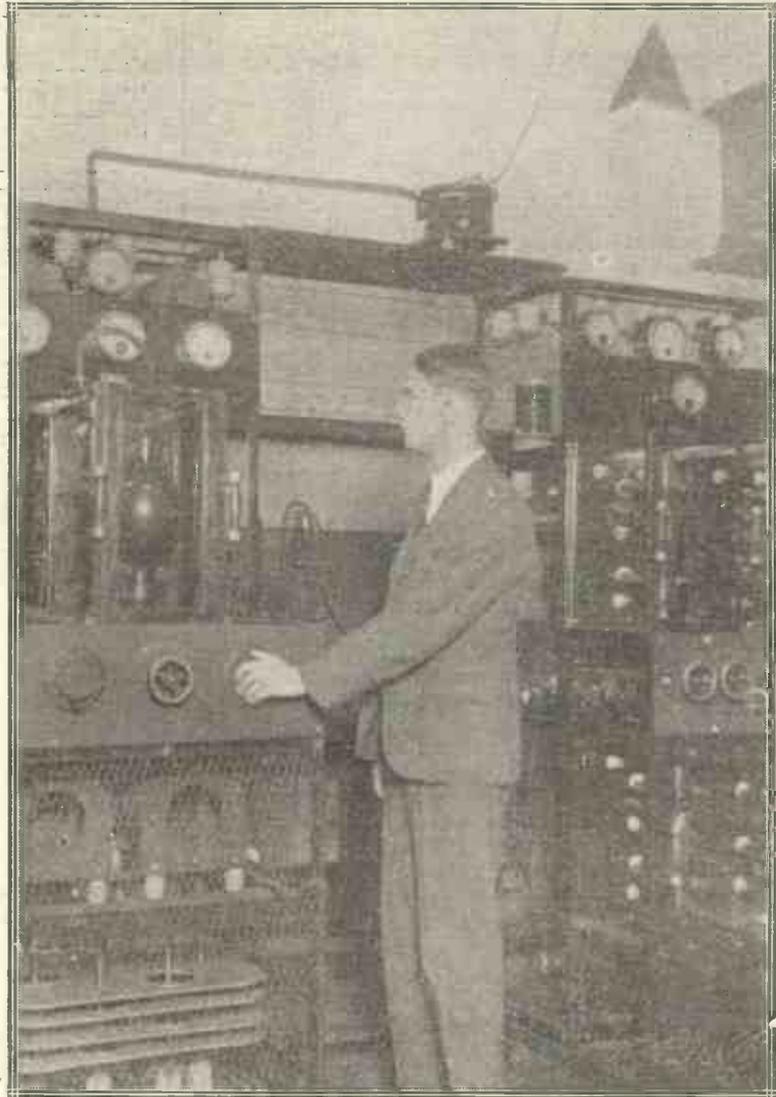

The Engineer, Mr. H. M. Hill, at the Main Oscillator.

QUERIES

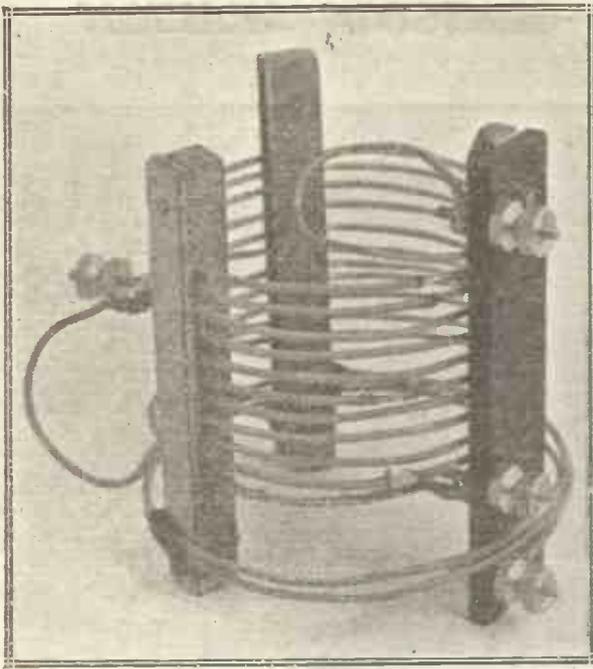Readers are reminded that the fee charged by RADIO PRESS LTD. for answering technical queries is 2s. 6d. per question. As a highly technical staff is devoting its whole time to replying to these queries it is impossible to answer any query which is unaccompanied by a remittance.



An efficient coil for short wave reception.

Reception on the Ultra-Short Waves

the powerful American station KDKA down to approximately 65 metres has inspired many in this country to try to receive him on the lower of the two wavelengths on which he is at present working.

Those who were privileged to listen-in to the Poldhu station recently, when transmitting to the "Elettra" and to the Antipodes, will realise the tremendous force with which a short wave station of a dozen kilowatts power will come in at some hundred miles—equivalent to 2LO at a dozen miles was the writer's own experience.

Conditions for Reception

The conditions for successful reception appear to be:—First: the use of a *short* single wire aerial, preferably vertical, and very carefully isolated, with a short direct lead-in. Second: the use of as few valves as is practicable, two for 'phone use, detector followed by an *efficient and silent* stage of low-frequency amplification. Third: keeping all tuning and distributed capacities as low as possible. The last point is not due to any vague mysterious "leakage" of signal energy due to stray capacities on the short waves, as is

IT is not an exceedingly difficult matter, requiring any extraordinary or unusual types of apparatus, to receive successfully the transmissions on the very short waves which are becoming increasingly popular (particularly since the remarkable feats of trans-oceanic telephony on about 100 metres have been made public). The recent move on the part of

aerials is approximately proportional to the *square* of the frequency. With a wavelength only one-sixth of the ordinary broadcast wavelength, the efficiency of signal energy transfer is very high, so that the most rudimentary aerial (or almost none at all) suffices to pick up as much energy in proportion as a high P.M.G. aerial on 360 metres.

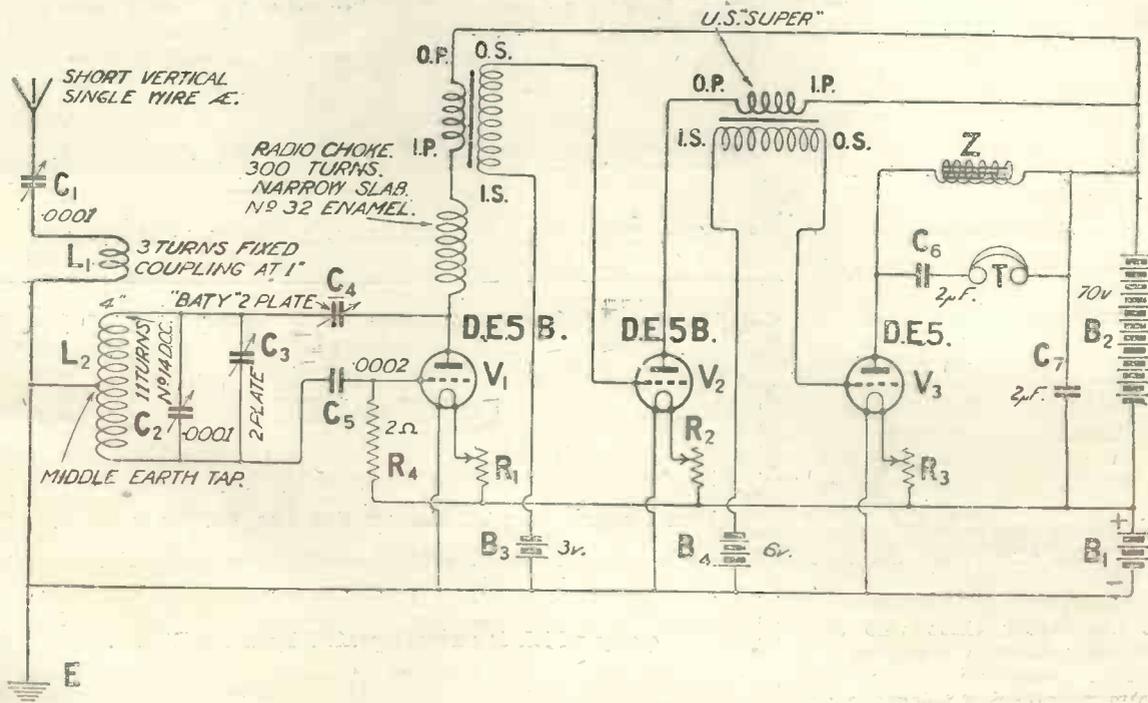


Fig. 1.—A powerful short wave circuit.

By A. D. COWPER, M.Sc.,
Staff Editor.

The present trend in wireless development is towards the use of very short waves, and this article forms a basis for much interesting experimental work in this direction.

often and inaccurately stated, but because the total available tuning capacity is necessarily low, and these stray capacities (often poor high-loss condensers in effect) must accordingly be kept down to a reasonable proportion of this limited maximum.

Tuning to Short Waves

On one-sixth of the ordinary broadcast wavelength we need one-sixth of the inductance and one-sixth of the tuning capacity (for the wavelength is proportional to the square root of the product of these, according to the familiar formula), so that we may retain the ratio of inductance to capacity in the tuning circuit at about the right order for a similar degree of efficiency. So with an inductance of the order of 20 microhenries, we must combine a total tuning capacity of not much more than .0001 μ F (100 micro-microfarads). This needs quite careful work in the design of the tuning inductance. The distributed capacity of the No. 15 coil of a well-known type of plug-in coil is near 20 μ F, and its "natural" wavelength is given as being close to 50 metres. Apart from its very appreciable H.F. resistance, it is evident that such a type of closely wound fine wire coil is quite unsuitable for extremely short wave work, even if cut down to a small number of turns. The self-capacity can actually be brought lower by special types of winding, but at the cost of heavy dielectric losses and high H.F. resistance through the use of fine wire.


Reduce H.F. Resistance

It is essential for success on these very low waves to have the H.F. resistance as low as possible, not only to eliminate much of the interfering mush and atmospherics in reception, but in order that a minimum amount of reaction will suffice to bring the receiver into a sensitive condition. Clumsy strong reaction introduces so much trouble through stray capacities and continual interference with tuning as

reaction-coupling is varied, that it makes successful reception of distant stations almost impracticable.

While very little useful data on the subject is available, such as has been published shows that the high-frequency resistance of wire increases with great rapidity with increase of frequency below, say, 200 metres, and on 5,000,000 cycles (60 metres wavelength) is probably 5 to 7 (or more) times the D.C. resistance even for the larger gauges of wire. Accordingly,

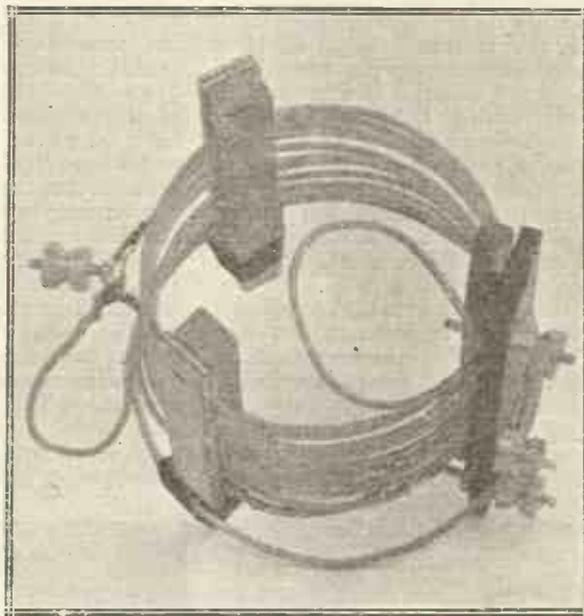it is necessary to break away from the practice of using wire that is easy to wind and cheap to buy and gives results of a sort on the B.B.C. waves, and to make the tuning inductance of a type really designed for short wave work. A lesson



Notice the similarity to transmitter inductances.

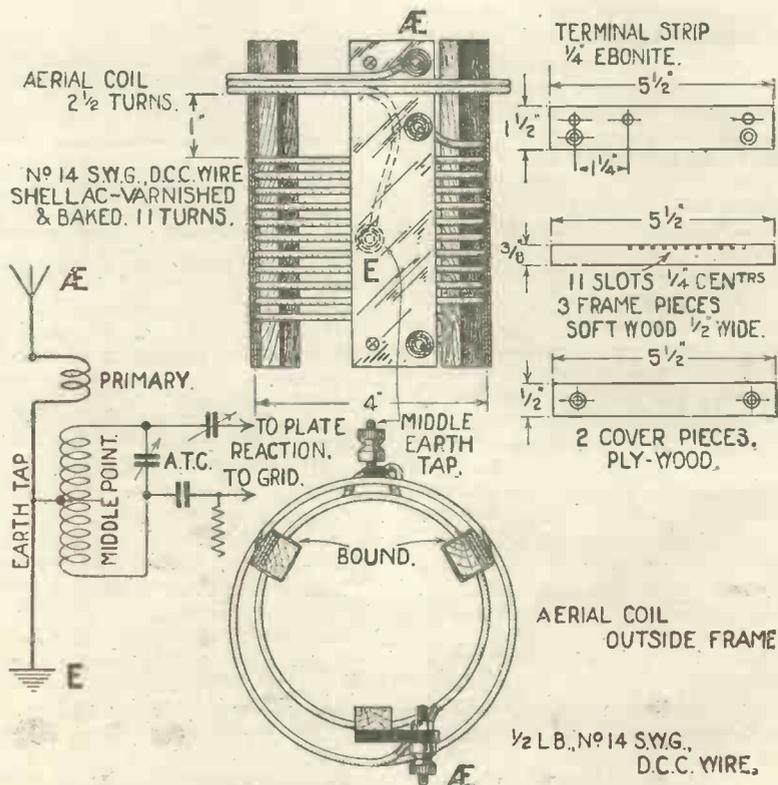


Fig. 2.—Details of a tuning inductance for 60 metres.

can be learnt here from the transmitting fraternity, who are forced by the relentless logic of their aerial ammeter to pay some heed to the quantitative efficiency of their tuning inductances. Their large air-core coils of bare copper strip or rod represent the ideal, to which one must make some approximation here. Hence the design indicated for the A.T.I. is that of an air-core coil, well spaced, of, say, No. 14 s.w.g. wire. As we are not dealing with high potentials and can stand some limited loss with the help of moderate reaction, we can use d.c.c. wire and a simple wooden frame, leaving the troublesome job of stringing ebonite strips bored with a row of holes on bare-wire coils, as is customary, for those who are interested in actual transmission.

A.T.I. Design

The design for the A.T.I. is indicated in the figures. Eleven turns of No. 14 d.c.c. wire (which is stiff enough for such a purpose and has a fairly low resistance even on 60 metres) are first wound on a handy jam-pot, preferably with the assistance of another person. The diameter should be about 4 in. when sprung off. For the frame, three pieces of soft wood are cut, about $5\frac{1}{2}$ in. by $\frac{1}{2}$ in. by $\frac{3}{4}$ in., and notches (deep enough to take the wire) are cut by a saw across the wider face, 11 in number, and spaced as nearly as possible at $\frac{1}{4}$ in. Two slips of stout three-ply wood are then required, $5\frac{1}{2}$ in. by $\frac{1}{2}$ in., and a strip of $\frac{1}{4}$ in. ebonite $5\frac{1}{2}$ in. by $1\frac{1}{2}$ in. The ebonite strip is drilled to take two small screws for fixing on the frame, and has three terminals, one at each end and one $1\frac{1}{4}$ in. from one of the latter, all arranged to one side of the strip. The frame-pieces are arranged at 120 degrees around the inductance, inside, and the ply-wood and ebonite pieces fixed on outside the wire by two small brass wood-screws apiece at the ends, the turns of the No. 14 wire being arranged in the grooves in order. The ends of the latter are secured under the end and the intermediate terminal respectively. The middle of the length of the wire is then bared of insulation, pulled out a little, and a third terminal soldered on securely. This provides the earth-tap, mentioned later.


On account of the small maximum capacity permissible, direct coupling to the aerial is hardly practicable. Hence a fixed semi-aperiodic primary coil is used with a very small series condenser, if on a long aerial. For this

purpose a coil of only three turns of No. 14 d.c.c. wire is wound on the projecting frame-ends of the tuning inductance, outside the cover-strips. The aerial (outer) end of this is secured to the vacant terminal at the top, and the lower end is bent round so as to clear the turns of the tuning inductance by a good margin, and is brought to the central earth-tap point and soldered there. The small coil of 3 turns (actually more nearly $2\frac{1}{2}$) is secured in place with insulating tape at about 1 in. from the top turn of the other coil, no particular care being necessary here to space the turns. The whole is varnished with shellac (it will do no harm here, with good air-spacing) and thoroughly baked to exclude

alone was found by measurement to be $4.8\mu\text{F}$, as compared with a standard R, which gave $3.6\mu\text{F}$. The greater power of the first valve surely justified an increase in tuning capacities of about $1\mu\text{F}$!

Stray Capacities

Two panels with four-leg valve-holder in place, grid condenser and leak, showed capacities from the grid connection to earth of 5 and $7.7\mu\text{F}$ respectively. A lead of about a foot of flex, fairly well isolated, gave the surprising figure of $5.5\mu\text{F}$, a thing seldom realised amongst amateur constructors. As the zero capacity of the low minimum Peto-Scott $.0001\mu\text{F}$ tuning condenser (ebonite frame) to be used was $6.6\mu\text{F}$, the total

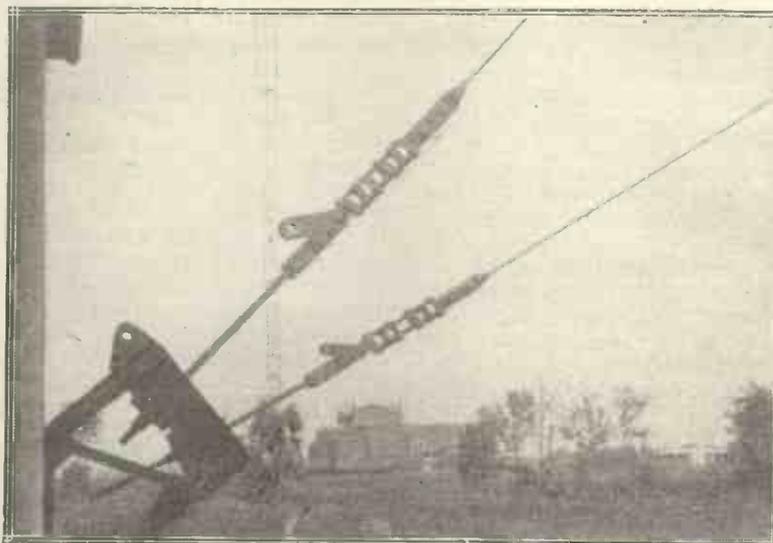

A view of the Nauen station. Time signals from this station are regularly received in the United Kingdom, and on 73 metres experimental transmissions are being carried out with both telephony and C.W.

moisture. Damp wood is almost a conductor for high-frequency work, so moisture should be avoided even when the minimum of wood is present.

Types of Valve

The tuning range depends on the stray capacities present. As ordinary types of valves and standard types of panel-mounting were desired, the writer investigated to what extent these give an unwelcome load of stray capacities. In order to take advantage of the high efficiency reached in a detector-valve with an amplification factor of 20, he desired to use a D.E. 5B valve here, which is scarcely what some authorities would recommend for extremely short wave work. The total grid to earth capacity of this valve

casual capacities, apart from distributed capacity in the inductance, were around $24\mu\text{F}$ even if short leads were practicable. With a tuning condenser range of $100\mu\text{F}$, the wavelength range could not be very great. With the experimental temporary bench hook-up, involving a total of more than two feet of leads to tuning and fine-tuning condensers, the actual range was found to be from around 40 to just below 80 metres, when loaded to some extent by an aerial.

Wavelength Range

Unloaded, it was possible to go a little lower, and with a $.0002\mu\text{F}$ tuning condenser and the aerial load the highest point was about 105 metres. These were repeatedly checked against higher

harmonics of a heterodyne wave-meter, itself standardised against a Townsend wave-meter and the B.B.C. stations, of range 300 to 600 metres. The fourth, fifth and sixth harmonics could be picked up in succession by very careful manipulation with the heterodyne meter standing close to the short wave receiver; up to the twelfth harmonic could sometimes be traced.

At first the aperiodic primary was wound on the frame right over the tuning inductance, but the distributed capacity to earth of this arrangement proved excessive. The measured capacity between

a familiar type of transmitting circuit, across grid and plate, with a blocking condenser in the plate lead. As shown recently by the writer, this forms a handy, powerful circuit for use with frame aerials, if this anode condenser is made a small, low minimum variable one and reaction effects are controlled by it. A centre earth-tap is needed in the tuning inductance, and the grid condenser and leak are arranged in the conventional manner. Then no other reaction coil is needed and casual capacities are kept at a minimum.


The Radio Choke

The radio choke needed in this

hand-capacity effects are very pronounced. So long as H.F. leads are as short as possible and well isolated no other special features seemed called for in the arrangement of the receiver. The reaction condenser was conveniently a two plate Baty condenser, as a very low minimum is called for at times, and a maximum approaching $0.003\mu\text{F}$. An extension handle was fitted to this. A further control over reaction is provided, with D.E. valves, by the filament control.

High Amplification

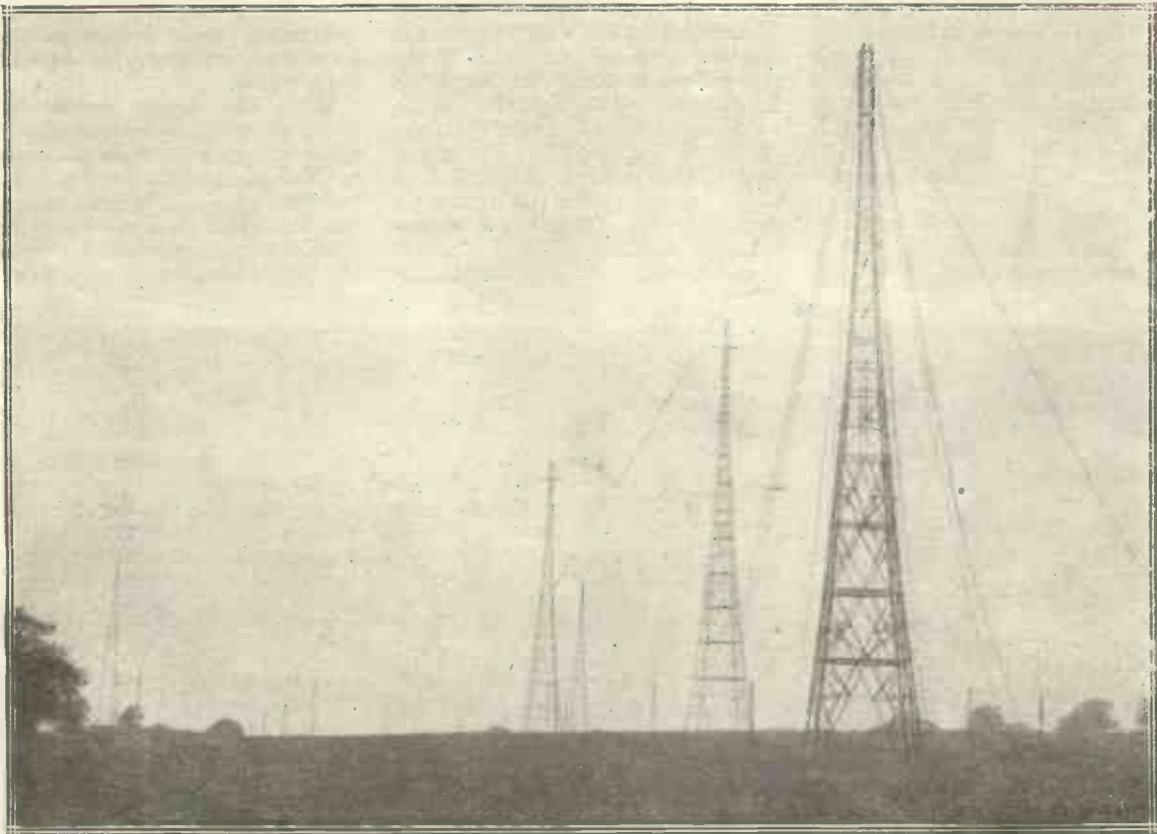As one had to rely largely on L.F. amplification, a high degree



The great aerial system of the Ongar Station contrasts with the type of that used for short wave transmission.

the coils arranged thus was actually $30\mu\text{F}$. The range, accordingly, was limited and not as low as it was desired to get. This was subsequently changed as indicated, the primary coil being arranged 1 in. above and away from the other, with favourable results.

In order to keep the effect of casual capacities still lower and to give an effective but finely controllable reaction, the grid coil was not put between grid and earth, but arranged after the manner of

circuit must be a particularly good one; a layer wound solenoid which operated well on 400 metres was useless here. A very narrow slab coil of, say, 300 turns of No. 32 enamel insulated wire, wound edge-wise in saw slots in a small plywood frame, sufficed admirably and was easily made. The outside diameter was about 3 in. with 1 in. centre.

A two plate fine tuning condenser and at least a 6 in. handle on each condenser are quite necessary, as

of amplification with but few valves (to avoid the usual "atmospherics") was sought with the aid of the D.E. 5B valve (with its M of 20) and a fairly high ratio transformer, the Pye No. 1. Small power amplification was used, on occasion, for the last valve, consisting of a high ratio U.S. "Super" L.F. transformer and a D.E. 5 valve (of fairly high M), each with its suitable grid bias and favourable H.T. The resulting L.F. amplification was terrific, and

great care had to be taken as to grid bias and arrangement of primary leads to avoid whistling. The effect of the high ratio valves and efficient transformer coupled amplification can be judged when it is mentioned that a buzzer wavemeter a couple of feet away from the set gave an overpowering roar from the loud-speaker. At first, although real atmospherics were not very bad in the receiver, nothing could be done at all with three valves until filter circuits were introduced into both detector and amplifier H.T. leads, consisting of audio-chokes (L.F. transformer secondaries) in series and $2\mu\text{F}$ condensers across them, as otherwise battery noises sounded like a distant artillery barrage. Then, although the real atmospherics were very bad on the longer waves, on the last occasion interfering appreciably with local broadcast reception, on 50 metres they were no more than an occasional swish or loud click, with the loose coupling and low resistance tuned circuits used here.

The results obtained in a necessarily brief trial of the circuit were very encouraging. With the

first arrangement of the primary right over the grid inductance, a number of successive harmonics of different broadcasting stations were picked up, using a vertical aerial of "Amplifitone Aerial" copper ribbon of about 8 ft. effective height above a corrugated iron shed-roof. Also, after the B.B.C. stations had closed down, another station, presumably of Continental origin, was heard.

Results

A test transmission from the German Telefunken station came in clearly and at good strength around 80 metres or so, being readily tuned in on the loud-speaker on two valves. (The receiver had not yet been calibrated.) Some extra-short wave experimental transmissions have been recently announced in the Press from this station. Several amateur Morse transmissions came in; some at loud-speaker strength on two valves.


When the modified arrangement, giving a lower range of wavelength, was tried on a succeeding night under quite unfavourable circumstances (very bad atmospherics, a damp, muggy, windless evening, and on a low horizontal

70 ft. test aerial, thoroughly screened locally, in Essex) at 10 p.m. there appeared to be little going on, but presently, on between 60 and 70 metres (about 150 degrees on condenser), a powerful wave came in (on the two valves), and by extremely careful tuning and reaction adjustment was recognised as speech and music, which persisted for a considerable time. The strength was about on a par with the irregular casual noises, so that, although the modulated wave was readily found on the L.S. (new pattern "Ultra") on three valves without headphones, the effect was not intelligible or enjoyable. On a more favourable night, undoubtedly KDKA would have been more enjoyable. Using the vertical 8 ft. aerial without any series condenser, some amateurs were heard very low down on the wavelength scale.

With the larger aerial more noises came in, and care had to be taken to set the series condenser so that the natural wavelength of the whole aerial and aperiodic coil was less than that on which one was receiving, as otherwise the set mysteriously refused to oscillate.



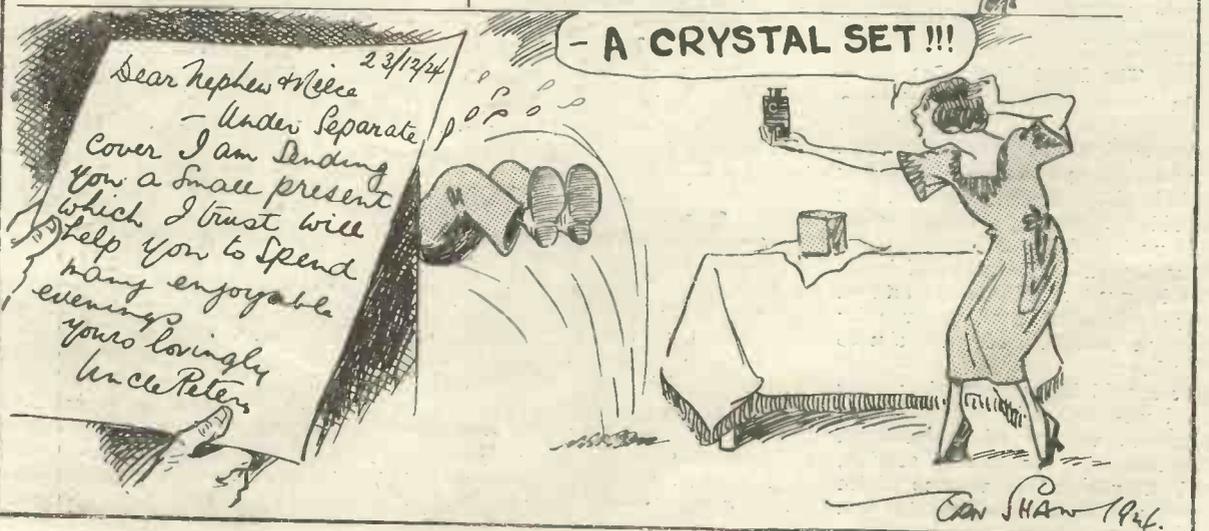Canadian trans-continental trains are now being equipped with wireless sets to relieve the monotony of long and tedious journeys.



UNCLE PETER'S CHRISTMAS BOX.

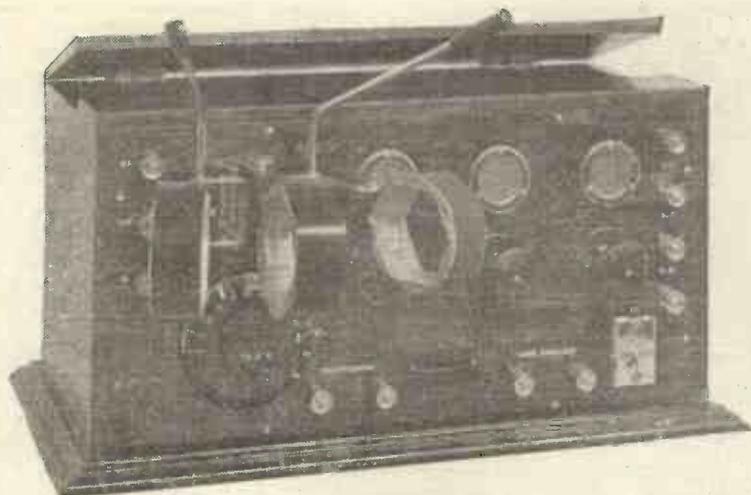


Fig. 1.—The set presents an extremely handsome appearance.

The Home Three-Valve Receiver

By E. REDPATH.

READERS with some little experience of wireless will no doubt agree that, when asked "What is the really ideal receiving set?" the reply must be to the effect that it depends upon the purpose for which the set is required.

In some circumstances a good crystal receiver may be ideal, whilst, in others, the use of two high-frequency valves and a detector valve may be indicated. The production of a good volume of sound from a loud-speaker may be the desire of one intending constructor, and the reception of distant stations in telephone receivers the special object of another.

Some enthusiasts may not object to the tuning of their receiver demanding a considerable amount of "knob twiddling," whilst with others simplicity of operation is a *sine qua non*.

The Ideal Home Set

In the opinion of the writer, a receiving set designed for the purpose of providing entertainment in the home should certainly include the following features. It should be easily operated, even by unskilled members of the owner's family; capable of being left in proper adjustment and of being put into or out of use by the movement of a simple switch.

It should be capable of making a loud-speaker reproduce an adequate volume of sound from the nearest broadcasting station, and a reasonable volume from two or more alternative stations. In order to accomplish this, a fair degree of selectivity should be provided for without complicating the tuning arrangement.

Complicated switching should be avoided, but it is certainly considered desirable that provision should be made for using one valve only with telephone receivers, which enables "searching" to be done with economy in current consumption and without the emission of sundry unpleasant noises from the loud-speaker, the change-over to "all valves and loud-speaker" being made when signals are satisfactory in the telephones.

Lastly, it is considered that the set should be suitable for use with bright or dull-emitter valves, compact and of pleasing appearance. All these requirements have been kept in view in the design and construction of the three-valve receiving set illustrated and described in these pages.

General Description

The external appearance of the completed set is shown in the photographs, Figs. 1 and 3. There are three valves—detector and two low-frequency amplifying valves—fitted inside the cabinet and visible, when their filaments are glowing, through the respective circular valve windows of wire gauze.

In order to provide for the reception of all wavelengths, "plug-in" inductance coils are employed in conjunction with a three-coil holder, seen on the upper left-hand side of the front panel in the photograph.

Immediately below the three-coil holder is the tuning condenser. The operation of the set, once the necessary external leads are connected, consists in rotation of this condenser dial and move-

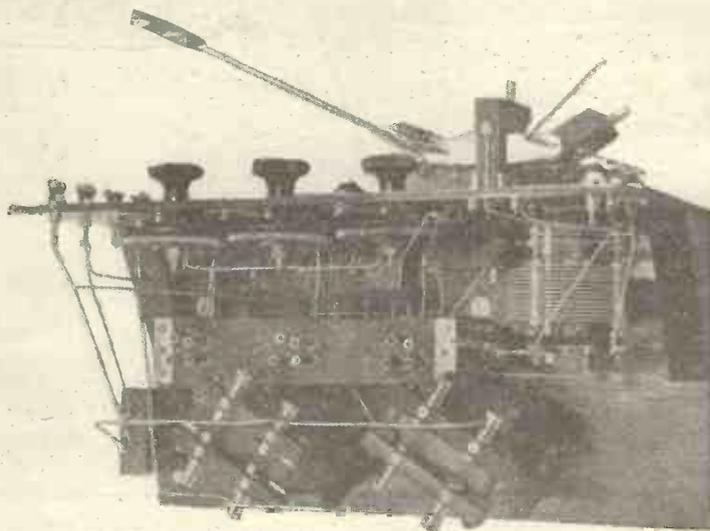


Fig. 2.—A plan view of the wiring.

In the following article Mr. Redpath gives full constructional details of a straight three-valve receiver which, by reason of its excellent appearance and ease of operation, will appeal particularly to those who desire to build the set for home use.

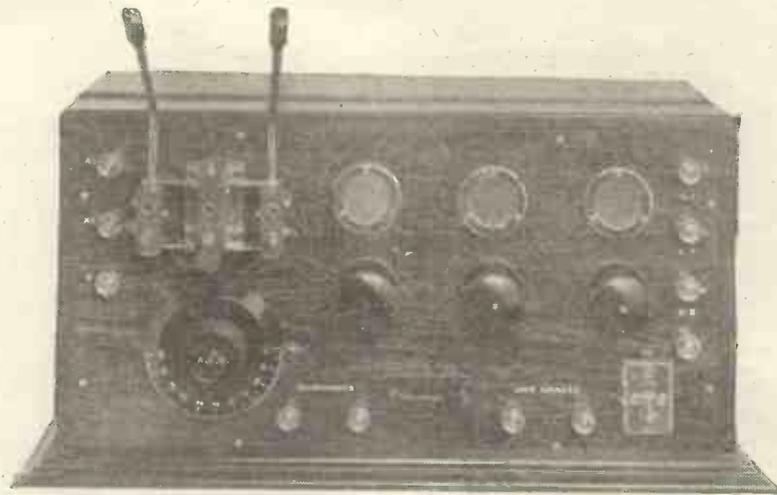


Fig. 3.—With coils removed, the terminal arrangements are clearly seen.

ment of the two outer coils by means of the extension handles on the coil holder.

The three terminals immediately on the left of the coil holder are for aerial and earth connections, and the four terminals on the extreme right of the panel are for the high tension, filament lighting and grid-bias batteries.

Telephone Terminals

Of the four terminals at the foot of the panel the two on the left are for telephone receivers, which are in use with one valve only when the lever of the centre switch (between the pairs of terminals) is over towards the left. Moving the lever of this switch to the right lights the two low-frequency valves and brings into operation the loud-speaker connected to the remaining pair of terminals at the foot of the panel, at the same time cutting out entirely the telephone receivers.

Filament Control

Each valve is provided with a separate filament rheostat to permit of individual adjustment

of filament brilliancy, and the filament current to all three valves is switched on or off by the small nickel-plated switch in the lower right-hand corner of the panel.

The Circuit Arrangement

Fig. 4 is a complete theoretical circuit diagram of the receiver. Referring to the figure, the filament lighting circuits, with three rheostats R and switches S₂ and S₃, may easily be traced. S₃ is the small switch which lights or extinguishes all three valves simultaneously, whilst S₂, in reality one arm of a double-pole change-over switch, cuts off the filament current from the two amplifying valves when the telephones are in use.

Tuning Circuits

With the aerial AE connected to the terminal A₁, the aerial circuit includes the untuned inductance coil L (the left-hand movable coil) which is inductively coupled to the fixed coil L₁. In these

circumstances, the inductance L₁ and variable condenser C₁ form a closed oscillatory or secondary circuit. By connecting the lower end of the coil L₁ to earth and providing an additional terminal A₂, the aerial lead may be connected to the upper end of L₁; the coil L may then be dispensed with and the set becomes a single circuit direct coupled receiver.

By using both coils, with a fairly loose coupling between them, the tuning will be found to be selective whilst single-control of tuning is retained. For instance, at a distance of about 15 miles from a broadcasting station (2 LO), the vernier of the variable condenser C₁ will be found very useful for fine adjustment of tuning.

Further, the coil L₁ may be much larger than when the aerial is connected to terminal A₂, with consequent increase in the wavelength range covered by a given coil on the condenser C₁.

The Oscillatory Circuit

The oscillatory circuit L₁C₁ is connected to the grid and filament positive of the first valve, the former connection being made via the usual grid condenser C₂ and gridleak R₂.

The anode or output circuit of the first valve includes the reaction coil L₂ (the right-hand movable coil) which is inductively coupled to the coil L₁ in the correct sense so as to produce a reaction or regenerative effect. L₂ is also connected to the change-over switch S₁ by means of which the connection to the positive terminal of the H.T. battery is completed, either through the telephone receiver TEL (shunted by the fixed con-

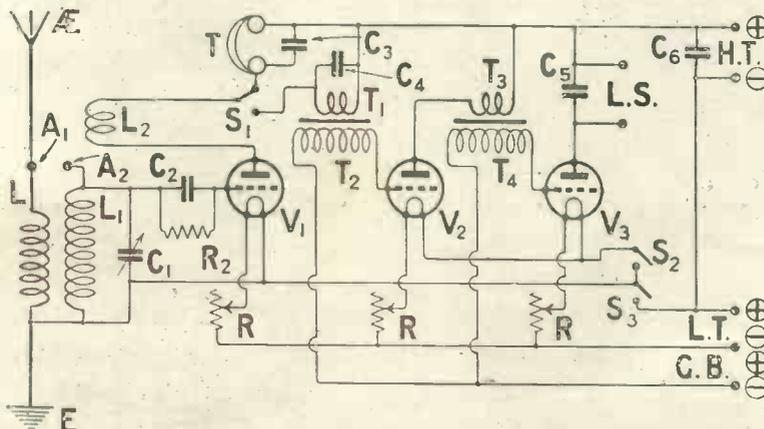


Fig. 4.—The theoretical circuit. Note, S₁ and S₂ are operated by the middle switch in Fig. 3.

denser C_3) or through the primary T_1 (shunted by fixed condenser C_3) of the low-frequency iron-core transformer T_1, T_2 .

Actually the switches S_1 and S_2 are mounted upon a common insulating spindle and moved together, so that when the telephones are put in circuit the filaments of the second and third valve are extinguished, being re-lighted when the switch S_1 connects to the primary of the iron-core transformer.

The L.F. Circuit

The rectified pulses of current in the anode circuit of the detector valve, traversing the primary winding of the transformer T_1, T_2 , induce currents of higher voltage in the secondary winding, one side of which is connected to the grid of the first amplifying valve, and the other, via the grid biasing battery, to the negative terminal of the filament lighting battery.

The amplified currents in the anode circuit of the first amplifying valve are further increased in potential and applied to the grid and filament negative of the third valve by means of the iron-core transformer and in the anode circuit of this latter valve is connected the loud-speaker shunted by the fixed condenser C_5 . C_5 is a large capacity fixed condenser, known as the reservoir condenser, connected directly across the H.T. terminals and therefore across the high-tension battery.

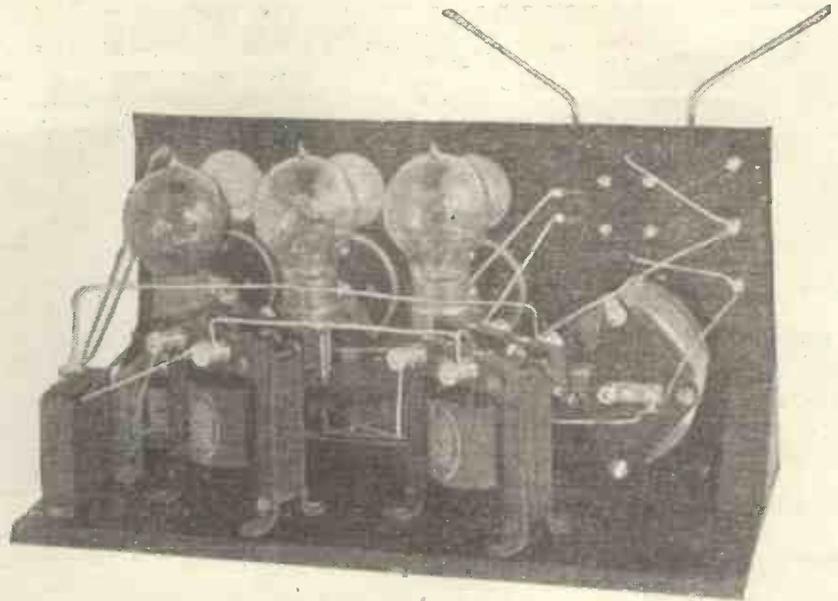


Fig. 5.—The transformers are mounted in staggered formation.

Components Required

The following is a list of components required, and includes (batteries, etc.), in addition to the items indicated in the circuit diagram, Fig. 4, the references of which are given to facilitate identification. For the convenience of readers, the make of components used in the original set is specified. Other good makes can of course be substituted.

- 1 Radion panel, 7 in. by 14 in. by 3/16 in. thick.
- 1 3-coil holder. (Burne-Jones, "Magnum.")
- 3 filament resistances, R, (Burndept, "Dual.")
- 3 valve windows (Bowyer Lowe).
- 1 variable condenser (0.0005 μ F with vernier). (Bowyer Lowe "Square Law.")
- 1 switch, S_3 , (Connecticut).
- 1 double-pole change-over switch


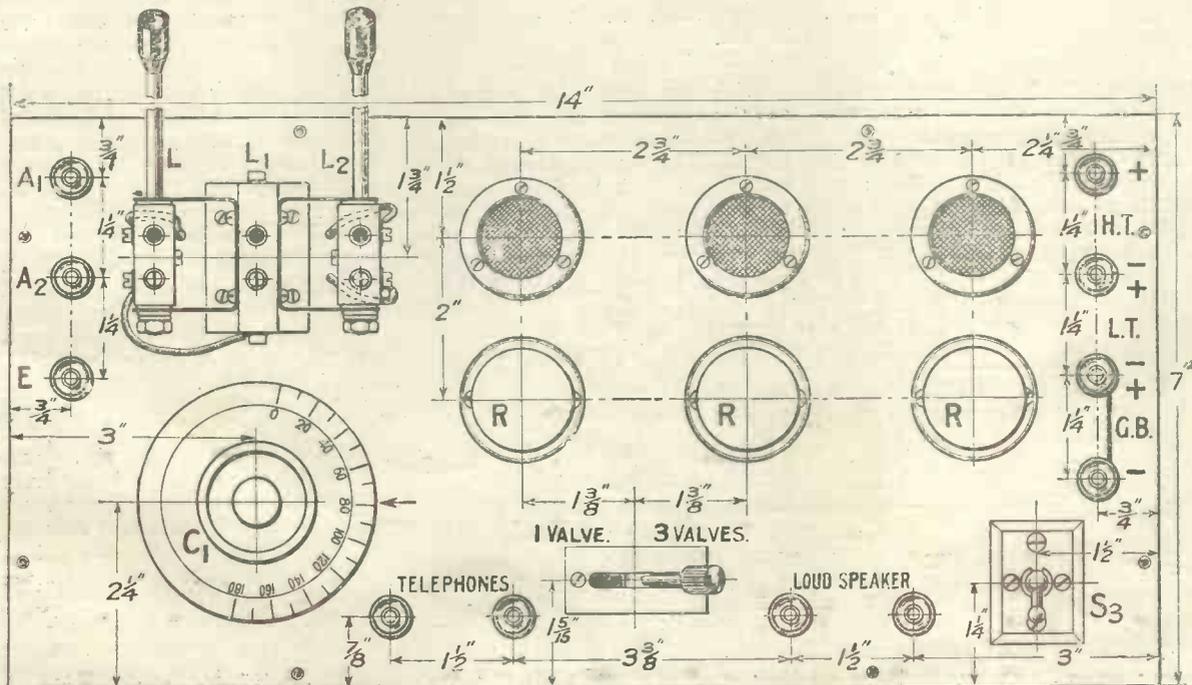


Fig. 6.—Front of panel drilling diagram. Blueprint No. 77A.

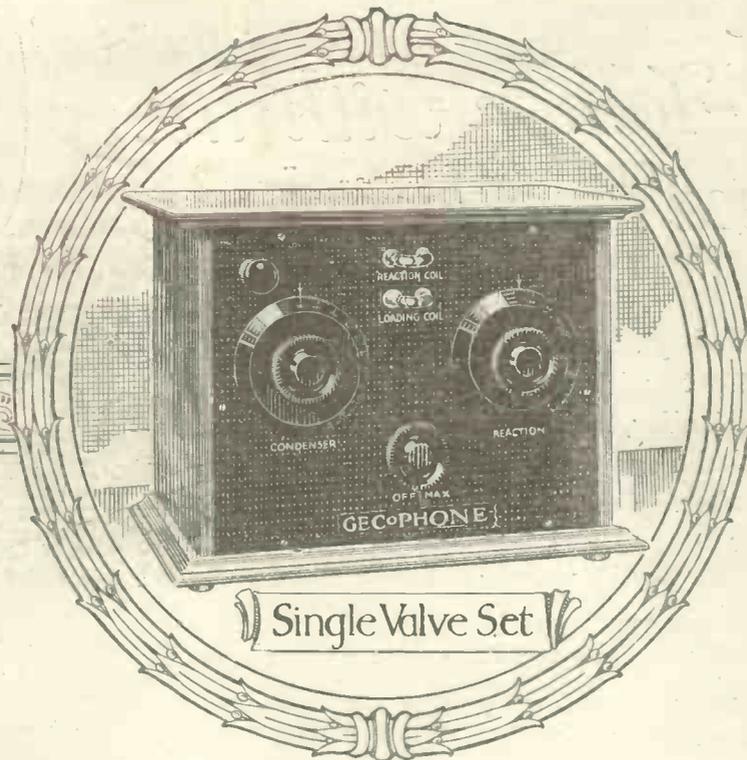

For Service & Satisfaction

GECOPHONE

(REGISTERED TRADE MARK)

NEW MODELS

The model illustrated above is the GECOPHONE Single Valve Set which meets the demand for an efficient popular-priced instrument. It is supplied either with D.E.R. Valve for use with an accumulator or with D.E.3 Valve for use with dry battery. In the latter form it is particularly useful to those living in the country or who do not wish to be bothered with the trouble of accumulator charging. It covers the British Broadcasting wave-length band, whilst Loading coils can be added for Chelmsford or higher wave-lengths. Its range for broadcasting is rated at 80-100 miles. Operation is simplicity itself. Connections are made simply by pushing plugs into sockets.

Cat. No. B.C. 3000, Set only with D.E.R. Valve	£5 18 0
Cat. No. B.C. 3001, Ditto, but with all necessary batteries, headphones, etc.	£10 0 0
Cat. No. B.C. 3050, Set only, with D.E.3 Valve	£7 12 0
Cat. No. B.C. 3070, Ditto, but with all necessary batteries, headphones, etc.	£10 5 0

Ask your dealer to demonstrate this model to you.

GECOPHONE Sets are sold by GECOPHONE SERVICE DEPOTS, Electrical Dealers, Stores, etc.

Ask for price list (No. B.C. 3425).


Advertisement of The General Electric Co., Ltd. (Manufacturers and Wholesale only), Magnet House, Kingsway, W.C.2.

Tune the Table-Talker with the "Matched Tone" Headphones




OH, boy! What fun you'd get with the *Table-Talker*, as well as your "Matched Tone" Headphones. Ask Father. Can you think of a better gift for Christmas?

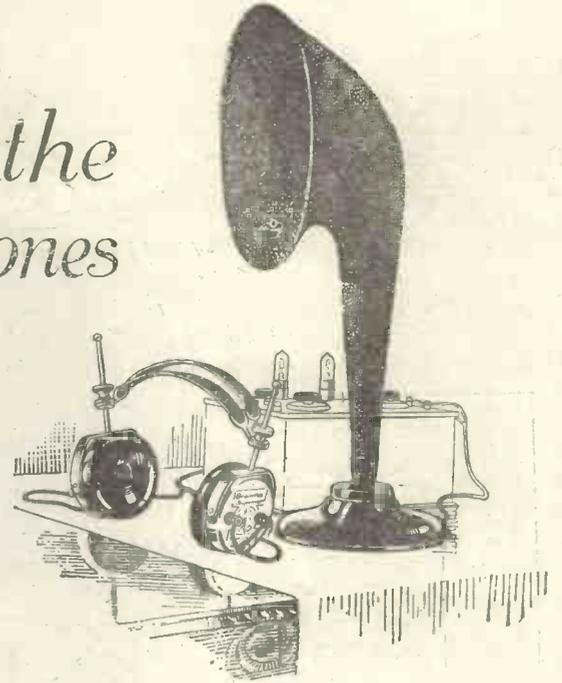Just real fun—fun for the Christmas Vac.—fun all the year round. You will hear every blessed word as plain as though your own form-master were speaking—and it's heaps more interesting. You'd hear real music just as loud as you hear that girl thumping on the piano next door—but no false notes. Oh, no! And it's so pleasantly natural. Ask your Dealer for Brandes.



All Brandes' products carry our official money-back guarantee, enabling you to return them within 10 days if dissatisfied. This practically constitutes a free trial.

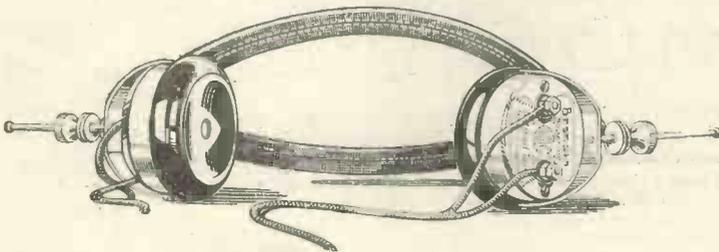The "Matched Tone" feature was embodied as the distinctive characteristic of Brandes Headphones in 1908, and means that both your ears hear exactly the same sound at the same instant—and you learn a new beauty of tone. They are tested and re-tested for just this one vital point, and in addition their strength, long-wearing comfort and reliable efficiency make them undoubtedly superior. **25/-**




The *Table-Talker* is a Brandes' quality product at a moderate price. The non-resonant specially constructed horn is matched to the unit so that the air resistance produced will exactly balance the mechanical power of the diaphragm. This means beautiful sound-balance and remarkable tone qualities. It is twenty-one inches high and has a self-adjusting diaphragm and is finished a shade of neutral **42/-** brown.

British Manufacture (B.B.C. Stamped)

Brandes

Result of
16 Years
Experience

The name
to know in Radio

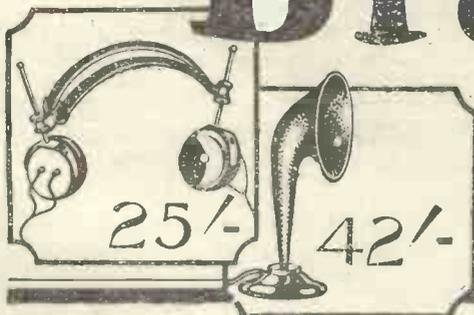

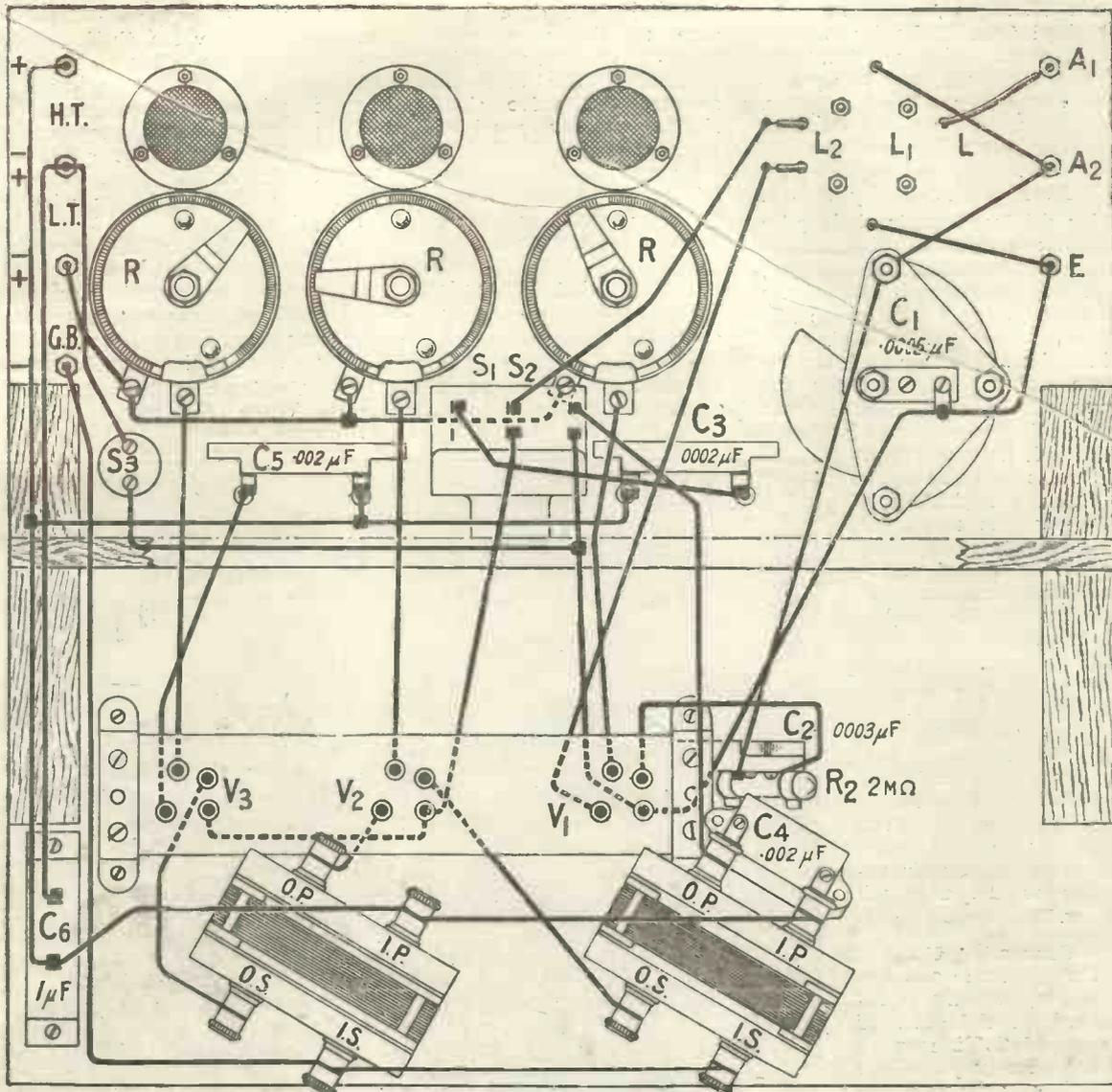


Fig. 7.—With the aid of this diagram wiring is a simple matter. Blueprint No. 77B.

S₁, S₂ (Wilkins and Wright "Utility").

2 L.F. transformers, T₁ T₂ T₃ T₄ (U.S. Radio "Super").

1 grid condenser C₂, (0.0003μF) and gridleak R₂, 2 megohms (Dubilier).

3 fixed condensers, C₃, C₄, C₅, each 0.002μF (Dubilier).

NOTE.—With some loudspeakers it may be found desirable to increase the capacity of the condenser C₅, say, to 0.004μF.

3 valve holders (i.e. 12 sockets).

1 strip of ebonite, 1½ in. by 7¼ in. by ¼ in. thick, and two mecano strips (13 holes) to make the valve shelf shown in Fig. 7.

1 fixed condenser, C₆, capacity 1μF. (T.C.C.)

11 terminals.

Tinned copper wire, 16 S.W.G., for internal connections.

1 mahogany cabinet. (Baker and Russell.)

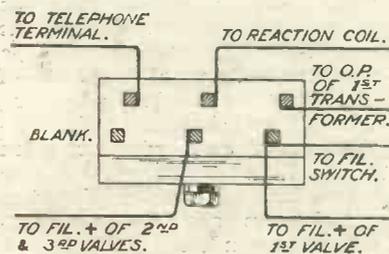


Fig. 8.—The double-pole switch connections.

Inductance Coils.

- 1 25 or 35 turn coil, L.
- 1 50 or 75 turn coil, L₁.
- 1 35 turn coil, L₂.

3 valves, bright or dull emitters. Any of the well-known makes of valves may be used, but it should be noted that the detector valve should be a hard valve, suitable for operating with a high-tension voltage of from 60 to 100 volts.

1 high-tension battery, 60 to 100 volts.

1 six-volt accumulator (for bright emitter valves), or dry battery to suit the particular type of dull-emitter valves used.

Grid battery suitable for anode voltages of 80 volts and over (a 4½ volt dry battery with accessible inter-cell connections).

Preparing the Panel

The ebonite panel should be carefully marked out in accordance with the drilling plan, Fig. 6.

or direct from the full-sized blue print (No. 77A), which may be obtained from Radio Press Sales Department, price 1s. 6d., post free. There are only two points which may prove difficult, namely, the cutting of the 1-inch diameter holes for the valve windows and filament switch and the slot for the lever of the Utility switch.

By drilling a centre hole $\frac{3}{16}$ inch or $\frac{1}{4}$ -inch in diameter in the centre of each 1-inch circle, and the subsequent careful use of an ordinary 1-inch centre bit on both sides of the panel, discs of ebonite will be removed, leaving clean holes. The slot for the lever of the switch can be cut by drilling a series of $\frac{3}{16}$ -inch holes and filing, or by the use of a fretsaw.

When the drilling of the panel is completed, all terminals, valve windows, filament rheostats, variable condenser and switches may be fitted in place and the panel itself may be secured to the false bottom of the cabinet, as shown in Fig. 10.

Now construct the valve shelf and place it in position according to the measurements given in Fig. 10, but at this stage do not fit the transformers, reservoir condenser or the three-coil holder.

Connecting Up

The general arrangement of all the components at the back of the panel is illustrated in the photographs, Figs. 2 and 5, and although it may look as if the wiring would prove very complicated, it is not so in reality, and all that is required is a little patience and care in the use of the soldering iron.

Deal with the filament lighting circuit first. Solder one end of a length of the 16 gauge tinned wire to the L.T. negative terminal, secure it beneath the screw on the third rheostat (adjacent to the battery terminals) and pass on to the corresponding screw on the second rheostat. A shorter piece of wire can then be secured beneath the screw of the first rheostat and then soldered to the first wire.

Connecting the Valve Panel

Next make loops in the ends of two pieces of wire, and secure one to the first and the other to

the third rheostat, and solder the remaining end of each piece of wire to the negative filament socket of the first and third valve-holders. The stiff wire will support the valve shelf fairly rigidly, and the panel and shelf together may be entirely removed from the wooden baseboard and laid face downward upon the table or bench to facilitate the work of connecting up.

Remaining Connections

The remaining connections are to be made in accordance with the wiring diagram (Fig. 7), a full-sized blue print of which is available. In order to overcome

transformers after the completely wired panel with variable condenser attached, valve shelf and transformers are all secured in place upon the wooden baseboard. The remaining transformer connections and the connections to the reservoir condenser do not present any difficulty.

The grid condenser, with clip-in gridleak, is soldered direct to the grid socket of the first valve, but if this method is found inconvenient, a length of wire may be soldered to the grid socket, and the condenser and leak may be brought up close to the variable condenser.

Testing and Operating the Set

When the set is wired up

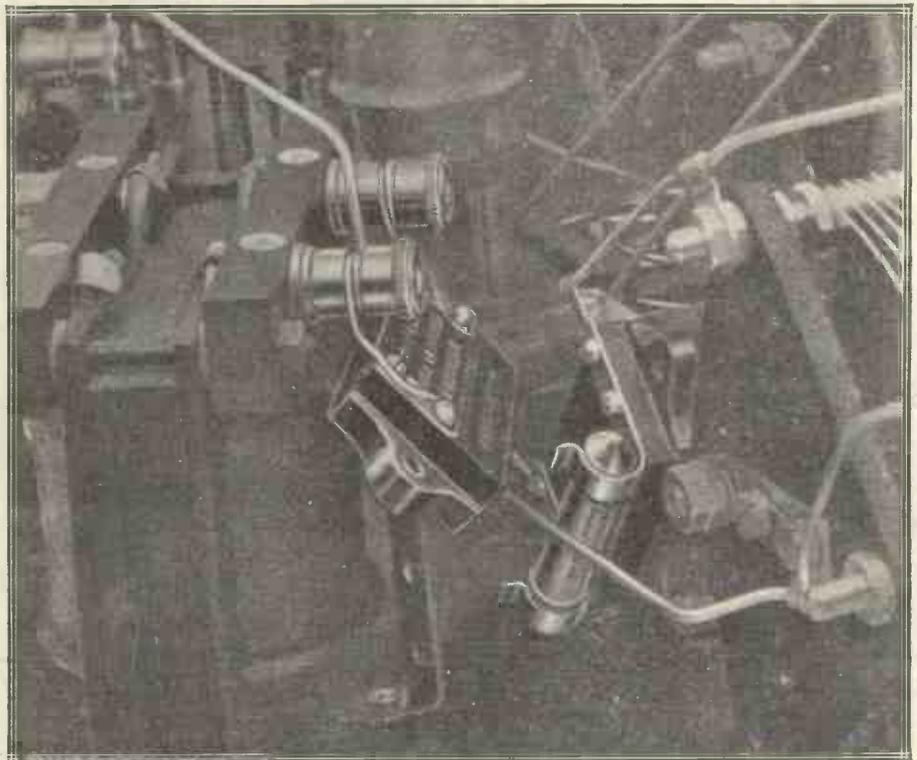


Fig. 9.—This photograph shows how the grid condenser is supported.

any difficulty which may be experienced in connecting up the double-pole change-over switch, a separate drawing of the back of this switch, showing projecting "tabs" and indicating the destination of each wire, is given in Fig. 8.

So far, of course, the two transformers and reservoir condensers are not in position. A piece of the copper wire, about 8 inches in length, is to be soldered to the grid socket of the second and third valve, and to the anode socket of the first and second valve, and left projecting for subsequent connection to the L.F.

complete, make a preliminary test as follows:

Connect the six-volt accumulator to the correct terminal, place the filament switch in the "off" position and insert three valves. Place the lever of the change-over switch to the right, turn all three filament rheostats back to zero, move the filament switch to the "on" position and light the filament of each valve in turn by means of its own rheostat. With all three valves alight, move the change-over switch to the left, which should extinguish the two amplifying valves. Moving the filament

LISSENIUM

TYPES OF MAGNETIC CONCENTRATION

With many types of coils the magnetic field is mostly concentrated in the centre of the coil, and the field does not extend to any appreciable degree. The characteristics of the magnetic field in such coils is closely analogous to the ordinary solenoid inductance.

In the case of LISSENIUM (pronounced LISSEN-AGON) coils, however, the magnetic field, in addition to being very strong in the centre of the coil, is also distributed on each side of the coil. This accounts for the remarkably strong magnetic linkage obtained with LISSENIUM coils in reaction circuits, and ALSO FOR THE PECULIAR EFFICIENCY OF THE COILS WITH EDDY CURRENT TUNING.


LISSENIUM TUNING CHART.

Note the Intermediate coils, 30, 40 and 60.

TABLE I. Wavelength range when used as Primary Coils with Standard P.M.G. Aerial and '001 mfd. condenser in parallel.			TABLE II. Wavelength range when used as Secondary Coils with '001 mfd. condenser in parallel.		
No. of Coil.	Minimum Wave- length.	Maximum Wave- length.	Minimum Wave- length.	Maximum Wave- length.	PRICE.
25	185	350	100	325	4/10
30	235	440	130	425	4/10
35	285	530	160	490	4/10
40	360	675	200	635	4/10
50	480	850	250	800	5/-
60	500	950	295	900	5/6
75	600	1,300	360	1,100	5/4
100	820	1,700	500	1,550	6/6
150	965	2,300	700	2,150	7/7
200	1,885	3,200	925	3,000	8/5
250	2,300	3,800	1,100	3,600	8/9
300	2,500	4,600	1,400	4,300	9/2



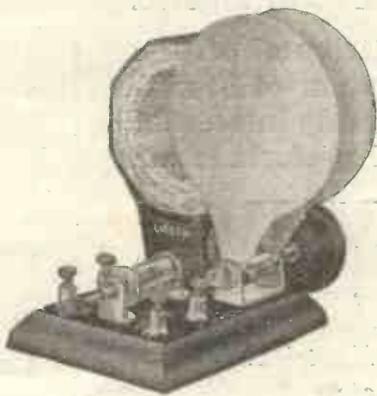IF YOU EVER WANT
COILS WHICH INTEN-
SIFY TUNING — USE
LISSENIUM COILS



SIGNALS ARE ALWAYS STRONGER —

when capacity is low and inductance is high. If, where, say, a No. 35 coil is ordinarily used with added capacity to tune it to a given wavelength, a No. 60 coil can be used, AND WITHOUT ADDED CAPACITY, other things being equal, it follows that signals would be stronger.

In the new LISSENIUM CRYSTAL SET a form of tuning has been introduced which permits of a No. 60 LISSENIUM (pronounced LISSEN-AGON) coil being used, and dispenses with the need of added capacity to tune it. A big signal voltage is built up. But apart from its high inductance efficiency, too, there are other considerations which place this receiver far above all other crystal sets, NO MATTER WHAT THE PRICE.

THERE IS AN UNDISTURBED ELECTRICAL CIRCUIT, for instance. The only moving part is the metal plate, and although this is entirely unconnected with the electrical circuit, its influence on the inductance is effectively applied through the medium of the magnetic field created.

In conjunction with the principle of EDDY CURRENT TUNING employed in this new LISSENIUM CRYSTAL SET, LISSENIUM COILS ARE PECULIARLY EFFICIENT. No other coils give the same results.

By fitting the appropriate LISSENIUM (pronounced LISSEN-AGON) coil, the LISSENIUM CRYSTAL SET can be used for any station within range. Two coils would be needed for London and Chelmsford, for instance—to change over from one station to the other, take one LISSENIUM coil out, and plug the other one in.

On long aerials it would be possible to use a coil one size less in each case e.g., No. 40 instead of 50; 50 instead of 60; 60 instead of 75; 200 instead of 250.

NOTE.—One LISSENIUM coil must be ordered with each set—the receiver will not be sold without a LISSENIUM coil because the use of these coils ensures very high efficiency.

- Price of receiver (includes crystal), patent pending .. **10/-**
- No. 50 LISSENIUM coil (covers 300 to 350 metres on this receiver) **5/-**
- No. 60 LISSENIUM coil (covers 350 to 400 metres on this receiver) **5/4**
- No. 75 LISSENIUM coil (covers 400 to 500 metres on this receiver) **5/4**
- No. 250 LISSENIUM coil for Chelmsford **8/9**

No paper—no cardboard—no loose contacts—no loose wires—connections are stamped-out strips—the whole receiver is an instrument throughout—robust—and THE MOST EFFICIENT CRYSTAL SET MADE—WITH THE MOST EFFICIENT INDUCTANCE.


LISSENIUM LIMITED,

20-24, WOODGER ROAD, GOLDHAWK ROAD, SHEPHERD'S BUSH, LONDON, W.12.

TELEPHONES : Riverside 3380, 3381, 3382, 1072.

TELEGRAMS : "Lisssenium, London."

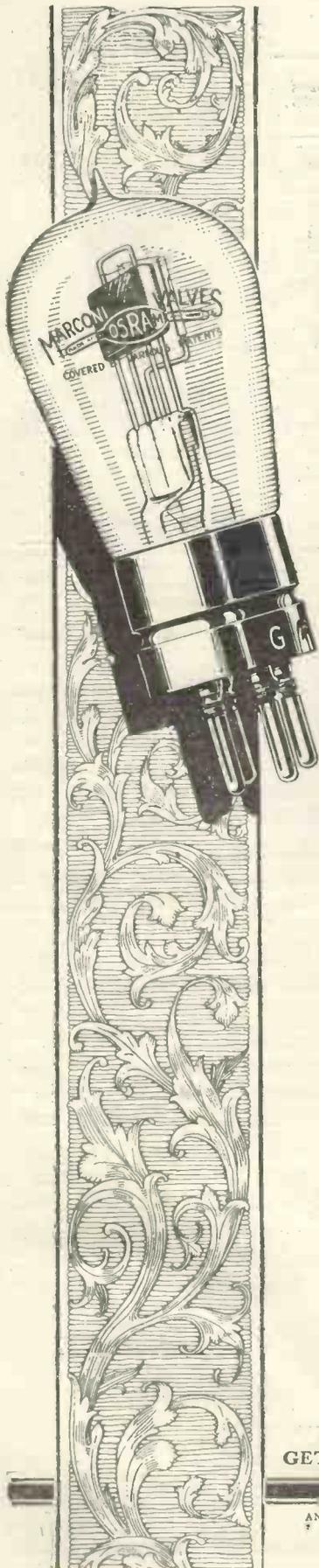In replying to Advertisers, please use Order Form enclosed.



The HEART of WIRELESS

As the human heart is to the human body, as the lens is to the camera, and the engine to the motor car, so is the valve to the wireless set.

It is the main essential 'Get the essentials right' is the common-sense policy in wireless reception as in all else.

Common-sense is the attribute of the majority, and perfect reception of broadcasting the aim of every keenly interested listener ; hence the general preference for

MARCONI VALVES
MADE AT THE OSRAM LAMP WORKS

Sold by Wireless and Electrical Dealers, Stores, etc.

Have you read the now famous wireless publication—The Book of MOV ? It is the most authoritative work of its kind—and free. Get a copy at once from your dealer, or cut out and use the voucher below.

Messrs. The M.O. VALVE Co., Ltd.
Brook Green, London, W. 6.


Please send me, post free, a copy of The Book of MOV.

Name

Address



.....

M.W.—Dec.

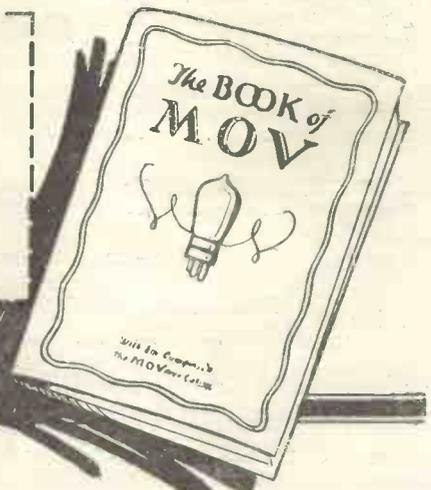

GET THE VALVE IN THE PURPLE BOX!

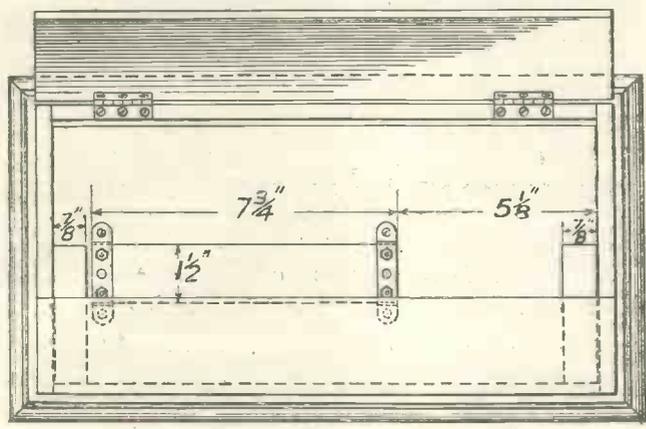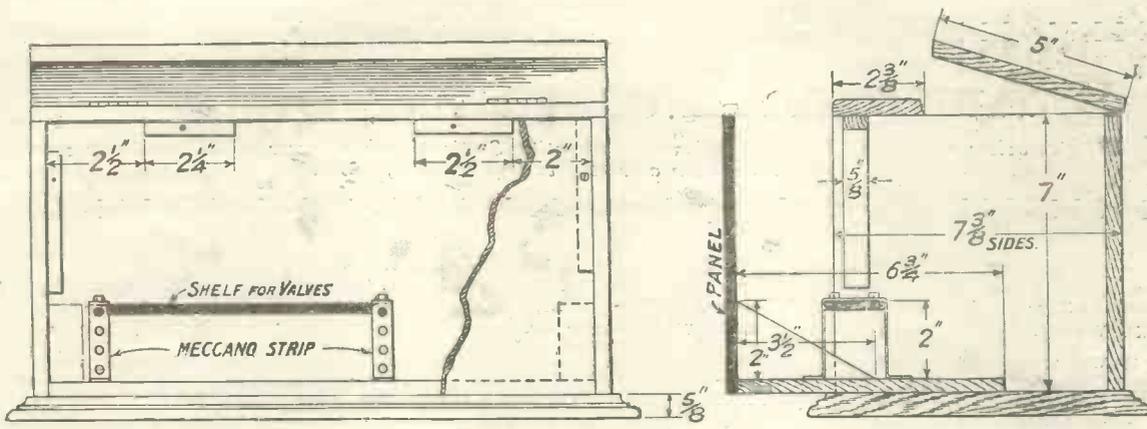ANNOUNCEMENT OF THE M. O. VALVE COMPANY, LIMITED.



NOTE:—ALL WOOD FINISHED $\frac{3}{8}$ " THICK, UNLESS DIMENSIONED OTHERWISE

Fig. 10.—The position of the valve shelf and dimensions of this and the cabinet may be obtained from these diagrams,

switch to the "off" position should extinguish one or all valves.

Coils to Use

If this preliminary test is satisfactory, connect up telephones, loud-speaker and high-tension battery. Also connect the earth lead to terminal E and, to commence, the aerial lead to terminal A₂. This, it will no doubt be remembered, gives a direct coupled single circuit receiver. Two coils only are required, a No. 35 or a No. 50 turn coil in the fixed holder and a No. 50 (or possibly a No. 75) coil in the reaction coil-holder.

Switch over to "one-valve-and-telephones" and, keeping the reaction coil well away from the aerial coil, search for signals by slowly rotating the variable condenser.

Reaction Effects

When signals are received, moving the reaction coil nearer to the aerial coil should strengthen signals considerably, but care must be taken not to make the coupling between the coils too tight or distortion of the speech, music, etc., will occur, whilst still further

tightening of the coupling, i.e., increase of reaction effect, will cause the set to generate oscillations, and not only prevent satisfactory reception, but most certainly cause considerable interference with other receiving sets in the vicinity. If the proper reaction effect is not obtained at the first attempt, reverse the leads on the coil-holder.

The change-over from direct to inductively-coupled tuning is effected by transferring the aerial lead from terminal A₂ to terminal A₁, inserting a No. 25 coil in the left-hand movable holder, a No. 50 or 75 turn coil in the fixed holder and a 35 turn coil in the reaction or right-hand holder.

It will now be found that tuning with the variable condenser is very much sharper, the reaction effect is easier, and, provided that the correct coupling between the aerial and secondary coil is obtained, signals from the local broadcasting station will be at least as strong as with the previous arrangement.

The Coupling

Generally an angle of about 25 to 30 degrees between the

coils will be about right, and the further the aerial coil is away from the secondary the more selective will the tuning become. Therefore, when searching for a more distant station, commence by having the aerial coil fairly close to the secondary coil and bring up the reaction coil to the safe limit. If the aerial coil is now moved further away from the secondary coil, the set may break into oscillation and it may be found necessary to reduce the reaction coupling.

Test Report

Within a few hours, of experimenting with the set, very loud signals from the local station, 15 miles distant, were obtained; reasonably loud music, etc., from Newcastle, Glasgow, and Birmingham, and moderate loud-speaker signals only from Cardiff and Aberdeen.

All these of course were audible in the telephone receivers, using only one valve. Unless they are, it is of little avail to add low-frequency amplifying valves and the loud-speaker. The experiences of readers who construct the set, particularly with regard to the slight departure from the ordinary in the tuning arrangement, will be received with interest by the writer.

American Broadcasting Stations

We give below a complete list of American Broadcasting Stations with a power of 250 watts or over, which has been corrected to September 2, 1924.

Call Letters	Name	Location	Power and Wave Length	Call Letters	Name	Location	Power and Wave Length	Call Letters	Name	Location	Power and Wave Length
KDKA	Westinghouse Electric & Mfg. Co., East Pittsburgh, Pa.		1000-326	WBAP	Wortham-Carter Publishing Co. (Star-Telegram), Fort Worth, Texas		750-476	WJAR	The Outlet Co. (J. Samuels & Bro.), Providence, R.I.		500-360
KDPM	Westinghouse Electric & Mfg. Co., Cleveland, Ohio		500-270	WBAV	Erner & Hopkins Co., Columbus, Ohio		500-423	WJAS	Pittsburgh Radio Supply Co., Pittsburgh, Pa.		250-286
KFAE	State College of Washington, Pullman, Wash.		500-330	WBAY	The Western Electric Co., N.Y.		500-492	WJAX	Union Trust Co., Cleveland, Ohio		500-300
KFAF	Western Radio Corporation, Denver, Colo.		500-273	WBBG	Irving Vermilya, Mattapoisett, Mass.		500-248	WJJD	Mooseheart, Mooseheart, Ill.		500-278
KFCL	Leslie E. Rice, Los Angeles Union Stock Yards, Los Angeles, Calif.		500-236	WBBR	Peoples Pulpit Association, Rossville, N.Y.		500-273	WJY	R. C. A., New York, N.Y.		750-405
KFGH	Leland Stanford University (P. O.), Stanford Univ., Calif.		273-369	WBT	Southern Radio Corp., Charlotte, N.C.		250-360	WJZ	R. C. A., New York, N.Y.		500-455
KFGX	First Presbyterian Church, Orange, Texas		500-250	WBZ	Westinghouse Electric & Mfg. Co., Springfield, Mass.		1000-337	WKAR	Michigan Agriculture College, East Lansing, Mich.		500-280
KFGZ	Emmanuel Missionary College, Berrien Springs, Mich.		500-286	WCAD	St. Lawrence University, Canton, N.Y.		250-280	WKBF	Dutec W. Flint, Cranston, R.I.		500-286
KFI	Earle C. Anthony, Inc., Los Angeles, Calif.		500-469	WCAE	Kaufman & Baer Co., Pittsburgh, Pa.		500-462	WLBL	Wisconsin Department of Markets, Stevens Point, Wis.		500-278
KFLX	Reorganised Church of Jesus Christ of Latter Day Saints, Independence, Mo.		250-240	WCAJ	Nebraska Wesleyan University, University Place, Neb.		500-283	WLS	Sears, Roebuck & Co., Chicago, Ill.		500-345
KFKB	Brinkley-Jones Hospital Association, Milford, Kan.		500-286	WCAL	St. Olaf College, Northfield, Minn.		500-310	WLW	Crosley Radio Corp., Cincinnati, Ohio		500-423
KFKX	Westinghouse Electric & Mfg. Co., Hastings, Neb.		1000-236	WCAP	Chesapeake & Potomac Telephone Co., Washington, D.C.		500-469	WMAF	Round Hills Radio Corp., Dartmouth, Mass.		100-500-360
KFMX	Carleton College, Northfield, Minn.		500-283	WCAU	Durham & Co., Philadelphia, Pa.		250-286	WMAK	Lockport Board of Commerce, Lockport, N.Y.		500-273
KFNF	Henry Field Seed Co., Shenandoah, Iowa		500-266	WCAV	Milwaukee Civic Broadcasting Station, Milwaukee, Wis.		250-266	WMAQ	Chicago Daily News, Chicago, Ill.		500-413
KFOA	Rhodes Dept. Store, Seattle, Wash.		500-455	WCBD	Wilbur G. Voliva, Zion, Ill.		500-345	WMAV	Alabama Polytechnic Inst., Auburn, Ala.		500-250
KFPO	Colorado National Guard, Forty-fifth Division Tank Co., Denver, Colo.		500-231	WCBK	E. Richard Hall, St. Petersburg, Fla.		500-266	WMC	Commercial Memphis, Tenn.		500-500
KFPR	Los Angeles County Forestry Department, Los Angeles, Cal.		500-231	WCBT	Clark University, Worcester, Mass.		250-238	WMH	Ainsworth-Gates Radio Co., Cincinnati, Ohio		750-309
KFPT	Cape & Johnson, Salt Lake City, Utah		500-263	WCX	The Detroit Free Press, Detroit, Mich.		500-517	WNVC	City of New York, New York, N.Y.		1000-526
KFQX	Alfred M. Hubbard, Seattle, Wash.		250-233	WDAE	Tampa Daily Times, Tampa, Fla.		250-360	WOAI	Southern Equipment Co., San Antonio, Texas		500-335
KFQZ	Taft Radio Co., Hollywood, Calif.		250-240	WDAF	Kansas City Star, Kansas City, Mo.		500-411	WOAW	Woolmen of the World, Omaha, Neb.		500-526
KFSG	Echo Park Evangelistic Association, Los Angeles, Calif.		500-278	WDBY	Lit Bros., Philadelphia, Pa.		500-395	WOAX	Franklyn J. Wolf (Monument Pottery Co.), Trenton, N.J.		500-240
KGO	General Electric Co., Oakland, Calif.		1000-312	WDFW	North Shore Congregational Church, Chicago, Ill.		500-258	WOC	The Palmer School of Chiropractic, Davenport, Iowa		500-484
KGU	Marion A. Milrony, Honolulu, Hawaii		500-360	WDFW	American Telephone & Telegraph Co., New York, N.Y.		1000-492	WOI	Iowa State College, Ames, Iowa		500-360
KGW	Portland Morning Oregonian, Portland, Ore.		500-492	WEAF	Cornell University, Ithaca, N.Y.		500-286	WOO	John Wanamaker, Phila., Pa.		500-509
KHJ	Times Mirror Co., Los Angeles, Calif.		500-395	WEAI	The Ohio State University, Columbus, Ohio		500-360	WOQ	Western Radio Co., Kansas City, Mo.		500-360
KJS	Bible Institute of Los Angeles, Los Angeles, Calif.		750-360	WEAO	Will Horwitz, Jr., Houston, Texas		500-360	WDR	L. Bamberger & Co., Newark, N.J.		500-405
KLS	Warner Bros. Radio Supplies Co., Oakland, Calif.		250-360	WEAY	Edgewater Beach Hotel Co., Chicago, Ill.		1000-370	WOS	Missouri State Marketing Bureau, Jefferson City, Mo.		500-441
KLX	Tribune Publishing Co., Oakland, Calif.		250-509	WEBH	Third Ave. Ry. Co., New York, N.Y.		500-273	WPAB	Pennsylvania State College, State College, Pa.		500-283
KLZ	Reynolds Radio Co., Denver, Colo.		500-283	WEBJ	The Dallas News, The Dallas Journal, Dallas, Texas		500-476	WQAA	Horace A. Beale, Jr., Parkersburg, Pa.		500-360
KOB	New Mexico College of Agriculture and Mechanic Arts, State College, N.M.		500-360	WFAA	University of Nebraska, Dept. E. E. Lincoln, Neb.		250-275	WQJ	Calumet Rainbo Broadcasting Co., Chicago, Ill.		500-448
KOP	Detroit Police Dept., Detroit, Mich.		500-286	WFAV	Concourse Radio Corp., New York, N.Y.		500-273	WRBC	Immanuel Lutheran Church, Valparaiso, Ind.		500-278
KPO	Hale Bros., San Francisco, Cal.		500-423	WFBH	Strawbridge & Clothier, Philadelphia, Pa.		500-395	WRC	Radio Corp. of America, Washington, D.C.		500-469
KQV	Doubleday Hill Electric Co., Pittsburgh, Pa.		500-270	WFI	The South Bend Tribune, South Bend, Ind.		250-360	WRL	Union College, Schenectady, N.Y.		500-360
KSD	Post Dispatch (Pulitzer Pub. Co.), St. Louis, Mo.		500-546	WGAZ	Thomas F. J. Howlette, Philadelphia, Pa.		500-360	WRM	University of Illinois, Urbana, Ill.		500-360
KTW	First Presbyterian Church, Seattle, Wash.		750-360	WGN	Drake Hotel-Whitestone Co., Chicago, Ill.		1000-370	WRW	Tarrytown Radio Research Laboratory (Koenig Bros.), Tarrytown, N.Y.		500-273
KWH	Los Angeles Examiner, Los Angeles, Calif.		250-360	WGR	Federal Telephone Mfg. Co., Buffalo, N.Y.		750-319	WSAC	Clemson Agricultural College, Clemson College, S.C.		500-360
KYW	Westinghouse Electric & Mfg. Co., Chicago, Ill.		1000-536	WGY	General Electric Co., Schenectady, N.Y.		1000-380	WSAI	United States Playing Cards Co., Cincinnati, Ohio		500-309
WAAC	Tulane University, New Orleans, La.		400-360	WHAS	Courier-Journal and Louisville Times, Louisville, Ky.		500-400	WSAJ	Grove City College, Grove City, Pa.		250-360
WAAM	I. R. Nelson Co., Newark, N.J.		250-263	WHAZ	Rensselaer Polytechnic Institute, Troy, N.Y.		500-380	WSAP	Seventh Day Adventist Church, New York, N.Y.		250-263
WAAW	Omaha Grain Exchange, Omaha, Neb.		500-286	WHB	Sweeney School Co., Kansas City, Mo.		500-411	WSB	Atlanta Journal, Atlanta, Ga.		500-429
WABN	Ott Radio, Inc., LaCrosse, Wis.		500-244	WHN	George Schubel, Loew's State Theatre Bldg., New York, N.Y.		500-360	WSY	Alabama Power Co., Birmingham, Ala.		500-360
WABX	Henry B. Joy, Mount Clemens, Mich. (near)		500-270	WHO	Bankers Life Co., Des Moines, Iowa		500-526	WTAM	Willard Storage Battery Co., Cleveland, Ohio		1000-390
WBAA	Purdue University, West Lafayette, Ind.		250-283	WIAK	Journal-Stockman Co., Omaha, Neb.		250-278	WTAS	Charles E. Erlstein, Elgin, Ill. (near)		500-286
				WIP	Gimbel Bros., Philadelphia, Pa.		500-509	WTAW	Agricultural & Mechanical College, College Station, Texas		250-280
				WJAG	The Norfolk Daily News, Norfolk, Neb.		250-283	WTAY	Oak Leaves Broadcasting Station, Oak Park, Ill.		500-283
								WWI	Ford Motor Co., Dearborn, Mich.		250-273
								WWJ	Detroit News (Evening News), Detroit, Mich.		500-517



Sterling Baby Loud Speaker

How quickly Christmas comes round. Well, there's one thing about Christmas 1924 that is more easily solved than ever before, and that is the question of Presents: One would have to go a long way before one found a better gift than the Sterling "Baby" Loud Speaker.

For fifty-five shillings the Sterling "Baby" Loud Speaker brings years of constant entertainment and is ever a reminder of the kindly spirit prompting the gift.

Every Radioist knows that the "Baby" was the first perfect junior loud speaker, remains the most perfect, and that if ever a better junior loud speaker is produced, the Sterling Company will produce it.

There will be tens of thousands of people saying this year: "Now we shall have a Merry Christmas."

The Sterling "Baby" Loud Speaker is supplied in **55/-**
 Black, or Brown tinted finish; 2,000 ohms resistance
 Black and Gold floral design - - - £2:17:6
 Black matt finish, decorated in Oriental style £4:15:0


Give Radio Presents this Xmas.

A few suggestions.—Sterling Lightweight Headphones; "Baby," "Dinkie," "Audi vox" and "Primax" Loud Speakers, and the "Amplivox"—a Loud Speaker and Amplifier combined.

Your Radio Dealer can supply

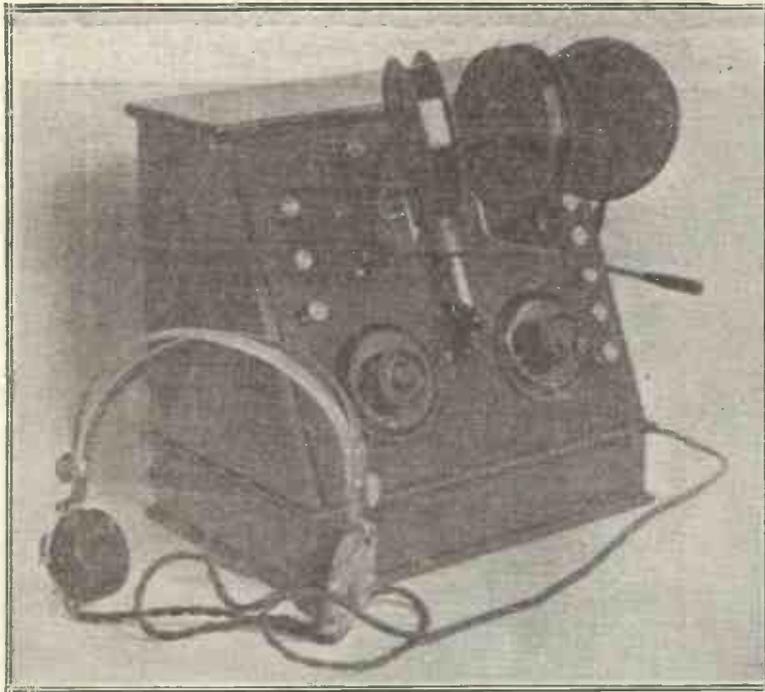Adot. of **STERLING TELEPHONE & ELECTRIC CO., LTD.**, Manufacturers of Telephones and Radio Apparatus, etc.
 210-212, Tottenham Court-Road, London, W.1. Works - - DAGENHAM, ESSEX





The complete receiver is of very handsome appearance.

A Long-Distance Single-Valve Receiver

BY JOHN W. BARBER.

THOSE readers who habitually use two or more valves in their receivers, and who have not given much thought to the modest one-valve set, will have missed a great deal of interesting work, and also, incidentally, a lot of valuable instruction. A single valve receiver, on a reasonably efficient aerial, will give results which are, in frequent cases, envied by users of two or more valves, the reason being that an experimenter who really means to get the best out of his one-valver gets right down to it, and traces out all possible causes of inefficiency in his apparatus, while his fellow worker may be content to add another valve. Many examples of excellent long-distance reception are known in cases where one-valve sets are in use, and when the experimenter is desirous of getting the utmost out of every valve he uses, he will do well to study thoroughly the possibilities of the single-valve set first before proceeding further.

The Circuit

The present receiver is modelled on the lines of a modification of the well-known Flewelling circuit, and has given excellent results in at least three cases well known to the writer. This modification of the circuit is very easy to handle, and as a loosely coupled aerial circuit is employed the circuit is exceedingly selective. A beginner even, therefore, may have

no qualms about making up this set, as he will find both the construction and operation quite simple, and he will gain much valuable knowledge which will be of great benefit to him when he decides to "graduate" to more valves.

General Considerations

Owing to the proximity of my station to 2LO, I am, naturally, troubled by interference from that station, and hence have to use selective circuits in order to hear any other transmissions. The set in question was used first of all at a friend's station further away from the local station, a direct-coupled aerial circuit being employed. Severe interference was experienced, however, as was expected.

and it was therefore decided to incorporate a loosely coupled aerial circuit in the present receiver, in order to help others who are in a similar position. At close range it is always difficult to eliminate the local station, in the fullest sense of the word, and as telephony occupies a wave-band on either side of the true wavelength, there will always be a difficulty in getting rid of one station and receiving another whose wavelength is only slightly different from that of the interfering station. In the present receiver, however, 2LO can be so reduced in strength as to be practically inaudible, while the other British stations, with the exception of Cardiff and Manchester, whose wavelengths are too close to that of 2LO, may be brought in without any unpleasant undercurrent of talk and so on from London.

It is realised, however, that a loosely coupled aerial circuit may prove awkward to use, at first, if the user has had no previous experience of such a method of coupling, and two terminals have therefore been included A₂ and E₂,

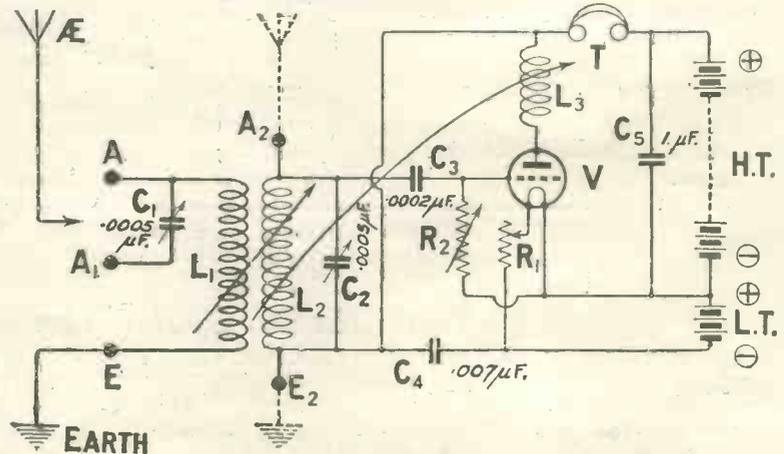


Fig. 1.—The circuit arrangement of the receiver.


A loosely coupled Receiver which employs a modification of the well-known Flewelling circuit.

by means of which the direct type of aerial coupling may be employed. The user is thus able to use the simpler coupling if he is not much troubled by interference, and it may prove useful when first operating the receiver. Some slight loss may be experienced when using the loose coupling, but this is compensated for by the added selectivity obtained. When skill has been attained, there will not be much to choose between the two forms of coupling, and to my mind the loose coupled aerial circuit wins every time.

Some readers may feel a little dubious about attempting this receiver, on account of the circuit having been dubbed a "super," but let me at once dispel any fears on this account. This set is no more difficult to handle than a "straight" single valve circuit, and, as far as I have been able to ascertain, causes no interference by oscillation to other listeners, provided that the coil L_3 is kept at a reasonable distance from L_1 , the secondary circuit inductance.

Grid Leak

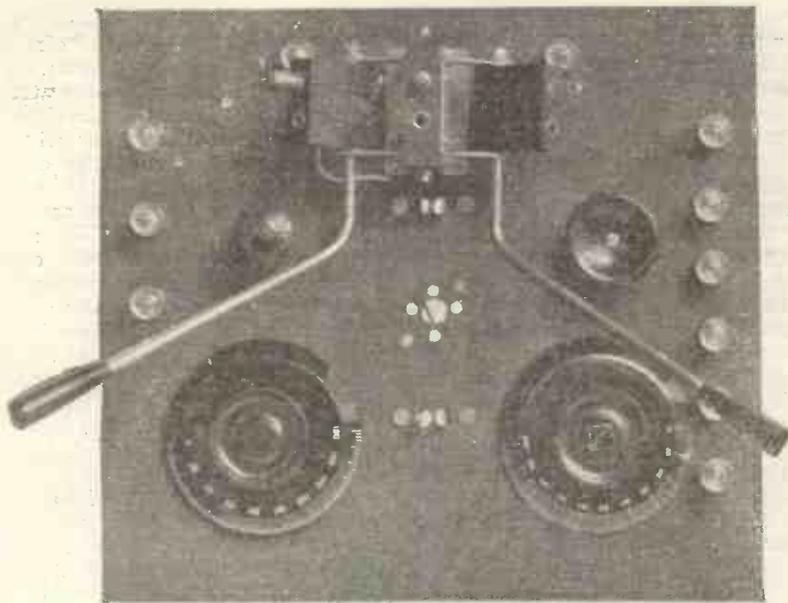A variable grid leak seems absolutely essential in this receiver, and I have therefore included one which is very satisfactory and quiet in action. The condenser C_4 is not at all critical, any value from



A plan photograph of the panel. Note that Myers or four-pin valves may be used.

around .005 up to .01 being quite suitable.

A Point regarding Valves

I am a great believer in low-capacity valves, and like to use them in all possible cases, so this receiver is provided with clips for Myers valves, as it is intended for use with this type of valve. There is also included a low-capacity mounting for an ordinary four-pin valve in order that either type may be used at will. Should readers desire, they may omit the holder for the type of valve they do not intend to employ. The double socket arrangement is very useful, however, as it permits four-pin valves to be compared with the low-capacity type. For those who so desire, clips for the V_{24} or QX valve may be substituted for the Myers clips.

Components required

For the benefit of those who like to know just what parts are used

in a set, the names of the manufacturers are given, but it must be understood that there is no obligation for the parts used to be of the make specified, it merely being necessary to be sure that good quality material is employed. As regards values, those given should be adhered to, as I have tried different capacities and so on, and have decided upon those marked. As I said previously, C_4 is not critical, and constructors may use just what capacity condensers they may have at hand.

- 1 ebonite panel, 10 in. by 9 in. by $\frac{1}{4}$ in. (Paragon).
 - 1 3-way coil holder (Magnum, Burne Jones and Co.).
 - 1 .0005 μF square law condenser (Bowyer-Lowe).
 - 1 .0005 μF square law condenser (Jackson Bros.).
 - 1 .0002 μF fixed condenser (Dubilier).
 - 1 .007 μF fixed condenser (McMichael).
 - 1 set of clips for Myers valves.
 - 1 valve holder (H.T.C. Type C).
 - 1 1 μF condenser (T.C.C.).
 - 1 filament resistance (Shipton).
 - 1 variable grid leak (Bretwood).
 - 11 nickel-plated terminals (Burne Jones and Co.).
- Square section wire for wiring up.

The Panel

This is made from the ebonite appearing at the head of the above list, and is to be drilled in accordance with the figure showing the layout. Constructors should always satisfy themselves that the

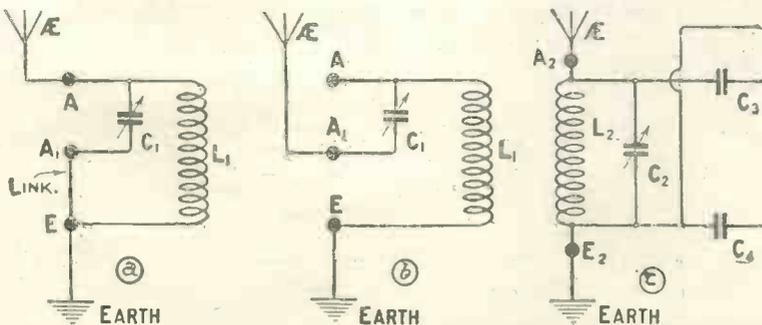


Fig. 2.—How the various aerial circuit arrangements are obtained.

ebonite they use is of good quality and free from surface leakage, the most satisfactory way being to buy only branded ebonite. Should unguaranteed material be used, however, the shiny surface should be removed by rubbing both sides with emery cloth after the holes have been drilled. The black appearance may be restored to the ebonite by means of a little oil on a piece of clean rag. Do not use too much, but make a little go a long way, and rub with a circular motion.

The holes for the terminals have all been tapped to the correct size (4 B.A.), but it is understood that some may not possess the necessary taps, in which case clearance holes may be drilled, and the terminals secured with nuts in the usual manner.

Wiring

The photographs of the underside of the panel will reveal the

simplicity of the wiring, and the actual connections can be clearly seen in the wiring diagram. It must be pointed out here that Radio Press, Ltd., have developed a new system of showing wiring on practical diagrams. The older method consisted of showing "loops" where two wires crossed but were not joined. The new method, which saves much confusion once the idea is fully grasped, is simply that wires run from point to point, as in the actual receiver, joins being shown by a black square. Thus, if two wires cross but do not join, there is no loop, but there is no black square, so it will be perfectly clear which wires join and which do not.

While on the subject of wiring, I should like to draw readers' attention to the terminals I have used. The bottom of the shank is drilled out, to take the end of a piece of square section wire of the size usually referred to as No. 16,

and thus the task of soldering a piece of this wire to a terminal shank, in the "end-on" fashion, is considerably simplified, all that is necessary being to insert the wire, touch with flux, and apply the iron in the usual manner.

Naturally, if the constructor desires he may use No. 16 tinned copper wire of round section, many people, in fact, preferring this to the square wire. In any case, follow the usual practice of spacing the wires as much as possible.

Valves

Almost any good general purpose valve will work well in this receiver, provided the makers' instructions regarding anode voltage and filament current are adhered to. I have incorporated a bright emitter rheostat in my receiver, but if dull emitter valves are to be used, a suitable type of rheostat should replace that used.


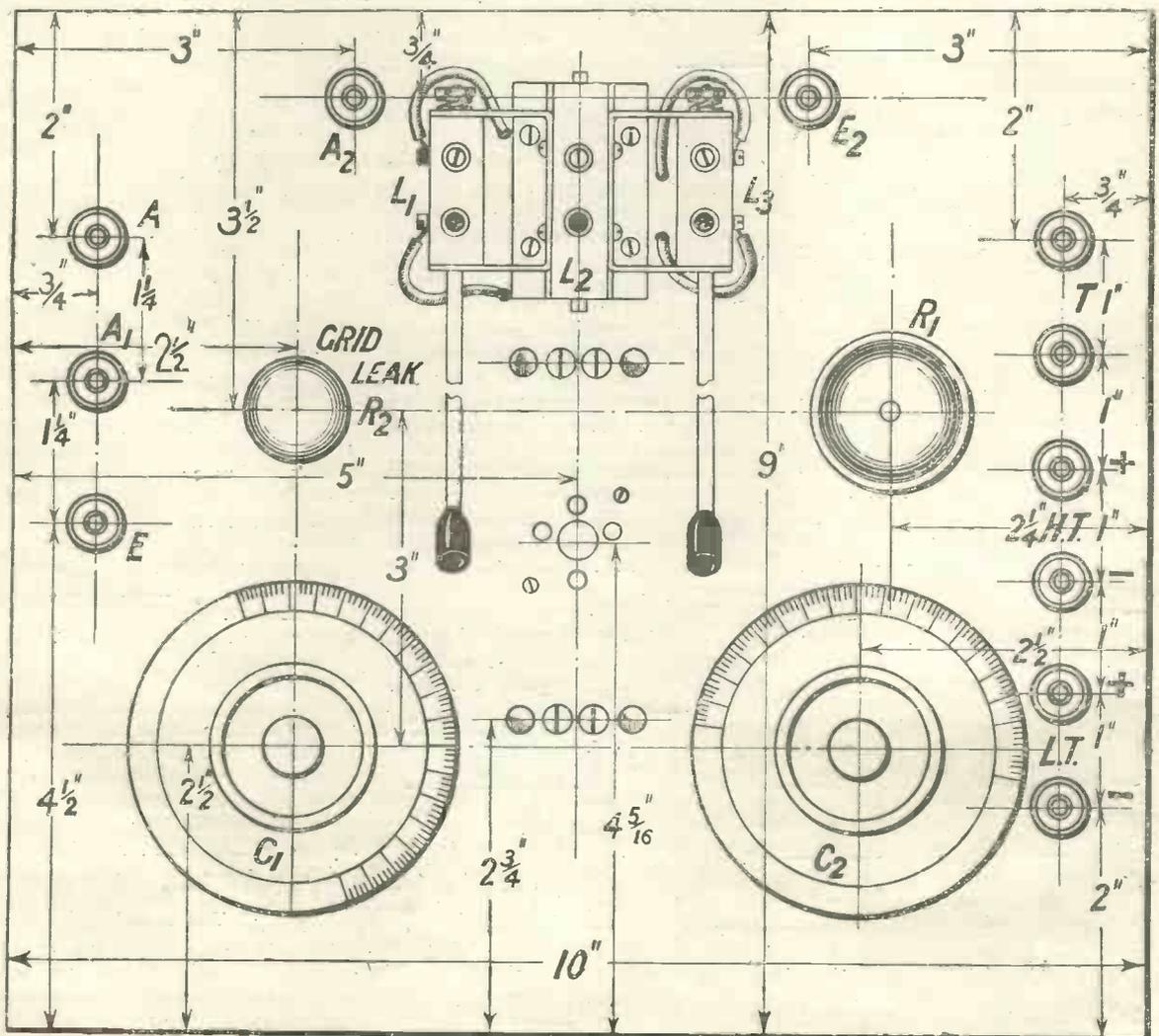


Fig. 3.—The panel layout. Blue Print No. 80A.

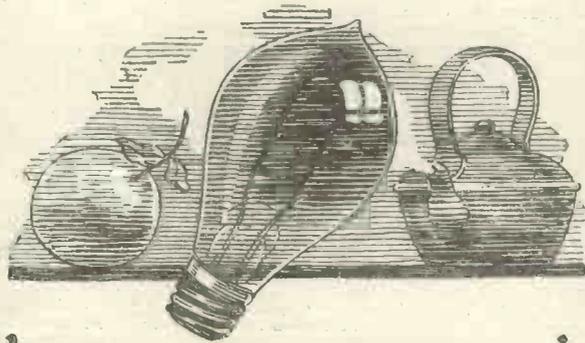

What one man saw in a blackened bulb

THE history of progress is tied up with trivialities. Newton made history under an apple tree; Watts saw it in a tea kettle. Modern "wireless" came from a blackened bulb. It was an ordinary carbon filament lamp. Everybody knew that it turned black as it grew older. One man wondered why—and made it his business to find out. What he found was the principle of the thermionic valve. Dr. Fleming was the man

and his experimental valve was made in the Ediswan Laboratories.

That was 30 years ago. Since then many developments have taken place in the evolution of the valve. Ediswan Valves retain the lead they won in the early days of wireless. They are wholly reliable — experienced workers and careful testing see to that.

Ediswan Valves will bring the best out of your wireless set—get some on the way home and enjoy a better programme from to-night onwards. All dealers sell them.

THE EDISON SWAN ELECTRIC CO. LTD
QUEEN VICTORIA ST., LONDON, E.C. 4

An interesting study of early wireless history may be made at the Science Museum, South Kensington, London, where the complete series of Dr. Fleming's experimental valves can be seen.

EDISWAN VALVES

162-12

A new departure
in Wireless Components for
the home constructor.

Whether you are a beginner or a more advanced worker, it will pay you to study the unique and original features embodied in



WIRELESS COMPONENTS.

If you have never built a set before—or if you contemplate building a new set—the name "EFESCA" on the components will ensure success. One hole fixing is a standard "EFESCA" refinement.

For the wireless enthusiast who perhaps has neither the skill nor tools, complete home-constructor sets are available. These are extremely simple to put together and will be found particularly efficient in their working. All "EFESCA" parts and "EFESCAPHONE" sets are stocked by wireless dealers, ironmongers and electricians.

Everyone interested in wireless should send a postcard for the "EFESCA" Catalogue—No. 522—which contains the full range of "EFESCA" Components and "EFESCAPHONE" Receiving Sets.

The Components Illustrated are:—

- (1) EFESCA AERIAL TUNER.—Wavelength range 150-2,600 metres in conjunction with .001 condenser. A convenient form of self-contained tapped coil, possessing minimum self-capacity, low resistance and high inductance. Tappings arranged to obviate dead end effects. Complete, as illustration, 19/—.
- (2) EFESCA ANTI-CAPACITY SWITCH (Patent applied for).—A double pole, double throw switch, specially designed to minimise the capacity which exists in most change-over switches. The contact brushes are of phosphor bronze and present only their edges to each other with a comparatively wide air gap—thus practically eliminating all capacity effects. The operating lever is at no time in electrical contact with the carrying block which makes contact with the brushes. Price 8/- each.
- (3) EFESCA VARIABLE REACTION COIL.—For use in either Aerial or Anode Circuits. Wound on ebonite former, totally enclosed, complete as illustration, 17/6.
- (4) EFESCA TAPPED HIGH-FREQUENCY REACTANCE, for one-stage of high-frequency amplification. It is self-tuned and requires no condenser. Wavelength range, 150-2,600 metres. Complete, as illustration, 21/- each, or embodying grid-leak and condenser (.0003 mfd.), 25/- each.
- (5) EFESCA VERNISTAT (Patent applied for).—Of unique construction the Vernistat gives extremely delicate control and is smooth and silent in operation and is specially suited to high-frequency and Detector Valve filament control. Resistance 5 ohms, 6/- each, complete, as illustrated.
- EFESCA HIGH-FREQUENCY TRANSFORMER.—Specially recommended where more than one stage of high-frequency amplification is required. Can be employed immediately preceding a reactance coupling to form two high-frequency stages or any number of separate transformers may be used in combination. Can also be used as a Tuned Anode Transformer by shunting the primary with a .0003 mfd. variable Condenser in any number of stages. Wavelength range, 150-2,600 metres, complete as illustration, wound on ebonite former, 21/- . Ditto, employing Grid Leak and (.003) Condenser, for use as Transformer connected to Detector Valve, 23/-.


Here are two new lines of great interest.

The "PURAVOX" LOUD SPEAKER. The principle employed enables speech and music to be reproduced with quite exceptional purity and maximum volume: The "PURAVOX" Standard Table Model is a full size Speaker at a medium price. The "PURAVOX" Junior is suitable for smaller rooms. 2,000 ohms resistance, £4 10 0 each. This model £2 10 0 each. The EFESCA GIANT H.T. BATTERY. These Batteries employ extra large cells which give longer life and greater freedom from breakdown than the usual standard type of battery. A unique feature is the 1 mfd. condenser embodied in these batteries which smooths out all crackling noises frequently associated with H.T. Batteries. Sixty volt with Tappings and sockets in 6 volt steps from 30 Volts and 1 pair of wander plugs, 23/-

FALK STADELMANN & Co. Ltd.,
Efesca Electrical Works, 83-7, Farringdon Rd.
London, E.C.1.

And at
Glasgow,


Manchester and
Birmingham

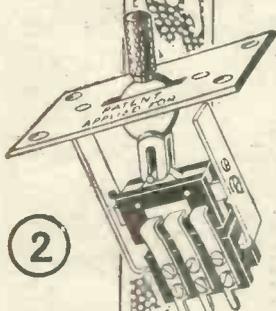

Operating Details

To use loose coupling, the aerial is connected to terminal A for parallel aerial tuning condenser, the earth being joined to E, while A_1 and E are linked together. For series condenser the aerial is joined to A_1 , earth to E, terminal A being left free. In both these cases the terminals A_2 and E_2 , at the back of the receiver, are left free, as they relate only to the direct-coupled circuit. When it is desired, for reasons of simplicity, say, to use the direct-coupled circuit, the aerial and earth leads are joined to A_2 and E_2 respectively, the terminals A, A_1 and E being left free.

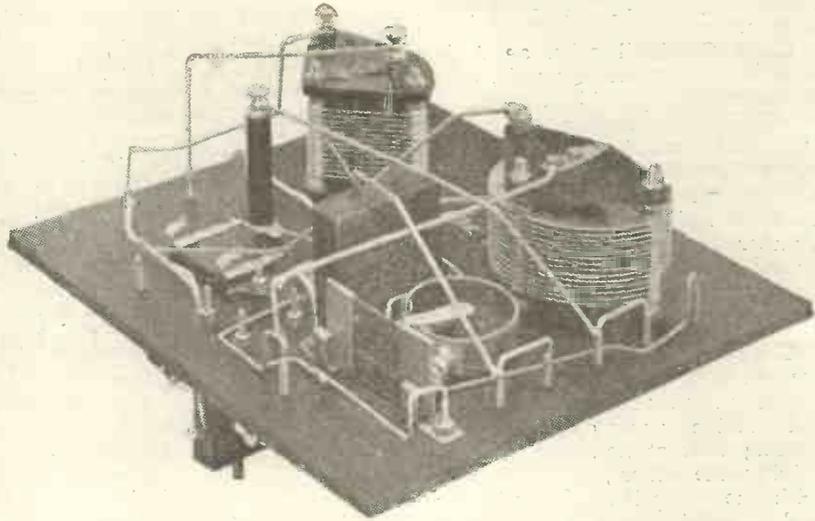Tuning is carried out by simultaneous variation of the tuning condensers, the coil L_3 being kept fairly well away from L_2 . The aerial coil L_1 , for the most selective reception, should not be kept too close to the secondary coil L_2 .



A view of the underside of the panel, showing how the wiring is carried out.

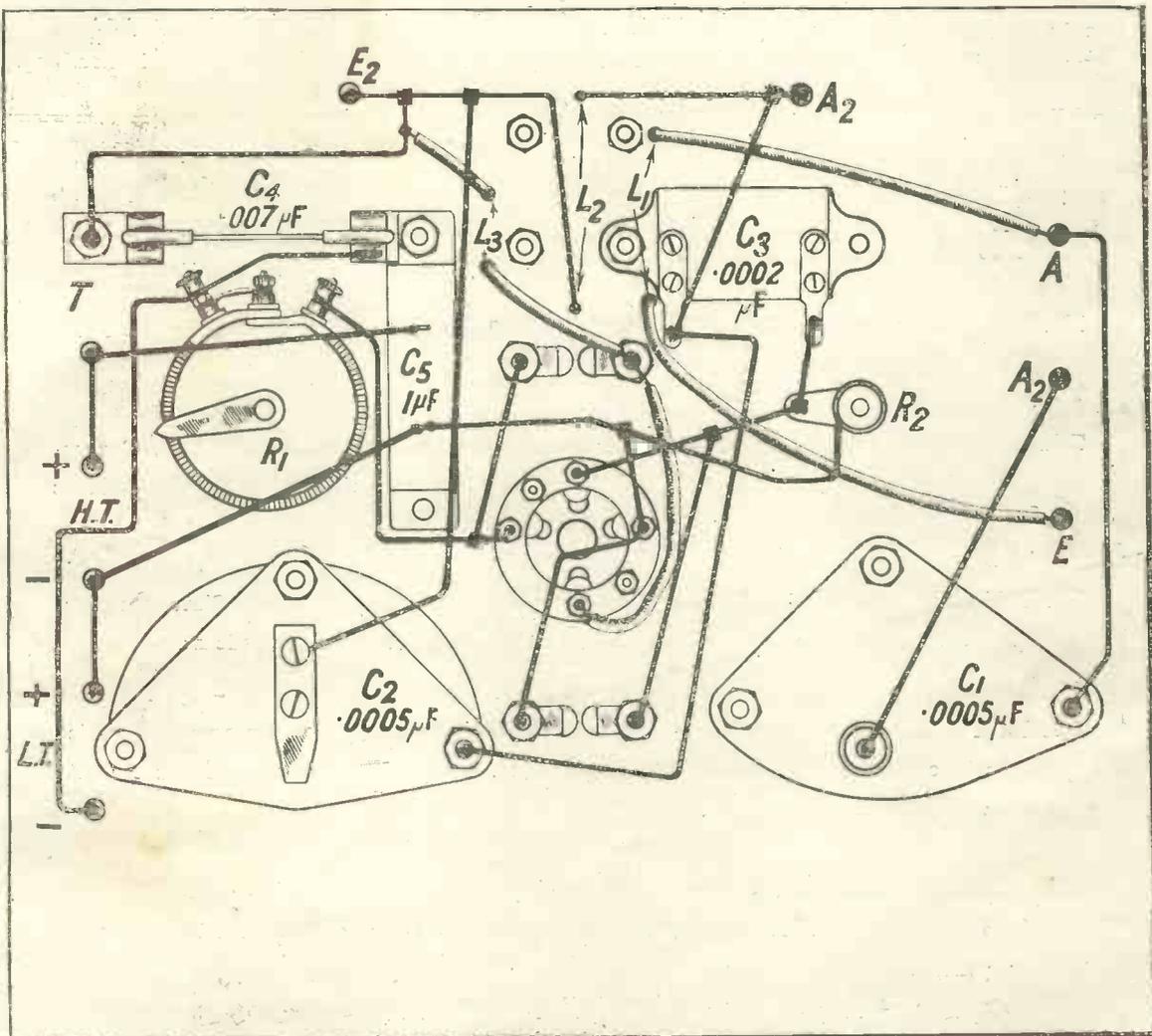



Fig. 4.—The wiring diagram. Note that where two wires join a black square is placed, no loop being shown where there is no join. Blue Print No. 80B.

there being a best position for each station.

Using Gambrell coils, an A is required in the aerial circuit, a B in the secondary, while another A is suitable for reaction. The size of this last-named coil may vary in different cases, especially when the direct-coupled circuit is used, owing to aerial resistance. In the usual numbered ranges of coils, a No. 50, 75 and 50 will be suitable for L_1 , L_2 and L_3 respectively.

Test Report

The set as described was given a test on my aerial in S.E. London, about six miles from 2LO. Very little difficulty was experienced in cutting that station out and receiving the others, all of which, with the exception of Manchester and Cardiff, were received at good 'phone strength. Radio-Paris and 5XX came in well, using Nos. 150, 200 and 100 in the respective positions, aerial, secondary, reaction. L'Ecole Supérieure was also heard at good strength, while Madrid was audible at about

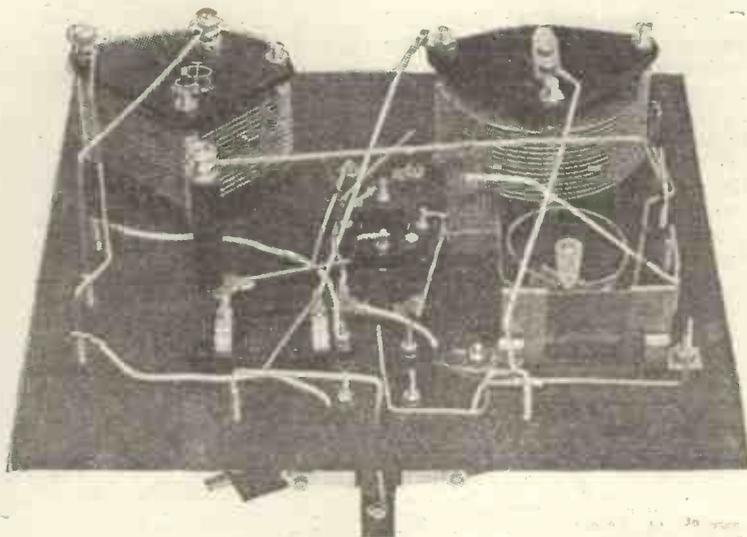

Another view of the wiring.

two feet from the 'phones. Several low-power amateur stations at long distance were received well.

Given a reasonably good aerial,

this receiver will provide much interesting work, and will give excellent results with a little patience and care in handling.

THE CHRISTMAS PROGRAMME FROM 2LO

MONDAY, 22nd December, 1924.—The opera, "Hansel and Gretel," conducted by Mr. Percy Pitt, will be simultaneously broadcast to all stations.

TUESDAY, 23rd December, 1924.—In order to give the London staff a short rest, Bournemouth, Cardiff, Birmingham and Manchester stations will each give simultaneous broadcast turns of half-an-hour to the London area.

WEDNESDAY, 24th December, 1924.—John Coates (tenor) will give a recital of Christmas songs from 8.40 to 9.20 p.m. At midnight carols and waits will be broadcast.


THURSDAY, 25th December, 1924.—Each station will broadcast its own programme, which will consist of light seasonable items, dance music, etc. Only one News Bulletin will be issued—at 10 p.m.

SATURDAY, 27th December, 1924.—For the benefit of children a modified version of "Hansel and Gretel" will be broadcast. The "Roosters" Concert Party will broadcast the pantomime "Cinderella."

The Savoy Bands will play each evening until about midnight.

Charge your own ACCUMULATORS at home—FREE

Cut out the continual weekly expense of having your accumulators re-charged. Eliminate the annoyance of being left with accumulators run down just when you want them most, and the trouble of carrying them to the nearest garage for re-charging. Do away with all this NOW by charging your own accumulators at home, and absolutely without cost. If you have a Direct Current supply of electricity of any voltage in your house either for lighting or heating purposes, all you need to charge your own accumulators at home is the

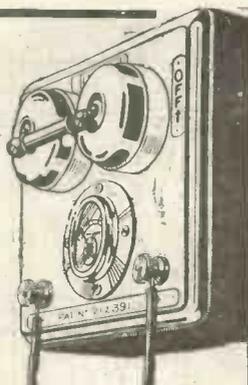

FOR DIRECT CURRENT ONLY

ULINKIN

PATENT No. 212391.

THE D.C. HOME CHARGER

which charges your batteries automatically whenever you have lights, radiators, electric irons or vacuum cleaners in use in any part of your house, without consuming any extra current, and therefore free of cost.

PRICE **£2:2:0** CARR. FREE.

Complete with simple instructions.

Send 42/- for a ULINKIN To-day, or writz for illustrated booklet and fuller particulars.

Trade Enquiries Invitel.

The Gran - Goldman Service
(Dept. M. 22), 71, Fleet Street, London, E.C.4

An Electrical Engineer says:

"Please forward another of your 'Ulinkin' Chargers. The last one I installed gives every satisfaction. It has practically paid for itself already. A splendid little instrument."

AUTOMATIC IN ACTION.
Requires no attention.
Cannot go wrong.


McCLELLAND Variometer

One of the Best

Please order from your local Wireless Dealer.

A WELL-MADE and most efficient instrument. Wound on ebonite and covering a wave-length range of 240-740 metres. Close coupling of rotor and stator windings ensures maximum results and exceptionally fine tuning.

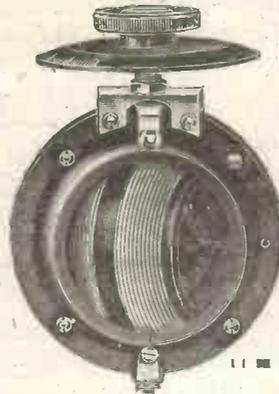List No. RV61/15, with knob and dial, each, 14/-



BROWN BROTHERS, LTD.

ALLIED COMPANIES:

Thomson & Brown Brothers Ltd., Brown Brothers (Ireland), Ltd., Great Eastern Street, London, E.C.2, 118, George Street, Edinburgh, and Branches.

Dance to Real Music at Home



LOUD SPEAKER

enables you to spend a delightful evening in this way, thanks to the excellent dance programmes now being broadcasted. An efficient set, plus a C.A.V. LOUD SPEAKER, gives all the advantages of a first-class orchestra at an infinitesimal cost.

120 ohms, £4 15s. 2,000 ohms, £5. 4,000 ohms, £5 10s.
C.A.V. Junior £2 15s. C.A.V. Tom Tit 30s.

Write now for Illustrated Loud Speaker Folder from

Telephone: Chiswick 2000



C.A. Vandervell & Co., Ltd.
ACTON VALE, LONDON, W. 3.

Telegrams: "Vandervell," Phonos.



In replying to Advertisers, please use Order Form enclosed.

IGRANIC
Low Frequency
Transformer

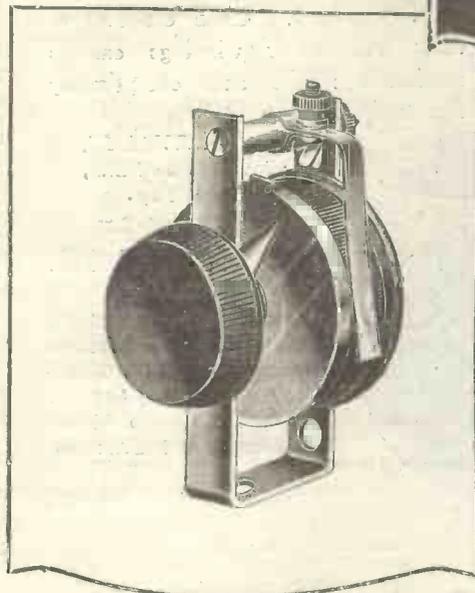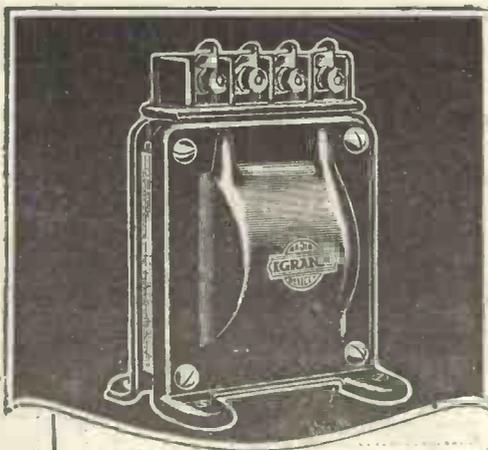

IGRANIC
Filament Rheostat
(30 ohms)

**Two strong
links in a radio set**

That old saying "a chain is as strong as its weakest link" affords an apt simile applied to wireless. For an inferior component, though serving a purpose in a radio set, weakens your circuit and cannot produce the first-class results you expect and assuredly get from quality components such as bear the name IGRANIC.

The two Igranic Devices illustrated are but two strong links with which you should build your set. For when *all* Igranic parts are used in correct circuit, then are you assured that perfect team-work which results in perfect reception.

Igranic components are obtainable of all Reputable Dealers.

Write for List Z 335.

IGRANIC
RADIO COMPONENTS

include

- Variometers
- Vario-Couplers
- Honeycomb Coils
- Bi-plug Coil Holders
- Tri-plug Coil Holders
- Filament Rheostats
- Battery Potentiometers
- Intervale Transformers
- Vernier Friction Pencils, etc.



149, Queen Victoria Street, London.

Works: Elstow Rd., BEDFORD.

GLASGOW: 50, Wellington Street.


MANCHESTER: 30, Cross Street.

BIRMINGHAM: 73/4, Exchange Buildings.

BRADFORD: 18, Woodview Tce., Manningham.

NEWCASTLE: 90, Pilgrim Street.

CARDIFF: Western Mail Chambers.

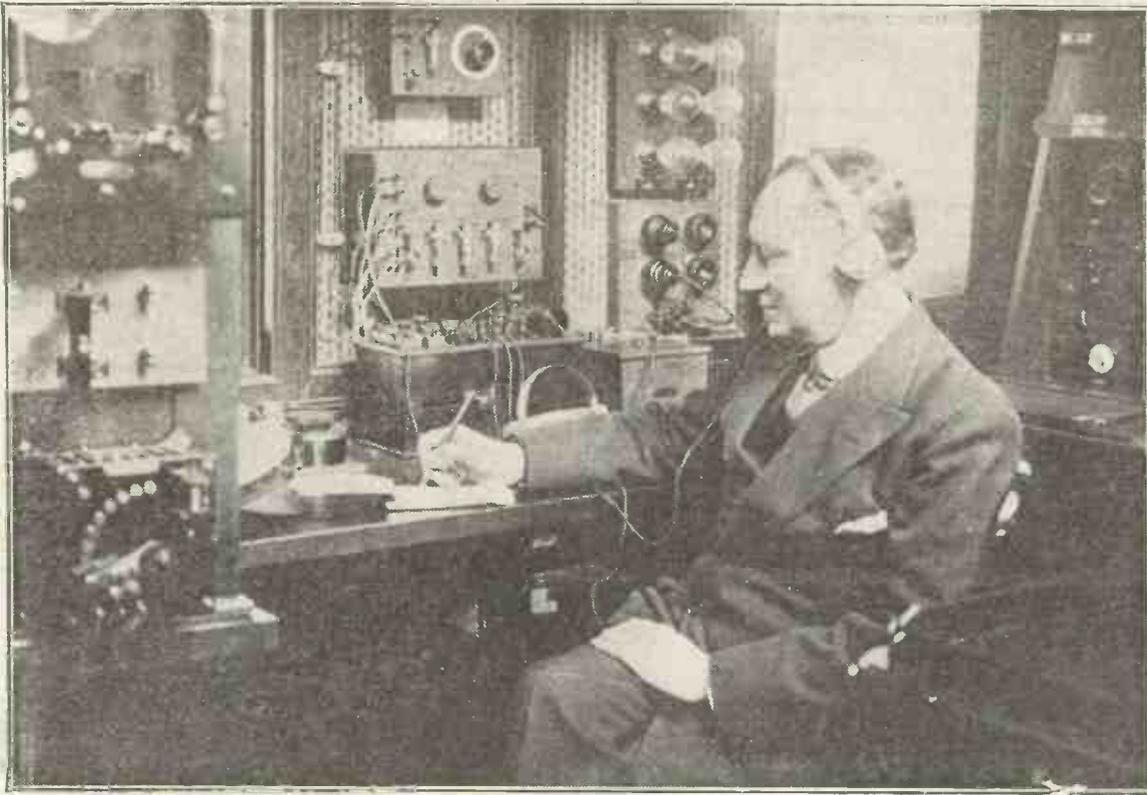

Senatore G. Marconi on his yacht "Elettra."

Marconi's Wireless Beam

By Lt.-Col. Chetwode Crawley, M.I.E.E.,

Deputy-Inspector of Wireless Telegraphy, G.P.O.


WE all know now that wireless communication over long distances does not necessarily entail the use of high-power and long waves; but it was only four years ago that Mr. Alexanderson, one of the world's foremost wireless engineers, stated in a paper read before the American Institute of Radio Engineers that "in radio communication it has been observed that the distance over which reliable communication can be maintained is about 500 times the length of the ether wave used."

Shorter wavelength and greater distance

Now, Marconi, using only 25 kilowatts and a wavelength of about 90 metres, has established reliable communication, at any rate during darkness, not only over about 45,000 metres (about 28 miles), but over 2,800 miles.

The range given by Alexanderson must have seemed to many, even four years ago, to be absurdly small.

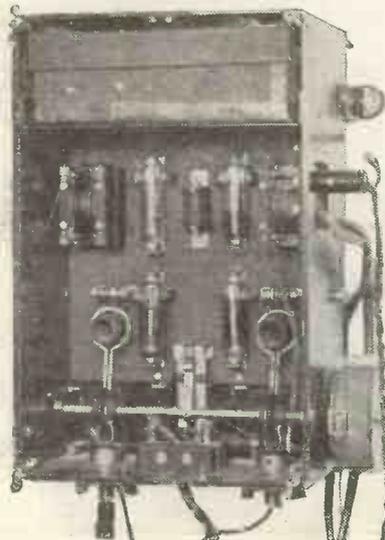From his statement an ordinary ship's installation could not then be expected to give "reliable com-



The ship type of Marconi Beam Receiver.

munication" over more than about 200 miles, whereas such installations were commonly used for communicating over far greater distances by day, and sometimes even up to ten times that distance by night.

Now Alexanderson, of course, knew all about these ranges, but was careful in his statement to use the expression "reliable communication," and it is just this expression which has always been so troublesome to the wireless enthusiast.

The first long-range work


The first long-range wireless telegraph service was that established by Marconi in 1902 between stations in England and Newfoundland, which were installed with quite small power, in fact about the same power as that proposed for the new "beam" stations for our imperial communications. But this Transatlantic working twenty-two years ago could not by any legitimate stretch of imagination be called

reliable. It was very slow and only possible at all under good atmospheric conditions; in fact, it was distinctly unreliable, but it was the brilliant opening of a completely new system of world communication.

Reliability

Up till now nearly all improvements at the transmitting stations have involved the use of more and more electrical power; in fact, the 30 horse-power first used for Transatlantic communication has now been increased tenfold, and this although the sensitivity of the receiving instruments has been enormously improved. The cry has always been, "Give us more powerful transmitting stations and then we shall show you what we can do"; and at the present moment the Government are erecting at Rugby one of the most powerful wireless stations in the world.

This steady increase of power has produced a very marked improvement in the efficiency of communication, so that now Transatlantic working is reasonably reliable and the speed of signalling has been increased about tenfold, which makes the service comparable with that given by cables. At the moment, however, there are only two stations in this country, and, for the matter of that, in the Empire, capable of providing a satisfactory long-range service—the Post Office station near Oxford and the Marconi Company's station at Carnarvon. The Oxford station carries out services with Canada,

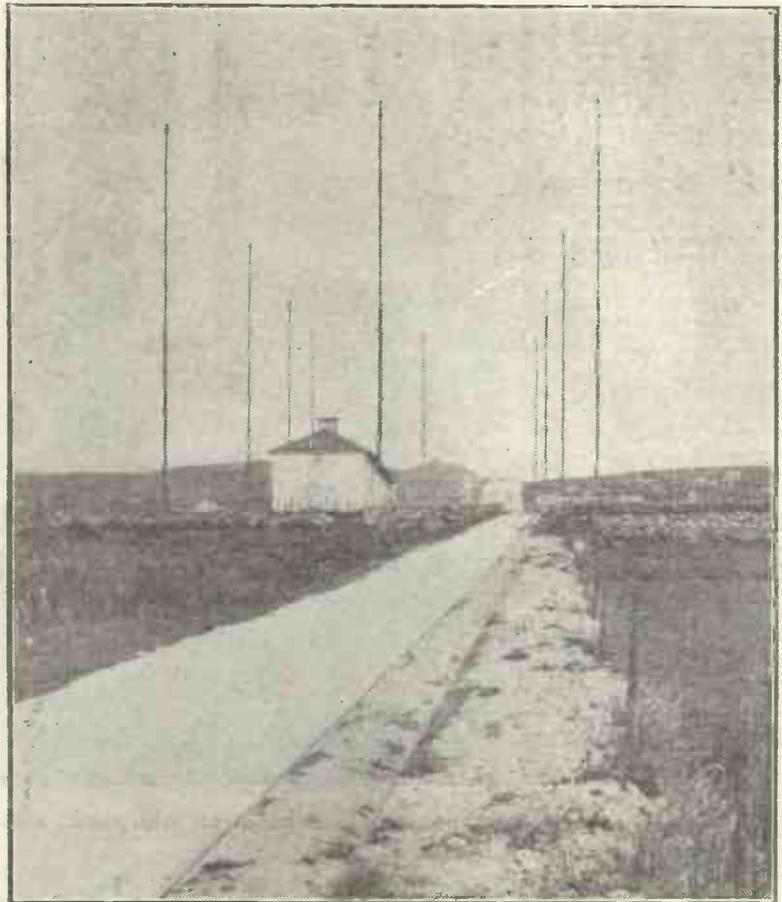


The Marconi Carnarvon Station represents a modern long wave high-power station.

Egypt, and with ships; and the Carnarvon station works with America.

Facilities in Other Countries

This state of affairs compares most unfavourably with the facilities for long-range wireless communication in the United States of America and in France. The United States have thirteen large stations, and France has five, apart from stations in their possessions overseas. Five of the United States stations are worked by private enterprise and conduct services with England, France, Germany, Norway and Japan, the eight other stations being worked by the Government for State purposes. Two of the French stations are worked by private enterprise and conduct services with the United States of America, Argentine, and Syria, the three others are worked by the Government for State purposes and commercial services to French possessions abroad.

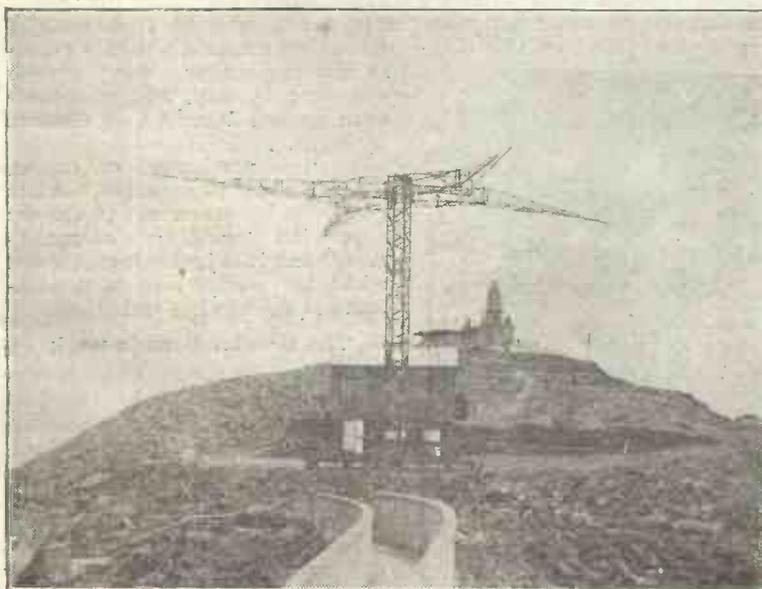In Italy there are two large stations which communicate with her Colonies and with the United States, and in Germany there are three, which are used principally for communication with the United States.



The Parabolio Rotating Beam Transmitter at Inchkeith Island.

A DELIGHT TO USE

SUCCESS Vernier Coil Holder

The absolute and definite control which the SUCCESS Vernier Coil Holder gives over coil coupling demonstrates the increased efficiency gained when accurately tuned coils are accurately adjusted for any given wave-length. It requires not more than five minutes of operation to discover that this accuracy—so easily obtained—is a delightful enthusiasm for which the SUCCESS Vernier Coil Holder is responsible.

It cannot be demonstrated quite so emphatically that good components do give better reception than when you have carried out one or two experiments with the SUCCESS Vernier Coil Holder. The ability to tune up to the razor-sharp point requires a balance of coupling and capacity.

Accuracy is sometimes obtained—by a fluke—but that fine point seems just beyond the persuasion of skilful tuning.

Incorporate the SUCCESS Coil Holder—its rigidity, combined with a quick and micrometer action, will persuade the very utmost from your aerial tuning system:

Price 5/6 (For Panel Mounting).

As used in the T.A.T. Receiver described by Mr. JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E., in the current issue.



Experimenters working on the very short-wave Transatlantic transmissions are recommended to use the SUCCESS Vernier Coil Holder. Its design—simplicity in itself—reduces capacity effects to the irreducible minimum: a very desirable feature for the critical short wave receivers.



Successful reception of the short waves requires the simplest of arrangements—detector and one note magnifier—which involves one very important component—the low frequency transformer. Choice of this instrument cannot be too deliberate. It need not be emphasised how, in so critical a receiver as one designed for the reception of KDKA on 68 metres, an ill-designed L.F. Transformer can mar your reception beyond skilful tuning. Tested under every conceivable condition, the SUPER-SUCCESS unconditionally gives you power amplification, and represents a new experience with which you should not delay your acquaintance.

PRICE 21/-

OTHER SUCCESS RADIO COMPONENTS

SUCCESS TUNER

Covers all Broadcasting and Continental Stations with one initial expense. A very useful component for crystal users.

Price 21/-

SUCCESS ANODE CAPACITY REACTANCE

A highly successful method of High Frequency Amplification combined with a vernier control of reaction.

Price 50/-

SUCCESS ERTHAREL LEAD-IN SWITCH

Safeguards life and property from damage by lightning. The switching arrangements operate outside: control inside the house.

Price 6/6



COMPONENTS


Obtainable from all dealers.

WHOLESALE DISTRIBUTORS.

London: Beard & Fitch, Ltd., 34, Aylesbury Street, E.C.
Cable & Electrical Supplies Co., 234, Pentonville Road, N.
Manchester: Beard & Fitch, Ltd., 1, Dean Street, Piccadilly.
Birmingham: Cooke & Whitfield Wireless, Ltd., 24, St. Paul's Square.
Bristol: Fred. Burris & Sons, 7/15, Redcliffe Street.
Wholesale Fittings Co., Ltd., 14, North Street, Stokes Cross.

WHOLESALE SELLING AGENTS.

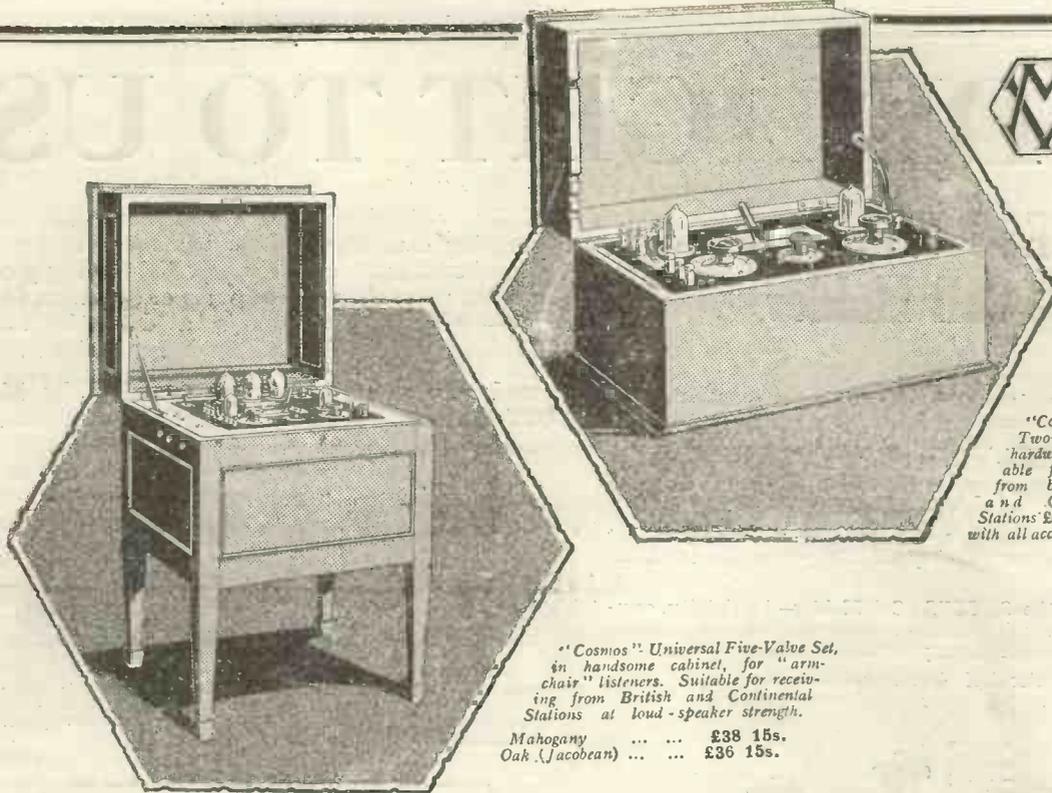Conradi & Braun, 52, Theobalds Road, London, W.C.1.
Full list of wholesale distributors appears in the Manufacturers Directory, November "Broadcaster and Wireless Retailer."



"Cosmos" Universal Two-Valve Set in hardwood case, suitable for receiving from both British and Continental Stations £17 10s., with all accessories.

"Cosmos" Universal Five-Valve Set, in handsome cabinet, for "arm-chair" listeners. Suitable for receiving from British and Continental Stations at loud-speaker strength.
 Mahogany £38 15s.
 Oak (Jacobean) £36 15s.

Experience counts—

SEND SIX PENNY STAMPS FOR A COPY OF THE "COSMOS" CATALOGUE AND HANDBOOK D.S. 7117/1.

A hundred pages of Radio matter, chiefly concerning "Cosmos" Sets, Parts and "Radiobrix."

TWENTY-FIVE years' experience in the production of Electrical Plant of every description, ranging from - large Generators to delicate Measuring Instruments, naturally finds some expression in the design, workmanship and efficiency of the


"COSMOS" UNIVERSAL RADIOPHONE.

Buy the set that embodies experience—it's as good as an extra valve. Obtainable from all Wireless Dealers.

"Cosmos" Radiophones Speak for Themselves.

METRO-VICK SUPPLIES, Ltd.

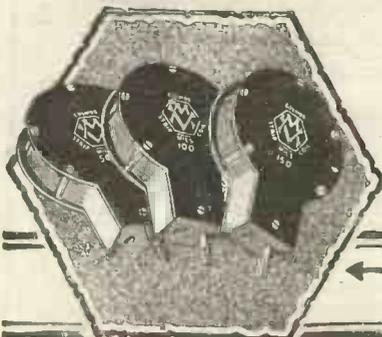(Proprietors: Metropolitan-Vickers Electrical Co., Ltd.),
 4, CENTRAL BUILDINGS, WESTMINSTER,
 LONDON, S.W.1.



← USE "COSMOS" STRIP COILS—Minimum Resistance—Low H.F. Resistance—Low Self-Capacity—Remarkably Efficient—Sound Construction.

R
 273

Such then is the position at the moment as regards facilities for long-range wireless communication with the principal countries in the world, and the need for increasing such facilities in the British Empire is obvious, and was recognised as long ago as 1913, when the Government signed an agreement with the Marconi Company for the erection of long-range stations throughout the Empire. This scheme was abandoned owing to the

ment for transmitting wireless signals on short wavelengths in the form of a beam, somewhat similar to the searchlight's beam of light waves, which of course consist also of ether waves but of far shorter wavelengths than those used for wireless signalling.

The Use of Short Waves

The lengths of the waves used by Marconi for signalling over long ranges were about 100 metres

early results, and diverted research into channels which have given us the long-wave high-power station of to-day. Nothing further in fact was done with short-wave beams until 1916, when Marconi again returned to his long-abandoned investigations in connection with certain war requirements.

Concentrating the Beam


In his present Beam system the reflector used at the transmitting and receiving stations consists of a number of wires placed parallel to the aerial and spaced around it on a parabolic curve of which the aerial forms the focal line, and in the Government agreement it is laid down that the power input should be at least 20 kilowatts, and that the emitted waves shall be concentrated within 30 degrees. The station for communication with Canada is to be able to communicate each way at a speed of 100 words a minute, exclusive of repetitions, during a daily average of 18 hours. Additional units are to be similarly guaranteed except that the periods of working with South Africa, India and Australia are to be respectively 11, 12 and 7 hours daily.

The speed of working contemplated is thus much greater than would be expected from high-power stations, as high-speed signalling is facilitated by the use of low-power and short waves. But the daily average periods of working are smaller than would be expected from high-power stations, as the intensity of signals on these short waves varies inversely in proportion to the mean altitude of the sun when above the horizon; in other words, very great distances are not obtained in daylight.

Beam Stations and High Power Stations

From these considerations it will be seen that beam stations working between fixed points may be able to exchange as many words in 24 hours as high-power stations, and as the capital cost of the beam station should be only about an eighth of the large station, and the running expenses also much less, it is obvious that this new system of communication has great possibilities.

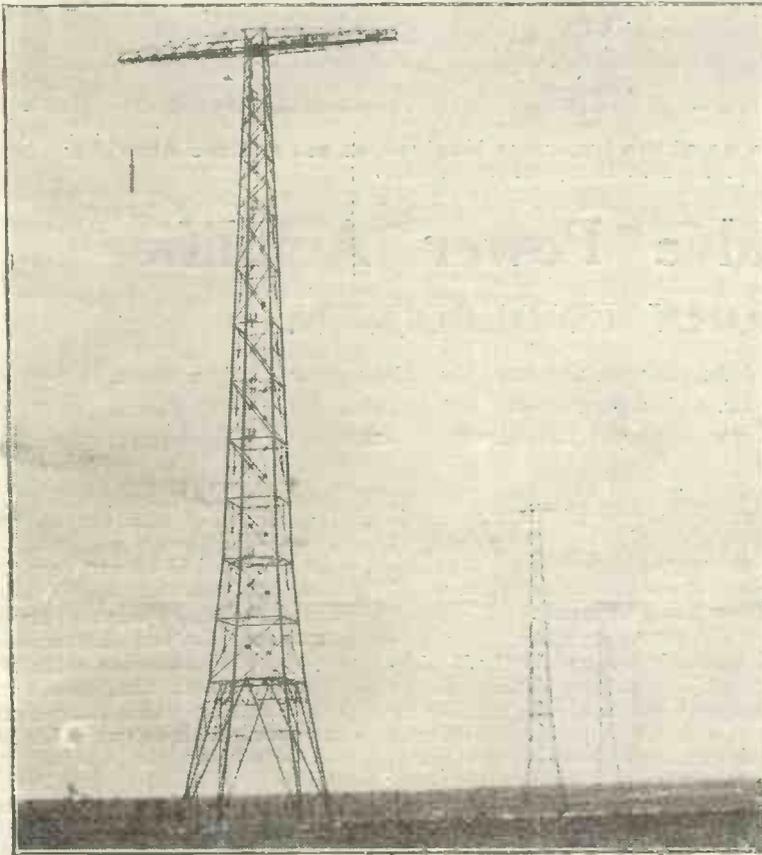On the other hand, the fact that the high-power stations can transmit to any part of the world at any time during the 24 hours is obviously a point of great importance, so much so indeed that the Government are, as already mentioned, erecting such a station at Rugby in addition to arranging for the erection of the Beam stations.



[Photo: Underwood & Underwood, N.Y.]

Will Beam wireless abolish tall towers like these of the Radio Corporation of America at Long Island?

war, and in 1920 a new scheme was adopted by the Government.


The Beam System

At this juncture Mr. Marconi made known the results which he had recently obtained with the Beam system, and in July last the Government entered into an agreement with the Marconi Company for the erection of a Beam station for communication with a corresponding station in Canada, with provision for its extension so as to provide similar communication with corresponding stations in South Africa, India and Australia.

The Beam system is an arrange-

whereas those used by the latest long-range stations are as great as 20,000 metres, and the power used by Marconi was about 20 kilowatts compared with 500 to 1,000 kilowatts used by some of the present large stations.

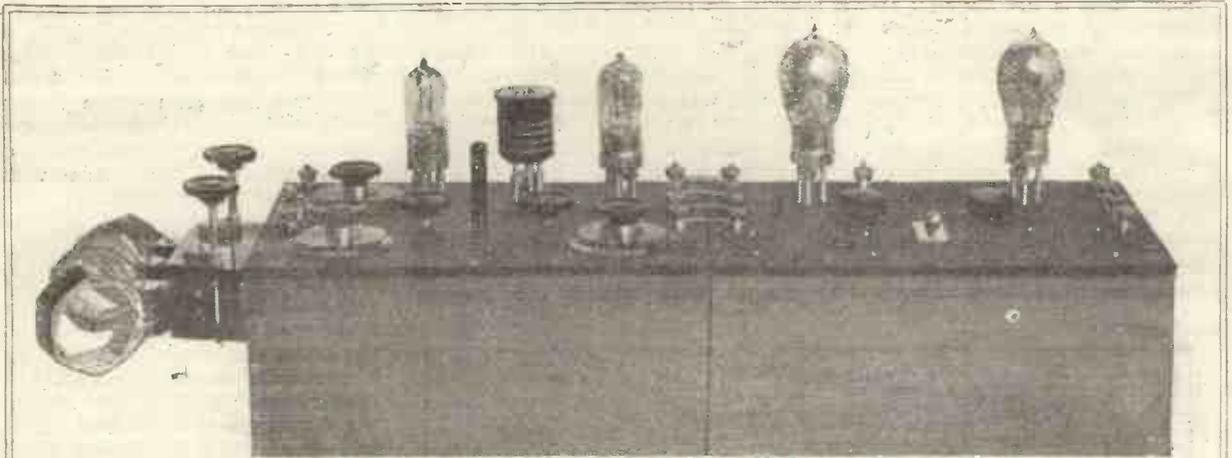Short wireless waves were used by Hertz in his classical experiments at the birth of wireless, nearly forty years ago, and about ten years later were used as a beam by Marconi at his first demonstrations in this country, after which the rapid and spectacular progress made with long-wave working completely overshadowed those



A complete receiver made up of the two-valve Neutrodyne set and the Amplifier described in the present article.

A Two-Valve Power Amplifier

By JOHN UNDERDOWN.

Although primarily designed for use with the two-valve Neutrodyne receiver shown above and described by Mr. Underdown in our last month's issue, this efficient two-valve unit may be used with many sets, both crystal and valve, where powerful loud-speaking is required.

IN last month's article on "A Double-circuit Neutrodyne Receiver," it was expressly stated that the set therein described was eminently suited for long-distance work rather than great volume on a nearby station. Listening on phones, although fascinating to the wireless enthusiast, is rather an unsociable affair, restricting movement and conversation amongst the rest of the family, and the two-valve unit about to be described is primarily designed so that ample loud-speaker strength may be readily obtained, allowing all to participate in the general enjoyment of the excellent programmes now transmitted from an ever-increasing number of stations.

Cross-Connections

The unit is of the same dimensions as the high frequency and detector set, and is so arranged that when standing side by side they are simply connected together by straight-through links eliminating many unnecessary and unsightly wires straggling about the table. Since it is particularly convenient to be able to obtain pleasant strength for the average room or great volume for dancing or large halls, a two-way switch has been provided. This, by throwing from one position to the other, permits the use of one or two

note-magnifying valves without any other alterations or attention whatsoever being necessary.

Applications

Although designed for the Double-circuit Neutrodyne, it must not be imagined that it is only suitable for use with this receiver. With any other set, crystal or valve, it works equally efficiently, and is particularly adaptable for the experimenter, as with the majority of circuits the low-frequency side is very much standardised.

Form of Coupling

The amplifier is transformer coupled

since this method of coupling gives the maximum step-up of signal voltage per valve of any system of low-frequency amplification, with no noticeable signs of distortion with well-designed modern transformers and valves working under their correct conditions. Although much has been written against the use of low-frequency iron-cored transformers, with the well-designed instruments now obtainable from a number of manufacturers the purity of reproduction obtained is easily comparable with that given by resistance coupling, added to which fact two transformer,

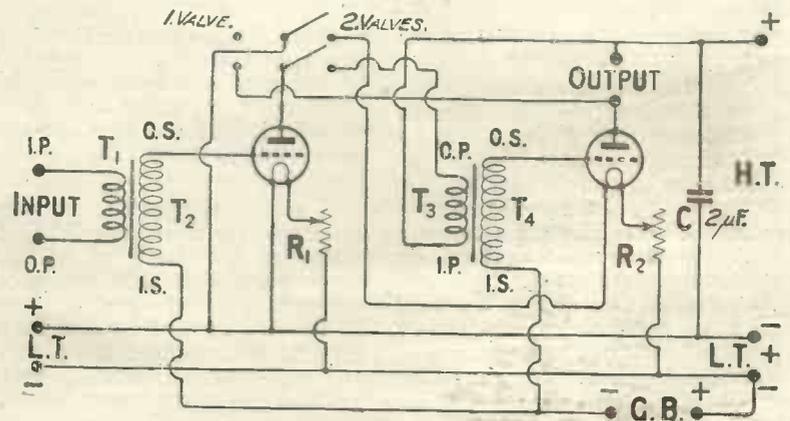


Fig. 1.—The theoretical circuit.

CURTIS CONSTANT - TUNED H.F. AMPLIFIER

The Curtis "Constant-Tuned" High-Frequency Amplifier is the only automatic high-frequency amplifier which, when connected in circuit, guarantees high efficiency for two stages of radio amplification on any wavelengths between 300 and 3,000 metres, and requires no additional controls, NOR MORE EFFORT, SKILL OR PATIENCE IN TUNING, THAN IS REQUIRED FOR THE OPERATION OF THE USUAL ORTHODOX SINGLE STAGE TUNED ANODE CIRCUIT.



THE CURTIS CONSTANT-TUNED HIGH-FREQUENCY AMPLIFIER CHANGES THE WHOLE CHARACTER AND QUALITY OF WIRELESS REPRODUCTION.

With its automatic simplicity, combined with increased selectivity and power, is destined to make two stages of high-frequency amplification a sine qua non of every Wireless Receiver for the Experimenter and Home Constructor, or the purchaser who prefers to buy a professionally constructed instrument.

For the greater convenience of the constructor, and so as to conform with existing panel design, the Curtis Constant-Tuned High-Frequency Amplifier is designed for use (and must be connected up in exactly the same way) as an ordinary High-Frequency Transformer.

Type A 300 to 800 Metres. Price 15/- Postage 6d.
Type B 800 to 3,000 Metres. Price 17/6

BUILD your own automatically tuned **LONG-DISTANCE RECEIVER.** Complete set of parts, including drilled and engraved Paragon Panel and Polished Mahogany Cabinet, with suitable circuit diagrams. From 54 15s. 0d.

Duodyne

A Genuine
Long-Distance
Receiver of
Exclusive Merit.

Two Stages of
High-Frequency
Amplification.

Automatic
Tuning.



In the Duodyne III the fullest advantage has been taken of the extraordinary virtues of the Curtis Constant-Tuned High-Frequency Amplifier. The first valve functions through the Curtis High-Frequency Amplifier, the second tuned anode, and the last as a rectifier. Guaranteed perfect reception at full power and of extraordinary purity from anywhere in the United Kingdom of any broadcasting station from Aberdeen to Madrid. Used in conjunction with the CURTIS EJECTOR will cut out local station at 1 1/2 miles (Relay Station 200 yards) and tune in ANY British Station at will. Price 310.

DUODYNE V combines the Duodyne III with a two-stage power Amplifier. Price 18 Guineas.

THE CURTIS EJECTOR

While designed for use with CURTIS RADIO INSTRUMENTS and DUODYNE MODELS, will also function with equal efficiency with any High-Frequency Receiver with sufficient reserve of receptive power to operate with a wave-trap. Price 35/-

CURTIS RADIO INSTRUMENTS

*EXCLUSIVE in DESIGN
and in the
QUALITY of REPRODUCTION*



The luxuriously silent functioning of the Curtis Models is the exclusive characteristic which places the Rolls-Royce car somewhat above ordinary comparison.

We would be happy to advise clients as to the model best suited to their requirements and to supervise the efficient erection of the complete installation in conjunction with their local agent.

Prices range from
£25 to 200 Gns.

Catalogue of Curtis Radio Instruments is free on application when particularly requested.



THE RADIONETTE


Two New Models.

PERFECT RECEPTION
AT
160 TO 200 MILES!

From the high-powered station. No extra Coils required. The many thousands of satisfied Radionette users are a solid guarantee of uniform RADIONETTE efficiency.

THE RADIONETTE DE LUXE in handsome French Polished lidded Oak Cabinet (200 to 1,850 metres). Price 21/-

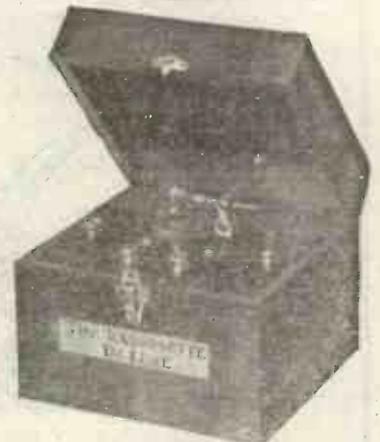THE RADIONETTE JUNIOR DE LUXE for local Broadcast. French Polished lidded Oak Cabinet. All-Ebonite Variometer tuning. Price 16/-



PARAGON CURTIS Products are always of uniform and dependable quality. Ask your local agent for full particulars and illustrated Catalogues.

PETER CURTIS, LTD.

75, CAMDEN ROAD, N.W.1.

Telegrams: "Paracurtex."

Phone: North 865.

BIRMINGHAM: 76, Newall Street. Central 7236.
MANCHESTER: 312, Deansgate. Central 5095.

In conjunction with

The PARAGON RUBBER MFG. CO., Ltd.

Signals unheard
with TEN other
headphones—
perfectly audible
with this super
head-set



Bechstein

"Headphones that Amplify"

This is a notable result of tests carried out on a one-valve reaction set with no amplification.

American Stations WGY and KDKA, also Canadian amateurs and most European Stations, have been consistently received with a singular absence of distortion.

Bechsteins are almost the equivalent of a valve amplifier when used in conjunction with a crystal set, the range of which is increased by roughly ten miles.

With a one-valve set, employing no

amplification, the range covers a vastly increased radius over which formerly no signals have been logged. Get what you are missing—and improve what you are getting in wireless, by insisting on the "Headphones that Amplify." Bechsteins are the last word in comfort, and every pair is guaranteed.

Further particulars are given in an illustrated folder on request. If your local dealer does not stock Bechstein, write direct giving his name and address to:—



5,000 OHMS

Folder on Request

25/-

Bechstein

RADIO COMPANY
4, CANAL ROAD, BRADFORD, YORKS.

WHOLESALE DISTRIBUTORS:—Liverpool: H. Kniveton, Norman Road, Runcorn, Chesh. London: Penton Engineering Co., 15, Cromer Street, King's Cross, W.C.1. Manchester: Accelero Co., 7, Liverpool Road. Leeds: Radio Productions Ltd., 107, Portland Crescent. Sheffield: Sheffield Wholesale Motor Supplies, 43, Carver Street. Glasgow: London Radio Stores, 11, Bath Street. Nottingham: Super Radio Co., 32, Parliament Street.

coupled valves give equal volume to that of three using the latter method.

The Circuit

No claim for originality is made for the circuit. It is merely the well-known one for the form of coupling adopted. A common high tension voltage is used on both valves, and also a common grid biasing voltage. This means that in most cases two similar valves will be required here, and the small type of power valve such as the B.T.H. B₄ or similar type valves by other makers are advised. First and second stage low-frequency transformers have been adopted, and in practice a high order of amplification is obtained without distortion. A double-pole double-throw switch permits of the use of one or two valves without it being necessary to make any external alteration to the amplifier connections. In the one-valve position the first valve only is used, the second being completely out of circuit. On throwing over to the second switch position the other valve is lit, and the loud-speaker transferred from the anode circuit of the first to that of the second valve.

Terminal Arrangements

Reference to the photographs and drilling diagram will show that there are four terminals at each side of the panel. Two pairs of these are common terminals, arranged thus for convenience in connecting to the companion receiver previously mentioned, so as to obviate duplicating battery connections. The two pairs to the rear of the sides of the panel are for the low-tension supply.

Of these the ones in the corners are common terminals to L.T. + and

H.T. —; whilst the other two are for L.T.—. This is all made perfectly clear by the diagrams.

On the left side of the panel the other pair of terminals is for the input from either a crystal or valve detector. The remaining two on the right hand side marked "Output" in the drilling diagram serve for the loud-speaker. At the back of the panel there are three terminals, the functions of which are, reading from

left to right, Grid Volts +, Grid Volts —, and H.T. +.

Panel Layout

The two sets of valve sockets are near the back of the panel, and are tapped into the panel, but receivers can use nuts and washers here without any detrimental effects. The filament rheostats are in front of the valve sockets, and are of the bright emitter type, although these can be easily changed for dull emitter or dual types if desired, as ample panel space has been left with this object in view.

To the front centre of the panel is situated the switch controlling the number of valves used. When the lever of this is pointing towards the valves both are in circuit; pointing away the last valve is extinguished and thrown out of circuit.

At the back of the panel the two low-frequency transformers are arranged one at either side of the switch and towards the front. That to the right is a first stage instrument, whilst the other is a special second stage transformer, so placed as to have its longitudinal axis at right angles to the former to minimise interaction effects if any.

Notes on Components required

In order to assist readers who wish to exactly duplicate the amplifier, the names of manufacturers are given together with the components used. Should changes be made only the best material is really advisable and

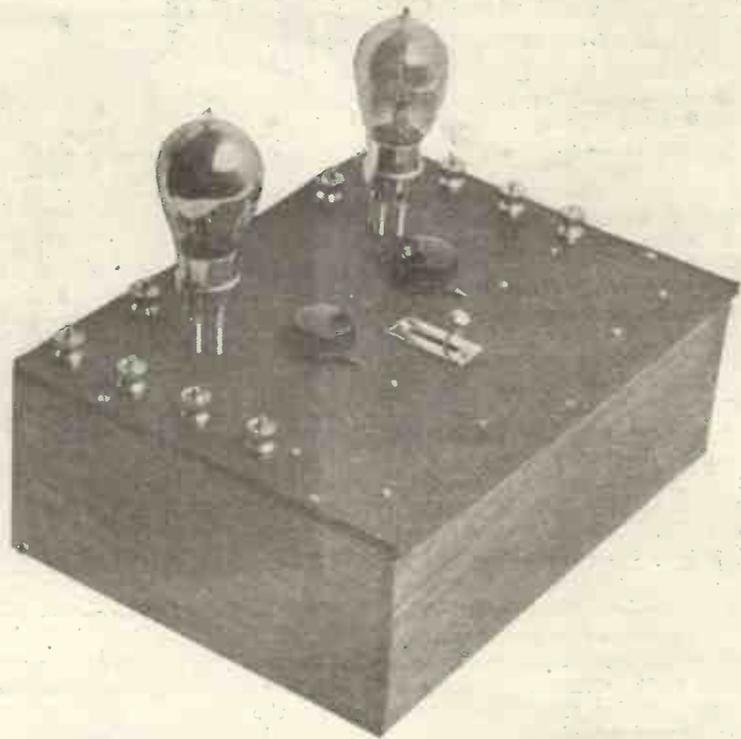


Fig 2.—With the switch in this position one valve only is in use.

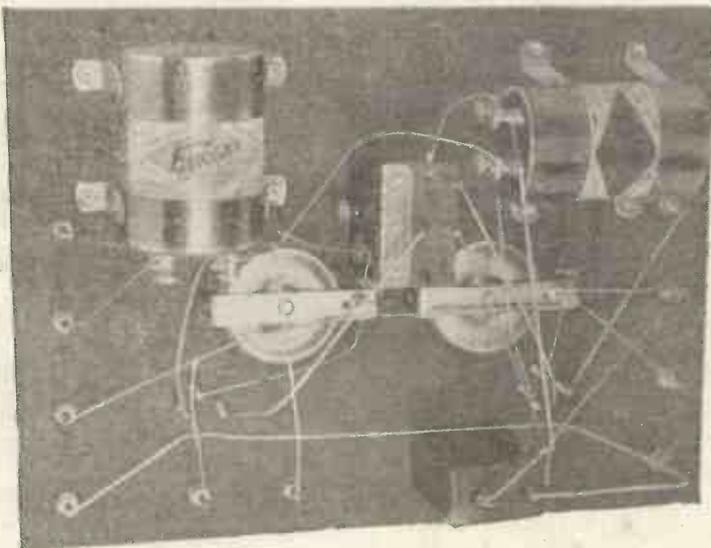


Fig. 3.—This photograph clearly shows the valve connections.

unnamed components should be avoided.

1 Ebonite panel measuring 12 inches by 9 inches by $\frac{1}{4}$ inch thick, either with matt surface or guaranteed free from surface leakage. (Paragon, Peter Curtis, Ltd.).

1 Oak or mahogany tray to take the above panel. That used was 5 inches deep and of wood $\frac{3}{8}$ inch thick.

8 Valve sockets or two-valve holders.

2 Filament resistances (Igranic).

1 2-pole 2-way anticapacity switch (Utility).

1—First stage L.F. transformer (Eureka Concert Grand, Portable Utilities.)

1—Second-stage L.F. transformer. (Eureka No. 2.)

1—2 μF Mansbridge Condenser.

11 4 B.A. W.D. type terminals.

8 6 B.A. $\frac{1}{2}$ inch screws and nuts.

Quantity of 16 gauge tinned copper wire.

Drilling the Panel

If the panel is guaranteed free from surface leakage the drilling may be carried out without preliminary matting of the panel with emery paper and oil, after it has been set out by reference to the drilling diagram. Those who wish for the minimum

amount of trouble can obtain a full-size blue print, which may be placed over the panel and the centres obtained with a centre-punch. Failing this the templates supplied with the resistances and switch should be

used, and one of the many drilling templates for valves now on the market, e.g., the Morris template. The slot for the switch lever arm can easily be made by drilling two $\frac{1}{4}$ inch holes, $1\frac{1}{4}$ inches apart, and cutting

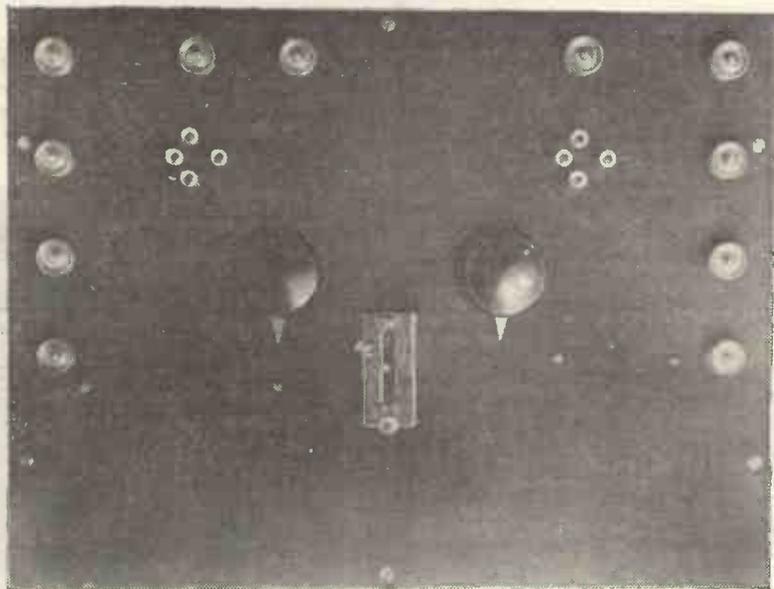


Fig. 4.—A plan view of the panel.

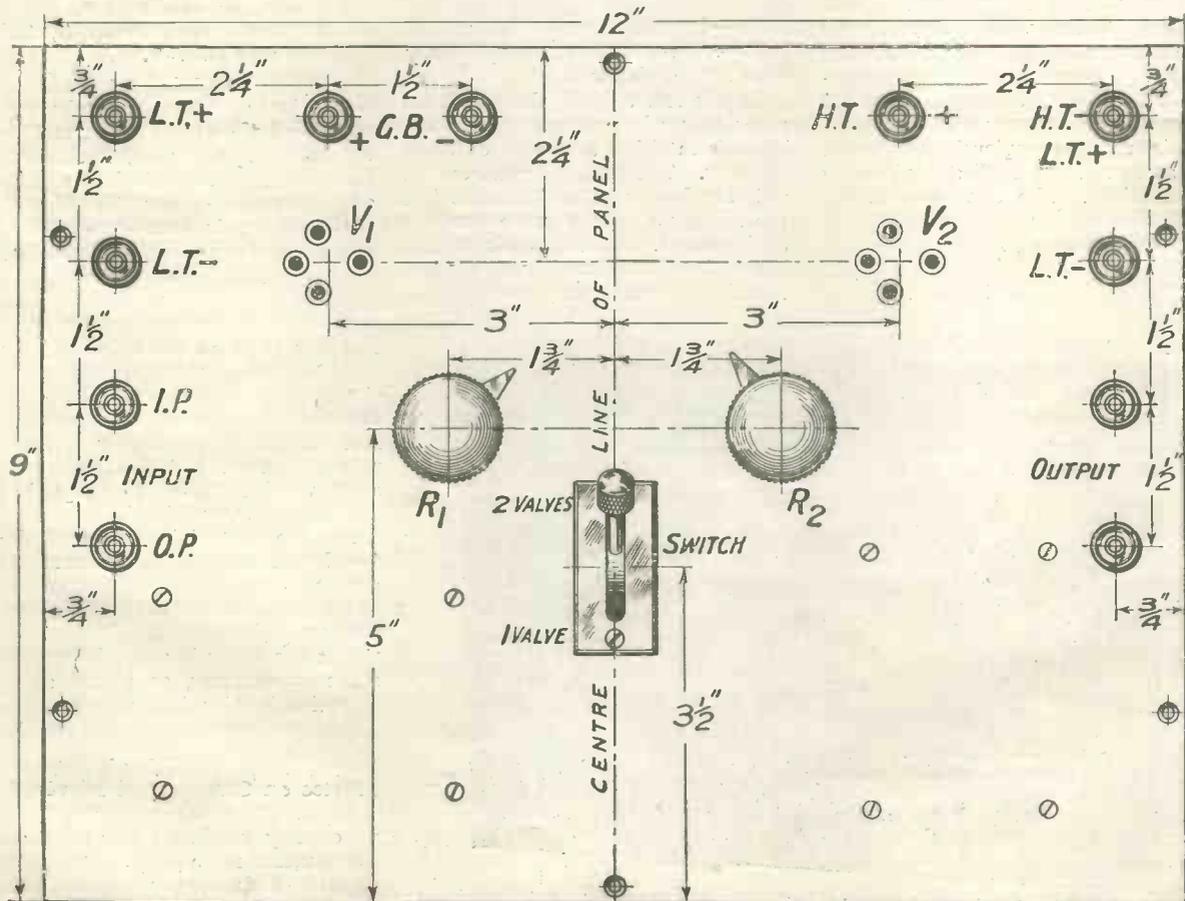


Fig. 5.—This drilling diagram should be used for marking the panel.


LISSENIUM.

GIVE THE VALVE A FAIR CHANCE—


Your valve will detect with extraordinary power with LISSENSTAT control. Only by accurate control of critical electron emission can success in distant telephony be achieved—and with no other rheostat can the performance of the LISSENSTAT be duplicated. A separate LISSENSTAT for the detector valve, one for each H.F. valve, and (desirable, but not quite so important) one for each L.F. valve, too, and you will get sharper tuning than ever you have known before. By its structure and its composition, LISSENSTAT control gives the valve a capacity to detect as no other rheostat can.

Made in three types.

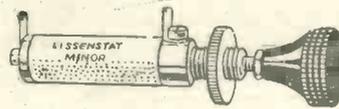LISSENSTAT MINOR (patents pending)
—is replacing thousands of discarded and inefficient rheostats. Provides LISSENSTAT control at a popular price. LISSEN ONE-HOLE FIXING, OF COURSE 3/6



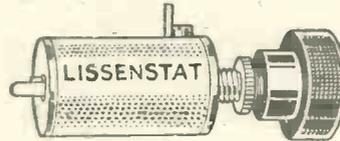LISSENSTAT MAJOR (patents pending)
—gives the most acute tuning possible. LISSEN ONE-HOLE FIXING.. .. . 7/6



LISSENSTAT UNIVERSAL (patents pending)—with its protective device for dull emitters. LISSEN ONE-HOLE FIXING, OF COURSE 10/6



RECEIVERS
FITTED
WITH
LISSENSTAT
CONTROL
ARE
EQUIPPED
FOR THE
FINEST
DETECTION
POSSIBLE.

THE APPROPRIATE LEAK VALUE—

Every different condition of reception may call for a different leak value—you can get it with the LISSEN Variable Grid Leak (patents pending). Distant stations—near-by transmissions—strong signals or weak—reaction or not—hard valves or soft—straight circuit or reflex—if you are using the LISSEN Variable Grid Leak you are certain of getting the utmost sensitivity out of your tuning. Every range of resistance value required of a leak is covered, with minute variation throughout.

LISSEN ONE-HOLE FIXING,
OF COURSE. 2/6



LISSEN VARIABLE
ANNODE RESISTANCE

SMOOTH OUT YOUR LOUD-SPEAKER DISTORTION BY PUTTING A LISSEN VARIABLE GRID LEAK ACROSS THE SECONDARY OF the last transformer or across the loud-speaker itself. First position is better, last may be easier. The difference will be very noticeable.

20,000 to 250,000 ohms, same outward appearance as the LISSEN Variable Grid Leak 2/6

PARTS THAT PULL TOGETHER—When you know that every vital part in your receiver is pulling strongly with each other, you know that you have a receiver which is the best you can ever get.

BUILT WITH ALL LISSEN PARTS—there is one for every vital place.


LISSEN LIMITED

20-24, WOODGER RD., GOLDHAWK ROAD, SHEPHERDS BUSH, LONDON, W.12.

Telephones: Riverside 3380, 3381, 3382, 1072.

Telegrams: "Lissenium London."

Issued by the Publicity Department of Burndeft Ltd.

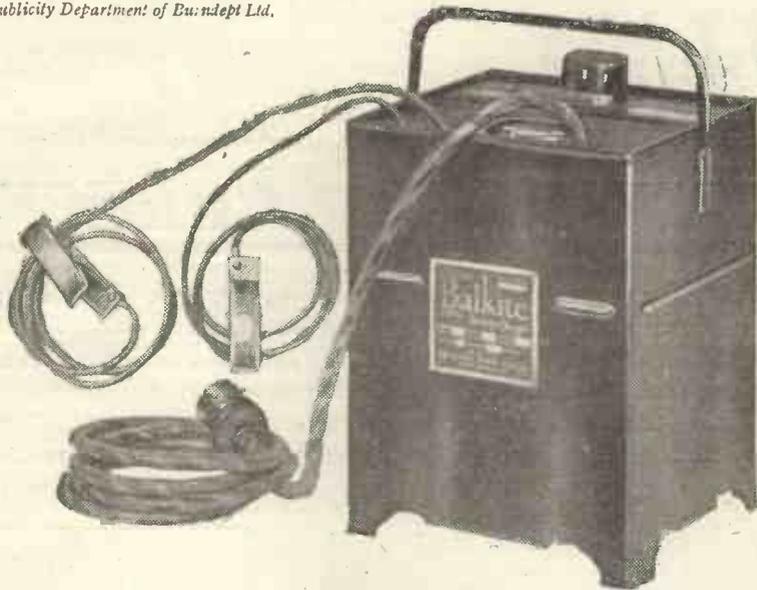

No. 491. Balkite
Battery Charger.
200-240 volts, 50-60
cycles (alternating
current) without acid
or oil.
£5 15s. 0d.

A noiseless Battery Charger[®] without valves, vibrators or moving parts

YOUR wireless set will give the best results if you keep your battery fully charged—and the life of the battery will be considerably prolonged. If your electric supply is alternating, the Balkite Charger is the cheapest, simplest, cleanest and most convenient method—you only plug it into your electric light socket.

The Balkite Battery Charger is entirely noiseless. It is based on a new principle, the use of Balkite, a rare metal which changes the ordinary A.C. current used for lighting to the D.C. current necessary for charging accumulator batteries, without the use of noisy vibrators, contact points, fragile bulbs or valves.

This Charger has no moving parts, and nothing to break, adjust or get out of order. It cannot deteriorate through use or disuse. It delivers a taper charge, and cannot discharge, short circuit, or damage the battery by overcharging. It needs no attention other than an occasional filling with distilled water. Its operation does not create disturbances in your set or your neighbours'. It is simple, efficient, cannot fail to operate if properly connected, and is practically indestructible except through abuse.

It operates on a supply from 200-240 volts, at a frequency of 50-60 cycles. Several other voltages and frequencies can be supplied to order. The charging rate being 2½-3 amps., a 6-volt 50-ampere accumulator will be completely charged in 20 hours at a cost of less than ½d. per hour.

Can be obtained through leading Radio dealers everywhere, and at Burndeft Agents and Branches.

BURNDEPT LTD., Aldine House, Bedford St., Strand, London, W.C.2.

Telephone : Gerrard 9072.
CARDIFF : 67, Queen Street.

Telegrams : Burndeft, Westrand, London.
NORTHAMPTON : 10, The Drapery.

LEEDS : 12, Basinghall Street (near City Square).

BURNDEPT
WIRELESS APPARATUS

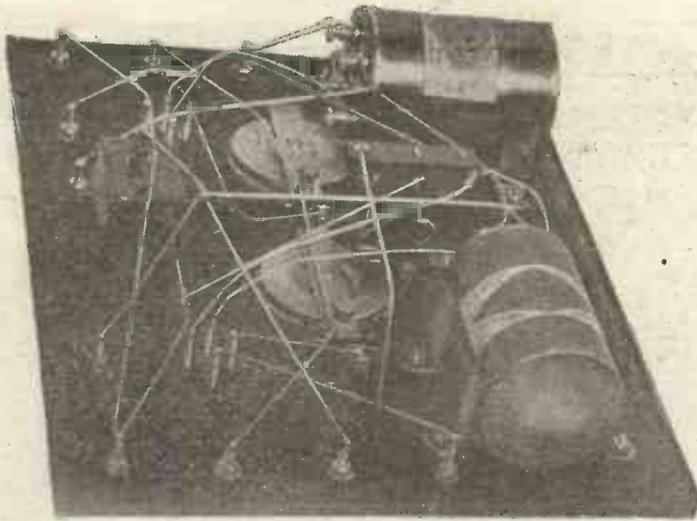


Fig. 6.—Notice that the transformers are arranged at 90°.

away with a fret-saw a 1/4 inch strip between them. This may finally be cleared smoothly by using a flat file.

Mounting the Components

Mounting the components is a simple and straightforward procedure, so that little need be said here. It is easiest first to mount the valve sockets and terminals; next follow

the switch and the rheostats and finally the transformers. These latter are held by 6BA screws through the panel and nuts. As the fixing holes vary slightly it is advisable to mark their positions with the transformers in place.

The Wiring

Wiring is carried out with 16

gauge tinned copper wire which was obtained on a reel. To straighten this out the best procedure to follow is to secure one end to some fixture run off two or three yards and stretch until it is felt to give. It can then be cut off in suitable lengths, giving a perfectly straight and professional appearance to the finished wiring. Joints as far as possible should be soldered rather than secured by lock-nuts, and a few soldering hints may not be amiss here. Before soldering file the tops of terminals and valve leg shanks to give a perfectly bright surface. Give them the merest touch of flux and then tin with a really hot clean iron. An iron at the right temperature assures that the tinning is quickly done before the shanks become heated and tend to become loose. As a precautionary measure the nuts may be given a half-turn when tinning is completed. Now, referring to the photographs and wiring diagram, proceed with the remainder, keeping the leads short and well spaced. So that no difficulty should arise with the switch connections a close-up photograph of these is given in Fig. 8, and the points to which individual wires are taken is indicated. Comparison of this with the other photographs of the wiring

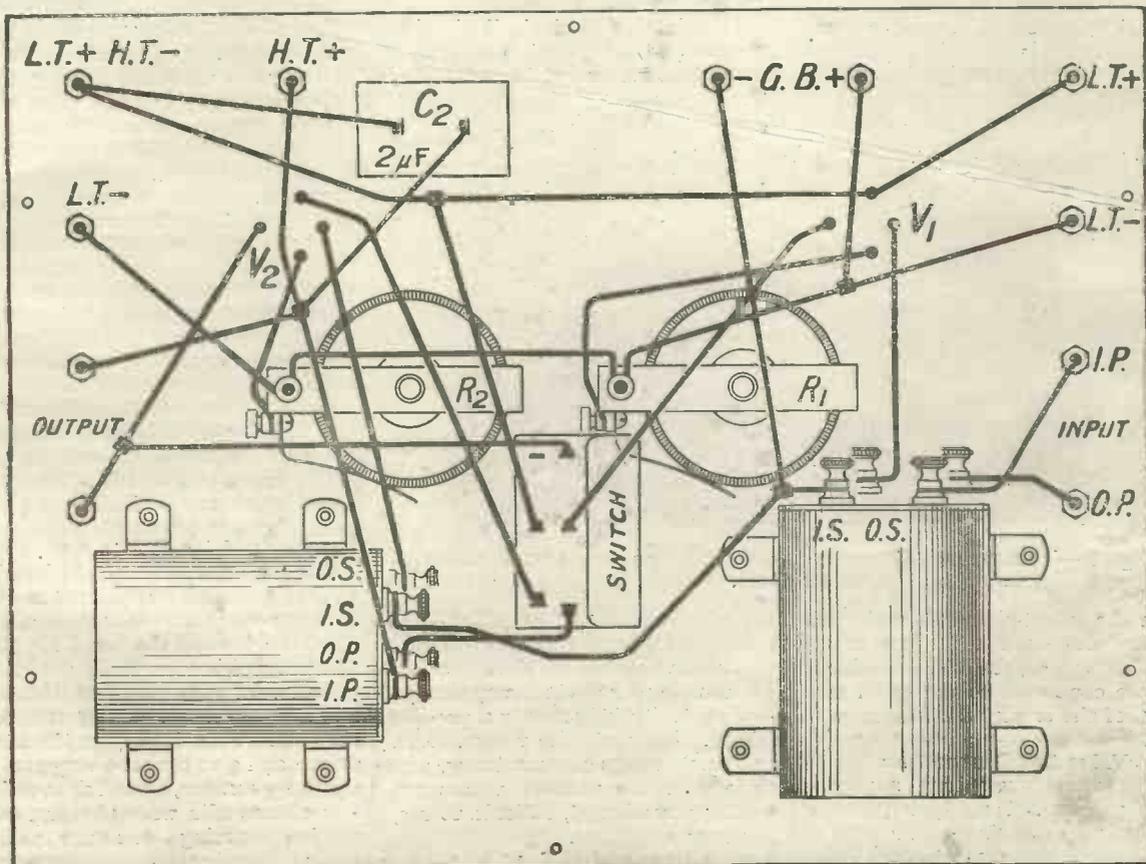


Fig. 7.—Back of panel wiring diagram. Where wires are joined is shown by the black squares.

will clearly show how the leads go. The $2\mu F$ reservoir condenser across the H.T. supply is not fixed to the panel, but is securely held by its soldered connections. In the case of connections to the transformers which are not soldered, the terminals should be firmly screwed up, as any noise due to loose contacts is amplified to the same degree as the received signals.

Fixed Condensers

From the circuit diagram it will be seen that no condenser is placed across the Input terminals. This is omitted since in most sets there is already one across the telephone terminals. If this is omitted on the detector unit one of $.001$ to $.002 \mu F$ may be connected externally across the Input terminals.

Connections for a Crystal Receiver

When a crystal receiver is used as the detector unit the connections are as follows:—

The telephone terminals are taken to Input terminals of the amplifier, and the L.T. terminals on the left of the panel are left free. H.T. and L.T. connections are made to the appropriate terminals to the right of the panel; H.T. — and L.T. + being taken to the corner one. Phones or loud-speaker are connected to the Output terminals. Depending on the type of valve and H.T. voltage used a suitable grid battery should be connected to the terminals marked Grid Bias + and —, care being taken to get the polarity right. If a low value of H.T., usually under 60 volts or so is used these terminals may

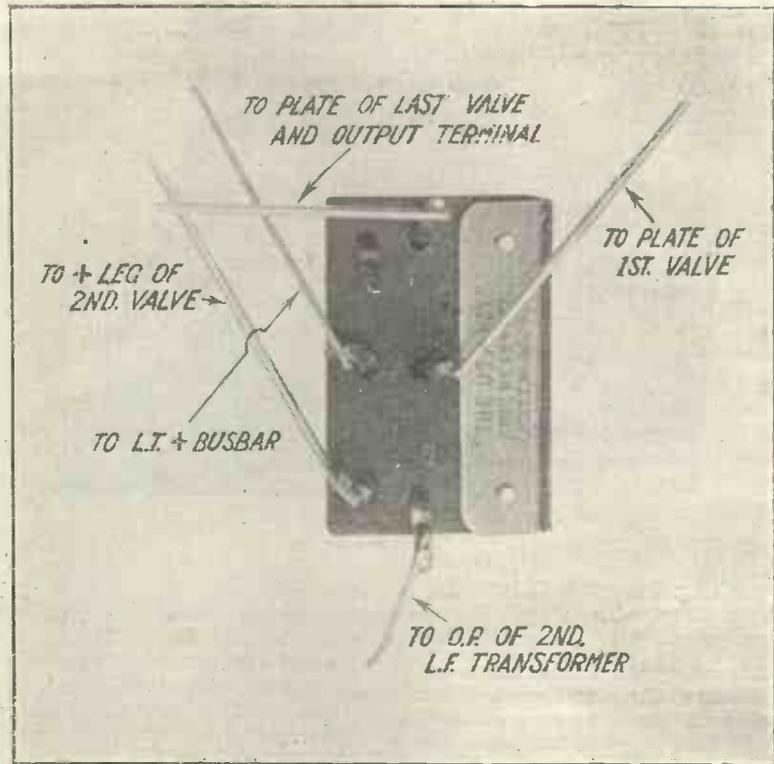


Fig. 8.—A close-up view of the switch connections.

that previously described. With other valve sets than this no difficulty should be experienced in connecting up.

Power Amplification

When the word "power" is con-

valves of the 6 volt, .25 ampere type will be found quite suitable with 60 to 100 plate volts and from 3 to 5 volts negative on the grid. Ordinary general purpose valves may be used, and in this case with a 100 volts a suitable grid bias value is of the order of 3 volts.

Test Report

On an extremely poor temporary aerial of flex, 100 feet in length and 15 feet average height some 15 or so miles S.E. of 2L.O. that station gave excellent loud-speaker strength with 2 valves and crystal, being pleasantly audible in the next room.

With the Neutrodyne set several of the B.B.C. and Continental stations gave uncomfortable volume on the loud-speaker even with the poor aerial which was available.

Blue Prints

For the benefit of readers who wish to have a minimum amount of trouble in constructing the instrument, a full-size blue print of the panel No. 78 A and of the wiring No. 78 B is available, price 1s. 6d each post free from our Sales Department. Panel transfers may also be obtained from the same source, and give the set a very professional appearance, as well as avoiding any chance of a wrong battery connection burning out the valves through leaving the terminals unmarked. To the beginner their use is particularly advised.



Fig. 9.—The connections to the first transformer are seen to the left.

often be short-circuited and this battery dispensed with. In many cases, as is usual, the L.T. — terminal may be connected to the earth terminal of the crystal set with advantage.

Valve Set Connections

With the Neutrodyne set previously described straight through connections are made by cross-linking as shown in the photographs of the two units; whilst battery connections are made in similar manner to

connected with that of "amplifier," the uninitiated usually jump to the conclusion that the amplifier is much too complex for the ordinary man to deal with. This is merely a popular fallacy. Only suitable valves, H.T., and transformers are necessary, and these with the modern valves are neither complicated, difficult to use, nor very expensive.

Valves and H.T. to Use

Where large volume of sound is desired the modern small power



INDISPENSABLES TO MAXIMUM RADIO EFFICIENCY



GOOD COMPONENTS DESERVE A GOOD PANEL

UNIFORM
FINE GRAIN
DEAD MATT
FINISH
GUARANTEED
NON-METALLIC
SURFACE
FREE OF LEAKAGE

PARAGON "The Best Made." EBNONITE PANELS

Radio Quality
Post Office Specification

TESTED
AND
RECOMMENDED
BY
"MODERN
WIRELESS"

Special panels for Receivers described in this or any previous issue of
"Modern Wireless"—CUT, EDGES SQUARED and GROUND,
1d. per square inch. Postage 6d.

STANDARD SIZES.

8 x 6 x 3/8	2/6	24 x 10 x 1/4	14/6	18 x 6 x 1/4	6/9
8 x 6 x 3/4	3/3	24 x 12 x 1/4	17/6	12 x 8 x 1/4	6/-
10 1/2 x 8 1/2 x 1/2	5/3	8 x 5 1/2 x 1/4	2/9	10 x 8 x 1/4	6/9
12 x 10 x 1/2	7/3	10 1/2 x 7 x 1/4	4/7	10 x 5 x 1/4	2/3
12 x 12 x 1/2	8/6	12 x 6 x 1/4	4/6	10 x 9 x 1/4	5/8
14 x 12 x 1/2	10/-	22 x 11 x 1/4	15/3	9 x 5 1/2 x 1/4	3/5
16 x 12 x 1/2	11/6	16 x 9 x 1/4	9/-	10 x 5 x 1/4	3/3
18 x 12 x 1/2	13/-	12 x 11 x 1/4	8/3	12 x 9 1/2 x 1/4	7/6

PARAGON POLISHED MAHOGANY EBNONITE


Is NOT a composition, but GUARANTEED POST OFFICE QUALITY EBNONITE,
and is of similar specification to the now universally used PARAGON EBNONITE.

PANELS CUT TO SIZE, Squared, edges ground, 1d. per square inch.

THE NU-GRAVING

PANEL MARKING PROCESS


COMPLETE AS SHOWN, 6d.

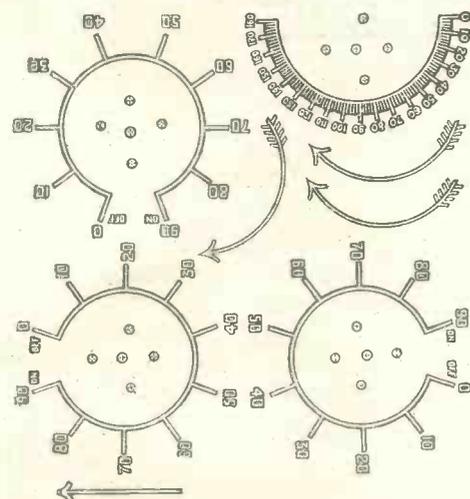

AERIAL EARTH TUNER
REACTION CONDENSER
TELEPHONIC SERIES
CRYSTAL AMODE INPUT
H.T. H.T. ON ON
L.T. L.T. OFF ON
H.F. H.F. L.F. L.F.
VALVES A.T. I.A.T. I
OUTPUT H.F. G.A.T.G
REC. LOUD SPEAKER
ON (A) (E) (D) DET.
AMPLIFIER PARALLEL
MAX. A.T.L.C. REGEN.
OFF OFF OFF OFF
+ + + + +
- - - - -
PREAMPLIFIER DUAL
LOADING COIL. FINE
1 2 3 4 5 6
7 8 9 10 11 12
REACTION GRID BIAS
A B C D E F G GRID LEAK
COARSE REVERSE
100 RESISTANCE JACK
200 RESISTANCE DUAL
CAPACITY VERNIER
VARIOMETER H.F. C

REDUCTION IN PRICE.

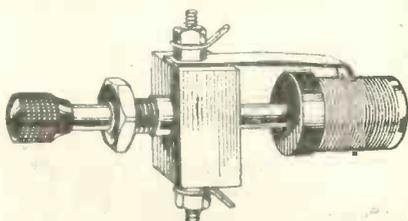The following reduced prices for Nu-graving series operate from 15th Nov. :
Series 1, 2 and 8, 3d. each. Series 3, 4, 5, 6 and 7, 2d. each.



CURTIS FILAMENT RHEOSTAT.

That better reception is obtained if filament control is perfect can only be understood by fitting the CURTIS. 0 to 40 ohms; quick and slow action; D.E. valves may be used in conjunction with 6-volt battery if your Rheostats are CURTIS.

Price 5/-

PARAGON-CURTIS ONE PIECE MICA CONDENSER



Accurate and Uniform Capacity.

Technical and Constructional Authorities reiterate their opinion that the successful home construction of receivers implies the close adherence to the original specification. The ordinary method of fixed condenser manufacture prevents any guarantee of uniform capacity. The method adopted, however, in the PARAGON-CURTIS not only guarantees uniform capacity throughout production, but guarantees also 5 per cent. accuracy. It will be realised that in any published circuitous specification of fixed condensers of a specific value—the PARAGON-CURTIS you buy is uniform with its fellow used in the original design.

An Important Consideration.

.0008 to .006	2/6
Complete with Grid leak Clips	2/9
Grid leak	1/8

Home constructors who wish to build a successful receiver should apply for our 16 pp. catalogue of "Raw Materials and Accessories" free on request.

Paragon-Curtis Products are always of uniform and dependable quality. Ask your local agent for full particulars and illustrated catalogues.

PETER CURTIS, LTD. 75, CAMDEN ROAD, N.W.1.

Telegrams: "Paracurtex." Phone: North 866.

BIRMINGHAM: 76, Newall Street. Central 7236.
MANCHESTER: 312, Dean-gate, Central 5995.

In conjunction with

THE PARAGON RUBBER MFG. CO., LTD.

They notice the improvement immediately

A NOTICEABLE improvement from every standpoint is the immediate outcome of fitting a Powquip Transformer. Every word, every sound is clearer, truer and more distinct. The volume of sound obtained is greater, yet the tone is richer, softer. All distortion of sound, all vibrating or internal noise is entirely absent.



TRANSFORMERS

THE "POWQUIP" is thoroughly tested, thoroughly finished, thoroughly reliable. It works in conjunction with the ordinary standard valves. The increasing demand for the Powquip Transformer, which this year is already 300 per cent. greater than that of last year, shows the confidence that Wireless Enthusiasts generally place in its abilities. The 12 months' guarantee which is attached to every "Powquip" proves that we ourselves are confident that we are giving full value for money.


Stocked by all recognised Wireless Dealers

Open Type 14/6 Shrouded Type 18/-

The
POWER EQUIPMENT
 COMPANY LIMITED

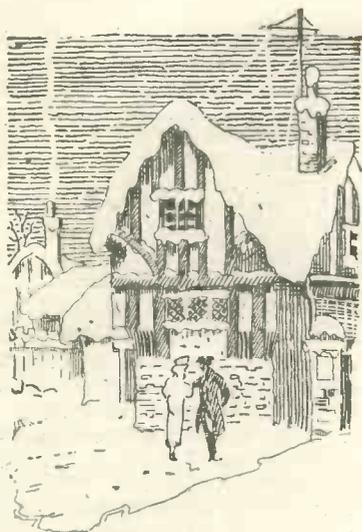
Kingsbury Works, The Hyde, Hendon, N.W.9.





How the Advent of Radio and Broadcasting has Changed our Christmas

By D. J. S. HARTT, B.Sc.

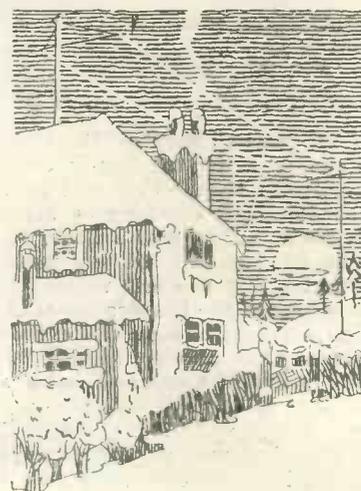

AT Christmas time the natural human instinct for enjoyment and freedom from the worry and strain of everyday life asserts itself. Remembering the origin of this time-honoured festival we can appreciate how the spirit of festivity and carnival has been fostered through the ages. Modern conditions and the progress of civilisation have rendered it even more prominent and more general. Let us then picture the Christmas before the era of wireless and broadcasting, and show how the latter has influenced Christmas and the manner in which we spend it. People in all stations of life make preparations for some time beforehand in the hope of spending those few days in a manner appropriate to the occasion.

What the Old Time Christmas lacked

Take, for instance, the town-dwellers. Their Christmas provided them with new pleasures, sources of fresh activities, a rest, in the sense of a change from their normal existence, and also the opportunities of forming new friendships. To country folk some of these enjoyments and privileges were denied. Yet they, in their simpler manner, perhaps, also made arrangements and preparations to celebrate the occasion in a fitting manner. Others, less fortunate, living in isolated and possibly desolate regions, sought to break the monotony of their existence as best they could. Constituting another section of the community to whom Christmas means more than is sometimes realised are the invalids and occupants of our hospitals, many of whom are destined to suffer until the end of their days. Only those responsible for the care of such unfortu-

nates realise to what an extent they look forward to an occasion such as Christmas, when they enter, temporarily it is true, upon a new existence, when the clouds of despair lift and reveal the promise of a brighter future. But what did all these people lack, not only during their everyday lives, but particularly at Christmas? Their unity of purpose was



well defined, but something was lacking to provide, so to speak, a link between them. The science of wireless has provided this link. The wide appeal of wireless and broadcasting cannot be denied. Children and adults, poor and rich alike, have succumbed to its charms. In recent years science has given us many things, some of which are luxuries, and others are regarded as a necessary part of our

daily life. To the latter category belongs the science and art of broadcasting, which has assuredly come to stay.

Broadcasting in everyday life

Before we analyse how the introduction of broadcasting has influenced our Christmas, it will be interesting to see what effect it has had on our daily life. Apart from the training in aural observations, as an aid to stimulating the imagination, which it must necessarily give, it has widened our outlook on life in general. The lectures have incited further interest to read more, to get to know more of the world, its history, its peoples and their activities—more, in fact, than we should ever learn while confined to the comparatively narrow channels of our own small spheres. The musical programmes, dramas and plays have given us additional pleasures and food for meditation and thought. The time signals, weather forecasts and news bulletins have proved of interest to many, and a boon to those who previously lived a life of comparative isolation. The educational value of broadcasting, its power to give pleasure to all classes under varied conditions, and its extensive appeal are indicated very briefly in these few remarks.

Creating the right atmosphere

Its appeal will doubtless be more extensive at Christmas time. It will forge that link between not only our own people, but between them and the inhabitants of other countries, giving them a common interest. On this occasion it will be both a national and an international aid for our enlightenment and our pleasure. It will serve to unite the people in their common

rejoicing, help to create the essential atmosphere, and spread it throughout the land.

Christmas entertainment at home

We can well imagine the evening scene in a typical family during Christmas time. Gathered round the fire, each comfortably settled in his or her favourite chair, they will be listening to the music, speeches and concerts transmitted from one of the broadcast stations. The darkness outside will enhance the comfort and security within. The spirit of Christmas, with all its attendant joys and pleasures, will pervade the air. No doubt the programmes will be arranged to heighten the effect, and help to create and maintain that atmosphere which only Christmas brings. For family use the loud-speaker will probably be most used, but others will derive equal enjoyment by listening with the telephones. They are all happy and comfortable in their own home and have no need to seek their pleasure farther afield. The state of the weather does not inconvenience them; they are at home but still in touch with the outer world, invisibly but realistically linked. Thousands of others, in common with them, share the same pleasure. The people who will appreciate it most are undoubtedly those who live in the less densely populated parts of our country.

The Broadcasting of Church Services

Here may be mentioned an innovation which, due to the characteristic enterprise of broadcasting companies, has been carried out successfully. I refer to the broadcasting of church services. Many, it is true, object to the use of broadcasting for such purposes. This may be due to prejudice, or inability to keep pace with the times. However, it is a matter for personal opinion, and there are others, particularly those whose disabilities confine them to their homes or to the seclusion of hospitals and similar institutions where they are almost cut adrift from external affairs and happenings, who appreciate the enterprise and courage of the broadcasting companies in this direction. An occasion such as Christmas is perhaps more fitting than any other for the broadcasting of some form of church service. Doubtless this will be arranged as a special part of the programmes from the various broadcasting stations.

Simultaneous Broadcasting

The progress of wireless is fully illustrated in the great strides recently made in the matter of simultaneous broadcasting. During the Christmas period this, again, should prove a powerful factor in, so to speak, uniting all sections of the community in various parts of the country, and perhaps in forging the links of greater international friendship. Christmas is such a time when people are more susceptible to these influences. Our large cities and towns will be linked to, say, London through the medium of simultaneous broadcasting. All listeners, even those possessing the humblest set, will be able to participate in the enjoyment of the same programme. It is wonderful to picture the state of affairs at Christmas time, for instance, existing in a country where simultaneous broadcasting has been developed into the complex, yet reliable, system we have in the



country. Entertainment will be provided for millions of listeners. To those unfamiliar with the technical side of the question the wonder of such an achievement is still more remarkable.

There is, however, still another side to the matter. How will the more serious wireless man, the experimenter, spend his Christmas? Frankly, one cannot say. Will he take this opportunity to have a rest from the work which constantly claims his attention, keeps him deeply interested night after night, and which is of great importance and value to the advancement of the science? Or will he be only too pleased to avail himself of this extra spare time to do further work. One is at a loss to know, but so great is the hold which experimental wireless has on many amateurs that one would not be surprised if they adopted the latter course. Their work alone is to many a pleasure, and so they will be amply compensated for

what they may miss of the enjoyment of broadcasting, and of the more usual Christmas pastimes. In the course of their work they may even get into touch with very distant lands through the medium of wireless, and one can imagine the exchange of seasonal greetings which would take place. Another tie of friendship would thus be made, and this on a particularly appropriate occasion.

Catering for the Dancer

A further influence of broadcasting on our Christmas festivities concerns those interested in dancing. Here the medium of broadcasting proves of immense value. Dance music will be broadcast from many of the stations during the Christmas period, and dancers provided with the proper receiving equipment, and having access to a suitable room or hall, will have the pleasure of dancing to the accompaniment of some of the best orchestras and bands in the country.

Such enjoyment is by no means confined to the actual dancers, for many who do not take an active part in the dancing still enjoy the music and the atmosphere of pleasure.

A Better Christmas

Sufficient has been indicated to show how the advent of wireless, its expansion and simplification, its application to broadcasting, so that it has become both the hobby and the pleasure for millions of people, has changed our Christmas. We now enjoy this festival more collectively and in a wider sense, and no one can doubt that it is to our benefit. It has helped to spread a broader spirit of comradeship, a wider outlook, and last, but not least, a better appreciation of our common needs and troubles.

In conclusion, we owe to broadcasting a linking together of the peoples, a breaking down of their insularity, and consequent spread of a better spirit of co-operation, and at Christmas time the influence of these factors is more strongly felt.

As a source of Christmas entertainment nothing is more adaptable, and so far-reaching, as the medium of broadcasting. Always a difficult problem, the provision of satisfactory programmes may perhaps be a little easier at Christmas, for all listeners will have only one object, that of being entertained by light music, good humour, and, say, an interesting play or opera. A few may be disappointed, but it is certain that good entertainment will be provided for the vast majority to pass the happy hours, and promote a bright atmosphere for their Christmas activities.



You have a friend

who is interested in Wireless. Probably like yourself he is a keen constructor and investigates the claims made for each new circuit brought out in MODERN WIRELESS.

When the inevitable problem of Christmas gifts presents itself, solve it as far as he is concerned by giving him a useful wireless component. Such things as variable condensers, change-over switches, resistances, etc., are certain of a ready welcome on any wireless bench.

From the wide range of Dubilier products you will have no difficulty in selecting a present which will be at once useful and out of the ordinary.

Moreover, if your present bears the Dubilier name you will have the satisfaction of knowing that you have selected the very best article in that particular line.

No friend could expect more. No friend should give less.




Mullard Double

Mullard H.F. & L.F. Dull Filament Master Valves

THE introduction of the dull filament valve was met with sincere appreciation from those who realised the marked advantages made possible by this design. With customary thoroughness, the Mullard dull filament type valves showed steady improvements in this design, till to-day you can obtain Mullard specialised dull filament valves for both H.F. and L.F. operation.

Mullard Double Ring Valves (named to distinguish them from the Bright Filament H.F. and L.F. Single Ring Valves) have an efficiency in operation that will surprise you, the secret of their reliability and power being the wonderful precision in design and assembly that is maintained during their manufacture, and the extreme care that is taken to ensure their perfect evacuation and final testing. Their sensitivity does not become weakened in service, and their mechanical strength does not permit any possible internal contact between the filament and electrodes.

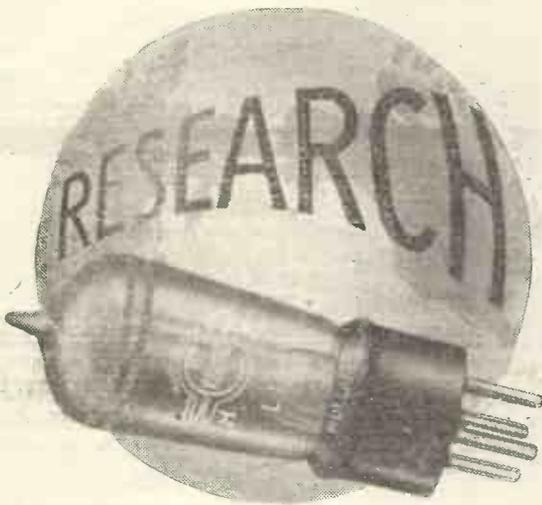

Mullard

THE • MASTER • VALVE

Obtainable from all electricians, wireless dealers, ironmongers, etc., etc.

Ring DULL FILAMENT Valves

Are you Missing

- | | |
|---------------------------------------|----------------------------|
| (1) Powerful amplification. | (5) Purity of tone. |
| (2) Minimum current consumption. | (6) Constant sensitivity. |
| (3) Reduced battery cost and trouble. | (7) Mechanical robustness. |
| (4) Long filament life. | |

Then you need Mullard H.F. and L.F. Dull Filament Valves in your set.

Ask for Mullard H.F. Double Red Ring Valves for


H.F. AMPLIFICATION,
Type D.3 for accumulators,
Type D.06 for dry cells,
25/- each.

The "REAL" Long Distance Valve.

Ask for Mullard L.F. Double Green Ring Valves for

L.F. AMPLIFICATION,
Type D.3 for accumulators,
Type D.c6 for dry cells,
25/- each.

The "REAL" Pure Tone Valve.

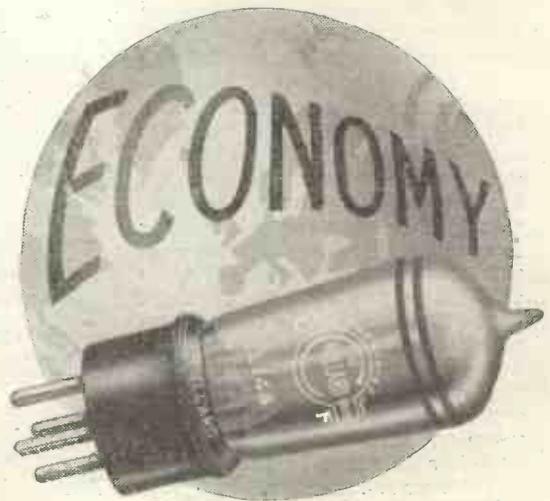


Mullard

THE MASTER VALVE

Advt. The Mullard Radio Valve Co., Ltd. (M.W.), Nightingale Works, Balham, S.W.12.

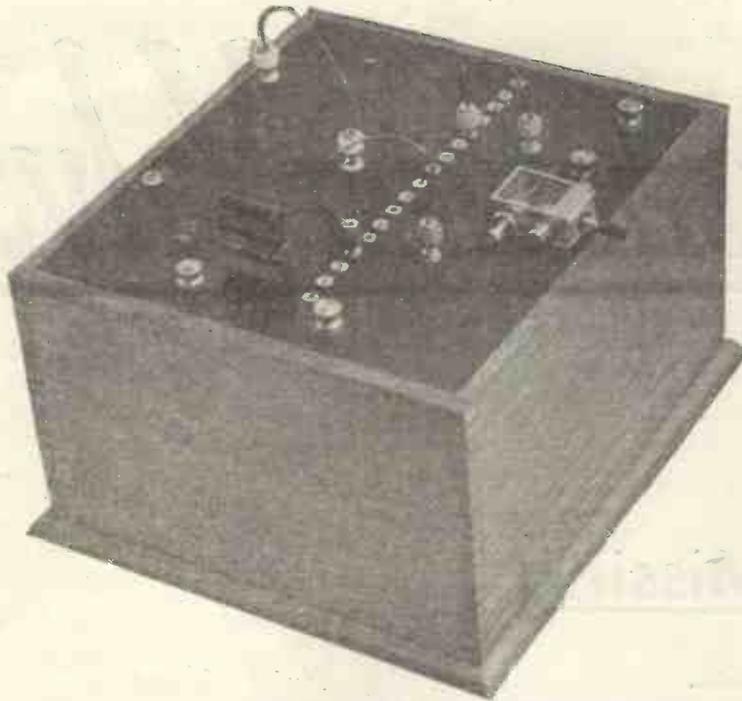In replying to Advertisers, please use Order Form enclosed.



A Low-loss Crystal Set.

By **STANLEY G. RATTEE**,
Member I.R.E., Staff Editor.

A simple set which may be used on short waves and yet covers the ordinary B.B.C. waveband and 5XX. with a loading coil.

The finished receiver presents a neat appearance.

IT is almost safe to say that every crystal user finds his main interest in the reception of his local broadcasting station or else in the tuning to 5XX. In such circumstances it may be of further interest to listeners to know that there are many fascinating experiments which may be carried out in the reception of stations using wavelengths below those devoted to B.B.C. transmissions, as, for instance, the many amateur transmitters. These stations using low powers are for the most part to be heard working on wavelengths well below 300 metres, and apart from the C.W. telegraphic communications in which they indulge, and which incidentally cannot be received upon the straightforward crystal set, there are a good many telephony transmissions which offer considerable scope in the practice of short-wave reception.

Clix Arrangements

The crystal set about to be described is particularly suitable for work of this kind, in that the tuning arrangements permit by various movements of the Clix plugs, one, two, three, four, five, up to sixty-five turns of the inductance to be connected in the aerial circuit. These sixty-five turns are of large gauge wire and are wound upon a special former which will be described later.

For the reception on the B.B.C. wavelengths these same turns are used plus thirty-five turns of a

smaller gauge wire wound upon a separate former, also to be described later. The tuning arrangements in this case are carried out in precisely the same way as for the short waves, by varying the positions of the Clix plugs.

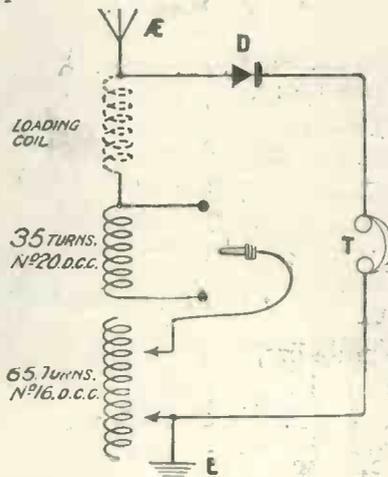


Fig. 1.—The theoretical arrangement.

Those desirous of receiving the longer wavelengths, including Chelmsford, are also catered for in that the receiver is fitted with a coil socket for suitably loading the inductance within the set; tuning in these circumstances being carried out as before by changing the positions of the plugs until the correct number of turns is in circuit.

Neat Appearance


The photographs of the receiver will give the reader some indication of the appearance of the instrument and will also make clear how the scheme of things relative to tuning is made practicable. Those photographs showing the back of the panel will indicate that no very great skill in wiring is called for, and also give some indication of how the coils are made and mounted. The coil with the vertical winding is for the reception of short waves, whilst the same coil connected in series with the second coil, the turns of which are wound horizontally and crossing each other, permits of the reception of the B.B.C. stations. In some circumstances, such as when the receiver is connected to a large aerial, the B.B.C. stations will be best received upon the sixty-five turn coil alone.

Terminal Connections

Looking, for the moment, at the photograph showing the face of the panel, the two terminals on the left are for the aerial and earth connections, whilst between them will be seen the coil mount for the loading coil; this socket will be short-circuited, of course, when it is desired to receive either short wavelengths or the B.B.C. stations exclusive of 5XX. The two terminals in the bottom right-hand corner of the panel are for the telephone receivers. Referring now to the long line of Clix sockets which extends across the panel,

Wireless Values only Obtainable at **GAMAGES**

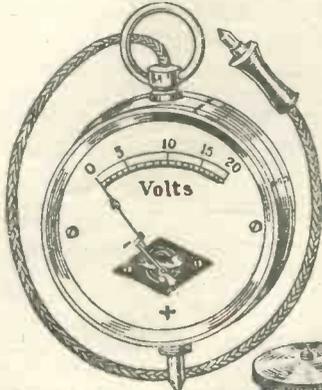Here is a further Selection of Gamage Acces-
sories — all calculated to improve your
Results and make things easier for you. Distant
customers may Order by Post with every confi-
dence—Satisfaction or money refunded in full!



The finest Crystal in the
World, and the one to give
utmost results is Gamages famous

PERMANITE

Regd. No. 438341.

Get a piece! Gives clear, power-
ful results, is highly sensitive,
and remains in adjustment
longest. In two Sizes.


Large piece (easily broken), Price, **1/6** post free
Smaller Size to fit the cup, Price, **1/-** post free

Voltmeters

Dead-beat Type. Very reliable. Nicely made and finished.

Readings, 0-3, 0-6, 0-12, 0-15, 0-20 volts.

Price, each **5/-** Post 6d.

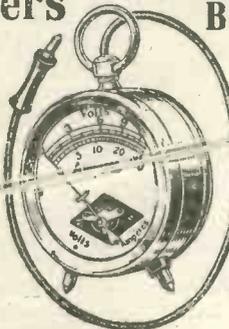

Basket Coil Holders

This Basket type Coil Holder is beautifully made and finished in the best ebonite. The quality is of Gamages usual high standard. Price **1/6** Post 3d.

Insulated HOOKS

Well made and nicely finished.

Ideal for Indoor Aerials. Size 2 ins. or 1 1/2 ins. over all. These hooks come under the usual Gamage guarantee of Quality. Send for a sample lot to-day. Price per dozen **1/6** Post 3d.



Volt - Ammeters

Beautifully made and nicely finished.

Watch Type Combined Dead-Beat Volt-Ammeter.

In Nickelled Brass Case.

Readings, 0-12 volts; 0-30 amps. In the usual high standard of quality. Price **7/6** Post 6d.




New Coil Socket

Pay us a visit of inspection


Order direct from this announcement on money-back guarantee

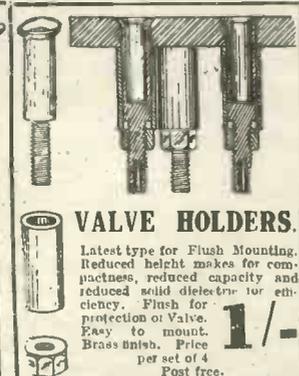New Type Coil Socket with support for Home-made Coils. Best ebonite socket. Each **1/6** Post 2d.



VALVE HOLDERS.

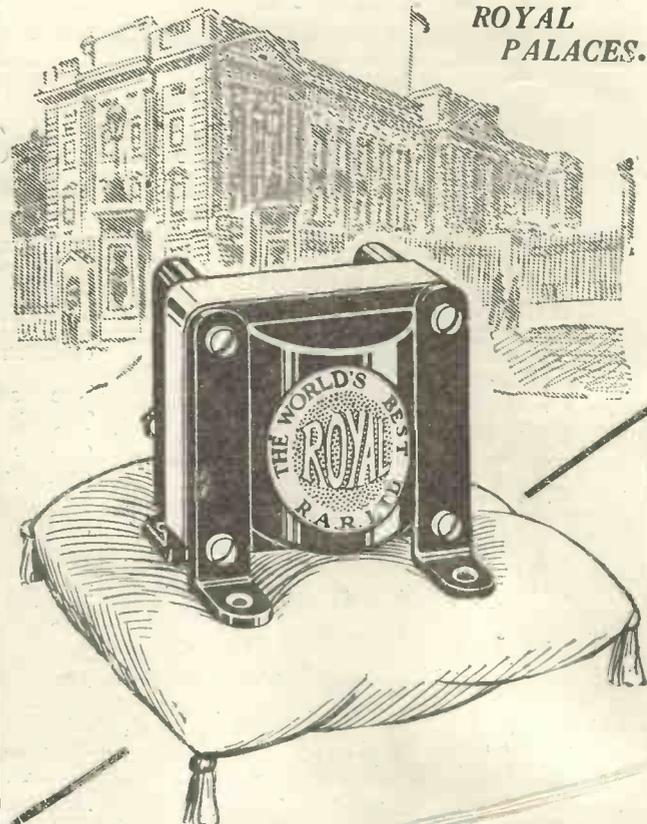Latest type for Flush Mounting. Reduced height makes for compactness, reduced capacity and reduced solid dielectric for efficiency. Flush for protection of Valve. Easy to mount. Brass finish. Price **1/-** per set of 4 Post free.



POWER & TONE

To secure the Luxury of Pure Tone, Brilliant, Clear and Undistorted

USE A

"ROYAL"

Standardised by Manufacturers of the Best Sets. Price **£1**

FULLY GUARANTEED.

AN OFFER We are so confident of the supreme quality of the "ROYAL" Low Frequency Super-Transformers that we are willing for you to test them against ANY other on the strict understanding that we will refund the purchase cost on return to us within fourteen days, post paid.

R. A. ROTHERMEL, L^{TD}

Manufacturers and Suppliers of all kinds of Radio and Scientific Instruments

24 & 26, MADDOX ST., LONDON, W. 1

Phones: MAYFAIR 578 & 579.

A. W. GAMAGE, Ltd., Holborn, London, E. C. 1
And at BENEFINKS, CHEAPSIDE, E. C. 2

In replying to Advertisers, please use Order Form enclosed.

A perfect unison of power and quality

IT can be said that both efficient and distortionless amplification is attained for the first time—a perfect unison of power and quality. The Marconiphone "Ideal" Transformer gives high and equal magnification of all notes in the musical scale—of every tone and overtone.

The sound construction of the Marconiphone "Ideal" Transformer starts by unsparing use and exhaustive tests of the highest grade materials, and is completed by an entirely new method of checking the assembled instrument for actual amplification at various frequencies. Its perfect design is particularly demonstrated in the successful way the "Ideal" is used in multi-stage amplification, without risk of low frequency oscillation.



The great claims of the Marconiphone "Ideal" Transformer for highly efficient and distortionless amplification are upheld by the guarantee which each instrument carries.

Apart from its excellent performance, it is only necessary to examine the materials and workmanship of the Marconiphone "Ideal" Transformer to realise that in price it is moderate.



Marconiphone "IDEAL" TRANSFORMER GUARANTEED DISTORTIONLESS

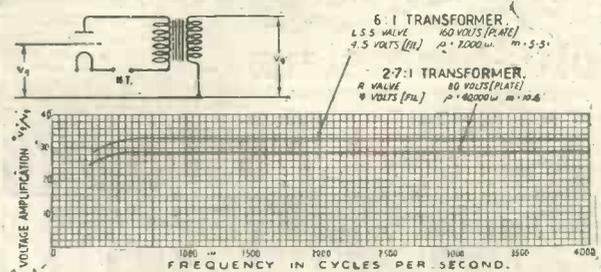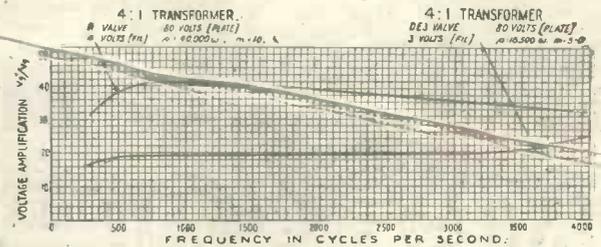
PRODUCED
IN THREE RATIOS:
2.7 to 1, 4 to 1, 6 to 1.
PRICE - £1 15s. EACH.



THE GUARANTEE

which goes with each Marconiphone "Ideal" Transformer guarantees that the amplification curve at all points comes within five per cent. of the example shown above, when used with a valve with the same constants as quoted. The guarantee also provides for free replacement where a break in the winding occurs within six months.

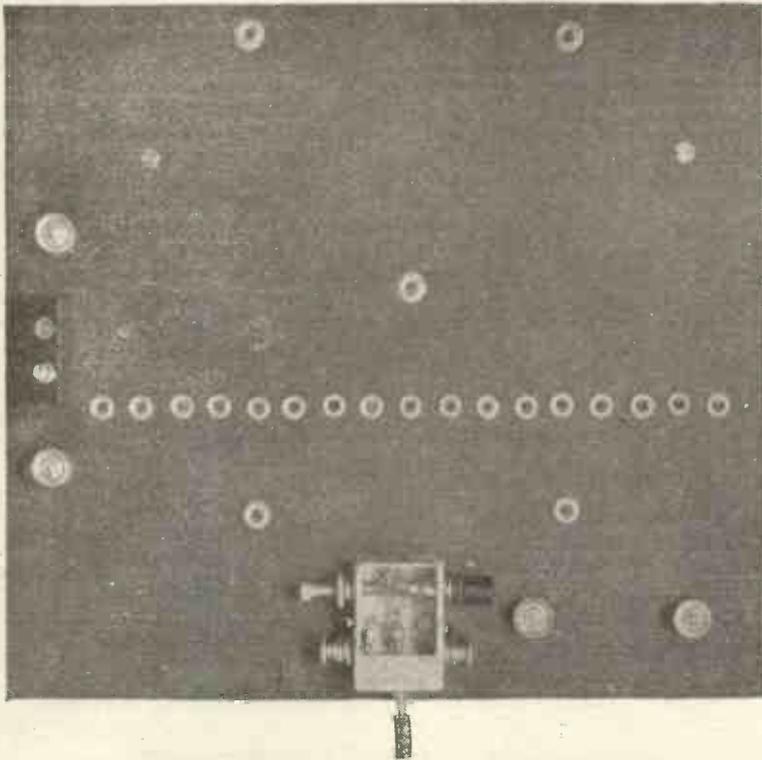Advertisement of The Marconiphone Company, Ltd., Marconi House, Strand, W.C.2.



A plan view of the panel showing the lay-out.

these are connected to tappings made upon the sixty-five turn coil; reading from the left the first eleven sockets have one turn between them, the eleventh and twelfth have five turns between them, and the twelfth, thirteenth, fourteenth, fifteenth, sixteenth and seventeenth have each ten turns between them.

The Smaller Coil

The two sockets which may be seen below the seventeenth just referred to represent as it were the connecting links between the coil and the remainder of the circuit, the number of turns of the coil in use being connected to these two sockets by means of Clix plugs and flexible wire.

The three sockets situated above the line of seventeen introduce or cut out the thirty-five turns coil, the socket in the centre of the panel being common to both conditions. With this socket connected externally by means of Clix plugs and flexible wire to the left hand socket of the three under discussion, the thirty-five turns coil is not in circuit, whilst with the connection taken to the right-hand socket the thirty-five turns are in series with the sixty-five turns coil, the whole being tuned by varying the number of turns of the larger coil, the minimum number in the whole circuit being thirty-six (35

turns plus 1 of the 65 turns), and the maximum being one hundred (35 plus 65).

Materials and Components

In accordance with the usual practice of this journal, the components and materials embodied in this receiver are given below, together with the names of the manufacturers concerned.

- One ebonite panel, measuring 9 in. by 10 in. by $\frac{1}{4}$ in.
- Four brass terminals.
- One coil mount (McMichael).
- One crystal detector (Belling-Lee).
- Twenty-eight Clix with lock-nuts.
- Two Clix insulators (blue).
- Two Clix insulators (red).
- Two Clix insulators (one white, one yellow).
- Five Clix bushes (one blue, one red, one white, two yellow) (Autoveyors, Ltd.).
- One pound No. 16 d.c.c. copper wire (Burne-Jones).
- One pound No. 20 d.c.c. copper wire (Burne-Jones).
- Quantity No. 16 tinned copper connecting wire.
- Two strips of ebonite, 8 in. by 3 in. by $\frac{1}{4}$ in.
- Two wood blocks, 3 in. by 2 in. by 1 in.
- Two pieces of ebonite, 3 in. by 2 in. by $\frac{1}{4}$ in.
- Twelve $\frac{3}{4}$ in. wood screws.
- Three pieces of rubber-covered flex, each 6 in. long.
- Containing box to take panel 9 in. by 10 in. by $\frac{1}{4}$ in., and not less than 6 in. deep.

Constructing the Former

The former upon which the sixty-five turns coil is wound is rectangular in shape, being made up from the two ebonite strips, 8 in. by 3 in. by $\frac{1}{4}$ in., separated by the two wood blocks, 3 in. by 2 in. by 1 in.

First drill a 3-16 in. hole in each corner of the two ebonite strips as shown in the illustration giving constructional details of the former. Now set up on its 1-in. by 3-in. edge one of the wood blocks (3 in. by 2 in. by 1 in.) and along its top surface rest one end of the ebonite strip with its 3-in. edge flush with the 3-in. edge of the block. By means of a small bradawl make, through the drill holes in the ebonite, two small holes in the wood to act as guides for the screws, and then secure the ebonite to the block by means of two $\frac{3}{4}$ -in. wood screws. With this operation completed, the same procedure is adopted with the other end of the same ebonite strip and the other block, the final shape being an inverted letter U but with right-angle corners. At this stage the former is laid with the strip of ebonite just secured, acting as its base, or in other words the former is turned over to make the letter U the right way up, the top of the arms being formed by the 3-in. by 1-in. edges of the two wood blocks. Along the tops of these two edges is now laid the remaining ebonite strip (8 in.

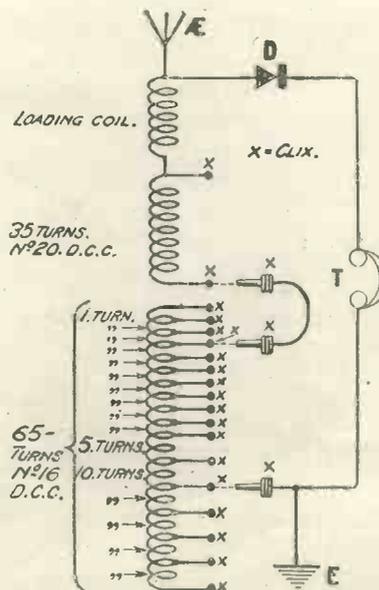


Fig. 2.—Shows how the coils are tapped.

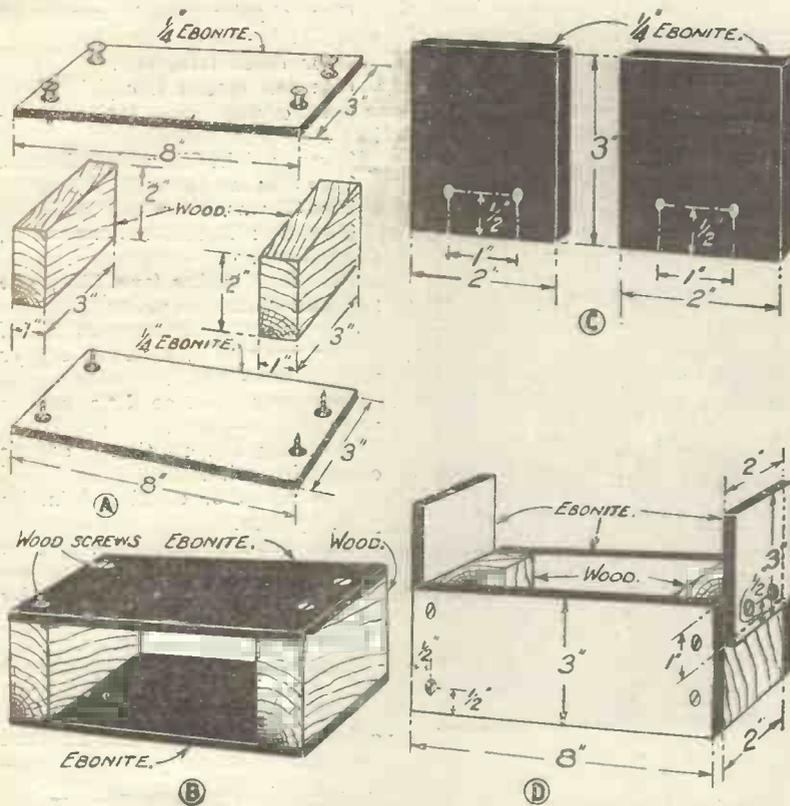


Fig. 3.—Constructional details of the former.



by 3 in. by $\frac{1}{4}$ in.), with the 3-in. edges of the ebonite flush with the 3-in. edges of the wood blocks, when the ebonite is secured to the wood as before, the former should have the appearance of the illustration B in Fig. 3.

The next operation in constructing the former is to secure the two ebonite pieces (2 in. by 3 in. by $\frac{1}{4}$ in.) to the outside faces of the wood blocks, as illustrated in Fig. 3, D, wherein all dimensions are given.

In making this former the ebonite used may be any old scrap that may be lying about, such as an old panel, but it must be remembered that the edges whereon the wire will rest must be perfectly straight, meaning that there must not be the remains of an old drill hole or saw cut or other similar disfigurement.

Winding the Inductance

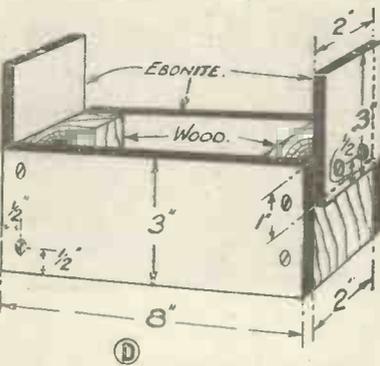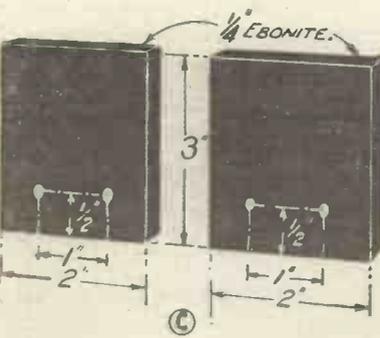The winding of the sixty-five turns coil is first carried out and is made upon the former, consisting of the two wood blocks and the two ebonite strips. First drill in one strip of ebonite, $\frac{1}{4}$ in. from the edge and $\frac{1}{4}$ in. from the block, a 1-16 in. hole through which pass the No. 16 d.c.c. wire; bend back the coil wire so that the winding may begin at the same point



wire as No. 16 d.c.c. is to seek assistance in rotating the coil while the constructor himself rotates the former, taking up the slack as paid out by the assistant. In this manner sixty-five turns are wound tightly and closely together to prevent slipping, and finally secured by making another drill hole at the other end of the former, threading the wire through as before and giving the end a sharp bend close up to the ebonite.


The winding of the thirty-five turns coil is now commenced by drilling a 1-16 in. hole, $\frac{1}{4}$ in. from the edge of one of the side ebonite pieces (2 in. by 3 in. by $\frac{1}{4}$ in.), and $\frac{1}{4}$ in. above the edge of the wood block.

Securing the Winding

Thread the end of the No. 20 d.c.c. wire through this hole, giving it about three turns round the ebonite between the hole and the near edge, and commence the winding by stretching the wire from this point of security to the opposite side of the other ebonite piece (diagonally) round the 2-in. edge of this support back to the first support, but on the opposite side so as to form an X. A glance at the photographs indicates exactly what is meant. In this manner thirty-five complete turns are wound and the end secured in precisely the same way as was done with the beginning of the coil, leaving about six spare inches of wire for connecting purposes. No shellac or other material should be used upon these coils.

Method of Winding

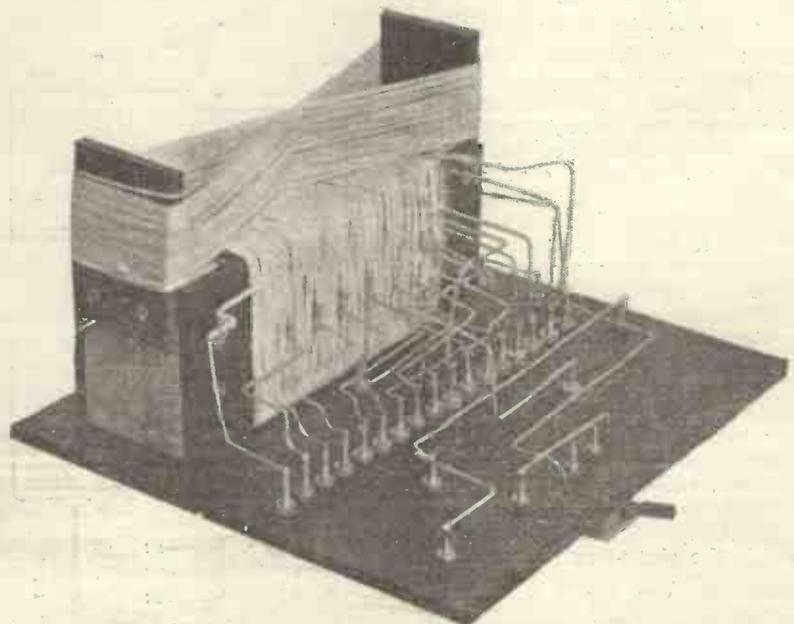The best method to adopt in winding a coil with so stiff a



The tappings are taken to Clix sockets.

Dull Emitters Repaired! Quick 10/6!

Good News! D.E.s repaired for 10/6. With 2 volt .25 amp. filaments. As good as new. Prompt service.

Can't repair "WECO" type or kind having electrodes brought out at opposite ends of tube (i.e., low capacity type). We return your valve with same characteristics as new.

RADIONS Ltd., BOLLINGTON, MACCLESFIELD. Near

New Radion Cool Valves, 18/6

- C1. Fil. 2 volts .25 amp. For general purposes.
- C2. Fil. 2 volts .35 amp. For L.F.
- C. Fil. 3 volts .06 amp. 21/- each. Anode 20-30, and amplification ab ut 9 in each case.

ULTRA

REGISTERED TRADE MARK

NEW IMPROVED MODEL



"Nothing to touch it"

ASK YOUR DEALER FOR IT

Should you have any difficulty in obtaining same, write direct to
Messrs. EDWARD E. ROSEN & CO.,
158/160, City Road, London, E.C.
with the name of your Dealer.

27/6

THE GRID LEAK IN REGENERATIVE CIRCUITS.

The peculiar effect of a grid leak having the wrong value is an experience which has to be tried to be fully understood. "Floppiness" and "Fluffiness" in circuits where Regeneration is employed are caused purely by a leak of the wrong value.

Ability to adjust grid leak resistance to just the correct proportion for the full employment of regeneration is only possible with a **VARIABLE GRID LEAK**. By working the detector valve on the correct portion of the curve for perfect rectification—**AND HERE A VARIABLE GRID LEAK IS INDISPENSABLE**—the detector valve may be sufficiently controlled to give maximum signals without any possibility of the rectifier tripping the set into self-oscillation. **CHOOSE ALWAYS A WATMEL. IT GIVES DELICATE CONTROL. BUT BE SURE YOU FIT A**

Watmel

Watmel

All goods of our manufacture bear this mark. It is your only guarantee.

are now fitted with a spring contact on the control ensuring good and permanent electrical connection.

IMPORTANT NOTICE to intending purchasers



Patent 206098

- 5 to .5 Megohms . . . 2/6
- 50,000 to 100,000 Ohms. 3/3
- Other Resistances to suit any circuit.

Send P.C. for Descriptive Folder. SEE THE TRADE MARK.

Watmel

ON EVERY GRID LEAK, BEWARE OF IMITATIONS.

The Watmel Wireless Co. wish to notify the trade and public that their Variable Grid Leak Patent Application No. 206098 was contested in the Comptroller's Court and on Appeal; in both instances the Patent Grant was upheld and costs awarded.

It is the aim of this Company to protect traders', customers', and also its own interests by securing Patent protection for the novelties in its specialities, as it is these novelties, invented by experts and exhaustively tested, which are the Hall Mark of all Watmel Products.

THE WATMEL WIRELESS CO.

332a, Goswell Road, London, E.C.1.


Telephone

CLERKENWELL 7990.

Silvertown


WIRELESS ACCESSORIES

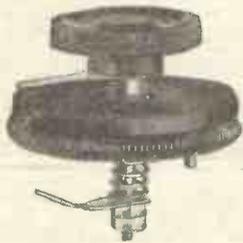Quality guaranteed by over 50 years' electrical manufacturing experience



FILAMENT RHEOSTATS.

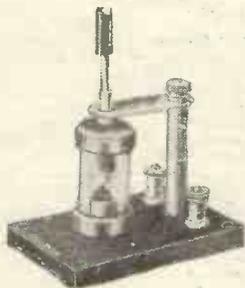With finished and lacquered brass bush for panel mounting. Resistance wire wound on insulating rod, thereby giving perfectly smooth adjustment. Each supplied with diagram giving drilling dimensions. 3/6 each.




CRYSTAL HOLDERS.

Mounted on ebonite base, 3 in. by 2 in., with glass to protect crystals from dust. 4/- each.



EBONITE CONDENSER DIALS AND KNOBS.

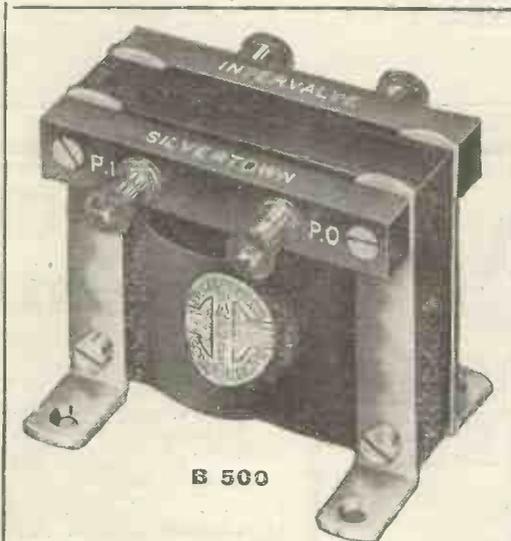In one piece, graduated in white 0-180 deg., highly finished, complete with fixing screw, dial approximately 3 in. diameter. Complete 1/3 each. Dials only 10d. each.



B 500

Price **21/-** each.

Guaranteed for 12 months.

This transformer has been adopted by leading manufacturers of Wireless Receiving Sets and discriminating amateurs in all parts of the world.

High amplification without distortion and complete freedom from internal noises.


Correct design, high-class finish.

Excellent results have been obtained on tests carried out by the National Physical Laboratory. Copy of the curve can be had on application.




VARIABLE CONDENSERS.

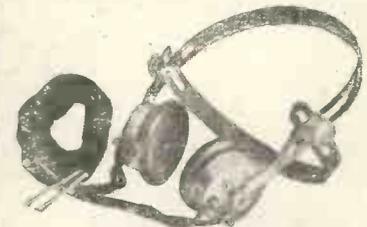(For panel mounting.) Strongly constructed. Moving vanes are shaped to give low minimum capacity. Fitted with a stop to allow of a movement of 180 deg. only. From 5/3 each.



TELEPHONE HEADPIECES.

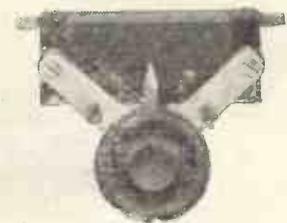The "Stalloy" diaphragms are matched so as to secure a balance of tone and quality. Resistance from 120 to 12,000 ohms. Price 4,000 ohms) 25/- each.



POTENTIOMETERS.
(For panel mounting.)

On rectangular ebonite former, complete with knob and pointer. Former mounted on cast brass frame. Resistance approximately 400 ohms. 7/6 each.

Makers : **THE SILVERTOWN COMPANY,**

106, CANNON ST., LONDON, E.C.4.

BELFAST : 75, Ann Street,
 BIRMINGHAM : 15, Martineau Street.
 BRISTOL : 4, Victoria Street.
 CARDIFF : Pier Head Chambers, Bute Docks.
 DUBLIN : 15, St. Andrew Street.
 GLASGOW : 15, Royal Exchange Square.
 LEEDS : 1, New York Road.



Works: Silvertown, London, E.16.

LIVERPOOL : 54, Castle Street.
 LONDON : 100 and 102, Cannon Street.
 MANCHESTER : 16, John Dalton Street.
 NEWCASTLE-ON-TYNE : 59, Westgate Road.
 PORTSMOUTH : 49, High Street.
 SHEFFIELD : 88-90, Queen Street.

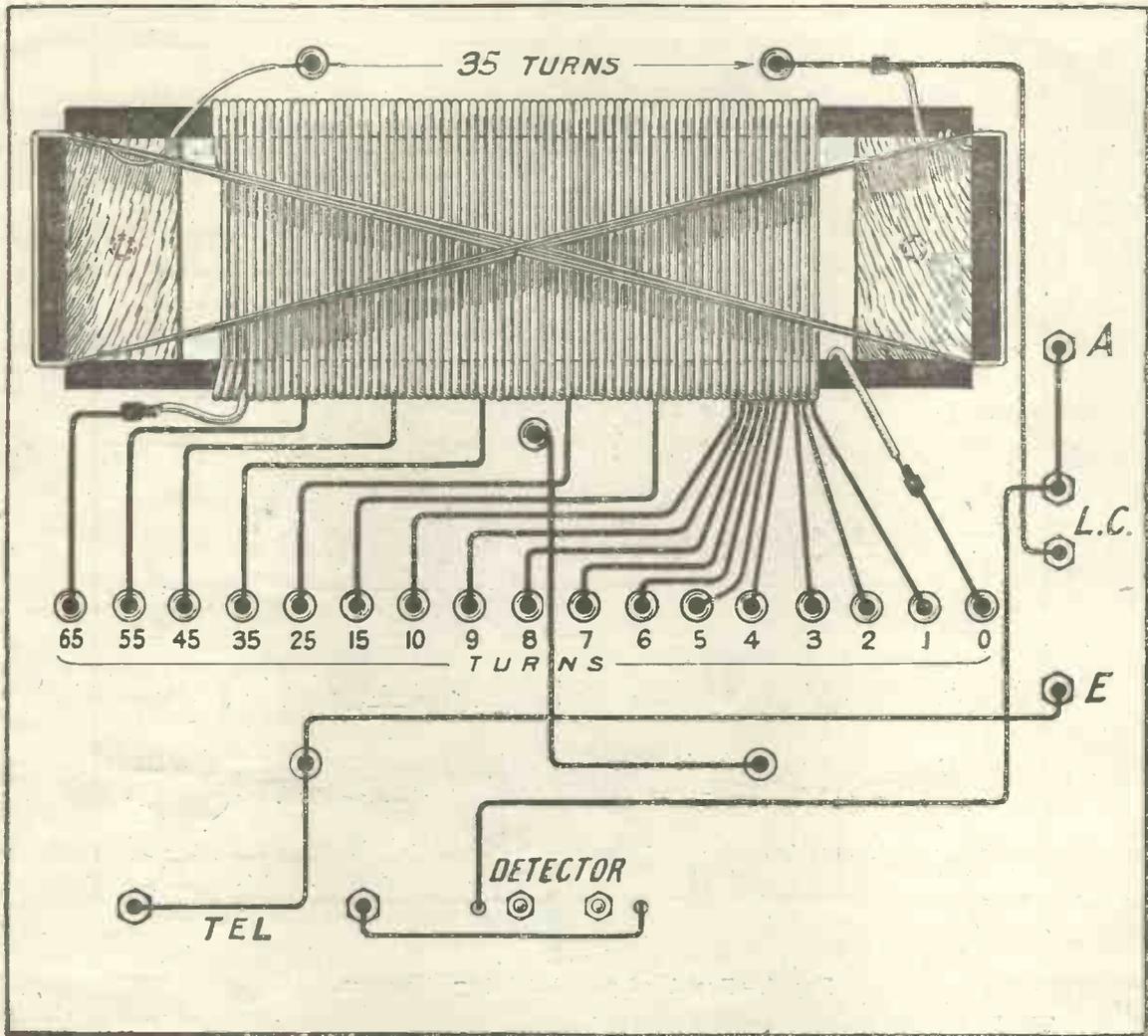


Fig. 5.—Back of panel wiring diagram.

and now, working from the left to the right, scrape the insulation away for about $\frac{1}{4}$ in. from the tenth, twentieth, thirtieth, fortieth, fiftieth, fifty-fifth, fifty-sixth, fifty-seventh, fifty-eighth, fifty-ninth, sixtieth, sixty-first, sixty-second, sixty-third, and sixty-fourth turns, and tin with a soldering iron. Again working from the left, first connect the end of the coil to the first Clix, the tenth turn to the second Clix, the twentieth turn to the third Clix, and so on until the fiftieth turn is connected to the sixth Clix. The fifty-fifth turn is now connected to the seventh Clix, and each succeeding turn is now connected to each succeeding Clix until the end of the coil is connected to the seventeenth Clix. Wiring the coil in this manner gives easy accessibility to all its connections, and once done makes easier the accessibility to other components.

Operating the Receiver


The operation of this receiver is perfectly straightforward and calls for no especial skill. Tuning is effected by varying the number of turns in the aerial circuit, either in "tens" or "ones" until the desired signals are heard, when further tuning may be effected by varying the inductance by plugging the 35 turns coil in circuit and varying the plugs in the line of seventeen sockets. With large aerials the tuning of these stations may be effected by using the 65 turns alone. On a given station the number of turns required to give the best signals will show whether or not that station can be received on the 65 coil alone.

Crystal Set (S. G. Rattee) Test Report

The set was tested in the evening about eight miles S.W. of 2LO on an average aerial 30 ft. high and 60 ft. long, un-screened, and using really efficient earth, signals from 2LO were of very good strength in the 'phones. A Baby Sterling loud-speaker was connected in their place, and the music was audible at 8 ft. from the L.S. Using only the thicker wire coil, tapplings for the best results were taken at the first and the ninth sockets starting from the right. On the same aerial and using a loading coil, Chelmsford came in well, and there was little to choose between the strength of signals from this station and from 2LO. Morse was clearly heard on several settings, and one amateur (no call sign given) was also picked up after 2LO had closed down.

and now, Brussels...

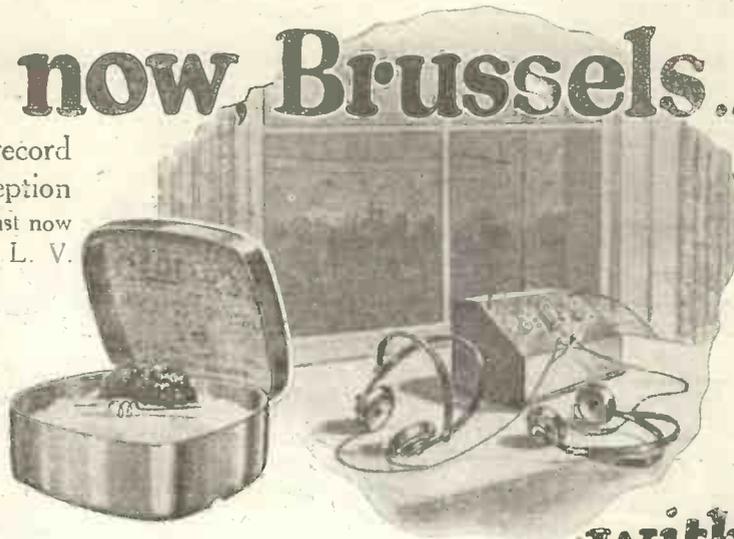To the wonderful record of long-distance reception with Neutron Crystal must now be added that of Mr. L. V. Clark, of Experimental Station 5 B T Chiswick, London, who reports receiving clear telephony from BRUSSELS on a Neutron Crystal, without the aid of Amplifiers.



—with Neutron, the Crystal that is doubling the range of the Crystal Receiver

Sooner or later, you will use Neutron, and then stop searching for better results. You may secure a good crystal by just asking for "a crystal"; but you may also try twenty or thirty first. On the other hand, if you ask for Neutron, in the black-and-yellow tin,

you will inevitably secure optimum results at once—and save the expense of further tests. This was the experience of "W. T. T." Harrietsham, Kent, who writes:—"I have tried crystal after crystal, but I have never had such a good result before as I have to-day

with a Neutron." The reason why you can depend upon Neutron is that each Neutron is carefully tested and selected, and before ever it reaches your crystal-cup it has been proved at maximum efficiency, for loudness, clearness, and complete sensitiveness.



The Concert-Tested and Guaranteed Radio Crystal

Stocked by the Best Radio Dealers. Packed in airtight tin, with silver catswhisker. Insist on Neutron, in the Black and Yellow Tin—**1/6**

Long Distance
Circuit Diagram

FREE

Ask your Dealer for Free Diagram (given to each purchaser of a Neutron, on request), of the circuit used by "5.B.T." in receiving Brussels from Chiswick on a Neutron. We send one direct with sample Neutron if you enclose stamped envelope and **1/6** with Dealer's name.

Sole Distributors:—V. Zeitlin & Sons, 144 Theobalds Road, London, W.C.1. 'Phons Museum: 3795 and 6841.

Produced by:—Neutron Ltd., Sicilian House, Southampton Row, London, W.C.1. 'Phone: Museum 2677.

District Agents:

Scotland: R. F. Miller & Co., 22, York Place, Edinburgh.
 Plymouth: Mumford & Sons, 68, Mutley Plain, Plymouth.
 Birmingham: Cooke & Whitfield Wireless Ltd., St. Paul's Buildings 24, St. Paul's Square, Birmingham.

North-East Yorks: Smith & Jordan, The Arcade, Redcar, Yorks.

Manchester: Garnett's, Islington Grove Works, Salford, Manchester.

Ireland: Pettigrew & Merriman Ltd., Corporation Street, Belfast.

B.T.H. Headphones

ensure perfect reception

because they are supreme in all respects—in sensitiveness, tone, permanence and comfort. The constructional features noted below explain why B.T.H. Headphones are best.

- A The body is of special insulating material, carrying perfectly wound permanent magnets of cobalt steel.
- B The stirrup moves freely within the slider, and takes up and retains its position without any locking device.
- C The special slider obviates the use of screwed parts for adjustment purposes.
- D Spring steel headbands give the "just right" pressure to the ears in order to exclude extraneous noises. The two portions of the headband are held rigidly apart and cannot catch in the hair.
- E A leather covering, threaded over the wide headband gives perfect comfort.
- F The earpieces are designed to fit closely to the ears and to exclude unwanted noises.
- G Six feet of really flexible cord are supplied for connecting to receiver.
- H The nickel plated connector enables two or more pairs of 'phones to be connected in series.



Obtainable from all Electricians & Wireless Dealers

The British Thomson-Houston Co. Ltd.

Works: Coventry.

Offices: Crown House, Aldwych, London, W.C.2

Branches at: Belfast, Birmingham, Bristol, Cardiff, Dublin, Glasgow, Leeds, Liverpool, Middlesborough, Manchester, Newcastle, Swansea, Sheffield

2171

A Proof of Superiority

Ask your dealer to tune his demonstration set down until you can barely hear. Then substitute B.T.H. Headphones and you will be amazed at the clearness with which you can hear every word and note of music.

Regular Programmes from Continental Broadcasting Stations

Telephony except when otherwise stated. Corrected up to November 20th, 1924.

Edited by CAPTAIN L. F. PLUGGE, B.Sc., F.R.Ae.S., F.R.Met.S. Strictly Copyright.

WEEK DAYS.

Ref. No.	G. M. T.	Name of Station.	Call Sign and Wave-length.	Situation.	Nature of Transmission.	Closing Time or Approx. Duration.	Approx. Power used
	a.m.						
1	6.25	Hamburg	— 395 m. . .	Germany . .	Time Signal in C.E.T. . .	5 mins.	700 Watts.
2	6.40	Eiffel Tower	FL 2600 m.	Paris	Weather Forecast . .	5 mins.	5 Kw.
3	6.55	Munster	— 413 m.	Westphalia	Time Signal in C.E.T. . .	5 mins.	1.5 Kw.
4	7.05	Lausanne	HB2 850 m.	Switzerland	Weather Report . .	5 mins.	300 Watts.
5	7.55	Persbureau Vaz Dias	PCFF 2125 m.	Amsterdam	Stocks, Shares and News . .	10 mins.	2 Kw.
8	9.23	Eiffel Tower	FL 2600 m.	Paris . .	Time Signal in G.M.T. (Spark)	3 mins.	—
9	9.55	Persbureau Vaz Dias	PCFF 2125 m.	Amsterdam	Stocks, Shares and News . .	10 mins.	2 Kw.
10	10.00	Eiffel Tower	FL 2600 m. . .	Paris . .	Time Signal in Greenwich Sidereal Time (Spark)	5 mins.	—
156	10.00	Radio Wien . .	— 530 m. . .	Austria . .	Concert	Noon	1 Kw.
11	10.30	Lyons	YN 470 m. . .	Lyons . .	Gramophone Concert . .	30 mins.	500 Watts.
12	10.30	Kbel . .	— 1150 m.	Prague . .	Exchange quotations . .	10 mins.	1 Kw.
13	10.44	Eiffel Tower	FL 2600 m.	Paris . .	Time Signal in G.M.T. (Spark)	3 mins.	—
14	10.55	Eiffel Tower	FL 2600 m. . .	Paris . .	Fish Market Quotations—Cotton Exchange.	10 mins.	5 Kw.
15	10.55	Frankfurt . .	— 467 m.	Frankfurt	Time Signals (spoken) followed by News (in C.E.T.)	5 mins.	1 Kw.
16	11.00	Stuttgart . .	— 443 m.	Wurtemberg	News and Opening Prices . .	10 mins.	1 Kw.
17	11.10	Persbureau Vaz Dias	PCFF 2125 m.	Amsterdam	Stocks and Shares . .	20 mins.	2 Kw.
18	11.14	Eiffel Tower	FL 2600 m. . .	Paris . .	Time Signal in Greenwich Time (Spoken), followed by Weather Forecast.	5 mins.	5 Kw.
20	11.15	Voxhaus . .	— 430 m.	Berlin . .	First News Bulletin and Weather Reports.	5 mins.	700 Watts.
19	11.55	Konigsberg . .	— 460 m.	East Prussia	Time Signal in C.E.T. . .	5 mins.	1 Kw.
21	11.55	Voxhaus . .	— 430 m.	Berlin . .	Time Signal in C.E.T. . .	5 mins.	700 Watts.
22	11.55	Leipzig . .	— 454 m.	Germany . .	Time Signal Relayed from Baven	5 mins.	700 Watts.
23	11.57	Nauen . .	POZ 3100 m.	Berlin . .	Time Signal in G.M.T. (Spark)	8 mins.	—
157	12.00 noon	Zurich . .	— 650 m.	Switzerland	Weather Forecast, Shares and News.	45 mins.	500 Watts.
24	12.00	Persbureau Vaz Dias.	PCFF 2125 m.	Amsterdam	Stocks and Shares . .	8 mins.	2 Kw.
	p.m.						
26	12.15	Geneva . .	HB1 1100 m.	Switzerland	Lecture	12.45 p.m.	300 Watts.
25	12.30	Kbel . .	— 1150 m.	Prague . .	Exchange Quotations . .	10 mins.	1 Kw.
27	12.30	Lausanne	HB2 850 m.	Switzerland	Weather Reports, Time Signal in C.E.T. and News.	15 mins.	300 Watts.
30	12.45	Stockholm . .	— 440 m. . .	Sweden . .	Weather Forecast . .	5 mins.	500 Watts.
31	12.45	Persbureau Vaz Dias.	PCFF 2125 m.	Amsterdam	Stocks and Shares . .	10 mins.	2 Kw.
32	1.00	Radio-Paris . .	SFR 1780 m.	Clichy . .	Concert followed by News . .	2 p.m.	8 Kw.
33	1.00	Haeren . .	BAV 1100 m.	Brussels . .	Weather Forecast in French and English.	8 mins.	150 Watts.
34	1.00	Munich . .	— 485 m.	Bavaria . .	News and Weather Report . .	10 mins.	1 Kw.
36	1.00	Stockholm . .	— 440 m.	Sweden . .	Time Signal	3 mins.	500 Watts.
37	1.15	Voxhaus . .	— 430 m.	Berlin . .	Stock Exchange News . .	5 mins.	700 Watts.
35	1.15	Komarow . .	— 1800 m.	Czecho-Slovakia.	Stock Exchange and Late News	10 mins.	1 Kw.
40	2.30	Munster . .	— 410 m.	Westphalia	Stocks, Shares and News . .	10 mins.	1.5 Kw.
38	2.40	Persbureau Vaz Dias.	PCFF 2125 m.	Amsterdam	Stocks, Shares and News . .	10 mins.	2 Kw.
39	2.45	Eiffel Tower	FL 2600 m. . .	Paris . .	Exchange Opening Prices. (Sat. excepted).	8 mins.	5 Kw.
158	3.00	Zurich . .	— 650 m. . .	Switzerland	Hotel Concert, Relayed . .	5 p.m.	500 Kw.
159	3.10	Radio-Wien . .	— 530 m.	Vienna . .	Concert	5 p.m.	1 Kw.


Ref. No.	G. M. T.	Name of Station.	Call Sign and Wave-length.	Situation.	Nature of Transmission.	Closing Time or Approx. Duration.	Approx. Power used.
----------	----------	------------------	----------------------------	------------	-------------------------	-----------------------------------	---------------------

WEEK DAYS (Contd.)

42	p.m. 3.30	Frankfurt	— 467 m.	Germany	Light Orchestra	5 p.m.	1 Kw.
43	3.30	Konigsberg	— 460 m.	East Prussia	Light Orchestra	1 hour.	1 Kw.
44	3.30	Voxhaus	— 430 m.	Berlin	Concert, followed by News	5.30 p.m.	700 Watts.
45	3.30	Munich	— 485 m.	Bavaria	Concert	4.30 p.m.	1 Kw.
46	3.30	Leipzig	— 454 m.	Germany	Concert	5 p.m.	700 Watts.
47	3.35	Eiffel Tower	FL 2600 m.	Paris	Exchange Quotations (Sat. excepted).	5 mins.	5 Kw.
48	3.55	Persbureau Vaz Dias.	PCFF 2125 m.	Amsterdam	Stock Exchange and News	10 mins.	2 Kw.
49	4.00	Kbel	— 1150 m.	Prague	Shares and News	10 mins.	1 Kw.
160	4.00	Breslau	— 418 m.	Silesia	Light Orchestra	5 p.m.	1.5 Kw.
51	4.30	Radio-Paris	SFR 1780 m.	Clichy	Concert preceded and followed by News.	5.45 p.m.	8 Kw.
52	4.30	Eiffel Tower	FL 2600 m.	Paris	Exchange Closing Prices (except Saturday).	8 mins.	5 Kw.
53	4.45	Stuttgart	— 443 m.	Wurtemberg	Concert followed by Weather Report (Saturdays excepted).	6 p.m.	1 Kw.
54	5.00	Radio-Belg.	SBR 265 m.	Brussels	Concert followed by News	6 p.m.	2.5 Kw.
177	5.00	Barcelona	EA J 1. 325 m.	Spain	Tests	7.00 p.m.	650 Watts.
161	5.30	Munich	— 485 m.	Bavaria	Light Orchestra	6.30 p.m.	1 Kw.
55	5.55	Lausanne	HB2 850 m.	Switzerland	Weather Report	5 mins.	300 Watts.
162	6.00	Eiffel Tower	FL 2600 m.	Paris	Concert followed by News Bulletin	6.55 p.m.	5 Kw.
163	6.00	Leipzig	— 454 m.	Germany	Lecture (Saturdays excepted)	6.30 p.m.	700 Watts.
57	6.30	Kbel	— 1150 m.	Prague	Concert and News	7.30 p.m.	1 Kw.
178	6.30	Seville	EA J5 350 m.	Spain	Concert	7.45 p.m.	1 Kw.
58	7.00	Eiffel Tower	FL 2600 m.	Paris	General Weather Forecast	8 mins.	5 Kw.
60	7.00	Radio-Wien	— 530 m.	Vienna	Concert	9 p.m.	1 Kw.
61	7.00	Konigsberg	— 460 m.	East Prussia	Concert and News	8.30 p.m.	1 Kw.
62	7.00	Hamburg	— 395 m.	Germany	Concert and Late News	9.50 p.m.	700 Watts.
63	7.00	Stuttgart	— 443 m.	Wurtemberg	Concert and News	9.30 p.m.	1 Kw.
66	7.00	Lausanne	HB2 850 m.	Switzerland	Concert (Monday excepted)	9.30 p.m.	300 Watts.
179	7.00	Radio-Iberica	RI 392 m.	Madrid, Spain	Concert and News	8.00 p.m.	3 Kw.
64	7.15	Zurich	— 650 m.	Switzerland	Concert followed by Late News	9.15 p.m.	500 Watts.
65	7.15	Leipzig	— 454 m.	Leipzig	Concert and News	8.35 p.m.	700 Watts.
67	7.30	Frankfurt	— 467 m.	Frankfurt	Concert and News	10 p.m.	1 Kw.
69	7.30	Breslau	— 418 m.	Silesia	Concert	9 p.m.	1.5 Kw.
59	7.30	Munster	— 410 m.	Westphalia	Concert followed by News	9 p.m.	1.5 Kw.
72	7.30	Voxhaus	— 430 & 505	Berlin	Concert followed by News and Weather Report.	9.15 p.m.	0.7 and 1.5 Kw.
73	7.30	Munich	— 485 m.	Bavaria	Concert and News	8.40 p.m.	1 Kw.
164	8.00	Radiofonica Italiana.	— 422 m.	Rome	Concert followed by News	9.30 p.m.	4 Kw.
74	8.15	Radio-Belg.	SBR 265 m.	Brussels	Concert preceded and followed by News.	10.10 p.m.	2.5 Kw.
75	8.30	Ecole. Sup. des P. & Tg.	FPTT 450 m.	Paris	Concert, sometimes preceded by Lecture, usually outside broadcast.	9 p.m.	500 Watts.
76	8.30	Radio-Paris	SFR 1780 m.	Clichy	Detailed News Bulletin	9 p.m.	8 Kw.
77	9.00	Radio-Paris	SFR 1780 m.	Clichy	Time Signal followed by Concert	9.50 p.m.	8 Kw.
78	9.30	Radio-Iberica	— 392 m.	Madrid	Concert, Advertisements	Midnight	3 Kw.
79	10.00	Eiffel Tower	FL 2600 m.	Paris	Time Signal in Greenwich Sidereal Time (Spark).	5 mins.	—
80	10.10	Eiffel Tower	FL 2600 m.	Paris	General Weather Forecast	5 mins.	5 Kw.
81	10.44	Eiffel Tower	FL 2600 m.	Paris	Time Signal in G.M.T. (Spark)	3 mins.	—
82	11.57	Nauen	POZ 3100 m.	Berlin	Time Signal in G.M.T. (Spark)	3 mins.	—

SUNDAYS

83	a.m. 7.00	Frankfurt	— 467 m.	Germany	Morning Prayer	1 hour	1 Kw.
84	7.55	Hamburg	— 395 m.	Germany	Time Signal	5 min.	700 Watts.
85	8.00	Leipzig	— 454 m.	Germany	Morning Prayer	1 hour	700 Watts.
165	8.00	Konigsberg	— 460 m.	E. Prussia	Morning Prayer	8.45 a.m.	1 Kw.
86	9.00	Komarow	— 1800 m.	Czecho-Slovakia.	Sacred Concert	1 hour	1 Kw.
87	9.23	Eiffel Tower	FL 2600 m.	Paris	Time Signal in Greenwich Mean Time (Spark).	3 mins.	—
166	9.30	Munich	— 485 m.	Bavaria	Sacred Concert	10.30 a.m.	1 Kw.
88	9.40	Konigswusterhausen.	LP 680 m.	—	Concert	1 hour	3 Kw.
89	10.00	Eiffel Tower	FL 2600 m.	Paris	Time Signal in Greenwich Sidereal Time (Spark).	5 mins.	—
90	10.00	Kbel	— 1150 m.	Prague	Classical Music	1 hour	1 Kw.

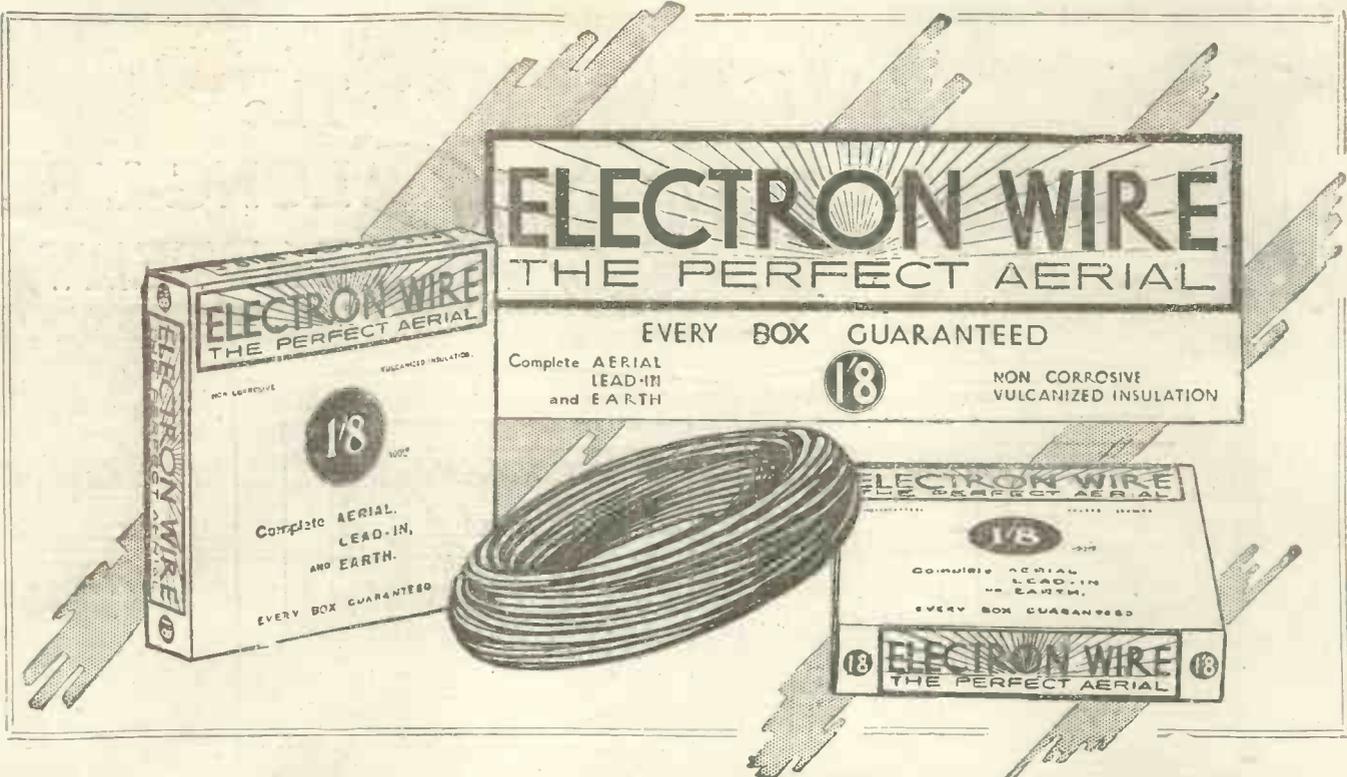

WITHOUT ELECTRON WIRE YOU CANNOT KNOW REAL AERIAL EFFICIENCY

Wireless enthusiasts must be on their guard. There are dealers all over the country who are trying to foist upon the public colourable imitations of the famous 'ELECTRON WIRE.'

IF 'ELECTRON WIRE' IS THE WIRE YOU WANT BE CAREFUL THAT YOU GET IT.

It brings envied results. Multitudes of experts as well as enthusiasts all over the world are using 'ELECTRON WIRE.'

Every day we get shoals of letters telling us of the remarkable reception amateurs are getting with 'ELECTRON WIRE.'

If ever you find a better aerial get it. A good reception is worth any price you pay.

BUT AVOID DECEPTION. LOOK AT THE NAME AND THE SPECIAL BOX. If it is not our distinctive box, refuse it and save disappointment.

Some dealers may even tell you that we cannot get supplies of boxes for 'Electron Wire,' and may try to sell you another wire coiled to look like 'ELECTRON WIRE.' Refuse it.

Ask for and insist upon 'ELECTRON WIRE' in our distinctive white box ONLY printed in blue. Refuse any wire which may look like 'ELECTRON WIRE,' and may even be boxed under a similar name to 'ELECTRON WIRE.'

TAKE NOTICE OF THIS WARNING!

Buy "Electron Wire" in our distinctive box only, plainly printed in blue on every side with  and the price 1/8. Refuse all others.

Try It—then you will know why it is so popular. Ask your dealer for ELECTRON WIRE. But you must agree to return it if it does not "prove up" to every claim made for it. If your dealer does not sell ELECTRON WIRE yet, he can get it for you, or we will send it direct to you upon receipt of P.O. or cheque.

The **CHEAPEST AERIAL** **1/8**
and the Best in the World. POSTAGE 6d.

Also laid double for extending Phones, Loud Speaker, etc.

Two 150 feet lengths twisted. 300 ft.

Two 250 feet lengths twisted. 500 ft.

Two 500 feet lengths twisted. 1,000 ft.

5/-

8/-

15/-

Carriage Paid.

NEW LONDON ELECTRON WORKS, Ltd.

(Members of the B.B.C.)

Telephones: East 1821. 99, REGENT'S DOCK, LONDON, E.14. Tel. "Stannum, London."

'BUSES Nos. 15, 23, 40. 1d. from Aldgate.

(Near East Stepney Station, L.N.E.R.)

Exide

The LONG-LIFE BATTERY

The Exide Battery

How to choose a suitable Exide Wireless Battery

1.—Number of cells required.
 For up to 2 volts use 1 cell.
 " between 2 & 4 volts use 2 cells
 " 4 & 6 " " 3 "

2.—Size of cell required.
 Ascertain the current required per valve from the table on pages 18 and 19.
 Add all these values together.
 Find the total current thus obtained on the centre column of the chart on this page.
 Read off on either the right hand or left hand column the number of hours for which this current can be maintained continuously using the size of cell given in the outer column.

3.—Description of Battery.
 The battery is described by using the number of cells as a prefix followed by the size of cell, e.g., 1 CZ4, 3 HZ2.
Example.—3 valves, 5 volts, 65 amperes.
 (1) Number of cells required = 3
 (2) Size of cell required—
 Total current = 3 x 65 = 195 amperes.
 From chart—95 amperes will be given continuously for 21 hours by CZ4 cells, or for 47 hours by CX6 cells.
 (3) Description of battery—
 3 CZ4 or 3 CX6.
 For further details of these cells see pages 6 and 7.

The Chloride Electrical Storage

The Exide Battery

SIZE OF CELL	HOURS CONTINUOUS	AMPERES	SIZE OF CELL
CX8	15	15	CX8
CX7	20	20	CX7
CX6	25	25	CX6
CX5	30	30	CX5
CX4	35	35	CX4
CZ6	40	40	CZ6
CZ5	45	45	CZ5
CZ4	50	50	CZ4
CZ3	55	55	CZ3
CZ2	60	60	CZ2
C03	65	65	C03
C02	70	70	C02
C01	75	75	C01
CYP	80	80	CYP

How to Determine
 It is important to...
 If the resistance is too high a valve will be...
 useful...

More than a mere Catalogue

The latest Exide Catalogue "W" of batteries for wireless work is something new in battery catalogues.

Whilst every type of battery is described and fullest details of actual capacities, sizes and prices quoted, this Catalogue gives also extensive details of the characteristics of every type of valve, list of the wave-lengths of British and Continental stations, notes on the care of batteries, and much other interesting information useful to the enthusiast.


Exide Batteries can be obtained from your usual dealer, or the nearest Exide Service Station.

450 Service Agents.



Look for this Sign.

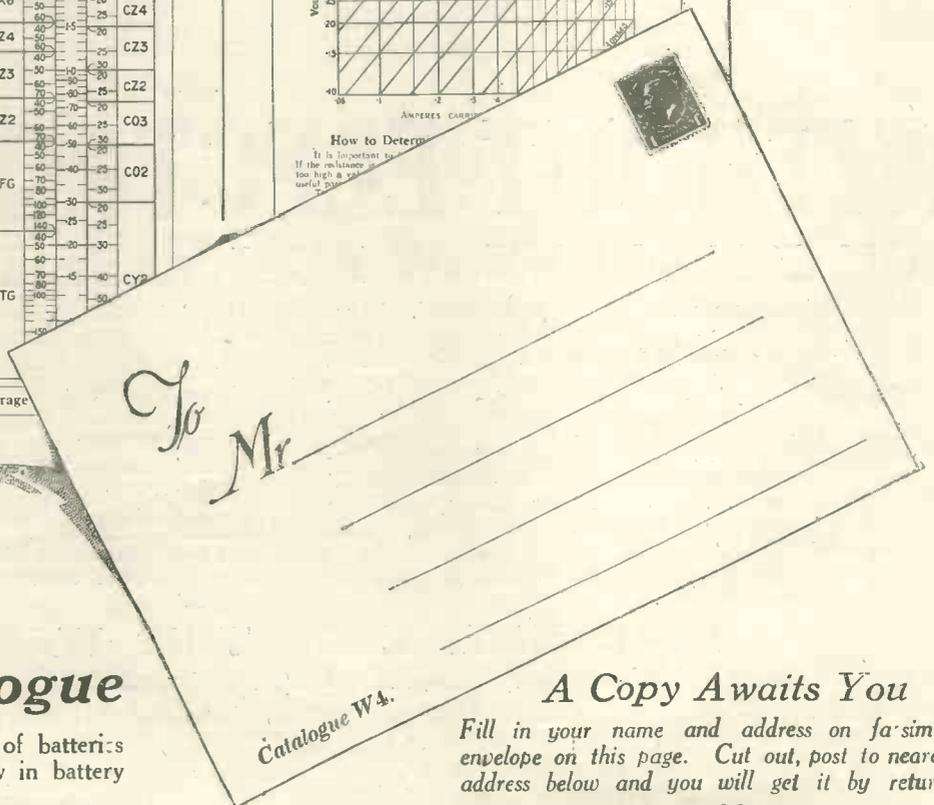In replying to Advertisers, please use Order Form enclosed.



A Copy Awaits You

Fill in your name and address on facsimile envelope on this page. Cut out, post to nearest address below and you will get it by return.

Manufactured by—

THE Chloride ELECTRICAL STORAGE COMPANY LIMITED.

at CLIFTON JUNCTION, Nr. MANCHESTER.

Showrooms and Depots
LONDON: 219-229, Shaftesbury Avenue, W.C.2.
BRISTOL: 22, Victoria Street.

BIRMINGHAM: 58, Dale End.
MANCHESTER: 1, Bridge Street

Ref. No.	G. M. T.	Name of Station.	Call Sign and Wave-length.	Situation.	Nature of Transmission.	Closing Time or Approx. Duration.	Approx. Power used.
----------	----------	------------------	----------------------------	------------	-------------------------	-----------------------------------	---------------------

SUNDAYS (contd.)

91	a.m.	Breslau	— 418 m.	Silesia	Concert	1 hour	1.5 Kw.
92	10.00	Radio-Wien	— 530 m.	Vienna	Concert	2 hours	1 Kw.
93	10.30	Lyons	YN 470 m.	Lyons	Gramophone Records .. .	11 a.m.	500 Watts.
94	10.30	Stuttgart	— 443 m.	Wurtemberg	Classical Concert .. .	1 hour	1 Kw.
95	10.44	Eiffel Tower	FL 2600 m.	Paris	Time Signal in G.M.T. (Spark)	3 mins.	—
96	10.50	Konigswusterhausen.	LP 2450 m.	Berlin	Concert	11.45 a.m.	6 Kw.
97	10.55	Eiffel Tower	FL 2600 m.	Paris	Fish Market Quotations, followed by Weather Report.	12 mins.	5 Kw.
98	11.00	Stockholm	— 440 m.	Sweden	Divine Service .. .	12.15	500 Watts.
101	11.57 p.m.	Nauen	POZ 3100 m.	Berlin	Time Signal in G.M.T. (Spark)	3 mins.	—
102	1.00	Radio-Paris	SFR 1780 m.	Clichy	Concert, followed by News .. .	2.00 p.m.	8 Kw.
103	2.40	Ned. Radio Industrie.	PCGG 1070 m.	The Hague	Concert, followed by Announcements in English.	5.40 p.m.	1.3 Kw.
104	3.00	Breslau	— 418 m.	Silesia	Children's Stories .. .	3.45 p.m.	1.5 Kw.
105	3.00	Stuttgart	— 443 m.	Wurtemberg	Light Orchestra .. .	5.00 p.m.	1 Kw.
107	3.00	Frankfurt	— 410 m.	Germany	1 Kw.
167	3.00	Zurich	— 650 m.	Switzerland	Local Hotel Concert .. .	5.00 p.m.	500 Watts.
106	3.10	Radio-Wien	— 530 m.	Vienna	5.00 p.m.	1 Kw.
168	3.30	Konigsberg	— 460 m.	E. Prussia	Light Orchestra .. .	4.30 p.m.	1 Kw.
169	3.30	Voxhaus	430 & 505 m.	Berlin	Light Orchestra .. .	5.15 p.m.	1 Kw.
170	3.30	Leipzig	— 454 m.	Germany	Light Orchestra .. .	5.00 p.m.	700 Watts.
108	3.30	Munich	— 485 m.	Bavaria	Concert	5.00 p.m.	1 Kw.
171	4.00	Frankfurt	— 410 m.	Germany	Children's Corner .. .	5.00 p.m.	1 Kw.
172	4.45	Stuttgart	— 443 m.	Wurtemberg	Concert	6.00 p.m.	1 Kw.
110	4.45	Radio-Paris	SFR 1780 m.	Clichy	Concert, followed by News .. .	1 hour	8 Kw.
111	5.00	Radio-Belg.	SBR 265 m.	Brussels	Concert	1 hour	2.5 Kw.
185	5.09	Barcelona	EAJ 1 325 m.	Spain	Tests	7.00 p.m.	650 Watts.
112	6.00	Eiffel Tower	FL 2600 m.	Paris	Concert, followed by News .. .	1 hour	5 Kw.
178	6.30	Seville	EAJ 5 350 m.	Spain	Concert	7.45 p.m.	1 Kw.
114	7.00	Radio-Wien	— 530 m.	Vienna	Concert	8.30 p.m.	1 Kw.
115	7.00	Stockholm	— 440 m.	Sweden	Concert	10.00 p.m.	500 Watts.
118	7.00	Konigsberg	— 460 m.	E. Prussia	Concert	9.00 p.m.	1 Kw.
119	7.00	Hamburg	— 395 m.	Germany	Concert	9.00 p.m.	700 Watts.
120	7.00	Eiffel Tower	FL 2600 m.	Paris	General Weather Forecast .. .	8 mins.	5 Kw.
124	7.00	Breslau	— 418 m.	Silesia	Light Orchestra .. .	9.00 p.m.	1.5 Kw.
125	7.00	Stuttgart	— 443 m.	Wurtemberg	Concert	9.15 p.m.	1 Kw.
173	7.00	Frankfurt	— 410 m.	Germany	Entertainment provided by Frankfurter Zeitung.	10.00 p.m.	1 Kw.
121	7.15	Lausanne	HB2 850 m.	Switzerland	Concert	8.30 p.m.	300 Watts.
122	7.15	Zurich	— 650 m.	Switzerland	Concert	9.15 p.m.	500 Watts.
123	7.15	Leipzig	— 454 m.	Germany	Symphony Concert .. .	8.40 p.m.	700 Watts.
116	7.00	Munster	— 410 m.	Westphalia	Classical Concert .. .	9.00 p.m.	1.5 Kw.
174	7.30	Munich	— 485 m.	Bavaria	Concert	8.30 p.m.	1 Kw.
126	7.40	Ned. Seintoesl. Fabriek.	NSF 1050 m.	Hilversum	Concert	10.10 p.m.	1 Kw.
175	8.00	Radiofonica Italiana.	— 422 m.	Rome	Concert, followed by Late News	9.30 p.m.	4 Kw.
176	8.00	Copenhagen	— 750 m.	Denmark	Concert, followed by News .. .	9.30 p.m.	2 Kw.
127	8.30	Radio-Belg.	SBR 265 m.	Brussels	Concert, followed by News .. .	10.10 p.m.	2.5 Kw.
128	8.30	Radio-Paris	SFR 1780 m.	Clichy	Detailed News Bulletin .. .	9.00 p.m.	8 Kw.
129	8.30	Ecole Sup. des P. et T. Gs.	FPTT 450 m.	Paris	Concert or Lecture. May begin 15 mins. earlier or later.	10.30 to 12 p.m.	500 Watts.
130	9.00	Radio-Paris	SFR 1780 m.	Clichy	Concert, followed by Dance Music.	10.00 p.m.	8 Kw.
131	9.30	Petit Parisien	— 340 m.	Paris	Concert (Items announced in English as well as French.)	11.30 p.m.	400 Watts.
132	9.30	Radio-Iberica	— 392 m.	Spain	Concert	midnight	3 Kw.
133	10.00	Eiffel Tower	FL 2600 m.	Paris	Time Signal in Greenwich Sidereal Time (Spark).	3 mins.	—
134	10.44	Eiffel Tower	FL 2600 m.	Paris	Time Signal in G.M.T. (Spark)	3 mins.	—
135	11.57	Nauen	POZ 3100 m.	Berlin	Time Signal in G.M.T. (Spark)	8 mins.	—

SPECIAL DAYS.

137	p.m.	Lausanne	HB2 850 m.	Switzerland	Mon.	Children's Stories .. .	1 hour	300 Watts.
140	5.15	Zurich	— 650 m.	Switzerland	Mon., Wed., Fri.	Children's Corner .. .	5.50 p.m.	500 Watts.
141	5.15	Zurich	— 650 m.	Switzerland	Thurs., Sat.	Lecture	30 mins.	500 Watts.

Ref. No.	G. M. T.	Name of Station.	Call Sign and Wave-length.	Situation.	Nature of Transmission.	Closing Time or Approx. Duration.	Approx. Power used.
SPECIAL DAYS (contd.)							
142	p.m. 5.40.	Ned. Seintoesl. Fabriek.	NSF 1050 m.	Hilversum	Mon.	Children's Hour	6.40 p.m. 1 Kw.
146	7.00.	Svenska	— 470 m.	Stockholm	Wed.	Concert	10 p.m. 300 Watts.
147	7.00	Stockholm	— 440 m.	Sweden	Fri., Sat.	Concert	10 p.m. 500 Watts.
148	7.40	Smith and Hooghoudt.	PA5 1050 m.	Amsterdam	Wed.	Concert	9.40 p.m. 500 Watts.
149	8.10	Middelraad	PCMM 1050 m.	Ymuiden	Sat.	Concert	9.40 p.m. 300 Watts.
150	8.40	Ned. Radio In	PCGG 1070 m.	The Hague	Mon.	Concert	10.10 p.m. 1.3 Kw.
151	8.40	Amsterdam	PX9 1050 m.	Holland	Tues.	Concert	10.40 p.m. 600 Watts.
152	8.40.	Ned. Seintoesl. Fabriek.	NSF 1050 m.	Hilversum	Fri.	Concert	9.40 p.m. 1 Kw.
153	9.00	Le Matin	SFR 1780 m.	Paris	2nd & 4th Sat. of mth.	Special Gala Concert	10.50 p.m. 10 Kw.
154	9.30	Petit Parisien	— 340 m.	Paris	Thur.	Concert (Items announced in English as well as French).	11.30 p.m. 400 Watts.
155	10.00	Radio-Paris	SFR 1780 m.	Clichy	Wed., Fri.	Dance Music	10.45 p.m. 8 Kw.

ONE of the new wireless converts in this district recently spoke to me in the following manner:—

"Look here, old chap, I want to buy a loud-speaker and it's the dickens of a job to decide which one to have. You old hands at the game are so very confusing to a beginner. You still stick to your A—. Your next door neighbour has a B—. A couple of doors away there is a C—. Further down the road there is a U—. The father of us all, our worthy wireless president, has an S— and a W—. Next door to my place there is an M—, which functions extraordinarily well on a Sunday afternoon, just when I am trying to make up for a little of the sleep I've lost the night before sitting up and listening in to America. The funny thing about it all is that I like every blessed loud-speaker I've heard. What is the best thing to do?"

"Buy one of each sort and have

Buying a Loud-Speaker


By "OLD CHAP"

a loud-speaker in every room. Call the upstairs rooms with loud-speakers Aberdeen; Glasgow and Edinburgh. Put a loud-speaker in the bathroom and call it Manchester. Have London, Birmingham, Bournemouth and Sheffield on the ground floor, hollow ground in the case of Sheffield. Put Cardiff and Newcastle in the coal-cellar and Plymouth on the rockery in the garden. Rig up a simultaneous broadcasting switchboard on the wall near your set, and there you are. Fine loud-speaker scheme, don't you think?"

"I'm talking seriously, and I want serious advice."


"Well, the best advice I can give you is to get your dealer to bring half a dozen loud-speakers to your house and for you to hear them demonstrated on your own set and in your own receiving room. Choose the one which behaves the best under your own actual working conditions and you will not go far wrong."

The wireless convert acted according to the advice given him. At his own house he heard all the loud-speakers he had mentioned to me, and he heard others also. His final choice lay on a loud-speaker of a type he had never heard before. Now he is going about telling everybody that such and such a loud-speaker is the best of the lot, which is a little unfair of him. What he should be telling everybody is that such and such a loud-speaker suits him the best when used with his own set in his own house.

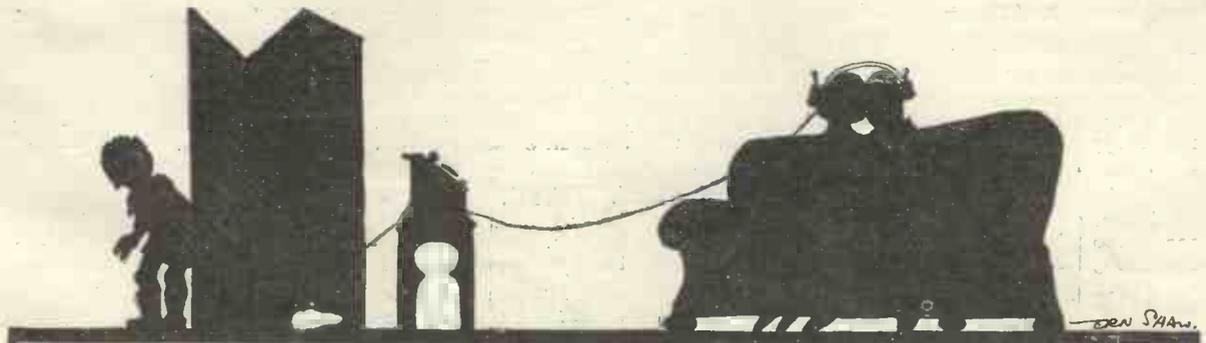

December, 1924

GUARANTEED—

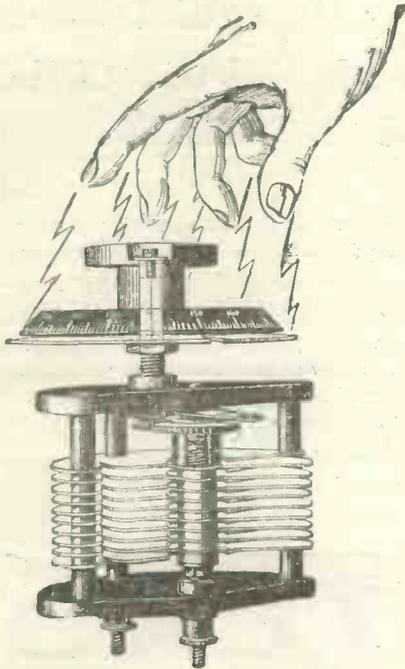

TO ABOLISH HAND CAPACITY

The Naylor "Fulstop" Condenser is the only Condenser which entirely eliminates hand capacity effect. That irritating distortion you hear every time your hand approaches the operating knob cannot exist if you have a "Fulstop" Condenser.

Get the best out of your set by getting a "FULSTOP" SQUARE LAW CONDENSER.

The abolition of hand capacity effects is guaranteed unconditionally by the makers and money will be refunded if any instrument does not give absolute satisfaction.

PRICES:

.001..... 13/6	.0003..... 10/3
.0005..... 11/3	.0002..... 9/6

Stocked by most Wireless Dealers. If you have any difficulty send direct to

J. H. NAYLOR, LTD., WIGAN.



VARIABLE CONDENSER

MODERN WIRELESS



Good night Everybody!

"Good night, everybody," says my Volutone Loud Speaker, and I find myself saying "Good night, thank you, good night." And, after all, why shouldn't I? I know that my Volutone has been a very real friend to me. All through the summer he was with me, indoors and out of doors, and now that shorter days and long, dark evenings are here, I value his friendship more than ever. Ready to talk if I want to listen, to play to me or to sing to me. And if I join in his song (as indeed I do) is he annoyed? What a friend of friends!!

On a boisterous evening when we are all laughing and fooling, the Volutone plays with the loud pedal down and fills the room with music. On such a night as this, when I sit quietly by the fire, he sings softly and sweetly for me alone.


Yes, I will say good night to my Volutone. "Good night, old friend, until to-morrow. Goodnight, Everybody."

Mulle Fellows


FELLOWS WIRELESS

Advt. of the Fellows Magneto Co., Ltd., Park Royal, London, N.W.10.

E.P.S. 92.

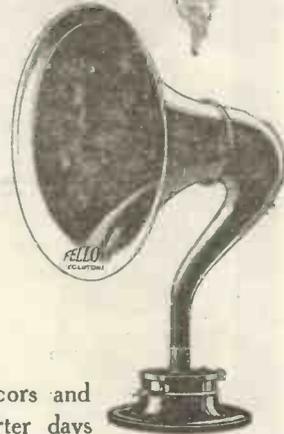

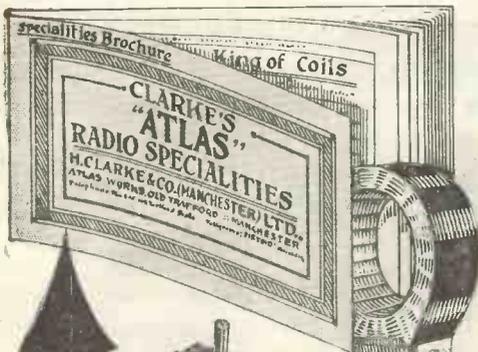Fellows Volutone. £4 : 10 : 0
 Fellows Junior. £1 : 10 : 0
 Both fitted with adjustable diaphragms



— They're all in the brochure, and more besides.

A copy of the new "Atlas" Brochure is yours for the asking. It should be in the hands of every wireless man who knows the value of components designed and guaranteed by practical radio experts.

There isn't an "ordinary" component in the whole of the range. Many of the devices are patented, and in more than one instance the components are complimented by "the sincerest form of flattery."

As for prices—well, send a P.C. or fill in the coupon, and wait for a pleasant surprise.

CLARKE'S ATLAS SPECIALITIES

SOLELY MANUFACTURED BY—
H. CLARKE & CO.
 (MANCHESTER), Ltd.,
 Radio Engineers,
 Atlas Works, Old Trafford,
MANCHESTER

Grams: "Pirtoid, Manchester."
 Phones: 683 & 793 Trafford Park.



Please send by return a copy of the
 Name _____
 Address _____
 Clarke's "ATLAS" Brochure.

M.W.



Some Two-Valve Reflex Circuits

These Circuits afford a basis for interesting experiments for the two-valve man.

Arranged by JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.

The S.T. 75

THE Fig. 1 circuit has achieved popularity on account of its sensitiveness and effective operation. It involves a stage of high-frequency amplification, a stage of low-frequency and a valve detector between the two stages.

The first valve V_1 acts as a high-frequency amplifier, the amplified currents appearing in the circuit $L_2 C_2$, which is the anode circuit of the first valve. For broadcast wavelengths L_1 may be a No. 35, 50, or 75 coil, L_2 a No. 50 or 75, the condenser C_1 being of $.0005 \mu F$ and C_2 of $.0005$ or $.0003 \mu F$ capacity. A lead is taken, as shown, from the bottom of L_2 to the $.0003 \mu F$ grid condenser C_4 , and then to the grid of the second valve V_2 , which acts as the detector. Across the grid and positive filament of V_2 is connected a 2-megohm gridleak R_3 . In the anode circuit of this second valve we have the reaction coil L_3 , for which a No. 75 coil will be suitable, and also the primary T_1 of a step-up intervalve transformer $T_1 T_2$, which conveys the low-frequency currents to the grid circuit of the first valve which thereupon amplifies them.

The amplified low-frequency currents pass through the loud-

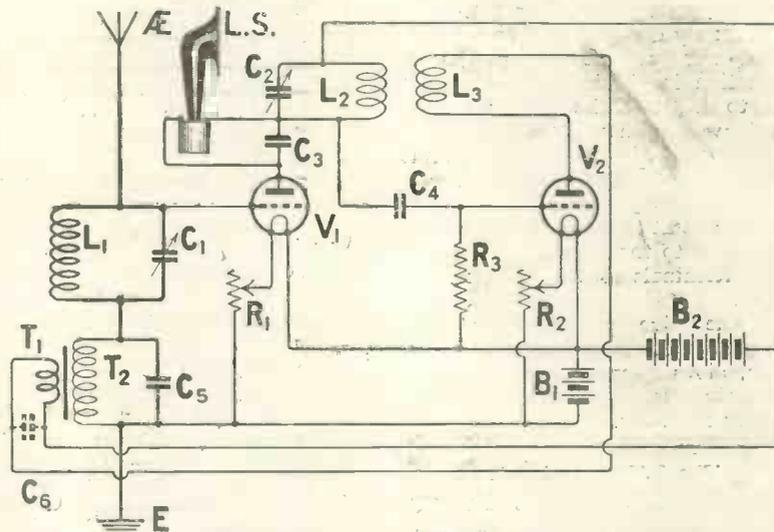


Fig. 1.—The S.T. 75, a sensitive reflex circuit.

speaker LS, which is included between the anode of the first valve and the circuit $L_2 C_2$, a condenser across it of $.002 \mu F$ (the best value may be found by experiment) being preferably provided. A condenser C_5 , of not more than $.001 \mu F$ capacity, is connected across T_2 to allow the high-frequency currents to pass through. The condenser C_6 of, say, $.0003 \mu F$ capacity is optional, and experiment will prove

if it is necessary with the particular apparatus used. Care should be taken to keep the loud-speaker away from the accumulator and the high-tension battery, and it should be well insulated. When telephones are used instead of the loud-speaker, there is frequently some difficulty in tuning.

The popular S.T. 100

Fig. 2 shows the well-known S.T. 100 circuit, in which the secondary T_2 of the step-up intervalve transformer $T_1 T_2$ is connected directly in the aerial-earth circuit.

The first valve V_1 acts as a high-frequency amplifier, and its anode circuit contains the tuned circuit $L_2 C_2$, which is tuned to the incoming wavelength. For the broadcast band of wavelengths the aerial coil L_1 may be a No. 50 or 75, and L_2 a No. 50 or 75. The condensers C_1 and C_2 may both have a capacity of $.0005 \mu F$. The crystal detector rectifies the amplified currents set up in $L_2 C_2$, the resultant low-frequency currents being then amplified by the valve V_1 , the transformer $T_1 T_2$, applying the low-frequency currents to the grid of this valve.

The amplified low-frequency currents in the anode circuit of the first valve pass through the primary

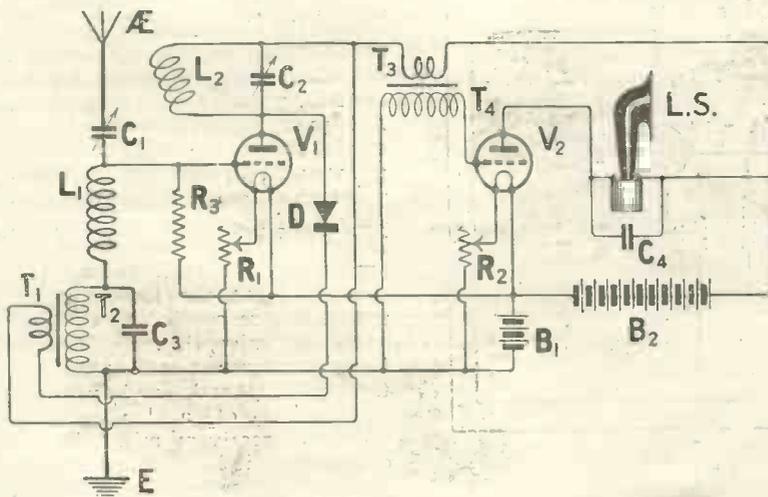


Fig. 2.—The theoretical circuit of the S.T. 100.

T_3 of the step-up transformer T_1T_2 , the secondary of which is in the grid circuit of the second valve. In the anode circuit of the second valve we have the loud-speaker LS, preferably shunted by a condenser C_4 , of about $.002 \mu F$ or $.004 \mu F$ capacity, which is for the purpose of improving the tone of the signals. The anode voltage should preferably be not less than 100 volts.

The condenser C_3 , shunted across the secondary of the transformer T_1T_2 , may conveniently be a fixed condenser of $.001 \mu F$ capacity. Reaction is obtained by coupling L_2 to L_1 , but the circuit works quite well without reaction. The resistance R_3 is 100,000 ohms, and may, if desired, be variable. If there is any tendency on the part of the circuit to buzz, try changing the leads to the primary or secondary terminals of the transformer T_1T_2 .

A negative potential on the second grid, and sometimes on both, gives improved results, particularly if the high-tension voltage is over 100 volts.

The S.T. 111 circuit

Fig. 3 shows another two-valve receiver in which there is a stage of high-frequency amplification accompanied by reaction, rectification by means of a crystal detector and two stages of low-frequency amplification. The circuit differs from the S.T. 100 in that the rectified currents are passed through the primary of a transformer T_1T_2 , the secondary of which is connected in

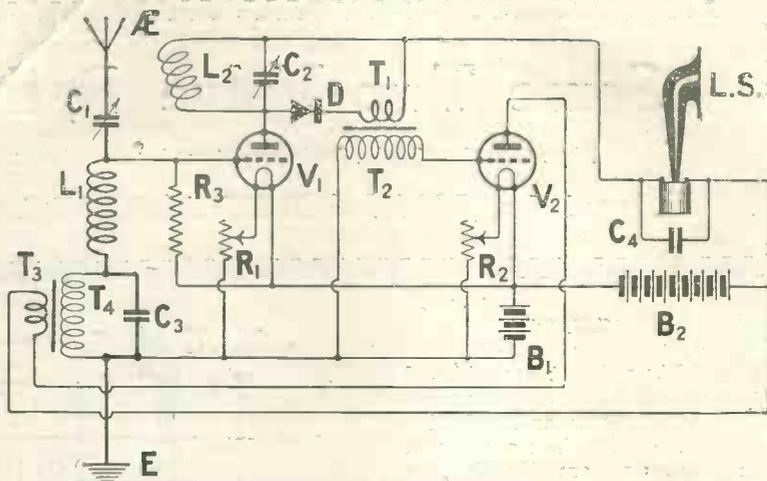


Fig. 3.—With the S.T. 111 circuit the first valve gives the last stage of note magnification.

the grid circuit of the second valve instead of the first.

It will be noticed that the anode circuit of the second valve contains the primary T_3 of a second interval transformer T_3T_4 . The secondary T_4 of this latter transformer is included in the grid circuit of the first valve, and the result is that the low-frequency currents, after two stages of amplification, pass through the loud-speaker LS, which is included in the anode circuit of the first valve. The loud-speaker is usually shunted by a condenser C_4 of about $.002 \mu F$ capacity, although the use of this condenser, like other fixed condensers in these circuits, is a matter for experiment. A fixed condenser might be tried across the primary T_1 of the step-up transformer T_1T_2 .

Suitable values for both the coils L_1 and L_2 are Nos. 50 or 75, although a No. 75 for L_2 will probably be found most effective. These values refer to the broadcast band of wavelengths. A 100,000 ohms resistance R_3 is connected across the grid and that filament of the first valve which is connected to the positive side of the filament accumulator B_1 . The condenser C_3 might be $.001 \mu F$ capacity, though the best value should be determined by experiment. The variable condensers C_1 and C_2 may conveniently be $.0005 \mu F$ capacity.

The S.T. 150

Fig. 4 shows a useful two-valve circuit, in which the first valve acts as a high-frequency amplifier, reaction being introduced into the circuit L_1C_1 by coupling the reaction coil L_2 to L_1 . The reaction coil L_2 is tuned by means of the variable condenser C_3 , and a connection is taken from the anode side of the circuit L_2C_3 to the grid of the second valve which acts as a detector. Suitable values for L_1 are Nos. 35 or 50 coils, and for L_2 , Nos. 50 or 75. In the anode circuit of the second valve we have the primary T_1 of the step-up interval transformer T_1T_2 , the secondary T_2 of which is connected both in the aerial circuit and in the grid circuit of the first valve. The result is that the low-frequency potentials are applied to the grid of the first valve, the amplified low-frequency currents passing through the loud-speaker LS and operating it. Instead of a loud-speaker, telephone receivers might be included, and it is a matter for experiment to see whether the fixed condenser C_4 of $.002 \mu F$ or more is necessary or not. If telephones are

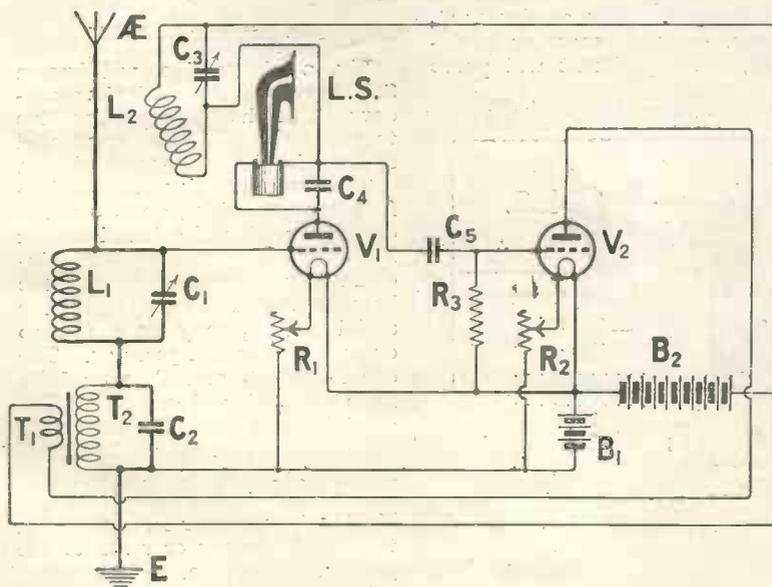


Fig. 4.—The theoretical circuit of the S.T. 150.

BACKED BY GENEROUS GUARANTEE—BONTONE

We agree to replace any 'phone not giving complete satisfaction if returned to us within seven days of purchase undamaged. We further agree to repair, adjust, re-test any Bontone 'Phone, irrespective of the date of purchase, for the sum of 3/6, plus 6d. postage, if returned to us intact, with remittance.



4,000 OHMS PER PAIR

14/6

Post Free.

BONTONE are made throughout in our own works. Made of the best materials procurable and covered by a guarantee. Compare these BONTONE advantages with the conditions when purchasing Continental Telephones. BONTONE are sensitive—we make our own magnets, wind the bobbins, make them from beginning to end.—BONTONE are British Made.

Manufactured up to High-Efficiency down to a Popular Price.

BONTONE are durable and comfortable. The pleasures of "listening-in" are trebled if your headphones are comfortable. Easily adjustable, BONTONE are for every member of the family.

BONTONE LIGHTWEIGHT

15/6

Post Free.

Apply to your Dealer, or write direct giving your dealer's name and address to:

B. D. & Co. (EDWARD A. BOYNTON)

Works: GOSWELL ROAD and CITY ROAD, LONDON, E.C.1.

Offices: 167-173, GOSWELL ROAD, LONDON, E.C.1.

Admiralty, War Office and India Office Contractors.

Barclays 340.

FACTS ABOUT THE MOST EFFICIENT COILS

that Wireless Research has yet produced

If your receiver suffers from flat tuning, substitute Diamond Sunflower Coils and note how sharp the tuning becomes. Diamond Sunflower Coils gives razor-sharp tuning—their self-capacity is low and H.F. Resistance is low—electrical facts which make Diamond Sunflower Inductances preferable in any receiver.

A VERY IMPORTANT CONSIDERATION

The choice of an inductance for any given wave length is one of considerable importance. Many factors do intervene which make a coil between the usual sizes desirable for maximum signal strength. Technical authorities—Mr. John Scott-Taggart practically—point out its advantages. It enables the highest inductance to be used with the lowest convenient variable condenser capacity. This does give better reception.

Diamond Sunflower are made in intermediate sizes—one of the many reasons why you should fit Diamond Sunflower Coils to your set. Besides, they will save you shillings on a complete set of coils.

Obtainable from your dealer or direct from the manufacturers.



Note swivel mounting.

PROV. PAT.



PLUG-IN

COILS

DIAMOND WIRELESS, LTD., 184a, OXFORD STREET, LONDON, W.1.
Telephone: MUSEUM 1380. Entrance: GT. TITCHFIELD ST.

Barclays 350

Lathes

The Lathe has been called King of the Tools, and the description is apt. The amateur, the professional, the experimenter and the manufacturer all find the lathe the most essential aid if they construct their own plant. Not only for Wireless, however, is a handy lathe so valuable. In all branches of model and experimental work, aid in car and motorcycle overhauling, etc., it is always a prime essential.

For the home worker the best is the

DRUMMOND 4 in. Universal Lathe.

This tool will cover an almost infinite variety of work, including all plain turning in metal, wood, ebonite, etc., screw-cutting, drilling, boring, facing, milling, coil-winding, slotting, etc. The saddle and top slide are provided with bolt slots to enable work to be readily mounted. These work tables have a height adjustment relative to the lathe centres—a very valuable feature; this is effected by sliding saddle about the circular bed. We illustrate the lathe arranged on stand for treadle drive; note the heavy flywheel. Other forms of drive are supplied, and an extra long bed model is available at small extra cost. A Service Department is at your disposal—consult us.

Machines to suit all requirements, supplied on deferred payment plan if required. Write for lists.


DRUMMOND Bros. Ltd.

Reid Hill, Guildford.

In replying to Advertisers, please use Order Form enclosed.

A SQUARE LAW with a Conscience.

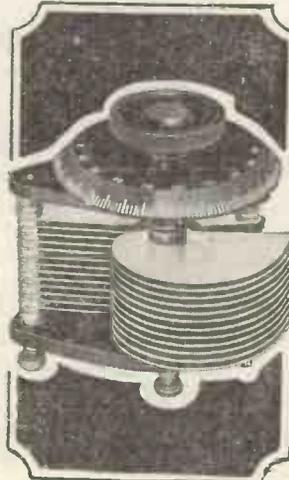"Dead Men Tell No Tales." If only some of the mutilated remains of the old type condensers, which are disguised as Square Law, could but give up their secrets? It would be a tale of hopeless inefficiency caused by under capacity and a "very curved" straight wave-length tuning.



Set builders who have neither the means nor the time to test their tuners for the wave-length range or the straightness of the curve can, however, assure themselves that J.B. Condensers are highly efficient. The curve is straight—the capacity guaranteed—not idly but actually.

.001	- 9/6	.00025	- 6/3
.00075	- 9/-	.0002	- 5/6
.0005	- 8/-	.0001	- 5/3
.0003	- 6/3	Vernier	- 4/6

It is needless for us to warn set builders that there is only one safeguard—it is to look for our mark on every condenser. It signifies the highest efficiency—at a popular price—in shillings not pounds.



Go to your dealer first. If he cannot supply send direct—it's well worth it. Post: One, 6d. Two, 9d. Three, 1s.

The J.B. Square Law by virtue of its accuracy is desirable for use in Wavemeters and calibrated circuits.

JACKSON BROS.
8, POLAND ST- OXFORD ST.
LONDON - W.1
Telephone: GERRARD 7414
(First Floor)

Barclays 37

Find the true worth of your set!

Find out how many stations you can really get! Don't be satisfied with simply picking up a distant station, but bring it in with all the beauty and strength of tone that you so easily get from your local Broadcast Station. Ask your Dealer for **ORMOND SQUARE LAW CONDENSERS (ALL ORMOND PRODUCTS ARE BEST)**, and give your set a real opportunity to prove its merits.




PRICES.
Without Vernier.


.001	...	10/6
.0005	...	9/6
.0003	...	9/-
.00025	...	8/6

PRICES.
With Vernier.

.001	...	12/-
.0005	...	11/-
.0003	...	10/6
.00025	...	10/-

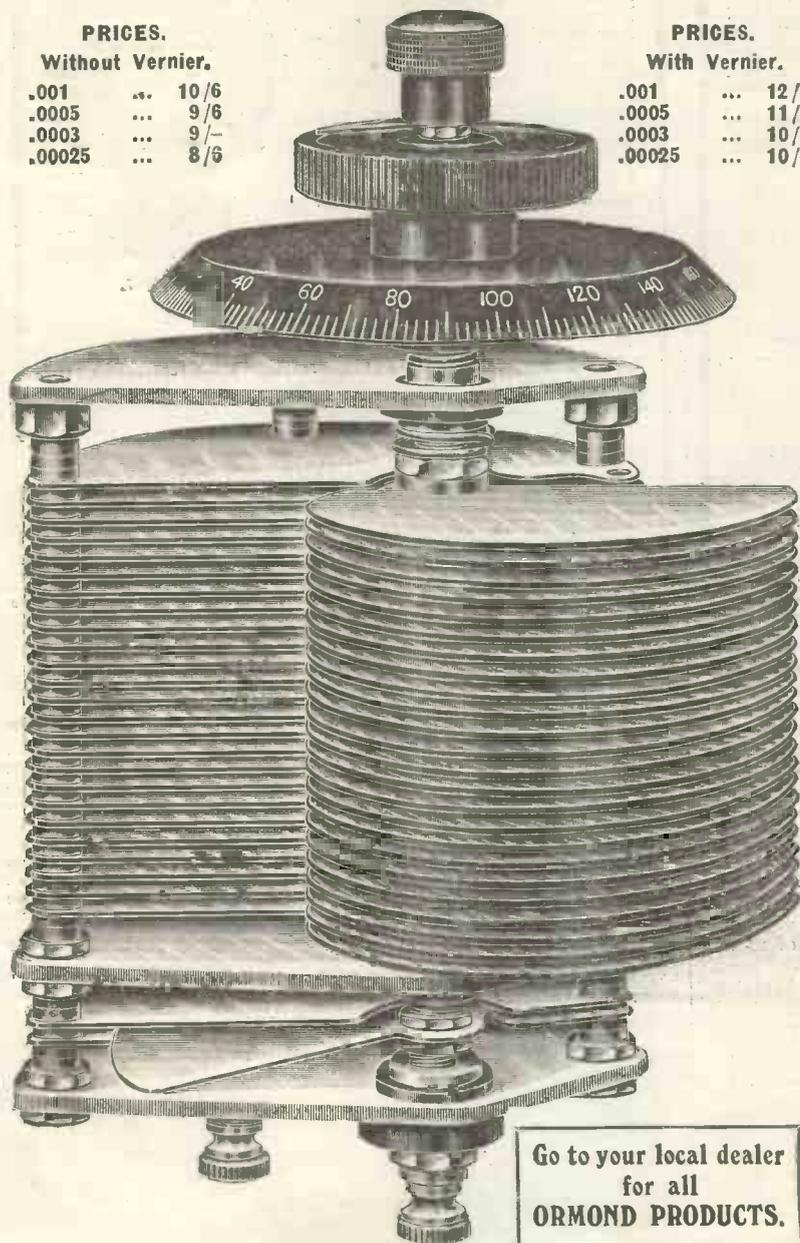

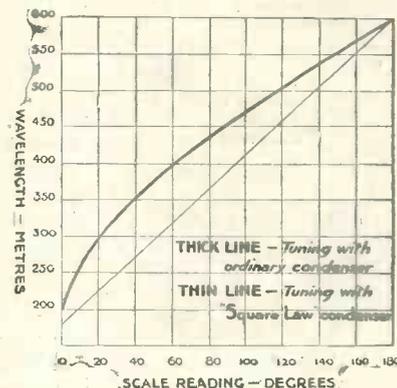Go to your local dealer
for all
ORMOND PRODUCTS.



The "Square Law" Type Variable CONDENSER

The use of a "Square Law" Condenser renders the tuning of a Receiver a very simple matter indeed. A calibration chart may be made up by the following simple means:—

Tune in a Station of known wavelength on the lower part of the condenser scale and plot it on the chart. Repeat this process with another station of known wavelength which is received on the upper part of the condenser scale. Draw a straight line through the two points and the chart is complete.

Owing to details of its design, this type of Variable Condenser possesses a negligible minimum capacity, and the specially shaped vanes give an ease of control which is entirely unknown to users of the ordinary type.

We specialise in turning Brass and Steel Screws and Machined Parts and Accessories of all descriptions.

All Cheques and Postal Orders should be crossed and made payable to "The Ormond Engineering Company."

Ormond Engineering Co.,
199-205, Pentonville Road, King's Cross, London, N.1.

'Grams—"ORMONDENGI, KINGCROSS."

'Phone—Clerkenwell 6652 and 7833.

25 YEARS' BRITISH MANUFACTURING EXPERIENCE.

used it is desirable that their insulation should be perfect. A loud-speaker is, in general, greatly to be preferred to telephone receivers with this circuit. Suitable values for other components are $.0005 \mu\text{F}$ capacity for the variable condensers C_1 and C_3 , $.0003 \mu\text{F}$ for the grid condenser C_2 , and 2 megohms for the gridleak R_3 .

A Modified S.T. 75

Fig. 5 shows a modification of the Fig. 1 circuit whereby reaction is introduced into the aerial circuit and H.F. transformer coupling between the two valves is used. The incoming oscillations in the aerial circuit L_1C_1 cause varying potentials to be set up across the grid-filament circuit of the valve V_1 . Corresponding amplified currents pass through the primary L_2 of an H.F. transformer L_2L_3 of suitable design for the wavelength range to be covered. The secondary L_3 is tuned by the condenser C_2 of $.0005 \mu\text{F}$ or $.0003 \mu\text{F}$ capacity. This secondary is connected across the grid and filament of the valve V_2 , the usual grid condenser C_4 and gridleak R_3 being provided. Thus the amplified high-frequency oscillations in L_3 are passed on to the second valve, which rectifies them, the resultant low-frequency currents being fed into the grid circuit of the first valve via the step-up intervalve transformer T_1T_2 .

A reaction coil L_4 of, say, 35 or 50 turns, coupled to L_1 , is included in series with T_1 in the anode circuit of the valve V_2 . Provision is also made for adding grid bias to the first valve by connecting a suitable grid battery GB, as shown, in the earth-filament lead. It will

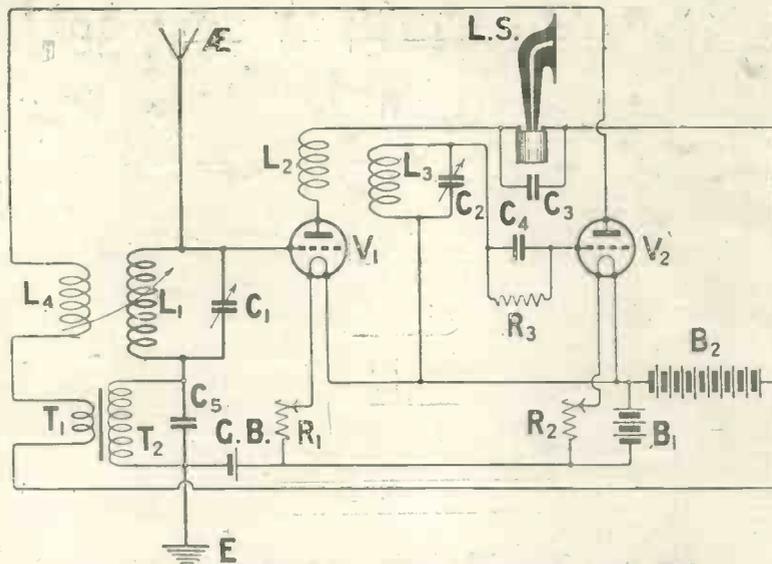


Fig. 5.—A modification of Fig. 1 circuit, using H.F. transformer coupling.

be observed that no condenser is shunted across T_1 . With some apparatus, however, a small fixed condenser is necessary here, but usually the self-capacity of the primary windings is sufficient.

The S.T. 75 with aerial reaction

In Fig. 6 is shown a circuit similar to that of Fig. 5, except that tuned anode coupling is used instead of high-frequency transformer coupling between the two valves. The first valve acts in a dual capacity as a high-frequency and a low-frequency amplifier, while the second valve acts as the detector.

The incoming oscillations in the aerial circuit L_1C_1 cause varying potentials to be applied to the grid

of the valve V_1 . As a result amplified high-frequency oscillations are set up in the anode circuit L_2C_2 , which is tuned to the incoming wavelength. A lead is taken from the anode end of L_2 to one side of the grid condenser C_3 , the other side of which is connected to the grid of V_2 , the usual leak R_3 being provided. The amplified high-frequency oscillations are thus applied to the grid of the valve V_2 , which rectifies them. The resultant low-frequency currents are fed into the grid circuit of the first valve through the step-up intervalve transformer T_1T_2 , and are further amplified by the valve V_1 . The loud-speaker LS is in the anode circuit of the valve V_1 , and is shunted by a by-pass condenser C_4 of $.002 \mu\text{F}$. As before, provision may be made for grid bias on the first valve.

In series with T_1 in the anode circuit of V_2 , is a reaction coil L_3 coupled to L_1 . For broadcast reception L_1 may be a No. 25, 35 or 50 coil, and for L_2 and L_3 Nos. 50 or 75 will be found suitable. The values of the other components are the same as those mentioned in reference to the Fig. 5 circuit.

Intervalve coupling using a choke

Fig. 7 shows a modification of the Fig. 6 circuit. The tuned anode is replaced by a choke coil L_2 , the grid circuit L_3C_2 of the second valve being tuned by the variable condenser C_2 . The loud-speaker LS is in the anode circuit of the first valve, as shown. By means of this arrangement any L.F. potentials established across the loud-speaker LS will not be

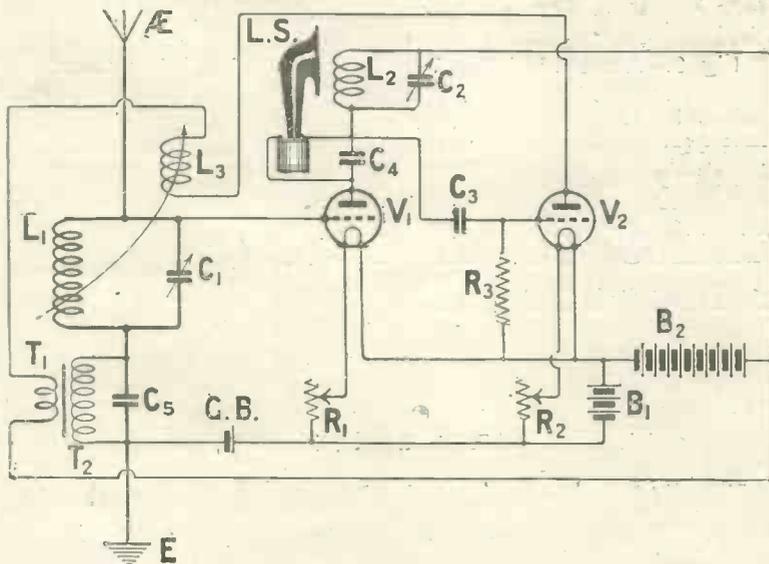


Fig. 6.—A modified S.T. 75 with aerial reaction.

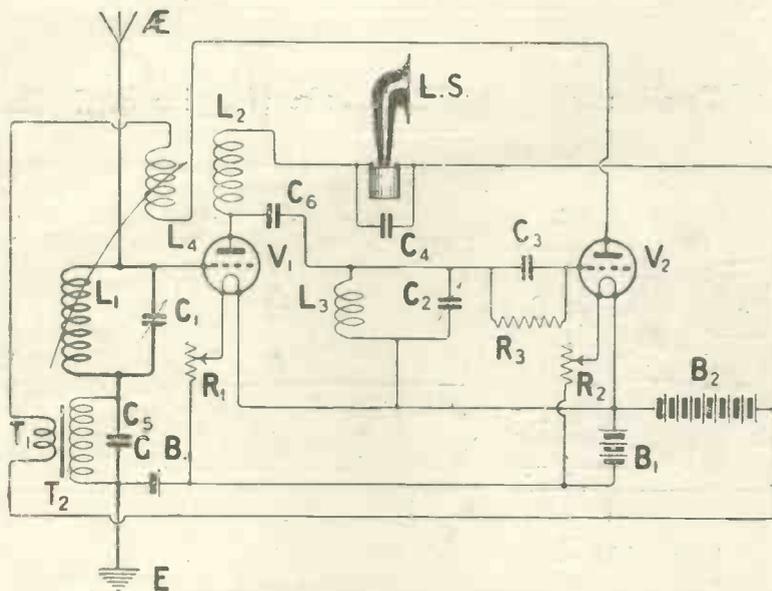


Fig. 7.—With this arrangement the loud-speaker is not at high-frequency potential.

applied to the grid of the valve V_2 because of the short-circuit provided for L.F. currents by the coil L_3 . A chain of low-frequency amplification, with consequent buzzing, is thus prevented.

It will be observed that no condenser is shown shunted across the primary T_1 of the transformer T_1 , T_2 . A small fixed condenser may be necessary with some apparatus, but usually the self-capacity of the primary winding suffices. Reaction on to the aerial is provided by coupling a coil L_4 , in the anode circuit of the second valve, to the coil L_1 , and grid bias may be put on the first valve by including a grid battery GB, as shown. To cover the broadcast band of wavelengths, L_1 may be a No. 35 or 50 coil, L_2 being Nos. 50 or 75, while a No. 50 for L_4 will probably be found suitable. For L_2 a convenient coil is a No. 200.

A further modification

The Fig. 8 circuit shows a modification of that of Fig. 7. In this case reaction on to the aerial is omitted, and in its place is substituted reaction on to the grid circuit of the second valve, obtained by coupling a coil L_4 , in the anode circuit of the valve V_2 , to the coil L_3 . This will, to a large extent, minimise re-radiation from the aerial. The same arrangement as is used in the Fig. 7 circuit in order that the loud-speaker should not be at high-frequency potential to earth is incorporated in this circuit. A fixed condenser across the primary T_1 of the transformer T_1 , T_2 is not shown, but experiments may be tried with condensers of different values, or with a variable condenser of, say, $0.001 \mu F$ capacity, to determine whether a condenser in this position is an advantage or not.

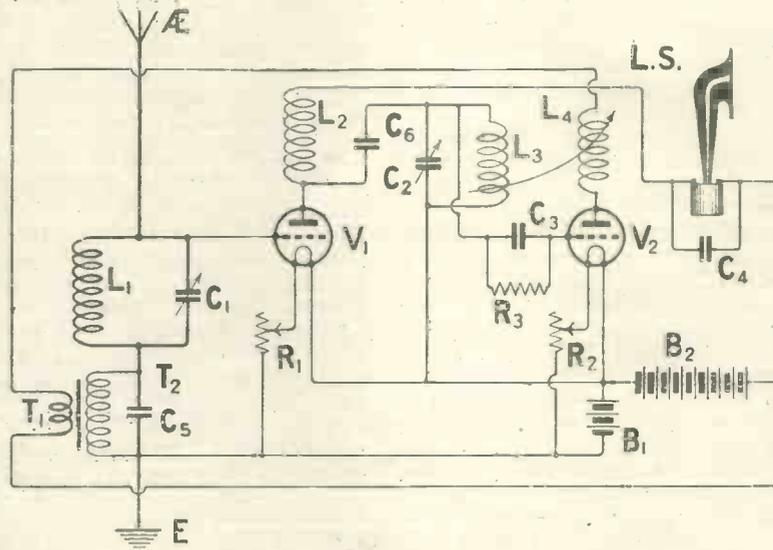


Fig. 8.—A modified Fig. 7 circuit employing inter-valve reaction.

Do not miss the Next Number of
"THE WIRELESS CONSTRUCTOR,"
 out DECEMBER 15th.

In this issue Mr. Harris describes a Special Six-Valve Receiver using three stages of high-frequency.

There is also a complete article by John Scott-Taggart, F.Inst.P., A.M.I.E.E., on the "Twin-Valve" Reflex Set, a new receiver which gives reliable loud-speaker results up to 50 miles. This set does not use a crystal; and an L.F. Transformer is employed.



Look to your Valves

GENERAL PURPOSE VALVES:

Type R. ... 12/6 each

Filament Voltage.....4 volts
 Filament Current.....0.7 amp.
 Maximum plate voltage...100 volts
 Plate resistance.....27,000 ohms.

Type B 3 ... 21/- each

Filament voltage.....18 volts
 Filament current.....0.35 amp.
 Maximum plate voltage...80 volts
 Plate resistance.....27,000 ohms.

***Type B5. ... 25/- each**

Filament voltage.....2.8-3 volts
 Filament current...0.06 amp. (at 3 v.)
 Maximum plate voltage...80 volts
 Plate resistance.....17,000 ohms.

POWER AMPLIFYING VALVES:

Type B4. ... 35/- each

Filament voltage.....5-6 volts
 Filament current...0.25 amp. (at 6v.)
 Maximum plate voltage...120 volts
 Plate resistance.....6,000 ohms.

***Type B6 ... 35/- each**

Filament voltage.....3 volts
 Filament current.....0.12 amp.
 Maximum plate voltage...120 volts
 Plate resistance.....9,000 ohms.

***Type B7 ... 37/6 each**

Filament voltage.....6 volts
 Filament current.....0.06 amp.
 Maximum plate voltage...120 volts
 Plate resistance.....9,000 ohms.

*For use with Dry Cells




They are chiefly responsible for the quality of reproduction. Badly exhausted valves, otherwise "soft" valves, are short-lived and give poor results. "Soft" valves cost less to make than "hard" valves, but they are expensive and unsatisfactory in use. B.T.H. Radio Valves are exhausted by a special patented B.T.H. process which produces an exceedingly high vacuum.

FIT B.T.H. VALVES & MAKE YOUR SET A GOOD SET

From all Electricians and Radio Dealers

B.T.H. RADIO VALVES

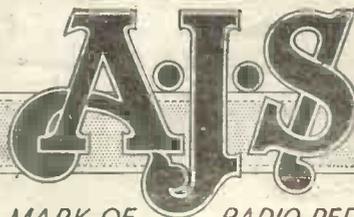

THE HALL MARK OF RADIO PERFECTION

NEW MODELS

THERE are definite and convincing reasons why the new A. J. S. Models will claim the attention of every Radioist. In the first place the name alone is evidence of entire reliability in every detail of construction, design, material and finish. Beyond that are many unique features which speak for themselves. For instance, the special method of stabilising the first H.T. Valve ensures that the Inductances are undamped, which means stronger signals, greater selectivity and the power to pick up and amplify very weak signals. With the 4-Valve Set the 3rd or 4th Valve can be used as a Power Amplifier when switched on to the Loud Speaker, so that when three Valves are used the 3rd Valve acts as a Power Amplifier and when four Valves are in use the 4th Valve acts as a Power Amplifier.

Ask your nearest A. J. S. dealer to show you these and other A. J. S. improvements, or write direct to:—

**A. J. STEVENS
& CO (1914) LTD**
WIRELESS BRANCH
WOLVERHAMPTON

*Phone: 1550. Wireless Call Sign: 5RI. 'Grams: Reception, Wolverhampton.

Each Set complete with all accessories, ready for instant use (Valves, 'Phones, H.T. and L.T. Battery, Aerial Wire, Insulators, Lead-in Tube).

The following details apply to the 2, 3 and 4-Valve Sets:—

Polished Walnut Cabinet of handsome appearance, sloping front and hinged top, which conceals all connecting wires and terminals. Best quality ebonite Panel, matt finish; plated fittings. Filament Resistance to each Valve. Valve Switch for Low-Frequency Valves. Best quality Valves of well-known make. 100-Volt H.T. Battery. 60 ampere-hour, 6-Volt L.T. Battery in polished wood crate for 2 and 3-Valve Sets. 80 ampere-hour 6-Volt L.T. Battery in polished wood crate for 4-Valve Set. Ebonite Lead-in Tube, 9 ins. long, terminal each end, 7.22 best quality copper. Aerial Wire. Special Shell Type Insulators. Brandes "Matched Tone" Headphones.

PRICES.

(Including all Royalties and ready for immediate installation).

Two-Valve Set	£17 10 0
„ Panel only	£12 0 0
Three-Valve Set	£22 5 0
„ Panel only	£15 17 6
Four-Valve Set	£27 5 0
„ Panel only	£20 5 0



The Japanese Operators' Difficulties

An Explanation of the Complex Japanese Telegraph Code.

MANY an exasperated operator in the Pacific, cooped up in his stifling wireless cabin on a hot and sultry tropical night, has torn the 'phones from his aching and perspiring head almost with feelings of murder in his heart at being hopelessly jammed by a near-by Japanese ship sending what appears to be an inextricably muddled series of signals quite incomprehensible to any of the Western nations. Little does he realise the difficult lot of the Japanese operator who is making his life unbearable.

The Japanese Alphabet

It is the object of this article to present in an interesting manner the tremendous obstacles which have had to be solved before telegraphic transmission of the language of Japan was possible, and to give some idea of the severe training undergone before the Japanese operator is posted to a ship and of his difficulties afterwards.

In order to do this, it is first necessary to tell something of the complex language of the country and of its writing systems. Although not strictly so, Japanese writing is almost letterless, and, unlike Chinese, from which modern Japanese has largely been derived, it has been developed into a phonetic system of syllables denoted by forty-seven symbols and twenty-six diacritical marks. Fortunately, of the latter only one is absolutely essential for telegraphing. Using these symbols and marks, all Japanese sounds, and hence words, can be reproduced.

Complex Writing

This system is only one of the many methods of writing used in the country, and, although despised by academicians, is used in many publications, since by its means it is possible to express foreign terms, and scientific meanings which cannot be made clear by any of the other writing systems. Hence it follows that this is the only form of writing which can possibly be telegraphed.

The Japanese operator has also to understand and be able to translate into the phonetic system another form, largely derived from the Chinese, which has from three to six thousand roots and can only be written, being unintelligible when spoken.

From the complex methods of writing previously mentioned it will at once be seen what a difficult problem had to be mastered before the introduction of telegraphy was an accomplished fact. Combinations of dots and dashes had to be found

and dashes, as there are not enough short ones to go round; no less than eighteen groups each contain five dots and dashes.

Morse Equivalents

The illustration shown is that of the forty-eight phonetic symbols, with their morse equivalents and, as far as is possible, their approximate pronunciation. Of these symbols two sound exactly alike when spoken, but are written and used differently. As an example, the translation of a simple tele-

"Home Friday. Love and kisses. Mary"

Home
tsu - koo

ツ ㄣ

Friday
keenyo

ㄝ ヨ ㄣ

Love and kisses
Yo - ro - shee - koo

ㄣ ㄣ ツ ㄣ

Mary
Hannah - ko

ハ ㄝ ㄣ

This Message in Japanese reads "Friendly Compliments."

adequately to express the forty-seven symbols and the one vitally essential diacritical mark of the phonetic system. A code was worked out by European and Japanese experts before the year 1900, but this was modified somewhat after the war between Russia and Japan.

The resultant code is consequently a difficult one, since forty-eight letters or symbols have to be expressed, as compared with the twenty-six of our own alphabet. This, of course, necessitates the use of a number of long groups of dots

gram into Japanese is given. The "love and kisses" has been seriously altered, making the translation very tame, as even mention of kissing is thought highly improper in Japan.

Japanese Operators' Hard Lot

From these remarks you will gather that the lot of the Japanese "Sparks" is not an easy one when compared to that of his British counterpart. Again, the Japanese language is absorbing new words and ideas from the Western nations, making for an increase in the

number of symbols and marks needed clearly to express these. Eventually this may compel an extension being made to the existing telegraphic code. The operator must, of course, be capable of translating and telegraphing the common, polite and Chinese-derived writing systems, of which the latter

sound knowledge of wireless law and theory.

Comparing conditions between Japanese and American operators as far as pay is concerned, there is not a great deal of difference, but in status the Jap is regarded much more favourably. He is one of the genuine officers in the ship, and

for the great strength of their signals.

In Japan all wireless apparatus is built, installed and used under the strictest Government supervision, and transmitting by amateurs is not allowed except in the case of one or two powerful newspapers. Receiving is also illegal, but in the

イ	--	ee	ワ	---	wah	#	-----	wee	サ	-----	sah
ロ	----	row	ク	----	kah	ア	----	no	キ	----	kee
ハ	----	ha	コ	--	yo	オ	-----	oh	ク	-----	you
シ	----	nee	カ	--	tah	ケ	----	koo	ケ	-----	zay
ホ	--	hoe	シ	---	ray	カ	----	yah	エ	-----	nee
ヘ	.	hay	ソ	----	so	ク	----	mah	ツ	-----	shse
ト	----	toe	ツ	----	tsu	ケ	----	kay	エ	-----	aye
チ	----	tchee	チ	----	neigh	フ	----	too	ヒ	-----	shse
リ	---	ree	フ	---	nah	フ	-----	kwo	エ	-----	moh
メ	---	new	フ	---	rach	イ	-----	ach	セ	-----	zet
ル	-----	roo	ム	-	moo	テ	-----	tay	フ	-----	soo
ヲ	-----	wawk	ウ	---	ugh	ト	-----	ai	ソ	-----	n

Morse Symbols for Japanese Alphabet and their Approximate Pronunciation.

is in some cases capable of several interpretations determined merely by position.

Good Education Necessary

An exceedingly good general as well as technical education is a necessity for an operator. There are many cases where the students, not being attached to military or naval schools, are forced to work long hours to pay for their tuition; and this, together with the strain of overstudy, is largely responsible for the high percentage of tragedies among the technical students in Japan. Faced with hunger and overwork, a number end their troubles in suicide.

The students who succeed in passing the strict examinations imposed are granted, in most cases, a second-class commercial licence by the Government. A first-class certificate is usually competed for after two years or so at sea, and to gain this the operator must be able to send and receive a hundred symbols a minute and at twenty words a minute in English in the Continental code, as well as have a

dines with the captain and chief engineer in the first-class passengers' saloon, mixing with the latter freely. The American operator, on the other hand, even though he is a chief, is rated below the third mate. The position of the Japanese operator when on board is one of unusual authority. Under certain conditions his position is unassailable by even the captain or the owner of the vessel. He is a naval reservist, and responsible only to his Government with whom he keeps all his records and accounts.

Equipment

A few words regarding the usual equipment to be found on Japanese ships may be of interest here. In the majority of vessels this is of an obsolete type similar to the Telefunken sets of fifteen years ago. The transmitters are seven-kilowatt type, direct-coupled and using the quenched-spark system. Although so old, they are usually in magnificent condition, as the operators regard it as a labour of love to look after them; whilst anyone who has listened in the Pacific can vouch


near future it is expected that receivers for broadcasting will be allowed to be used, subject to a number of restrictions.

We are indebted to the American journal "Radio" for much of the above information about the Japanese morse code.

British students learning the code should feel lucky that they were not born in the land of the Rising Sun!

The "Ultra" Loud Speaker.

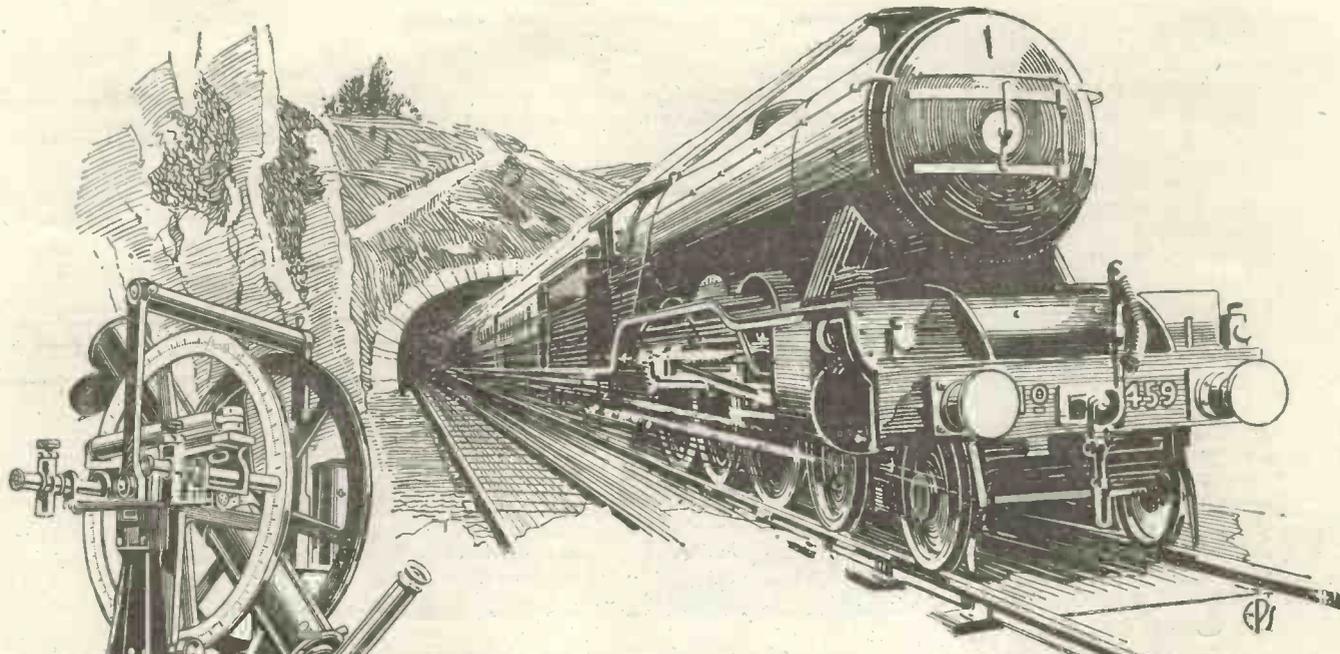In the advertisement of Messrs. Ed. Rosen & Co., in the November issue of "Modern Wireless" a slight error occurred. Width of base 10 inches should read; Width of flare 10 inches.



Let the Cobbler stick to his last

THE Railway Engineer requires his instruments to be of the greatest precision.

When he chooses a theodolite, he goes not to an upholsterer, nor to a maker of gramophones, but to a firm whose speciality is the manufacture of surveying instruments.

He knows that instruments if defective may cost him thousands of pounds, so he is careful to buy them only from a firm whose long specialised knowledge is a guarantee of good results.

The small fixed condensers in your wireless set are perhaps not so delicate as surveying instruments, nor is a faulty choice likely to cost you thousands of pounds. But the manufacture of good condensers most emphatically is the work of specialists, and a poor condenser will certainly ruin your reception of broadcasting and cost you many disappointing evenings.

Many thousands of constructors have found that in spite of appearance condensers *are* specialised instruments, and that best results can only be expected if they buy condensers backed by long specialised experience.

That explains why 60,000 Dubilier Condensers are sold each day throughout the world.

YOU should specify Dubilier.

DUBILIER
CONDENSER CO LTD

In replying to Advertisers, please use Order Form enclosed.



Yesterday

—the explorer braved hardships to chart the seas.

WUNCCELL DULL EMITTERS

- W.1. (For Detector and L.F. use). Operating at 1.8 volts ... 21/-
- W.2. (With red top) for H.F. use. Operating at 1.8 volts ... 21/-
- Types W.R.1 and W.R.2 as above but with resistance incorporated in base to operate off 2, 4 or 6-volt accumulator .. 23/6

The Wuncell is fully described in a comprehensive Folder which will be sent post free to any experimenter on receipt of a postcard. Don't invest in a Dull Emitter Valve until you have read about the Wuncell.


While the explorer of long ago had to set sail and face almost incredible hardships in his praiseworthy efforts to chart the globe, his successor sits by the fireside and logs Foreign Broadcasting Stations with almost absurd ease. From America to the borders of Russia and from Scandinavia to the shores of the Mediterranean the ether is available for his exploration.

But the man who is enthusiastic over long distance reception will see that he is not handicapped either by his Set or his Valves. His Set should employ at least one stage (and two for preference) of high-frequency

amplification, and for his Valves he should use those which have been specially developed for the work.

Undoubtedly the most popular high-frequency amplifier to-day is the Cossor P2—the valve with the red top. Hundreds of thousands of these valves are in use at this moment among all grades of wireless enthusiasts—from the expert to the novice—and everywhere it is giving the most complete satisfaction.

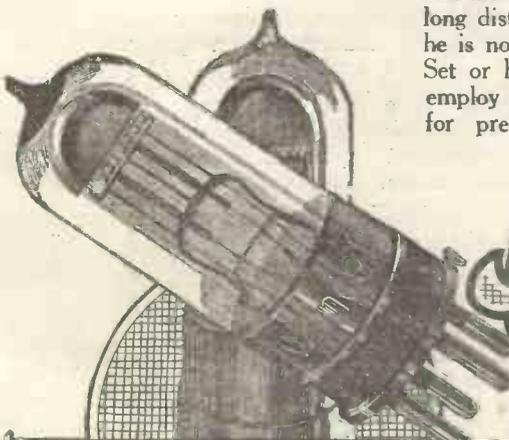Its striking success is undoubtedly due to its design. As every wireless enthusiast knows, the working of a valve depends upon the correct use being made of its electron emission.



Cossor

Get Cossor Valves—they cost no more

Advertisement of A. C. Cossor, Ltd. Highbury Grove, London, N. 5.



To-day

—he charts the ether from the comfort of his fireside.

You must have noticed that when your accumulator begins to fail and the filaments of your valves grow dim that your Set falls off in sensitiveness and volume. A clear case that the emission from the filaments has decreased.

Obviously, therefore, the quantity of the electron emission is an important factor in valve efficiency.

Now compare the Cossor P2 with an ordinary Valve. Instead of a hood-shaped Anode and Grid totally enclosing an arched filament and almost completely entrapping its electron stream, we see that at each

end of the tubular Anode the filament is exposed and that a large proportion of the electron stream is obviously leaking away. Remember that for high-frequency use you cannot afford to risk inefficiency—feeble oscillations from Stations thousands of miles away will strike your aerial and you'll be none the wiser if your Valves are not sensitive to them.

The remedy is in your hands—for high-frequency use select the Valve specially developed for the purpose and chosen by the vast majority of Valve users in this country—the wonderful Cossor P2.


COSSOR BRIGHT EMITTERS.

P.1. For Detector and use	Low-Frequency	12/6
P.2. (With red top). For H.F. use only ..		12/6

TO THE TRADE:

Have you received copies of the new Cossor Electrical Testing Showcard? If not, send in your application at once.

Valves

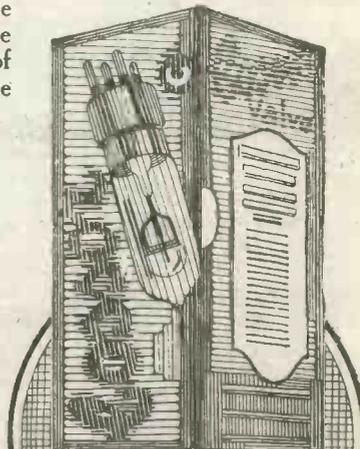

but what a difference in results!

In replying to Advertisers, please use Order Form enclosed.

Gilbert Ad. 1738

(Continued from page 745.)
 obtained in the presence of Mr. Clarabut, a prominent member of the Bedford Radio Society.

A separate table is shown giving the different values of condensers, etc., to obtain certain stations. I discarded the use of the constant aerial tuning condenser on this receiver, chiefly because I do not believe in a multi-stage H.F. circuit reducing the stabilising effect of an aerial. When first tuning in, the constant aerial tuning terminal, however, may be employed, although on a shorter wave length, including that on which 2LO works. I found that the reaction coil should be reversed, a No. 35 coil being employed. When the aerial was connected straight on to the aerial inductance, ordinary reaction, in all cases, improved signal strength. It must be remem-

bered, of course, that the nearest station was about 50 miles away.


Comparative Tests

Two aerials were tried. One was a single wire aerial of standard Post Office dimensions suspended at an average height of about 35 ft., and the other was a considerably smaller aerial about 65 ft. long and about 15 ft. high. The tests given in the table were made on the 100 ft. aerial, but very similar results were also obtained on the smaller aerial, although rather more careful tuning was necessary and signal strength was a little weaker. As, however, a number of the stations were obtained very well on the loud-speaker there was ample reserve of signal strength.

All the high-tension terminals were connected together, and 78

volts used. The valves used were of the general purpose type, one Cossor and three Ediswans being employed, although these were merely used because they were available and not for any technical reason. The last valve was occasionally replaced by a B₄ B.T.H. valve, or its dull emitter equivalent, the B₆. Both these valves are beautiful low-frequency amplifiers, and give improved strength, possible output and purity of reproduction. The Marconi Osram Company produce an equivalent valve, namely the D.E.5.

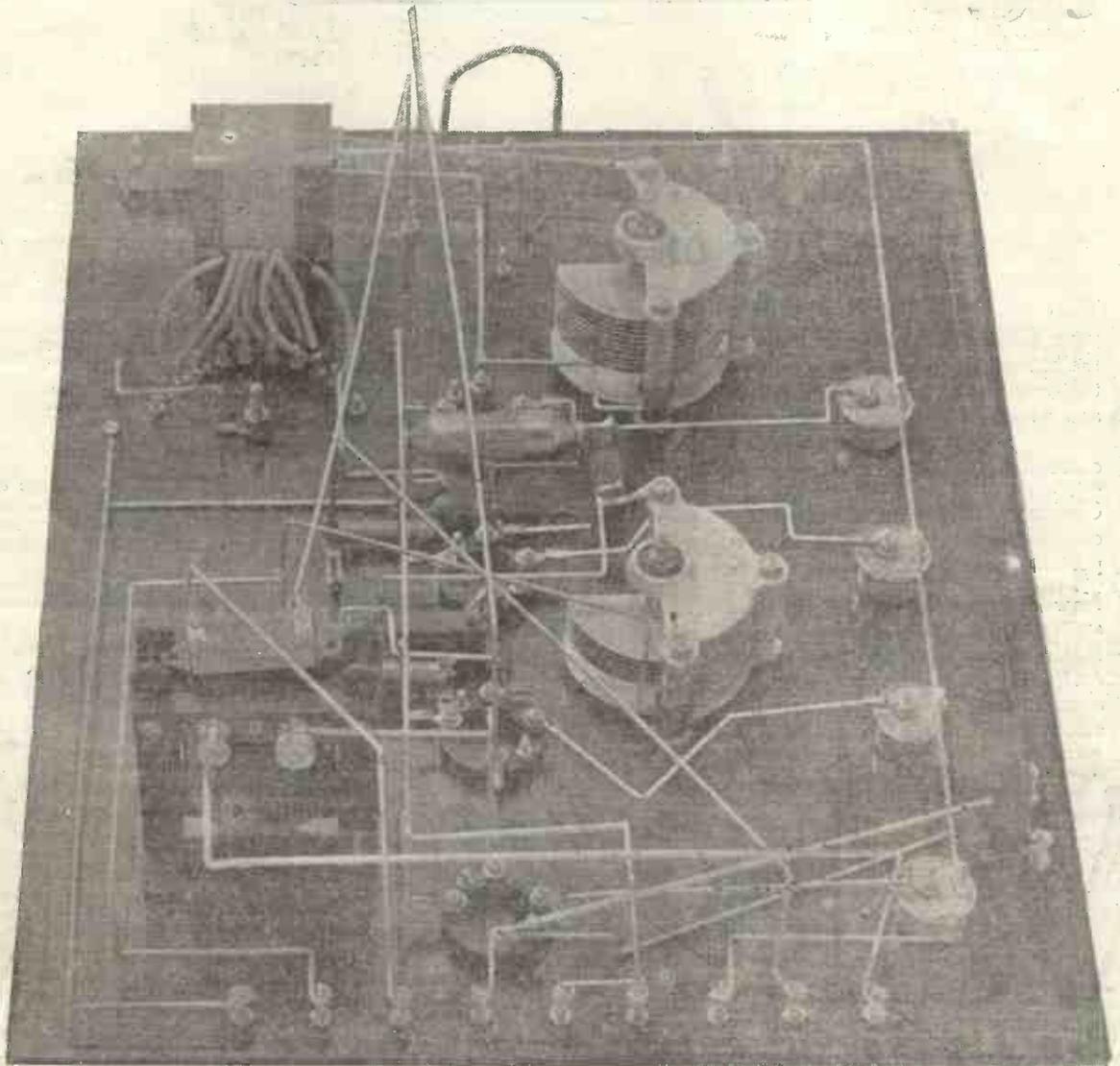I can strongly recommend the dull emitter valve, the B₆, which gives as good results as the B₄, but consumes much less filament current and costs about the same. I would not advise this valve for H.F. or detector purposes because the extra price does not justify any difference




This photograph shows the connections to the choke coil L 3.

As yet the effect of good filament control upon perfect reception is not fully appreciated. Try the difference between bad and good control by fitting the SHIPTON,

THE MOST PERFECT RHEOSTAT YET INTRODUCED

A special tension spring fitted on the spindle ensures a good, smooth contact. It is silent in use. Three models are available, so that whatever valve you may use there is a SHIPTON Rheostat to give you perfect filament control. Ask for it by name.

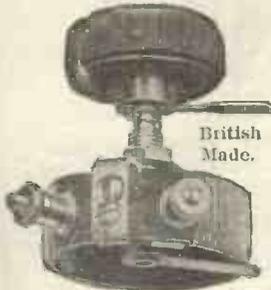The **SHIPTON New Type Strip Rheostat & Potentiometer**



British Made.

PROTECTS YOUR VALVES. However careful you may be, an occasion will arise when the H.T. will short across the filament. Avoid accidents by fitting the SHIPTON 7 ohm model which is fitted with a fuse. A spare fuse is packed in every box.

- SHIPTON New Type STRIP RHEOSTAT 7 ohm (with fuse) 3/-
- SHIPTON New Type STRIP RHEOSTAT 30 ohm - 3/-
- SHIPTON New Type STRIP RHEOSTAT 60 ohm - 3/-
- SHIPTON POTENTIOMETER 600 ohm - 4/6

Packed in neat linenette boxes.

Apply to your local dealer or direct giving your dealer's name and address

E. SHIPTON & CO., LTD.

37, Tothill Street, Westminster, S.W.1.


Telephone: Victoria 7. Telegrams: "Rentfones, Parl."

Also at 14, King Strast, Covent Garden W.C.

Barclays 322

THE FAMOUS FORMO

RADIO COMPONENTS

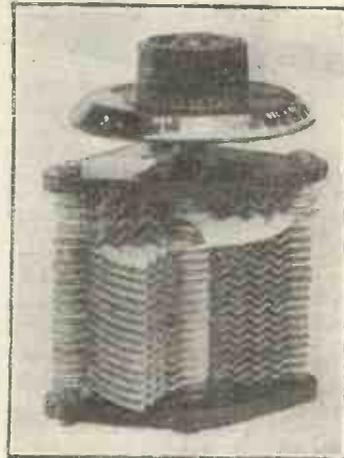

THE **FORMO-DENSOR** WITH **INTEGRAL VERNIER**

Coarse and Fine Tuning with **ONE MOVEMENT**

Supersedes so-called "Square Law"

BY GIVING

An Equally Efficient Wave Curve **BETTER RESULTS at LESS COST**

.001μF	10/6	.0003μF	8/6
.00075μF	10/-	.0002μF	7/6
.0005μF	9/6	3-plate Vernier	5/6
Dual, with Vernier	12/6	Dual, plain	10/6

The Dual Formo-Densor has two banks, each of .00025μF capacity.

FORMO TRANSFORMERS


are **WORLD RENOWNED** for their **CONSISTENT HIGH QUALITY** and **FINE PERFORMANCE.**

You take **NO risks** with **FORMO COMPONENTS** They are **UNCONDITIONALLY GUARANTEED**

Shielded Transformers.	
Ratio 1-5	18/-
" 1-4	
" 1-3	
" 1-2	
Telephone.	
Open Transformers.	
Ratio 1-5	12/6
" 1-3	

THE FORMO COMPANY

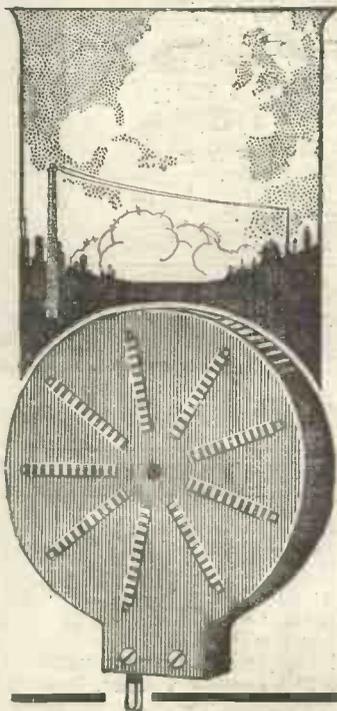(Arthur Preen & Co., Ltd.),
Contractors to the Admiralty, War Office, Air Ministry India Office, and Post Office.
Chief Offices and Works: Cricklewood Lane, N.W.2.
Scottish Branch: 22, York Place, Edinburgh. And at Birmingham, Newcastle, Manchester, Bournemouth.
Agents for Bristol and Cardiff: The Sloan Electrical Co., Bristol.



THE NEW RECEIVER UNITS

Illustrated and described in our new catalogue enable the public to purchase any type of receiver they fancy from a two- to a four-valve set, with the knowledge that they are obtaining the very latest practice at the minimum cost. Each Unit is complete in itself and is ready to instal by merely connecting it to its neighbour, and each has been especially designed for its particular work. The following is the list of the units which are being manufactured:—

- Unit No. 1.—Single Circuit Tuner.
- Unit No. 2.—Double Circuit Tuner.
- Unit No. 3.—H.F. Unit.
- Unit No. 4.—Detector and 1 L.F. Unit.
- Unit No. 5.—Detector and 2 L.F. Units.

The selectivity and efficiency of these Units are a revelation to those who have not heard Gumbrell Apparatus while their finish is of our usual high-class standard.

Full particulars are contained in our catalogue, which will be sent on request.

GAMBRELL BROS., LTD.

76, VICTORIA STREET, LONDON, S.W.1.


Works: MERTON ROAD, SOUTHFIELDS, S.W.18.

Phones: VICTORIA 9938; PUTNEY 3641-2.

West End Agent: J. V. Mulholland, 4, Blenheim St., New Bond St.; W.1. Mayfair 2686.

In replying to Advertisers, please use Order Form enclosed.

A NEUTRODYNE CONDENSER

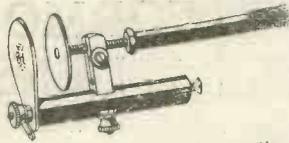

EVERY Neutrodyne Circuit needs a condenser whose minimum capacity is practically zero and whose maximum is less than the minimum of an ordinary condenser. The instrument illustrated fills these conditions. It has been carefully tested and yields admirable results in any Neutrodyne Circuit. The base rod and the operating spindle are of ebonite; the plates and standards are of heavy gauge brass. Fixing is by a single screw, with an additional $\frac{1}{2}$ in. hole in the panel for the operating spindle. Every detail of this production is up to the high standard demanded of Bowyer-Lowe Components. The price is exceptionally low.

PRICE 5/- EACH.

Each instrument is individually packed in a container bearing our name and trade-mark. Insist on seeing this before buying. Drilling template supplied.

"A SURFACE LIKE FINE PORCELAIN"




In these words a customer describes the first Bowyer-Lowe Panel he bought. Every Bowyer-Lowe Panel is finely finished, but what is more important, every one is guaranteed to be entirely free from metal and may be used without rubbing down.

BOWYER-LOWE TESTED RADIO PANELS

Sold in sealed packages. Semi Matt. $\frac{1}{4}$ d. p.r. sq. inch. Polished one side and all edges $\frac{1}{4}$ d. p.r. sq. inch. Drilled and engraved for Radio Press Set (except OMNI top panel) $\frac{1}{4}$ d. p.r. sq. inch. This knob $\frac{1}{4}$ inch in all cases. Order direct if your Dealer does not stock.

THE Set you make is just as good as the parts you put into it. Those who use Bowyer-Lowe parts obtain reception of unusually fine quality, because these components are all of the highest mechanical and electrical efficiency. Bowyer-Lowe parts make successful sets. Insist on having them. If your dealer cannot supply, order direct.

A STANDARD OF PERFORMANCE

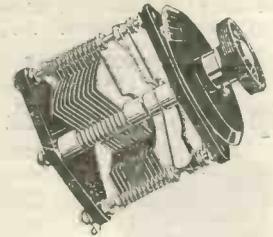

Prov. Pat. 7213/24.

MONEY cannot buy condensers of higher efficiency than the Bowyer-Lowe type. They have the highest capacity ratios in wireless, and as a result yield signals of a purity and volume not otherwise to be obtained. Install them in your sets and notice the difference they make. Tuning will be simplified, your wavelength range will be increased, and you will obtain reception free from distortion.

FOUR TYPES MADE.

- Standard, .0003 to .0015 m.f.
- Vernier, .0002 to .001 m.f.
- Double, .0001 to .0005 m.f.
- Triple, .0002 to .0003 m.f.
- Quadruple, made to order.

AT PRICES FROM 1/6


Order direct or from your Dealer.

Bowyer-Lowe Tested Components

Bowyer-Lowe Co. Ltd.

Sold by all Reliable Dealers

Letchworth

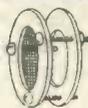

A BETTER VALVE WINDOW


Of heavily nickel-plated brass, Bezel rounded on outer and inner circumferences. Nuts, bolts, backing plate and gage supplied. Outer diameter $\frac{1}{2}$ in., inner diameter $\frac{1}{4}$ in. Each window individually packed in carton bearing our trade-mark.

Price 9d. each.



H.F. TRANSFORMERS.

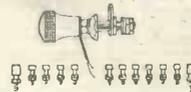You may buy at random any two Bowyer-Lowe Plug-in H.F. Transformers of the same range and they will match perfectly. There is no necessity to ask for special matching for H.F. Stages if you buy the standard transformers of guaranteed quality. All terminals clearly marked. All ranges at a uniform price. Particulars on request. Price 7/- each.



STUD SWITCH PARTS.

Complete sets of parts for Stud Switches, 2 to 10-way, with $\frac{1}{2}$ in. radius arms. Set comprises Switch Arm with Ebonite Knob, Bush, Contact Plate, 10 Studs with 2 Nuts each, and 2 Stops. Lacquered finish. Drilling template supplied. Sold in boxes bearing our name.

Price 2/3 complete.



ANTI-CAPACITY VALVE HOLDER.

Made at the suggestion of Mr. P. W. Harris in a form to give high efficiency, especially on short wavelengths. Can be fitted to Panel without nuts, as the ebonite base plate is tapped. Lacquered finish.

Price 1/2 complete.

in results, and the high capacity of the valve for H.F. work makes it unable to compete with the ordinary general purpose valve. For low-frequency amplification, however, it is very hard to beat.

From the table it will be seen that London (50 miles), Manchester (120 miles), Bournemouth (110 miles), Newcastle (200 miles), Glasgow (300 miles), Birmingham (65 miles), Aberdeen (350 miles), were all received perfectly well on a loud-speaker. I would like to say that telephone receivers were not employed during the whole test, which occupied about an hour.

Tuning on Loud Speaker

All the stations mentioned in the table were properly identified by their wavelength and the programme, and they were all tuned in by the aid of a loud-speaker only.

Manchester and Cardiff were subject to interference from 2LO, and the signals, while tunable on a loud-speaker, could not be said to be of loud-speaker strength. They have therefore been classified as good phone strength. It is a curious thing that these two stations are never heard very well in the south-east of this country, but readers in these two districts must not make the beginner's mistake of imagining that because the report on the signal strength was not glowing the set was in any way not to blame. In a different part of the country the results would probably be entirely different.

It will be seen that Lissen and Tangent coils were employed, but there is no particular reason for using these coils; both types of coils, of course, are of excellent make, but it must not be assumed because they were used on this occasion that there was any technical reason for so employing them.

Chelmsford

Chelmsford, of course, came in very well on almost any kind of an aerial, but there was no very large difference in signal strength between choke coupling (a 300 turn choke was found best) and the 100,000 ohm resistance, which may also be connected in circuit as an alternative when working on wavelengths above about 1,000 metres.

In addition to the stations mentioned, two German stations working on about 440 metres and 380 metres were heard on the loud-speaker. These were not identifiable in view of the short time available. Two relay stations of the B.B.C. were also heard, but they were not identified.

In all cases reaction helped greatly, and except when receiving Chelmsford a No. 35 turn coil was used throughout.

In this table the condenser readings are only approximate. Most of the stations were so loud that the same signal strength was obtained over several degrees of the condensers, although with the exception of Cardiff and Man-

chester each station was received without interference from any of the others.

Where there may be an apparent discrepancy in the condenser readings, as, for example, where two readings appear too close together when considering the wavelength difference between the stations, it must be remembered that the different readings were obtained at different times, and that the reaction was adjusted in each case to obtain the best results, the reaction adjustment, of course, altering the tuning of the circuit.


No grid bias at all was used, although, no doubt, it would have been preferable to have given about 1½ volts negative to the grids of the amplifying valves.

Parallel Tuning

In all cases a parallel condenser was employed, the C.A.T. condenser not being used. The table shows the number of the stud employed on the specially wound choke coil, and also the number of the plug-in coil connected in series when such a coil was used. In some cases no additional coil was used, and consequently the coil holder was shorted by a dummy shorting plug. The number of the stud used was not critical, and consequently no special deduction should be made regarding the relationship between the stud used and the wavelength of the station received on that stud.

TABULATED TEST RESULTS.

Call Sign and Wavelength.	Name.	Distance. Mils.	Aerial Coil.	Aerial Condenser	1st Anode Coil.	2nd Anode Coil.	2nd Anode Condens.	Reaction Coil.	Results.
5 WA 351 m.	Cardiff	120	35 Lissen	30°	Stud 6, Plug shorted	50 Lissen	83°	35 Lissen	Good phone strength.
2 LO 365 m.	London	50	35 Tangent	35°	Stud 7, Plug shorted	50 "	64°	35 "	Very good loud-speaker.
2 ZY 375 m.	Manchester	120	35 "	45°	Stud 7, Plug shorted	75 "	27°	35 "	Good phone strength.
6 BM 385 m.	Bournemouth	110	35 "	55°	Stud 10, Plug shorted	75 "	30°	35 "	Good loud-speaker.
5 NO 400 m.	Newcastle	200	50 "	nearly 0°	Stud 7, Lissen 75	75 "	64°	35 "	Medium loud-speaker.
5 SC 420 m.	Glasgow	300	50 "	3°	Stud 8, 75 Lissen	75 "	39°	35 "	Medium loud-speaker.
5 IT 475 m.	Birmingham	65	50 "	8°	Stud 7, 50 Lissen	75 "	55°	35 "	Very good loud-speaker.
2 BD 495 m.	Aberdeen	350	50 "	13°	Stud 10, 50 or 75 Lissen	75 "	63°	35 "	Good loud-speaker.
440 m.	German Station		50 Lissen	10°	Stud 10, 75 Lissen	75 "	47°	35 "	Medium loud-speaker.
380 m.	" "		35 "	55°	Stud 7, 75 Lissen	75 "	28°	35 "	Medium loud-speaker.
5 XX 1,600 m.	Chelmsford	45	150 "	3°	Resistance or 300 Lissen (any stud).	200 "	70°	150 "	Very good loud-speaker.

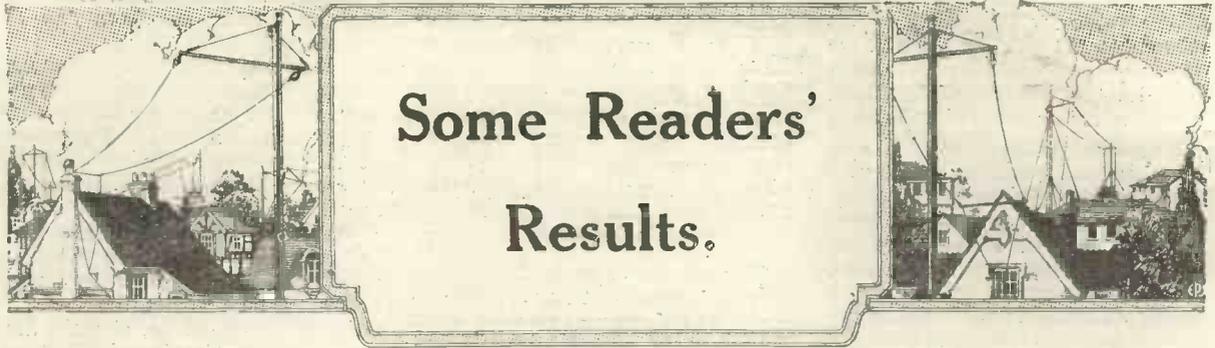

Some Readers' Results.

The No. 3 Envelope

To the Editor of MODERN WIRELESS.

SIR,—I recently purchased your Envelope No. 3 (How to Construct the "Simplicity" Three-valve Set). I followed the instructions contained, and have completed a set which is giving satisfaction beyond expectations. I get all B.B.C. stations, also several stations in France and Germany, with very good results. The earphones, when placed on the table, give the effect of a loud-speaker, which can be heard all through the house. I cannot speak too highly of the results obtained.

Hoping your R.P. envelopes will have a wide circulation.—Yours truly,

W. BAKER.

Hornden, Co. Durham.

The 3-Valve Dual

To the Editor of MODERN WIRELESS.

SIR,—Re your three-valve dual as described in MODERN WIRELESS, April, 1924, you will be glad to hear some of the results obtained. Having built several of your sets for myself and friends (my first being a three-valve set out of MODERN WIRELESS, March, 1923), I was so struck with the three-valve dual that I decided to convert my own and also to assist a friend to convert his. Result—all the B.B.C. stations on loud-speaker, practically all the Continental stations on the loud speaker—Manchester, Birmingham 5XX, Radio-Paris and Berlin—with great volume; in fact, they could be heard quite clearly 300 yards from the speaker. On Monday evening at 11.10 p.m. I was fishing around for anything, when I tuned-in a station on a wavelength between 400 and 500 metres. It was probably a Spanish station, as it did not sound like French. It was transmitting till 12.30 a.m. Tuesday morning, and appeared to come from some opera house or concert hall.

The station then closed down, and I could not get the call sign, as it was so distorted, and I could not get it clear, as the least touch on

condensers or filament and the carrier wave was gone; it was practically as loud as Birmingham. I got on with another station, but could not tune-in, as it was very critical and set was going into violent oscillation over or under the wave. At 1.25 a.m. I was fishing around and, to my surprise, I heard the announcer say "WGY, General Electric Co., Schenectady; stand by one moment," then "WGY Orchestra will now play a piece of the opera called —," It sounded like "Mal Gall" to me; anyway,

speech, which concluded at 2.35 a.m., when the announcer said that WGY was closing down. The above was very clear, and I could have got it through the loud-speaker, as it came through in great volume in the headphones. A cup of tea after the excitement, and then another fish round. At 9 minutes to 3 a.m. a fox-trot suddenly came in, and then the announcer said "WHAZ," pianoforte solo, announcer; 3.10, man singing "Old Kentucky Home," announcer, another song called "Just a Song at Twilight"



An exterior view of the Nauen Station which now transmits on short-waves.

the music was very clear; at 1.30, song, piano and soprano; 1.35 a.m., piano and soprano again; 1.42, 'cello or violin; 1.45, 'cello or violin; 1.50, WGY Orchestra; 1.55 piano and soprano again; 2 a.m., announcer said: "This concludes our programme for studio. We are now going to relay Mr. Charles Davies' Democrat candidate speech from the Albany, New York"; 2.9 a.m., chairman announcing speaker, band or orchestra struck up with "The Star Spangled Banner"; 2.12 a.m., Mr. Davies'

3.18, comic song with what I should call step time at the end of the song, announcer; 3.30, fox-trot, announcer, fox-trot called "Somebody Stole My Girl," and then I switched off as I had had enough excitement for one night.


I think it is the best three-valve set that has been before the public for all-round work; in fact, nothing to beat it with three valves.

Wishing yourself and MODERN WIRELESS the success that you deserve.—Yours truly, F. JONES.

Penketh.



Louden

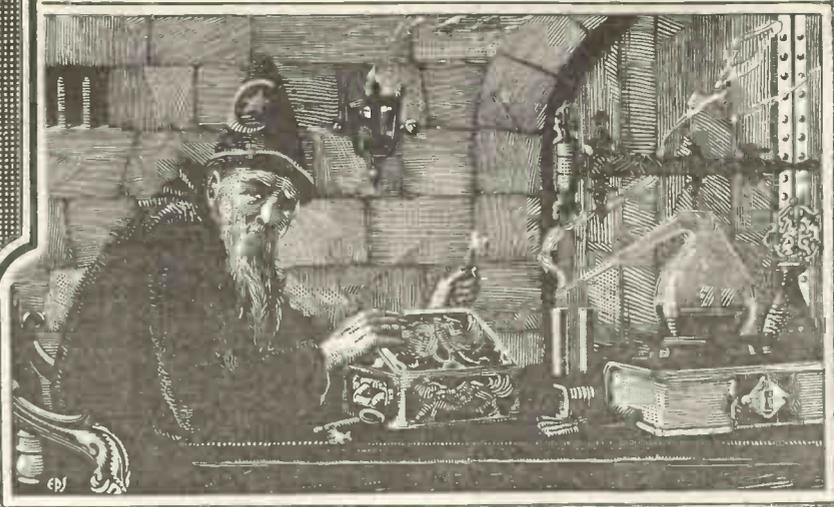

The Secret

10/-

Magicians and Sorcerers had their "Secrets of Healing" and "Secrets of Success," which they would dispense for a consideration, but in these less romantic times success is more apt to be won on sheer merit.

Take the case of the Louden Valve. Four months ago it was unheard of—to-day there are thousands of enthusiastic "slaves of the lamp" who will never go back to the old type of valve.

Why? Well, because however you consider the Louden Valve it is a sound investment.

It costs only ten shillings. It takes so little current that your accumulators will last twice as long as they do with ordinary

bright filament valves, and in spite of the fact that the anode is "full of holes" volume is, if anything, above the normal, showing that a full use is made of the electron stream.

It is the *unwanted* charges that escape through the turns of the anode, and strangely enough this is precisely what we intend to happen.

It gives a silver clear reproduction which is the delight of all who have heard it, and the life of the filament is exceptionally long.

So naturally the Louden is outstripping all other valves in popularity.

There is no secret—only merit.

**Louden
VALVES**



The Plain Louden for
Detecting and Low Fre-
quency Amplifying.

The Blue Louden for
H.F. Amplification.

Filament Volts .. 4.8-5
Filament Amps. ... 0.4
Anode Volts .. 40-80

**FELLOWS
WIRELESS**

Manufactured throughout
in Great Britain.

All Loudens are silver
clear and free from mush.

The current consumption
is very low and the life long.


Louden Valves - Silver Clear

ADVT. OF THE FELLOWS MAGNETO CO., LTD., PARK ROYAL, LONDON, N.W.16.

E.P.S.6.

In replying to Advertisers, please use Order Form enclosed.

The New Valve

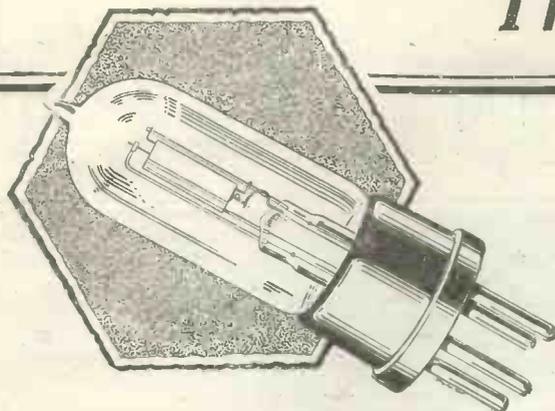

The "Cosmos" Type D.E. 11 Dull-Emitter Valve is the result of prolonged experiment and research. Thoroughly tested and tried out and manufactured commercially at their Cosmos Lamp Works at Brimsdown, the Metropolitan-Vickers Electrical Company Limited now confidently offer it to the public as being characteristically reliable and efficient.

COSMOS
D.E 11 VALVE

Here are Six Reasons why you should use this new "Dry Battery" valve:

CHARACTERISTICS :

- Low Capacity Cap
- Standard 4-pin contacts
- Filament Voltage 1.3 V.
- Filament Current 0.25A
- Anode Volts (Detector) 20-45 V.
- Anode Volts (Amplifier) 40-100 V.
- Amplification 6.5

PRICE

25/-

from all Wireless dealers.

Ask your dealer for a copy of the leaflet D.S. 4117/3.

- 1—The Filament "lights" off a single Dry Cell
- 2—It has a robust filament which is practically unbreakable
- 3—It has a remarkably long life, due to its platinum filament, heavily coated with active material
- 4—It is a highly sensitive valve for all reception purposes... ..
- 5—It is an exceptionally good Amplifier, being capable of handling considerable output without distortion
- 6—It is the best "Dry Battery" Valve for Loud Speaker work

COSMOS
DULL EMITTER
TYPE D.E 11
VALVE

The Valve that is



"Crystal Clear."

Advertisement of Metro - Vick Supplies Ltd., London.

R
Voz

Some New Radio Press Activities

This article makes clear to new readers some of the facilities which Radio Press affords to its adherents.

Readers who have already bought one or more of the Radio Press envelopes will welcome the two new envelopes that have just appeared; while for those who have not yet tried them they present an excellent opportunity of discovering their great utility. These two envelopes are Nos. 8 and 9.


Envelope No. 8

Envelope No. 8 contains complete instructions for the construction of a single-valve reflex set, by Herbert K. Simpson. This circuit is one that has proved itself extraordinarily popular with our readers, probably for two reasons. First, it gives not far short of "three-valve" results with the consumption and ease of control of one valve only; and, secondly, as it employs a crystal detector, the quality of reproduction is very good. The single-valve reflex stands in a class by itself, for it is a set that is very stable in action and yet extremely sensitive. Here in London it has been possible not only once but several times to receive Birmingham on a reflex set with a frame aerial only two feet square, and other stations have also been received at times, while 2I.O. is just clearly audible in the loud-speaker. The set described employs two condensers for tuning; one, the aerial tuning condenser, tunes the aerial circuit, and a plug-in coil of any size suitable to the particular station you wish to receive can be employed; the high-frequency amplification is obtained by means of a plug-in high-frequency transformer the secondary of which is tuned by the other variable condenser. The filament current is controlled by a rheostat that can be used either for bright or dull emitters. This is a set that will prove of great interest to any experimenter who has not yet made up a receiver on these lines, while the beginner who wishes to try out this circuit will find the detailed instructions given will

enable him to complete a set from which he can obtain valuable experience with the certainty of making a success of it.


Envelope No. 9

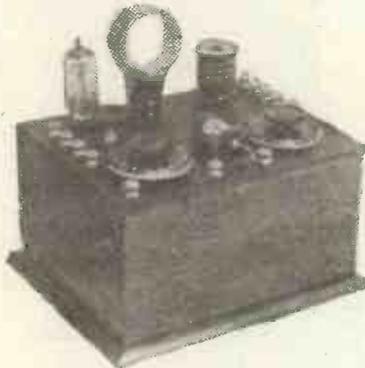Envelope No. 9, by the same author, gives all the necessary directions for making an efficient single-valve receiver. Although many hundreds of circuits have appeared from time to time, the



A Single Valve Reflex Set

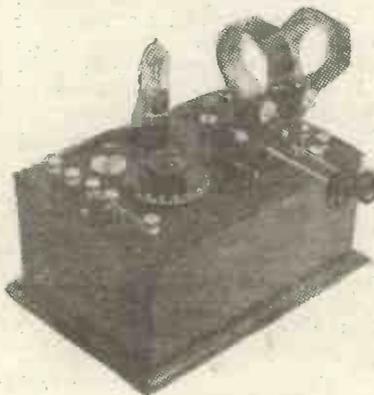single-valve set, or "one-valver" still retains a large measure of popularity because of the reliable and efficient results that can be obtained with it. It is one of the easiest sets to handle after the humble crystal set, and owing to the employment of reaction is extremely



An Efficient Single Valve Set

sensitive. In this set reaction is magnetic, and the usual two-coil holder serves to couple the reaction coil to the aerial coil. Terminals are provided for constant aerial tuning, the advantages of which are too well known now to require further comment or explanation. A further refinement is provided in the form of a variable grid-leak; this will be found of help in making final adjustments when receiving distant or weak transmissions. The filament resistance is designed to control either dull or bright emitters. With this set, favourable conditions obtaining, all the B.B.C. stations can be received on an average P.M.G. aerial, and many Continental stations as well. While if the constructor goes to the trouble of making himself special short-wave coils, he can always find many transmissions of interest down on the short waves, and it is even possible to receive KDKA on a single valve under favourable conditions.

Both the above receivers have already been built by our readers, and many extremely favourable reports have been received. They are simple to construct, and the exact and detailed directions given enable even the veriest novice to build either of these sets and be sure of success.

Radio Press Transfers

How many an experimenter has looked at a finished set with pride and thought: "If only I could get this engraved cheaply and without trouble." This is now possible. Results equal in every way to engraving can be obtained by a means which he can employ himself. The Radio Press Transfers, costing but a humble sixpence, provide him with an adequate solution to this problem. Each set of transfers is placed in a sealed envelope for protection, and contains 80 different transfers. Full instructions are given how to apply them, and they can be put on to a set in a few minutes, and so give the completed instrument an

appearance of professional finish. Make sure when ordering transfers to get "Radio Press"; they have been specially produced for the amateur by men who know the experimenters' and constructors' every need.

The Wireless Constructor

No. 2 has now appeared, and will be found full of special articles, not only of interest to the beginner, but also containing helpful and useful tips for the more advanced amateur. By the way, get your copy at once, or you may be disappointed and find they are all sold out. Under the editorship of Percy W. Harris, this publication has been specially designed to meet the needs of the newcomer to the ranks of wireless enthusiasts, and any experimenter who knows of anyone just starting to learn about this fascinating subject should place a copy of the *Wireless Constructor* in his hands. The beginner will find articles giving full and detailed particulars with regard to the construction of a large variety of receiving sets. Not only are full dimensions, wiring diagrams and drilling diagrams provided, but tricky points in the constructional work are carefully explained and all possible difficulties dealt with. For the constructor with limited practical workshop knowledge there are articles which will tell him how to use the various tools that he is not familiar with and so enable him to put his best work into a set, not only improving its appearance but also its performance. If you have any constructional difficulties you should read the *Wireless Constructor*, and to make sure of obtaining your copy every month and not miss a single valuable issue, it would be advisable if you were to place a standing order with your stationer or direct with us. Why not fill in the order form enclosed with this issue of MODERN WIRELESS and post it to-day?

Our Blue Print Service

If you are contemplating building any valve set from a "single-valve" to a "five" it is now possible for you to obtain blue prints which have been made from the actual sets and original drawings of the author. The veriest beginner in wireless work is enabled to profit by the experience of technical wireless experts. The actual lay-out of the set is shown on one blue print which is full size, and can therefore be used as a drilling template, while the other gives a complete wiring diagram, which is copied direct from the original set itself, and is a full-size reproduction of the back of the

panel with all the connections appearing. These blue prints are 1s. 6d. each, post free, and will be found well worth this. We have started this service specially for the benefit of those readers who like to be able to obtain exact information of sets as made up by members of our technical staff. If you will write to the Sales Manager he will be pleased to send you a complete list of all these blue prints which cover every set from a five-valve receiver to a single-valve set, including many dual and reflex sets. From this list of over 70 sets you can choose just the set that is going

send you a complete report. This small charge we make is actually only a fraction of the cost to us for this highly-skilled work, and this offer is an earnest of the confidence we place in sets built and designed by our technical staff.

What Coil Shall I Use?

A good deal of doubt frequently arises as to the right size coils to use so as to receive a certain transmission. The Radio Press have published the MODERN WIRELESS Coil Table, by means of which this difficulty can be solved at a glance.

The various wavelengths em-



Mr. Kellaway, who has succeeded Mr. Godfrey Isaacs as managing director of Marconi's Wireless Telegraph Co., is here seen at his desk.

to meet your particular requirements. Write to-day and the list will come to you without delay.

The Special Test Department

So confident are we in the design of our sets and so sure that the public will find them satisfactory, that we have opened a special test department. This department is completely equipped with up-to-date precision instruments of various kinds.

Would it not be worth time and money to you to be able to benefit by the use of such apparatus in testing out a set that, for some reason or another, has proved faulty?


If, then, you make up a set from our design which you feel is not up to what you expected, you may send it to us and for the nominal sum of 2s. 6d. per valve we will test the set out thoroughly and

employed in broadcasting have been classified, and different makes of coils are given, together with their designating numbers or letters, covering different wavelengths. It is therefore only the work of a second to determine which coil is wanted for the reception of a desired transmission. In order that this table may be kept as a permanent record, it has been printed on stout card, and may be obtained at 6d. each. Other data and useful information can be obtained as to our series of books, and a card to the Sales Manager will bring you a list of these.


Readers will find a note elsewhere in this issue drawing their attention to the importance of using our special order form when purchasing articles advertised in our columns. Unless this is done, we cannot help the purchaser if any question should arise at any later date.

CONSTRUCT YOUR OWN SET

to Proved Designs.

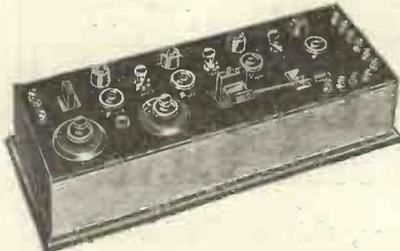

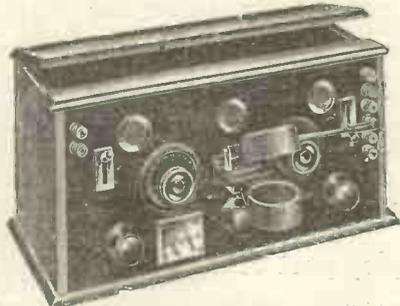CONSTRUCT THE 4-VALVE FAMILY for £9. (Envelope No. 2.)



CONSTRUCT THE ALL CONCERT de LUXE for £9 9s. Od. Including Sterling Condensers. (Envelope No. 4.)

RADIO PRESS ENVELOPES.

	Post free.
No. 1. S.T. 100	1/8
No. 2. 4-Valve Family	2/9
No. 3. Simplicity 3	2/9
No. 4. All Concert de Luxe	2/9
No. 8.	1/8
No. 9.	1/8
R.P. Hot Pad Transfers	8d.

1lb. Hank No. 16 D.C.C. Wire for P.W. Harris Crystal Set, **3/- post free.**

Anode Coil, tapped and complete, as used in the simplicity 3 and T.A.T. **8/- post free.**


Magnum H.F. Transformers, entirely new design **7/- each.**

Guaranteed Matched **14/- per pair.**


3-VALVE REINARTZ.

As described in this issue by Mr. Percy W. Harris.

	£	s.	d.
1 Polished Mahogany Cabinet, as described	0	13	6
1 Ebonite Panel, 12 by 10 by 1/2 Sq. Matt and Drilled	0	10	0
1 Igranic New Type Intervalve Transformer	1	1	0
1 Ferranti Do. Do. Do.	0	17	6
1 Magnum 3-Coil Holder	0	12	6
3 Igranic D.E. Filament Rheostats	1	1	0
3 H.T.C. Valve Holders, type C	0	4	6
2 Jackson Sq. Law Condensers, .0005	0	16	0
1 Bretwood Variable Grid Leak	0	3	0
1 Lissen Push-Pull Switch	0	2	9
13 Terminals, Lacquered and complete	0	2	2
1 Choke, as described	0	5	0
1 Dubilier Fixed Condenser, .0003	0	2	6
5 yards No. 16 Sq. Sec. T.C. Wire	0	0	7
1 Set Radio Press Transfers	0	0	6
	£6	12	6

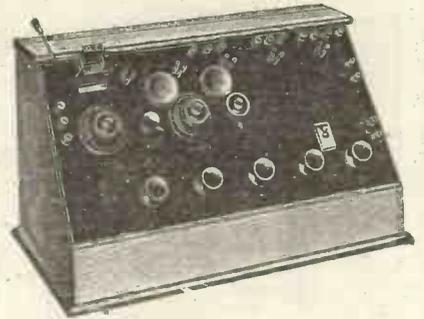

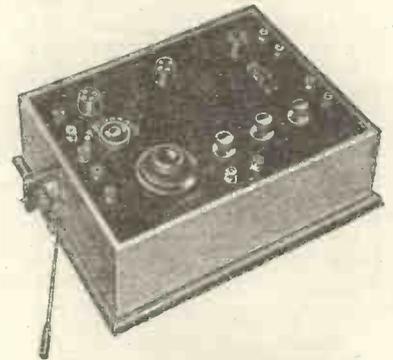CONSTRUCT THE TRANSATLANTIC V., £11 13s. 11d.



CONSTRUCT THE SIMPLICITY 3-VALVE for £4 13s. 2d. (Envelope No. 3.)

3-VALVE RECEIVER.

As described in this issue by Mr. Redpath.

	£	s.	d.
1 Polished Mahogany Cabinet, as described	1	5	0
1 Radion Mahogany Panel, 14 by 7 by 3-16, Drilled	0	13	6
1 Baseboard with Supports	0	2	6
2 U.S. Super Intervalve Transformers	1	17	0
1 Magnum 3-Coil Holder	0	12	6
3 Burndept Dual Rheostats	1	2	6
12 Valve Legs, complete	0	1	0
1 B. Lowe Sq. Law Condenser and Vernier, .0005	1	0	0
1 Ebonite Shelf with supporting Brackets Drilled	0	2	3
1 Nickel D.P.D.T. Utility Switch	0	5	6
3 Nickel Valve Windows	0	2	0
11 Nickel Terminals, complete	0	2	3
1 Nickel Connecticut Switch	0	2	3
1 Mansbridge Condenser, 1 mfd.	0	6	0
2 Dubilier Fixed Condensers, .002	0	6	0
1 Do. Do. Do. .001	0	3	0
1 Do. Do. Do. .0003	0	5	0
and Grid Leak, 2 meg.	0	5	0
6 yards No. 16 Sq. Sec. T.C. Wire	0	0	9
1 Set Radio Press Transfers	0	0	6
	£3	7	6

Carriage and Packing Free on RETAIL ORDERS value £2 and over.

BURNE-JONES & Co., Ltd.
Magnum House, 288, Borough High Street, LONDON, S.E.1.
Telephone: HOP 6257.

Send stamps for Illustrated List and set of leaflets dealing with S.T. 100, 4-Valve Family, Simplicity 3, All Concert de Luxe, Omni, Transatlantic 4, Transatlantic 5, Puriflex, All-Britain, 3-Valve Neutrodyne, Tri-Cell, P. W. Harris Crystal Set, Magnum Coils and Coil Holders.

MAGNUM COIL HOLDERS.
As used in Simplicity 3, All Concert de Luxe, Transatlantic 5, Puriflex, etc., etc. 2-way 9/6, 3-way 12/6. Post. 6d. When ordering Please state name of set.

MAGNUM TAPPED COIL.
No. 1 12/6. No. 2 15/-.
No. 1 equivalent to Nos. 23, 35, 50, 75 Plug-in coils.
No. 2 equivalent to Nos. 100, 150, 200, 250 Plug-in coils.

Barclays 354.

XMAS & NEW YEAR GREETINGS

TO ALL OUR CUSTOMERS AND THE BEST OF RECEPTION TO YOU IF YOU BUILD YOUR SET TO RADIO PRESS DESIGNS, USING

S.A.C. CABINETS, PANELS & COMPONENTS.

Send 2d. stamp for our new 100-page list and folder descriptive of Radio Press Sets.

Example.	Cabinet.	Ebonite Panel.	Radion Panel.
Transatlantic Four	26/-	14/-	17/6

(Packing and carriage extra)

All cabinets are best seasoned walnut, hand-made and polished. Panels are guaranteed electrically, edges squared, accurately drilled and engraved.

RADION PANELS A SPECIALTY.

"S. A. CUTTERS,"

15, Red Lion Square, London, W.C.1.
Phone: Chancery 8042.

H.T. EFFICIENCY AS IT "WASN'T ON WEDNESDAY"

Asked the meaning of the word revolution, a small boy said that it was "something on Saturday as it wasn't on Wednesday." "Hovimo" Connectors are a revolution in H.T. Efficiency. Their use avoids soldering and cheapens cost of complete battery by from 25 per cent. to 50 per cent. The "Hovimo" also ensures perfect "silent" working, is everlasting, allows easy replacement of units, will take ordinary wander-plug, and makes it possible to keep your H.T. at an equal voltage... British Made.



M. MOLBACK, 27, HIGH HOLBORN, LON.
DON, W.C.1.
Phone: Chancery 8391.

Ask your dealer for them.

1/6

Per Doz. From dealers or direct.





Columbia Radio "A" DRY CELLS

For all types of DULL EMITTER VALVES

DESIGNED especially for Wireless, this world-famed dry cell has been adopted as standard by leading valve manufacturers and is recommended by them for operating the filament of the various types of DULL EMITTER VALVES. Exhaustive laboratory tests have proved conclusively that the **Columbia** is not only the **BEST** but by far the most reliable, efficient and economical dry cell manufactured for filament heating.

Fixed List Price, 2/6 Sample, post free, 3/3

Ask your local dealer; or, if unable to supply, direct to Distributors,

Write for Descriptive Leaflet giving FIVE reasons why you should use these dry cells.

E. SHIPTON & CO., Ltd.,

37, Tothill Street, Westminster, S.W.1.
 'Phone—Victoria 7. 'Grams—'Rentfones,' Parl.
 Also at 14, KING STREET, COVENT GARDEN, W.C.1.
 Write for list of other SHIPTON Products. Trade Enquiries Invited.

T. O. BUSS

SCIENTIFIC INSTRUMENT MAKER

77, Clerkenwell Rd., London, E.C.1

Estb. 1850. Exhibition Awards: London, 1862; Sydney, 1879; Melbourne, 1880.

INTERVALVE TRANSFORMERS

Made like an Instrument by a Scientific Instrument Maker.



Correct priming impedance. Wound with correct gauge and quantity of wire. Heavy iron core to give good magnetic field—and will carry heavy currents.

PRICE
18/6

Ratio 5 to 1.

MADE LIKE AN INSTRUMENT.

This instrument is thoroughly tested and is **GUARANTEED FOR TWO YEARS.**

Barclays 353



'TURRET'
Columbian Pine Masts
2,000 IN USE:

Designed by Nava Experts.

27 ft. Turret Two complete	44/6
28 ft. Turret Super Mast	59/6
36 ft. in 3 sections	79/6
42 ft. Telescopic Mast	84/-
45 ft. Super Telescopic	90/6
55 ft. Doubly Telescopic	£6/15/6
58 ft. Super Mast	£3/19/6

Light, neat and efficient. The telescopic sections enable the 42ft. to be erected as a soft, and the 48ft. as a 35ft. Mast—Send for List, or phone Gerrard 2650

SIMPSON & BLYTHE, 8-9, Sherwood St., Piccadilly, W.



Ask your LOCAL RETAILER for the **"SIMPLEX"**

Lead-in Strip. No holes to bore, no tools required.
1/6. Postage 2d.

THE **"MORRIS"** (all-steel) Valve Template. Saves TIME, TEMPER and EBONITE.
10½d. post free.

J. O. NICHOL & CO.,
46, Lancaster Avenue, Fennel St., Manchester. Tel.: City 1769.



"Sparta" Crystal Receiver.

A neat little crystal receiver, enclosed in an imitation leather case only 6½ in. by 4½ in. in size, has been submitted by Messrs. Fuller's United Electric Works, Ltd. The tuning is by a flat basket-coil type of variometer with limited angular movement; two alternative earth connections are provided which correspond to different tapping-points in the tuning inductances, and thus provide two ranges of tuning for aerials of different characteristics. Provision is made for a loading coil for the 1,600 metre station, a short-circuiting loop being normally inserted in its place. Two phone terminals only are supplied. We would like especially to commend the crystal detector incorporated in this set; the crystal—quite a small fragment suffices—is held by a spring plunger which allows of immediate adjustment or replacement, a hinged cover protecting the crystal when not in use; a cat's whisker mounting is adopted which is at the same time firm and extremely versatile in its setting. The aerial and earth connections are of the plug-in type, and adapted for shorting the aerial when not in use by simply inserting the one plug in the end of the other, after removing them from the set. We think, though, that the majority of broadcast listeners would prefer to be able to close down the box-lid without altering any connections.

The wave-length range, on test, proved to be from about 310 to 485 metres on the "Short" terminal range, and from 425 to 700 metres on the "Long" with a standard P.M.G. aerial of .0003 μ F capacity; or from below 300 to

420 metres on an aerial-capacity of .0001 μ F, corresponding to a small aerial, e.g., a short and well-isolated indoor one. With the loading-coil, and on a P.M.G. aerial, the tuning-range was (on the "Long" arrangement) from about 1,470 to just above 1,600 metres.

In practical tests in actual reception, on a moderate indoor

At the same point, 5XX (which is at practically the same distance) gave excellent phone strength, and a value of about 6 microamperes. The tuning in the latter case was not sharp, the variometer adjustment making but little difference when the small enclosed loading-coil provided with the instrument had been inserted. The general appearance and the finish of the instrument are excellent.



The "Sparta" crystal receiver.

aerial 6 miles from 2LO, the signals were quite comfortably strong on more than one pair of phones: 5XX was just audible here. At 35 miles out in the country, on a low 70 ft. test aerial, London came in at quite good strength in the evening, the signal-strength measuring up to a good proportion of the standard as determined on the same aerial, i.e., about 1¼ microamperes in this case, for the whole rectified wave.

"Uralium" Crystal.

Specimens of "Uralium" crystal, marketed together with a special cat's whisker in small boxes with a transparent cover, which is at the same time a seal, have been submitted to us for test by Messrs. G. Street and Co., Ltd. This crystal is a bright, rather coarse-granular type of synthetic galena. On test, it gave really excellent results, the sensitive spots being very plentiful, and the crystal gave on cutting a fresh surface equally good results. It was not unduly brittle. We would like especially to commend the cat's whisker, described as "silver," supplied with each crystal. This is of just the right degree of springiness and fineness of point. Actual measurement shows but little difference between cat's whiskers of varying materials; but the physical conditions are of great importance, and this whisker appears to have been adjusted accurately in this respect. Some little care is necessary in mounting it in some types of holders, as the wire was found to be rather brittle. We can strongly recommend this combination of crystal and cat's whisker for distant crystal reception.

NO AERIAL

EARTH ACCUMULATORS, OR OUTSIDE CONNECTIONS REQUIRED FOR THE

"Rolls" Portable

It is no longer necessary to disfigure your house with an unsightly aerial or to drape your rooms with a multitude of wires.



THE SIMPLEST, NEATEST, CUTEST, CLEVEREST, MOST EFFICIENT AND MOST PORTABLE 2-VALVE SET IN THE WORLD. EXQUISITELY FINISHED AND FITTED IN A REAL HIDE CASE. Size 15 by 11 by 5 ins.

PRICE **£14 14 0**

COMPLETE. ALL READY FOR USE AND MARCONI ROYALTIES PAID.

No Complicated Controls and no Knowledge of Wireless Required.

ABSOLUTELY UNAFFECTED BY LIGHTNING.

Write, 'phone or call for further particulars. Demonstrations anywhere at any time.

3-Valve Model guaranteed to work a loud-speaker really well anywhere within 10 miles of a Broadcast Station. Price £18 18s. 0d. No Extras.

Purchase out of Locom can be arranged.

All parts for "M.W." and "W.C." Circuits stocked. Quotations by return of post.

Bargains in Second-hand SPEAKERS, PHONES, TRANSFORMERS, Etc.

(Everything sold guaranteed perfect.)

WE WILL BUY OR TAKE IN PART EXCHANGE ANY FIRST-CLASS BRITISH GOODS

(except Valves). Ask for Special List.

WE ARE SPECIAL AGENTS FOR—

CROIX TRANSFORMERS,

06 RADIO VALVES,

AIRMAX COILS,

LION DETECTORS,

INSULITE PANELS (Black and White), ETC.

See our Advertisement in November issue "Modern Wireless," page 719.

See our Advertisement in November issue "Wireless Constructor," page 719.

DEALERS! Write for Lists, Trade Terms and particulars of Agency for your district. Good Terms.

ONE THOUSAND AGENTS WANTED.

H. LLOYD MARSHALL & CO.

5, WESTMORELAND BUILDINGS, E.C.1.

"Britezite" Crystal.

Some specimens of their "Britezite" synthetic galena type of crystal have been sent us for test by Messrs. British Central Electrical Co., Ltd. These were of medium coarseness of texture, and rather duller than usual in appearance. On trial, the behaviour was somewhat erratic, some pieces having an excellent proportion of good spots which (in actual reception with measurement of resulting signal-strength) were up to the standard of good galena; whilst other pieces were not of the same order. The crystal was rather brittle to cut.

Variable Grid-Leak

The general experience of variable grid-leaks is that their most conspicuous property is variability; certainly, but usually not a conveniently and permanently controllable variation over a desirable range of resistance. A type of variable grid-leak which seems to bid fair to overcome some of the weaknesses of many of the existing varieties is the "Panleak," samples of which have been submitted for test by Messrs. A. H. Hunt, Ltd. This is of the step-by-step variety, giving by a 7-point switch a convenient choice of leak values, the ranges quoted by the makers being from $\frac{1}{2}$ to 5 megohms, from 0 to 3, and from 0 to 8 megohms, with a special model rated at 10,000 to 100,000 ohms.

Those submitted were in the form of a small square of insulating composition a little over 2 in. square, adapted for fastening behind the panel by four small bolts and with a centre spindle which is taken through the panel and carries the controlling knob. The latter is knotted deeply to engage with a special anti-capacity extension handle 5 in. long, supplied with the instrument. The 7-point switch is in the rear. Small terminal nuts are provided, which might with advantage be made rather larger for experimental work. The contact finger is kept up to its work by a strong spiral spring, and is apparently intended to be secured on a D-shaped spindle-end, to prevent working loose in use. In one of the samples submitted, on removing the small screw at this end (as is necessary in order to pass the spindle through the panel in mounting it thereon) it was found that this had not been properly fitted, and the small screw stripped its thread when efforts were made to secure the finger again. This

was easily remedied, and the screw replaced by a somewhat longer one. The instrument then operated correctly and gave a range from about $\frac{1}{2}$ to 7 megohms on test; another sample tested from .8 minimum to about 10 megohms maximum, in each case by six convenient steps. The resistance-values appeared to be reproducible with reasonable accuracy, and a continuous current of 10 microamperes through the whole resistance made a difference of the order of 10 per cent. only in



A photograph of the variable grid-leak with its extension handle.

some hours. As far as it is possible to tell by a strenuous laboratory test of necessarily somewhat short duration, and by trial in critical circuits (such as "grid-leak-howl" types of "super" circuits), it would appear as if these variable grid-leaks possess the elements of success.

Substitute Filament Resistance

In cases where low consumption valves (e.g., of the 06 D.E. type) have replaced the more greedy bright emitters it is generally necessary to replace the old filament resistances with new ones of considerably higher value, or else to introduce a high external resistance, thereby abandoning any appreciable power of control over filament temperature by means of the original filament resistances. Messrs. Ward and Goldstone, Ltd., have just brought out a substitute resistance fitting, intended to replace the old low-resistance spiral of the usual type in circular filament rheostats, and with a suitable

value for controlling dull-emitter valves, which promises to get over this difficulty in a very simple way.

Samples submitted to us consisted of a spiral of fine resistance wire, with a maximum value of around 20 ohms, wound on a pliable cylindrical asbestos core of about $\frac{1}{4}$ in. diameter. This is bent round the usual circular grooved former in place of the old spiral; the core is soft enough to permit of good contact with the resistance brush, whilst at the same time providing a heat-proof mechanical support for the fine wire.

With reasonably careful fitting this substitute resistance should give a satisfactory solution of the problem provided by a change over to dull emitter valves.

"Amplifytone" Aerials.

Another pattern of copper-ribbon aerial material, to replace the customary 7.22's cable, is included in the "Amplifytone" aerial outfit submitted by Messrs. United Manufacturers and Agency, Ltd. The outfit consists of a cardboard box containing a 100-foot roll of thin $\frac{1}{4}$ in. copper tape, a 10 in. lead-in insulated with rubber tubing, insulators, and copper sleeves for securing loose ends in a simple manner. The aerial was tested in a similar manner to that in which other ribbon aerials have been investigated, by direct comparison of signal strength on crystal and a two-valve reaction set, measuring resulting signal strength directly and comparing reaction requirements and aerial capacity with this aerial and an exactly similar one of a standard material hoisted rapidly in its place. In this case, stranded thinly-insulated aerial wire was used for comparison. With the phones in series with the microammeter the crystal signal strength (from 2LO, 35 miles away, with an aerial about 70 feet long and 25 feet high, in a good geographical position but locally screened), with the standard low-resistance crystal-tuner and an excellent galena crystal, was 2.5 microamperes with the stranded wire, and 3 microamperes with the ribbon. With low-resistance microammeter alone, the figures were 3.5 and 4 microamperes respectively. The difference in audio signal strength, as judged by casual aural observation, was naturally inappreciable. With the two-valve reaction set there was no measurable difference in audio signal strength (as measured in mean (R.M.S.) volts across the phones, on a fairly uniform transmission) between the two aerials,

though a slightly higher capacity and lower reaction demand was noticed with the copper ribbon.

That there was nothing to be gained by a further increase in the cross-section or area of a single element (without spacing by cage or cross-bar) was shown by the fact that the two aerials when hoisted together practically in contact, after adjusting for the increased capacity, gave exactly the same crystal strength as the $\frac{1}{4}$ in. ribbon alone. The effective resistance of the aerial is already so low with the standard type of wire that there is little margin for improvement in reception; resistance-damping and other losses elsewhere are predominant.

With this reservation, it is evident that the "aerial outfit" provides a convenient equipment for the erection of an aerial of low resistance. The greater wind-resistance of the ribbon should be taken into account in putting up the aerial outdoors.

"Lydden" Crystal Detector

A practical point in crystal-reception which is very often overlooked by the makers of component parts is that of rapidity and ease in changing the all-important crystal. The result is that crystals are very seldom changed as often as they should be, and a low general standard of reception is perforce tolerated.

In the "Lydden" crystal detector, a sample of which has been sent us by John T. Nichols, a special point is made of ease in changing the crystal. The instrument is of the vertical type, glass-enclosed; but the whole top, carrying whisker-holder and cover, is held down on the panel, over, but not mechanically connected to, the crystal-cup, by a single terminal milled-head nut. The cup base is a fixture in the panel, a single screw in its base ensuring this; and the stud on which the terminal-head screws is also a fixture, and provides the second electrical connection necessary. The crystal is held simply in a cage which screws easily over the fixed cup-base. As a result of this ingenious mechanism, the crystal can be got at and removed in five seconds by actual trial, although it is thoroughly protected and securely held. The broad ebonite base of the top portion imparts adequate steadiness to the whisker-holder with the fixing nut only lightly screwed up.

The whisker holder has the usual ball and socket universal joint, but with adjustable spring pressure on


Tuning Methods.

The first consideration when designing a new set, whether it be a single circuit crystal or a multi-valve "super-net" is to select the right means of tuning, because if the tuner is inefficient no care in the rest of the set can compensate for it.

Tuning coils may be divided into Slider and Tapped coils, variometers and the movable coils, which plug into a coil holder of which there are a multitude of types manufactured. The first two types are very efficient if wound for use on a definite wave length, but their size on anything but the shorter waves make them impossible to incorporate in a set, and if used over a wide range the "dead-end" effect causes serious losses. Sliders almost always cause trouble from imperfect contact and stud switches frequently develop similar faults. Added to this is the serious difficulty when building this type of coil into a set of arranging for an efficient and adjustable coupling for the secondary and reaction coils.

Experience proves that the plug-in inductance with a two- or three-way coil holder is the most convenient to use and the most efficient if a suitable form of coil and a properly designed coil holder are used. The ease with which one can change from one wave length to another by simply changing coils and the exactness with which one can arrange the secondary and reaction circuits by plugging in suitable coils give the maximum results with a minimum of trouble.

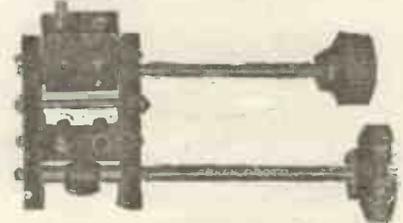No coil holders are better made or more efficient than those manufactured by the GOSWELL ENGINEERING CO., LTD., who stock over twenty different kinds to suit all tastes and pockets, their CAM-OPERATED VERNIER COIL HOLDER has a separate handle for adjusting a particularly sensitive fine tuning attachment.



This coil holder used in conjunction with the **Quality** Duplex RADIO

Basket Coils, mounted on standard plugs, will give you perfection in tuning. All these coils and coil-holders can be supplied fitted with a patented Reaction Reverse Switch which is a great convenience and saves much complicated wiring. Advertisement of GOSWELL ENGINEERING CO., LTD., 121, Pentonville Road, London, N.1.

Quality RADIO
Manufacturers of
Coil Holders and Components. New illustrated price list, free and post free. If your dealer cannot supply one, we send post free if you mention his name and address.

the joint, and has a small chuck for the actual whisker. On trial, it was found to operate smoothly and firmly. The base of the instrument provides a drilling-temple for the second hole needed for fixing it on the panel. The glass tube has an opaque back, for better vision in the operation of setting the whisker. On test, the ebonite passed a severe insulation test.

We can strongly recommend this ingenious and extremely practical detector, which should do a good deal towards raising the standard of crystal reception in many cases.

Crystal Detector

A type of vertical enclosed crystal-detector which is provided with a micrometer adjustment for the cat's whisker is the No. 922 pattern supplied by Messrs. A. H. Hunt, samples of which have been submitted for test. This instrument is mounted on a composition base 1 3/4 in. square, which carries two miniature terminals and the crystal-cup, the latter of small size and provided with the usual three small fixing-screws for the crystal. The glass tube which encloses the crystal is fixed down by means of

a metal frame screwed to the base: this has to be unscrewed when a crystal is inserted or changed, an operation which proved somewhat troublesome on trial, and which would present difficulty to many users with the present design of the detector. The usual ball and socket joint on the top is adjustable by a screwed cap, and the cat's-whisker holder has a longitudinal adjustment by means of a fine-thread screw working against a spring. A second crystal cup can replace the cat's-whisker for certain crystal combinations. We found the whisker supplied unduly stiff and thick, without the fine point which is generally called for. The screw-adjustment feature, and the operation of the cat's whisker in general, in searching for and holding sensitive settings, proved on trial to be quite satisfactory.

NOTE ON A "DOUBLE-CIRCUIT NEUTRODYNE."

With reference to the grid-leak connection at the point X in the wiring diagram of the above set, it is essential that the clip should be severed when in position as stated in the article. On no account should the clip be removed to do so, as this will break the internal connections and render the condenser useless.

[A Single Valve Set.]

To the Editor of MODERN WIRELESS

SIR,—I constructed the one-valve set described by Mr. Herbert K. Simpson in the June number of MODERN WIRELESS and I am writing to tell you of the success I have achieved with it. It was my first valve set, but I experienced no difficulty in making it. The first time I tried it out it worked very well and received J.B. (i.e., the Johannesburg Broadcasting Station) which works on a 450 metre wavelength, with a number 50 coil in aerial socket and a 75 in reaction socket and using parallel tuning. This form of tuning gave the loudest and clearest signals.

J.B. is 40 miles away and only uses 500 watts. power for transmission. I use an Ediswan A.R. .06 valve, which works very well.

Congratulations on producing two such fine papers as *Wireless Weekly* and MODERN WIRELESS.—
Yours truly, R. L. SIMPSON.

Pretoria, S. Africa.

CHOOSE AND USE—

"Tangent" Tuning Coils

and ENSURE LOW SELF CAPACITY.



"No second-rate effects will satisfy the intelligent purchaser for whom 'TANGENT' fittings are designed."

UNSHROUDED EFFICIENCY

In order to obtain satisfaction you must have a Tuning Coil that is

RIGID AS A MOTOR WHEEL

STRONG & YET HIGHLY EFFICIENT

In the "TANGENT" self-capacity has been reduced to a minimum owing to the fact that the impregnated cord not only passes between the layers and thus provides air-spacing, but also firmly braces up the whole coil so that no swathing or shellac is required.

Ask your Dealer—Take no substitute for "Tangent."

SIZES.	
Coil No.	Price
25	4/3
35	4/3
50	4/3
75	4/6
100	5/-
150	6/-
200	7/-
250	7/6
300	8/-
400	9/-
500	10/-

GENT & Co. Ltd. Faraday Works, LEICESTER. Estd. 1872.


Manufacturing Electrical Engineers.

LONDON: 25, Victoria St., S.W.1;

NEWCASTLE/TYNE: Tangent House, Blackett St.

Complete set of 4 Concert Coils (Nos. 25 to 75)—16/- the set.
Complete Set of 11 Concert Coils (Nos. 250 to 500)—£3 7 0 the set.

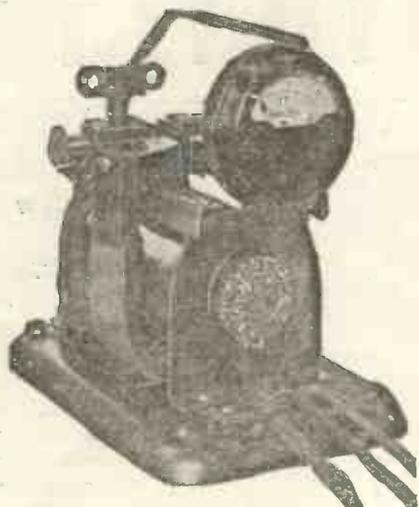"ELLA"
BATTERY CHARGERS
They work from a lampholder




A.C. Model.

Output 5/10 amps. 9 volts. Complete with Pole Indicating Ammeter and all connecting leads and adapter £6 6 0



AT HOME

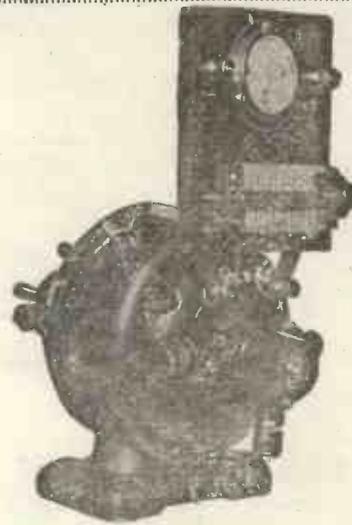

D.C. Model.

Output 5 amps. 9 volts. Machine only £5 12s. 6d. With Switchboard and Pole Indicating Ammeter and Regulating Resistance as illustrated - £8 15 0

There is an "ELLA" Battery Charger for every supply voltage. BATTERIES charged at home have much longer life and give better service than when charged outside. "ELLA" Battery chargers save their cost many times over.

Send for descriptive leaflet. Trade Supplied.

LIONEL ROBINSON & CO. 3a, Staple Inn, London, W.C.2.

'Phone: Holborn 6323 (Two Lines).

A Set of Wireless Parts as a Present for Xmas
IS MOST ACCEPTABLE TO YOUNG & OLD.

Think of the pleasure in making, followed by happy months of pride of accomplishment as one's relatives and friends listen in with keen enjoyment! And that sense of boredom on Winter evenings will be banished together with the "want to go somewhere" feeling.

RADIO "STOCKS" (B. HAINE, Proprietor) of LONDON

GUARANTEE EFFICIENCY and CERTAIN SATISFACTION

IF YOU BUY RADSTOCK COMPONENTS AND FOLLOW THE SIMPLE INSTRUCTIONS WITH EACH SET.

All Goods on 24 Hours' Approval to Post Customers. Money Refunded if not Satisfied.

	No. 1.	No. 2.	Cabinet and drilled Ebonite Panels will be supplied for
CRYSTAL SETS	9 9	7 6	6 6
ONE VALVE SETS	£1 10 9	£1 3 6	11 9
TWO " "	£2 5 9	£1 17 6	15 0
THREE " "	£3 8 9	£2 15 6	15 6
FOUR " "	£5 3 9	£3 15 6	£1 2 6
S.T. 100 (Two Valve and Crystal Reflex)	£4 16 9	£3 14 6	£1 6 0

Any Circuit quoted for.

N.B.—No. 1 Sets are with Best well-known Parts. No. 2 Sets are with "Radstock" Guaranteed Parts. If parts Nos. 1 or 2 are sold with cabinet and ebonite as "a complete set of parts," Marconi Royalty of 12/6 per Valve must be added to above prices.


COMPLETE WITH WIRING DIAGRAM, FULL INSTRUCTIONS AND ALL NECESSARY PARTS; CABINETS OF BEST POLISHED HEAVY OAK. BEAUTIFUL JAPANESE CABINETS QUOTED FOR; SEND SIZES REQUIRED.

(Phones, Batteries, Valves and Coils extra—See Lists.)

EVERYTHING FOR WIRELESS AT ROCK-BOTTOM PRICES. SEND FOR FREE LISTS.

RADIO "STOCKS" (B. HAINE, Sole Proprietor),
RADIO HOUSE, NEWMAN STREET, LONDON, W.1

'PHONE: MUSEUM 3205.

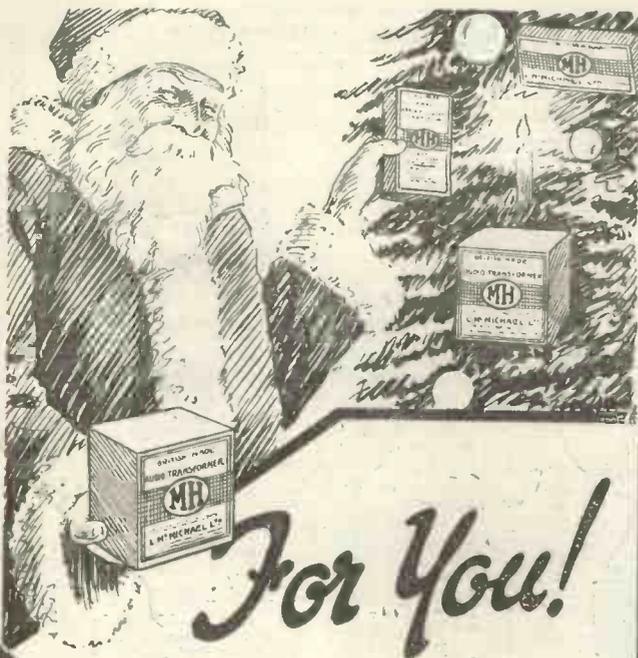

For You!

—or your friends who are interested in wireless nothing will give greater pleasure and satisfaction than receiving just the set or components desired. A seasonable and reliable gift is assured provided M.H. products are chosen.

PLUG-IN TRANSFORMERS

A series of H.F. Plug-in Transformers in six ranges of wavelength. They are made of our highly polished non-loss ebonite. The windings are carried in staggered slots, well protected, ensuring low self capacity and high efficiency.

Each and every transformer is tested to a standard oscillation and any not coming within very narrow limits are rejected. Perfect matching is thus ensured.



PRICES (in cartons)		each			each
No. 00, 80 to 150 metres	10/-	No. 2, 550 to 1200 metres	10/-		
" 0, 150 " 300 "	10/-	" 3, 1100 " 3000 "	10/-		
" 1, 300 " 600 "	10/-	" 4, 2500 " 7000 "	10/-		

Complete set Nos. 00 to 4, 55/-.
Any number of each transformer can be supplied matched, at no extra cost, if specified when ordering.

REVERSINE COIL HOLDER



A beautifully made, perfect action coil-holder. It is made of polished ebonite with lacquered brass mountings. The contacts with the moving coil are by rubbing spring brushes, terminals at one end provide for the circuit connections of both the fixed and movable coils. Standard plugs and sockets take the ordinary type dualateral coils.

This M.H. coil holder enables the moving coil to be completely reversed in both its physical and electrical relationship with the fixed coil. It is a perfect variometer as well as a loose coupler and means of applying re-action. If you need to reverse re-action there is no need to reverse the movement of the moving coil.

PRICE (in carton) : 2 coil, 21/- ; 3 coil, 39/-



HIGH GRADE SETS AND COMPONENTS ARE WORLD FAMOUS.

Our Standard receiving apparatus is used in every quarter of the globe, and our components are in demand everywhere. We have sets and components for every requirement.


L.M. MICHAEL LTD

IN CONJUNCTION WITH B. HESKETH LTD

Wireless Engineers, 179, Strand, London, W.C.2.

"UTILITY"

VARIABLE

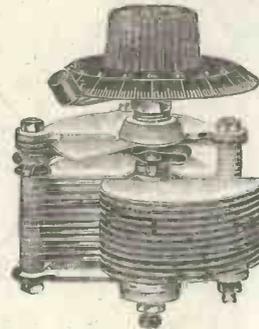

W.11. 124

PRICES
SQUARE LAW
OR
ORDINARY.

		each
WM. 123	.001 ...	12/6
WM. 144	.00075 ...	11/9
WM. 124	.0005 ...	10/6
WM. 125	.0003 ...	8/9
WM. 145	.0002 ...	7/9
WM. 146	.0001 ...	7/6

Vernier 2/6 extra.

Manufactured by

WILKINS & WRIGHT, LTD.,
Utility Works, Kenyon Street,
BIRMINGHAM.

CONDENSERS

HULLO!! G.Q., WILL DAY CALLING

T'ANDCO BASKET COILS (100 to 4,500 metres).

No. 31. Duplex wound, 25 gauge D.C.C. wire, sewn supports unaxed, very firm and strong, recognised as the finest type coils yet made.

Size	Approximately	150 to 300 metres	5s. each.	Enamelled.	No. 1.	4d. each
2. 2 1/2 in.,	250 to 400	6d.	2. 5d.			
3. 2 1/2 in.,	350 to 550	7d.	3. 6d.			
4. 3 in.,	450 to 650	8 1/2 d.	4. 7d.			
5. 3 1/2 in.,	600 to 750	10d.	5. 8d.			
6. 4 in.,	700 to 1,000	1 1/2 "	6. 9d.			
7. 4 1/2 in.,	950 to 1,350	1 3/4 "	7. 10d.			
8. 5 in.,	1,300 to 1,750	1 1/2 "	8. 1 1/2 "			
9. 5 1/2 in.,	1,700 to 2,660	2/-	9. 1 1/2 "			
			10. 1 1/4 "			
			11. 1 1/6 "			
			12. 1 1/8 "			

The new "Dayzite" Variable Condensers fitted with Aluminium End Plates, and both sets of Vanes adjustable. .001, 7/9 ea. ; .0005, 5/8 ea. ; .0003, 5/1 ea. ; .0002, 4/7 ea. ; Vernier, 3/11 ea. Postage 6d. each extra.

Do not fail to secure one of the new Climax Earth Tubes, 5/-

Write for new Catalogue sent Post Free on mentioning this Paper. Postage and Carriage on all Goods extra.

MAKE NO MISTAKE IN YOUR SELECTION. Do not keep wasting money on crystals of unknown repute. GET A CRYSTAL THAT HAS STOOD THE TEST OF TIME.

DAYZITE REGD.

As one delighted customer writes:—"Send another Dayzite Crystal for my friend. It is as good as a valve, and if the price was 5s. each it would be cheap." Secure a Registered DAYZITE Crystal, sold only boxed with silver Cat's-whisker, 2/6 each, postage 3d. extra. Makes excellent contact with Zincite for a Perikon Detector.

WILL DAY, LTD.,

19, Lisle St., Leicester Square, London, W.C.2.

Phone: Regent 4577. Telegrams: "Title s, Westrand, London."



Interference from Trains

By E. H. CHAPMAN, M.A., D.Sc.

Staff Editor.

An article of interest to those living near Railway Lines

ONE of the most peculiar forms of interference which can be experienced in the use of a wireless receiver is that arising from trains travelling along a railway line. Fortunately, the majority of wireless experimenters live too far away from our railways to be within range of this kind of interference. When, however, an aerial is erected near to a railway line, it is possible for interference from trains to be a decided nuisance, especially if the aerial wires run parallel to the railway lines.

A case of interference from railway trains has recently come under the writer's notice, and a number of careful observations made at different times are worthy of consideration and comparison with similar observations. The receiver used was one of a well-known type of two-valve set. The aerial was of the twin-wire variety, the wires being suspended at the open end from a mast and at the down-lead end from a chimney on a house. The aerial wires were placed parallel to the railway lines, the possibility of interference from trains having been overlooked. An earth connection to a mass of buried metal was made. Fig. 1 is a sketch showing the position of the aerial with respect to the railway lines.

Noises due to interference from trains may be of at least two kinds. There may be a series of distinct "knocks" occurring at regular or irregular intervals or there may

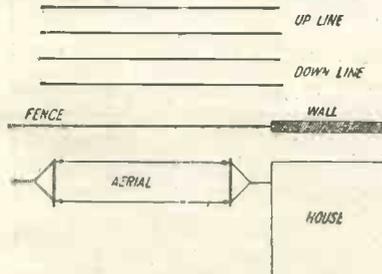


Fig. 1.—Severe interference was experienced with this aerial arrangement.

be a very pronounced and continuous scratching noise. From the observations made in the case under consideration, it would appear that atmospheric conditions must have something to do with the intensity of the noises heard, since on some evenings the noises

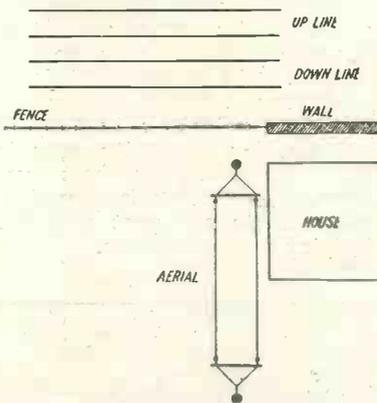


Fig. 2.—In this position interference was reduced.

were most pronounced, whereas on other evenings the noises were hardly audible.

The following table is a specimen

of the observations recorded on an evening when the interference was at its worst.

On the two following evenings the noises were nothing like so noticeable. On the third evening following that for which the table is given, a passenger train travelling on the up line caused slight knocking noises as the train approached, and as it passed the aerial there was a loud click in the telephones, and this loud click was followed by a most peculiar scratching noise, which persisted for some seconds as the train receded in the distance.

It is, of course, highly probable that a train made up of carriages fitted with dynamos which revolve when the train is travelling may cause interference in a wireless receiver, but it is a little difficult to explain how a goods train can cause such interference.

The interference from trains in the case under consideration was noticeably reduced by moving the aerial so that the wires were at right angles to the railway lines. (See Fig. 2.)

Time p.m.	Train.	INTERFERENCE FROM TRAINS.	
		Line.	Observations.
4.30	Passenger.	Up.	Knocking noises at regular intervals as train approached. Slight scratching noises as train receded.
4.45	"	Down.	Loud knocking noises.
4.50	"	"	Knocking noises.
4.57	"	Up.	" "
7.7	Goods.	"	Indistinct noises.
8.20	Passenger, going slowly	Down.	No effect.
9.4	Passenger, going quickly.	"	Slight knocking.
9.11	Passenger.	"	Knocking noises.
9.16	"	Up.	Slight knocking noises.
9.42	Passenger, going quickly.	"	Distinct hard knocking.
9.48	Passenger.	Down.	Slow and distinct knocking noises.
10.0	"	"	Rapid " " "
10.5	"	"	Slow " " "
10.8	"	Up.	Irregular knocking noises.
10.50	Goods.	"	Noises only just audible.

The Advantages and Disadvantages of Plug-In Coils

An article of particular interest to the amateur which may prove helpful to those undecided as to what coil to use.

PLUG-IN coils have come into extensive use, probably because, as far as a certain class of wireless amateur is concerned, their advantages greatly outnumber their disadvantages. The latter are, of course, less obvious, but will be indicated briefly here, together with the former.

The main advantages of such coils lie in their compactness, their general all-round efficiency, the fact that they are (with one or two exceptions) a standardised commercial product of fairly reasonable price, thus allowing easy interchange, and also that a wide range of wavelengths may readily be covered with the same receiver, provided a sufficient number of coils is available. A very important consideration is that harmful dead-end effects are completely obviated.


Against these undoubted advan-

tages must be weighed the following disadvantages:—

It is not easy in every case to provide, by any combination or arrangement of plug-in coils, for such tuning arrangements as those due to Reinartz, with their many modifications; also for short wave work, bringing out two leads so close together is a disadvantage.

On such short waves a much thicker gauge of wire is in many cases advisable, the turns being well spaced to minimise dielectric losses and reduce self-capacity, and a smaller area of support for the wire is desirable for the same reasons. The usual type of plug-in coil does not always comply with this specification, for the dielectric losses and self-capacity may be relatively high. For short wave work, therefore, it is sometimes advisable to construct coils embodying the above points.

It has been observed that receiving sets incorporating coils of special design, which must necessarily be made by the constructor himself, do not find great favour among our readers. Here it must be pointed out that the object of incorporating a coil of special design is simply to obtain greater efficiency. It is not known whether the apathetic attitude is due to lack of confidence on the part of the constructor in his ability to obtain good results with such coils constructed by himself, or not; but it is hoped that this attitude will not continue, for it is detrimental to the progress of the science of wireless. The writer has constructed many such sets of special design, and has, in fact, practically abandoned the use of the ordinary type of plug-in coil in favour of the former for nearly all purposes.

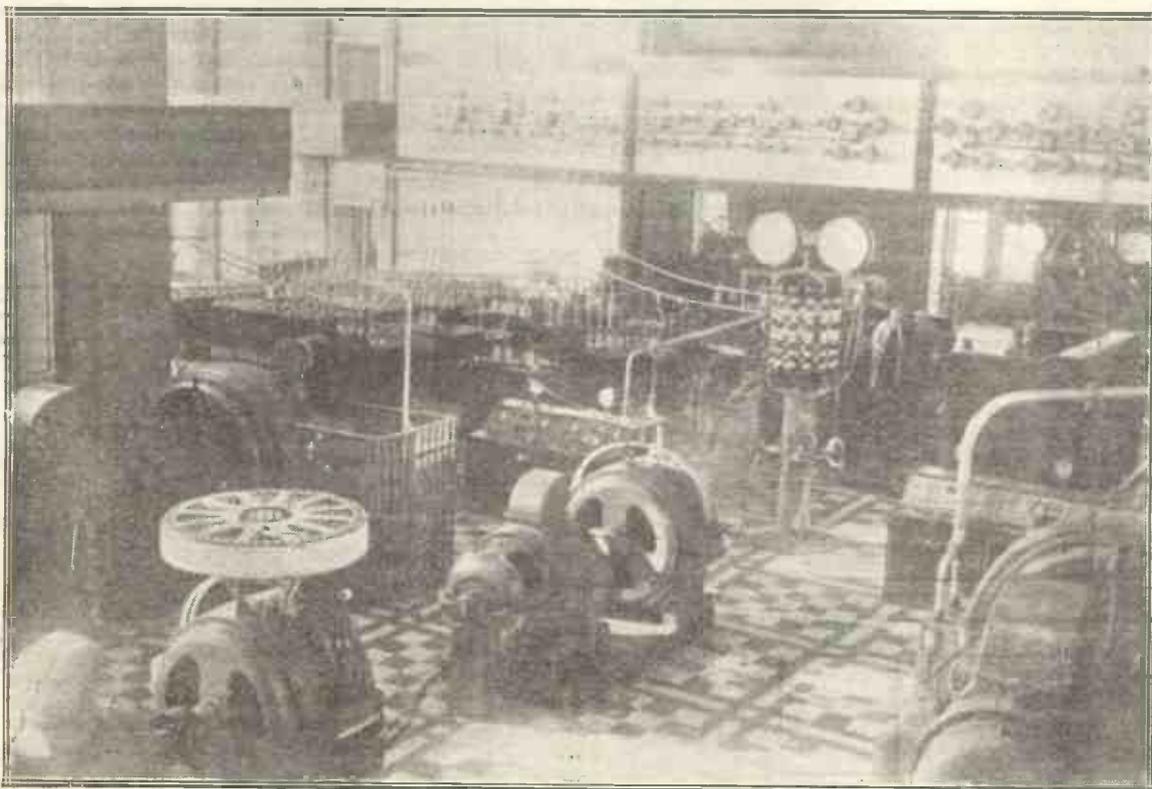

The capacious engine hall at the Nauen Station, showing the generators.

The real 'Slow Motion' device for Condensers. Will pick up that elusive distant station. If you can't get it with a 'Fynetune'—get it up. Over 1,500 sold in 2 days at White City post free 2/6



The Fynetune MICRO ADJUSTER

"Radioha" Bus Bar, Flush Panel Valve and Coil Sockets, Ribbon Aerial, Parts supplied for all W.W. and M.W. sets. Send for particulars.

Sparks Radio Supplies 43, Gt. Portland St., London, W.1.

REPAIRS
TO HEADPHONES
TO LOUD SPEAKERS
TO COILS

Rewound to any Resistance and made equal to new. Price quoted on receipt of instruments. Prompt Delivery.

THE VARLEY MAGNET CO.
(Dept. M), WOOLWICH, S.E.18
Established 26 years.
Phone: Woolwich 888.

FOR SECURING YOUR AERIALS and a thousand purposes where great strength and strain is needed. FLEXIBLE STEEL WIRE ROPE, Aeroplane Cable made to Government specification to specified breaking strains. PRICES BELOW COST. Orders of 10/- and over carriage paid, otherwise, please add 1/- for postage.

No.	Dia.	Strain.	100 ft.
0	1/16	5 cwt.	4/6
51	5/32	25 cwt.	10/-
52	3/16	35 cwt.	11/-
53	7/32	45 cwt.	12/-
5	1/4	70 cwt.	14/-
7	11/32	100 cwt.	20/-

Strainers for use with above, right and left-hand threads, 9d. each or 8/6 per dozen. SMITH & ELLIS, Ltd. (Dept. 85), 11, Little Britain, E.C.1. Tel.: City 8994.


PANELITE. Will withstand 5,000 Volts. Black Finish. WILL NOT FRACTURE. 6 in. by 6 in. by 3/16 in., 1/-; 7 in. by 5 in., 1/1; 8 in. by 5 in., 1/2; 9 in. by 5 in., 1/4; 9 in. by 6 in., 1/6; 10 in. by 9 in., 2/2; 12 in. by 10 in., 2/9; 14 in. by 12 in., 4/6 post paid. Other sizes and thickness, pro rata.

CROIX L.F. SHROUDED TRANSFORMERS. Ratios 4 to 1 and 5 to 1, 50,000 already in use. New improved, 9/6; Super Model, 11/- post paid. Send for price list of H.T. Batteries, Headphones, Valves, etc.—**RADIO PANEL CO.**, Dept. "M," 143, Fetter Lane, London, E.C.4.

AERIAL SATISFACTION!!
Use clear reception "Radio wire" for your aerial, and lead direct to set. Easily fixed, requires no insulators. Only 1/8 for 100 ft. with instructions!! Useful for earthing and 'phone extensions and is waterproof insulated. From your dealer, or post free from—

DAVID GREEN & SON, 657, Department LYTHAM.

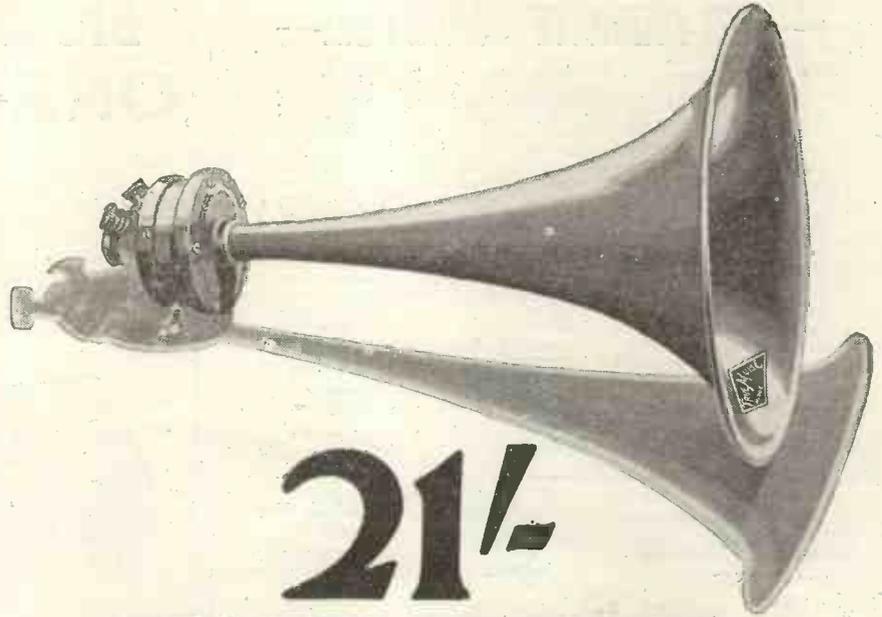WHY PUT A GOOD SET in a SOAP BOX?
Your New Receiver will be worthy of a well-made and nicely-finished Cabinet. We can make it for you—cheaply and promptly. TRY US. Quotations per return for any cabinet described in this journal, or to your own special design. Write now. **BAKER & RUSSELL**, 91, Gibraltair Walk, Bethnal Green, E.



21/- TRUEMUSIC : MINOR :

"An infinite capacity for taking pains" is still our motto and never was it better illustrated than in the TrueMusic Minor.

This wonderful little instrument gives ample volume and perfect articulation for all purposes. Its sensitiveness can be judged from the fact that excellent results have been obtained 6 miles from 2LO on a crystal set.

No illustration can do justice to its appearance. The whole of the outside—horn and base—is finished in nigger brown, and the inside of the horn (which is of copper) is sand-blasted. The wonderfully rich and warm effect of the brown and copper must be seen to be appreciated.

The TrueMusic Minor is the Loud Speaker for every home.

You can get yours from the nearest dealer. If you have any difficulty write to us direct.

LOUD SPEAKERS.


TrueMusic Minor	21/-
TrueMusic Junior	£2 10 0
TrueMusic Standard	£5 0 0
TrueMusic Concert Grand	£6 10 0
T.M.C. Clear as Crystal Headphones	£1 2 6



The Telephone Manufacturing Co., Ltd., Hollingsworth Works, West Dulwich, S.E.21.

E.P.S. 205.

ANTI-CAPACITY SWITCH

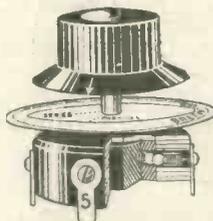


We have pleasure in presenting another first-class speciality, which is the outcome of the famous **BRETWOOD ANTI-CAPACITY VALVE HOLDER**, which has gained such popularity among the wireless public on account of its scientific design and smart appearance. The **Bretwood Switch** is constructed on similar lines, and we claim that it is, like the Valve Holder, absolutely free from capacity effects, and we feel confident that this component will meet with the most exacting requirements of the present-day experimenter. One of the principal features of the **Bretwood Switch** is its beautifully smooth

action, made possible by the spring loaded balls, and the wiping or rolling motion of the Phosphor-Bronze balls always ensures clean and perfect electrical contact.

Features.—1. Absolute freedom from capacity. 2. Perfect contact. 3. Sweet and smooth action. 4. Practically no wear-and-tear. 5. First-class finish and neat in appearance. 6. Easy to fix (one-hole fixing). 7. Very easy to make wire connections. 8. Like our other components, it is fully guaranteed. 9. For value offered the price is moderate.

Price
5/-
postage
3d.

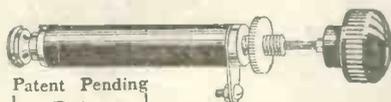

Patent Pending
Price
3/-
Postage 3d.

It's the LEAK that Counts

The **Bretwood Grid Leak** (Guaranteed) tunes a carrier wave from the silent point up. The **Bretwood** is recognised by highest experts and experimenters as the only variable and reliable Grid Leak.


THE BRETWOOD PATENT VALVE HOLDER

Eliminate poor reception by adopting this scientifically designed Valve Holder, and obtain 100 per cent. efficiency. Easy to fix. No capacity. No leakage. Always perfect contact. No soldering. Can be mounted on front or back of panel. Price 1/9. Postage 3d.

RADIO IMPROVEMENTS, LTD., 12-18, London Mews, Maple St., London, W.

ALL BRETWOOD SPECIALITIES ARE OBTAINABLE FROM MOST WIRELESS DEALERS.

Brclays 347.

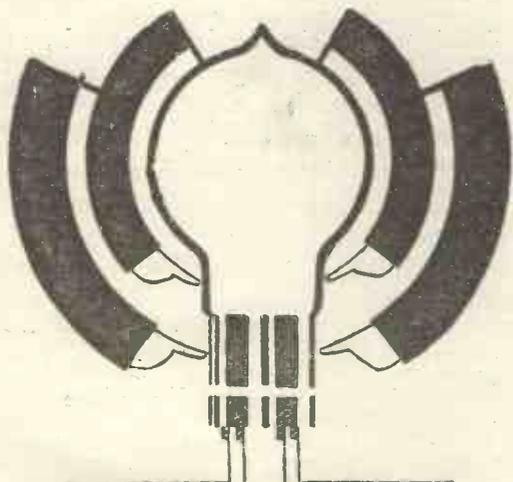


**FIT THE NEW
RADION
G.P. VALVE
AND SIMPLIFY RECEPTION.**

Here's an economical bright-emitter general-purpose valve with amplification factor of 9. Filament 3.5 to 4 volt .48 amp. Anode 30 to 90. Use it in any part of your set. Let us send you free and post free the curve for this valve. Just a p.c. will do.

RADIONS LTD., BOLLINGTON, NR. MACCLESFIELD

From Dealers **10/-** or Direct

"BIG-BEN" LONG RANGE ONE-VALVE SET

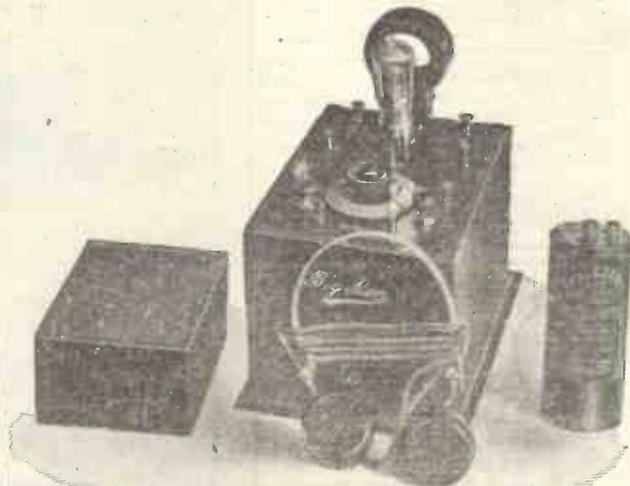

COMPLETE AS SUPPLIED.

This Set will work a Loud-Speaker 10 miles from the Broadcasting Station and has at least a 50 miles range with 'phones.

Supplied complete with B.T.H. Valve (25/-), 1 pair 'Phones, High and Low Tension Batteries, with Marconi Tax paid. Retail Price **£7 12s. 6d.**

Arrange a demonstration at your local Dealer's. If he cannot supply, instruct him to write to us or write direct to:—

STOCKALL, MARPLES & CO. (1912) Ltd.
6/10, CLERKENWELL ROAD, E.C.1.

Telephone: Clerkenwell 6345/6.

Telegrams: Stockalls, Smiths, London.

WHOLESALE ONLY.

Brandes

WIRELESS DEALERS—Our new 120 page illustrated list of Radio Parts now ready, showing Trade and Retail Prices. It is yours for the asking.



Matched Tone
Radio Headphones

Large Stocks of Brandes Phones.
Large Stocks of Igranic Coils.

AUTHORISED FACTORS OF ALL N.A.R.M. SPECIALITIES

Complete Sets, Accessories and Component Parts.

We were one of the very first Wholesale Factors of "Wireless," and carry the largest stocks of Radio goods in the British Empire.

THE LARGEST TRADE RADIO LIST EVER ISSUED.

STAGGERING PRICES. HUGE STOCKS.
Get To Know Us—It Will Pay You.

Ask for our "**CAPITOL**" SPEAKER
(Retail Price £1 : 11 : 6)


Buy from an Established House.
IMPORTANT—Trade only Supplied.

HOBDAY BROS., LTD.

(Dept. D),

21, 23, 25 & 27, Gt. Eastern Street,
LONDON, E.C.2.

'Phone: Clerkenwell 2800 (6 lines).

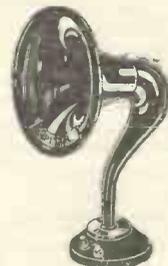

"Capitol" Speaker

Electrostatic Reaction

An Explanation

By D. J. S. HARTT.,
B.Sc.

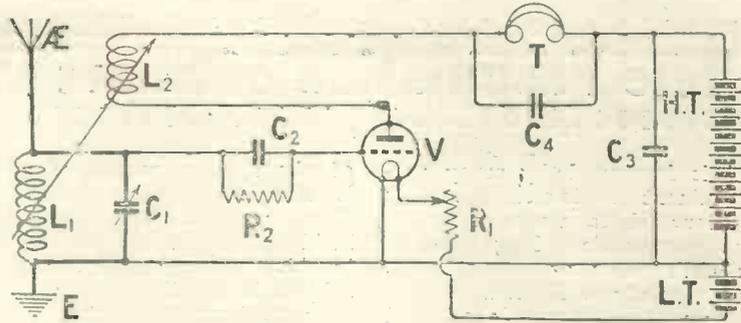


Fig. 1.—Reaction is obtained by coupling L_2 to L_1 .

ELECTROSTATIC reaction is less frequently used by wireless amateurs than the more usual type of reaction achieved by the use of ordinary inductive coupling, the reason probably being that the former is very little understood. It is hoped, therefore, that this short article will assist in clearing up any doubts that may exist.

Magnetic reaction

Let us take the simple case of a single valve receiver with reaction on to the aerial, and show the two methods.

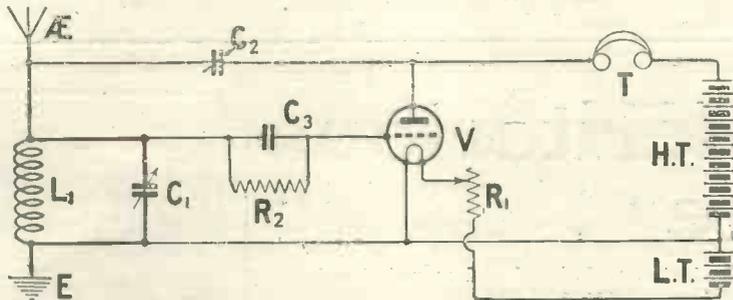


Fig. 2.—The reaction condenser C_2 gives smooth control.

Fig. 1 shows the usual arrangement, whereby magnetic reaction is introduced by coupling a coil in the anode circuit to the aerial or grid coil. Fig. 2 shows how electrostatic reaction may be provided, the coupling between anode and aerial or grid circuits being obtained by connecting a small variable condenser directly between the aerial and the plate of the valve.

A Comparison

In the former case the incoming radio-frequency oscillations set up varying potential differences across the grid-filament circuit of the valve which, by the action of the valve, cause corresponding audio-frequency currents in the anode circuit. These, pass through the anode coil L_2 , and since a magnetic coupling exists between L_2 and the aerial coil L_1 , a transfer of energy from the plate circuit into the aerial circuit takes place. Thus

when L_2 is correctly connected it increases the potential variations across the grid-filament circuit. This results in a corresponding increase in anode current, which, passing through the telephones T, gives greater signal strength.

Electrostatic reaction

Comparing this with the second case of electrostatic reaction, we find a similar state of affairs. The radio-frequency oscillations in the aerial circuit L_1, C_1 cause varying potential differences to be applied across the grid-filament circuit of the valve V. Due to valve-action,

this condenser is omitted, the reason being that in the second case (electrostatic reaction) a radio-frequency choke must be provided in the anode circuit, otherwise the H.F. oscillations in the aerial will have a direct path through the telephones T and the H.T. battery circuit to earth. Normally, on broadcast and higher wavelengths, high resistance telephones will function as an efficient radio-frequency choke, but on the shorter waves it is necessary to include a choke consisting, say, of a 200-300 turn, low self-capacity coil, L_2 , between the telephones and the anode of the valve V, as shown in Fig. 3.

Double reaction

This will provide an effective block to H.F. oscillations while not preventing the passage of audio-frequency currents through the telephones.

On practical trial it will be found that the electrostatic method provides a smooth and easy control of reaction with an even build-up of signal strength by simply varying the capacity of C_2 . It is usual in receivers employing more than one valve to arrange the anode-aerial capacitive coupling between the anode of the detector valve and the aerial; some experimenters, however, have introduced double reaction by effecting a similar coupling between the aerial circuit and the anode of a low-frequency amplifying valve.

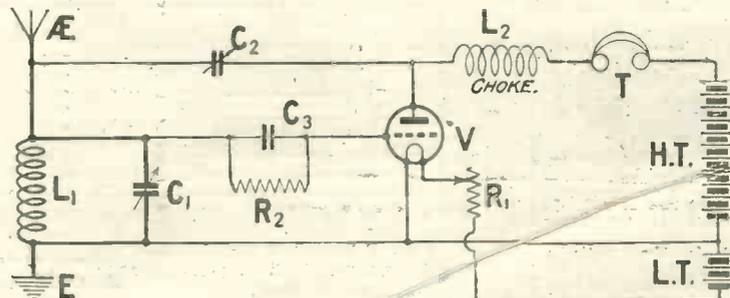


Fig. 3.—How to connect a choke when using capacity reaction on short waves.

The Fascination of Short Wave Reception

IT is forecasted by many prominent radio experts that very short waves may in time supersede long waves for both short and long range work. Only a little while ago long wavelengths were considered essential to transmit over great distances, but recent developments have shown that ultra-short waves have remarkable penetrative powers. But, as many readers well know, reception is much more difficult on these low wavelengths, and much attention is now being given to the efficient reception of waves below 100 metres, necessitating a certain amount of modification of existing apparatus.

In the issue of *Wireless Weekly* dated October 22 there commenced an extremely interesting series of articles on "Supersonic Heterodyne Reception" by John Scott-Taggart, F.Inst.P., A.M.I.E.E. No one who is anxious to learn the principles of this fascinating method

of short wave reception, which is now so popular across the Atlantic, can afford to miss these lucid articles, which are the first in this country which tackle the subject in detail.

Apart from this series, several articles of outstanding interest have appeared in recent numbers of *Wireless Weekly*. In the issue for October 29 Mr. A. D. Cowper contributes an article on "Neutral Grid Coupling," an interesting method of obtaining stability in high-frequency amplifiers, of which original method he is the author. A wavemeter for amateur transmitters was described by Mr. Percy W. Harris, and under the title of "Some Record-breaking Achievements" the wonderful two-way wireless communication accomplished between this country and New Zealand is detailed.


The issue for November 5 was the second of our special numbers, containing twelve pages of superb

photogravure reproduction, the first having been published on October 22. Mr. A. D. Cowper writes on "Long-Distance Reception with the 'Neutral Grid' Method of H.F. Coupling"; while Mr. R. W. Hallows contributes an article of universal interest entitled "Your Accumulator—How It Works." A two-valve and crystal receiver employing the S.T. 152 circuit is described, a special feature of this set being its immunity from A.C. hum.

In the November 12 issue is an article on the "Super-Autodyne," which describes a new method of obtaining extreme selectivity with minimum equipment. The popular combination of valves employed as H.F. amplifier, detector, and L.F. amplifier has been adopted by Stanley G. Rattee in his description of "A Transformer Coupled Three-Valve Receiver." Flat-dwellers and experimenters are well catered for by Mr. R. W. Hallows in an article describing a "Novel Frame Aerial."

Equal In Meritorious Performance

Patents Applied for.

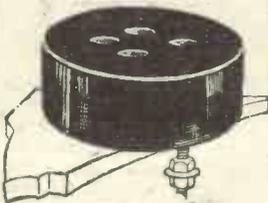

TYPE A (above panel).
This model appeals to those who prefer above-panel mounting. Be sure you get the H.T.C. by looking for the template: it is your guarantee.



TYPE C (below panel).
The special advantage of this type is the method of mounting below panel. This model is the particular object of imitation. Constructors are advised to be certain that they buy the H.T.C.—look for the template.

H. T. C. Products are designed and manufactured with 25 years' experience of Electrical Instrument Design and Manufacture. The Electrical performance of our productions is unrivalled.

LOW CAPACITY VALVE HOLDERS


High technical opinion on the H.T.C. principle

Mr. John Scott-Taggart, F.Inst.P., A.M.I.E.E. :—"The widely-spaced contacts on certain types of special valve holders are particularly suitable for high-frequency work. The ordinary arrangement where the socket pins are very close together, the nuts and washers being frequently only a matter of 1/16th inch apart, is entirely unsuitable for high-frequency. OR, IN FACT, FOR ANY OTHER WORK."


Type A (above panel) Template Supplied 1/6

Type C (below panel) Template Supplied 1/6

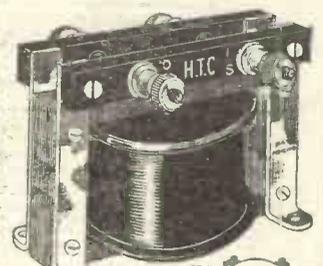
Insist upon the original and genuine Low Capacity Valve-Holder.



LENGTH - 2 1/2"
HEIGHT - 2 1/4"

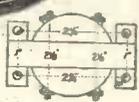

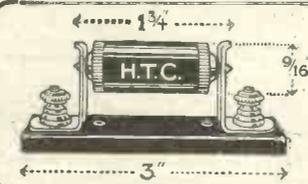An excellent transformer at a very moderate price. A gift of a ten shilling note is really made with this instrument as you need not pay more than the cost of an H.T.C. if you want perfect reception. Price 15/-




A Fixed Detector—NEW and RELIABLE

This Detector was primarily designed to simplify our experiments when using our L.F. Transformers on the famous S.T.100. These detectors are in use on our own test sets with good results, and our confidence and experience is now passed on to users of crystal detectors. In our experience the H.T.C. is the most stable crystal detector yet made. One model has been repeatedly dropped on a floor from a height of 5ft. and has not suffered deterioration in any way. H.T.C. Detector, 3/6 Complete with Ebonite Base clips and terminals, 4/6. Postage 2d.

IF YOUR LOCAL DEALER CANNOT SUPPLY, WRITE DIRECT TO:

H.T.C. ELECTRICAL CO., LTD.
2 and 2a, BOUNDARIES ROAD, BALHAM, S.W.12.
Trade Enquiries Invited.

TELEPHONE: Battersea 374

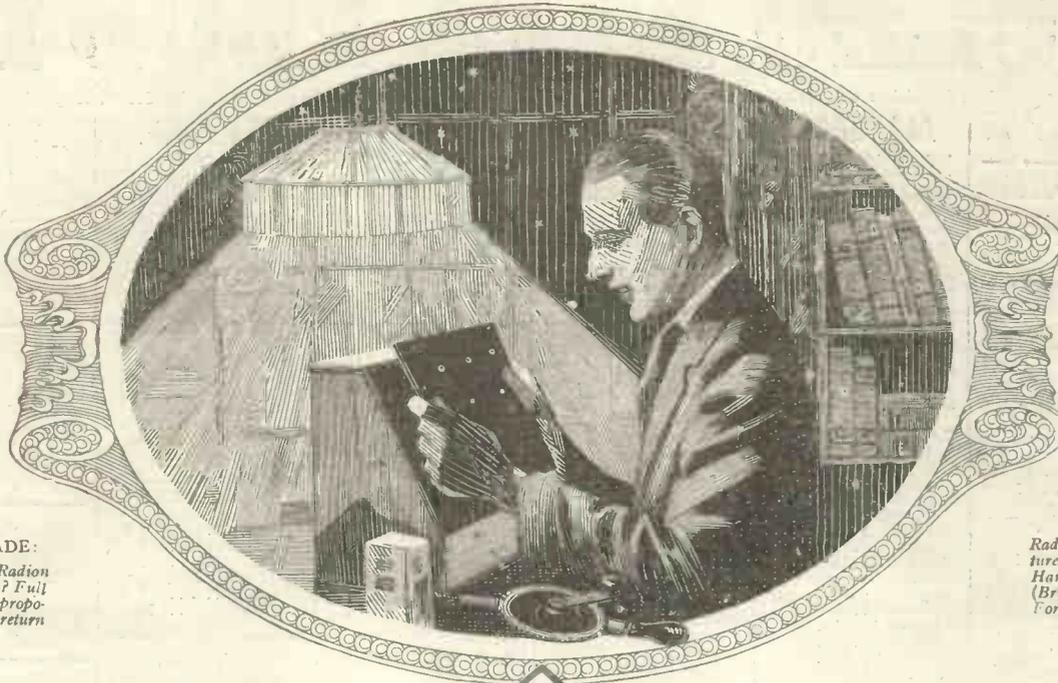

TO THE TRADE:
 Are you stocking Radion Panels and Dials? Full details of our proposition sent by return on request.

Radion is manufactured by American Rubber Co., (Britain), Ltd., 13a, Fore Street, E.C.2.

Radion Panels

EVERY Wireless Magazine of note is emphasising the necessity of using only the very finest grades of ebonite guaranteed free from surface leakage. Writing in *Wireless Weekly* (dated November 12th), Mr. Percy Harris stresses the point that the average man cannot tell the difference between good ebonite and inferior ebonite by merely looking at it. The acid test is to use it—but no one wants to spend time and money on building a Set only to find that it won't work.

The safe way, therefore, is to be sure to choose an ebonite that is fully guaranteed in every respect and backed by a manufacturer whose name is well known. Radion, for example, is made in the largest factory in the world devoted to the manufacture of ebonite. Radion is more than

ebonite, for its manufacturers found that ordinary ebonite was not sufficiently free from leakage for wireless use. Its beautiful polished surface—either in black or mahogany—need not be removed before use. Not only will it convey a most distinctive appearance to any Receiver, but it is absolutely dust and moisture proof.

Radion is sold by all Dealers in 21 different sizes—each panel being given perfectly square edges and packed in a stout manila envelope. Dials and knobs to match can also be obtained.

Its cost is so little—if any—above ordinary ebonite that it would be sheer folly to build up an expensive Receiver only to find after annoying delays that the fault lies in the panel. Get Radion, therefore, and know that yours is the best panel money can buy.

PRICES OF RADION PANELS.		
Size	Black.	Mahog-anite.
6in. by 7in.	3/6	4/3
6in. by 10in.	5/3	6/3
6in. by 14in.	7/-	8/6
6in. by 21in.	10/6	12/9
7in. by 9in.	5/3	6/6
7in. by 10in.	5/9	7/3
7in. by 12in.	7/-	8/6
7in. by 14in.	8/-	10/3
7in. by 18 in.	10/6	12/9
7in. by 21in.	12/3	15/-
7in. by 24in.	14/-	17/3
7in. by 26in.	15/-	18/6
7in. by 30in.	17/9	21/6
7in. by 48in.	28/-	34/6
8in. by 28in.	17/6	21/3
9in. by 14in.	10/6	12/9
10in. by 12in.	10/-	12/-
12in. by 14in.	13/3	16/-
12in. by 21in.	18/9	24/3
14in. by 18in.	19/9	24/3
23in. by 21in.	39/6	48/-

Every panel 3-16 in. thick—absolutely sufficient owing to the immense strength of Radion.

Use Radion—your Set will look better and work better.

In replying to Advertisers, please use Order Form enclosed.

Gilbert Ad. 1770.

HULLO EVERYBODY!!

Post Orders accepted for despatch in strict rotation. Not possible to execute otherwise. Extra Post must be sent with Foreign Orders. All previous lists cancelled.

ALL VALVES ON POST SENT AT PURCHASER'S RISK.

VALVES

THORPE K4 .. 17/6
5 PL3
PHILLIPS 4 ELEC-TRODE .. 12/6
(Both for UNIDYNE)

Bright Emitter 12/6 each.

B.T.H. R. Type
Ediswan A.R. " "
Marconi-Osram R or R 5 V " "
Mullard-Ora " "
Cossor P.1 " "
Cossor P.2 " "
Myers-Universal
Mullard H.F. (Red Ring)
Mullard L.F. (Green Ring)

Dull Emitter

21/- each Type
B.T.H. B.3
Ediswan A.R.D.E.
Marconi-Osram D.E.R.
25/- each Type
B.T.H. B.5
Ediswan A.R.O.0
Marconi-Osram D.E.3
Mullard D.F.Ora

DULL EMITTER POWER VALVES
For use with A.R.D.E. and D.E.R. Valves.
Marconi-Osram, Type D.E.6, 2-2 1/2 volt, 25 amps. 25/-

DULL EMITTER POWER VALVES
For use with '06 Valves.
B.T.H. Type B.6 35/-
Marconi-Osram D.E.4 30/-
Mullard D.F.A.2 30/-

DULL EMITTER POWER VALVES
For use with Bright Emitters.
B.T.H. B.4 35/-
Marconi-Osram D.E.5 35/-
Mullard D.F.A.1 35/-

'06 French Metal 17/6
'06 Dutch 12/6
Phillips '04 Type 17/6

HEADPHONES

We can recommend these as being excellent Headphones, with a great reputation for telephone designs behind them. British Thomson-Houston, Sterling, Brown's Featherweight, Geophone, 4000 ohms resistance, each £1 5 0
British Ericsson, 4000 ohms resistance, each £1 6 6
G.R.C., 4000 ohms resistance, each £1 0 0
B.T.H., 4000 ohms resistance, each £1 5 0
Brandes Matched Tone, 4000 ohms resistance, each £1 5 0
Brown Type A, 4000 ohms resistance, each £3 2 0
Sterling, 4000 ohms resistance, each £1 5 0
Geophone, 4000 ohms resistance, each £1 5 0

ALL GOODS ON THIS PAGE ARE SENT BY POST (See notice).

L.F. TRANSFORMERS

Eureka Concert Grand This is a really high grade transformer for Inter-valve use. We can thoroughly recommend its use where first class results are required. It increases power and the purity of signals. Made in two sizes but only one quality.

"Concert Grand" Model .. £1 10/-
No. 2 (Second Stage) .. £1 2/6
R.I. 5-1 Ratio .. 25/-
Igraite, 5-1 Ratio 21/-
The Ferranti, 4-1 Ratio .. 17/6
The Silvertown, 5-1 Ratio .. 21/-
The G.R.C. 5-1 Ratio .. 15/-
The G.R.C. 10-1 Ratio .. 20/-
Marconi Ideal Power .. 35/-
Burndebt L.F. 5-1 Ratio .. 25/-
Lissen T.1 L.F. .. 30/-
" T.2 L.F. .. 25/-
" T.3 L.F. .. 16/6
Success, 5-1 Ratio 15/-
Ditto, Super .. 21/-
Ormond .. 14/11

LOUD SPEAKERS

BABY MODELS
Sterling, 4000 ohms .. £2 15/-
Sterling Dinkie 1 10/-
Brown's 2000 ohms 2 3/-
Amplion Junior 1 7/6
Dragon Flv. .. 25/-

PARTS FOR 2-VALVE "UNIDYNE" RECEIVING SETS.

The 4-Electrode Valve Thorpe K4 each 17/6
6 Terminals for 10d.
2 Microstat Filament Resistances each 2/9
1 Variable Grid Leak 2/6
1 Single-Pole Double-Throw Switch 1/9 or 2/-
1 '0005 Variable Condenser, with Vernier 7/3
1 Cam Vernier 2-way Coil Holder .. 9/-
Panel, 5 1/2 in. by 1 1/2 in. by 1 in., drilled to hold 2 5-Pin Valve Holders .. for 2/-
2 5-Pin Valve Holders each 1/6
1 Fixed Condenser, '001 .. 1/2, 2/2, 3/-
1 Fixed Condenser, '0002 .. 1/2, 2/2, 3/-
1 Shrouded L.F. Transformer G.R.C. 10-1 .. 20/-
8 yds. No. 18 Gauge Tuned Copper Wire 1/2 Necessary Screws, Nuts, and Washers, Free if above lot purchased.
Post Extra.

BRUNET (genuine)

4000 ohm Double 16/6
4000 ohm Single 8/11
2000 ohm Single 7/6
Post Free.

ENERGO

H.F. Plug-in Transformers.
No. 1. 150-450 .. 3/6
No. 2. 250-700 .. 3/11
No. 3. 450-1200 4/3
No. 4. 900-2000 4/6
No. 5. 1600-3000 4/9
No. 6. 2200-5000 4/11

FILAMENT RHEOSTATS

Wire Wound Type. Rotary Action.



IGRANIC

The "different" filament resistance with stationary contact arm, extremely silent in operation, the plain type is recommended for amplifying valves. For the rectifier use the Vernier adjustment.

IGRANIC ohms each

Plain Type .4 & 7 4/6
With Vernier Adjustment .. 4 7/-
Plain Type .. 30 7/-
The Raymond 6 1/8
The Ormond .. 2/-
The T.C.B. Type, B 13 4/-
The T.C.B. Type, D 30 4/-
The Burndebt, Dual, 222 5 & 30 7/6
Microstat .. 2 9/-
Lissenstat, Minor 3/8
Lissenstat .. 7/8
Lissenstat, Universal .. 10/6
Lissen Auxiliary Resistance .. 1/3

SHIPTON'S

30 ohms .. 3/-
60 ohms .. 3/-
80 ohms Potentiometer .. 4/6
Highly recommended.

T.C.B.

6, 13, 30 ohms 4/-
300 ohms Potentiometer .. 5/-
Highly recommended

IGRANIC COILS

Coils: 25, 5/- 35, 5/-
50, 5/2; 75, 5/6; 100, 7/-; 150, 7/10; 200, 8/8; 250, 9/-; 300, 9/5; 400, 10/3; 500, 10/6

DUBILIER, Post 2d.

.001, .002, .003, .004, .005, .006, Fixed .. 3/-
.0001, .0002, .0003, .0004, .0005 .. 2/6
Type 577, .01 .. 7/8
Grid Leaks each .. 2/6
Anode Resistance 50,000, 70,000, 80,000, 100,000, on stand complete 5/6

EBONITE

COIL HOLDERS

Polar 2-way, with Vernier .. 11/-
Polar 3-way, with Vernier .. 17/-
Polar-Junior, 2-way Cam Vernier 6/-
Polar Junior, 3-way Cam Vernier 9/6
Polar Universal 2-way .. 10/6
Goswell 2-way coil holder .. 5/6
Goswell 2-way Vernier Coil Holder 9/-
Goswell 2-way Coil Holder .. 7/6
Goswell 2-way Panel Mounting .. 3/-
Goswell 3-way Panel Mounting .. 5/-
Franco Cam Vernier 2-way .. 12/6
Goswell 3-way Cam Vernier .. 12/6

BASKET COIL HOLDERS

No. 1 .. 2 for 2/-
No. 2 .. 2 for 2/6
(both with plug)
Coil Stand 2-way for Basket Coils 5/6
Universal 2-way for Basket Coils 5/11

'BABY' COIL STANDS

2-way on base .. 3/-
3-way on base .. 4/9
(brass fittings)
2-way ex handles 4/6
3-way do. 5/6
(nickel fittings)
2-way Cam Vernier high class .. 5/9
Several high-grade patterns.
2-way .. at 5/- 5/6
3-way .. at 6/11 7/6

POLAR CONDENSERS

(Variable.) For Panel Mounting only.
A new form of Variable Condenser, constructed with a di-electric of air and high-grade mica, reducing losses to a minimum. Tested for insulation on 1000 volts potential. Adaptable to any type of Panel.

Each
'001 mfd. .. 10/6
'0005 .. 10/6
'0003 .. 10/6
'00025 .. 10/6

'Sterling' Square Law

Variable Condensers

A new type of superior quality, distinctive design of moving plates, with Vernier Adjustment. The auxiliary knob controls the Vernier.
Each
'001 mfd. .. £1 10/6
'0005 .. £1 5/6
'00025 .. £1 3/-



ACCUMULATORS MADE BY WELL-KNOWN FIRM FOR ME.

POST PRICES.
2 v. 40 amps. .. 10/6
4 v. 40 amps. .. 17/6
4 v. 60 amps. .. 20/6
4 v. 80 amps. .. 24/6
6 v. 60 amps. .. 29/-
6 v. 80 amps. .. 34/6
6 v. 105 amps. .. 40/6

EDISON BELL.

'0001 to '0005 Fixed .. 1/3
'002 to '006 .. 2/-
'001 .. 1/3
'0003 with Grid Leak .. 2/6
Variometer .. 10/-
Twin Detector .. 5/6

BRETWOOD (New Model)

Var. Grid Leak .. 3/-
Anode Resistance 3/-

Genuine DR. NESPER HEADPHONES

Adjustable diaphragm, detachable receivers, double leather-covered head-springs, long flexible cords, nickel plated parts. Very comfortable fitting to the head. LOOK FOR THE TRADE MARK. 4,000 ohms .. 12/11
Post 6d. pair.

McMICHAEL'S H.F. TRANSFORMERS

150-300 10/-
300-600 10/-
1,100-2,000 EACH
(Manufacturer's advance.)
100,000 ohms Fixed .. 2/6
2 meg. Leak .. 2/6
Both with clips.

WATMEL

Var. Grid Leak .. 2/6
Anode Resistance 3/6

NOTE!

OUR WONDERFUL MICRO METER ADJUSTMENT GLASS ENCLOSED DETECTOR. WHY PAY MORE? 1/9
POST 6d. each

WATES MICROSTAT



For D.E. or R. Valves .. 2/9
Post Free.

FRENCH THOMSON HOUSTON

JUST TRY THEM. 4,000 ohms 15/11
Per pair

HAWK COILS HONEYCOMB
25 .. 2/4 150 .. 4/8
35 .. 2/6 200 .. 5/4
50 .. 3/- 250 .. 5/8
75 .. 3/4 300 .. 6/-
100 .. 3/10 400 .. 6/8

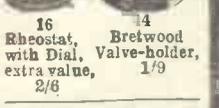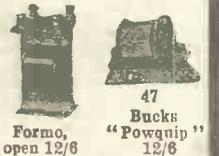"MURRAY" (Prov. Pat.)
Valve Holders .. 1/3
High Finish. Absolutely Safe. Low Capacity.



17/6 N & K 17/6
No. 3
LATEST MODEL.

RIGHT OPPOSITE DALY'S GALLERY DOOR

K. RAYMOND

27, LISLE STREET, LEICESTER SQUARE, W.C.2

NO RESPONSIBILITY ACCEPTED ON POST ORDERS UNLESS CHEQUES AND POSTAL ORDERS ARE CROSSED AND MADE PAYABLE TO THE FIRM. MONEYS SENT MUST BE REGISTERED

HOURS OF BUSINESS: DAILY - 9 to 7.45 SUNDAY - 10 to 1

'Phone: GERRARD 4637.

CALLERS' PAGE OVERLEAF


ALL GOODS ON THIS PAGE SENT BY POST

Please Note. Large stocks kept, but orders accepted on distinct understanding that same will be despatched in strict rotation at the earliest possible date. Not answerable for delays in manufacturers' supplies. Right reserved to return cash.

RAYMOND'S VARIABLE CONDENSERS

ALL OUR CONDENSERS HAVE BEEN TESTED AND RECOMMENDED BY LEADING JOURNALS—UNSOLICITED.

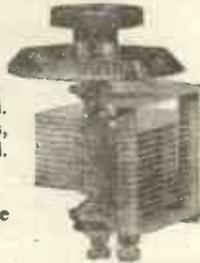- Exclusive Design.
- Stout Vanes.
- Extra Insulation, Very Compact.
- Narrowest Spaces (Pressed Aluminium).
- Centre Rod cannot bend.
- Terminal Connections, Capacity Guaranteed.
- Perfect Efficiency.
- Handsome Design.
- Takes up very little space in panel.
- Nickelled Fittings.
- Beautifully Made.
- New one-hole fixing method.
- Wonderful for Portables.



UNSURPASSED FOR FINE TUNING.

Costs a trifle more, a few pence only, and is just what you want. Nice dial and knob included.

'DE LUXE' MODEL

AS SHOWN, WITH DIAL, KNOB AND BUSH.

- 001 - 7/3
- 0005 - 5/11
- 0003 - 5/4
- 0002 - 4/11

POST 6d. SET.

John Blair, Esq.,
Rexall Pharmacy
says:—
Your Condensers are a REVELATION to me as a Dealer. Sept., 1924.


C. Walton, Esq., Andover.
Tested your Condensers on Megger and got "INFINITY"

NEW MODEL

SQUARE LAW WITHOUT VERNIER

- 0005 .. 7/9
 - 0003 .. 6/6
 - With Vernier.
 - 0005 .. 10/6
 - 0003 .. 9/6
- Post 6d.
- Knob & Dial included.

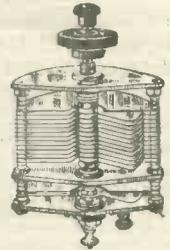- 001 - - 6/6
 - 0005 - - 5/3
 - 0003 - - 4/11
 - 0002 - - 4/6
 - Vernier, ·0005 3/9
- With knob and dial
Post 6d. Set.



TWIN CONDENSER

Composed of two equal units of '00025 or '0003 mid., operated by one Knob and Dial, thereby enabling you to tune two circuits by one turn of the dial. Can be used in series or parallel. Complete as shown, with Knob and Dial.



- WITH VERNIER
- 001 - - 9/3
 - 0005 - - 7/3
 - 0003 - - 6/9
- WITH EBONITE DIAL and Two Knobs.
Post 6d. Set.

SQUARE LAW TWIN VARIABLE CONDENSERS

EBONITE ENDS. KNOB AND DIAL

- 00025 - - - 12/6
- 0003 - - - 12/6
- 0005 - - - 18/11

VALVE DETECTOR & REACTION from Anode Circuit to A.T.C. 1 L.F. Valve.

PARTS FOR P.W. Standard 2-valve Set (Nov. 8th, 1924) For Telephone reception UP TO 40 MILES. The following is a list of materials and cost of the chief parts for the 2-valve Set.

JACKSON BROS. "J.B." VARIABLE CONDENSERS ORDINARY MODELS

Standard Super. Microdenser			
·001	8/6	9/6	11/6
·00075	7/-	8/-	10/-
·0005	5/9	6/9	8/9
·00025	5/9	6/9	8/9
·0002	5/-	5/6	8/-
·0001	4/9	5/3	7/9
Vernier	4/-	4/6	Post 3d. set.

SQUARE LAW			
·001	9/6	·00025	6/9
·00075	9/-	·0002	5/6
·0005	8/-	·0001	5/3
·0003	6/9	Vernier	4/6

EBONITE

Post Prices.

	3/16 in.	1/2 in.
6 x 6	1/6	2/-
7 x 5	1/6	2/-
8 x 6	2/-	3/3
9 x 6	2/2	3/3
10 x 8	3/-	4/2
12 x 6	3/3	4/2
12 x 9	4/3	5/6
12 x 12	5/6	7/6
14 x 10	5/6	7/6

Cut to Size. 3/16 in. at square inch.

Callers' prices elsewhere

"N & K" No. 3

17/6 LATEST MODEL 17/6

New 3-pole Laminated Magnets, which ensure an even magnetic pull and still greater volume. Windings well insulated. Large size earpieces and leather headbands of standard "N&K" comfortable design. Technically, "N & K" Headphones represent the last word in Wireless Reception. IMPOSSIBLE TO EQUAL FOR CRYSTAL SETS.



EBONITE, 12 x 9 x 1/2
·001 Var. Condenser.
L.F. Transformer.
2 Rheostats.
Grid Leak & Condenser.
Two valves (Bright).
Two coils (Igranio).
2-way coil holder.
Valve Sockets.
Terminals and Wire.

All above are **75/-** BEST QUALITY. Panel Drilled. the lot

SPECIAL !! CRYSTAL SET AND 1-VALVE AMPLIFIER. Fittings for Chelmsford. Enclosed box. Splendid quality.

Post 1/6 **39/11**

"HART" Accumulators stocked.

MYERS VALVES UNIVERSAL D.E. 12/6 21/-

BROWNE "IMPROVED" WIRELESS SET, 7/6 Post 1/-.

"POLAR" MICROMETER 5/6 CONDENSER

DIAMOND WEAVE BASKET COILS (5) EXTRA AIR SPACE (DUPLIX WAXLESS) Equal to Honeycomb. 25, 35, 50, 75, 100 (wave-lengths marked). Post Free 3/9

53 for 1/6 29 49 Formo Shrouded, 18/-

5 6 With Clips, 2 for 1/3 ALLEN Variable Grid Leak, 1/6

25 S.P.D.T. 1/9 D.P.D.T. 2/6 China Base.

3 EDISON Bell Wedge, 2 for 2/-

36 EBONITE 1/- 37 Dubilier Fixed 25/- Dragon Fly, 25/-

54 EBONITE Variometer with dial, 4/11, 5/11

51 Enclosed Detector Micrometer Adjustment 2/3

55 One-Hole Filing, 1/6

42 CAM VERNIER 2-way (see lists).

46 Cut from Rod 1/3 Legless 1/3

48 5-1 11/9

34 Wates Microstat 2/9

43 BASKET 2-way, 4/11.

33 ENERGO (see list) Raymond 2/9 to 3/6

"M' Mich'l H.F. Bar-rel 10/-

33 Ferranti INTER-VALVE TRANSFORMER 17/6

BASKET HOLDER Without Terminals, 1/-, 1/3 each With Terminals, 2 for 2/9

RIGHT OPPOSITE DALY'S GALLERY DOOR
Phone: GERRARD 4637.

K. RAYMOND 27, LISLE STREET, LEICESTER SQUARE, W.C.2

No responsibility accepted on post orders unless cheques and postal orders are crossed and made payable to the firm. Moneys sent must be registered

HOURS OF BUSINESS:
DAILY . 9 to 7.45
SUNDAY . 10 to 1

POST PAGES OVERLEAF.

THIS PAGE IS FOR CALLERS ONLY

ALL POST ORDERS FROM THE OTHER TWO PAGES

Prices subject to alteration without notice. Every endeavour made to keep large stocks; but am not responsible for manufacturers' non-deliveries.

NO POST ORDERS FROM THIS PAGE.

OPEN
WEEKDAYS
9 to 7.45
SUNDAYS
10 to 1

SUNDRIES.

- Legless Valve Holder .. 10d.
- Solid Ebonite .. 1/5
- 'Phone Cords (6 feet) .. 7 1/2d.
- Nugraving .. 3d.
- Similar Sets (Titles or Scales) .. 2d.
- Good Knobs .. doz. 4 1/2d.
- Studs, Nuts and Washers .. 3d.
- Switch Arms .. Sd. to 1/-
- Copper Foil .. ft. 2 1/2d.
- 18g. Sq. Tin Copper .. 5 ft. 5d.
- 16g. Sq. Tin Copper .. 10 ft. 5d.
- Round Tin Copper, various Sizes.
- Insulated Staples .. 5 a 1c.
- Insulated Hooks .. 4 for 3c.
- Rubber Lead-in .. 30ft. 1/-
- 7,22 Copper Aerial, 100 ft. 1/10
- Extra Heavy Aerial, 100 ft. 2/- and 2/3
- Good Valve Holders .. 3d.
- H.F. Transformers, 300/600 .. 2/9
- Empire Tape, 1/2 in., 2 yds. 1d.
- 6 in. Ebonite Anticlip Handles .. 8d.
- Connecticut Switches .. 3/4
- Sorbo Rubber Ear Caps .. pr. 1/4
- Adhesive Tape Roll .. 2 1/2d.
- Allon var. Gd. Lk. .. 1/3d.
- Allon Anode Res. .. 1/3
- Scales, 0-180, 2d., 3d., 4d.
- Dial and Knob (Ed. Bell) .. 1/3
- Dial (Ebonite) .. 10d.
- Brunet Headphones .. 14/6
- Twin Flex .. 4 yds. 6d.
- D.C.C. Bell Wire, 10 yds. 5d.
- (Indiarubber covered).
- Steering .. yd. 4d.
- Wander Plugs .. pr. 3d.
- Coloured Plugs each 1 1/2d.
- (All screw pattern).
- Electron Aerial .. 1 3/4
- Polished Boxes, 8 by 6 .. 3/6
- Strong Valve Template .. 4d.
- Egg Insulators .. 1d.
- Reel ditto .. 1d.
- Thick Rubber Lead-in per yd. 2d., 3d.
- Ribbon Aerial, 100 ft. 1/10
- Panels Drilled.
- Radio Press Envelopes.
- Raymond Fixed Condensers, .001, .0001 to .0005 .. 10d.
- .002, .003, .004 .. 1/-
- .006, 1/3; .01, 1/9; .02, 1/9
- Polar Micrometer Condenser .. 5/6
- 2 Meg. Grid Leak .. 10d.
- Rubber Lead-in, 10 yds. 1/-
- Valve Windows, 6d., 7d., 9d.
- R.I. Choko Coil .. 10/-
- Lissen Ditto .. 10/-
- Bretwood Valve Holder 1/9

SWITCHES ON.

- Porcelain D.P.D.T. .. 1/7 1/2
- Porcelain S.P.D.T. .. 1/7 1/2
- Ebonite D.P.D.T. .. 1/8
- Ebonite S.P.D.T. .. 1/3
- Min. Panel D.P.D.T. .. 10d.
- Min. Panel S.P.D.T. .. 10d.
- Tungstalite .. 1/-
- Microstat .. 2/6
- Tumbler Switches (Ebonite) .. 1/4
- Fibre Strip (for Coils) 3 ft. 2 1/2d.
- D.C.C. Wire, per 1/2 lb. .. 9d.
- 18g. .. 9d. 20g. .. 10d. 22g. .. 10d. 24g. .. 1/-
- 26g. .. 1/1 28g. .. 1/3
- 30g. .. 1/6 Etc., etc.
- Solder .. per stick 2d.
- 2 Colour Flex .. yard 3d.
- Shellac .. 5d.
- Battery Box .. 4/6
- (with clips for 36 v.)
- Nickel Pillar Terminals .. 2d.
- Nickel Contact Studs .. 2 for 1 1/2d.
- Nickel Switch Arm .. 1/-
- (one-hole fixing).
- Loading Coil and plug .. 8d.
- Condenser Brushes .. 6d.

BRASS PARTS.

- W.O. Terminals .. 1d.
- Small Pillar .. 1d.
- 'Phone 4 B.A. .. 1d.
- 'Phone 2 B.A., 2 for 2 1/2d.
- Valve Sockets .. 4 for 3d.
- (Above with Nut Washer)
- Valve Pins and Nuts, 2 a 1d.
- Stop Pins and Nuts, 2 a 1d.
- Plug and Socket .. pr. 1d.
- Spring Washers .. 4 a 1d.
- Spade Screws .. 1d.
- Pin Screws .. 2 for 1 1/2d.
- Spade Tags .. 5 a 1d.
- Spring Pillar Terminals 2 1/2d.
- Nuts, 2, 4, 5, 6 B.A. doz. 2d.
- Washers (Brass) 12 a 1d.

DETECTORS, &c.

- Enclosed Brass, large .. 1/3
- Ditto, Nickel or Brass, large .. 1/6
- Small Brass .. 9d.
- Ebonite, enclosed .. 1/-
- Burndep .. 1/-
- Easi-Fix Cups .. 1d. and 1 1/2d.
- Gold Spearpoint .. 3d.
- Neutron Crystal .. 1/6
- Hertzite (Shaw's) .. 1/-
- Midite .. 6d.

VALVES.

- Dutch Detector .. 4/9
- Dutch "R" .. 5/-
- Phillips "R" .. 7/6
- French "Metal" .. 6/11

TOOLS.

- Set of Spanners .. 1/4
- Taps, 0, 2, 4, 6 B.A., set .. 2/-
- Small Soldering Irons .. 6 1/2d.
- 7-Twiss Drills .. 1/4

SHAW'S HERTZITE

BEATS ALL OTHER "ITES." 1/-
Impossible to Advertise All the Goods Stocked.

MYERS VALVES.
UNIVERSAL D.E. 12/6 21/-

EXIDE. D.T. 9 Type. 2 Voits. (Glass). (For .06) 5/-

EBONITE PARTS.

- Good Coil Plugs from 4 1/2d.
- Edison Bell Shaped .. 1/-
- Raymond Ditto .. 10d.
- Basket Adapters .. 3 1/2d.
- Also at 1/- and 1/3
- 2-way Coil Stands .. 2/6
- With Extens. Handle .. 2/11
- Also at 3/6, 4/6, 5/6
- 3-way .. 4/8, 4/6, 5/6
- Goswell Cam Vernier .. 9/-
- Franco Cam Vernier .. 12/6
- Polar Cam Vernier .. 11/-
- Etc., etc.
- Coil Plug on Stand .. 1/-
- Ditto, Swivel Movement 1/3
- Coil Plug and Clips .. 6 1/2d.

H.T. BATTERIES.

- Best Made 30 v. .. 4/6
- Best Made 60 v. .. 7/6
- Best Made 66 v. .. 3/6
- B.B.C. 9 volts .. 3/-
- B.B.C. 60 volts .. 9/6
- B.B.C. 36 volts .. 5/6
- B.B.C. 16 volts .. 2/6

EBONITE STOCK SIZES
3/16 in. 6 x 6 1/4
7 x 5 1/4
8 x 6 1/10
9 x 6 2/-
10 x 8 3/-
12 x 6 3/-
12 x 9 4/3
12 x 12 5/6
14 x 10 5/8

Cut to size 1/2 sq. inch. WE STOCK 1/2 in. EBONITE.

CRYSTAL DETECTOR.

Glass enclosed. Micrometer adjustment. 1/9

MURRAY VALVE HOLDER (Patent) 1/3

Blue and Red TUNGSTALITE

MIDITE. GEGOSITE. NEUTRON Stocked.

SIMPLEX LEAD-IN 1/3

"POPULAR WIRELESS" FREE TO CALLERS. (Limited number, of course.)

BRASS FORMER. (DOUBLE) 23 spokes each side 2/11
Make your own coils.

BEST SWITCH ARM 12 Studs. THE LOT 12 Nuts. 12 Washers. 1/-

FAMOUS N & K New Model Headphones. Genuine 4,000 ohms. BEWARE OF RUBBISH. Price 17/6

"METAL" (FRENCH) '06 VALVES. 15/11.

DR. NESPER. (SEE TRADE MARK) 4,000 OHM 'PHONES 12/11 (NOT DR. "ANYTHING"!)

VARIOMETERS.

- Impregnated Board, Wound D.C.C. and Clips, 200/600 metres Very Good Value, Wound D.C.C. and Knob .. 1/8
- Ebonite D.S. Wound, with Ball Rotor and Knob, 200/700 metres .. 5/11
- Ebonite, 200/600 .. 3/11
- Raymond Inside Winding 8/11

RHEOSTATS.

- Small 5 ohms "C" .. 1/3
- One Hole Fixing .. 1/3
- Ormond .. 1/9
- Ebonite Former .. 1/6
- Ditto and Dial .. 1/10
- Igranic, T.C.B. and all known makes.

16g. D.C.C. USUALLY IN STOCK

FIBRE STRIP (For Coils) 3 ft. long, 1 in. wide. 2 1/2d. per length.

BREAST DRILLS. 0 to 1/2 chuck Cut Bevel and Gear 4/9

BOXES
7 x 5 9 x 6 12 x 9
8 x 6 10 x 3 12 x 12

BASKET COILS

- LUXE WAXLESS (5) 1,200/2,000 metres .. 1/3
- WAXLESS SET OF 5 .. 1/11
- 25, 35, 50, 75, 100 .. 3/9
- Ditto with extra air space .. 1/3
- D.C.C. CHELMSFORD .. 1/2
- ENAMELLED Do. .. 1/8
- WAXED (6) 200/3,600 .. 1/10
- Ditto (7) 150/3,600 .. 1/10
- (For Broadcasting only)
- D.C.C. COIL FOR CHELMSFORD complete with adapter .. 2/3
- (to use with 650 variometer)

Best BATTERIES 4'5, 5d.

MANSBRIDGE TYPE FIXED CONDENSERS With 2 Fixing Lugs. .25 Special Price 3/6
2 Microfarad .. 3/11

"ORMOND" L.F. 13/11 A WONDERFUL TRANSFORMER.

ACCUMULATORS MADE BY WELL-KNOWN FIRM FOR ME.
2 v. 40 amps. .. 9/6
4 v. 40 amps. .. 16/6
4 v. 60 amps. .. 17/11
4 v. 80 amps. .. 23/6
6 v. 60 amps. .. 17/6
6 v. 80 amps. .. 23/-
6 v. 105 amps. .. 23/6
Hart Accumulators Stocked.

PHILLIPS 4 ELECTRODE VALVE 12/6

DUTCH '06 VALVES 12/6

GAMAGES PERMANITE 1/-

COSSOR "WUNCCELL" 21/- Few only.

Experimenter's Sets of 4 Cat's-Whiskers 2d.

OUR WONDERFUL H.T. BATTERIES
30 v. 4/6 60 v. 7/6
66 v. 8/6

BROWNIE "IMPROVED" WIRELESS SET 7/6

RAYMOND CRYSTAL SETS
7/11 9/11 12/11

NO POST ORDERS FROM THIS PAGE.

RIGHT OPPOSITE
DALY'S
GALLERY DOOR
PHONE: GERRARD 4637.

K. RAYMOND
27, LISLE STREET,
LEICESTER SQUARE, W.C.2

HOURS OF BUSINESS:
DAILY - 9 to 7.45
SUNDAY 10 to 1

No responsibility accepted on post orders unless cheques and postal orders are crossed and made payable to the firm. Moneys sent must be registered.

Readers' Results with T.A.T. Circuits.

T.A.T. SUCCESSES. In N. Wales.

To the Editor of MODERN WIRELESS.

SIR,—As requested in your article on the T.A.T. system of H.F., I herewith send results obtained from the three-valve with the stage of L.F. —

All B.B.C. Main Stations.—Moderate L.S. strength.

Munich—Moderate L.S. strength.

Voxhaus—Fair L.S. strength.

Petit Parisien—Moderate L.S. strength.

Radiola—Moderate L.S. strength (300 choke, 200 anode, 150 aerial).

Madrid—Moderate L.S. strength.

Choke coil 110 (home-made), lattice coil 200 I find weakens signals considerably. H.T. voltage 55 actual, 6-volt. L.T., Manchester and Chelmsford can be heard at good 'phone strength without any aerial coil.

Manchester 70 miles and Chelmsford at good L.S. strength, with no reaction.

Yours truly,

BERTRAM BELL.

Rhyl, N. Wales.

[This circuit is similar to that of set described in this issue.]

In Ireland.

To the Editor of MODERN WIRELESS.

SIR,—I am writing to you to tell you how much I appreciate your articles on high-frequency amplification which appear in MODERN WIRELESS.

None of your articles, however, interested me so much as those appearing in the last issue, which were on the Tuned-Aperiodic-Tuned system. The article was most interesting all through.

I am seventeen years old and have been at wireless just over a year. I bought the components for a four-valve (1 H.F. Det. and 2 L.F.) set, but as I had never seen a set wired a wireless operator friend of mine wired it up for me.

The set worked well for about two months, when trouble developed, which, after I had taken the set to pieces for all the parts to be tested, was located in a faulty .0003 variable condenser and a .0003 fixed condenser.

To facilitate trying several circuits I soldered no connections when rewiring the set again. Since that I have tried nearly a dozen four-valve circuits, but none with 2 H.F. valves.

No. 12 Circuit.

When I read your article in MODERN WIRELESS I decided to try circuit No. 12 (2 H.F. and Det. with reaction on aerial), to which I added my fourth valve as L.F. and provided a switch to cut it out at will, but the L.F. is unnecessary. I may add that all connections are now by locknuts and terminals, but as I have now found an excellent circuit I think after a few additions have been made I will solder all joints.

As I was confined to bed last week until Saturday I did not get it tested on my good aerial but tested it on a very poor aerial and earth arrangement erected by my little nephew, aged seven.

A Bad Aerial.

The aerial is 25 ft. of electric light wire (3/20's) running from a plum tree 5 ft. high in the garden to my bedroom window. The earth is one strand of No. 24 S.W.G., D.C.C. wire, joined to a tin plate 3 in. by 2 in., buried 6 in. in sandy soil. The aerial, I may add, runs between two walls, 4 ft. apart, so it is badly screened.

With this very inefficient arrangement I can, when using the No. 12 circuit with 1 L.F. valve, tune in every B.B.C. station, relays included, and ten Continental stations. I also received six amateurs, one of these was 8AQ, and the language used was, I think, French.

Yesterday (Sunday) I tested it on my full size aerial with good earthing system. The results were truly amazing and were as follows:

All B.B.C. Stations.

Every B.B.C. station at excellent L.S. strength and eight Continental stations at same strength. Fourteen other Continental stations on three valves, and about thirty amateurs were received. I got 2 LK with such strength that I added a second L.F. valve and could hear him all over the house on the full size Claritone loud-speaker.

I have not yet sat up for any American stations, but hope to do so after I have recovered sufficiently from my illness. I will write later and let you know the results of my future experiments with the circuit.

The set is much more stable than any set I have tried, using reaction. The layout of my existing panel makes it possible to use extremely short wiring although all parts are well spaced, as there is plenty of room on the panel, which is 24 in. by 10 in.

Great Stability.

As the set is so stable I would like to be able to cut out one or both H.F. valves at will when listening to the local station (Belfast). Here again is a point worthy of note. Belfast is only about eight or ten miles away and I can, without wave-traps or any other fine tuning arrangements, cut him out and get any other station but Glasgow, without the slightest interference. Glasgow can be tuned in well enough to be free from serious interruption from the local station.

As I shall be at home some time, probably all winter, if there is any way I can help you in your experiments or otherwise I shall be pleased to do so, as it would help me to pass the time at home. I am studying wireless from some books and I have read almost every Radio Press book yet published.

Yours sincerely,

B. GRAY.

Dunadry,
Co. Antrim.

At Sheffield.

To the Editor of MODERN WIRELESS.

SIR,—I had given H.F. amplification up in disgust and come to the conclusion that a D. and L.F. system with a good tuner was all that one could desire from the standpoint of "D.X." reception. Last night I read your article on T.A.T., and decided to change my two-tuned anode set, which was the last word in instability, to your system. Using a 150 Basket coil as choke and No. 50 as reaction—stations to profusion. Yes! real amplification on such stations as Leeds, Manchester and Birmingham.

ham. I am going to change to 3 H.F., D., 1 L.F., for the next two weeks and will let you know results on America and other "D.X." stations. I am sure it is the last word in H.F., and will prove a system which has come to stay.—Yours truly,

ALAN G. STEWARD.

Sheffield.

[I advise you to try four stages of T.A.T. amplification instead of three.—Ed.]

In Spain.

To the Editor of MODERN WIRELESS.

SIR,—Just a short line of appreciation. A friend of mine here has been using a high-frequency receiver consisting of three H.F. valves and detector with excellent results on the long waves, using tuned anode coupling, the first two valves being tuned by a Bowyer-Lowe square-law double condenser and the third tuned by a separate condenser, reaction being applied to this valve from the detector; however, he has always experienced great difficulty in receiving the shorter wave stations until I told him about your T.A.T. system, and last night he connected up for the short waves using your figure 8 system, MODERN WIRELESS, Vol. III, No. 6, and was able to receive all B.B.C. stations, including Manchester, which is one of the most difficult stations to get here in Gibraltar. The set is very stable with this system, and for long-distance reception I do not think it can be beaten.

I, myself, am using a single-valve reflex neutrodyne, on which I have been receiving 5XX regularly here very clearly.

Wishing your periodicals every success in the future.—Yours truly,
C. W. BIDDULPH.

Gibraltar.

**America on "The
4-Valve T.A.T.
Receiver."**

On the night of the 19th instant, under unfavourable conditions, KDKA and WGY were received by the Author at Bush House, at moderate loud-speaker strength.



Under Sir Wm. Mitchell-Thomson, the new Postmaster General, amateurs hope to gain an improved status.

Special Note on the Transatlantic Four.

In the "Transatlantic Four" receiver, described by Mr. Percy Harris in the November issue, a Lissen Five Point Switch is used. In order to make the connections quite clear a special switch diagram was also inserted. This is perfectly correct for the switch used, but for some reason best known to themselves Messrs. Lissens have since altered the order of contacts, completely upsetting the accuracy of our diagram. The switch now supplied has the contacts arranged as if our diagram (Fig. 2) were viewed from the front of the panel. Those readers who find difficulty in making the correction are advised to return their five-point switch direct to Messrs. Lissens, who will supply in return a switch of the original pattern.

We take this opportunity of emphasising the importance of manufacturers adhering to their original designs in such matters, or, if they intend to change them, of advising Radio Press, Ltd., of their intentions.

Obviously, in the present case, we could do no more than indicate the exact arrangement of the switch points, and the manufacturers' alteration was quite unknown to us.


Readers who are wiring up the set from Fig. 4, and not from the blueprint (which is quite clear), should note that in some copies there appears to be a connection dotted between I.S. of the first H.F. transformer and the long dotted line (positive L.T. lead). This is superfluous and should be deleted. In V_1 , V_2 , the second transformer, V_3 and V_4 , the connection is necessary.

A great deal of doubt frequently arises as to the question of what coil is the correct one to use for reception on a certain wavelength. The MODERN WIRELESS Coil Table, which has just been published, enables you to solve this difficulty at a glance.

The various wavelengths used for broadcasting have been classified, and different makes of coils are given with their appropriate numbers or letters to cover these wavelengths. It is therefore only the work of a second to determine what coil to use in order to receive a certain transmission. So that this table may form a permanent record, it has been printed on stout card, and can be obtained for 6d. a copy, post free.


P.W.H.

"GOLTONE" LOW FREQUENCY TRANSFORMER.

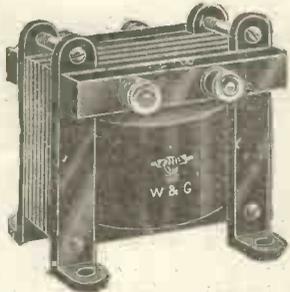

Regd. Unsurpassed for Silence, Efficiency and Reliability. Provides remarkable amplification with freedom from noise and distortion. Equally suitable with every type of Transformer gives better results.
Price 17/6

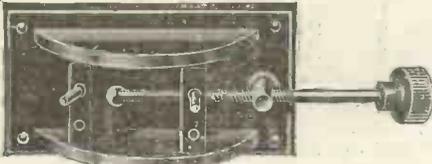"GOLTONE" MICROMETER REGULATING COIL HOLDER.



A high-grade instrument. Enables the finest possible tuning and considerably improves the Selectivity, Efficiency and Reliability of the Receiving Set.
TWO COIL TYPE 9/- each.
THREE COIL TYPE 12/6 each.
See Catalogue for other types.
W & G FIXED CONDENSER.



Stocked in all standard capacities. Mica dielectric. Each instrument laboratory tested.
No. 5701. 1/3 each.

THE BEST of all CIRCUITS

Is of little value if your components are inefficient. The use of our "Goltone" (Regd.) Transformer, combined with our "Goltone" Coil Holder, ensures the maximum possible results with simplicity of control.


"GOLTONE" NO-CAPACITY SWITCH.

Fitted with screwed front plate for Panel mounting.

Very compact, easily fitted and possesses a strong, quick and sure action.

No. R17/100
2-way Double Pole
3/6 each.


No. R17/110
4-way Double Pole
5/6 each.

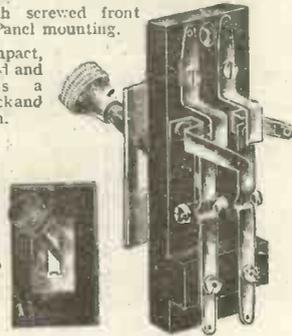

These lines are stocked by all high-class Radio and Electrical Stores.

"GOLTONE" Regd. WAVE TRAP.

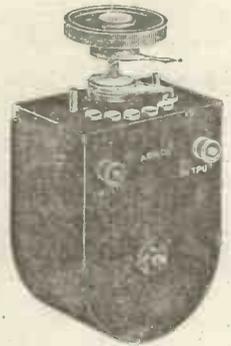An effective instrument when used in conjunction with a variable condenser .0005 mfd., for eliminating signal interference up to 600 metres. Easily fitted. No. R5/750 12/6 each. Complete with Variable Condenser, ready wired up and enclosed in polished hardwood case with Ebonite Panel.




No. R5/1750. 32/6 each.

"SAMPSON" ACCUMULATOR CARRIER.

Patent No. 214037/23. Light, strong and exceedingly useful.

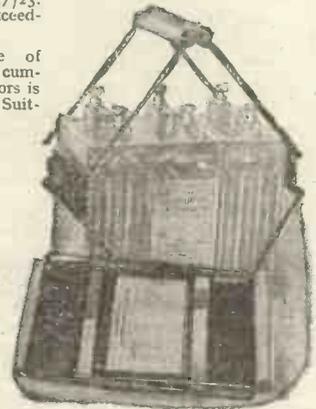The inconvenience of handling weighty, cumbersome accumulators is entirely obviated. Suitable for any size accumulators. Folds flat to fit the pocket. 3/- each.



WARNING!

Rigorous action will be taken against infringements of this patent.

Fully illustrated: Catalogue R/110; free on request; Enclose business card for Trade; Terms.



Address all communications to Head Office and Works: **PENDLETON - MANCHESTER**
Stocks also held at Glasgow Depot, 95, Pitt Street. Write direct if unobtainable.

B.B.C.

WIRELESS DRY BATTERIES

For **B.B.C.** Sets


No. 1 W.

Standard Pocket Lamp Size—4½ volt with patent spiral wire terminals and plug sockets to take Wander Plugs.

Note:—1 doz. = 54 volts.

Used units replaced easily.

Connect as illustrated.

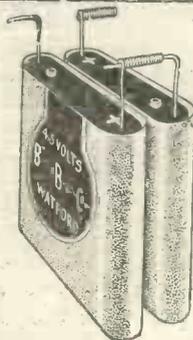

To connect in Series insert straight Terminal in Spiral of next battery. Bend spiral and thus ensure permanent electrical connection without soldering.

BRITISH MADE.

Patent applied for.

PRICE CARRIAGE PAID, 7/- PER DOZEN, WITH PLUG.

Standard Sizes:

No. 2 W. Slab. 16½ volts, 3-volt tappings. 9 x 1 x 3 ins.	Size approx.	Price 3/- each
No. 4 W. Slab. 36 volts, 3-volt tappings. 10 x 1½ x 3 ins.	Size approx.	6/6 "
No. 5 W. Block. 60 volts, 3-volt tappings. 9½ x 3½ x 3½ ins.	Size approx.	12/- "

Prices include Wander Plug. Carriage Paid.

Manufactured by—


Telephone: Watford 617.

The BRITISH BATTERY CO. LTD.
CLARENDON RD., WATFORD, HERTS.



SQUARE LAW CONDENSER

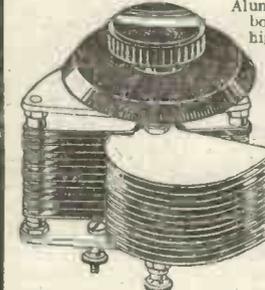A handsome unit of the Finston series of components, thoroughly efficient and possessed of those qualities which serve to make all Finston products immune from trouble in the most exacting and protracted use. They stand the test of time.




Aluminium top and bottom plates, high-grade ebonite composition knob and dial, cleanly engraved 0-180. Vanes 98 per cent. pure aluminium.

PRICES.

.001	9/-
.0075	8/6
.005	8/6
.003	7/6
.001	6/6
.0005	6/-

If your local dealer cannot supply Finston components, send your order to us together with his name and address.

FINSTON STANDARD VARIOMETER

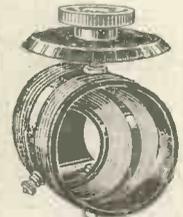

Another trustworthy component. Extremely moderate price.

Ebonite stator, high-grade ebonite moulding rotor, engraved dial and knob. Price 5/6

FIXED CONDENSERS
Guaranteed within 5% of stated capacity, this accuracy has never before been obtainable by the public. Buy one. Test one. It will prove our statements and thoroughly satisfy you. FEATURES: Reliability of Capacity. Finest grade mica by Mica Di-electric. Highest quality Copper Foil. Adapted for Terminal or soldered connections.


CAPACITIES:
.001 to .005, Price 1/3 each.
.002 to .006, Price 2/- each

LIGHTING SUPPLIES COMPANY
2, FINSBURY AVENUE, LONDON, E.C.1.

GET FINE TUNING

it means signal strength

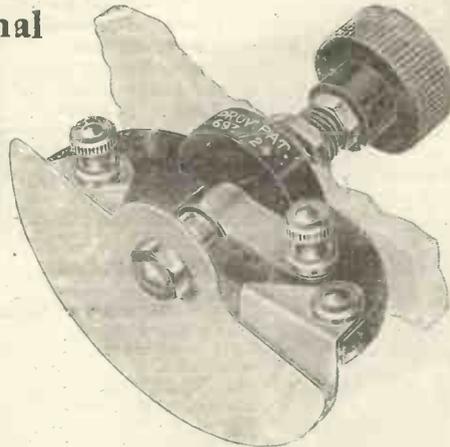To secure maximum signal strength requires something more than good components and a well-designed set. The best is only obtained from your sets when, besides skilful tuning, you have the means provided whereby skill may be rewarded with exceptional results.



PRICE
2/6

While the potential signal strength of any receiver may be good, large tuning condensers fail to balance circuits into resonance, so that the receiver cannot function at its best. With the use of large tuning condensers—since they do not allow delicate movement—tuning is never accurate. The advantages of circuits with razor-sharp tuning are therefore never used to their utmost capacity. But really accurate and delicate tuning is at once within the reach of every experimenter if fine tuning devices are incorporated. *Do not use a vernier in association with the large condenser.* Fit an independent vernier—it gives finer tuning. The COLVERN (max. cap. .000014 mfd.) will make your tuning razor-sharp, enable you to build selective receivers and will demonstrate that your set is more sensitive to perfect balance than you have yet experienced. Remember—the COLVERN.

If your local dealer does not stock the COLVERN TUNING CONDENSER, kindly send his name and address when ordering.

COLLINSON'S PRECISION SCREW CO., LTD.
Macdonald Rd., Walthamstow, London, E.17. Tel.: WAL 532

Barclays 318.

“UTILITY”

NO CAPACITY



W.M. 147/2.

LEVER PATTERN.		each
No. WM 147/1	(1 Pole C.O.)	4/6
No. WM 147/2	(2 „ C.O.)	5/-
No. WM 147/3	(3 „ C.O.)	6/-
No. WM 147/4	(4 „ C.O.)	7/6
No. WM 147/5	(5 „ C.O.)	10/-
No. WM 147/6	(6 „ C.O.)	10/-
KNOB PATTERN.		each
No. WM 130/1	(1 Pole C.O.)	3/9
No. WM 130/2	(2 „ C.O.)	4/-
No. WM 130/3	(3 „ C.O.)	5/-
No. WM 130/4	(4 „ C.O.)	6/-
No. WM 130/5	(5 „ C.O.)	7/-
No. WM 130/6	(6 „ C.O.)	8/-

Black Bronzed.

Lever type nickel plated 6d. each extra.


WILKINS & WRIGHT, LTD.,
Utility Works, Kenyon Street,
BIRMINGHAM.

SWITCHES

ADVICE TO THE HOME CONSTRUCTOR

**WHY
BUY
EBONITE ?**

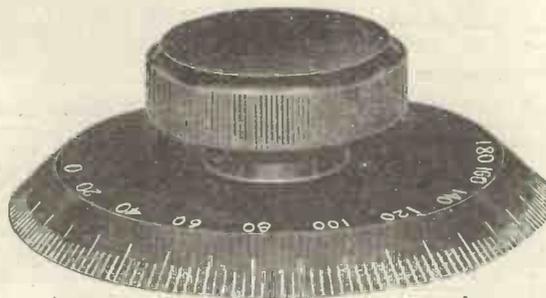It is expensive and its surface deteriorates under the action of light.



A Moulded TROLITE knob and dial.

**DON'T
BUY
INEFFICIENT
SUBSTITUTES
FOR EBONITE**

They bring untold troubles and are generally of poor appearance.

Ask your dealer for TROLITE

Trolite is backed by a National Physical Laboratory Certificate showing highest insulation resistance and dielectric strength combined with a low-power factor.

TROLITE FOR PANELS AND MOULDED PARTS has the following advantages over EBONITE :—

- (1) It is cheaper.
- (2) It does not discolour or lose its surface insulation under the influence of light.
- (3) It can be supplied with a brilliant polish free from surface leakage.
- (4) It is soluble in acetone, and this substance can be used as an adhesive. A joint made with acetone is as strong as the material itself. Trolite components can thus be fixed to a Trolite Panel without screws.
- (5) It can be supplied in various colours and fancy designs.

WHOLESALE
ONLY

F. A. HUGHES & CO., LTD.

204-206, Great Portland Street, London, W.1.

ESTABLISHED 1868.

Telephone : Museum 8630-2 (3 lines.)

Telegrams : “Distancing, Wesdo. London.”

WHOLESALE
ONLY



"THE ALL BRITAIN."

To the Editor, MODERN WIRELESS.

SIR,—In your September MODERN WIRELESS you ask for results from constructors who have made sets from the instructions given in your paper.

I have made up the "All-Britain" (three-coil) set according to your plans with the following exceptions.

I was unable to obtain "Clix" locally, and so used ordinary terminals.

Having by me a "Raymond" .0003 (with integral vernier) condenser, I did not use a separate vernier on the second valve circuit. I also used an old (and good) transformer. Otherwise I followed your instructions exactly.

After one hitch, the nature of which I will explain later, I was able to receive on the first night of trying all the British stations (except Manchester) and the relays, Radiola, Brussels, P. and T., and three German stations.

London, Chelmsford, Brussels and Radiola good on a loud-speaker. Newcastle fairly good, and Bournemouth, Glasgow and Aberdeen audible on the L.S.

When first trying the machine out I was able to hear nothing except Chelmsford very faintly.

The only new parts in use were a three-coil holder and a Utility switch.

The coil holder was bought by me from one of the large shops in London, and for which I gave a fair price. It was a beautiful looking affair and had the finest polish I have ever seen on ebonite. When I had taken it to pieces and thoroughly removed every bit of polish, the set functioned perfectly.—Yours truly,

R. C. B.

East Malling, Kent.

To the Editor of MODERN WIRELESS.

"A CRYSTAL SET."

SIR,—I have made the crystal set described by Mr. Harris in Sep-

tember MODERN WIRELESS, and tested same, and it is everything he states. It is the loudest and clearest set I have heard. I got Newcastle testing on Friday night, the 12-9-24, between 7-30 and 7-45 as clear as a bell. I can get Leeds on all studs. I have a good aerial 100 ft. long and 22 ft. high, $5\frac{1}{2}$ miles from Leeds. But the loudest place on the studs is with the aerial switch arm on stud 3 and the earth arm on stud 2.

I shall recommend anyone making a crystal set to make your model, as it is worth the cost.—Yours truly,
SAM LONGBOTTOM.

Morley, nr. Leeds.

To the Editor of MODERN WIRELESS.

SIR,—May I congratulate Mr. P. W. Harris for having designed still another first-class circuit. I refer to the crystal set described by him in MODERN WIRELESS, Vol. III. No. 4.

I have just completed this little set, and am truly delighted with it, as it is certainly infinitely better than any other crystal set I have ever listened to. I followed his instructions for erecting this set, but used components I could obtain locally. A list of these are: Woodhall variable condenser, Burndept micrometer adjustment detector (I find this a wonderful little component) and Bowyer Lowe switch-arms and studs, also that firm's coil-holder and short circuiting plug.

All these tests were made on an outside aerial about 90 ft. long, mounted on masts 8 ft. high on the top of a tenement building on the north side of this city.

Even with this height from the ground (approx. 150 ft.) we are still heavily screened from 2 EH, which is about two miles distant. This afternoon our local station was broadcasting an orchestral selection for one hour, which came through (very loud) on two pairs of phones (Brandes being used), the switch settings being as in Fig. 4 with 50 degrees on condenser:

After our station closed down at

4 p.m., I hunted round and got Glasgow, which is about 40 miles as "wireless" flies.

The best reception up till the time of writing is the Savoy Bands, which are coming in just now even louder than this afternoon's programme, with switch settings as in Fig. 4, but with only 35 degrees on condenser.

Taking into consideration that our station is not a strong one, and the distance and locality we are in, I think this speaks volumes for this little crystal set.

I can only conclude by wishing MODERN WIRELESS and *Wireless Weekly* every success which they most assuredly deserve.—Yours truly,
J. M.

Edinburgh.

"A THREE-VALVE RECEIVER."


To the Editor of MODERN WIRELESS.

SIR,—I recently constructed "A Three-Valve Set with Resistance Note Magnifier," by Mr. H. K. Simpson, in October MODERN WIRELESS.

I thought it may be of interest to know I received WBZ, Boston, Mass., on November 11-12, about 1 a.m. our time. The band came through at splendid 'phone strength, while speech occasionally faded. The programme I heard included a band selection, Armistice oration, address on "Eternal Youth." Band: "Keep the Home Fires Burning," "A Long Way to Tipperary."

The above songs were then sung (by a Mrs. Williams), accompanied on the piano. Coils used were 50 anode, 50 aerial, 75 reaction. Aerial, 50 ft. long (single), 30 ft. high. Aerial lead on terminal C. With constant aerial tuning the set works my Baby Sterling from Liverpool at about 5 miles, and Manchester about 40 miles (using 120 volts H.T.). My thanks to Mr. Simpson and success to M.W.—Yours truly, F. HAYNES.

Wallasey, Cheshire.

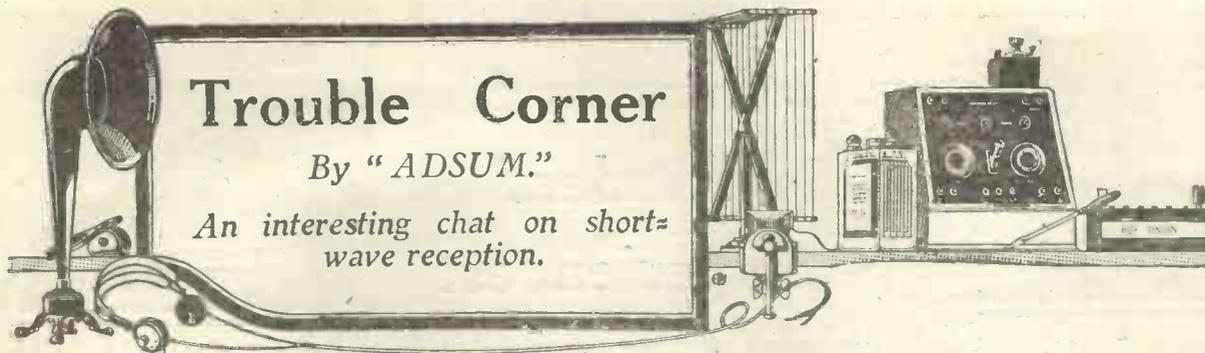

SHORT wave reception is becoming increasingly popular nowadays amongst amateurs, and it has a peculiar fascination of its own. In the first place, it is rather difficult even to get down to 100 metres and under, unless special care has been given to the design and construction of the set. Then the tuning is so sharp that signals may be missed altogether unless one is accustomed to doing very fine work. The problem of hand and body capacity also plays a very important part, and, in addition, we find that there are quite a number of troubles to be met with on the lower wavelengths which are practically unknown on the broadcast band and

with frequencies up to five or even six times this amount. Some idea of the sharpness of the tuning required is obtained by remembering that if we increase the wavelength from 60 to 75 metres, we vary the frequency from five million to four million per second—this is only for 15 metres. Lower down in the scale there is a frequency difference of a million in the 10 metres between 50 and 60 metres. On the broadcast band, if we turn from the Sheffield relay station (301 metres) to Newcastle (400 metres), an increase in wavelength of 100 metres, the frequency change is approximately from one million per second to 750,000 per second. That is to say a frequency difference of only a quarter of a million represents a wavelength change of 100 metres.

here that careless wiring of any kind is quite unsuitable. All wiring must be short, and every joint must be securely soldered. The wire used should be of heavy gauge—not less than 18 or 16—so that it may offer the smallest high-frequency resistance. In this connection it should be noted that plain copper wire has a smaller high-frequency resistance than that coated with tin. Personally I prefer wire to square rod for wiring. Whether wire or rod is used, the constructor must be careful to avoid any kind of parallelism at short range between leads at different potentials, and it is a good rule to keep leads at least one inch apart where they must cross each other. So far as is

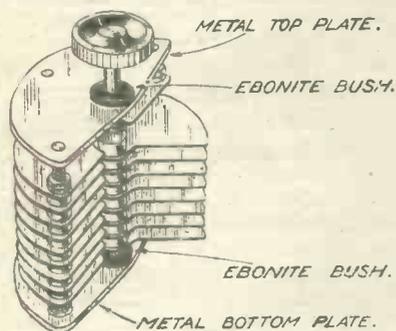


Fig. 1.—A condenser which may be unsuitable for short-wave work.

above it. Fortunately short wave signals come in at considerable strength, so that it is usually unnecessary to employ high-frequency amplification. This makes matters very much easier, for there is probably no "straightforward" method of high-frequency amplification which is at all stable when dealing with oscillations with frequencies ranging from three million to five million per second. These figures will help us to appreciate some of the difficulties involved. The highest frequency used in broadcasting in this country is slightly less than one million per second. The short-wave set must be capable of dealing effectively

Wiring and Design

When we get down to the very short wavelengths the effects of stray capacities become very much more marked than they are higher up the scale. This is only to be expected when we remember that the higher the frequency the smaller is the capacity needed to offer a perfectly free path to oscillating currents. This means that a set which will work quite well on the broadcast wavelengths may be "all over the place" on 100 metres or below. In designing a short wave set it is best to be on the generous side in the amount of space allowed for components. Besides preventing capacity couplings between them, it is also a very great help to tuning. If, for example, rheostats and condensers are crowded together, one cannot bring one's hand to the knob of a filament control without upsetting tuning owing to the effects of hand capacity on the condensers. Allow plenty of space and you will then have room to use the extension handles, which are practically essential to success. Now as regards wiring, there is no question

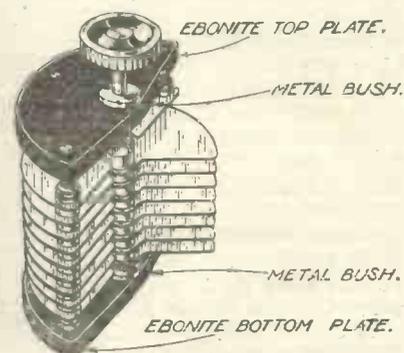


Fig. 2.—A good type of condenser for short-wave work.

possible all crossings should be at right angles. Before you make up a short wave set make quite sure that the ebonite which you intend to use for the panel is above suspicion as regards its insulating properties. The simple test described recently with a high-tension battery and the headphones is the best to employ for making certain that the ebonite is all that it should be.

Variable Condensers

For short wave work variable condensers must be of really good make and of a design that is beyond reproach. It goes almost without

saying that for ease in tuning they can be of the square law type. Fig. 1 shows a kind of condenser that may not be suitable for short wave work if really good results are to be expected. The top plate is of metal, either brass or aluminium, in direct electrical contact with the fixed vanes. The spindle to which the moving vanes are connected is insulated from the top plate by an ebonite bush through which it passes. The arrangements at the bottom plate are of the same kind.

Capacity due to Metal-End Plates

It will be seen at once that there must be capacity between the spindle and both top and bottom plates through the ebonite bushes. Ebonite has a dielectric constant which is rather more than that of air. In other words, if two plates have an ebonite dielectric between them the condenser thus formed will have a capacity more than double that of one with plates of the same size and spaced at the same distance, but with an air dielectric. The thinner the ebonite bush, the greater will be the field concentration between the end plates and the spindle, and therefore the greater will be the losses in the condenser at high frequencies.

Another point to be noted is that the insulating bushes are not always

ebonite but may be substitutes, of which there are, unfortunately; many, with very inferior insulating properties, and in which losses may be very high.

For these reasons condensers with metal end-plates and thin ebonite washers in which the fixed plates are in direct contact with the end plates, should not be fitted in sets intended for short-wave reception. A good type of variable condenser

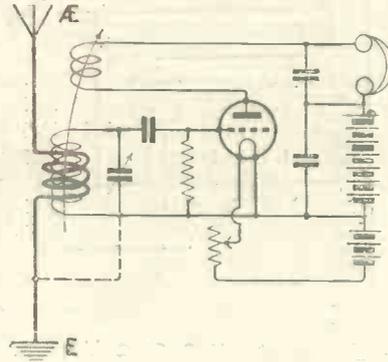


Fig. 3.—The secondary circuit should be earthed.

is that shown in Fig. 2. This is provided with end pieces made of good quality ebonite. The spindle passes at both ends through small metal bushes. An examination of either plate will show that the bush is so well separated from the points

in contact with the fixed vanes that capacity is reduced to the smallest possible amount. With the metal end-plate variable condenser the minimum capacity will usually be on the high side, whilst where ebonite end pieces are fitted it can be reduced to something very small indeed. It is of the utmost importance that the high potential end of any tuned circuit should be wired to the fixed plates of a variable condenser in order to reduce hand capacity effects as far as possible. This means that if you use a tuned primary the aerial must be connected to the fixed plates and the earth to the moving. In the secondary circuit the grid will go to the fixed plates, and the L.T. to the moving. The reason for this is quite obvious when it is remembered that the knob with which the hand comes into contact is fixed to the spindle to which are attached the moving plates. By connecting in this way we keep the moving plates at earth potential, which is practically that of the body.

Fixed Condensers

For work on very high frequencies fixed condensers must be of the very best quality obtainable. The grid condenser is the one which chiefly needs attention, for it is directly through it that oscil-



All "Sparta" components carry a comprehensive guarantee for 12 months. If during that period they develop a fault distinctly traceable to bad workmanship they will be instantly replaced. You can rely upon them.



"SPARTA" IRONCLAD TRANSFORMERS.

- Intervalve Type A. Ratio 1-5. 20/-
- Intervalve Type B. Ratio 1-4. 24/-
- Intervalve Type C. Ratio 1-4. 24/-
- Telephone Type T A. Ratio 1-10. 18/-
- Telephone Type T B. Ratio 1-10. 23/-
- Telephone Type T C. Ratio 1-10. 26/-

The deciding factor

"Smith and I set up exactly the same circuit and yet his results are twice as good as mine." How often this plaintive cry of the disappointed experimenter is heard. Yet how obvious the reason and the remedy. However brilliant the circuit, however careful the assembling, *the components employed are the deciding factor.* That's why we draw your attention to the famous "Sparta" series—built to get the best from any circuit. Of advanced design

and admirably produced, they provide the best means of obtaining permanently reliable reception. So certain are we of their satisfactory performance under all conditions that we say—"Ask the man who uses them."

Space only permits us to show three components here. Just send a card for List 316B—it fully describes the complete "Sparta" range.

Fullers United Electric Works Limited Woodland Works, Chadwell Heath, Essex


Telephone: Ilford 1200 (6 lines).
London Depot: 58, HIGH STREET, W.C.2.

Telegrams: "Fuller, Chadwell Heath."
Telephone: Gerrard 5070.



"SPARTA" VALVE HOLDERS.

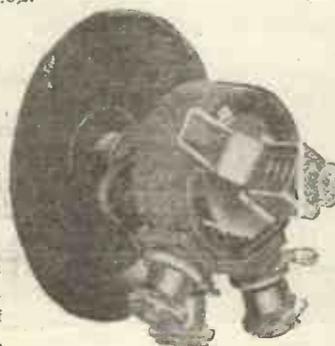Contacts marked on both sides. Earthing clip to valve cap. Low self-capacity. Made in two types. For front of panel 2/- each. For underside of panel 1/9 each.



"SPARTA" FILAMENT RESISTANCES.

Supplied for 1, 2, or 3 valves. Compact, and fitted with an "off" position, obviating the need for a special switch.

- 1 Valve Resistance 4/3
- 2 Valve Resistance 4/6
- 3 Valve Resistance 4/9

"SPARTA" Potentiometers (illustrated). Of similar design to the filament resistances, have a resistance value of 400 ohms. 6/-

In replying to Advertisers, please use Order Form enclosed.

lations reach the rectifying valve. If one of really good make is purchased no fears need be entertained as regards its efficiency, but it is the height of folly to fit to a short-wave set a cheap condenser of questionable origin. It may be found that better results are obtained by using a grid condenser of smaller value than 0.0003 or 0.00025 μ F or rather less used in conjunction with a gridleak whose value may be from .5 megohm to 1 megohm. The gridleak again must be of good quality if noisiness and instability are to be avoided.

Inductances

If we are to obtain a good voltage built up across the inductances of a short-wave set all losses by capacity must be avoided. For this reason it is undesirable to use coils made of too thinly insulated wire wound so that the turns lie side by side in contact with one another, or touching each other at various points in criss-cross winding. If turns touch there is between them the dielectric of the insulating material which may have a higher specific inductive capacity than air and be very inefficient. Heavy losses are therefore likely to occur both by capacity and by conduction through the

poor enamel covering. There are several excellent types of short-wave coil on the market in which the turns are provided with ample air space and no touching takes place between them. The experimenter will find that good results are to be obtained with these. Inductances should be wound with wire of fairly heavy gauge in order to reduce high frequency resistance,

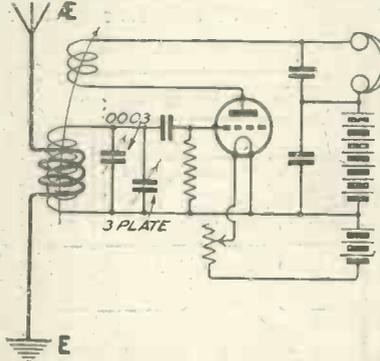


Fig. 4.—The use of a Vernier Condenser.

for any undue resistance will probably lessen the efficiency of the receiving set.

Valves

Experiments have shown that though it is best to use valves of the low capacity type such as the

V24, Q, QX, DEV, DEQ or Myers, quite good results can be obtained with those of the standard 4-pin type. It is, however, necessary to exercise a little care in mounting them. It is best to use separate valve legs of a short thin kind with 6.B.A. shanks and to screw them into tapped holes in the panel, using no securing nuts below. The tip which I gave a month or two ago for reducing capacity in valve holders is also most useful. At the centre of each group of legs drill a 5/16 inch hole right through the ebonite and from it make file cuts between each pair. In this way capacity is reduced whilst insulation is improved. The constructor need not be afraid that he will weaken his panels by doing this. I have treated all my valve-holders in this way for many months now without having a single casualty.

Some Special Troubles

Where any kind of double circuit tuner is used, whether the aerial is "aperiodic" or not, it will be found that the set is liable to become very unstable unless the secondary is earthed as shown by the dotted line in Fig. 3. By doing this we are able to keep large components such as the telephones and the low frequency transformer if one is used at

The mechanically sound Variometer

Amateurs with an appreciation of soundness in design will value the Woodhall No. 1 Variometer as being *right mechanically*.

The spindles of the Rotor are not screwed in; they are firmly moulded in, in perfectly true alignment. They cannot come loose or out of alignment, causing the Rotor to foul Stator.

Because of the degree of accuracy in alignment, we do not need a "safety-margin" of clearance, and therefore the coupling between Rotor and internally wound Stator is closer than in any other Variometer.

The spindle also has a metal bearing, giving a smooth "feel" of rotation that makes extremely fine tuning possible. All connections are internal, by spring contacts from Rotor to Stator. Two terminals are provided.

One-hole fixing for panel mounting; brackets adjustable for upright or horizontal mounting. Wave length 270 to 750 metres on 100 ft. aerial.



Sold by all Wireless Dealers, who can obtain supplies through their usual Factors.

Sole Distributors:

PRESSLAND ELECTRIC SUPPLIES, LTD., Hampton-on-Thames.

The Woodhall-Wireless Manfg. Co., Ltd.

12/6

ECONOMIC ELECTRIC LTD.



"DEXTRAUDION" DULL EMITTER VALVE
MAX. CONSUMPTION. 1 AMP. AT 1 VOLT.

1/10 OF ONE WATT!

The quality of the reception entirely surpasses anything hitherto obtained with any other valve.

It is a wonderful detector, H.F. and L.F. Amplifier, and gives marvellous rendering on a loud-speaker. **YOU HAVE NEVER HEARD ANYTHING LIKE IT!**

ABSOLUTELY NON-MICROPHONIC!

THE "DEXTRAUMER" L.F. TRANSFORMER

Specially designed for Economic Electric Ltd. by Messrs. Radio Instruments, Ltd., for use with the "DEXTRAUDION" VALVE.



PRICE

21/-

with guaranteed safe delivery.

PRICE **25/-**

MAKES A PERFECT COMBINATION.


ECONOMIC ELECTRIC LTD.

Head Office: 10, FITZROY SQUARE, LONDON, W.1.

Showrooms: 303, EUSTON RD. N.W.1

AVAILABLE MOUNTED ON POLAR BLOK PANELS

POLAR ACCESSORIES.

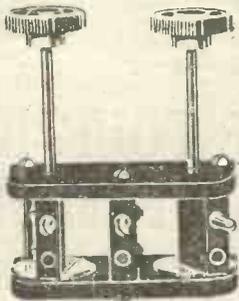


CAM VERNIER COILHOLDERS

JUNIOR TYPE
3-way Coilholder
Price 9/6

When buying a coilholder see that it is a **POLAR CAM VERNIER COIL-HOLDER**, because it has the following advantages:—

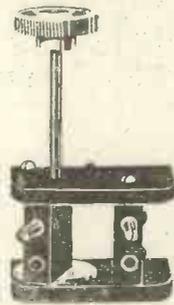- (1) A rough adjustment places the moving coil quickly into any desired position.
- (2) A cam driven by the control spindle provides a vernier adjustment at any point of the coil sweep, thus permitting extremely fine tuning.
- (3) Small dimensions.
- (4) Remarkably low cost, combined with robust construction and high-class instrument finish.
- (5) The usual Polar Guarantee



JUNIOR TYPE
2-way Coilholder
Price 6/-

RESISTANCE CAPACITY COUPLING UNITS



RESISTANCE CAPACITY Coupling Unit
Price15/-

It is impossible to obtain undistorted wireless reception if you use iron-core transformers in your low-frequency circuits.

The only way to obtain clear reception is to use Resistance L.F. amplification. To do this easily and efficiently you should substitute for your transformers the Polar Resistance Capacity Coupling Units.


As soon as the substitution is made your set will behave as it should do, giving perfectly pure reproduction. The change over is easily effected, as the R.C.C. Unit has four clearly marked terminals corresponding to the transformer terminals.

Write for an explanatory leaflet to-day,

WIRELESS OPERATORS WANTED

There are now vacancies on our Seagoing Staff for Junior Wireless Operators trained on our apparatus. Youths of good education, preferably between 17 and 25 years of age, wishing to enter the Wireless Profession should communicate with the Managing Director, London Radio College, 82/83, High Street, Brentford, Middlesex, who will be pleased to furnish particulars of the training course necessary to qualify for our service.

VARIABLE CONDENSERS

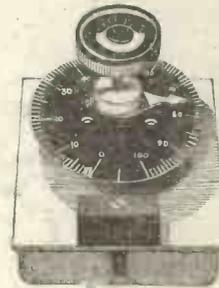

When operating any tuned oscillatory circuit, it is best, from an efficiency point of view, to utilise as much inductance and as little capacity as possible. This means in practice that a tuning condenser in a wireless circuit should always be used over the lower section of its scale.

If signals appear at maximum over the higher part of the condenser scale, then more inductance should be added to the circuit, when better strength will be observed.

In the case of a vane condenser most of its capacity is cramped over the lower section of its scale, thus necessitating a very small knob adjustment for a relatively large capacity change over that section of the scale which should always be used. The upper end of the scale, which should not be used for final tuning, gives a small adjustment of capacity for a relatively large knob movement.


The Polar Condenser was originally designed for our own ship installations to reverse this effect and so give operators a wide open scale over that section of the condenser which should be used.

If you use a Vane condenser properly, you must have an additional Vernier attachment to get fine tuning. This is unnecessary when using a Polar Condenser.

The above main advantage, combined with wide capacity limits, high insulation, complete metallic screening, robust construction and small overall dimensions, has influenced countless experimenters to incorporate Polar Variable Condensers in their circuits.

There are five standard capacities available:—
.001, .0005, .0003, .00025, and .0002 microfarads.
All capacities are of one size, 3 in. by 3 in. by 1 in. and one price—10/6.

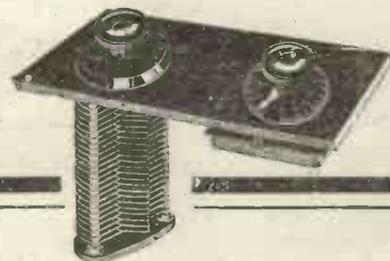We are showing below a panel on which are mounted side by side a common air condenser and the Polar Condenser. The economy in space is evident from the picture.



RADIO COMMUNICATION CO., LTD., 34-35, NORFOLK STREET, STRAND, W.C.2.

In replying to Advertisers, please use Order Form enclosed.



Cain & Abel

THE oldest story in the world illustrated a principle.

If you wanted your brother's goods you killed him and the rest was easy.

There are homicides to-day whose motives are cupidity, but they don't live long enough to enjoy their heritage.

Hence a new type has evolved—the persistent borrower.


Our advice is—be careful what you lend, for good things suffer in the lending. A battered coin still keeps its value, but a broken tool has none at all.

Don't let everyone know that your lathe is a Wade or you may never get the chance to use it yourself.

Below is illustrated the Wade No. 2 Lathe. It is back geared, self-acting, and screw-cutting. It has 13 change wheels, which cut all threads, right or left hand, from 6 to 60 T.P.I., including metric pitches. It takes work up to 4 in. in diameter and 12 in. in length. With it, you can turn up terminals, leading-in tubes and ebonite handles, or wind coils and drill ebonite for your wireless set.

If you would like one of our fully descriptive catalogues, post free, drop us a card to-day. Write to Dept. E.

WADE
Lathes

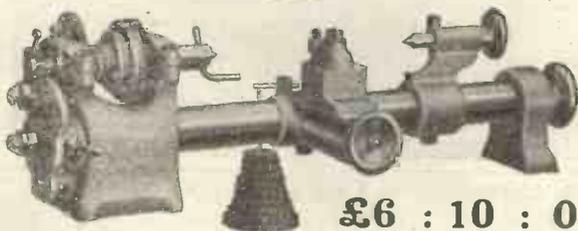

£6 : 10 : 0

C.A.V. Small Tools, Ltd., 181, Queen Victoria St., London, E.C.4.

E.P.S. 12



THERE WERE FOUR IN THE ROBINSON FAMILY

Also there were four sets of headphones.


Set No. 1 were pretty good on the whole, not too strong in reception but fairly light in weight—so Mrs. Robinson had those.

Set No. 2 were not bad—at least one earpiece was quite O.K., the other didn't match, but the carcass suited the delicate auditory organs of Miss Robinson—so she had set No. 2.

Set No. 3 were of doubtful foreign origin, but Robinson had bought them cheap, and anyhow they were not very much worse than the others although they did crackle a bit and fitted nobody but Master Robinson.

Set No. 4 were Robinson's own. Of course as a father it was his duty to keep the worst pair for himself. They might have been designed by the engineers of the Spanish Inquisition—heavy bands of steel that tortured his head, refractory screws and nuts galore to adjust, and withal a distorted reception that might have been America—but wasn't.

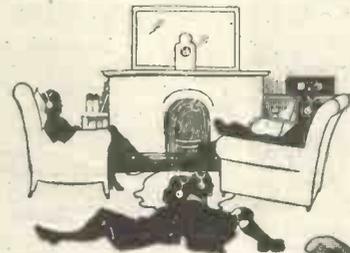Then he got acquainted with General Radiophones, and the Robinson family are now enjoying *real* radio for the first time.



GENERAL RADIOPHONES

Matched Tone.

Fully Guaranteed.

20/
per pair.

GENERAL RADIO COMPANY, LTD.,
Radio House, 235, Regent Street, London, W.1.

Telephone: Mayfair 7152. Telegrams: "Algenrad, London."

approximately high - frequency earth potential; but if the secondary is not earthed there may be a large capacity from each of these big parts to earth. For ease in tuning, the condenser in the grid circuit should have a very small maximum capacity. From 0.00025 to 0.0003 μ F is the largest size that should be used, and it will be found a distinct advantage to have a two or three plate "vernier" condenser in parallel with it. Without the vernier it is sometimes not at all easy to resolve carrier waves, and nothing is more tantalising than to pick them up one after another without being able to tune in the transmissions which they convey.

Use Vernier

Further, if it is annoying to the operator it is much more so to all dwellers in his neighbourhood who are trying at the same time for these transmissions. With the aid of a vernier condenser tuning is made both easier and quicker. The knobs of both main and vernier condenser should be fitted with extension handles 8 or 10 inches in length so that the hand need not come near them. These handles should be arranged in such a way that when moving them the hand does not travel over the inductances. An

extension handle will also be required for adjusting the coupling of the reaction coil.

The Use of Reaction

Until one gets the hang of it, the adjustment of the reaction coil may be found rather a difficult business. As oscillation occurs very easily on these very short wavelengths, the reaction coil should not be large. One of the same size as the secondary answers very well. This coil should be coupled to the secondary and the degree of coupling required will depend very much on the design and make up of the set. As a general rule it will be found to be fairly loose. If the aerial is "aperiodic," as it should be for the best results, the turns of wire forming the A.T.I. should not be close coupled to the secondary. Provision should be made for allowing the A.T.I. to be moved in relation to the secondary. As a general rule the coupling between the A.T.I. and the secondary will be on the loose side and here again adjustment is rather critical. It will be found too that the filament of the rectifying valve is critical in its current requirements. It is therefore desirable to use a rheostat which enables fine settings to be

made. A carrier wave which has previously defied all efforts at resolving may often be dealt with effectively by means of the filament rheostat.

Worth Trying

It cannot be denied that there are difficulties in getting down to the very short wavelengths, but it is very well worth while to do so, for quite apart from the thrill brought by the achievement, short wave work teaches one a very great deal not only about the design of sets but also about the best methods of operating them. Anyone with the smallest knowledge of wireless, or even with no real acquaintance at all of the working of a set, can tune in a nearby station on the broadcast waveband with success. But to deal satisfactorily with very high frequencies you must know exactly what you are doing and why. A single valve set, efficiently designed, is in most cases quite sufficient to bring in KDKA's 65 metre transmission at good telephone strength. With one or two stages of note amplification his signals can be brought up on a favourable night to such magnitude that they will operate a loud-speaker, so that it can be heard at a considerable distance.

Wonderful Wireless Invention

makes

"LESS" WIRELESS

Catwhiskerless, Batteryless, Worryless, Fuss-and-botherless Wireless.

The new invention, "Hovimo" Crystal Valve, is a revolution in wireless. The "Hovimo" Crystal Valve means no more batteries; no more fiddling and fumbling with catwhiskers and other delicate adjustments; no more fuss and bother; no more worry and disappointment; and no more "looking rather foolish" when a friend calls to hear the wireless and stays to stand by while you spend an evening tinkering about.

SIMPLE TURN OF MILLED SCREW FIXES THE "HOVIMO" CRYSTAL VALVE

—and you get results that will make friends marvel at your uninterrupted pure, clear and bell-like tone.

THE "HOVIMO" CAN BE ATTACHED TO ANY SET.

It is equally excellent for crystal sets and for circuits employing crystal rectification. Specially recommended for the S.T.100. Ask your dealer for this wonder-working invention to-day; also obtainable, in case of difficulty, post free from address below.



3/6

BRITISH MADE

Every One Guaranteed
M. MOLBACK
Phone: Chancery 8397.

27, High Holborn, London, W.C.1

The "Hovimo" is an entirely new invention and should not be confused with the ordinary "permanent" detector or compared with the silicon-carbonite and similar combinations.

The Newest Radiax Production

—No. 61. 2-Valve Regenerative—



Designed to meet the demand for a powerful, simply controlled, low priced set. This set enables you to get splendidly powerful reception under average conditions. It gives Loud-Speaker Reception at 20/25 miles and very much greater distances on Headphones.

Extremely selective, enabling British and Continental Stations to be heard in most parts of the British Isles.

Ordinary terminals are not used, instant connection or disconnection being made by plugs and sockets.

Strong cabinet with high quality camera finish, about a panel with nickel fittings throughout. Tunes to all wave-lengths.

Price: Including pair of Broadcast Coils, £4 15s. 0d.

Price: Complete with Phones, H.T. and L.T. Batteries, Two Valves, aerial and insulators, £8 13s. 6d.


Above prices plus 25% Marconi Royalty.

RADIAX LIMITED,

40, Radio House, Percy Street, Tottenham Court Road, London, W.1.
3 minutes from Tottenham Court Road and Goadge Street Tube Stations.



CLIMAX
RADIO
METAL FOR ME

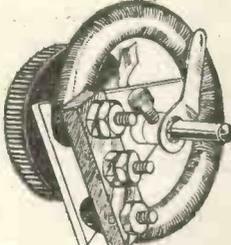

I've learnt the sound wisdom of metal.
It's sound, unbreakable and unburnable—that's why I use Climax Rheostats and Potentiometers.
They're meta-cooled, too! Just listen.

The resistance element is a wire spiral wound on a solid metal rod and insulated by vitreous enamel applied at a temperature of 1,300 Fahrenheit and capable of standing an electric pressure of 2,000 volts. The cooling far exceeds that obtained by any other method, making a single standard pattern equally suitable for one, two or three valves. Neither the insulating material nor the resistance element can be burnt, broken or displaced. The wire resistance element gives a perfectly smooth adjustment. It is solid, and therefore cannot be mechanically damaged. It is in intimate contact with a cooling mass of metal, and therefore cannot be burnt out.

No noise can be set up in the receiving set. These are marked points of superiority over all types of rheostat, including those employing granular or fibrous material.

TEN GOOD FEATURES.

- (1) Solid, rigid coil.
- (2) Perfect cooling.
- (3) Insulation stands high temperatures and voltages.
- (4) Unbreakable Bakelite terminal bar.
- (5) Large and well-spaced terminals.
- (6) Steel grub screw fixing for contact brush.
- (7) No lock nuts to work loose.
- (8) Riveted brush, with perfect brush contact.
- (9) Takes any panel up to 1/2 in. thick.
- (10) Bakelite knob with blind brush. Will not work loose.

Price:—Climax Rheostats, 6 ohm pattern, 3/6 each. Postage 3d.
Climax Rheostats, 30 ohm pattern, 4/6 each. Postage 3d.
Climax Potentiometer, 300 ohm pattern, 6/- each. Postage 3d.

CLIMAX PATENTS, Ltd.,
182, Church Street, London, W.8.
Telephone Park 2023.

5XX on the 4-valve
Family Set in S.W.
Africa.

To the Editor of MODERN WIRELESS.
SIR,—I suppose you will be surprised at hearing from someone in the outskirts of the Empire, but I am only writing you a few words of appreciation of the Family Four-Valve Set as outlined in Radio Press Envelope No. 2. This compact little set is by far the best operating set I have yet handled. Having had nearly 15 years' wireless

and detector. With note magnifier added signals are too loud for 'phones. The power of Cape Town is the same as 2LO, so these results are far better than could be hoped for. JB (Johannesburg), with 1/2 kw. in the aerial, comes in quite loud on two valves, his distance being 740 miles. Shipping comes in with a roar. 5XX comes in with fair 'phone strength on three valves. 2LO faint, and also 5IT with four valves. Three a.m. one morning I managed to pick up KDKA on three valves at good 'phone strength. All high-power morse stations come in well, and I can get them any time of day or night on two valves.

Hoping you will find this interesting, and congratulating you



John Henry is here seen broadcasting his impressions of the Lord Mayor's Show.

experimenting, I have naturally handled many sets. The general principles of the set are excellent and leave nothing to be desired, but in the set I have made up I have made some slight alteration to the original design in so far as the components are concerned, and also the top.

The wiring is carried out with bare 18 gauge wire with no systoflex covering, but special attention has been paid to this part of the construction—no wire runs parallel with another and if crossing is necessary it is at 90 degrees. The coils are Igranite.

As to results obtained, these exceeded anything like expectations. Cape Town (750 miles) comes in at good strength on H.F.

most heartily on your design of a thoroughly reliable and efficient set.—Yours truly,

PERCY F. SYMONS.

Windhoek,
S.W. Africa.

USE THE ORDER FORM.

In this copy of MODERN WIRELESS will be found a special order form for use when ordering goods or making enquiries from wireless firms. Radio Press, Limited, guarantee to see that all readers obtain complete satisfaction from advertisers when the order is written on this form. This is a great boon to all who order by post, and if you wish to safeguard yourself and prevent any possibility of disappointment, do not forget to use the order form. By using the form you will have the support of the largest wireless publishers in the world in the event of any query arising.

Unless the form is used, or if no mention of MODERN WIRELESS is made in your letter, the publishers accept no responsibility whatever.

Five new publications of the WIRELESS PRESS

MANY years ago—long before broadcasting was thought of—the WIRELESS PRESS were rendering dependable service to Experimenters. Nowadays this wealth of experience, combined with a finer knowledge of the Amateur's requirements, is manifest in all their publications. Receiving—Transmitting—Practical—Theoretical—there's a W.P. Book for every need. Here are new ones which will interest you.

THE W.P. EZI-WIRING SERIES.

Represents a definite and welcome innovation for the Home Constructor. All wiring diagrams are printed in *four colours*, thereby preventing any possibility of incorrect wiring. There are no loose sheets to go astray.
2/- each. By Post, 2/2.

No. 1 A Three-Valve Portable Receiver. By HUGH S. POCOCK.

This receiver can be used on any situation with a temporary aerial or with the frame aerial incorporated in the receiver itself.

No. 2 A Three-Valve Receiver. By F. H. HAYNES.

The tuning arrangements of this receiver are self-contained and cover a band of wavelengths between 200 and 2,000 metres. All the B.B.C. Stations are therefore within the range of this receiver when used in conjunction with an average outdoor aerial. A straight-forward three-valve set, consisting of a high-frequency amplifier, detector and note magnifier, with re-action on the aerial inductance.

No. 3 A Two-Valve and Crystal Reflex Receiver. By W. JAMES.

Reflex receivers are capable of giving a very high degree of amplification per valve. This two-valve and crystal receiver, unlike many reflex receivers, will be found perfectly stable in operation and will be capable of giving loud-speaker strength within a radius of thirty miles of a main B.B.C. Station.

No. 4 A Four-Valve Combination Set. By W. JAMES.

A four-valve receiver of this type is ideal for general reception both with telephones and a loud-speaker. Switches are provided so that two, three or four valves may be used at will. An entirely new principle is used to cut out the H.F. valve, no switches being employed. Loud-speaker results from most of the British and Continental Broadcasting Stations can be obtained with this receiver.

THE AMATEUR'S BOOK OF WIRELESS CIRCUITS.

By F. H. HAYNES.

This popular book gives the fullest possible details for wiring up no less than 117 circuits. Nothing is left to chance, every value is inserted—every detail carefully checked. Containing many additional features, it is the most complete and easily understood circuit book available to-day. 3/6. By Post 3/9.

WIRELESS VALVE TRANSMITTERS.

The Design and Operation of Small-Power Apparatus.

By W. JAMES.

A useful addition to wireless literature by a British author. The first and only *practical* book on transmitting.

Mr. James commences with the general principles of electricity, the meaning of high and low-frequency currents, inductance, capacity and reactance are fully explained and examples are given in such a way that the novice may thoroughly understand.

The following chapters deal with direct and alternating currents and many interesting and ingenious methods of obtaining high-pressure supplies are detailed. Rectification of both high and low-pressure A.C. are fully explained. Full particulars of microphones, speech amplifiers and every type of valve telegraph and telephone transmitter. 9/-.
By Post, 9/9.

The W.P. Wireless Diary.

Published in conjunction with
Charles Letts & Co.

The diary for 1925—full of Wireless data. Do you know the best way of erecting your aerial—how to construct and manipulate an efficient valve or crystal set? Would you like to know the call signs of Amateur and Experimenters in England and the Continent? You will find this information and countless other details in The Wireless Press Diary. 1/- cloth bound. 2/6 in leather case, containing 3 pockets, season ticket window and pencil.

The Wireless Press Limited

The Pioneer House for Authoritative Wireless Literature.

12-13, Henrietta Street,

Strand, London




In replying to Advertisers, please use Order Form enclosed.

Brown



Experientia docet.

It takes all these processes— and many more besides— to make the **Brown** Loud Speaker the perfect instrument that it is. When selecting your Loud Speaker remember the old Latin saying "Experientia docet" and appreciate that the very first Loud Speaker built for Wireless use was a product of S. G. Brown Ltd., Every good Dealer stocks the **Brown** in its several sizes and will be glad to give you an actual Demonstration of its super-lative tone.

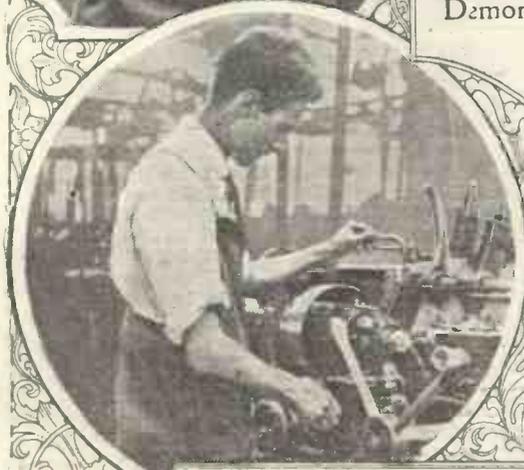

LOUD SPEAKERS

Adot. of S. G. Brown, Ltd., Victoria Road, North Acton, W.3.

Gilbert Ad. 1723.

GENUINE
LOW TENSION
FOR THE FILAMENT LIGHTING
"The Best in the World"

The Batteries detailed below will be found to cover all the requirements of the different valves.

PRICE LIST				H.T.
Codeword	Volts	Capacity	Price	Batteries
GLORY	1½	28	3/-	Write for
GLOBE	3	12	4/6	
GLARE	1½	56	7/-	L/let 134B
GLINT	3	28	7/-	
GLASS	3	56	14/-	
GLATE	4½	28	10/6	

GENUINE HELLESENS DRY BATTERIES FOR

HELLESEN DRY BATTERIES
OF WIRELESS VALVES
"The Best in the World,"

It is far cheaper to use one of the high capacity batteries than a number of the smaller types.


L.T. PRICE LIST				
Batteries	Codeword	Volts	Capacity	Price
Write for	GLOWE	1½	60	8/-
	GLOAT	3	60	16/6
L/let 142B	GLUPE	4½	60	25/-
	GLEAM	1½	130	16/-
	GLOAM	3	130	32/6
	GLISS	4½	130	49/-

A. H. HUNT, Ltd. (Dept. 5) H.A.H. WORKS, Tunstall Rd., Croydon, Surrey. "Keyage, Croydon."

Bargains from our 1924-5 Catalogue

—don't be without your copy—write to-day.

THE SUPRA L.F. TRANSFORMER.

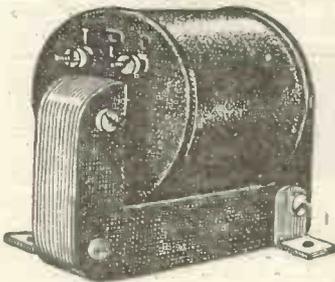

Ratio 5:1.

The windings being in insulated layers, each having 6 sections, this transformer gives the greatest possible amplification, but with no trace of distortion. It represents the finest value for your money obtainable.

12/6

83-5-Y PULL-PUSH THE MICROSTAT. SWITCH.




Insert this useful switch in your filament circuit—it saves constant adjustment and considerable current. One-hole fixing. Neat, good and cheap.

2/6

There is only one reason why the Microstat is so popular and is selling in such huge quantities—it is the finest possible form of filament control available. It gives micrometer adjustment from zero to 100 ohms—ideal for any type of valve. One-hole fixing.

2/9

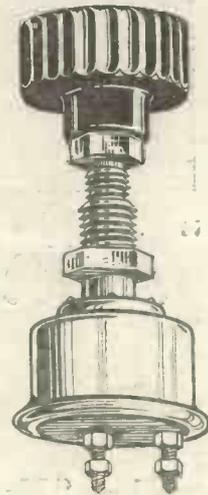

We are equipped to supply all Terminals and Brass Parts at rock-bottom prices.

- No. 1. Valve Sockets ... 8d. doz.
- No. 2. Valve Pin with Collar ... 8d. "
- No. 2. Valve Pin without Collar ... 4d. "
- No. 3. Terminals, Heavy Pattern 2 B.A. ... 2/2 "
- No. 4. Terminals W.O., 4 B.A. ... 1/- "
- No. 5. Telephone Terminals, 4 B.A. ... 1/3 "

- No. 6. Telephone Terminals, Small Barrel (special 4 B.A.) ... 1/- doz.
- No. 7. Fancy Terminals, 4 B.A. ... 10d. "
- No. 8. 3-part Terminals, 4 B.A. ... 10d. "
- No. 9. Rod Ball Joint and Whisker Holder ... 2½d. each
- No. 10. 4-Screw Crystal Cup ... 2d. "

- No. 11. Holder for Ball Joint ... 1d. each
- No. 12. Screw Nut for above ... 1d. "
- No. 13. Wander Plug, complete red and black ... 4½d. "
- No. 14. Spade Terminals 1/- doz.
- No. 15. Plug and Socket ... 1d. each
- No. 16. Contact Studs, 5 B.A. ... 4d. doz.

WATES BROS., LTD., 12-13-14, Gt. Queen St., Kingsway, W.C.2

Phone: GERRARD 575/6.

Grams: ZYWATESENG. WESTCENT.

Works: LONDON, BIRMINGHAM, and WESTCLIFF.



One hole fixing.
Handsome nickel dial.
Phosphor Bronze contact arm.

Prov. Pat. 12152.


2/6

6 ohms
15 ohms
30 ohms

Say **PEERLESS JUNIOR** When you want a better Rheostat

Winding cannot be damaged by ordinary use.
Size, 1½ ins. diameter, ½ in. high.
From all Wireless Stores or direct from:
The Bedford Electrical & Radio Co., Ltd.,
Electrical Engineers & Manufacturers,
22, Campbell Road, Bedford.

CARPAX PERMANENT DETECTOR SET

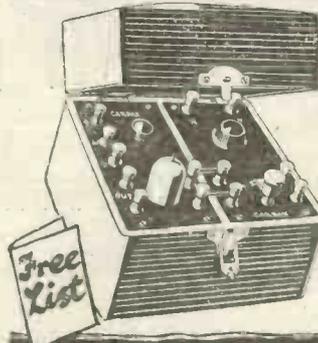

In beautiful dome-topped, solid polished mahogany cabinet, with safety catch. Fitted with efficient permanent detector. No fiddling with catswhiskers. Always set. Space for 'phones. Condenser tuned. Sockets for Chelmsford £1.10.0 coil. Earthing Switch

This Crystal Set has operated loud-speaker (with no amplification) 5 miles from 2ZY. Satisfaction guaranteed.

ONE-VALVE AMPLIFIER, to fit in the 'phone compartment of this handsome set **£3.3**

Works L.S. efficiently 70 miles from B.B.C. station. Let us send you full particulars.


CARPAX COMPANY LTD.
312, Deansgate, Manchester.



“Better Radio Reproduction”

The “New”
AMPLION
Junior-de-Luxe
—an aristocrat of
Loud Speakers—
with metal-ribbed
Wood Horn.

£3 : 5 : 0

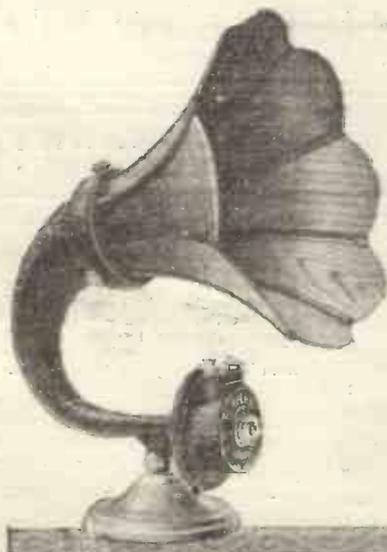

is assured by the scientific design and sound construction of all styles of the Amplion Loud Speaker.

Remarkable sensitivity with increased volume, exceptional clarity and purity of tone, the essential qualities of the 1924-25 models, are associated with artistic design and fine finish, so that the Amplion is a distinctive and decorative article in the household, as well as an instrument of high technical efficiency.

Obtainable from all Wireless Dealers and Stores

Write for illustrated list “WD.11” affording full particulars of all models, priced from 25/-.

AMPLION

Patentees and Manufacturers:
ALFRED GRAHAM & CO.,
(E. A. GRAHAM),
St. Andrew's Works, Crofton Park,
London, S.E.4.

Wires: “Navalhada, Catgreen, London.”

Phones: Sydenham 2820/1/2.

STEEL “LAKER” MASTS
STRONG, LIGHT, DURABLE.
BUILT FOR SERVICE.
Best Steel Tubing, 2" dia., in 10' sections. 25' 35/-; 30' 45/-; 35' 52/6; 40' 63/-; 45' 75/-; 50' 95/-. Complete with all Accessories.
Send Postcard for Catalogue
J. & J. Laker Co., 457, Romford Rd., London, E.7.

CABINETS YOU WANT



PICKETT'S Cabinets—they are good value, from 1/6 each, highly polished.

Cabinet Works, Albion Rd., Bexley Heath, S.E.1.

Write for Lists M.W.

Garnerium Crystal and Cat-whisker
Wonderful results. 50 per cent. better reception. Sensitive all over. Refund if dissatisfied. 1/6 post paid.
Portable Aerial. Indoor or Outdoor. Crystal range 10 miles. Valves Continental stations. Can be carried in jacket pocket. Price 3/- delivered.

E. T. GARNER (Dept. M.),
8, Westmoreland Buildings,
Aldersgate Street, E.C.1

TWO MORE!

Radio Press Envelopes

which are recognised as the greatest aid to constructors yet evolved.
How to make:

A ONE-VALVE REFLEX RECEIVER

By Herbert K. Simpson.

Loud Speaking with One Valve.

In this set the valve functions in a dual capacity, amplifying first at high-frequency, and then again at low-frequency. At short distances from a B.B.C. station it will therefore work a loud-speaker with sufficient volume for a small room if an outside aerial is used. Strong headphone signals can be obtained up to much longer distances.

Universal Wavelength Range

PRICE 1/6 (Postage 3d.)

AN EFFICIENT SINGLE-VALVE SET

How to build it.

By Herbert K. Simpson.

This set is so easy to build and so simple to work that it forms a perfect starting point for the novice. With an outside aerial a little practice will enable quite a number of the B.B.C. and Continental stations to be received with ease. A dull emitter valve can be used without any alterations.

The Ideal Beginner's Set

Will receive 5XX practically anywhere in Great Britain.

PRICE 1/6 (Postage 3d.)

“MODERN WIRELESS” COIL TABLE

See aside all doubts as to the correct coils to use for Aerial, Anode and Reaction.

PRICE 6d. (Postage 2d.)

Obtainable from principal wireless dealers and through all booksellers or newsagents—or direct from

RADIO PRESS LTD.

Bush House, Strand, London, W.C.2.

Wireless List "F"
Post Free.



A most efficient device to which ordinary headphones are clipped by simple pressure on the spring clips.

The
**"Gramaphix"
Loud-Speaker**

The Gramaphix requires (according to distance from the Broadcasting Station) at least one stage of low-frequency amplification to give satisfactory volume.

HORNS TO MOUNT ON GRAMAPHIX:
Straight Horn (Bell 10 in.) 6/-
Swan-necked Horn (Bell 11 1/2 in.) 15/-
Small Curved Horn (Bell 8 1/2 in.) 7/6
Post. 2d. extra.

Price
10/6
Postage 6d.

RICHARD MELHUISH, Ltd., Electrical Engineers and Wireless Experts,
50/51 & 84 Fetter Lane, London, E.C.4 Est. 1828



ATHOL
PORCELAIN
COIL MOUNT
With the perfect p'ug.
Will fit any coil:
1/- each.

ATHOL
COIL
RECEPTACLES
For anode coils, phone plugs, battery plugs, etc.
Moulded 1/- Ebonite 1/3


ATHOL
REVERSIBLE
VALVE
HOLDER
The only single hole fixing holder that fits any set.
1/3 each.

LISTS **ATHOL ENGINEERING CO.** FREE
CORNET St., Hr. BROUGHTON, MANCHESTER.

THE KAYNITE PATENT RADIO COIL WINDING MACHINE

PATENT No. 189376 OF 1923.

AN OLD FRIEND UNDER A NEW NAME.

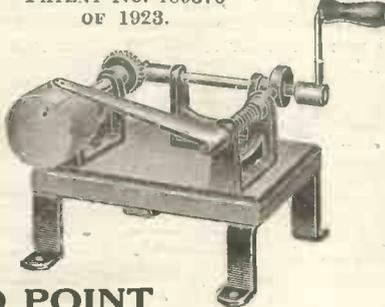

Every Experimenter Recommends it!!

IT IS RUDE TO POINT

but please excuse this time, as we feel it is our duty to point out that you can save pounds by winding your own sine wave lattice radio coils on the celebrated Kaynite Radio Coil Winding Machines. Model illustrated is Type A Machine, costing but 21s., and we can also supply the B Type Machine, fitted with automatic indicator, at 25s.

WRITE FOR DESCRIPTIVE PAMPHLET. A POSTCARD WILL DO.

If you cannot obtain locally send orders direct to the Sole Concessionaires,

A. W. KNIGHT LTD.
167, RYE LANE, PECKHAM, LONDON, S.E. 15.
Telephone - - - - - New Cross 2427.

EXPORT ENQUIRIES SPECIALLY SOLICITED.

HESTAVOX
QUALITY INSTRUMENTS AT FAIR PRICES.



Hestavox Loud Speakers are constructed on sound principles and of highest grade materials, excellent reproduction qualities, pleasing in both appearance and tone.


MINOR
£1 - 7 - 6
Height 18 in. Diam. of Flare 10 in. Adjustable Diaphragm.

CELESTE
£2 - 17 - 6
Height 26 in. Diam. of Flare 14 in. Adjustable Diaphragm.

WRITE FOR OUR COMPLETE LIST OF MANUFACTURES
HESTAVOX LTD.,
32, Palmerston Rd., Acton, London, W.3.

Barclays 370.

As good as a stage of H.F.

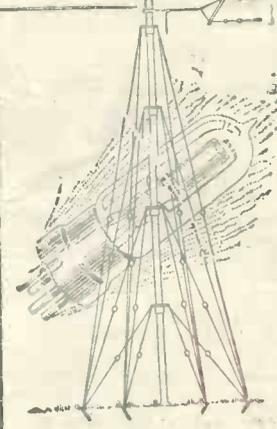

If you are out for telephony further afield than your local broadcasting station and better all-round reception let "Abbey" Steel Masts provide the essential aerial efficiency. By eliminating the screening effects of trees and houses, they improve your results almost to the extent of a stage of H.F. Don't take our word—ask any radio engineer.

Abbey Steel Masts are made in 10 ft. sections, light, strong and easily erected, and may be obtained in the following sizes: 10 ft., 28/-; 20 ft., 37/-; 30 ft., 50/-; 40 ft., 66/-; 50 ft., 90/-; 60 ft., 105/-; 70 ft., 137/- Complete with all accessories. All prices carriage paid.

For confined spaces, specify the "Abbey" Outdoor Directional Frame Aerial. 67/6

Send a card for illustrated list.


ABBAY ENGINEERING Co.,
WATTON, NORFOLK.

Perfectly simple and simply perfect

THE MIC-MET SUPER CRYSTAL DETECTOR

[REG.] (PATENT NO. 221943.)

This instrument is micrometrical in principle and ensures a perfectly adjusted and rigid contact between crystal and contactor. By a combination of movements between the three knobs, any portion of the exposed part of the crystal may be contacted. For S.T.100 and other circuits employing crystal rectification, the most efficient detector to use is the MIC-MET. Can be obtained from your local wireless dealer or direct from the manufacturers on receipt of 6s. P.O. Trade enquiries solicited.

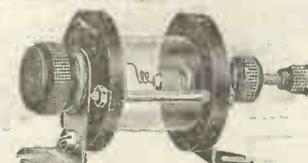

British Make.
Beware of imitations and infringements.

C. & J. ARRIGONI & CO., LTD., COMPTON PASSAGE, CLERKENWELL, LONDON, E.C.

"MAGNIPLEX" is a REVOLUTION IN AERIALS.

The Range, Strength and Clearness with both Valve and Crystal Set is increased in some cases up to 50 per cent.



Patent Applied for.

Our claim is backed by a guarantee that we refund your cash if results are not better than your present Aerial, and more than justify the extra cost of the MAGNIPLEX. Any user of MAGNIPLEX will give you a testimonial.

If your dealer does not stock them, send direct to us.

A few, among a great number of enthusiastic Users, write:—

Norwich,

16th Oct., 1924.

"Many thanks for your very prompt delivery of MAGNIPLEX Aerial. It is all that you claim for it. Using two valves only, I had excellent telephony and music from three American stations, WGY, WBZ, and one other call sign, of which I lost through spark jamming. This is the TYPE OF AERIAL WE HAVE BEEN WAITING FOR."

London, S.E.

3rd February, 1924.

"Tuning in Newcastle on a two-valve set a measured increase of signals of 35 per cent. was obtained, as compared with 12/22 copper aerial."

"I am sure you will agree with me that this is a remarkable result, and it is by no means a freak, as the two tests were made consecutively by

rolling up the wire and unrolling the MAGNIPLEX at the same time.

"On a test of a Crystal set 24 miles from 2LO an increase of just under 50 per cent. in signal strength was measured, as compared with 7/22 copper cable."

Shrewsbury

14th July, 1924.

"Just a line to say how pleased I am with the MAGNIPLEX you sent me some weeks ago. It does all you claim for it and easily adds a value to a set."

Cleader House,

Cornwall,

17th Sept., 1924.


"Thanks to your wonderful Aerial, last night I got Broadcast reception with my Home-made Crystal set over a distance of about 160 miles."

PRICES:— $\frac{3}{4}$ in. wide 3d. per ft.; $\frac{1}{2}$ in. wide 2d. per ft. Supplied in lengths of 50, 75 and 100 feet, including fittings, viz.:—End Terminal for Down Lead and Insulators ready for erecting. For lengths under 50 ft. fittings charged 1s. 3d. extra. Postage and packing paid.

HELIXO LTD., HENRY BUILDINGS,
GRESSE STREET,
RATHBONE PLACE, LONDON, W.1.
Phone: Museum 6039.

**BUILD THIS
FINE "SIMPSON"
SINGLE VALVE
SET!**

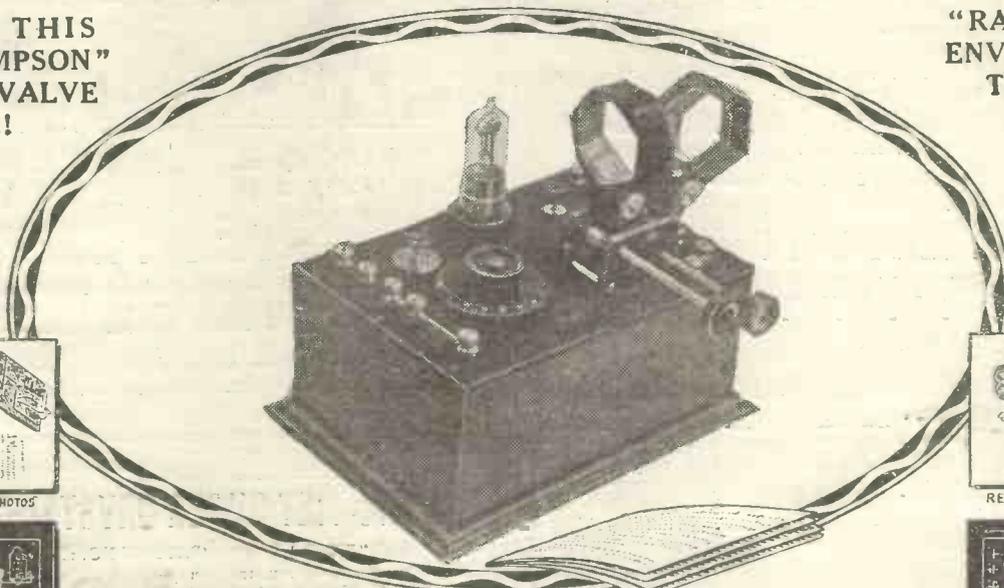
**"RADIO PRESS"
ENVELOPE No. 9
TELLS YOU
HOW!**



REPRODUCTIONS OF PHOTOS



BLUE PRINT

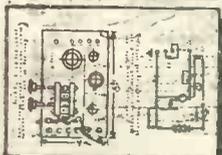

WORKING DRAWING



REPRODUCTIONS OF PHOTOS



BLUE PRINT



REPRODUCTIONS OF PHOTOS

ENVELOPE No. 9 CONTAINS ALL THE NECESSARY INSTRUCTIONS WITH WORKING DRAWINGS, BLUE PRINTS &c, FOR MAKING THE ABOVE

SINGLE VALVE SET

THIS set is designed by HERBERT K. SIMPSON, and dozens of letters have testified to its range and power. Order "Radio Press" Envelope No. 9 to-day **1/6**

RADIO PRESS Ltd., Bush House, Strand, London, W.C.2

Failure impossible

Even a man who has never built a Receiving Set before can achieve success at the first attempt by taking advantage of the Pilot Panel Service—the only method evolved for the Home Constructor that is backed by an efficient and experienced Service Department.

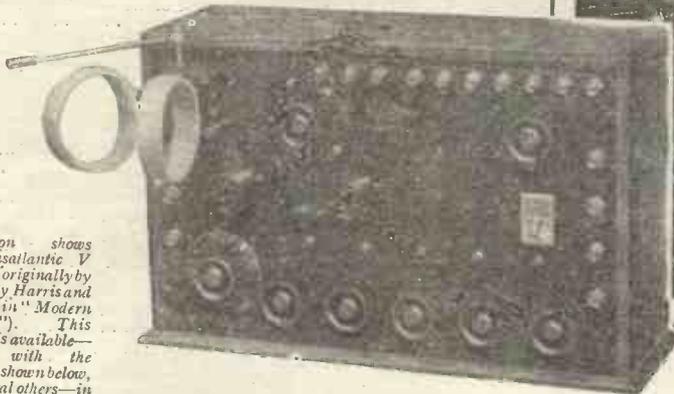


Illustration shows the Transatlantic V (designed originally by Mr. Percy Harris and described in "Modern Wireless"). This Receiver is available— together with the Puriflex, shown below, and several others—in a semi-manufactured state at the cost only of the actual components.

Peto-Scott's Wireless book contains much useful technical information and more than 80 Circuit Diagrams, 1, 3.

The only trouble-proof method for the Home Constructor—

USE the Pilot System and enjoy the following exclusive advantages:—

- 1 Absolutely no previous Wireless skill required—the only tools necessary are a screwdriver, soldering iron (optional) and a pair of pliers.
- 2 Every Set when completed is quite the equal in efficiency of the original.

- 3 Provides a high-grade instrument at the cost only of the components.
- 4 Success guaranteed—failure quite impossible if instructions are followed.
- 5 Every instrument designed by a recognised expert.
- 6 The only System for the Home Constructor backed by a Service Department.

Get particulars free to-day

BEFORE building your new Set be sure to write for a free copy of our new illustrated Folder describing the whole scheme. You will be glad to read that—if our instructions are followed carefully—any Set from the 2-Valve ST 100 to the 5-Valve Transatlantic is well within your ability without elaborate tools or equipment.

Every Set, in fact, can be readily assembled in a couple of evenings upon the kitchen table. Our Service Department is available for all who need its expert help and advice. Write to-day for the free Folder. Our new 48 page Catalogue—with prices that are the cheapest in England for high-grade guaranteed components—is yours for 3d. post free.

PETO-SCOTT CO., LTD.,

Registered Offices:
77, CITY ROAD, E.C.
(For all Mail Orders).

Branches:

LONDON: 62, High Holborn, W.C.1, and 230, Wood Street, Walthamstow.
CARDIFF: 94, Queen Street.
LIVERPOOL: 4, Manchester Street
PLYMOUTH: Near Derry's Clock.

The Transatlantic V


	£	s.	d.
Complete kit of components (can also be purchased individually), including everything except Valves, plug-in Transformers and coils	5	4	6
Pilot Panel, drilled and engraved	13	6	
Oak Cabinet with base board	17	0	
If all parts are purchased together a Marconi-Royalty of 62/6 must be remitted.			

The Puriflex


	£	s.	d.
Complete kit of components (can also be purchased individually), including everything except coils and valves	4	5	0
"Pilot" Panel, drilled and engraved	12	6	
Oak Cabinet with base board	17	0	
If all parts are purchased together a Marconi-Royalty of 37/6 must be remitted.			

Other first-class Receivers

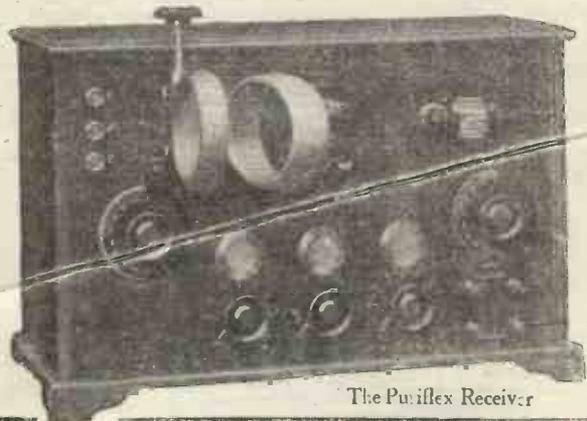Other guaranteed Pilot Receivers, including the ST-100, the All Concert de-luxe, the Resisteflex, the All Britain, and others. Write for full particulars to-day.



The Puriflex Receiver

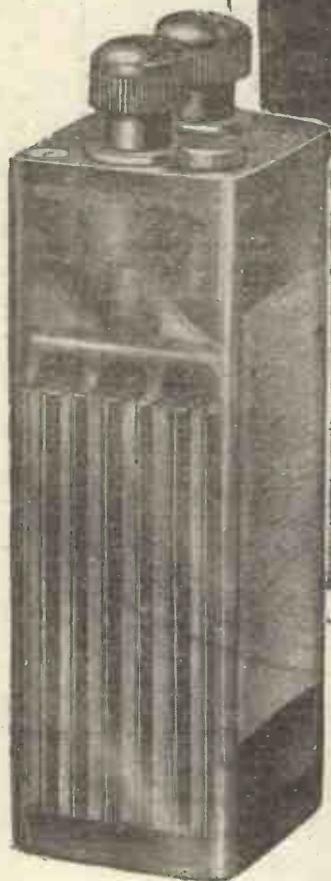

—the same portable and non-spillable Accumulator that the miner uses!

EVERYONE knows that the Miner's Electric Lamp must be able to withstand hard knocks and deliver a regular supply of light month in and month out. The Oldham Lamp has achieved a great reputation by reason of its special Activation Process—a unique method of accumulator platemaking which ensures a longer life and greater reliability.

The same long life Battery which is used in Oldham Miner's Lamps is now available for use with Dull Emitter Valves.

Hold it upside down—shake it even—and the acid cannot spill. Think how convenient a pocket-size accumulator will be. Made from strong seamless celluloid with generous terminals it is workmanlike and attractive in appearance. Just the accumulator for Wuncells, 1-volt Oras,

Wecos—and two of them in series will run a Dull Emitter of the .06 type for weeks at one charge.

See it at your Dealer's to-day and you will appreciate the wisdom of paying a shilling or two more to obtain an accumulator which will easily outlast two ordinary accumulators.

Two volts to ampere hours continuous **12/-**

OLDHAM & SON, LTD., Denton, Manchester.
LONDON - Gt. Chapel Street, Oxford Street, W. 1.
NEWCASTLE - - - - - 1, St. Mary's Place.

Even when the Oldham Portables held upside down the acid cannot spill. The ideal battery for all Dull Emitter Valves.



THE BOOKS for Beginners and Experts

The Radio Press Series.

No.		Price
1	Wireless for All	9d.
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
2	Simplified Wireless	1/-
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
3	How to Make Your Own Broadcast Receiver	1/6
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
4	How to Erect Your Wireless Aerial	1/-
	By B. Mittel, A.M.I.E.E.	
5	The Construction of Wireless Receiving Apparatus	1/6
	By P. D. Tyers.	
6	The Construction of Crystal Receivers... ..	1/6
	By Alan L. M. Douglas.	
7	How to Make a "Unit" Wireless Receiver	2/6
	By E. Redpath.	
8	Pictorial Wireless Circuits	1/6
	By Oswald J. Rankin.	
9	Wireless Valves Simply Explained	2/6
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
10	Practical Wireless Valve Circuits	2/6
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
12	Radio Valves and How to Use Them	2/6
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
13	500 Wireless Questions Answered	2/6
	By G. P. Kendall and E. Redpath.	
14	12 Tested Wireless Sets	2/6
	By Percy W. Harris.	
15	More Practical Valve Circuits	3/6
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
16	Home-Built Wireless Components	2/6
17	Wireless Sets for Home Constructors	2/6
	By E. Redpath.	
18	Tuning Coils and How to Wind Them... ..	1/6
	By G. P. Kendall, B.Sc.	
RADIO PRESS PANEL CARDS.		
1	How to Make the W.I. Receiver	1/-
	By Herbert K. Simpson.	
SIMPLEX WIRING CHARTS.		
1	For 2-Valve Set	1/-
2	For 3-Valve Set	1/-
3	For 4-Valve Set	1/-
RADIO PRESS WIRELESS PANEL TRANSFORMERS 8d.		
"MODERN WIRELESS" COIL TABLE for Aerial, Anode and Re-Action Coils 6d.		
RADIO PRESS ENVELOPES.		
1	How to Build an S.T. 100 Receiver	1/6
	By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	
2	How to Build a 4-Valve Receiver	2/6
	By Percy W. Harris.	
3	How to Build the "Simplicity" 3-Valve Set	2/6
	By G. P. Kendall, B.Sc.	
4	How to Build the All-Concert-de-Luxe Receiver	2/6
	By Percy W. Harris.	
5	How to Make a 2-Valve Reflex Receiver	1/6
	By Herbert K. Simpson.	
6	How to Build an Efficient Single-Valve Set	1/6
	By Herbert K. Simpson.	

The Radio Press Envelopes are the most complete guide to wireless construction ever devised. They contain exact size panel and wiring blue prints, complete working drawings, sheets of instructions regarding construction and working lists of components and many photographs on beautiful art paper showing the set and wiring from every possible angle. Every possible detail is explained and you cannot go wrong.
* Just Published

Any of the above publications can be obtained from principal wireless dealers and through any bookseller—or direct (plus 2d. postage, or, or Radio Press Envelopes 3d.) from

RADIO PRESS LTD.
BUSH HOUSE, STRAND,
LONDON, W.C. 2.



Manufactured only by
Portable Utilities Co., Ltd.,
Fisher Street, London, W.C.1.
Sold by all Dealers.

Made in two types :
Concert Grand 30/- ;
Eureka No. 2 (for second
L.F. Stage) 22/6.

The only Transformer guaranteed indefinitely against breakdown.

OUT of all the scores of Transformers on the market to-day, how many carry—either in letter or in spirit—the guarantee that is at the back of every Eureka? Not only must it satisfy your most critical demands—and you shall be the judge—within a reasonable period of trying it out, or your purchase price will be refunded in full, but we will actually guarantee it against breakdown throughout its normal life.

We make this offer for two reasons: first, because we have the most complete confidence in our Transformers, and secondly, because the unique construction of every Eureka prevents the possibility of any atmospheric influence acting upon it.

As is well known, the air is often heavily charged with dampness, which can be readily absorbed by any ordinary Transformer exposed to it for any length of time. This dampness—sooner or later—


will probably cause a breakdown in the insulation of any exposed winding, or at least create a serious falling off in signal strength.

But look at the Eureka, see its massive coppered-steel case, and know that the whole of its contents is hermetically sealed—actual tests have even demonstrated that fourteen days under water does not harm the Eureka in the slightest degree.

Thus the insulation—tested at 2,000 volts by Faraday House—is absolutely permanent.

But insulation is only one of the Eureka exclusive features—anyone who has had the opportunity of using one will enthuse over its wonderful volume and purity of tone.

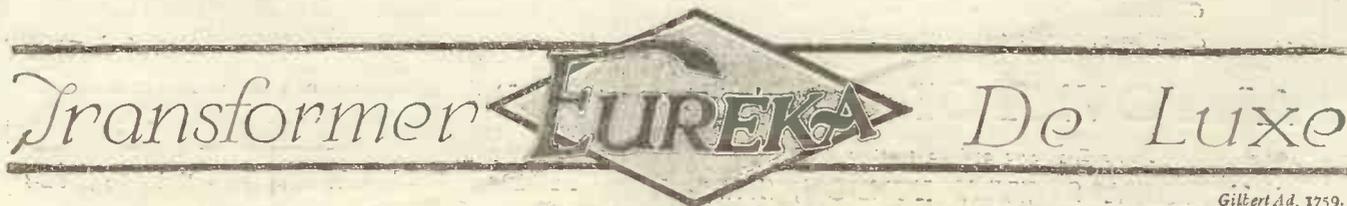
If you are building a new Set—or bringing your existing one up to date—be sure to fit a Eureka Transformer and have no regrets.



Gilbert Ad. 1759.

In replying to Advertisers, please use Order Form enclosed.

Variable Bridge Condenser

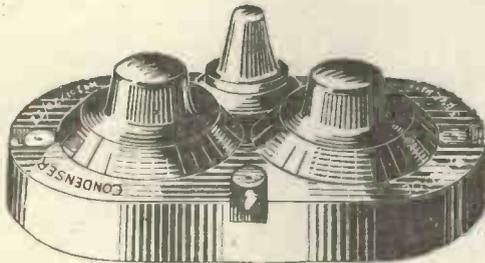

(Two-thirds Full Size.)

NEW MODEL A (Mica Dielectric 14/6

The Variable Bridge Condenser will be the Ultimate Radio Controller, for its fundamental principle presents finality in precision.

It provides a key to radio receptive circuits of far higher efficiency than those in common use to-day.

- | | | |
|--------------------|----------------------------------|------|
| Model B (3-E.V.C.) | Panel Mounting (Air Dielectric) | 37/6 |
| " C " | Cabinet Mounted (Air Dielectric) | 45/- |
| " D " | Bridge Tuning and Rejector Unit | 60/- |
| | Bridge Tuning and Rejector Coils | 7/6 |



CLIX COMBINATION PLUG-SOCKET—the Electro-Link with 159 uses—inaugurates a standardised system of instantaneous wiring.

- CLIX with Locknut 3d. each.
- CLIX Insulators (6 colours) 1d. each.
- CLIX Bushes (6 colours) 1d. per pair.

Obtained from all Wireless Dealers or direct from the Patentees & Manufacturers :

AUTOVEYORS LTD

Radio Engineers and Contractors

84 VICTORIA STREET, LONDON, S.W.1

Wireless Weekly, 6d net

Wireless Weekly

RESULTS

Not only do maximum results accrue from advertisements in the WIRELESS WEEKLY but far more important still is that its readers embrace the section that buys on the spot. You therefore get the twofold advantage of immediate and direct results to your advertisement—Write for particulars of this and other Radio Press Publications to the Advertisement Managers.

BARCLAYS ADVERTISING, Ltd.,
Advertising Consultants & Contractors,
BUSH HOUSE, STRAND, LONDON, W.C.2.
Telephone: City 9911 (Extn. 9).

When fitting an Earthing Switch fit the

LIGHTNING PROTECTOR

AND USE YOUR SET IN SAFETY EVEN DURING A THUNDERSTORM

PRICE — POST 3d **2s** COMPLETE WITH INSTRUCTIONS

Obtainable from all Wireless Dealers or direct from:
ANDERSON'S WIRELESS SALES AGENCY 915 Oxford Street W.1.
Telephone: Gerrard 1720 Telegrams: ANNVALSO, WESTCENT LONDON.

100% EFFICIENCY H.T. BATTERY. THE CONSTRUCTOR'S IDEAL.

Amazing value, positively unequalled. See "Apparatus Tested," April issue. Giant Unit Dry Cells, 1½ volts, 1½ in. diam. 300% more capacity. Compare tiny standard cells on photo. Terminalled and insulated. Cells, 4/- doz., carriage extra. 60 volt type in polished Oak Case, as reported, 19/6 carriage 1/9. All Cells replaceable. Lists free. Sample Cell 6d From actual maker only, saving 50% middlemen's profits. Money back guarantee. Orders in rotation. Sole Maker: **FINCHETT (C.A.), OLD ARMOURY, OSWESTRY.**

COUPON

Questions and Answers

In future this coupon must be accompanied with 2s. 6d. P.O.

"MODERN WIRELESS" December, 1924

*Safety
First*



The Mullard Service Safeguards All Valve Users

YOU can avoid accidents to your Valves by using Mullard Safety Discs. Your dealer will supply them **free on request**. These patented discs are perfect insulators under all conditions of service and are purposely designed to prevent filament burn out by H.T. battery short circuit. Complete instructions with each disc. Make sure you get these Mullard Safety Discs. Send us the name and address of your dealer if you cannot get what you want, and we will supply his requirements.

Mullard
THE · MASTER · VALVE

Obtainable from all Radio Stores, Electricians, etc.

Advt. The Mullard Radio Valve Co., Ltd., Balham, S.W.12.

In replying to Advertisers, please use Order Form enclosed.

AN OPINION THAT COUNTS

THE Radio Press test reports are respected in all wireless circles for their accuracy and fearless impartiality. The following are *verbatim* extracts from the test report made by A. D. Cowper, M.Sc., in last month's "Modern Wireless" (page 692), on the U.S. Super Transformer:—

1. "A handsome well-finished instrument with a large vertical coil and ample iron core."
2. "The favourable impression given by a first inspection of this instrument was borne out in actual test."
3. "The present instrument, if the high quality of the specimen submitted is an indication, can be heartily recommended, and indicates the vast strides that have been made recently in the design of really effective transformers for L.F. amplification."

IF YOU BUY A "U.S. SUPER" YOU KNOW YOU ARE SAFE.

"U.S." Transformers are British throughout. The letters have no connection whatever with the words "United States."

**Maximum Magnification
without Distortion**
— the Secrets here —

All-British made throughout, the U.S. Transformer's success lies in the excellence of its design. The core, with no bolts through it, is packed with finest Stalloy iron, allowing fullest amplification without hint of distortion; winding is done by experts; terminals are large and comfortable, with ebonite strips at top and soldering tags. Ratio guaranteed 5:1. Remember—it's British.

PRICE 18'6 EACH.

Two other U.S. Transformers are also made:
No. 1, suitable for first stage work. Price 14'6
No. 2, designed for following stages and power work. Price 11'6

All U.S. L.F. Transformers are tested and guaranteed.

**THE U.S. SUPER
TRANSFORMER**
U.S. Radio Co., Ltd.,
155, High St., Lewisham, S. E. 13. Phone:
Lee Green 2404.

Two U.S. Super Transformers are used by E. Redpath in his "Home 3-Valve" Set described in this issue of "Modern Wireless."



HUNT'S NEW

ACCESSORIES

CRYSTAL
Fig. No. 922.

DETECTOR

Codeword: "VERNIER."

MICROMETER ADJUSTMENT
(without turning catswhisker or cup),
LOCKING SCREW.
HEAVILY NICKEL-PLATED FINISH.

CATSWHISKER OR DOUBLE CRYSTAL
(spare cup with 3 screws supplied free).

DUSTPROOF GLASS CYLINDER.

PRICE 4/- EACH.


Complete as illustrated, but less Crystals.

(DEPT. 5) H.A.H. WORKS:
TUNSTALL RD., CROYDON
"KEYAGE CROYDON."



Fig. 828.
Codeword, "SAVEIT."
Valve Protector and Safety Wand Plug for protecting the filament of Wireless Valves.


Price 2/- each. Complete as illustrated.

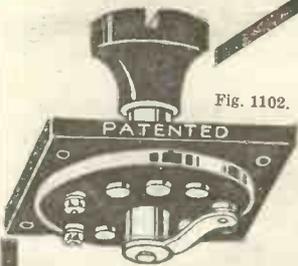

VARIABLE GRIDLEAKS.—An absolute necessity for delicate Long-distance Tuning. Each stop a definite and repeatable resistance. Standard resistance 1-5 megohms. Other resistances to order. No extra. Fig. 1100.—Top Panel Mounting, 4/6 ea. Fig. 1102.—Under Panel Mounting, 5/- ea. Fig. 1101.—Anticapacity Handle, 9d. ea.

Manufactured by

A. H. HUNT, LTD.

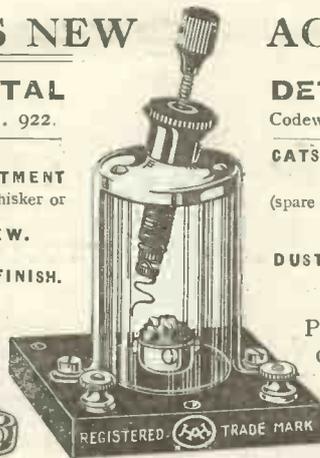

Fallon Fixed Condensers

Capacities up to .001, 1/3 each.

" " " .004, 2/- "

WHY PAY MORE?

Fix Fallon Condensers

—they improve results in all Sets.

Made of the highest quality mica and copper foil; each one tested and guaranteed, FALLON Fixed Condensers are right up to FALLON standard. Fitted with soldering tags and nuts for making clean connections.

British Reputation.—Your Condensers are not FALLON'S unless the name FALLON appears on same. Write direct for Trade Terms.

All Correspondence and Post Orders to:

FALLON CONDENSER CO., LTD.,

White Ribbon Works, Broad Lane, Tottenham, N. 5

Branches: 143, Farringdon Road, E.C. 1; 3, King's West, Deansgate, Manchester; 120, Wellington St., Glasgow; 7, Howard St., Belfast.



Fixed Condenser and Grid Leak COMBINED.

2 or 3 megohms, 2/6 each.

—They're as good as the Best

THE THIRD SOUND MEDIUM

for your advertising campaign

MODERN WIRELESS, WIRELESS WEEKLY

AND THE

WIRELESS CONSTRUCTOR

are the predominant media in Radio publications.


You cannot afford to ignore the responsive public that eagerly and consistently studies the advertisements in these journals which constitute an excellent established market for your goods.


Write at once for Advertisement rates:—

BARCLAYS ADVERTISING LTD.

Bush House, Strand, London, W.C.2.

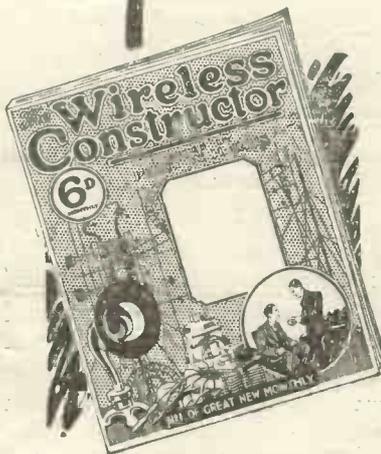* Advertisement Managers for Radio Press Publications.



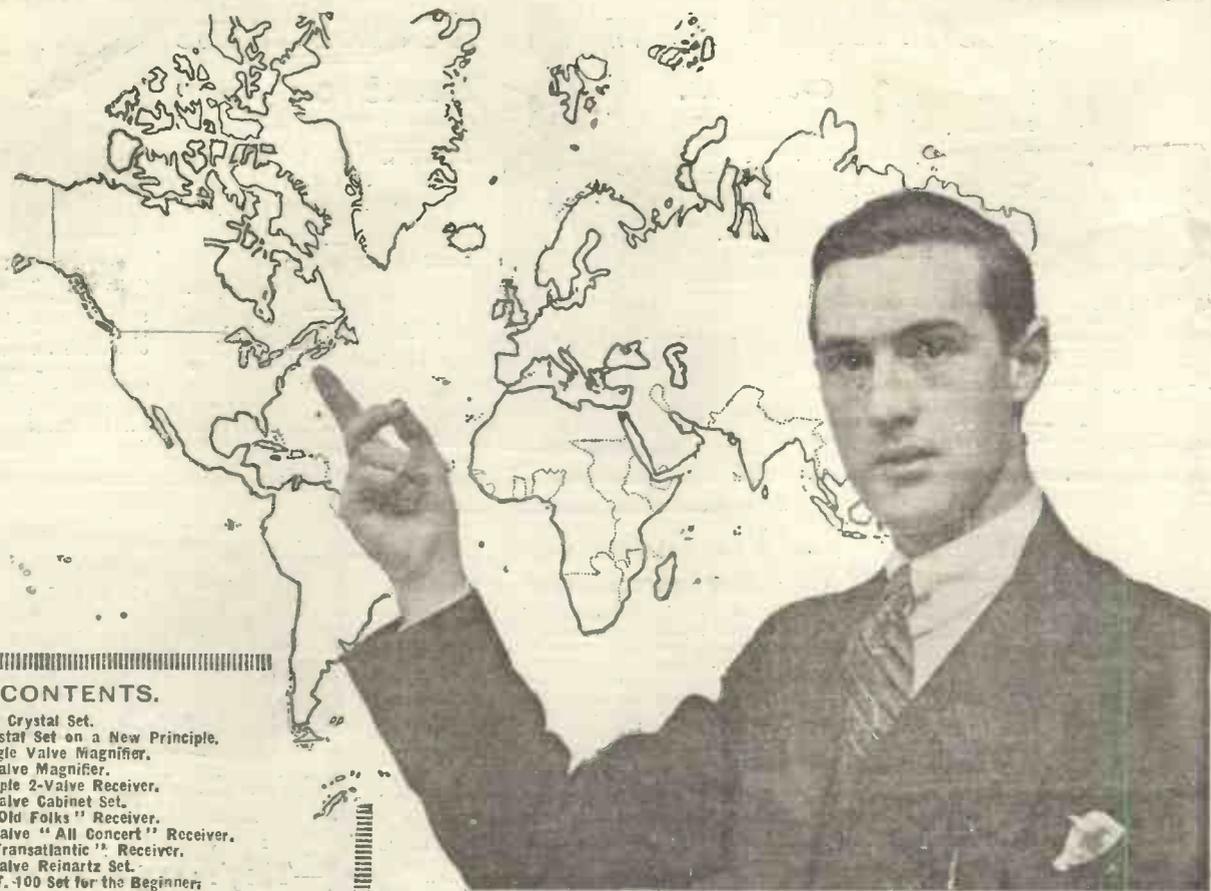

CONTENTS.

- 1 A 2/6 Crystal Set.
- 2 A Crystal Set on a New Principle.
- 3 A Single Valve Magnifier.
- 4 A 2-Valve Magnifier.
- 5 A Simple 2-Valve Receiver.
- 6 A 2-Valve Cabinet Set.
- 7 An "Old Folks" Receiver.
- 8 A 3-Valve "All Concert" Receiver.
- 9 A "Transatlantic" Receiver.
- 10 A 3-Valve Reinartz Set.
- 11 An S.T.-100 Set for the Beginner.
- 12 Wave Traps in Various Forms.

"I get these stations regularly"

So will you if you buy a copy of

TWELVE TESTED WIRELESS SETS

2/6 net.
Post Free
2/8

By **PERCY W. HARRIS**



And make one of the fine multi-valve sets such as the "Transatlantic." This is the season for receiving broadcasting from American and Continental stations, and there is no more fascinating or instructive pastime than searching for those elusive stations.

They will, however, not be elusive if you build a set produced by such an experienced designer as Mr. Harris,

Look at the varied contents and you will realise what a bargain such a cheap but reliable book is. Every set is not merely tested by the author but by hundreds, and sometimes thousands, of readers who have bought this book.

Buy it to-day from your wireless dealer or bookseller (2s. 6d. net) or send 2s. 8d. to the publishers:

RADIO PRESS, LTD., Bush House, Strand,
London, W.C.2.

Barclays A/c. 1173

THE RADIO PRESS ENVELOPE SYSTEM

THE Radio Press Envelope System is generally acknowledged to be the greatest aid to the constructor yet evolved. Each envelope contains working diagrams, exact size blue prints of wiring and of the panel (suitable for drilling), a set of photographs printed on real art paper and in a manner impossible in a book or periodical and showing the set and wiring from every possible angle, a list of components and the full instructions for making each set and using it.


These envelopes are obtainable from all principal wireless dealers and booksellers or direct from the publishers:

RADIO PRESS, LTD., Bush House, Strand, London, W.C.2.




R.P. Envelope No. 1. Price 1s. 6d. (1s. 8d. post free). How to Make an Efficient 2-Valve Receiver using the ST. 100 Circuit. By John Scott-Taggart, F.Inst.P., A.M.I.E.E.

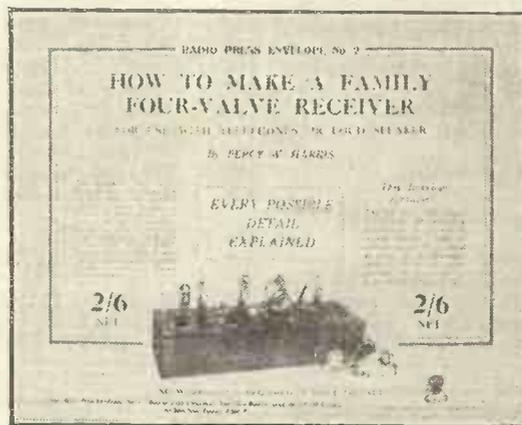A huge number of this ST. 100 envelope has been sold, and practically all the tens of thousands of successful ST. 100 sets in the country have been made from this design, which works a loud-speaker with ease up to 30 to 35 miles.



R.P. Envelope No. 2. Price 2s. 6d. (2s. 8d. post free). How to Make a Family 4-Valve Receiver. By Percy W. Harris.

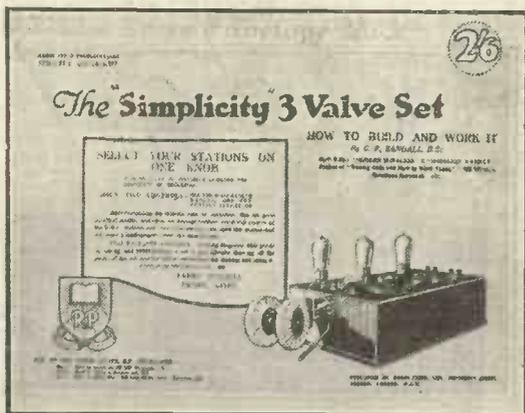This is the ideal easily-handled set for long range loud-speaker work. For those some distance from a station this set is ideal.



R.P. Envelope No. 3. Price 2s. 6d. (2s. 8d. post free). The "Simplicity" 3-Valve Set. By G. P. Kendall, B.Sc.

Notwithstanding extreme ease of operation this set gives excellent results and will receive all the B.B.C. stations and many Continental ones upon the 'phones and will work a loud-speaker from the nearest ones.



R.P. Envelope No. 4. Price 2s. 6d. (2s. 8d. post free). The "All-Concert de Luxe" Receiver. By Percy W. Harris.

A supremely efficient 3-Valve set with enclosed valves and all the latest technical improvements incorporated.

Index to Advertisers

	PAGE		PAGE		PAGE
Abbey Engineering Works	877	Finchett (C. A.)	882	Nichol (J. O.) & Co.	844
American Hard Rubber Co., Ltd.	857	Forno Co.	835	Oldham Accumulators	880
Anderson's Sales Agency	882	Fuller's United Elec. Works, Ltd.	867	Ormond Engineering Co.	824
Arrigoni (C. & J.)	877	Gamage, A. W.	803	Peto-Scott Co.	879
Athol Engineering Co.	877	Gambrell Bros., Ltd.	835	Pickett Bros.	876
Autoveyors, Ltd.	882	Garner	876	Portable Utilities Co., Ltd.	881
Baker & Russell	853	General Electric Co., Ltd.	763	Power Equipment Co.	796
B.D. & Co.	853	General Radio Co.	870	Pressland Elec. Supplies	868
Beard & Fitch	783	Gent & Co.	848	Radiax, Ltd.	871
Beechstein Radio Co.	788	Goswell Engineering Co.	847	Radio Communication Co., Ltd.	734, 869
Bedford Electrical Co.	875	Graham (A.) & Co.	876	Radio Improvements, Ltd.	854
Bowyer-Lowe Co.	836	Gran-Goldman Service	779	Radio Instruments, Ltd.	Cover iv.
Brandes, Ltd.	764	Green & Son (David)	853	Radio Panel Co.	853
British Battery Co., Ltd. (The)	803	Helix, Ltd.	878	Radio Stocks	849
British Thomson-Houston Co.	812, 827	Hestavox	877	Radiations, Ltd.	807, 854
Brown Brothers, Ltd.	779	Hobday Brothers	854	Raymond (K.)	858, 859, 860
Brown (S. G.), Ltd.	874	H. T. C. Electrical Co.	856	Robinson (Lionel) & Co.	849
Burndept, Ltd.	792	Hughes (F. A.) & Co.	864	Rosen (Ed.) & Co.	807
Burne-Jones & Co., Ltd.	843	Hunt (A. H.), Ltd.	885, 875	Rothermel (R. A.), Ltd.	803
Buss (T. O.)	844	Igranic Electric Co., Ltd.	780	"S. A. Cutters"	843
Carpax Co.	875	Jackson Bros.	828	Shipton (E.) & Co.	835, 844
C.A.V. Small Tools	870	Knight (A. W.)	877	Silvertown Co.	808
Chloride Elec. Storage Co., Ltd.	816	Laker Co.	876	Simpson & Blythe	844
Clarke (H.) & Co. (Manchester.) Ltd.	820	Lighting Supplies Co.	863	Smith & Ellis	853
Climax Patents	872	Lissen Co.	767, 791	Sparks Radio Co.	853
Collinson's Precision Screw Co., Ltd.	864	Louden Valves	839	Sterling Telephone Co., Ltd.	771
Cossor Valve Co.	832, 833	McMichael (L.), Ltd.	850	Stevens (A. J.) & Co. (1914), Ltd.	828
Cunningham & Morrison	733	Marconiphone Co.	804	Stockall, Marples & Co.	854
Curtis (Peter), Ltd.	787, 795	Marconi-Osram Valve Co.	768	Telephone Mfg. Co.	853
Day (Will), Ltd.	850	Marshall (H. Lloyd)	846	"U. S." Radio Co.	884
Diamond Wireless, Ltd.	823	Melhuish (Rd.) & Co.	877	Vandervell (C. A.)	779
Drummond Bros.	823	Metropolitan-Vickers Electrical Co., Ltd.	784, 840	Varley Magnet Co.	853
Drummond Condenser Co. (1921), Ltd.	799, 831	Molback (M.)	843, 871	Ward & Goldstone, Ltd.	863
Economic Electric, Ltd.	868	Mullard Radio Valve Co., Ltd.	800, 801, 833	Wates Bros.	875
Edison Swan Electric Co., Ltd.	775	Naylor (J. H.)	819	Watmel Wireless Co.	807
Falk, Stadelmann & Co.	776	Neutron, Ltd.	811	Wholesale Fittings, Ltd.	885
Fallon Condenser Co.	885	New London Electron Works	815	Wilkins & Wright, Ltd.	850, 864
Fellows Magneto Co., Ltd.	819			Wireless Press, Ltd.	873



RADIO PRESS ENVELOPE NUMBER 8. No. 1/6

HOW TO MAKE A ONE VALVE REFLEX RECEIVER

By HERBERT K. SIMPSON

EVERY POSSIBLE DETAIL GIVEN

THIS ENVELOPE CONTAINS

Radio Press Ltd. Bush House, W.C.2.

ALL THE INSTRUCTION NEEDED TO MAKE THIS

ONE VALVE REFLEX RECEIVER

IS CONTAINED IN OUR ENVELOPE No 8

RADIO PRESS ENVELOPE No. 8.

HOW TO MAKE A ONE VALVE REFLEX RECEIVER

By Herbert K. Simpson


1/6 NET. (Post free 1/9)

This envelope contains full and elaborate sheets of instructions, two full-size blue prints, three sheets of photographs on art paper and a sheet of working drawings.

An ideal one valve set for working a loud-speaker up to 10 miles from a broadcasting station. Strong 'phone signals are obtainable from many stations.

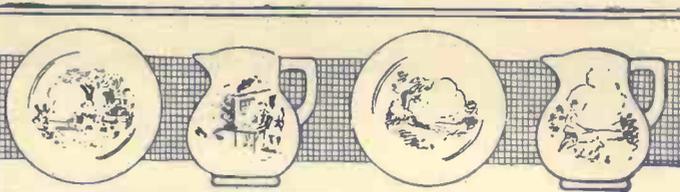RADIO PRESS, LTD., Bush House, Strand, W.C.2.





Give your Set that Professional Look!

About the year 1749 an engraver named John Sadler, of Liverpool, whilst taking proofs off a plate he had engraved, was suddenly startled by shouts of jubilation from his children in the room. On turning round to see the cause he found that one of them had picked up a still wet spoilt copy that he had thrown on the floor and applied it to a piece of crockery, and was triumphantly holding up the decorated piece of china. This accidental revelation was pursued by Sadler, and it is on record that together with a master printer named Green they, a short time afterwards, printed "1,200 earthenware tiles in about six hours, better and neater than one hundred skilful pot-painters could have painted in the common and usual way of painting with a pencil."

This is probably the earliest known transfer printing; after Liverpool many other factories, such as Battersea, Worcester, Bilston, Staffordshire, Swansea, Coalport and others, made transfer-printed ware.

Transferring is a common process in Lithography where it is used for "making up work," viz., transferring a lot of impressions either all of the same matter or different to a large stone so that they can all be printed at once.

Ladies use transfers for getting their designs on material for silk and other fancy work, in fact, its uses are innumerable.

The "Radio Press," were quick to realise the immense advantage the process offered to amateurs in lettering their panels as against the comparatively costly method of engraving, and thus have placed in the reach of everyone the Radio Press Panel Transfers.

PLENTIFUL SUPPLY NOW READY.
6d. per packet, or 8d. Post Free from

By using "RADIO PRESS WIRELESS PANEL TRANSFERS" (6d. per large packet of 80 labels), you can give to your set that finished appearance which makes all the difference. Not only are these transfers the cheapest and best but they are officially issued by the Radio Press for their sets. Buy a packet or two from your wireless dealer. They are also obtainable through every bookseller, but get the title right, if you want Radio Press quality.



Radio Press, Ltd.
BUSH HOUSE, STRAND, LONDON, W.C.2.

M. R. ...

Does your Volume Vanish in Smoke



The volume that ought to be there.

A GOOD aerial picking up strong signals, a highly efficient circuit, and yet the results . . . most disappointing.


Nine times out of ten what does it mean?

Transformers giving of their best only under particular circumstances, or else cheap and inferior transformers.

The low self-capacity is the point that counts if you want to get that distortionless volume you deserve from your set. The *R.I. transformer, with its unique sectional primary and secondary windings, has the Lowest Self Capacity of Any Transformer on the Market.*

But more than that, it is the *General Purpose Transformer* and gives equally fine tone and efficient amplification in every wireless circuit.

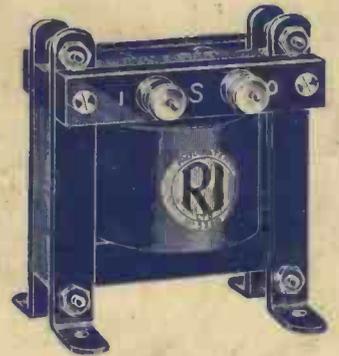A book of distortionless circuit diagrams supplied free with each instrument. Write for the new R.I. catalogue.



25/-



Radio Instruments Ltd.
12 Hyde Street, Oxford Street

Telephone: REGENT 6214 (3 lines) W.C.1. Telegrams: Instradio London.