There was no regular September FLYER. Our customers continue to express amazement at purchasing professional quality test equipment kits at low Heathkit prices. The secret is in the method of selling. Our customers do most of the actual selling by praising Heathkits and recommending them to their friends. It is not unusual for one customer in a community to account for the sale of ten or more Heathkits. Thus while most companies add 40 to 50% for selling costs, the cost of selling Heathkits is but a few pennies out of every dollar.

costs, the cost of selling Heathkits is but a few pennies out of every dollar. There have been large increases in the cost of some Heathkit parts. Meters are up 10%, all transformers 10%, etc., but it is the aim of the Heath Company to absorb these if possible. As long as our customers continue the wonderful job they are doing, we will endeavor to do our part. This also enables us to give helpful informative articles in our FLYER as evidence of our appreciation. Let's keep it up.

Fleathkit FM & TELEVISION SWEEP GENERATOR KIT

The newest and one of the most interesting family of Heathkits. A sweep generator brings to the service shop or experimenter the most essential instrument for properly aligning television and FM receivers. This Heathkit completely covers the entire FM and TV bands 2 Megacycles to 230 Megacycles. The unit is 110V 60 cy power transformer operated. Uses two 6J6 tubes, two 6C4 tubes and a 6X5 rectifier. An electronic sweep circuit is incorporated using both tripdes of a 6J6 to allow a range of 0 to over 10 Megacycles.

A selector switch allows either frequency modulated or R.F. signals to be used. An interesting new type of miniature high frequency socket is used with terminals spaced extremely wide for easy assembly. The panel incorporates a large easily read calibrated scale and the assembled unit is easily adjusted by beating against a known radio station.

A sawtooth horizontal sweeping voltage is provided for the oscilloscope assuring that the trace will always be synchronized. A phasing control is included to correct for phase shift.

The colls are ready assembled and precision adjusted to exact frequency. As in all Heathkits, the best of parts are supplied, Mallory metal cased filter condenser (60 MFD of filter compared to an average of 16 MFD), zero coefficient ceramic condensers for high frequency, all punched and formed parts, grey crackle cabinet, 5 tubes, test leads, etc. Better get it built now and be ready for the FM and TV business.

WEIG



I dentibying SURPLUS TRANSFORMERS

Most surplus power transformers are of very high quality and if properly identified will give long trouble free service.

Many, however, are not marked sufficiently to allow identification. After establishing continuity with an ohmmeter, a few volts of AC applied to the most likely winding will allow the other windings to be measured with an AC voltmeter. A comparison of these will identify the high voltage and filament windings. 110 Volts AC can then be applied to the identified primary and the actual outputs measured. The outputs will read 5 to 10% higher than actual when no load is applied. If the wire used in winding the transformer can be measured, the amperage of each filament winding can be established from the following chart.

WIRE SIZE	CURRENT	WIRE S		CURRENT
A.W.GA. DIA.	AMPS .	A.W.GA.	DIA.	AMPS.
10 .102	14	16	.051	3.2 2.1 1.2
12 .081	9 .	18	.040	2.1
14 .064	6	20	.032	1.2

In general, a winding under load which supplies rated voltage is not overloaded. Excessive drop of voltage is always an indication of drawing too much current. In average transformer construction, it is usual to provide 50 milliamperes of high voltage for every ampere of working tube filament. (Exclusive of rectifier filament.) (I.E. 6.3 at 4 Amps would give a 200 MA high voltage winding.)

PUSH PULL AMPLIFIER KIT

\$14.95

Shipping weight 20 lbs.

Accessories Available

12" high quality FM speaker matches the amplifier..\$6.95 Mahogany speaker cabinet size 142"1142"x8" for above speaker......\$8.75 The shipping weight of 20 pounds for the Heathkit Amplifier proves that the transformers used are quality conservatively rated parts.

The real surprise is when it is connected to an FM tuner or new long playing record player. The reproduction is truly superb. You hear the breath of the singer and the colorful harmonics of the musical instruments.

Many of the components of this Heathkit are surplus and when they are gone, there will be a considerable increase in price--better order one now.

Push pull circuit with one preemp stage and phase inverter stage. Response with \neq or - 1 db. between 35 cycles and 13,000 cycles. Complete with all tubes, punched chassis, volume and tone controls, etc. 110V 60 cy transformer operated.

Heathkit VACUUM TUBE

Everything you want in a VTVM. Shatterproof solid plastic meter face, automatic meter protection in burn-out proof circuit, push pull electronic voltmeter circuit assuring maximum stability. Linear DC and AC Complete selection of voltage ranges startscales. ing with 3 Volts full scale up to 1,000 Volts. Isolated DC test prod for signal tracing and measurements of voltage while instrument is in operation. An ohumeter section accurately measuring resistance of 1/10 ohm to one billion ohms with internal battery. Extremely high input resistance 11 megohus on all ranges DC and 6.5 megohms on AC. All these features and many more are the reasons hundreds of radio and television schools are using Heathkit VTVM's and recommending them to all students. Like all Heathkits, the VTVM kit is complete, 110V 60 cy power transformer, 500 microamp meter, tubes, grey crackle cabinet, panel, test leads, 1% ceramic precision divider resistors and all other parts. Complete instruction manual. Better start your laboratory now and enjoy it all winter.

Shipping weight 8 lbs -

Simple STROBOSCOPE from Audio Generator

An interesting stroboscope for stopping motion and observing moving machinery is easily assembled using your Heathkit Audio Generator. The only equipment necessary is an amplifier, NE42 neon bulb, and 600 Volt paper condenser between .1 and 1. MFD.

The bulb is coupled between the plate of the amplifier output tube and chassis ground using the paper tubular condenser as coupling condenser between plate and one side of neon bulb. The input of the audio generator is fed into amplifier at highest output.

The neon bulb should be mounted in a reflector. The lowest range of the generator should be used and the frequency should be multiplied by 60 to convert to R.P.M., thus, the low range measures from 1200 R.P.M. to 12.000 R.P.M.

The neon light held near a moving object in subdued light while the frequency is varied will appear to stop the movement. A chalk mark on one blade or arm of object will often aid in determining speed. Where one mark is made but two are seen, the speed is $\frac{1}{2}$ the indicated and where four marks are seen, the speed is $\frac{1}{4}$ indicated. The moving reed of radio vibrators may be observed and checked for proper contact in this manner.



An excellent article on converting and using the BC 645 Transceiver in the citizens band appeared in the August ELECTRONICS Magazine. This has been reprinted by the Heath Company and copies are available on request--include stamped self-addressed envelope.

The life of soldering iron tips can be extended many times by having new tips chrome plated. The plating prevents the oxidation taking place and yet allows the tip to be tinned.

A new folder on Heathkits is about ready for distribution--the schematic of each kit is shown. A copy will gladly be sent on request.

MN26C Bendix Owners. The loop control box and loop connecting cable are now available from the Heath Company.

Heathkit SINE & SQUARE WAVE AUDIO GENERATOR KIT

6 00

Experimenters and servicemen working with a square wave for the first time invariably wonder why it was not introduced before. The characteristics of an amplifier can be determined in seconds compared to several hours of tedious plotting using older methods. Stage by stage, amplifier testing is as easy as signal tracing. The low distortion (less than 1%) and linear output (I one db.) make this Heathkit equal or superior to factory built equipment selling for three or four times its price. The circuit is the popular RC tuning circuit using a four gang variable condenser. Three ranges 20-200, 200-2,000, 2,000-20,000 cycles are provided by selector switch. Either sine or square waves instantly available at toggle switch. All components are of highest quality, cased 110V 60 cycle power transformer, Mallory F.P. filter condensers, 5 tubes, calibrated 2 color pamel, grey crackle alwinum cabinet. The detailed instructions make assembly an interesting and instructive few hours. Shipping Weight 13 lbs.





We often receive letters with this query. There is no doubt that a vacuum tube voltmeter is the most essential instrument in any laboratory or shop. It is like a right arm to any electronics worker. with it, all the voltages of a unit under test can be measured (many that due to loading of the circuit could not be measured with ordinary voltmeters). It serves as an output indicator, an alignment indicator, it incorporates an extremely wide range ohmmeter, it measures batteries, resis tors, transformers, chokes, coils, condensers (for leakage). The voltage of A.V.C. systems, bias cells, oscillators, discriminators, etc., are easily checked. A vacuum tube voltmeter is truly the fundamental test instrument and should be first in any newly organized shop.

World Radio History



World Radio History

Heathkit RF SIGNAL GENERATOR KIT



This RF Signal Generator Kit is rapidly becoming our most popular kit. Cali-brated from 150 Kc. to over 100 Megacycles with fundamentals to 34 Megacycles it is adequate for every service need. An exceptionally complete assembly

and use manual makes it a lot of fun to build and no one needs to resort to slipshod methods of alignment when a quality Signal Generator Kit is available for less than a twenty dollar bill. The audio modulation is supplied by a relaxation type oscillator which also supplies a sawtooth audio voltage for amplifier testing.

The coils used are precision wound and factory calibrated eliminating the need for adjusting each band. The kit is complete with large calibrated scales on two color panel, grey crackle cabinet, 110V 60 cycle power transformer, precision coils, test leads, tubes and all other parts.

Shipping wt. 8 lbs.

that are read direct from the panel. NO CHARTS OR MULTIPLIERS NECESSARY. A condenser checker anyone can read without a college education. A leakage test and polarizing voltage for 20 to 500 volts provided. Measures power factor of electrolytics between 0% and 50%. 110V 60 cycle transformer operated complete with rectifier and magic eye tubes, cabinet, calibrated panel, test leads and all other parts. Clear detailed instructions for assembly and use. Why guess at the quality and capacity of a condenser when you can know for less than a twenty dollar bill. Add postage for 7 lbs.

Converting DYNAMOTORS 16 110V. MOTORS

Most types of war surplus dynamotors make excellent ball bearing 110V universal motors by a simple change. By drilling into the armature end and

Checks all types of condensers,

paper mica-electrolytic-ceramio



Heathkit

CONDENSER CHECKER




Heathkit TUBE ALL-W ADIO



ELSE TO BUY

A 3 tube 110V 60 cycle AC transformer operated radio using plug in coil to cover 550 Kc. to 6,000 Kc. Covers broadcast, police, aircraft, amateur, marine and foreign broadcasts. An excellent start in radio for boys or adults. Has been constructed successfully by 10 year old boys. An excellent way to keep the family radio for adults programs. Boys will enjoy this for years and gain practical knowledge using it. Every part supplied except speaker or headphones which are extra. Add postage for 3 lbs.

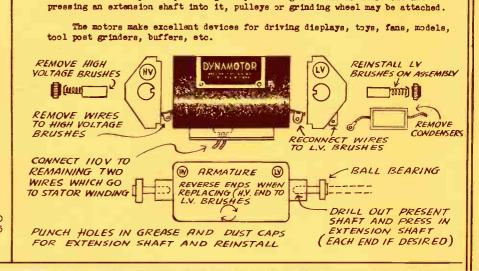Headphones (extra).....\$1.00 22" FM Loudspeaker (extra)... 1.95



The HEATH COMPANY BENTON HARBOR, MICHIGAN

Sec. 562, P. L. & R. U.S. POSTAGE 1º Paid Benton Harbor, Mich. Permit No. 273

