

FOR THE RADIO ENTHUSIAST ...

# Practical Wireless

MAY 1981

Australia \$1.25  
New Zealand \$1.30  
Malaysia \$4.00

65p

**FREE INSIDE** 2m Repeaters

**DATA CARD**

plus supporting article- **USING 2 METRES**

new series  
**SUPPRESSING  
& PROTECTING  
THYRISTORS**

**PW**  
**'STOUR'**



**TOP-BAND TRANSCEIVER**

Have You tried our  
Mail Order Service?

**Bredhurst**  
electronics

HIGH ST., HANDCROSS, W. SUSSEX 0444 400786

**BREDHURST NEWS**

TRY OUR TELEPHONE SALES SERVICE



FOR  
TWO METRES

**ICOM**  
**IC 2E £159**  
inc. VAT & CARRIAGE



**FDK MULTI 700EX**  
**£199**, inc. VAT  
free Delivery



**YAESU**  
**FT480R**  
**£359** inc. VAT  
free Delivery

**TRANSCEIVERS**



**FP707**  
**£109**

H.F.		
TRIO TS130V	£418.00	£404.00
SWAN 100MX	£465.00	
YAESU FT707S	£488.00	
TRIO TS130S	£529.00	
YAESU FT101Z	£569.00	
YAESU FT707	£613.00	
YAESU FT1012D	£639.00	
SWAN ASTRO 150	£690.00	
TRIO TS830S	£798.00	
YAESU FT107M		
SWAN 102BX		




**FT707**  
**£529**

HANDHELDS		
FDK PALM II	£99.00	
YAESU IC2E	£159.00	
FDK PALM IV (70 cms)	£166.00	
TRIO TR2300	£178.00	
A.O.R. AR245A	£195.00	
YAESU FT207R	£198.00	
TRIO TR2400	£209.00	
STANDARD C78 (70 cms)		



**FC707**  
**£80**

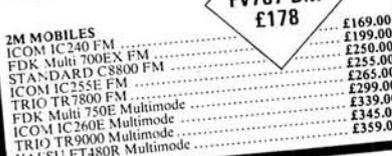

**FV707 DM**  
**£178**

2M MOBILES		
ICOM IC240 FM	£169.00	
ICOM Multi 700EX FM	£199.00	
STANDARD C800 FM	£250.00	
ICOM IC255E FM	£265.00	
TRIO TR7800 FM	£299.00	
FDK Multi 750E Multimode	£339.00	
ICOM IC260E Multimode	£345.00	
TRIO TR9000 Multimode	£359.00	
YAESU FT480R Multimode		

**RECEIVERS**



**TRIO**  
**R1000**  
**£285**

H.F.		
LOWE SRX30	£158.00	
YAESU FRG7	£189.00	
TRIO R1000	£285.00	
YAESU FRG7700	£309.00	
2M. F.M.		
SEARCH 9	£45.00	
FDK TM56B	£89.00	
A.O.R. AR22	£83.00	
SX 200	£137.00	
BEARCAT 220FB	£258.00	
MARINE VHF		
SEARCH 9	£45.00	
FDK TM56B	£89.00	
BEARCAT 220FB	£89.00	
AIRBAND		
RS17 Handheld	£49.50	



**YAESU**  
**FRG7700**  
**£309**

**ACCESSORIES**

MORSE EQUIPMENT		Carriage
HK 707 Up/Down Key	£10.50 (€0.50)	
MK 704 Squeeze paddle	£10.50 (€0.50)	
EK121 Elbug	£29.95 (€0.50)	
EK112 Matching side tone oscillator	£10.95 (€0.50)	
EK150 Electronic keyer	£74.00 (—)	
SWR - POWER METERS		
YW 3 Twin Meter	£11.50 (€0.50)	
TOYO T435 (144-435 MHz)	£34.45 (€0.75)	
TOYO T435 (1.8-150 MHz)	£35.00 (€0.75)	
DAIWA SW110A (1.8-150 MHz)	£49.95 (€0.75)	
WELZ SP200 (1.8-150 MHz)	£49.95 (€0.75)	
WELZ SP400 (130-500 MHz)	£52.80 (—)	
DAIWA CN620A (1.8-150MHz)	£69.95 (—)	
WELZ SP300 (1.8-500MHz)	£71.00 (—)	
SAFETY MICROPHONES		
ADONIS MM202S Clip on	£20.95 (€0.50)	
ADONIS MM202H Head + Band + Up/Down	£29.00 (€0.50)	
ADONIS MM202FU Swan Neck + Up/Down	£30.00 (€0.50)	
ADONIS MM202F infra red link	£45.00 (€0.50)	
DAIWA RM940 infra red link	£45.00 (€0.50)	
DESK MICROPHONES		
YAESU YD14S (Dual Imped)	£20.95 (€0.75)	
TRIO MC50 (Dual Imped)	£24.15 (€0.75)	
ADONIS AM502 Compressor Mic	£39.00 (€0.75)	
ADONIS AM802 Compressor Mic 3 O/P	£59.00 (€0.75)	
PROBLEMS WITH T.V.I.		
YAESU Low Pass Filter FF501DX (IKW)	£22.00 (€0.75)	
HP3A High Pass Filter (TV down lead)	£3.50 (€0.25)	
Ferrite Rings (Pair)	£0.80 (€0.20)	

**DRAE PRODUCTS**

**POWER SUPPLIES**  
fully protected  
overvolts - current limit - thermal.

4 amp	£27.95 (€1.50)
6 amp	£44.95 (€2.00)
12 amp	£69.00 (€2.00)
24 amp	£92.00 (€3.00)

**WAVE METER**  
**£24.95** inc. VAT  
and carriage.

A new wavemeter designed to meet the requirements of 2M operators.  
Frequency Range 130 kHz to 450 MHz

MOBILE ANTENNAE (All with PL259 fitting)	Carriage
14 MHz 1/4 (20SE)	£13.80 (€1.50)
14 MHz 1/4 (15SE)	£11.50 (€1.50)
21 MHz 1/4 (10SE)	£11.50 (€1.50)
28 MHz 1/4 (0dB)	£1.50 (€0.50)
144 MHz 1/4 (0dB)	£8.50 (€1.50)
144 MHz 5/8 (3dB)	£13.00 (€1.50)
144 MHz 7/8 (4-5dB)	£11.50 (€1.50)
432 MHz 2x5/8 (5-5dB)	£3.50 (€0.50)
CABLE MOUNT	£6.95 (€0.50)
GUTTER CLIP	£3.50 (€0.50)
MAGNETIC MOUNT	£3.50 (€0.50)
ROOT LIP MOUNT	
MICROWAVE MODULES	
NMC 144/28 converter	£27.90 (€0.75)
NMC 432/28 converter	£34.90 (€0.75)
NMC 432/144 converter	£34.90 (€0.75)
NMC 1296/28 23cm converter	£32.20 (€0.75)
MMK 1296/144 converter	£59.80 (€1.00)
MMT 144/28 transverter	£9.90 (€1.00)
MMT 432/28 transverter	£149.00 (€1.00)
MMT 432/144 transverter	£184.00 (€1.00)
MMT 1296/144 transverter	£59.00 (€0.75)
MML 144/25 linear	£77.00 (€0.75)
MML 144/40 linear	£142.60 (€1.00)
MML 144/100P linear	£77.00 (€1.00)
MML 432/20 linear	£119.00 (€1.00)
MML 432/50 linear	£228.00 (€1.00)
MML 432/100 linear	£69.00 (€1.00)
NMD 50/500 500 MHz counter	£14.95 (€0.75)
NMA28 10M Preamp	£34.90 (€0.75)
NMA 144V Preamp RF switched	

**MAIL ORDER - RETAIL CALLERS 9-5.30 PM.**  
**THE HIGH STREET, HANDCROSS, W. SUSSEX, 0444 400786**

TO ORDER ANY OF THE ABOVE ITEMS SIMPLY WRITE, ENCLOSING A CHEQUE OR PHONE YOUR CREDIT CARD NUMBER



**EDITORIAL OFFICES**

Practical Wireless  
Westover House  
West Quay Road  
Poole, Dorset BH15 1JG  
☎ Poole 71191

**Geoff Arnold G3GSR**  
Editor

**Dick Ganderton C.Eng., MIERE, G8VFW**  
Assistant Editor

**Peter Metalli**  
Art Editor

**John Fell G8MCP**  
Technical Editor

**Alan Martin G8ZPW**  
News & Production Editor

**Elaine Howard G4LFM**  
Technical Sub-Editor

**Rob Mackie**  
Technical Artist

**Keith Woodruff**  
Assistant Art Editor

**Sylvia Barrett, Sharron Breeze**  
Secretarial

**ADVERTISEMENT OFFICES**

Practical Wireless  
King's Reach Tower  
Stamford Street  
London SE1 9LS  
Telex: 915748 MAGDIV-G

**Dennis Brough**  
Advertisement Manager  
☎ 01-261 6636

**Roger Hall G8TNT (Sam)**  
Ad. Sales Executive  
☎ 01-261 6807

**Claire Gerrish**  
Secretary  
☎ 01-261 6636

**Colin R. Brown**  
Classified Advertisements  
☎ 01-261 5762

**Dave Kerindi**  
Make-up & Copy  
☎ 01-261 6570

**COPYRIGHT**

© IPC Magazines Limited 1981. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable.

We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

# Practical Wireless

MAY 1981

VOL. 57

NO. 5

ISSUE 890

## contents

- 18 CB UK—The Home Office Statement**
- 20 Bi-phase Comparator**  
*A. J. Birkinshaw G3DMC*
- 22 Radio Special Product Report**  
Yaesu FT-707 h.f. s.s.b. Transceiver
- 27 Suppressing and Protecting Thyristors—1**  
*Ben J. Duncan*
- 34 Computers in Radio**  
*Mervyn J. Axson G8WHG*
- 36 PW "Stour" Top-Band Transceiver—1**  
*David G. Barrell G4BMC*
- 44 Assessing the New RAE—the First Two Years**  
*Arthur Harada G4INX*
- 45 Kindly Note**  
*PW "Sherborne", Oct. 80. PW "Helford", Apr. 81. Mods No. 5, Apr. 81.*
- 48 Using 2 metres**  
*J. M. Fell G8MCP*
- 56 Ultra-fast Stereo Peak Indicator**  
*G. S. Macauley*
- 58 Mobile Suppression Techniques—2**  
*John M. Fell G8MCP*
- 62 Radio Special Product Report**  
Tono 0-7000E Communications Computer

Please see page 33 for a special announcement regarding the PW "Winton" Stereo Tuner

**FREE WITH THIS ISSUE****PW DATACARD "2m Repeaters"**

- |                        |                            |
|------------------------|----------------------------|
| <b>93 Advert Index</b> | <b>47 Next Month</b>       |
| <b>18 CB UK</b>        | <b>67 On the Air</b>       |
| <b>17 Comment</b>      | <b>42 Production Lines</b> |
| <b>45 Kindly Note</b>  | <b>17 Services</b>         |
| <b>46 Mods</b>         | <b>55 Uncle Ed</b>         |
| <b>19 News</b>         | <b>33 YL Column</b>        |

# THE SHIMIZU SS105S *80-10 metres ssb/cw transceiver*



This super new transceiver covers 80-10 metres, gives 10W out and is smaller than anything else we have seen so far. Ideal for transverter driving, the SS105S has FM transmit and receive options as well as excellent performance on SSB/CW for HF band use. The SS105S is supplied in semi kit form so as to keep down the price, but all the RF and mixer boards are ready built and aligned so no test equipment is required. All the cabinet work has been carried out so all you have to do is assemble the IF strip, xtal oscillator, and fit them to the completed chassis. Great idea and it brings back the flavour of home brew with the added advantage that the rig will work when you've finished it. For more info, just ask us or come along and see it. It's a great little rig.

			NETT. inc. VAT CARR.
SS105S	80-10m solid state SSB/CW/FM transceiver. Semi kit form	225.00	258.75 4.50
SE-NB	Noise blanker kit	6.75	7.76 .50
SE-FMrx	RX FM discriminator kit	15.00	17.25 1.00
SE-FMtx	TX FM generator kit	11.00	12.65 1.00
SE-MK	RX marker kit	9.60	11.04 .50
0.5 CWF	500 Hz CW filter	19.50	22.43 .50
	Optional band crystals	3.00	3.45 .25


**AR 22** *2 metre FM pocket synthesized, 141-149 MHz receiver.*

**AR 240A** *2 metre hand held synthesized 144-146 1½ watt transceiver*

**AR 22 £83 inc. VAT. AR 240A £158 inc. VAT. Carriage 1.50.**

*Also available is a marine version of the AR22, the AR22M, 156-162 MHz £89.*

## CORDLESS INFRARED MOBILE MIKE

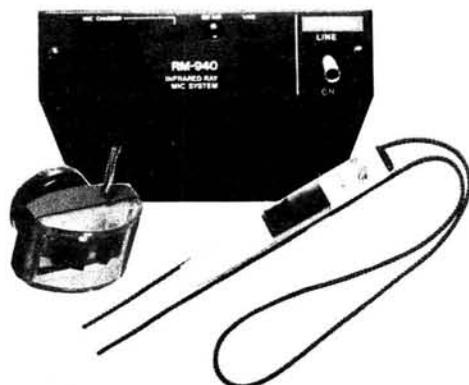

The Daiwa infrared mike system, comprising of a control box, sensor and infrared mike enables you to dispense with the hand mike and cable when operating in your car or shack. By using an infrared beam audio is transmitted from the mike to the sensor and then to the control box which activates the transmitter. To transmit, press the locking switch on the mike and talk. To receive, release the switch and your rig immediately returns to receive. When you have finished your contact return the mike to its slot in the control box and the mike nicad battery is maintained at full charge. For those of you who like fresh air and drive with all windows open there is a matching wind shield available at an additional 75p. So there we are, the latest in technology to bring safety to your mobile operation, the Daiwa infrared mike.

**DAIWA INFRARED MIKE SYSTEM**  
**£45.00 inc. VAT.**  
 Carriage £1.50.



## FREQUENCY COUNTER *Model HFC 55.*

The HFC55 is a sensibly priced, easy to use digital frequency meter covering 10 kHz-55 MHz in a single range. The bright 5 digit display gives a direct reading of frequency when the built in telescopic aerial is placed near a source of RF. The HFC 55 operates from internal dry batteries and is housed in a strong metal case to withstand regular and continuous use.

**HFC55 Frequency Counter £36.50 inc. VAT. Carriage £1.50**


## POWER SUPPLY UNITS

*the PP1305 4 amp 13.8 volts d.c. £18.40 inc. VAT.*

*the PP137 7 amp 13.8 volts d.c. £32.00 inc. VAT.*

*the PP1310 10 amp 13.8 volts d.c. £49.50 inc. VAT.*

*Carriage £2.00.*

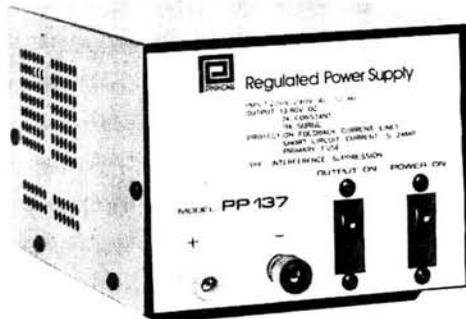

**LOWE  
 ELECTRONICS LTD**

**CHESTERFIELD ROAD, MATLOCK, DERBYSHIRE. Tel. 0629/2817.**



# TRIO *pacesetter in amateur radio*



**TR-7800 2 METRE FM TRANSCEIVER**  
*The only 2 metre FM mobile* £268



**TS770E 2m/70cm DUAL BANDER**  
*"towards new horizons"* £730.25



**TR2300**  
**2M PORTABLE**  
**£166.75**



**TR-8400 70cm FM TRANSCEIVER** *"70cm is on the move."*  
£279




**TR-9000 2M MULTIMODE**  
*"A new direction"* £345

**TR-2400 2M HAND PORTABLE** *"handshack"* £198.95




**R-820 AMATEUR RECEIVER** £690

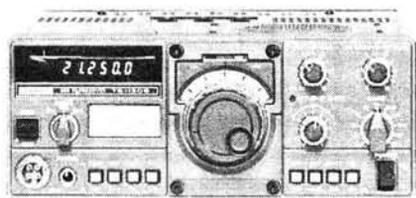

**TS 130 S/V** *"a big little rig"* £491/£404



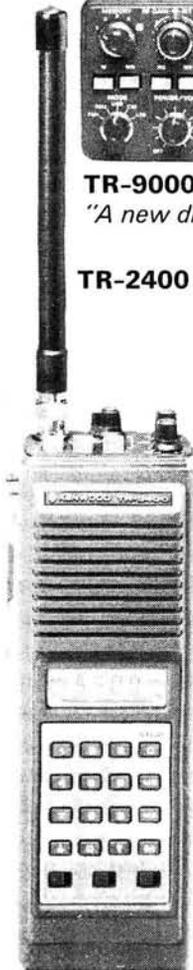**TS 830S 160-10M TRANSCEIVER**  
*"top notch"* £639.52



**R1000 GENERAL COVERAGE RECEIVER**  
*"hear there and everywhere"* £285



**TS180S 160-10M TRANSCEIVER** £679.65  
**PS30 POWER SUPPLY UNIT** £85.00

NOTE PRICES AS OF JAN 1981  
ALL PRICES INCLUDE VAT. CARRIAGE ADDED TO ALL ITEMS £4.50.

## HEAD OFFICE AND SERVICE CENTRE

Chesterfield Road, Matlock, Derbys. Tel. 0629 2817 or 2430.

Open Tuesday-Friday 9-5.30, Saturday 9-5.00. Closed for lunch 12.30-1.30.

For all that's best in ham radio, contact us at Matlock.

For full catalogues send 70p in stamps with your address. Mark enquiry PW.



# Get a great deal from Marshall's

## CRIMSON ELEKTRIK HI FI MODULES

CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	" "	£26.30
CE 1704	" "	£33.48
CE 1708	" "	£33.48
CPS 1	Power Unit	£19.52
CPS 3	" "	£23.52
CPS 6	" "	£30.00
CPR 1	Pre Amp	£32.17
CPR 1S	" "	£42.52

## SINCLAIR INSTRUMENTS

Digital Multimeter		
	PDM35	£34.50
" "	DM235	£52.50
" "	DM350	£72.50
" "	DM450	£99.00
Digital Frequency Meter		
	PFM200	£49.80
Low Power Oscilloscope		
	SC110	£139.00
TF200 Frequency Meter		£145.00
TGF 105 Pulse Generator		£85.00


## NEW

LCD Multimeter	TM351	£99.00
LCD Multimeter	TM352	£49.95
Prescaler	TP600	£37.50

## New

Presensitised PC Boards, Developer. U.V. units, Toyo miniature Fans 230v AC £9.95  
Mini Metal Detector/Voltage Tester for locating cable under plaster £9.95  
Flow/Speed Sensors for monitoring fuel consumption electronically in vehicles

## Just one of the exciting Leader range

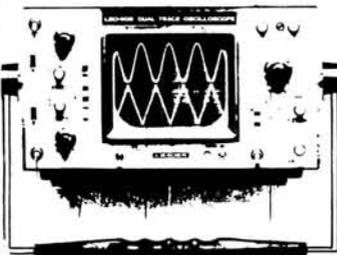

**LBO508A  
OSCILLOSCOPE**  
With 20MHz DC bandwidth and 10 mv input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications.

## Send SAE for details of full range.

Marshall's 80/81 catalogue is now available by post, UK 75p post paid Europe 95p post paid: Rest of world £1.35 post paid.

A. Marshall (London) Ltd., Kingsgate House,  
Kingsgate Place, London NW6 4TA.  
Industrial Sales: 01-328 1009  
Mail Order: 01-624 8582 24hr service.

Also retail shops: 325 Edgware Road, London W2.  
40 Cricklewood Broadway, London NW2. 85 West Regent St.  
Glasgow. 108A Stokes Croft, Bristol.

## ILP HI FI MODULES

Power Amplifiers		
HY30		£7.29
HYY60		£8.33
HY120		£17.48
HY200		£21.21
HY400		£31.83

## Pre Amplifiers

HY6		£6.44
HY66		£12.19

## Power Supplies

PSU30		£4.50
PSU36		£8.10
PSU60		£4.75
PSU70		£13.04
PSU180		£21.34

## MULTIPLEX NICKEL CADMIUM CELLS

Type S101 (HP4)		£0.98
Type SubC (HP11)		£1.75
Type SubD (HP2)		£1.95
Friwo Chargers for above Penlight		
4: accommodates 1-4 size HP7		£5.50
Combibox FW611: accommodates		
HP7, HP11		£13.25

**NOTE ALL PRICES NET.  
EXCLUDING VAT.  
POSTAGE/PACKING**

# J. BIRKETT

Partners: J. H. Birkett, J. L. Birkett)

Radio Component Suppliers  
25 The Strait, Lincoln. LN2 1JF

**SUPER JUMBO ORP12 CADMIUM SULPHIDE PHOTOCONDUCTIVE CELL TYPE RPY18** with data = £1.65 each  
**LEAD SULPHIDE PHOTOCONDUCTIVE CELL RPY75** with data = £3.50.  
**RPY75A WITH GERMANIUM FILTER** with data = £4.50.  
**ORP62 CELL** with data = £1.30 each.  
**COX85A GALLIUM ARSENIDE PHOSPHIDE NINE SEGMENT DISPLAY** for numbers 1 To 9 Red light with data = £1.85.  
**SUB-MINIATURE AXIAL RED LEDS CQV60** - 20p each.  
**MULLARD PHOTO TRANSISTORS BPX 70** - 50p each.  
**SLOTTED OPTO-SWITCH INFRA-RED SOURCE** = £1.50.  
**405 To 475 MHz 3 PORT CIRCULATOR AND ISOLATOR WITH CONNEX SOCKETS** Type HGA 3552-2 By Microwave and Electronic Systems Ltd. = £17.50 each.  
**BUTTERFLY PRE-SET VARIABLES** Spindles easily extended 25 x 25pf = 50p, 38 x 38pf = 60p, 38 x 38pf Wide Spaced = 65p.  
**X BAND GUNN DIODES** with data = £1.65.  
**X BAND TUNING VARACTORS** 1 To 2pf or 3 To 4pf Both £1.65 each.  
**X BAND DETECTOR DIODES LIKE SIM 2** - 15p, 1N23 - 25p.  
**X BAND DETECTOR DIODES CS88** - 25p.  
**SOLDER-IN FED THRU** = 6 Gp, 27pf, 300pf, 1000pf All 20p doz.  
**EDDYSTONE TRANSMITTING VARIABLE** 30 - 30pf (60pf) = £2.20.  
**MULLARD SUB-MINIATURE DISCS** 1000pf 63v.w. = 25p doz.  
**CRYSTALS SUB-MINIATURE 10MHz T05 Case** = £2.30, 10X Type 5MHz = 50p.  
**WIRE ENDED TYPE CRYSTALS** 28KHz, 28.5KHz. Both 50p each.  
**BFS21 MATCHED PAIR OF FETS** = 50p pair.  
**BSV81 INSULATED GATE VHF FET (MOST)** - 30p.  
**N CHANNEL FETS 2N 3822** - 30p, 2N 3823 - 25p.  
**4500 PIV 2 amp SILICON DIODES** = £1.50 each.  
**SOLID SILVER WIRE ENDED VHF AERIAL SWITCHING PIN DIODES** with circuits in Packs of 10, untested for £1.50.  
**HIGH POWER AERIAL SWITCHING PIN DIODES** Stud Mounting 200 Watts Plus = 45p each.  
**SINCLAIR AA TYPE NI-CAD BATTERY CHARGER** = £3.30.  
**FETS SIMILAR TO MPF 105 TEXAS TIS14** - 4 for £1.  
**VHF R.F. CHOKES** 100U.H., 330U.H., 330U.H. All 7p each.  
**FERRANTI WIRE ENDED SILICON DIODES** 800 PIV 750mA 12 for £1.  
**50 ASSORTED DISC CERAMICS** or 50 POLYSTYRENE CAPACITORS ASSORTED Both 60p.  
**MULLARD UHF MODULE BGY 21** 420-470 MHz 12 volt Min. Power Out 1.2 Watt, 20mW Drive with data = £12.  
**MULLARD UHF MODULE BGY 22C** 380-512 MHz 13 volt Min. Power Out 2.5 Watt 50mW Drive with data = £12.50.  
**MULLARD UHF MODULE BGY23** 12 volt 420-480MHz Min. Power Out 7 watt 2.5 Watt. Drive with data = £15.  
**MOTOROLA UHF MODULE 440MHz** 13 volt, 13 watt out, 150mW Drive Type MHW710/2 with data = £12.50.  
**MULLARD 175MHz POWER TRANSISTOR** 40 watt FM or SSM 5 watt Drive 28 volt Type 570BL with data = £8.30.  
**MULLARD HF-VHF POWER TRANSISTOR** 27 To 70MHz 28 volt 40 watt 2 watt Drive with data. Type 587BL with data £3.  
**MULLARD BLY55 175MHz 4 watt 13 volt 400mW Drive** £2.50.  
**MULLARD UHF TRANSISTOR BFR 64** 470MHz, 12-24 volt 4 watt with data = £4.  
**MULLARD HIGH POWER UHF TRANSISTOR BLW82** 13 volt 30 watt 470MHz = £9.80.  
**UNMARKED GOOD VHF POWER 2N 3886** - 3 for 75p.  
**MINIATURE AIR SPINDLE TRIMMERS** 50pf = 20p each.  
**6.2 Volt 2 watt WIRE ENDED ZENERS** 15p - 5 for 60p.  
**FERRANTI 2TX 108 TRANSISTORS** Plastic BC 108 - 6 for 50p.  
Please add 30p for post and packing, orders over £3 postfree.

## PCB's FOR PRACTICAL WIRELESS PROJECTS

July 79	A/F Voltmeter	WRO55	£1.35
July 79	AA/M/FM Fre quency Readout	WRO52	£3.96
July 79	V Mos Top Band Trans.	WRO56	£4.28
July 79	Sound Operated Switch	WK005/6	£4.00
August 79	Telephone Bell Repeater	WRO53	£1.35
August 79	Automatic Intercom	WRO45	£6.50
August 79	Automatic Intercom Part 2	WRO58	£0.90
September 79	Noise Blanka	WRO57	£1.85
October 79	Burglar Alarm	WRO59	£1.53
October 79	Burglar Alarm	WRO60	£2.25
January 80	Radio Control Receiver	WRO64	£3.25
January 80	A. F. Speech Processor	WRO68	£2.68
January 80	Parkhurst Alarm	WRO63	£2.81
January 80	Wide Band FF Pre Amp	WRO67	£1.05
January 80	Radio Control Encoder	WRO71	£1.35
January 80	Radio Control T.X.	WRO62	£2.56
March 80	Duel Trace Lnit-Special Offer-	WRO69	£4.00
April 80	Speed Controller	WRO65	£1.70
April 80	Stereo Auto Fader Mike Pre Amp	WRO71	£1.25
April 80	Stereo Auto Main Board	WRO72	£3.46
April 80	Signal Generator	WRO70	£3.00
April 80	Nimbus Relay	WRO75	£0.95
April 80	Nimbus Modulator	WRO74	£1.10
April 80	Nimbus Transceiver	WRO73	£1.35
May 80	Hundred Second Photo Timer	WRO78	£2.78
May 80	N.B.F.M. De modulator	WAD509	£2.20
June 80	Audio Limiter Main Board	WK076	£2.30
June 80	Audio Limiter	WK077	£1.45
June 80	Audio Limiter RF Input Board	WRO79	£1.60
June 80	VHF/UHF Repeater Timer Board	WRO80	£2.25
June 80	Nimbus Base Station Adpt.	WRO81	£2.90
June 80	Acoustic Flash Trigger	WK084	£1.65
August 80	Model Railway Controller	WRO85	£2.47
September 80	Transceiver Power Unit	WRO95	£1.00
September 80	Nimbus Tonburst/Timer Mod	WRO96	£2.15
September 80	Beginners 2 Meter Converter	WAD634	£1.38
September 80	Tamar Boar-Is. Full set-Special Offer-		£7.00
October 80	Direct Conversion Receiver	WRO82	£1.70
October 80	Nimbus 2	WRO97	£1.10
November 80	Linear Scale Res. Meter	WAD641	£1.25
November 80	Field Test Set	WK100	£1.25
November 80	Field Test Set	WK101	£1.25
November 80	Shorben S/n.		£2.59
December 80	P.W. Helford	C4CLF	Set of Two
December 80	P.W. Helford V.F.O.	WR104	£0.85
December 80	P.W. Helford Buffer Amp.	WR103	£1.25
December 80	Bird Scarer	WRO101	£1.29
December 80	Bird Scarer	WRO102	£1.40
January 81	P.W. Tynnt am Multimeter	WR111	£4.47
January 81	P.W. Helford Preslector	WRO54	£1.20
January 81	P.W. Helford T.X. Pre Amp	WR105	£1.20
January 81	P.W. Helford T.X. First Pre Amp	WR107	£1.20
February 81	Accented Metronome	WK102	£1.86
February 81	P.W. Morse Tutor	WRO81	£3.70
February 81	P.W. Morse Tutor Power Supply	WR114	£1.20
February 81	Tap Slide Controller	Set of three	£1.50
February 81	PW Auto-Scan	Set of three	£12.00
February 81	PW Helford	WR106	£1.85
February 81	PW Helford	WR108	85p
February 81	PW Helford	WR109	85p
February 81	PW Helford	WR115	95p
March 81	PW Helford	WR119	£2.20
March 81	PW Helford	WR120	80p
March 81	Active Antennas	WAD784	£1.15

Prices include VAT Post free  
Full range of R. S. Components available please phone for quote

# C. BOWES ELECTRONICS

252A STOCKPORT ROAD, CHEADLE HEATH, CHESHIRE SK3 0LX.  
Tel: 061-428 4497 ex. 5

**S.E.M.**  
**BOX 6, CASTLETOWN,**  
**ISLE OF MAN.**  
**TEL. MAROWN (0624) 851277.**

**THE NEW SENTINEL AUTO 2 METRE PRE-AMPLIFIER**

In the five years since we first thought of r.f. switched automatic pre-amps. we have learned a lot about them. The benefit of all this experience has been put into the Sentinel Auto Mk II. These include NEW PROTECTION circuit to give MAXIMUM LEGAL through power rating. Completely new (and unique) third generation DUAL GATE MOSFET pre-amp giving 1db N.F. and 20db gain with GAIN CONTROL and OFF switch (straight through when OFF). The r.f. switch has a delay for use on ANY MODE. High Q tuned circuits for high selectivity. 12V 25mA. Size: 1½" x 2¼" x 4". **£25.00\*** 2 or 4 metres, 70cm version **£28.00\***. All ex stock.

**PA5**

Same as above plus 240V ac supply **£30.00**. Ex stock.

**SENTINEL STANDARD 2 METRE PRE-AMPLIFIER**

Same performance as above but less r.f. switch. **£15.00\*** 2 or 4 metres, 70cm version **£17.50\***. All ex stock.

**PA3**

Same new circuit as above in about 1 cubic inch to fit inside your transceiver. **£7.95**. 70cm version **£10.70\***. Ex stock.

**SENTINEL 2 METRE POWER AMPLIFIER/PRE-AMPLIFIER**

The units have been re-designed making use of the latest techniques and transistors for highest reliability and performance. Infinite SWR PROTECTED devices. ULTRA LINEAR, all modes. R.F. switched. Same POWER GAIN at lower drive powers. Supply 13.8V nominal. Three models.

**1. SENTINEL 35**

Twelve times Power gain. 3W IN 35W OUT. Max. drive 5W 3.8 amps. 6" x 2¼" front panel, 4½" deep. **£57.50** ex stock.

**2. SENTINEL 50**

Five times power gain. 10W IN 50W OUT. Max. drive 16W 6 amps. Same size as Sentinel 35. Ex stock. **£69.50**.

**3. SENTINEL 100**

Ten times power gain. 10W IN 100W OUT. Max. drive 16W. Size: 6½" x 4" front panel, 3½" deep. 12 amps. Price: **£126.50**. Ex stock. All available less pre-amp for **£8.00** less.

**MAINS POWER SUPPLIES FOR SENTINEL POWER/PRE-AMPLIFIERS**

6 amps for the 30 and 50. **£34.50**. 12 amps for the 100. **£47.00**. Both ex stock.

**SENTINEL H.F. WIDEBAND PRE-AMPLIFIERS**

2-40MHz 15dB gain. Ideal for 15 and 10 metres and OSCAR or an ACTIVE AERIAL. 9-12V. Size: 2½" x 1½" x 3". Two versions.

**1. SENTINEL STANDARD H.F. PRE-AMPLIFIERS**

Performance as above **£10.00\***. Ex stock.

**2. SENTINEL AUTO H.F. PRE-AMPLIFIERS**

Same performance as above with a change over relay. r.f. operated by your transceiver for direct connection in your aerial co-ax. **£16.93\***. Ex stock.

**S.E.M. IAMBIC KEYS**

Undoubtedly the best keyer circuit, it uses the CURTIS custom designed CMOS LS1 chip. Sidetone, tune, etc. As users say "I've never been able to use one before." **£34.50** ex stock.

CMOS Twin Paddle Touch Key **£15.00** ex stock.

**S.E.M. TRAN Z MATCH** has had a few changes too. NOW covers 160-10M.

The most VERSATILE transmatching system. Will match from 15 to 5000 Ohms BALANCED or UNBALANCED at up to 1kW. Link coupled balun means no connection to the equipment, which can cure TV1 both ways. 160-10M TRAN Z MATCH **£57.00**. 80-10M **£50.00**. EZITUNE built in for **£19.50** extra. SO239 and 4mm connections for co-ax or wire feed. **S.E.M. FORWARD/REFLECTED POWER METER - £28.80**. Ex stock.

**NEW! SENTINEL L.F. CONVERTER**

10kHz-2MHz IN, 28-30MHz OUT. 9-12V. 5mA. **£20.80**. Ex stock.

**SENTINEL DUAL GATE MOSFET 2 METRE CONVERTERS**

IFs: 2-4MHz, 4-6MHz, 28-30MHz. 2dB N.F. 30dB gain. 9-12V. 15mA. **£24.73**. 4 metre 28-28.7MHz IF. **£24.73**.

**SENTINEL X 2 METRE CONVERTER**

Same as above plus mains power supply. **£28.80**. Ex stock.

**SENTINEL TOP BAND CONVERTER**

1.8-2.3MHz IN 14-14.5MHz OUT. 9-12V. 5mA. **£20.80**. Ex stock.

**SENTINEL 70 - 70cm CONVERTER**

432-434MHz IN 28-30MHz OUT. 12V. 20mA. **£28.80**. Ex stock.

**12 MONTHS COMPLETE GUARANTEE**

Prices include VAT and delivery. C.V.O. or credit cards. Phone card number for same day service. Items marked \* have Belling Lee sockets. Add £1.73 for SO239s. It's impossible to put everything in here but RING or WRITE for more information.

BL plugs 25p. PL259s 80p.

S.E.M. Lynwood, Union Mills, Isle of Man

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroids cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

**30VA** 70mm dia. x 30mm Weight 0.45 Kg **£4.71**  
 (+£1.00 p.p. + 0.86 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6+6	2.50
1X011	9+9	1.66
1X012	12+12	1.25
1X013	15+15	1.00
1X014	18+18	0.83
1X015	22+22	0.68
1X016	25+25	0.60
1X017	30+30	0.50

**50VA** 80mm dia. x 35mm Weight 0.9 Kg **£5.19**  
 (+£1.10 p.p. + 0.94 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
2X010	6+6	4.16
2X011	9+9	2.77
2X012	12+12	2.08
2X013	15+15	1.66
2X014	18+18	1.38
2X015	22+22	1.13
2X016	25+25	1.00
2X017	30+30	0.83
2X028	110	0.45
2X029	220	0.22
2X030	240	0.20

**80VA** 90mm dia. x 30mm Weight 1 Kg **£5.76**  
 (+£1.20 p.p. + £1.04 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
3X010	6+6	6.64
3X011	9+9	4.44
3X012	12+12	3.33
3X013	15+15	2.66
3X014	18+18	2.22
3X015	22+22	1.81
3X016	25+25	1.60
3X017	30+30	1.33
3X028	110	0.72
3X029	220	0.36
3X030	240	0.33

**120VA** 90mm dia. x 40mm Weight 1.2 Kg **£6.72**  
 (+£1.30 p.p. + £1.20 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
4X011	9+9	6.66
4X012	12+12	5.00
4X013	15+15	4.00
4X014	18+18	3.33
4X015	22+22	2.72
4X016	25+25	2.40
4X017	30+30	2.00
4X028	110	1.09
4X029	220	0.54
4X030	240	0.50

**160VA** 110mm dia. x 40mm Weight 1.8 Kg **£8.88**  
 (+£1.40 p.p. + £1.54 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
5X012	12+12	6.66
5X013	15+15	5.33
5X014	18+18	4.44
5X015	22+22	3.63
5X016	25+25	3.20
5X017	30+30	2.66
5X018	35+35	2.28
5X028	110	1.45
5X029	220	0.72
5X030	240	0.66

**225VA** 110mm dia. x 45mm Weight 2.2 Kg **£10.59**  
 (+£1.50 p.p. + £1.81 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
6X014	18+18	6.25
6X015	22+22	5.11
6X016	25+25	4.50
6X017	30+30	3.75
6X018	35+35	3.21
6X026	40+40	2.81
6X028	110	2.04
6X029	220	1.02
6X030	240	0.93

**300VA** 110mm dia. x 50mm Weight 2.6 Kg **£12.27**  
 (+£1.60 p.p. + £2.08 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
7X016	25+25	6.00
7X017	30+30	5.00
7X018	35+35	4.28
7X026	40+40	3.75
7X025	45+45	3.33
7X028	110	2.72
7X029	220	1.36
7X030	240	1.25

**500VA** 140mm dia. x 60mm Weight 4 Kg **£16.35**  
 (+£1.70 p.p. + £2.71 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
8X017	30+30	8.33
8X018	35+35	7.14
8X026	40+40	6.25
8X025	45+45	5.55
8X033	50+50	5.00
8X028	110	4.54
8X029	220	2.27
8X030	240	2.08

• I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

**CHOICE OF 3 PRIMARY INPUTS**

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.  
 For 220V Primary (Europe) insert 1 in place of "X" in type number.  
 For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V, 4A = 42013.

• CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.

**FREEPOST facility (U.K. only).**

Simply address envelope to **FREEPOST** to address below. NO STAMP REQUIRED.

**TO ORDER** Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. Also available from ELECTROVALUE and MARSHALLS.

**I.L.P. TRANSFORMERS**  
 A division of I.L.P. ELECTRONICS LTD.


**FREEPOST T1 GRAHAM BELL HOUSE ROPER CLOSE  
 CANTERBURY CT2 7EP**

Phone (0227) 54778 Technical (0227) 64723 Telex 965 780
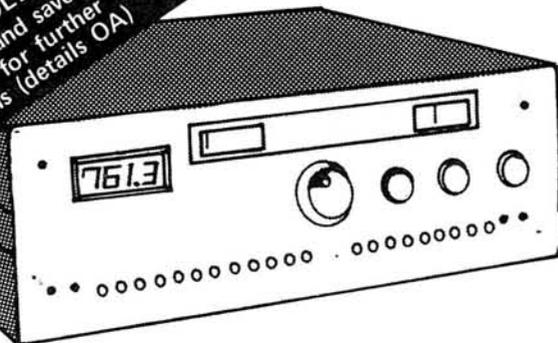
# RX 80 MkII - A DIY SOLID-STATE-OF-THE-ART MODULAR DUAL CONVERSION RECEIVER SYSTEM FOR THE ENTHUSIAST

AS DESCRIBED IN JAN/FEB/MAR 81 RADCOM BY TONY BAILEY-G3WPO : REPRINTS £1 inc

**CLUBS & COLLEGES:**  
Buy 5 kits and save 10%  
Buy more for further  
reductions (details OA)



- \* LOW DRIFT VARICAP TUNING (READILY ADAPTABLE FOR SYNTHESISED/ HUFF&PUFF STABILIZATION)
- \* DUAL CONVERSION BASED ON A 3-4 MHz SSB IF, WITH MECHANICAL IF FILTER, AUDIO DERIVED AGC, BALANCED MIXER, WITH ON-BOARD AF AMP AND VOLTAGE REGULATOR
- \* CAPACITY FOR UP TO 12HF/VHF/UHF 1 MHz WIDE CRYSTAL CONTROLLED CONVERTERS WITH TRACKED RF TUNING
- \* EACH CONVERTER SELF CONTAINED - SO MORE CAN BE USED EXTERNALLY IF REQUIRED. RF PATHS ARE DC SWITCHED AT LOW IMPEDANCE

## PRICES

RX 80 Mk II tuneable 3-4MHz SSB receiver/IF with MFL series 2.4kHz mechanical SSB IF filter	..£42.66
A/A but with low cost 4kHz CFM2 series filter	..£32.42
HF Converters, including crystal for the following bands: 1-2MHz, 7-8MHz, 10-11MHz, 14-15MHz, 18-19MHz, 21-22MHz 24-25MHz, 28-29MHz, 29-30MHz	..£9.10 ea
Hardware: Case, meters, pots, knobs (exc. DFM)	..£25.00
Complete RX 80, 6 converters, switches, case, PSU	..£132.50

## CURRENT OPTIONS INCLUDE

* LCD DFM with built in IF offset, interface PCB	..£23.75
* HUFF/PUFF vfo stabilizer	..£9.60
* NBFM adapter inc 8kHz multielement ceramic IF filter	..£9.95
* Constant Z PIN diode attenuator	..£4.95
* 12v low RF noise mains PSU	..£7.95

## PLANNED ADDITIONS TO THE SYSTEM


- 3-4MHz IF frequency synthesiser
- 'UP Conversion' front end system
- AM IF adapter
- Noise blanker
- VHF/UHF converters with helical filters



PRICES EXCLUDE VAT (15%). Postage 50p on orders under £12. Free postage on orders over £12, except please note any order including HARDWARE should be accompanied with a £2 carriage charge. General price lists are available FOC with an SAE - full AMBIT catalogues including a multitude of radio parts/components £1.80 a set - or 70p per section.


**AMBIT international** 200 North Service Road, Brentwood, Essex  
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
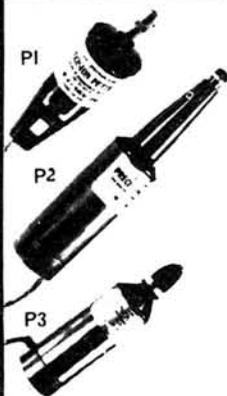
## PRECISION PETITE MINIATURE DRILLS AND ACCESSORIES for all your modelling needs



A choice of three power drills that fit snugly in the hand, so light they enable you to carry out the most intricate tasks - drilling, shaping, cutting, polishing etc in the minimum of time. There are two types of drill stand, S1 for P1 drill, S2 for all drills, plus all the necessary accessories in a remarkable range that fills every need. Fully illustrated literature is available and will be

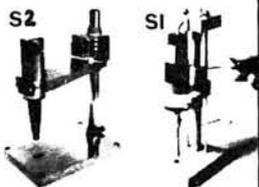gladly sent upon receipt of 9" x 4" stamped addressed envelope.  
Access & Barclaycard welcome



Sole UK Distributors **PRECISION PETITE LTD**  
119a HIGH ST. TEDDINGTON, MDX. Tel: 01-977 0878

## METALFILM RESISTORS 1% Tolerance, 1/4 Watt



### ONLY 3p EACH

Minimum order £10  
Minimum 5 pcs per value  
89 Values (E24)

100R	1k	10k	100k
110R	1k1	11k	110k
120R	1k2	12k	120k
130R	1k3	13k	130k
150R	1k5	15k	150k
160R	1k6	16k	160k
180R	1k8	18k	180k
200R	2k	20k	200k
220R	2k2	22k	220k
240R	2k4	24k	240k
270R	2k7	27k	270k
300R	3k	30k	—
330R	3k3	33k	330k
360R	3k6	36k	—
390R	3k9	39k	—
430R	4k3	43k	—
470R	4k7	47k	470k
510R	5k1	51k	—
560R	5k6	56k	560k
620R	6k2	62k	—
680R	6k8	68k	680k
750R	7k5	75k	—
820R	8k2	82k	820k
910R	9k1	91k	910k

Special Offer: 5 PCS OF EACH (445 RESISTORS) ONLY £11.50  
High Quality, High Stability, High Strength.  
VAT inclusive. Add £1.00 p&p all areas.

**ORION SCIENTIFIC PRODUCTS LTD.**  
10 Wardour St., London W1.



## DEACs VARTA BUTTONS (1.2-24V PER CELL)

VAT included  
P+P 70p per order  
RECHARGEABLE BATTERIES.

Size/Cell	225mA DKZ	600mA DKZ
4-8V Pack	25mm dia x 9mm	34 1/2 mm dia x 10mm
6-0V Pack	£3-20	£5-55
9-6V Pack	—	£6-94
		£11-10

**CYLINDRICAL NICADS** HP7 Size (500mAh) £1-00; HP11 (1800mAh) £2-35; HP2 (4000mAh) £3-20; PP3 £4-00; PP3 Charger £5-00; 1 to 4 HP7 nicads charger £7-45.

**CONSTANT CURRENT CHARGER** - Switched 9mA/25mA/50mA/120mA/200mA/400mA output - charges 1 to 12 nicads - £14-95.

**V & F SMALLCRAFT (POPLAR) LTD**  
38, STONELEIGH ROAD, CLAYHALL, ILFORD, ESSEX IG5 0JD  
Tel: 01-550-6642

LIMITED TRADE DISCOUNTS POSSIBLE ON DEACs.

LINEAR ICS		LINEAR ICS		LINEAR ICS		LINEAR ICS		4000 series		4000 series		TTL 'N' 'LPSN'		MICROMARKET		LEDS		LEDS							
TBA120S	1.00	SL1610P	1.60	HA11223	2.15	4000	0.18	4068	0.25	TTL 'N' 'LPSN'	8224	3.50	STD DOMED TYPES												
L200	1.95	SL1611P	1.60	HA11225	1.45	4001	0.18	4069	0.25	7400	0.13	0.20	7454	0.20	0.30	74128	0.74	74194	1.05	8251	6.25	5mm RED	12p		
U247B	1.28	SL1612P	1.60	HA12002	1.45	4002	0.24	4070	0.30	7401	0.13	0.20	7455	0.20	0.30	74132	0.73	74196	1.34	8255	5.40	3mm RED	15p		
U247C	1.28	SL1613P	1.89	HA12017	0.80	4007	0.30	4071	0.24	7402	0.13	0.20	7460	0.20	0.30	74136	0.40	74197	1.10	6800P	7.50	3mm RED	15p		
U257B	1.28	SL1620P	2.17	HA12402	1.95	4008	0.80	4072	0.24	7403	0.14	0.20	7463	0.20	1.24	74138	0.72	74199	1.60	6810	5.95	2.5x5 RED	17p		
U267B	1.28	SL1621P	2.17	HA12411	1.20	4008AE	0.80	4073	0.24	7404	0.14	0.24	7470	0.40		74141	0.75	74247		6820	7.45	5mm GRN	15p		
LM301H	0.67	SL1625P	2.44	HA12412	1.55	4009	0.58	4075	0.25	7405	0.18	0.26	7472	0.30		74142	2.65	74257	1.08	6850	4.90	3mm GRN	16p		
LM301B	0.30	SL624A	1.28	LC12741	1.10	4010	0.58	4076	0.90	7406	0.36		7473	0.35	0.45	74143	3.12	74260	0.69	6852	4.85	3mm GRN	16p		
MC308TC	0.65	SL1625P	2.17	SN76660N	0.80	4011AE	0.24	4077	0.35	7407	0.38		7474	0.35	0.35	74144	3.12	74279	1.60	6853	4.85	2.5x5 GRN	20p		
LM324	0.64	SL1626P	2.44			4011B	0.24	4078	0.30	7408	0.19	0.24	7475	0.56		74145		74279	0.88	6854	1.60	5mm YL	15p		
LM339N	0.66	SL1630P	1.62	FREQ. DISPLAY		4012	0.25	4082	0.28	7409	0.21	0.24	7476	0.41	0.45	74147	1.75	74283	1.20	6855	1.60	3mm YL	16p		
LM348N	1.10	SL1630P	1.62	AND SYNTH.		4013	0.56	4086	0.90	7410	0.18	0.24	7477	0.50	0.50	74148	1.09	74293	1.32	6856	1.60	3mm YL	15p		
LF351N	0.49	SL1641P	1.89	DEVICES		4015	0.95	4175	1.15	7412	0.26	0.32	7478	0.50		74149	0.99	74365	0.66	6857	1.60	2.5x5 YL	20p		
LF353N	0.76	TD42002	1.25	SA1056	3.75	4016	0.52	4503	1.15	7410	0.26		7480	0.52		74150	0.99	74366	0.66	6858	1.60	3mm YL	15p		
LM374N	3.75	ULN2242A	3.05	SAA1058	3.35	4017	0.80	4506	0.68	7413	0.32		7482	0.75		74153	0.70	74367	0.62	6859	1.60	2.5x5 YL	20p		
LM380N-14	1.00	SL12283B	1.00	SAA1059	3.35	4019	0.58	4076	0.90	7406	0.36		7485	1.04	0.99	74154	1.30	74368	0.94	6860	1.60	3mm YL	15p		
LM381N	1.81	CA3308E	1.84	LN1232	19.00	4021	0.82	4512	0.98	7416	0.30		7486		0.40	74155	0.75	74374	1.99	6861	1.60	5mm YL	15p		
ZN419CE	1.98	CA3309A	3.35	LN1242	19.00	4022	0.96	4514	2.55	7417	0.30		7489	2.05	0.40	74157	0.80	74377	1.99	6862	1.60	5mm YL	15p		
NE544N	1.80	CA3123E	1.40	MS1233	1.84	4023	0.25	4518	1.03	7420	0.19	0.24	7492	0.50	0.78	74158	2.10	74378	1.40	6863	1.60	5mm YL	15p		
NE555N	0.30	CA3130E	0.80	MSM5523	11.30	4024	0.76	4520	1.09	7421	0.38	0.24	7493	0.57	0.99	74160	0.99	74379	1.40	6864	1.60	5mm YL	15p		
NE566	0.50	CA3130T	0.90	MSM5524	11.30	4025	0.25	4521	2.36	7423	0.27		7494	0.85	1.25	74161	0.99	74380	1.40	6865	1.60	5mm YL	15p		
NE560N	3.50	CA3140E	0.46	MSM5525	7.85	4026	1.80	4522	1.49	7425	0.27		7495	0.70	1.15	74162	0.99	74381	1.40	6866	1.60	5mm YL	15p		
NE562N	4.05	CA3189E	2.20	MSM5526	7.85	4028	0.79	4529	1.61	7427	0.32	0.35	7496	0.58	1.20	74163	0.99	74382	1.40	6867	1.60	5mm YL	15p		
NE564N	4.29	CA3240	1.27	MSM5527	9.75	4029	1.04	4538	1.28	7428	0.35	0.32	7497	1.85		74164	1.20	74383	1.40	6868	1.60	5mm YL	15p		
NE565N	1.00	MC3357P	2.85	MSM5527.1	9.75	4030	0.59	4549	3.50	7430	0.17	0.26	7498	0.85	0.45	74165	1.20	74384	1.40	6869	1.60	5mm YL	15p		
NE566N	1.60	LM3900N	0.60	MSL2312	3.94	4035	1.20	4554	1.73	7432	0.32	0.28	7499	0.50		74166	2.50	74385	1.40	6870	1.60	5mm YL	15p		
NE570N	3.85	LM3909N	0.68	SPB829	3.85	4040	0.98	4560	2.18	7437	0.40		74109	0.63		74167	2.50	74386	1.40	6871	1.60	5mm YL	15p		
SL624	3.28	MC3914N	0.80	SPB847	6.00	4042	0.85	4566	1.59	7438	0.33	0.35	74110	0.54		74169	2.10	74387	1.40	6872	1.60	5mm YL	15p		
TBA851	1.81	LM3915N	0.80	SH90PC	7.80	4043	0.85	4568	2.18	7440	0.20	0.28	74112	0.68		74170	2.30	74388	1.40	6873	1.60	5mm YL	15p		
uA709HC	0.64	KB4400	0.80	HD10551	2.45	4043AE	0.93	4569	3.03	7441	0.74		74113	0.41	0.41	74171	1.05	74389	1.40	6874	1.60	5mm YL	15p		
uA709PC	0.46	KB4406	0.60	HD44015	4.45	4044	0.94	4572	3.00	7442	0.70	0.99	74114	0.85	0.40	74172	0.80	74390	1.40	6875	1.60	5mm YL	15p		
uA710HC	0.65	KB4412	1.95	HD12009	6.00	4046	1.30	4585	1.00	7443	1.12		74115	0.85	0.40	74173	0.84	74391	1.40	6876	1.60	5mm YL	15p		
uA710PC	0.46	KB4424	1.95	HD44752	4.45	4047	0.99			7444	1.12		74116	0.85	0.40	74174	0.84	74392	1.40	6877	1.60	5mm YL	15p		
uA710CH	0.66	KB4417	1.80	MC145151	12.45	4049	0.76			7446	1.32		74117	0.85	0.40	74175	0.84	74393	1.40	6878	1.60	5mm YL	15p		
uA7141C	0.27	KB4420B	1.95	MC145156	8.75	4050	0.55			7447	1.32		74120	1.15		74181	2.80	74394	1.40	6879	1.60	5mm YL	15p		
uA747CN	0.70	TD44420	2.65	MISC		4051	0.78			7448	1.32	0.89	74121	0.48		74184	1.35	74395	1.40	6880	1.60	5mm YL	15p		
uA748CN	0.70	TD44420	2.65	ICM7106CP	9.55	4052	0.79			7448	1.32	0.99	74123	0.73		74185	1.34	74396	1.40	6881	1.60	5mm YL	15p		
uA753	2.44	KB4424	1.65	ICM7107CP	9.55	4053	0.78			7449	1.32	0.99	74124	0.73	1.80	74190	0.92	74397	1.40	6882	1.60	5mm YL	15p		
uA758	0.35	KB4431	1.95	ICM7168P	19.50	4063	1.18			7451	2.00	0.25	74125	0.55	1.80	74192	1.20	74398	1.40	6883	1.60	5mm YL	15p		
TBA820M	0.78	KB4432	1.95	ICM7168P	19.50	4063	1.18			7453	2.00		74126	0.57	0.46	74193	1.42	74399	1.40	6884	1.60	5mm YL	15p		
TC9490E	1.80	KB4433	1.52	ICM7555	0.94	4066	0.57																		
TD102B	1.11	KB4434	1.95	CRYSTALS		4067	0.57																		
TD1029	2.11	KB4437	1.75	CRYSTALS		4068	0.57																		
TD1054	1.45	KB4438	2.22	32.768KHz	2.70	10.245	2.00	RC XTALS																	
TD1062	1.95	KB4441	1.35	100KHz	3.85	10.6985	2.50	AM TX/RX																	
TD1072	2.69	KB4445	1.29	45KHz	5.00	10.700	2.00	FM RX																	
TD1074A	2.44	KB4446	2.70	1.000MHz	2.95	10.7015	2.50	3rd ot/30pF																	
TD1083	1.95	KB4448	1.65	3.2768	2.70	11.00	2.00	HC25U	1.65																
TD1090	3.05	NE5044N	2.26	4.000	2.00	11.115	2.00	FMTC: Fund																	
HA1137	1.20	NE5532N	1.85	4.1934	2.00	11.520	2.00	20pF HC25U																	
HA1196	2.20	PE6000	3.55	2.00	2.00	8.9995	2.00	% freq	1.85																
HA1197	1.00	SL627E	2.00	4.032	2.00	9.0015	2.00	PAIRS...AM 3.10																	
LD1220	1.40	SL6310	2.03	4.433619	2.00	21.000	2.00	PAIRS...FM 3.25																	
LM1303	0.99	SL6600	3.75	4.800	2.00	24.000	2.00	CHANNEL LING:																	
LM1307	1.55	SL6640	2.75	5.000	2.00	25.000	2.00	27MHz; 50KHz																	
MC1330	1.90	SL6690	3.20	7.000	2.00	26.000	2.00	35MHz; 80KHz																	
MC1350	1.20	SL6700	2.35	7.68	2.00	18.000	2.50	XTAL FILTERS																	
HA1370	1.90	ICL8038CC	4.50	8.000	2.00	10M4B1: 10.7MHz, 15KHz BW,																			
HA1388	2.75	MSL9362	1.75	10.000	2.00	8 pole,																			
TD1490	1.86	MSL9363	1.75	10.000																					

# From the World-Record Joystick People! A REVOLUTIONARY ANTENNA THEY CALLED "IMPOSSIBLE"

## THE JOYFRAME (Patent Applied for) TVI-PROOF Amateur Bands 3.5-30MHz., incl. "new" bands and 27MHz. (where legal), SW BC reception. PLUS!! STOP PRESS NEWS!! TWO WAY OPERATION SOAK TEST ON 2 METRES SUCCESSFUL!!

The small package antenna for the poor QTH, that measures 21x21x21 (inches) and just stands on top of the gear in shack! Directive on 80, acts as vertical on higher freqs., many BC stns. G2VF with 30 watts has enjoyed world-wide QSO's. Incredible low angle radiation! Rotated by hand, two knob tuning. TRANSMISSION, particularly with respect to size and freq. range, by SUCH A SMALL UNIT, has - we believe - been generally thought IMPOSSIBLE. It has taken Partridge expertise, that product the JOYSTICK, etc., to prove otherwise and to bring you another efficient, compact, substantially harmonic-free complement to your hobby.

**COMPLETE JOYFRAME (incl. ATU) £60.00**  
(or write - 14p - or phone for literature)

**2 METRE STOP PRESS.** During recent opening, FM QSO's Western Europe and Western G proved JOYFRAME as super vertical for this band, INDOOR OPERATION!

## ANTENNAS (our regular lines)

**THE JOYSTICK VFA (Variable Freq. Antenna)**  
Only 230cm long, easily assembled and installed. Continuous tuning 0.5-30MHz. Omni-directional. Substantially harmonic-FREE  
**SYSTEM "A" For the SWL or 160m. Tx. £48.55**

One small antenna for 2m. band, 80/40/20/10m., + 3 "NEW" bands, 27 Mhz. CB Band (where legal). 500 w capability, no TVI creating harmonics. SWL's - SHORT WAVE BROADCAST BANDS AT THEIR BEST!

All this from the NEW PARTRIDGE

**SUPERMATCH SYSTEM £82.00**

Can be used from "impossible" locations, "no antenna space" locations, caravans, high rise blocks, adaptable for mobile!

The associated JOYMATCH

**SUPERMATCH ATU £50.00**  
converts your existing JOYSTICK VFA to a SUPERMATCH SYSTEM and will match about every other HF band antenna!

Receivers

Transceivers

# STOP PRESS!! CASH SAVING DEALS FOR YAESU GEAR

PARTRIDGE "DIAL-A-QUOTE" SERVICE

FRG/Rx's., FT/Tx's., with TVI-proof antennas if reqd., some FREE offers with Rx. deals. While you waited for this ad., PRICES HAVE FALLEN! REMEMBER it takes 2 MONTHS to get ads. updated, BUT you can PHONE US NOW for your QUOTE. SAVE TIME AS WELL AS MONEY. 0843 62535 (ext. ) or 62839 after office hours.



**G3CED  
G3VFA**

## JUST TELEPHONE YOUR CARD NUMBER

0843 62535 (ext 5) (62839 after office hours) or send 14p stamp for FREE literature. Prices correct as at press. NOTE our prices are always INCLUSIVE OF VAT. carriage. Prompt service too, goods usually despatched WITHIN 48 HOURS!

5 Partridge House,  
Prospect Road, Broadstairs, Kent CT10 1LD  
(Callers by appointment).



# AH ELECTRONICS

20 BARBY LANE, HILLMORTON,  
RUGBY, WARWICKSHIRE CV22 5QJ.  
TEL: 76473 EVE 71066.

Mail Order Only or callers by appointment.  
All prices include VAT but add 50p post & packing.

## VHF RF. POWER TRANSISTORS:-

Type	Gain (db)	Output (watts)	Volts	Freq.	Price
2N6083	5.7	30w.	12	175MHz	£6.50
BLY87A	9	12	12	175	£4.00
SD1212-6	8.2	3	12	175	£2.50
BLW16A	10	3	12	175	£0.75
PT4236A	10	1 min.	12	175	£0.75
PT4555	8	25	12	80	£3.50
PT4556C	7	40	12	80	£4.50
2N5070	13	25(pep)	24	30	£5.00

**MDA800** 8 amp 50 volt bridge rectifier OK for 12v PSU etc. **65p.** 2 for **£1.15.**  
**DUAL-GATE MOSFETS** 35K51 (40673) **80p.** BFR84 **75p.**

**FETs** E5565 (2N3819) **30p.** TIS88A **40p.** BF256C **40p.** 2N4381 **40p.**  
**BIPOLARS-** BF576, pnp VHF RF amp. FT1200 MHz **20p.** 2N4957 pnp VHF/UHF RF amp nly only 3 1/2 db = 1GHz **30p.** BF180 **30p.** BF166 VHF RF amp **25p.** BFY90 UHF RF amp **95p.** BF152 VHF mix/osc. **15p.**

**SILICON PIN DIODES** for switching oscillators etc. up to 1000MHz - BA243 (VHF) **20p.** BA244 (UHF) **25p.**

**AUDIO AMP IC.** TDA1010 6 watt output adjustable to 9 watt, = 14 volt single-line type & ideal for transceivers, receivers, record players, cassette players etc. BARGAIN OFFER ONLY **£1.35** two for **£2.40.** Supplied with data sheet showing construction of stereo amp. full data sheet (19 pages) **20p.**

**27-30 MHz RECEIVER PRE-AMP.** Have you a tired or old receiver with poor performance above 25MHz then one of our super pre-amps is what you want:- 50 ohm imp. in & out 25db gain with better than 1db nf. ready built on PCB 60mmx40mm. adjustable gain control. only **£8.00** or built into grey hammer finish die cast box with BNC sockets **£12.50.**

**10.7 MHz SSB CRYSTAL FILTERS** Cathode type BP4133 lower sideband only, new & unused small size 38mmx18mmx15mm 200 ohm imp. give away PRICE ONLY **£4.00** each two for **£7.00.**

**10.7 MHz CRYSTAL FILTER** for AM/FM 12 1/2 KHz channel spacing +3 1/2 KHz = 3db ITT type 024DE/923L. **£7.00 ea.**

**MOTOROLA CAR RADIO PCBs** complete less vol. cont. tuner etc. with circuit **80p ea.** four for **£3.00.**

**CAR RADIO** 470 KHz IF AMPS with stereo pre-amp IC. with circuit **65p.**  
**CAR RADIO/CASSETTE PLAYER** stereo amps 5 watt/chan. with multigang pot. matching amp to above IF amp board. Contains 2 TA7205P ICs, with circuit **£2.75.**

**BAG MIXED ELECTROLYTIC CAPACITORS** 2.2mf - 1000Mfd 100 **£1.60.**  
**BAG OF MIXED RESISTORS** 1/2 watt carbon film pre-formed type all with long leads plus some 1/2 watt std types 250 for **£1.60.**

**FEDTHROUGH CAPACITORS** 1000pf 500v solder in type 1/2" dia. 10 for **28p.**  
**FERRITE RINGS** 12mm dia **10p ea.** **FERRITE BEADS** FX1115 10 for **20p.**  
PRICE LIST 15p STAMP - FREE WITH ORDER.

## TV SPARE PARTS & COMPONENTS

The Practical Wireless TV Sound Tuner.  
Still unsurpassed! Parts still available. Price List, copy of original article supplied on request.  
(cost of set of parts £28.40 incl. p/p & VAT)

Callers still welcome at shop premises.

## MANOR SUPPLIES (Tel. 01-794 8751)

172 WEST END LANE, LONDON NW6.  
(near W. Hampstead Jubilee and British Rail Stations).

## MIGHTY NINETY PACKS ALL 90p Ea. Inc. VAT.

BUY SIX PACKS AND GET A SEVENTH PACK FREE!  
POSTAGE UP TO 4 PACKS 15p PER PACK. 5 PACKS OR MORE POST FREE.

MN1	300 1/2 watt pre-formed resistors.	MN31	15 assorted trimmer caps.
MN2	200 1/2 and 1/4 watt resistors.	MN32	15 30pF beehive trimmers.
MN3	100 1 and 2 watt resistors.	MN34	25 min. glass reed switch.
MN4	50 wire wound resistors.	MN40	50 polystyrene capacitors.
MN5	100 metal oxide resistors.	MN42	10 BC107 transistors.
MN6	12 assorted potentiometers.	MN43	10 BC108 transistors.
MN7	25 assorted pre-set resistors.	MN44	10 slide switches sp/co.
MN8	50 assorted electrolytic caps.	MN51	10 -2" red led.
MN9	100 assorted ceramic caps.	MN52	10 -125" red led.
MN10	100 mixed caps. poly, ceramic, elect. mica, etc.	MN53	20 0-1 mfd 25V ceramic disc.
MN13	20 assorted transistors.	MN54	20 0-0.1 mfd 25V ceramic disc.
MN14	40 1N4148 diodes.	MN58	2 x CA723 voltage reg.
MN22	8 -2" LED's with clips 4 red, 2 yellow, 2 green).	MN61	3 x TIP32 transistor.
MN23	1lb nuts, screws washers, etc.	MN62	3 x TIP31 transistor.
		MN63	30 mixed polyester caps., C280, Siemens, etc.

## CHORDGATE LTD (Dept C)

75 Faringdon Road, Swindon, Wilts.  
Tel. (0793) 33877

Retail premises at above address.

# BI-PAK NEW EXTENDED 1981 RANGE

<b>AERIALS</b> 105 Adjustable Aerial Gutter Mount <b>3.00</b> 106 C.8. Mobile Antenna <b>9.50</b> 107 FM Indoor Ribbon Aerial <b>0.50</b> 108 4 Section Car Aerial (Stainless) <b>2.16</b> 109 4 Section Car Aerial (Chrome) <b>1.80</b> 110 8 Section 1200mm Telescopic Aerial <b>2.00</b> 111 8 Section 750mm Telescopic Aerial <b>2.60</b> 112 5 Section 570mm Telescopic Aerial <b>2.64</b> 113 Roof Mounting Aerial (Car) <b>3.80</b>		<b>KNOBBS</b> 1101 Black/Silver Knob <b>0.28</b> 1102 Large Calibrated Knob <b>0.30</b> 1103 Alii PA100 Knob <b>0.46</b> 1104 Heavy Brushed Alii Knob 15mm <b>0.32</b> 1105 Heavy Brushed Alii Knob 22mm <b>0.40</b> 1106 Heavy Brushed Alii Knob 28mm <b>0.52</b> 1107 Matt Black Knob 17mm <b>0.40</b> 1108 Matt Black Knob 24mm <b>0.46</b> 1109 Matt Black Knob 28mm <b>0.56</b> 1110 All Metal Serated Edge Knob 15mm <b>0.34</b> 1111 All Metal Serated Edge Knob 24mm <b>0.48</b> 1112 All Metal Serated Edge Knob 30mm <b>0.60</b> 1113 Black Plastic Metal Skirt <b>0.24</b> 1114 Black Pointer Knob <b>0.22</b> 1115 Black/Chrome Instrument Knob 22mm <b>0.32</b> 1116 Alii Push Button Knob 11mm <b>0.12</b> 1117 Black Plastic Slider Knob <b>0.14</b> 1118 Chrome Slider Knob <b>0.20</b> 1119 Chrome/Black Slider Knob <b>0.22</b>		<b>SOLDERING EQUIPMENT</b> 1201 Soldering Iron MLX <b>5.46</b> 1202 Multicore solder 22 swg tube <b>1.00</b> 1203 Multicore solder 22 swg reel <b>3.50</b> 1204 Desolder braid <b>0.75</b> 1205 X25 Soldering Iron <b>4.20</b> 1206 X25 3/16" replacement Bit <b>0.50</b> 1207 X25 3/16" replacement Bit <b>0.50</b> 1208 X25 3/32" replacement Bit <b>0.50</b> 1209 X25 Replacement Element <b>1.80</b> 1210 Desolder Pump <b>5.56</b> 1211 Desolder Pump Nozzles <b>0.64</b> 1212 SK1 Soldering Kit <b>7.00</b> 1213 ST3 Iron Stand <b>1.60</b> 1214 Horizontal IC Desoldering Bit <b>1.95</b> 1215 Vertical IC Desoldering Bit <b>1.95</b> 1216 Antex Heat Shunt <b>0.15</b> 1217 CCN240 Soldering Iron <b>4.20</b> 1218 CCN240 3/32" Replacement Bit <b>0.50</b> 1219 CCN240 3/16" Replacement Bit <b>0.50</b> 1220 CCN240 3/16" Replacement Bit <b>0.50</b> 1221 C240 Soldering Iron <b>4.20</b> 1222 C240 3/16" Replacement Bit <b>0.50</b> 1223 C240 3/16" Replacement Bit <b>0.50</b> 1224 G Soldering Iron <b>4.20</b> 1225 Model G 3/32" Replacement Bit <b>0.50</b> 1226 Model G 3/16" Replacement Bit <b>0.50</b> 1227 Model G Replacement Element <b>1.90</b>					
<b>AUDIO LEADS</b> 114 5 pin - 3.5mm 3 & 5 connected <b>0.65</b> 115 5 pin - 3.5mm 1 & 4 connected <b>0.65</b> 116 Car Aerial Ext Lead <b>1.00</b> 117 Mains Cassette Lead <b>0.48</b> 118 2 x 2 pin Plug in Line Stereo Jack Socket <b>0.74</b> 119 Universal Car Adaptor Plug <b>1.20</b> 120 20ft. Coiled Guitar Lead <b>1.50</b> 121 5 pin to 5 pin DIN <b>0.65</b> 122 5 pin to DIN to open ends <b>0.65</b> 123 5 pin to DIN to 4 Phono Plugs <b>1.00</b> 124 5 pin Plug to 5 pin socket <b>0.72</b> 125 5 pin to 5 pin Plug (Mirror image) <b>0.75</b> 126 2 pin Plug to 2 pin Line Socket 5 mtrs <b>0.55</b> 127 2 pin Plug to 2 pin Line Socket 10 mtrs <b>0.85</b> 128 5 pin Plug to 2 Phono Plug <b>0.65</b> 129 Headphone ext lead 7 mtrs <b>1.50</b>		<b>MICROPHONES etc.</b> 1325 Crystal Desk Mike <b>3.30</b> 1326 Cassette Mike 2.4mm x 3.5mm Plugs <b>1.46</b> 1327 Dynamic Cassette Mike <b>1.86</b> 1328 Dual Imp Dynamic Mike <b>10.50</b> 1329 Dual Imp Condenser Mike <b>0.15</b> 1330 Plastic Mike Holder <b>0.66</b> 1331 Windshield Medium (Pair) <b>1.38</b> 1332 Windshield Large (Pair) <b>1.92</b> 1333 Gosenneck 320mm (Chrome) <b>2.60</b> 1334 Gosenneck 515mm (Chrome) <b>3.50</b> 1335 Mike Floor Stand <b>10.10</b> 1336 Cassette Deck Mike 5K ohm <b>5.30</b> 1337 Mike Boom Arm <b>8.80</b> 1338 Crystal Mike Insert <b>0.52</b> 1339 Two-Station Intercom <b>6.60</b> 1340 Mobile or CB Mike 600 ohms <b>5.98</b> 1341 Mobile or CB Mike 250 ohms <b>6.00</b>		<b>MAINS PLUGS AND SOCKETS</b> 1611 13 Amp Rubber Plug <b>0.52</b> 1619 13 Amp Plastic Plug <b>0.46</b> 1620 13 Amp Free Socket <b>0.50</b> 1621 13 Amp 2 way Free Socket <b>1.50</b> 1622 13 Amp 4 way Free Socket <b>4.20</b> 2019 2 Amp Terminal Block 12 way <b>0.24</b> 2020 5 Amp Terminal Block <b>0.24</b>					
<b>A.B.S. PLASTIC BOXES</b> 142 4" x 1" x 2" <b>1.08</b> 143 4" x 1.2" x 2.44" <b>1.24</b> 144 4.75" x 1.56" x 2.56" <b>1.30</b> 145 6.00" x 2.00" x 3.15" <b>1.50</b> 146 7.5" x 2.38" x 4.33" <b>2.64</b> 147 2.8" x 4.37" x 1.63" <b>1.40</b> 148 3.78" x 6.33" x 2.06" <b>1.92</b> 149 5.63" x 4.16" x 2.19" <b>2.14</b> 150 5.63" x 6.7" x 2.19" <b>2.62</b> 151 6.65" x 4.98" x 2.76" <b>3.84</b> 152 9.57" x 7.36" x 4.06" <b>5.82</b>		<b>ENAM. COPPER WIRE 2oz</b> 365 40 swg <b>1.00</b> 366 38 swg <b>0.88</b> 367 36 swg <b>0.80</b> 368 34 swg <b>0.82</b> 369 32 swg <b>0.80</b> 370 30 swg <b>0.80</b> 371 28 swg <b>0.76</b> 372 26 swg <b>0.74</b> 373 24 swg <b>0.66</b> 374 22 swg <b>0.62</b> 375 20 swg <b>0.60</b> 376 18 swg <b>0.50</b> 377 16 swg <b>0.52</b> 378 14 swg <b>0.52</b>		<b>SEMICONDUCTOR HARDWARE</b> 867 T0220 <b>0.20</b> 868 T03 <b>0.20</b> 869 SO55 <b>0.20</b> 870 T066 Insulating kits <b>0.20</b> 871 T064 in packs of 5 <b>0.20</b> 872 T048 <b>0.20</b> 873 T03 Single Heat Sink <b>0.26</b> 874 T03 Double Heat Sink <b>1.35</b> 875 Double Sided Heat Sink <b>2.65</b> 876 T05/29 Heat Sink <b>0.15</b> 877 T018 Heat Sink <b>0.15</b> 878 T01 Heat Sink <b>0.10</b> 879 T0220 Heat Sink <b>0.15</b> 880 T066 Transistor Cover <b>0.14</b> 881 T03 Transistor Cover <b>0.14</b>		<b>POTS</b> 1831 1K Lin Single Pots <b>29</b> 1832 2K2 Lin Single Pots <b>29</b> 1833 4K7 Lin Single Pots <b>29</b> 1834 10K Lin Single Pots <b>29</b> 1835 22K Lin Single Pots <b>29</b> 1836 47K Lin Single Pots <b>29</b> 1837 100K Lin Single Pots <b>29</b> 1838 220K Lin Single Pots <b>29</b> 1839 470K Lin Single Pots <b>29</b> 1840 1M Lin Single Pots <b>29</b> 1841 2M2 Lin Single Pots <b>29</b> 1842 4K7 Lin Single Pots <b>29</b> 1843 10K Log Single Pots <b>29</b> 1844 22K Log Single Pots <b>29</b> 1845 47K Log Single Pots <b>29</b> 1846 100K Log Single Pots <b>29</b> 1847 220K Log Single Pots <b>29</b> 1848 470K Log Single Pots <b>29</b> 1849 1M Log Single Pots <b>29</b> 1850 2M2 Log Single Pots <b>29</b> 1851 4K7 Lin Dual Pots <b>29</b> 1852 10K Lin Dual Pots <b>29</b> 1853 22K Lin Dual Pots <b>29</b> 1854 47K Lin Dual Pots <b>29</b> 1855 100K Lin Dual Pots <b>29</b> 1856 220K Lin Dual Pots <b>29</b> 1857 470K Lin Dual Pots <b>29</b> 1858 1M Lin Dual Pots <b>29</b> 1859 2M2 Lin Dual Pots <b>29</b> 1860 4K7 Log Dual Pots <b>29</b> 1861 10K Log Dual Pots <b>29</b> 1862 22K Log Dual Pots <b>29</b> 1863 47K Log Dual Pots <b>29</b> 1864 100K Log Dual Pots <b>29</b> 1865 220K Log Dual Pots <b>29</b> 1866 470K Log Dual Pots <b>29</b> 1867 1M Log Dual Pots <b>29</b> 1868 2M2 Log Dual Pots <b>29</b> 1869 Log Dual Pots <b>29</b> 1870 4K7 Lin switched pots <b>68</b> 1871 10K Lin switched pots <b>68</b> 1872 22K Lin switched pots <b>68</b> 1873 47K Lin switched pots <b>68</b> 1874 100K Lin switched pots <b>68</b> 1875 220K Lin switched pots <b>68</b> 1876 470K Lin switched pots <b>68</b> 1877 1M Lin switched pots <b>68</b> 1878 2M2 Lin switched pots <b>68</b> 1879 4K7 Log switched pots <b>68</b> 1880 10K Log switched pots <b>68</b> 1881 22K Log switched pots <b>68</b> 1882 47K Log switched pots <b>68</b> 1883 100K Log switched pots <b>68</b> 1884 220K Log switched pots <b>68</b> 1885 470K Log switched pots <b>68</b> 1886 1M Log switched pots <b>68</b> 1887 2M2 Log switched pots <b>68</b> 1888 100K Log Anti Log Dual Pot <b>68</b> 1889 5K Log pot 16mm switched <b>36</b> 1890 5K Log pot 17mm switched <b>48</b> 1891 10 ohm wire wound pots <b>85</b> 1892 22 ohm wire wound pots <b>85</b> 1893 47 ohm wire wound pots <b>85</b> 1894 100 ohm wire wound pots <b>85</b> 1895 220 ohm wire wound pots <b>85</b> 1896 470 ohm wire wound pots <b>85</b> 1897 1K ohm wire wound pots <b>85</b> 1898 2K ohm wire wound pots <b>85</b> 1899 4K7 ohm wire wound pots <b>85</b>		<b>MIN PRESETS 9p EACH</b> 1801 100 ohm Horizontal <b>29</b> 1802 220 ohm Horizontal <b>29</b> 1803 470 ohm Horizontal <b>29</b> 1804 1K Horizontal <b>29</b> 1805 2K2 Horizontal <b>29</b> 1806 4K7 Horizontal <b>29</b> 1807 10K Horizontal <b>29</b> 1808 22K Horizontal <b>29</b> 1809 47K Horizontal <b>29</b> 1810 100K Horizontal <b>29</b> 1811 220K Horizontal <b>29</b> 1812 470K Horizontal <b>29</b> 1813 1M Horizontal <b>29</b> 1814 2M2 Horizontal <b>29</b> 1815 4M7 Horizontal <b>29</b> 1816 100 ohm vertical <b>29</b> 1817 220 ohm vertical <b>29</b> 1818 470 ohm vertical <b>29</b> 1819 1K vertical <b>29</b> 1820 2K2 vertical <b>29</b> 1821 4K7 vertical <b>29</b> 1822 10K vertical <b>29</b> 1823 22K vertical <b>29</b> 1824 47K vertical <b>29</b> 1825 100K vertical <b>29</b> 1826 220K vertical <b>29</b> 1827 470K vertical <b>29</b> 1828 1M vertical <b>29</b> 1829 2M2 vertical <b>29</b> 1830 4M7 vertical <b>29</b>	
<b>VERO CASES</b> 152 1" x 2 1/8" x 1 1/8" Black <b>0.47</b> 153 1" x 2 1/8" x 1 1/8" White <b>0.47</b> 154 Vero 3" x 5 1/2" x 8" <b>4.82</b>		<b>TINNED COP. WIRE 4oz</b> 379 24 swg <b>0.94</b> 380 22 swg <b>0.83</b> 381 20 swg <b>0.86</b> 382 18 swg <b>0.90</b> 383 16 swg <b>0.78</b>		<b>METERS</b> 1305 2" Meter 2 Amps <b>2.88</b> 1307 2" Meter 500UA <b>2.88</b> 1308 2" Meter 100UA <b>2.88</b> 1309 2" Meter 500UA <b>2.88</b> 1310 2" Meter 1MA <b>2.88</b> 1311 2" Meter 50 Volts <b>2.88</b> 1312 SWR and FS Meter <b>9.50</b> 1313 SWR and Power Meter <b>11.90</b> 1314 VU Meter 100UA OPV <b>24.75</b> 1316 Multi Tester RE185M <b>40.00</b> 1317 Double VU Meter <b>3.25</b> 1319 100-0-100 UA Meter 45mm <b>1.90</b> 1320 Min Level Meter 23mm <b>0.95</b> 1321 VU Meter 100UA <b>1.90</b> 1322 Test Meter 1000VP <b>6.50</b> 1323 Test Meter 20,000 OPV <b>11.40</b> 1324 Test Meter 50,000 OPV <b>19.75</b>		<b>TRANSFORMERS</b> 2021 6-0-6V 100mA <b>0.90</b> 2022 9-0-9V 75mA <b>0.90</b> 2023 12-0-12V 100mA <b>1.15</b> 2024 0-6V-0-6V 280mA <b>1.60</b> 2025 0-12V-0-12V 150mA <b>1.60</b> 2026 0-6V-0-6V 1 Amp <b>2.40</b> 2027 9-0-9V 1 Amp <b>2.00</b> 2028 12-0-12V 1 Amp <b>2.50</b> 2029 15-0-15V 1 Amp <b>2.75</b> 2030 Multi tap 1 Amp <b>3.40</b> 2031 Multi tap 1 Amp <b>4.80</b> 2032 Multi tap 2 Amp <b>4.40</b> 2033 0-35V 1.7 Amp <b>4.90</b> 2034 0-55V 2 Amp <b>6.65</b> 2035 0-17V 750mA <b>2.85</b> 2037 Min audio output <b>0.25</b> 2038 min audio driver <b>0.38</b> 2039 0-20V 1 Amp <b>3.50</b> 2040 0-45-55V 1.5 Amps <b>6.45</b> 2041 0-55-65V 1.5 Amps <b>8.48</b> 2042 0-25V 2 Amp <b>4.50</b> 2043 15-0-15V 150mA <b>2.40</b>			
<b>INSTRUMENT CASES</b> 155 9" x 5 1/2" x 2" <b>1.70</b> 156 11" x 6" x 3" <b>2.63</b> 157 6" x 4 1/2" x 1 1/2" <b>1.64</b> 158 9" x 5 1/2" x 2 1/2" <b>2.20</b>		<b>HARDWARE IN PACKS OF 25</b> 839 08A 1" Bolt <b>0.70</b> 840 08A 1 1/2" Bolt <b>0.40</b> 842 28A 1" Bolt <b>0.35</b> 843 28A 1 1/2" Bolt <b>0.32</b> 844 28A 1 1/2" Bolt <b>0.30</b> 845 48A 1" Bolt <b>0.20</b> 846 48A 1 1/2" Bolt <b>0.20</b> 847 48A 1 1/2" Bolt <b>0.24</b> 848 68A 1" Bolt <b>0.18</b> 849 68A 1 1/2" Bolt <b>0.20</b> 850 68A 1 1/2" Bolt <b>0.20</b> 851 08A Solder Tags <b>0.20</b> 852 28A Solder Tags <b>0.16</b> 853 48A Solder Tags <b>0.14</b> 854 68A Solder Tags <b>0.12</b> 855 08A Full Nut <b>0.42</b> 856 28A Full Nut <b>0.26</b> 857 48A Full Nut <b>0.18</b> 858 68A Full Nut <b>0.18</b> 859 08A Washer <b>0.12</b> 860 28A Washer <b>0.09</b> 861 48A Washer <b>0.09</b> 862 68A Washer <b>0.09</b>		<b>SWITCHES</b> 1958 Min SPST Toggle Switch <b>0.70</b> 1959 Min SPDT Toggle Switch <b>0.75</b> 1960 Min DPDT Toggle Switch <b>0.80</b> 1961 Min DPDT Centre Off Switch <b>0.95</b> 1962 Push Button SPST <b>0.90</b> 1963 Push Button DPDT <b>0.98</b> 1964 Push Button DPDT <b>0.98</b> 1965 1P 12V Rotary Switch <b>0.60</b> 1966 2P 6V Rotary Switch <b>0.60</b> 1967 3P 4W Rotary Switch <b>0.60</b> 1968 4P 3W Rotary Switch <b>0.60</b> 1971 Min DPDT Slide Switch <b>0.16</b> 1974 8D Slide Switch <b>0.16</b> 1975 SPST Toggle Switch <b>0.33</b> 1976 DPDT Toggle Switch <b>0.46</b> 1977 Rotary On-Off Switch <b>0.56</b> 1978 Push to Make Switch <b>0.15</b> 1979 Push to Break Switch <b>0.19</b> 1981 SPST Rocker Switch (Black) <b>0.32</b> 1982 SPST Rocker Switch (White) <b>0.32</b> 1983 SPST Rocker Switch (Blue) <b>0.32</b> 1984 SPST Rocker Switch (Yellow) <b>0.32</b> 1985 SPST Rocker Switch (Luminous) <b>0.32</b> 1986 Sub min SPST Toggle Switch <b>0.54</b> 1987 Sub min SPDT Toggle Switch <b>0.58</b> 1988 Sub min DPDT Toggle Switch <b>0.62</b> 1989 Keyboard 24 way <b>1.50</b> 1990 Keyboard 40 way <b>1.60</b> 1991 Keyboard Switch <b>0.20</b> 1992 Push to Make Switch (metal body) <b>0.32</b>		<b>TOOLS CROC CLIPS ETC</b> 2001 Insulated croc clips (Red) <b>0.06</b> 2002 Insulated croc clips (Black) <b>0.06</b> 2003 1/2 insulated croc clips (Red) <b>0.07</b> 2004 1/2 insulated croc clips (Black) <b>0.07</b> 2005 30 Amp croc clips 100mm per pair <b>0.74</b> 2006 Test Leads <b>0.55</b> 2007 Test Lead Kit <b>1.70</b> 2008 4mm Test Lead Set <b>1.36</b> 2009 4mm Test Prods Set <b>0.52</b> 2010 Pincer Action Prod Set <b>1.40</b> 2011 Cutters <b>5.50</b> 2012 Pliers <b>3.95</b> 2013 Croc clip test set <b>1.00</b> 2014 Resistance sub box <b>4.30</b> 2015 IC Extraction Tool <b>0.64</b> 2016 Neon Mains Tester/Screwdriver <b>0.52</b>			
<b>ALUM BOXES</b> 159 5 1/2" x 4 1/2" x 1 1/2" <b>0.83</b> 160 6" x 4 1/2" x 1 1/2" <b>0.83</b> 161 4" x 2 1/2" x 1 1/2" <b>0.83</b> 162 5 1/2" x 4 1/2" x 1 1/2" <b>0.93</b> 163 4" x 2 1/2" x 2" <b>0.83</b> 164 3" x 2 1/2" x 1 1/2" <b>0.57</b> 165 7" x 5" x 2 1/2" <b>1.30</b> 166 6" x 4" x 1 1/2" <b>1.68</b> 167 6" x 4" x 2" <b>1.12</b> 168 Sloping Box - Large <b>6.97</b> 169 Sloping Box - Small <b>4.63</b>		<b>FUSES:</b> <b>Quick Blow 20mm:</b> 611 150mA <b>0.06</b> 612 250mA <b>0.06</b> 613 500mA <b>0.06</b> 614 800mA <b>0.07</b> 615 1 Amp <b>0.06</b> 616 1.5 Amp <b>0.07</b> 617 2.0 Amp <b>0.06</b> 618 2.5 Amp <b>0.06</b> 619 3.0 Amp <b>0.06</b> 620 3.15 Amp <b>0.07</b> 621 5.0 Amp <b>0.06</b> <b>Semi Delay: 20mm</b> 622 100MA <b>0.07</b> 623 250MA <b>0.07</b> 624 500MA <b>0.07</b> 625 1 Amp <b>0.07</b> 626 1.6 Amp <b>0.07</b> 627 2 Amp <b>0.07</b> 628 2.5 Amp <b>0.07</b> 629 3.15 Amp <b>0.07</b> 630 5.0 Amp <b>0.07</b> <b>Quick Blow: 1 1/4":</b> 631 250MA <b>0.06</b> 632 500MA <b>0.06</b> 633 800MA <b>0.06</b> 634 1 Amp <b>0.06</b> 635 1.5 Amp <b>0.06</b> 636 2 Amp <b>0.06</b> 637 2.5 Amp <b>0.06</b> 638 3 Amp <b>0.06</b> 639 4 Amp <b>0.06</b> 640 5 Amp <b>0.06</b> 641 6 Amp <b>0.06</b> 642 8 Amp <b>0.06</b>		<b>CABLE</b> 390 Light Mic Cable <b>per metre</b> 391 Twin Mic Cable <b>0.10</b> 392 Fig 8 Stereo Cable <b>0.12</b> 393 4 Way SCR Cable <b>0.35</b> 394 4 Way Ind. Screened Cable <b>0.18</b> 395 Heavy Mic Cable <b>0.25</b> 396 3 Amp 3 Core Mains Cable <b>0.16</b> 397 Twin Oval Mains <b>0.10</b> 398 Fig 8 Speaker Cable <b>0.07</b> 399 Low Loss Coax. 75 ohms <b>0.20</b> 400 Uniradio 76-50ohms coax. <b>0.64</b>					
<b>BATTERY HOLDERS</b> 200 Batt Holder 2 x HP7 short <b>0.18</b> 201 Batt Holder 4 x HP7 short <b>0.19</b> 202 Batt Holder 6 x HP7 short <b>0.20</b> 203 Batt Holder 4 x HP7 long <b>0.19</b> 204 PP3 Battery Clips <b>0.12</b> 205 PP9 Battery Clips <b>0.12</b> 206 Batt Holder 4 x HP11 long <b>0.25</b> 207 Batt Holder 4 x HP11 short <b>0.25</b> 208 Batt Holder 4 x HP2 long <b>0.30</b>		<b>ETCHANT AND PENS</b> 1610 Dalo Etch Resist Pen <b>0.90</b> 1611 Ferric Chloride 1lb pack <b>0.95</b> 1612 Pentel Etch Resist Pen <b>0.65</b>		<b>2017 PICK UP FOR ACOUSTIC GUITAR £5.50</b> <b>2018 TELEPHONE PICK UP COIL £0.66</b>					

Send your orders to Dept PW5 BI-PAK PO BOX 6 WARE HERTS. SHOP AT 3 BALDOCK ST. WARE HERTS. TERMS: CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED, TEL. (0920) 3182. GPO 388 7006 ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



### SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high  $\times$  6" wide  $\times$  7 1/2" deep. AC 200/250V. PRICE **£18-40**, P. & P. £2-50.

### HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 30 watts music power. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12 1/2" wide  $\times$  5 1/2" high  $\times$  7 1/2" deep. Special price **£29-00** + £3-25 carriage and packing.

### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2"  $\times$  14 1/2"  $\times$  1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only **£9-20** each + p. & p. (one £11-40, two £11-80).

A brand new 22 transistor hi-fi stereo amplifier of superior design made by a well-known British manufacturer, for a now cancelled contract order. The unit is supplied new & tested on a printed circuit panel size approx. 6 1/2"  $\times$  4 1/2"  $\times$  1 1/2" h. using high grade discrete components. Brief specification: 15 watts r.m.s. per channel O/P into 8 ohms. (o/p stages fully protected against s/c) I/P 60mV, for ceramic cartridge. Provision for tape v/p & o/p. Only requires the addition of a 40 volt  $\pm$  2 amp. power supply & the bass, treble, balance & vol. control. (standard types). FULL Circuit diagram & connection details supplied. Price with edge connectors. Only **£9-00** + 80p p. & p.

**IF ORDERED WITH AMPLIFIER:** \*2 stage pre-amp. for mag. cart. RIAA corrected **£2-50**. Mains transformer, rectifier, smoothing condenser **£4-00** + **£2-50** p. & p. Set of 4 pots. **£2-50** (while stocks last).

### MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp

Indicator. Built in Pre-sets with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV r.m.s. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2"  $\times$  4"  $\times$  9 1/2" approx. **LIMITED NUMBER ONLY at £29-00 + £2-60 P. & P.**
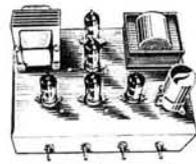
### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 50p + SAE (Free with parts). **All parts sold separately. ONLY £18-40**, P. & P. £3-20. Also available ready built and tested **£22-50**, P. & P. £3-20.



### STEREO DECODER MK.II

SIZE 1 1/2"  $\times$  2 1/2"  $\times$  1 1/2" ready built. Pre-aligned and tested for 10-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions supplied **£7-00** plus 30p P. & P. Stereo beacon light if required **40c** extra.

Mullard LP1159 RF IF module 470kHz **£2-50** + P. & P. 50p. Full specification and connection details supplied. Pye VHF FM Tuner Head covering 88-108MHz 10-7 MHz I.F. output. 7.8V + earth. Supplied pre-aligned, with full circuit diagram with precision geared F.M. gang and 323PF A.M. Tuning gang only **£3-40** + P. & P. 60p.

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ.  $\pm$  1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2"  $\times$  2 1/2"  $\times$  1 1/2" H. **£3-20** + 30p P. & P.

### HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response:  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 80mV into 1  $\Omega$   $\Omega$ ; Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35V. at 1-0 amp.

Overall Size 12" w.  $\times$  8" d.  $\times$  2 1/2" h. Fully detailed 8 page construction manual and parts list free with kit or send 50p plus large S.A.E. **AMPLIFIER KIT £14-95 P. & P. £1-20** (Magnetic input components 33p extra) **POWER PACK KIT £6-20 P. & P. £2-00** **CABINET £6-20 P. & P. £2-00**

**SPECIAL OFFER—only £25-80 if all 3 items ordered at one time plus £2-80 P. & P.** Full after sales service **Also avail. ready built and tested £32-20**, P. & P. **£2-80.**


### HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls. 2 pin din speaker sockets & 5 pin din tape rec. play socket are mounted on the printed circuit panel, size approx. 9 1/2"  $\times$  2 1/2"  $\times$  1 1/2" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only **£10-40** plus 90p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at **£2-15** + 70p P. & P. if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

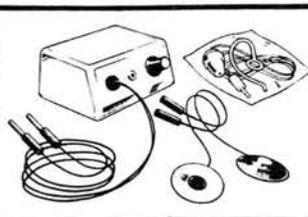**HARVERSON SURPLUS CO. LTD.** (Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985  
Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.



### BIO FEEDBACK

A high sensitivity GSR monitor for development of your inner potential and powers. Kit contains ALL you will need, including ready drilled case, to build and experiment with the monitor. Accessories include skin electrodes, conductive jelly, earpiece, and full instructions for assembly and use.

Kit **£9.80** Built and tested **£12.13**  
Details supplied FREE — just send S.A.E.

**TRANSISTORS**  
C1L108 (plastic BC108), BC171A, BC320, BF393, 2N5447, 2N5449, all at 9p each, 10 for 70p, 100 for £5.80.



### OPTO SWITCH

Type OPB814. Consists of an infra-red source and sensor in a slotted mounting allowing the beam to be broken by any solid object in the 3 x 8mm slot. Useful for limit switching, end of tape detection, and even contactless electronic ignition.

R.S. Components trade price £2.25 each. OUR PRICE 85p each! 10 for £7.20



### ZETTLER LOW PROFILE RELAY

Type AZ535-08-1. Only 11mm deep, allowing PCB's to fit in confined spaces. Coil resistance 440R, operating voltage 17.5V to 28V (24V nominal). Contacts: SPc/o silver with gold flash. Rated 110V D.C. 125V A.C. Max. current 3A. A high quality professional relay at a ridiculously low price: 48p each, 10 for £3.60.



### TRANSFORMER

240V primary, tapped for 115V. Secondary 12-0-12, rated 4VA. Connections by spalls for PCB mounting, wire wrap, or normal soldered connections. 95p each, 10 for £7.40



### OPERATIONAL AMPLIFIER

Op. amp. type 709. A general purpose device in a 14-pin DIL package. Applications similar to 741, but external frequency compensation allows operation at higher frequencies too. 18p each, 10 for £1.50.

### MIXED COMPONENT PACKS CAPACITORS

Assorted types and values, polyester, polystyrene, ceramic, electrolytics, etc. A fine selection of useful components. 100 for £1.00 500 for £3.20.

**RESISTORS**  
Carbon film, composition, oxide, etc. Mainly 5% E24 series, 1/4 and 1/2 Watt, but some precision 1% and 2% generally included, also a few 1 Watt and above. A wide range for all purposes. 250 for £1.20 1,000 for £3.60.

**ELECTROLYTICS**  
Radial, axial and PCB types, values from 1mF to 1000mF. Not to be missed! 100 for £2.60 500 for £10.80.

Bargain lists of quality components FREE Send S.A.E. for your copy today!  
Postage free above £10.00, please add 60p below this amount. 15% VAT should be added to your order total.  
ACCESS orders accepted: write or phone Dean (0594) 41267.

**Wye Valley Electronics**  
15 HIGH STREET, LYDNEY, GLOUCESTERSHIRE GL15 5DP

### SPECIAL OFFER SURPLUS STOCK TO CLEAR. BULK PURCHASE

QTY	PENCE	QTY	PENCE	QTY	PENCE	QTY	PENCE
8	2114	2	AU110	250	5	BU208	450
8	4116	2	AU113	250	5	C106D	130
1	2708	10	BC107	80	5	DL707	300
1	2716	10	BC108	80	5	DL747	600
1	2114	10	BC109	80	5	LM380	325
114	4116	5	BCY34	200	5	LM381	500
10	7805	10	BD131	250	50	NE555	900
10	7812	10	BD132	250	5	OC29	350
10	7815	10	BD135	210	10	OC35	800
10	7818	10	BD136	210	5	R2540	550
10	7824	10	BD137	210	3	TBA520	300
10	7905	10	BD138	210	5	TBA530	300
10	AC126	160	BD139	210	3	TBA540	300
10	AC127	160	BD140	210	3	TBA550	300
10	AC128	160	BF180	180	3	TBA560	300
10	AC187	160	BF258	180	3	TBA800	150
10	AC188	160	BFY50	140	3	TBA920	315
5	AD149	250	BT108	315	5	TIP29	100
10	AD161	230	BT110	325	5	TIP30	100
10	AD162	230	BU105	400	5	TIP32	100
2	AU103	250	BU205	400	5	TIP41	120

Callers by appointment only.

Please add 30p. P&P and VAT at 15%. Govt. Colleges, etc orders accepted.

Quotations given for Large Quantities.

### SUNMIT ELECTRONICS LTD.

96 PEEL ROAD, WEMBLEY, MIDDLESEX, ENGLAND. TEL. 01-908 1928

### PROGRESSIVE RADIO

ALL ORDERS DESPATCHED BY RETURN POST

**SEMICONDUCTORS.** 2N5062 (100V 800mA) SCR 18p. BX504 opto isolator 25p. CA3130 95p. TDA2611A £1.70p. Tag4443 SCR 45p. Texas 10138 power trans. 50p. TDA1151 25p.  
**SWITCHES.** Min. toggles, SPST 8x5 7m 42p. DPDT 8x7 7m 55p. DPDT c/off 12x11x9mm 77p. HEAVY DUTY-DPDT 240VAC 10 Amp 35p. PUSH TYPE, push on 16x6mm 15p, push to break version 17p. MERCURY (TILT) Switch, 1"  $\times$  1 1/2" 35p.  
**ANTEX SOLDERING IRONS:** Models C15, CX17 and X25 all **£3.95** each. NSA1198 8 1/2 digit multiplexed displays, com. cath. with data sheet **£1.45p**. **SPECIAL OFFER** TIL209 Red LED's 10 for 75p. 0.2" LEDs, red, yellow, green 10p each.

**LINEAR I.C.'s.** LM300 40p, LM301 55p, LM308 £1.30, LM324 £1.00, LM388 95p, LM358 50p, LM386 90p, LM390 80p, LM3909 75p, CA1310 £1.70, CA3018 £1.00, CA3028 £1.30, CA3035 £2.20, CA3046 85p, CA3098 95p, CA3130 95p, CA3140 37p, MC1303 £1.40, MC1312 £1.60, MC1330 £1.40, MC1458 40p, NE550 £1.00, NE544 £1.40, NE565 £1.70, NE566 £1.70, TAA550 40p, TAA621 £2.20, NE556 50p, C106D SCR 35p.  
**JACKSONS C804** 50p var. capacitors 50p each.  
**STABILISED POWER SUPPLY,** 240 vac input 13.8 volts at 3/5 Amps DC output. **£14.75p**.  
**JUMPER TEST LEAD SETS.** 10 pairs of leads with insulated crocs each end **90p**.  
**40KHZ TRANSDUCERS,** RX/TX £3.50 pair.  
**STC BREAK GLASS FIRE ALARM UNITS,** new with mounting box **£1.50p**.  
**MINIATURE SOLID STATE BUZZERS,** 2 voltages available, 6 or 12VDC 75p each, Loud 12 volt buzzers 85p.  
Cash with order please, official orders welcome from schools etc., please add 30p postage and packing, VAT inclusive. SAE for latest illustrated stock list.

**31, CHEAPSIDE, LIVERPOOL L2 2DY**

# LISTEN TO THE WORLD

WITH A  
RECEIVER  
FROM

**Catronics**

Best Selection  
LOWEST  
PRICES

## MEDIUM WAVE/SHORT WAVE

**Trio R-1000** is a high class general coverage receiver covering 30 bands between 200kHz and 30MHz with a PLL synthesiser. Both digital display readout (1kHz resolution) and analog display (10kHz) resolution are provided for easy and accurate tuning. The R-1000 also includes a quartz digital clock with timer, three IF filters, RF ATT and tone control, etc. to ensure the best receiving conditions for each mode. 240V AC, 12V DC supply. **£285**

## AIRBAND (VHF)

**Signal R517** portable, fully tuneable 118 to 143MHz with provision for 3 crystals (extra) 1.8µV Sensitivity, Fine Tuning control, Telescopic aerial. **£49**

**Lowe AP12** portable 12 crystal controlled channels, rechargeable batteries & charger included. Micro-computer tuning. 0.5µV sensitivity **£89** + crystals **£2.80 ea.**

**Signal R512** - automatically scans up to 8 crystal controlled channels, lock-out facility. 240VAC/12VDC supply. Incl. 8 chs. **£146.50**

**Regency Digital Flight Scan** - fully synthesised to search 108 to 136MHz + 16 selectable scan channels + 2 priority channels. 240VAC/12VDC supply. **£215**

## MARINE/AMATEUR (VHF)

**Search SR9** - fully tuneable coverage + provision for 11 crystals. Fine tuning and Squelch controls. 12VDC supply. **£46**

**Lowe FS10** portable, 10 crystal controlled channels automatically scanned. Rechargeable batteries & charger included. Telescopic aerial. **£82** + crystals **£2.80 ea.**

**Belcom AMR217B** - automatically scans up to 7 crystal controlled channels with provision for 10 additional fixed channels. 240VAC/12VDC supply. Incl. 8 channels. **£120**

**Regency K100** - fully synthesised to search 30-50, 144-174, 440-512MHz + 10 selectable scan channels 240VAC/12VDC. **£180**

## SYNTHESISED SCAN - AIR/MARINE ETC

**Bearcat 220FB** - fully synthesised Scanner covering 66-88, 144-174, 420-512MHz FM plus 118-136MHz airband 240VAC/12VDC supply. **£258**

**SX200** - the ultimate fully synthesised scanner + digital clock. Covers 26-88, 108-180, 380-514MHz AM AND FM: i.e. just about everything for only **£237**

Additional crystals for above receivers: Airband & Marine, £2.80; Amateur, £2.40. All prices include VAT but add carriage: S.W. & Regency receivers, £5.50; others £1.50. **EASY TERMS available. Access and Barclaycards welcome**

**CATRONICS LTD., COMMUNICATIONS HOUSE,  
(Dept. 185) 20 WALLINGTON SQUARE,  
WALLINGTON, SURREY, SM6 8RG.**

Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat 1 p.m.) Closed lunch 12.45-1.45

# Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

## Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

## Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

**POST OR PHONE TODAY FOR FREE BOOKLET.**

**ICS To: International Correspondence Schools**

SINCE 1890  
Dept. 276G Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest .....

Name .....

Address .....

Telephone Number .....



68  
LARGER  
PAGES

The larger  
Catalogue  
that means  
FREE POSTAGE  
IN U.K.  
•  
ADDITIONAL  
DISCOUNTS  
•  
KEEN PRICES  
•  
GUARANTEED  
SATISFACTION  
•  
GOOD STOCKS  
GOOD DELIVERY  
•  
We Pay Postage

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

**ELECTROVALUE**

**FREE FOR THE ASKING**

ELECTROVALUE LTD. (PW2),  
28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB.  
Phone: 33603 (London 87) STD 0784. Telex 264475.  
NORTHERN (Personal Shoppers Only): 680 Burnage Lane, Burnage,  
Manchester M19 1NA. Phone (061) 432 4945.



# MICROWAVE MODULES LTD

## 2 METRES??

### MMT 144/28

#### 2 METRE LINEAR TRANSVERTER



- FEATURES INCLUDE:
- ★ 10 WATTS RF OUTPUT
  - ★ HIGHLY SENSITIVE RECEIVE CONVERTER
  - ★ LINEAR ALL-MODE OPERATION
  - ★ RF VOX CHANGEOVER

This 10 watt linear transverter will allow 28MHz transceivers to be used at 144MHz. It is a complete device and requires only a 12 volt DC supply (2.5 amps) and a suitable 2 metre aerial to enable full operation. It covers 144-146MHz, corresponding to 28-30MHz input, from the drive source, and will accept all modes of operation.

£99.00 inc VAT (p&p £2.00)

### MMA 144V

#### 2 METRE ULTRA LOW-NOISE RF SWITCHED PREAMPLIFIER




- Power gain: 15dB  
Overall noise figure: Better than 1-3dB  
RF connectors: 50ohm BNC  
Power requirements: 12-5 volts at 75mA

This highly versatile module will improve the receive performance of any existing 2 metre equipment. It may be left in the aerial lead at all times, and has a through power capability of 100 watts. Also, should the DC supply fail to the unit, a straight through connection is made, so making the unit fail-safe.

£34.90 inc VAT (p&p £0.80)

### MMC 144/28

#### 2 METRE MOSFET CONVERTER

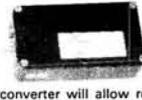

- Gain: 30dB  
Noise figure: Better than 2-5dB  
Power requirements: 12-5 volts at 50mA

This converter will allow reception of the popular 2 metre band, on any good HF receiver which covers 28-30MHz (eg. TRIO R1000, YAESU FRG7, FRG700 etc). By connecting it to the aerial socket of the receiver, and by connecting a suitable 2 metre aerial to the input of the converter, reception of the full 2 metre band is possible by tuning 28-30MHz.

£27.90 inc VAT (p&p £0.80)

### QUALITY PRODUCTS BRITISH MADE BY MICROWAVE MODULES

### MML 144/25

#### 2 METRE 25 WATT LINEAR AMPLIFIER AND RECEIVE PREAMPLIFIER



- FEATURES INCLUDE:
- ★ LINEAR ALL-MODE OPERATION
  - ★ RF VOX CHANGEOVER
  - ★ LOW NOISE RECEIVE PREAMPLIFIER
  - ★ SUPPLIED WITH ALL CONNECTORS

This device is intended to provide mobile or fixed station performance from any of the popular hand-portable 2 metre transceivers (eg. TR2300, TR2400, IC2E, IC202 etc). When used in conjunction with such equipment, this amplifier will produce: 25 watts output for 3 watts input  
10 watts output for 1 watt input.

The inclusion of a low noise receive preamplifier will also improve reception.

£59.00 inc VAT (p&p £2.00)

### MML 144/40

#### 2 METRE 40 WATT LINEAR AMPLIFIER AND RECEIVE PREAMPLIFIER



- FEATURES INCLUDE:
- ★ LINEAR, ALL-MODE OPERATION
  - ★ 40 WATTS OUT FOR 10 WATTS IN
  - ★ RF VOX CHANGEOVER
  - ★ LOW NOISE RECEIVE PREAMPLIFIER
  - ★ SUPPLIED WITH ALL CONNECTORS

This unit is compatible with any 10 watt transceiver (or less) and will provide 40 watts output. It is suitable for mobile/portable and base station use and is suitable for all modes of operation. The inclusion of a low noise preamp will generally improve reception.

£77.00 inc VAT (p&p £2.00)

### MML 144/100

#### 2 METRE 100 WATT LINEAR AMPLIFIER



- FEATURES INCLUDE:
- ★ 100 WATTS RF OUTPUT
  - ★ RF VOX CHANGEOVER
  - ★ LINEAR ALL-MODE OPERATION
  - ★ SUPPLIED WITH ALL CONNECTORS

This unit will provide a 10dB increase in transmit power, from 1 watt to 12 watts. It is ideal for fixed station use, or alternatively may be used in a mobile situation.

ALSO AVAILABLE WITH LOW NOISE RECEIVE PREAMP AT NO EXTRA COST - MML 144/100P  
N.B. This version does not have a straight through mode.

£142.60 inc VAT (p&p £3.50)

### ALL MICROWAVE MODULES PRODUCTS ARE FULLY GUARANTEED FOR 12 MONTHS (INCLUDING PA TRANSISTORS)



## MICROWAVE MODULES

BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND

Telephone: 051-523 4011 Telex: 628608 MICRO G

CALLERS ARE WELCOME, PLEASE TELEPHONE FIRST

HOURS:  
MONDAY-FRIDAY  
9-12.30, 1-4.30

WELCOME

### INTERESTED IN ELECTRONICS? TRY A ZEDPACK! COMPONENTS AT A PRICE EVERYONE CAN AFFORD

- Z1 300 mixed  $\frac{1}{2}$  and  $\frac{1}{4}$  watt resistors £1.95
- Z2 150 mixed 1 and 2 watt resistors £1.50
- Z3 300 mixed capacitors, most types £3.95
- Z4 100 mixed electrolytics £2.20
- Z5 100 mixed polystyrene caps £2.20
- Z6 300 mixed printed circuit components £1.95
- Z7 300 mixed printed circuit resistors £1.45
- Z9 100 mixed miniature ceramic and plate caps £1.20
- Z10 25 assorted pots. £1.50
- Z11 25 assorted presets, skeleton etc. £1
- Z12 20 assorted vdr's and thermistors £1.20
- Z13 1lb mixed hardware. Nuts, bolts self-tappers, sleeving, etc. £1.20
- Z14 100 mixed, new and marked, full spec. transistors. Pack includes:- BC148, BF154, BF274, BC212L, BC238, BC183L, PBC108 and, or lots of similar types. £4.95
- Z15 100 mixed diodes including:- zener, power, bridge, signal, germanium, silicon etc. All full spec. £4.95
- Z18 20 assorted zeners, 1 watt and 400mw £1.50
- Z20 10 assorted zeners. Slide, push-button, multibank, miniature, read etc. £1.20
- Delux FIBREGLASS printed circuit etching kits. Includes 100 sq. ins. of copperclad F/G board, 1lb ferric chloride, (made for U.S. Army to MIL. SPEC.), 1 dalo etch resist pen, abrasive cleaner, tweezers, etch resist dish and instructions. OUR PRICE £5.95 1lb of FeCl. £2.25
- 150 sq. ins. single sided board. £2.20
- 150 sq. ins. double sided board. £3.30
- UHF, Transistors T.V. TUNER with slow motion drive, AE.skt. and leads. £1.95
- 100 Miniature read switches. £2.30

#### MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4.5V-0-4.5V at 250MA.  $1\frac{1}{2}'' \times 1\frac{1}{2}''$ , all sorts of uses. ONLY £1.3 for £2.50

PP3 Battery Connectors 10 for 50p

To: "GEMINI ELECTRONIC COMPONENTS" DEPT PW  
"THE WAREHOUSE" SPEEDWELL ST. LONDON S.E.8.  
Please Quote ZED Code Where shown. Send Cheque or Postal Order. Add 60p P&P + 15% VAT.  
\*Schools etc. SEND OFFICIAL ORDER  
ZED PACKS now available for Callers at 50 Deptford Broadway, London, S.E.8.

- Miniature Press to Make Switches, Red knob. 3 for 50p
- Subminiature S.P.C.O. Slide Switches. 6 for 50p.
- Miniature D.P.C.O. Slide Switches. 6 for 50p.
- Standard 2P, 3 Position Slide Switch. 4 for 50p.
- 4 x HP11 Battery Holders (2 x 2 Flat type) with leads. 2 for 50p.
- Assorted Fuse Holders including 20mm, P.C. Panel and chassis types. Pack of 7 for 50p.
- 3.5mm Jack Sockets, switched. Enclosed type. P.C. or panel mounting. With nuts and washers. 4 for 50p.

#### R.C. SUPPRESSORS

250V.  $1'' \times \frac{1}{2}'' \times \frac{1}{4}''$ . Ideal for fluorescent light suppression, car, and relays. Also for snubber networks. 3 for £1

**ALTERNATOR RECTIFIERS**  
Make lovely 60 amp 150V bridges. Ideal for High Power Battery Chargers. Type 4AFI. Set of 4 (2 neg. case - 2 pos. case) £2.

**Special Purchase enables us to offer Mullard C280 Polyester Capacitors** (Aquorice Allsorts) at the unbeatable price of £2 for 100 mixed. These consist of factory clearance lots i.e. spillages, floor sweepings, cosmetic rejects etc. Also Mullard miniature electrolytics 200 mixed £2.

#### TELESCOPIC AERIALS

Chrome on brass. 9 section 25" extended. Plugs into any 3.5mm jack socket. Ideal for S.W.R., metre, portable TV, etc. ONLY £1

**5 ASSORTED VIDEO GAME BOARDS**, new but bits missing. Contain 100's of useful components. CMOS, IC's, Caps, Transistors, sockets, switches etc. ONLY £3.50.

**Professional quality TV Plugs** (coax.) Diecast alloy body, Silver Plated solid brass centre pin, brass grub screw fixing for centre conductor. 50p ea, 5 for £2. Ideal for video's.

#### UHF MODULATORS

Calibrated to Channel 36 625 line UHF. Housed in metal box,  $2\frac{1}{2}'' \times 2'' \times \frac{1}{2}''$ . Complete with 9 feet of coax lead and TV plug. 9V operation, ideal for video games, computers etc. £2.50 ea with connection Data.

Vernitron FM4 10.7MHz ceramic filters 50p ea, 3 for £1.

### THE VALVE AND TUBE SPECIALIST VALVES AT NEW LOW PRICES RECEIVING, SQ. TRANSMITTING, DISPLAY, GAS FILLED, ETC.

Type No.	Price ea.						
BK448	95.65	EF37A	4.43	M8137	1.20	QY4-250	72.00
BT58	33.15	EF39	2.10	M8162	4.00	QZ06-20	24.10
D77	0.80	EF80	0.80	M8163	2.65	RG1-240A	16.00
DF61	0.56	EF85	0.91	M8212	0.85	TY2-125	61.80
DM160	3.20	EF86	0.80	ME1400	3.50	TY4-400	62.27
YV86/B7	0.64	EF89	0.72	OA2	2.10	XG1-2500	59.60
E55L	15.00	EF91	1.85	OB2	2.55	504G	1.95
E90CC	5.65	EF92	2.20	EN92	3.10	5V4G	1.35
E90CF	11.02	EF93	0.60	PC86	0.83	6AK6	2.40
E90F	6.32	EF95	4.88	PC87	0.83	6AQ6	1.30
E82CC	1.85	EF183	1.60	PC88	0.83	6AU6	0.95
E83CC	3.50	EF184	0.75	PC97	1.40	6BH6	1.20
E83F	2.10	EH90	0.86	PC900	0.58	6BQ7A	1.85
E86C	6.20	EK90	0.90	PC85	1.10	6BR7	6.00
E88C	5.84	EL34	1.64	PCC89	1.50	6B85	4.00
E88CC	4.00	EL36	0.82	PC189	1.75	7BW6	5.30
E92CC	1.65	E37	5.20	PCF80	0.87	6BW7	1.45
E99F	4.00	EL81	1.48	PCF86	1.58	6C4	1.30
E130L	16.30	EL84	0.96	PCF200	2.15	6L6GT	1.60
E180CC	4.65	EL86	1.66	PCF801	0.95	65A4	1.25
E180F	5.45	E90	1.25	PCF802	0.81	6S7JG	1.10
E182CC	8.00	E91	5.85	PCF805	1.40	6SN7GT	2.68
E186F	5.50	E95	1.28	PCF808	1.40	6SN7GT	0.90
E288CC	7.40	E360	6.20	PCZ200	1.10	6V6GT	0.95
E810F	14.47	EN91	2.56	PCL82	0.74	6X5GT	0.95
EAF801	3.15	EN92	3.18	PCL84	0.83	12AL5	1.85
EBC81	0.85	EY51	1.66	PCL85	0.85	12AU6	1.85
EB91	0.95	EY84	8.08	PCL86	0.85	12BH7	0.95
EC91	1.82	EY86	0.64	PD500	3.90	12SN7GT	2.00
EC92	0.94	EY88	1.25	PLF200	1.40	12X4	10.00
ECC81	0.78	EY500A	1.65	PL32	1.15	29C1	1.20
ECC82	0.60	EY802	0.96	PL81	0.80	30FL2/1	1.20
ECC83	0.78	E280	0.58	PL84	0.75	30PL14	1.95
ECC84	1.19	E281	0.75	PL95	1.10	90C1	2.80
ECC85	0.82	E290	1.30	PL504	1.58	90CG	13.68
ECC88	1.20	GXU1	15.00	PL508	1.85	90CV	9.00
ECC91	2.10	GZ32	1.45	PL509	2.75	92AG	7.96
ECC2000	4.50	GZ33	1.55	PL802	2.90		
ECF80	0.80	GZ34	1.45	PY88	0.78		
ECF82	0.80	KT61	5.10	PY800A	1.55		
ECF81	0.75	KT66	4.25	PY800	1.20		
ECL80	0.95	KT88	7.15	PY81/801	0.88		
ECL82	0.63	M8079	10.69	QV06-20	11.50		
ECL85	0.82	M8081	4.40	QV06-20	22.75		
ECL86	0.94	M8082	2.14	QV06-40A	21.85		
		M8190	3.50	QV02-6	12.04		
		M8136	0.85				


CASH WITH ORDER  
Carriage 50p. VAT 15%.

Account facilities available for established customers. Quotations given for large quantities.

**INTEL ELECTRONIC COMPONENTS LTD.**  
30/50 Ossory Road, London SE1 5AN. Tel: 237 0404
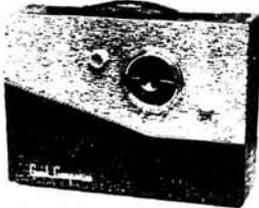
### PORTABLE RADIO CASE

Size: 11 x 8 x 3 1/2 ins approx. Made from plywood, pleasingly covered. Suitable for any normal radio circuit. Has studs for mounting 5" speaker and the front is drilled to take a tuning condenser in the centre and normal controls either side. £2.30 + £1.50 post.



### LAST MONTH'S SNIP — STILL AVAILABLE

And it still carries a free gift of a desoldering pump, which we are currently selling at £6.35p. The snip is perhaps the most useful breakdown parcel we have ever offered. It is a parcel of 50 nearly all different computer panels containing parts which must have cost at least £500. On these boards you will find over 300 IC's. Over 300 diodes, over 200 transistors and several thousand other parts, resistors, condensers, multi-turn pots, rectifiers, SCR, etc. etc. If you act promptly, you can have this parcel for only £8.50, which when you deduct the value of the desoldering pump, works out to just a little over 4p per panel. Surely this is a bargain you should not miss! When ordering please add £2.50 post and £1.27 VAT.



**MAINS MOTORS** Precision made as used in record players, blow heaters, etc. Speed usually 1,400. All have ample spindle length for coupling fan blade, pulley, etc. Power depends on stack size. 5/8" stack £2.00; 3/4" stack £2.50; 7/8" stack £3.00; 1" stack £3.50; 1 1/4" stack £4.50. Add 25% to motor cost to cover postage, and then add 15% VAT.

### YOUR LAST CHANCE FOR THIS BARGAIN

100 twist drills, regular tool shop price over £50, yours for only £11.50. With these you will be able to drill metal, wood, plastic, etc. from the tiniest holes in P.C.B. right up to about 3/8". Don't miss this snip — send your order today.

### MAGNETIC LATCH

Low voltage (4 - 8 volt AC/DC operation). Only £1.50 each.



### PUNCHED TAPE EQUIPMENT

For controlling machine tools, etc., motorised 8 bit punch with matching tape reader. Ex-computers, believed ingood working order, any not so would be exchanged. £17.50/pair. Post £3.00.

### STEREO HEADPHONES

Japanese made so very good quality. 8 ohm impedance, padded, terminating with standard 3/4" jack- plug. £2.99 Post 60p.



### BRIDGE RECTIFIER

1 amp 400v 30p each. 10 for £2.50, 100 for £20.00



### SOLENOID WITH PLUNGER

Mains operated £1.99 10 - 12 volts DC operated £1.50.

### MOTORISED DISCO SWITCH

With 10 amp changeover switches. Multi-adjustable switches all rated at 10 amps, this would provide a magnificent display. For mains operated 8 switch model £6.25, 10 switch model £6.75, 12 switch model £7.25.



### PANEL METERS

Japanese made, full vision front, size 2 1/4" x 2 1/4". 0 - 100 uA £2.85. Similar but size 2" x 1 1/4" 100 uA, scaled Vu. Ditto, but scaled 0 - 100. (note: front covers easily removable if you want to rescale these £2.30 each) Ditto but size 1 1/2" x 1 1/4", scaled Vu, sensitivity 100 uA, £1.50.

**MINI-MULTI TESTER** Deluxe pocket size precision moving coil instrument, jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0 - 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test probes and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 50p post and insurance.

**FREE** Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

### SUPER HI-FI SPEAKER CABINETS

Made for an expensive Hi-Fi outfit - will suit any decor. Resonance free cut-outs for 8" woofer and 4" tweeter. The front material is carved Dacron, which is thick and does not need to be stuck in and the completed unit is most pleasing. Colour black. Supplied in pairs, price £6.90 per pair (this is probably above the original cost of one cabinet) carriage £3.50 the pair.



### LOUDSPEAKERS

8" woofer and 4" tweeter, 4 ohms 35 watts power rating £6.90 per pair. Ditto but 8 ohms, £11.50 per pair. Post £2.00.

### ELECTRONIC VOLT-METER/ SENSITIVE RELAY


Consists of a 4 1/2" square drop through panel volt meter, 0 - 10 fed. Built into the front of the meter are two screw adjusters which move two pointers, up and down the scale, to set a minimum and maximum. A unique "under" and "over" circuit inside the meter operates one of two reed relays to bring an "under" or "over" circuit into action. The scale plate is detachable via two screws to be calibrated to your own individual requirements. The 10 transistor "under" and "over" circuit is completely separate from the meter movement so does not have to be connected to use this as a standard 0 - 1 meter. Many uses including level controls, light controls, auto battery chargers, alarm units, etc. Manufacturers list price of over £120 each. An unbelievable snip at £9.95 (less than the value of the meter alone).



## THIS MONTH'S SNIP

**VU METER** Approximately 1 5/8" square, sensitivity 0 - 500 uA suitable for use also as a recording level meter, power output indicator or many similar applications. Full vision front cover easily removable if you wish to alter the scale. Special snip price £1, or 10 for £9, post & VAT paid.

### CHASSIS BARGAIN

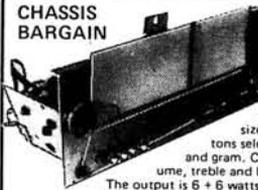

3 wave band radio with stereo amplifier. Made for incorporation in a high-class radiogram, this has a quality of output which can only be described as superb. It truly hi-fi. The chassis size is approx. 14". Push buttons select long, medium, short and gram. Controls are balance, volume, treble and bass. Mains power supply. The output is 6 + 6 watts. Brand new and in perfect working order, offered at less than value of stereo amp alone, namely £6.90. Post £2.50.

### MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy to assemble modular form this should sell at about £30 - but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16.75 including VAT and post. **FREE GIFT** - buy this month and you will receive a pair of Goodman's elliptical 8" x 5" speakers to match this amplifier.




### VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are new but without case, but we can supply plastic cases (base and cover) £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/offs per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.


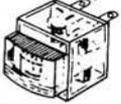
### DELAY SWITCH

Mains operated - delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps - second contact opens a few minutes after 1st contact. £1.95.



### LEVEL METER

Size approximately 3/4" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.

### ADVANCE ADVERTISING BARGAINS LIST!

Our FREE monthly list gives details of bargains arriving or just arrived - often bargains which sell out before our advertisement can appear - it's an interesting list and it's free - just send S.A.E. Below are a few of the Bargains still available.

### TRANSMITTER SURVEILLANCE (Not licencable in U.K.)

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox - all electronic parts and circuit. £2.30.

### RADIO MIKE (Not licencable in U.K.)

Ideal for discos and garden parties, allows complete freedom of movement. Plug through FM radio or tuner amp. £6.90 comp. kit.

### SAFE BLOCK

Mains quick connector will save you valuable time. Features include quick spring connectors, heavy plastic case and auto on and off switch. Complete kit. £1.95.

### LIGHT CHASER

Gives a brilliant display - a psychedelic light show for discos, parties and pop groups. These have three modes of flashing, two chase patterns and a strobe effect. Total output power 750 watts per channel. Complete kit. Price £16. Ready made up £4 extra.

### FISH BITE INDICATOR

Enables anglers to set up several lines then sit down and read a book. As soon as one has a bite the loudspeaker emits a shrill note. Kit. Price £4.90.

### 6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 mhz. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit includes case materials, six transistors, and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy if you have an amplifier to connect it to or a pair of high resistance headphones. Price £11.95.

### SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 65p. High resistance headphones (gives best results) £3.75. Kit includes chassis and front but not case.

### RADIO STETHOSCOPE

Easy to fault find - start at the aerial and work towards the speaker - when signal stops you have found the fault. Complete kit £4.95.

### INTERRUPTED BEAM

This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components - relay, photo transistor, resistors and caps etc. Circuit diagram but no case. Price £2.30

### OUR CAR STARTER AND CHARGER KIT

has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post.

### GPO HIGH GAIN AMP/SIGNAL TRACER.

In case measuring only 5 1/2in x 3 1/4in x 1 1/4in is an extremely high gain (70db) solid state amplifier designed for use as a signal tracer on GPO cables, etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4 1/2v battery and has input, output sockets and on-off volume control, mounted flush on the top. Many other uses include general purpose amp, cueing amp, etc. An absolute bargain at only £1.85. Suitable 800hm earpiece 69p.

### 3 CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit controlling over 2,000 watts of lighting. Use this at home if you wish, but it is more than rugged enough for Disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 3/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Price £14.95, complete kit and case.

### 8 POWERFUL BATTERY MOTORS

For models, Meccanos, drills, remote control planes, boats etc. £2.50.

### WATERPROOF HEATING WIRE

60 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses - around water pipes, under grow boxes in gloves and socks. 23p per metre.

### COMPONENT BOARD Ref. W0998

This is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including 4 3amp 400v types (made up in a bridge) 8 transistors type BC 107 and 2 type BFY 51 electrolytic condensers. SCR ref 2N 5062, 25 0V 100v DC and 100uf 25v DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

**FRUIT MACHINE HEART.** 4 wheels with all fruits, motorised and with solenoids for stopping the wheels with a little ingenuity you can defy your friends getting the "jackpot". £9.95. + £4 carriage.

### DESOLDERING PUMP

Ideal for removing components from computer boards as well as for service work generally. Price £6.35.

### 4-CORE FLEX CABLE

White pvc for telephone extensions, disco lights, etc. 10 metres £2, 100 metres £15. Other multicore cable in stock.

### MUGGER DETERRANT

A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

### HUMIDITY SWITCH

American made by Honeywell. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive microswitch. Very sensitive breathing on it for instance will switch it on. Micro 3 amp at 250V a.c. Only £1.15.

### EXTRACTOR FANS - Mains Voltage

Ex-Computer, made by Woods of Colchester, ideal also as blower; central heating systems, fume extraction etc. Easy fixing through panel, very powerful 2,500 rpm but quiet running. Choice of 2 sizes, 5" £5.50, 6" £6.50, post £1 per fan.



### TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs. £2.50.

# J. BULL (Electrical) Ltd.

(Dept. PW), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU.

J. BULL (Electrical) Ltd - Established 25 years. MAIL ORDER TERMS: Cash with order - please add 60p to all orders under £10, to offset packing, etc. ACCESS & BARCLAYCARD WELCOMED. Our shop is open to callers. BULK ENQUIRIES INVITED. Telephone: Haywards Heath (0444) 54563.




**SIMPLY AHEAD**  
and staying there

# The range grows bigger... better...

## New Profile Amplifiers - Two New Series

**MOSFET**

**CHOOSE AN I.L.P. MOSFET POWER AMP** when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified "New Profile" extrusions. These ensure optimum operating efficiency from our new MOSFETs, and are easier to mount. Connections via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**

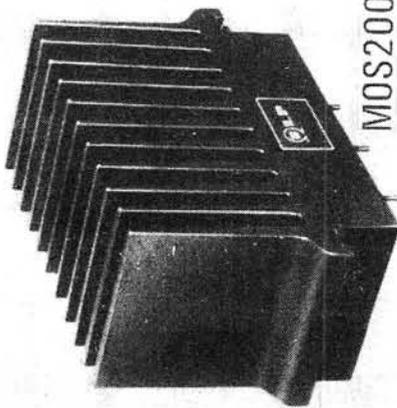


MOS200




HY60

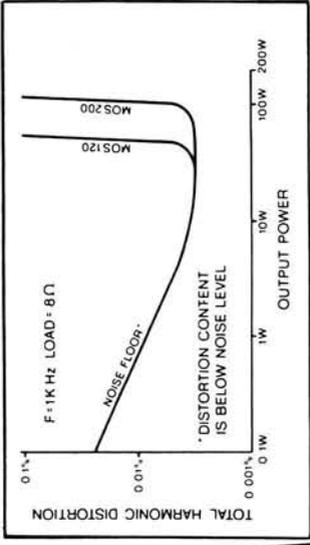**I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE**



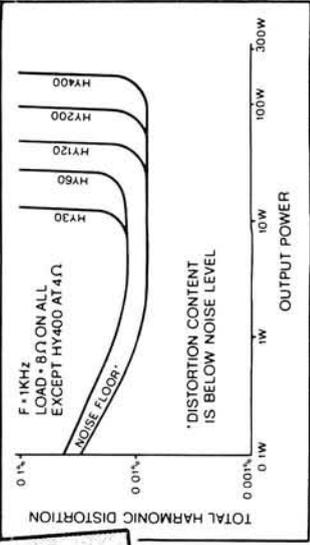Load impedance both models 4Ω - ∞ Input sensitivity both models 100KΩ Frequency response both models 15Hz-100KHz - 3dB



Load impedance all models 4Ω - ∞ Input impedance all models 100KΩ Input sensitivity all models 500mV 15Hz-60KHz - 3dB

**STANDARD O/P TRANSISTORS**

**BIPOLAR**

**CHOOSE AN I.L.P. BIPOLAR POWER AMP** where power and price are first consideration while maintaining optimum performance with hi-fidelity and wide choice of models. From domestic hi-fi to disco and P.A. for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

**THE NEW PROFILE EXTRUSIONS**

The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages: - Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



# I.L.P. PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide  $\pm 12$ dB cut and boost. Inputs Sensitivity - Mag. PU - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV. Main O/P - 500mV; Frequency response - D.C. to 100kHz - 3dB.

HY6 mono £6.44 + 97p VAT Connectors included  
 HY66 stereo £12.19 + £1.83 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT  
 B66 Mounting Board for one HY66 99p + 15p VAT

# I.L.P. POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembling building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.


- PSU30  $\pm 15$ V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS
- PSU36 for use with 1 or 2 HY30's £8.10 + £1.22 VAT
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.32 + £2.45 VAT
- PSU95 for use with 1 MOS200 £21.34 + £3.20 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.46 + £3.22 VAT
- PSU185 for use with 1 or 2 MOS200

## ★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.
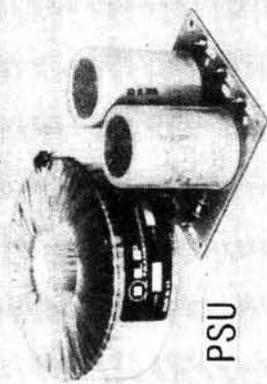
## ★ TO ORDER


Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



**NO QUIBBLE 5 YEAR GUARANTEE**  
**7-DAY DESPATCH ON ALL ORDERS**  
**BRITISH DESIGN AND MANUFACTURE**  
**FREEPOST SERVICE**



**I.L.P. ELECTRONICS LTD.**  
 FREEPOST 1 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.  
 Telephone (0227) 547778 | Technical (0227) 64723 | Telex 965780  
 Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

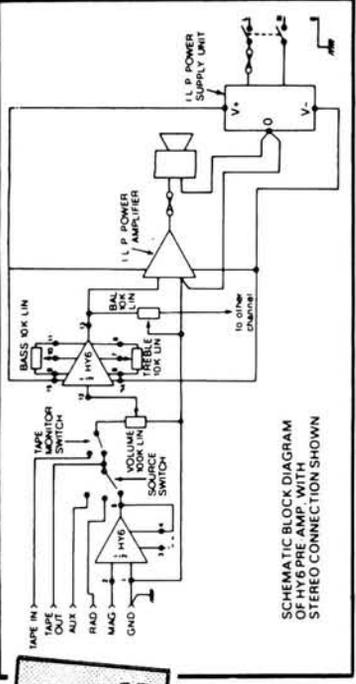

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY  $\pm 15$  to  $\pm 60$ V

**IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS**

# 1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

# BRITAIN'S LEADING QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply..... Total purchase price £.....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No.....

NAME.....  
 ADDRESS.....  
 Signature.....

**ALL U.K. ORDERS DESPATCHED POST FREE**

**TRIO****LAR****AUTHORISED****DEALER****...the sign of fine communications**

Authorised Distributor for TRIO equipment in Yorkshire and the North East.

**THIS MONTH'S LAR SPECIAL - Trio CO1303G 5MHz monitor-scope with two-tone oscillator £140.00 inc VAT.**

MC50	De luxe desk microphone dual impedance .....	24.15
MC35S	50K fist microphone (noise cancelling) .....	13.80
MC30S	500 ohm fist microphone (noise cancelling) .....	13.80
LF30A	HF low pass filter 1kW 90dB. Stop band rejection .....	18.40
LAR	1kW P.E.P. 3-way antenna switch .....	16.95

**VHF AMATEUR RECEIVERS**

SR9	Tuneable/crystal 2m FM receiver 144 146MHz.....	46.00
AMR217B	Scanner. The best mains/battery operated .....	120.75

**HF MOBILE ANTENNAS**

'G' whip tribander helical 20/15/10 .....	24.72
'G' whip multimobile 20/15/10 .....	28.75
L.F. coils for the above whips (specify whether tribander or multi-mobile) .....	6.56
Telescopic whips for the above .....	3.34
Base mounts for all 'G' whips .....	4.48

**VHF/UHF 'J' BEAM S. All 'J' Beam products available**

Famous Ringo Ranger 2m co-linear .....	27.60
Slim Jim 2m vertical .....	21.00
GDX2 VHF/UHF Discone Antenna 50-480MHz .....	39.50

**ROTATORS**

Sky King SU2000 .....	46.00	
DR7500	Will take 3 element tribander .....	108.10
DR7600	Will take a 2 element 40 metre beam .....	154.10
DR8600P	As above but with preset or manual controller .....	204.70
	Channel Master 9502A .....	56.00
	Channel Master HD/9508 .....	78.00

**VHF MOBILE WHIPS A.S.P. (Telecoms Accessories)**

All ASP mobile antennas and accessories available

**NEW HF VERTICAL ANTENNA**

HF5	80 10m vertical .....	48.50
HF5R	Operational radial kit for roof mounting .....	28.00

**ICOM PRODUCTS**

IC240	FM mobile synthesised transceiver 2m .....	169.00
IC202S	SSB portable (LAR PS1200 available!) 2m .....	169.00
IC211E	All mode 2m transceiver .....	450.00
IC255E	25 watt FM 2m mobile with memory and scanner .....	255.00
IC2E	2m FM hand portable .....	159.00
IC260E	2m all mode mobile .....	339.00
IC251E	All mode transceiver .....	479.00
IC720	0.1 to 30MHz in 1MHz steps .....	699.00

Securicor delivery arranged if required

**TRIO EQUIPMENT**

	Price inc. VAT	
<b>NEW!</b>	Trio 9000 multi-mode .....	<b>£345.00</b>
R1000	200kHz to 30MHz PLL Receiver with digital readout .....	285.00
R820	The ultimate matching receiver to the TS820 .....	690.00
TS830S	160 10M transceiver with the new bands. Successor to the TS820 .....	639.52
VF0230	Digital VFO with memories and digital readout .....	194.45
AT230	All band ATY and power meter. Matches TS830S .....	106.72
SP230	External speaker unit with switched filters .....	33.14
DFC230	Digital frequency remote controller. Four memories etc. ....	163.13
YK88C	500Hz CW Filter .....	26.45
YK88CN	270Hz CW Filter .....	28.75
SM220	Monitor scope .....	197.80
BS8	TS820 scan board for SM220 .....	48.30
TL922	HF linear amplifier 160-10m/2kW P.E.P. ....	595.70
SP520	Matching speaker .....	17.25
YG3395C	CW filter .....	37.95
TS120V	80-10m mobile transceiver 20W P.E.P. ....	347.30
TS130S	8 band 200W pep mobile transceiver .....	491.05
TS130V	8 band 20W pep mobile transceiver .....	404.34
SP40	New mobile speaker unit .....	26.89
TL120	80-10m 200W P.E.P. linear .....	128.80
PS20	AC power supply for TS120V .....	44.85
MB100	Mobile mounting bracket .....	17.25
YK88C	CW filter .....	26.75
SP120	Matching speaker .....	25.30
VF0120	Remote VFO .....	89.70
AT130	Antenna tuner (100W) .....	72.89
TS120S	80-10m mobile transceiver 200W P.E.P. ....	432.40
PS30	AC PSU for TS120S, TA130 & TS180S .....	85.10
TS770E	2m 70cm all mode dual bander .....	730.25
SP70	Matching speaker .....	18.40
TR7600	2m synthesised mobile FM 10 Watt .....	220.00
TR7800	2m synthesised mobile FM 25 Watt .....	268.00
PS8	PSU for TR7625 only .....	80.00
TR2300	2m FM portable transceiver .....	166.75
VB2300	10W booster .....	49.45
MB2	Mobile mount .....	17.25
RA1	Helical rubber antenna .....	6.90
TS180S	160 10m Solida State Transceiver. Digital memory system. 200W pep .....	679.65
VF0180	External VFO .....	96.60
SP180	Speaker .....	36.80
AT180	1.8 30MHz antenna tuner .....	95.45
PB10	Pack of 10 ni-cad batteries .....	10.35
TR2300	Spare power lead .....	1.30
LAR PS1200	Power supply unit and ni-cad charger for TR2200GX/TR2300/TR3200 and ICOM portables. You can charge and operate at the same time .....	29.50
SRX30	0.5 to 30MHz SWL Receiver .....	<b>£158.00</b>
HS5	Communications headphones, tailored response .....	21.85
HS4	Communications headphones, tailored response .....	10.35

**HOW TO BUY!**

OFF THE PAGE - Simply choose the product and then complete the coupon and enclose cheque.

\*Open Mon-Fri 9.15-6.00pm

Saturday 9.15-5.30pm

\*H.P. Terms on request

**POST NOW**

I enclose cheque for £..... Plus 50p for Brochure \* to purchase.....

Name.....

Address.....

CITY LIBRARY	No. 27	COOKRIDGE STREET
THE HEADROW		

FROM THE SHOP - We're close to the station and car parks. Do call in and discuss your requirements.

Authorised Distributor for TRIO, Equipment &amp; Area Distributors for JAY BEAM, ANTENNA SPECIALISTS &amp; HILOMAST PRODUCTS.

**LEEDS AMATEUR RADIO**

27 Cookridge Street, Leeds 2

Telephone: Leeds 452657

Post to: Leeds Amateur Radio, 27 Cookridge Street, Leeds 2.

TO BARCLAYCARD/ACCESS

I authorise you to debit my Barclaycard/Access Account with the amount of £..... My No. is

--	--	--	--	--	--	--	--

Signature



PW2

PW2



# comment...

## It's Coming!

AT LONG LAST we have a Government announcement on the legalisation of CB in the UK, though it doesn't reveal a lot of the things we need to know. There are to be two services, one on the 27MHz band and one around 930MHz, both using frequency modulation. Technical details such as channels, powers, etc., and licensing arrangements have not yet been finalised, and the whole thing will not become legal until the autumn, at the earliest.

The solution chosen by the Government is a technically elegant one. It can provide a limited number of channels on 27MHz, which gives a reasonable range for use in open country, on motorways, etc. The adoption of f.m. brings with it the benefits of "capture effect", and of reduced interference to other services. The CB enthusiasts like to maintain that they do not cause interference to radio, TV and hi-fi, but I know from first-hand experience that this is not so, and they should remember that **any** transmitter can cause interference. On 930MHz, there is the potential for a far greater number of channels, which will be needed to beat congestion in big cities, coupled with limited range, to allow re-use of a channel in other parts of a city.

The use of 27MHz a.m. transceivers will remain illegal, this fact is naturally causing some gnashing of teeth among enthusiasts already illicitly using a.m. sets, and a few importers with warehouses bulging with the things. What may happen about possible modification of these sets to the f.m. mode depends upon

the way the new regulations are framed. And what will happen to the existing multi-mode (a.m./f.m.) sets?

If CB is really to help ordinary people in emergencies, in the way its promoters say it will, one essential will be to get away from the use of the American truckers' CB slang so beloved of the present illegal users. It's going to be no good for example, asking the little old lady who's just been mugged: "What's your 20?" Plain language is a must.

\* \* \* \* \*

In response to requests from our readers, we have decided to devote the whole of future issues of *Practical Wireless* to radio. We shall cover all aspects and applications of radio of interest to the enthusiast, plus components and techniques used in radio, but we shall not be carrying designs for burglar alarms, ignition systems or household gadgets and the like.



# services

## QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the **Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG**, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

## PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

## CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

### Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

### Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

### Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

## SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £11.80 per annum, from "**Practical Wireless**" Subscription Department, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Airmail rates for overseas subscriptions can be quoted on request.

## BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 95p each, including post and packing to addresses at home and overseas.

Binders are available (Price £4.30 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF**. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.



# CB UK

## CITIZENS BAND

The following is the full text of the Home Office announcement, made on 26 February 1981.

### CITIZENS BAND RADIO APPROVED ON 27MHz FM AND 930MHz FM.

#### 27MHz AM EQUIPMENT REMAINS ILLEGAL

Britain is to have a legal citizens band radio service. Mr William Whitelaw, the Home Secretary, announced this today in a Parliamentary answer to Mr Patrick Wall MP. It is hoped that the new service will be introduced in the autumn.

The new personal two-way service will be authorised on 27MHz f.m. (frequency modulated), and a further frequency will be made available around 930MHz. Equipment will be required to meet a technical specification, and users will have to buy a licence.

The 27MHz a.m. (amplitude modulated) equipment currently being used in this country is illegal and will remain so.

Commenting on the introduction of the new service, Mr Timothy Raison, MP, Minister of State at the Home Office, said today:

"We are offering a new service which we hope will provide enjoyment for many people. It will give as good a service as the illegal a.m. equipment—indeed some of this is already obsolete. It should soon cost about the same and should cause fewer problems for others. The interference which illegal CB equipment is causing to TV reception and emergency services is giving rise to concern, and now that the Government has gone so far towards meeting the wishes of supporters of CB, I hope that we can rely on those with illegal equipment to act responsibly and stop using it."

#### Choosing the Frequency

The Home Secretary said in a written Parliamentary reply on 18 December 1980 that he favoured the introduction of a CB facility on a frequency around 930MHz, but because of public demand for an alternative he undertook to consider the possibility of legalising additionally on a lower frequency. The final decision had to take into account the need to introduce a legalised service with the minimum of delay; the risk of interference to radio, TV and other authorised services both in the United Kingdom and in neighbouring countries; the availability of frequencies; and the desirability of adopting an international standard. The frequency selected—27MHz f.m.—should give CB enthusiasts the performance they want at about the same cost as illicit equipment with far less interference to other users. France, the Netherlands and Germany are among those European countries who have legalised on 27MHz f.m. equipment and the Irish Republic has recently announced its intention to do the

same. The other frequency proposed—around 930MHz—is going to be adopted in North America and some European countries, and is seen as being capable of giving a good quality service, especially in towns and cities, with the minimum of interference. It offers the prospect of an international market for British manufacturers.

Other alternative frequencies, such as 41MHz and 450MHz, were reviewed but none was free of interference difficulties or met the other requirements.

Existing authorised users of the 27MHz band, for example, hospital paging systems, may be affected by the Government's decision and the implications for them will be taken into account during the planning period.

#### Existing Equipment

Existing illegal 27MHz a.m. (amplitude modulated) equipment will not be legalised. The volume of interference from CB sets using 27MHz a.m. equipment is increasing—in the last five months alone there were nearly 5000 complaints of interference to radio, TV and hi-fi which were directly traced to the use of illegal 27MHz a.m. sets; this represents an increase of about one-third of all recorded complaints of interference from all sources. Emergency services have also been affected. Although recent a.m. equipment of US origin causes less interference to some services than earlier models, its potential for interference to TV remains high.

#### Equipment Specification

Specifications for the new f.m. (frequency modulated) equipment will be drafted to ensure that it causes the minimum of interference to other radio users; standards will be set to which manufacturers, importers and assemblers will conform. The equipment will have to be permanently marked so that a purchaser knows the set he is buying meets these standards. Such specifications are vital to ensure that other radio services (police, fire, aviation) are not adversely affected.

#### Licensing

Users of the new service will have to buy a licence, renewable annually, which will entitle them to use equipment on either frequency. Talks are taking place with the Post Office to see if they can issue licences on behalf of the Home Office. It is too early to say what the cost of a licence will be.

#### Commencement Date

It is hoped to complete the arrangements for technical specification, equipment marking and licensing, and bring the new service into operation, by the autumn.

# NEWS NEWS NEWS

## Rallies and Events

Spalding and District Amateur Radio Society are once again holding their "Tulip Time Rally" on Sunday, 3 May 1981, at Spalding Grammar School.

Further details from: *Hon Sec, G. C. L. Parker G4EMK, 29 Saxon Way, Bourne, Lincs.*

The Welsh Amateur Mobile Rally, organised by the Barry College of Further Education Radio Society will be held on Sunday, 10 May, at the Barry Memorial Hall.

Further details from: *Simon Lloyd Hughes GW8NVN, 1 Min Y Mor, Barry, South Glamorgan CF6 8QG.*

Otley Radio and Electronics Society will be holding the Northern Mobile Rally on Sunday, 17 May, at the Victoria Park Hall, Keighley, between 1100hrs and 1630hrs. Wheelchair and blind visitors will be welcome at 1045hrs.

Further details from: *Rally Manager, Mrs P. A. Horne G8KRU, 14 Fieldhead Road, Guiseley, Leeds LS20 8DT.*

East Suffolk Wireless Revival, organised jointly by Ipswich Radio Club and Martlesham Radio Society, will take place on Sunday, 24 May, at the usual venue, the sports ground of the Ipswich Area Civil Service Sports Association, Straight Road, Ipswich (between Bucklesham Road and Felixstowe Road (A45) and adjacent to the Suffolk Show Ground).

Further details from: *Jack Tootill G4IFF, 76 Fircroft Road, Ipswich IP1 6PX. Tel: (0473) 44047.*

Hull and District Amateur Radio Society will be holding their Mobile Rally 1981 on Sunday, 7 June, at Hull University.

Further details from: *I. B. Carress G8EAH, 124 Dayton Road, Priory Road, Hull, Yorks.*

## Video Recording Techniques

With UK sales of video recorders expected to rocket during 1981, both Sony and JVC have produced literature to assist customers in utilising the facilities of their recorders in all aspects of making home video movies.

Sony has produced a 48-page handbook which is amply illustrated and uses simple non-technical

language, the handbook—entitled "How to Video"—is currently on sale at *Sony London Showroom, 134 Regent Street, London W1*, price 60p. It is also available by post from the showroom (30p extra).

JVC's publication entitled "Video the Better Way", comprises five volumes, each illustrated with colour and black and white photographs and diagrams. Each volume contains an aspect of video—"Basics", "Production", "Enhancement", "Applications" and "Supplements". Costing around £3.95, "Video the Better Way" is available from JVC dealers and specialist video outlets.

## Keep Your Eyes Open

Following a meeting at a hotel in Bournemouth on 6 February, Martin Linda G4GTH, RAYNET controller for SE Dorset, returned to his car to find his mobile rig had been stolen.

The rig comprised a Trio TR2300, serial No. 921187, with reverse repeater and without case or strap, and a homebuilt 25W amplifier, housed in a 300 x 75 x 75mm dark grey case with two switches and l.e.d.s on the right and three fuse holders on the left of the front panel.

If you have any information regarding this equipment, please contact either Bournemouth Police or G4GTH QTHR (Tel: 0202 763899).

## CW Course

It is hoped that a new course will shortly be available in the Cheshunt area of Hertfordshire for potential Class A licence holders. The Cheshunt and District Radio Club are currently trying to organise the course at the East Herts. College at Turnford, starting late in April (the beginning of the summer term) for approximately 12 weeks and is intended for absolute beginners in c.w.

If the course is successful, it may be possible to repeat the course in the new college year starting in September.

For further details, please contact: *Jim Sleight G30JI, QTHR. Tel: Ware (0920) 4316.*

## Sale of Surplus Stock

In a joint effort, Home Radio, Harvesons and G.P. Transformers have organised a "bargain sale", at which will be offered resistors, capacitors, potentiometers, speakers, transformers, tools etc., at exceptionally low prices (many items below manufacturing cost).

Home Radio are turning over their first floor to the sale, and it will run from Saturday 25 April until Saturday 2 May, between 9.00am and 5.30pm (Wednesday 1.00pm).

Ample parking space is available at the sale venue at: *269A Haydons Road, London SW19. Tel: 01-543 5659.*

## Club News

Saltash and District Amateur Radio Club would like to extend a welcome to prospective new members and visitors.

The Club, G4GXX, has approximately 70 members and meets on the first and third Friday of each month at 1930hrs.

Further details from: *Paul Lamerton, 17 Baber Court, St Diminick, Saltash, Cornwall.*

## Introduction to Amateur Radio & SW Listening


As a result of the success of this short course last year, it has been decided to repeat it at two centres in Nottingham immediately following the current RAE courses.

Commencing on 18 May 1981 at Hucknall College of Further Education and on 20 May at Arnold and Carlton College of Further Education, the course runs for five weeks excluding Spring Bank Holiday week.

The syllabus includes an outline of the RAE, some basic theory, receiver operation for the amateur and commercial bands and practical points concerning construction techniques and aerials. In short, a useful preliminary to the RAE.

Further information can be obtained from: *The Course Tutor, Alan Lake G4DVW, on Nottingham (0602-382509), from Hucknall CFE (0602-637316) or from Arnold and Carlton CFE (0602-876503).*

# BI-PHASE COMPARATOR

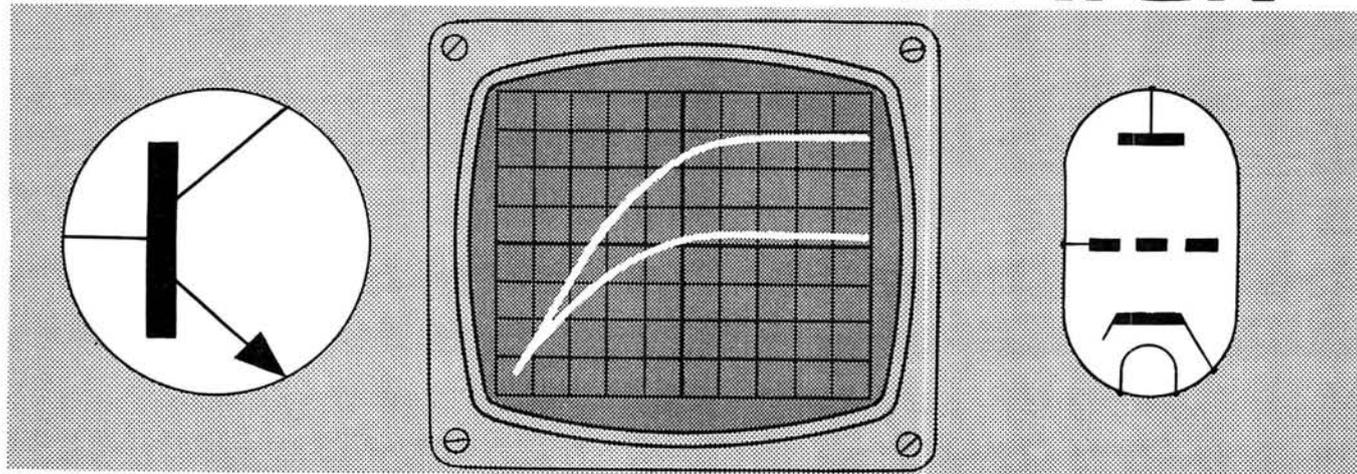

A.J. BIRKINSHAW G3DMC

Valves and transistors provide the active elements of most electronic equipment. The term "characteristic" is used to identify distinguishing electrical features and values of active devices.

Manufacturers' data sheets normally include a graph of anode or collector current plotted against supply voltage in the form of a characteristic curve. Families of curves, each at a different bias setting, may be used for the determination of performance and the calculation of additional parameters.

Although well designed circuits will tolerate a wide change in characteristics there are extremes that will affect overall performance.

A valve will eventually degenerate with age due to loss of emission, reducing gain, or release of gas occluded in metal electrodes causing hysteresis. Gain does not normally change as a transistor ages; defective transistors can readily be detected because they will have little or no gain and exhibit a shorted or open-circuit condition or have excessive leakage.

## Curve Tracing

Characteristic curves may be displayed on an oscilloscope for comparison with published data enabling ageing devices to be identified and compared with younger or unused samples.

Whilst the instruments and techniques to be described in this article are capable of a wider application, their use will be confined to analysis of 6.3 volt heater valves and popular silicon *npn* transistors.

The bi-phase comparator is a measuring instrument for simultaneously comparing the characteristic curves of two electronic valves or semiconductor devices whilst varying the operating conditions of either. A bi-phase source of alternating voltage energises each device alternately and the sweeps of applied voltage versus current are graphically displayed by horizontal and vertical deflection of a cathode ray tube. The rapidly alternating images ap-

pear to the eye simultaneously. If one device is operated at a fixed bias whilst the bias on the other is controlled manually the controlled characteristic curve may be adjusted in comparison to the fixed curve.

Calibration of each ordinate is pre-set: horizontal voltage deflection against a reference voltage supply and vertical current deflection by the volts per milliampere across a calibrated resistor.

The instrument is used to test devices against published characteristic curves, to check samples against a standard, to check deterioration of used devices, to match two samples for pairing in symmetry circuits or to decide the optimum bias required for a particular application. The characteristic of each device is traced alternately at a rate dependent on the supply frequency.

The display section of the instrument can be separate in the form of a basic oscilloscope having d.c. amplification to both X and Y plates.

The power supply unit can be specially built or adapted from a similar unit having a bi-phase secondary winding on the power transformer.

Fig. 1


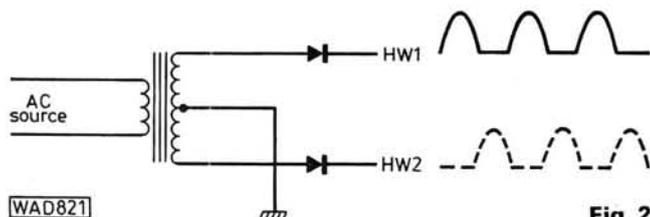
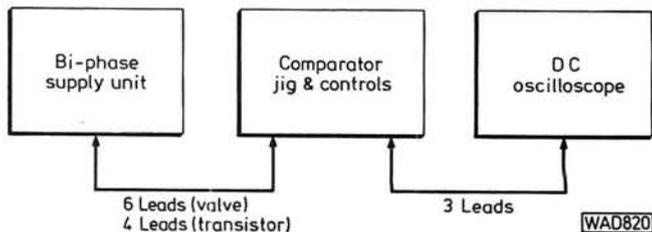


Fig. 2

Fig. 3

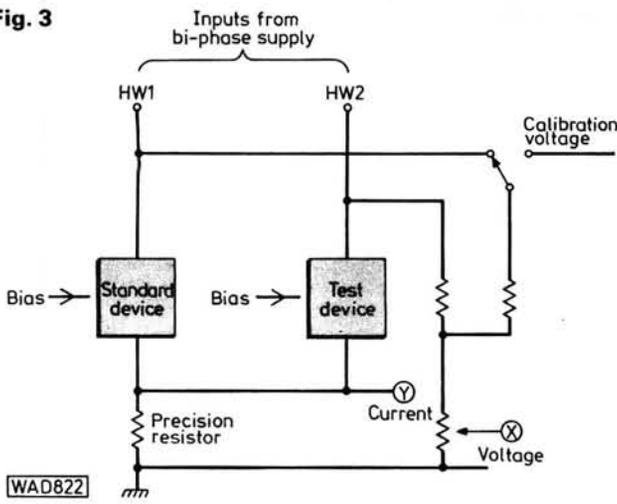

### Basic Principle

The arrangement of units is shown in block form in Fig. 1 coupled by connector lead assemblies.


A suitable bi-phase source is shown in Fig. 2 and consists of a transformer with a centre tapped secondary winding feeding two rectifiers to provide alternate unidirectional half-wave outputs HW1 and HW2. During the sweep of one half wave the other output remains at zero.

The half-wave voltages are applied separately to each device being compared in Fig. 3, current flowing through a precision resistor common to both circuits—the small voltage sweeps across this resistor are proportional to the currents passing through each device providing the vertical Y input of an oscilloscope.

Horizontal sweep voltages are taken from a combined potentiometer circuit across the half-wave inputs giving X input proportional to the applied voltage.

Internal d.c. amplifiers of the oscilloscope produce the characteristic display of device current plotted against applied voltage shown in Fig. 4. Trace identification is available by altering the bias to one of the devices.

Fig. 4

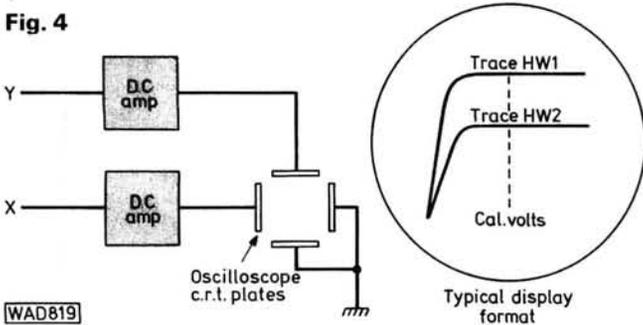

### Calibration

Vertical current is known by the volts per milliampere at the precision resistor and the calibrated volts per centimetre of the oscilloscope Y input. Horizontal volts are checked by switching one leg of the potentiometer chain to a voltage reference source and setting the output control for an unswept vertical trace to a graticule line.

Fig. 5

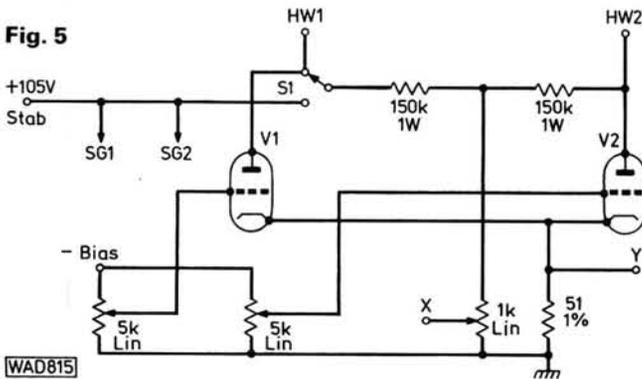


Fig. 7

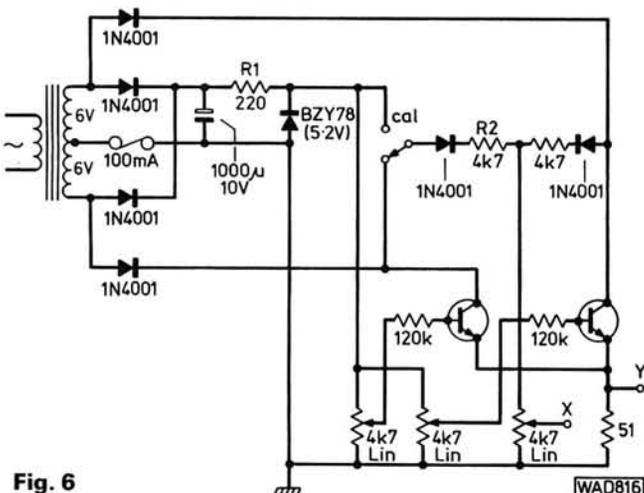
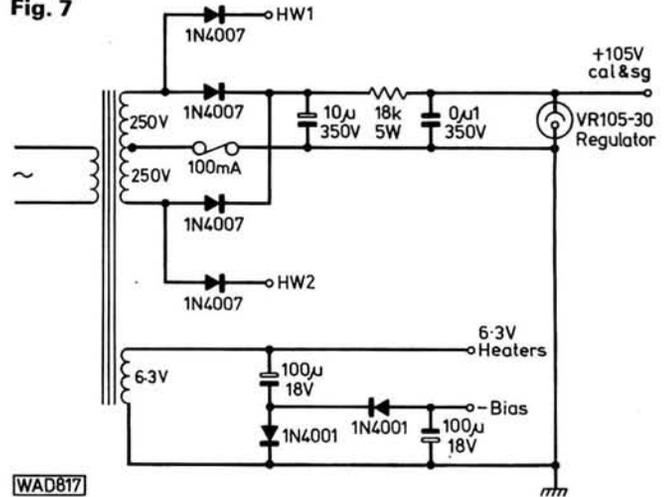


Fig. 6

### Construction

Although the circuit is simple and the wiring layout not critical, attention should be paid to adequate mechanical arrangement of interconnections. These will consist of a four or six pole plug and socket lead assembly to the power supply unit, 4mm plug leads to the oscilloscope and pairs of valve or transistor sockets suitable for the devices being tested.

A slow blow 100mA fuse at the centre tap point is essential. The transistor comparator is shown in Fig. 6, complete with its own power supply, as this is less cumbersome than the valve arrangement, allowing assembly in a small plastics box.

continued on page 41 ▶▶▶



# HF TRANSCEIVER

The Yaesu FT-707 "Wayfarer" is part of a matching range of units including the FP-707 power supply for a.c. mains operation (the FT-707 is a 13.5V d.c.-powered unit), the FC-707 antenna coupler, and the FV-707DM external digital v.f.o. The FT-707 covers all the amateur bands from 80 to 10 metres including the WARC '79 additions, with a nominal power output of 100 watts on s.s.b. and c.w., and 50 watts on a.m. (d.s.b.). There is also a low-power version, the FT-707S, with a power of 10 and 5 watts for the respective modes. Our photographs are of the FT-707S, but most of our tests were carried out on its big brother, which differs in appearance by the addition of the 100W p.a. heatsink on the rear of the case.

The transmitter is basically designed for s.s.b. use, being of the balanced ring modulator/filter format, with an 8987.5kHz i.f., followed by a diode ring mixer to convert the signal up to the final radiated frequency for delivery to the power amplifier. The output of the p.a. passes via bandswitched low-pass filter networks and a directional coupler to the rear-panel SO239 antenna socket. On c.w., a separate 8988.3kHz carrier signal is generated and fed to the ring modulator which is unbalanced by the application of a d.c. bias. Keying is carried out in the r.f. amplifiers driving the p.a. On a.m., the microphone modulates the 8988.3kHz carrier and the s.s.b. filter is bypassed. On c.w. and a.m., the power output can be reduced to around 10W by means of the front-panel carrier level control. Both manual and voice-operated transmit/receive switching are provided, the VOX operates on c.w. as well. There are external controls for VOX sensitivity and hang-time, and an internal anti-VOX adjustment.

The p.a. is protected against excessive antenna v.s.w.r. by using a signal from the directional coupler to reduce the gain of the r.f., i.f. and a.f. stages of the transmitter. Protection against over-driving or overheating of the p.a. transistors is also provided, and there is a temperature-controlled fan for the p.a. heatsink. The a.l.c. (automatic level control) circuit allows the FT-707 to develop 50 per cent of its full rated output power safely into a load with a v.s.w.r. of 3:1. Operation of the a.l.c. circuit and the power output can be monitored by means of the l.e.d. level meter.

On the receiver side, the antenna is fed via a 1.7MHz high-pass filter (for enhanced medium-wave broadcast band rejection) and individual antenna coils for each band to a dual-gate MOSFET amplifier. A 9MHz i.f. trap improves i.f. rejection to a level which we measured as 88dB—a very creditable figure. The amplified signal passes via diode-switched band-pass filters to a Schottky barrier diode ring mixer, which produces the 8987.5kHz i.f. signal. This is fed via a 20kHz monolithic crystal filter to the noise blanker, which is a very impressive performer indeed. For example, impulsive noise causing an S4 meter reading and completely

obliterating a weak station on 10m, could be virtually eliminated to improve the wanted signal to Q5.

From the noise blanker, the signal goes to a variable bandwidth circuit, which can be adjusted between 300Hz and 2.4kHz at the -6dB points on s.s.b. and c.w. Very effective a.g.c. is provided, with a choice of fast and slow decay time-constants. A diode ring demodulator converts the signal to audio, which is ultimately fed to the loudspeaker via an i.c. amplifier.

Concentric r.f./i.f. and a.f. gain controls are provided, and a clarifier permits a receiver shift of up to  $\pm 3$ kHz relative to the transmitted frequency. A 25kHz crystal calibrator is available for scale checks.

Both digital and analogue (dial skirt) frequency readouts are provided. The tuning rate is 100kHz per revolution of the main dial, rather faster than the ideal for resolution of s.s.b. signals, but the knob is well-placed, clear of other controls and very smooth in operation, and no problems were experienced in tuning on s.s.b. The l.e.d. level meter operates as an "S" meter on receive, and was found to be accurate within  $\pm 1.5$ dB above the S9 mark.

Special filters with -6dB bandwidths of 350Hz and 600Hz are available as an optional extra for use on c.w., but neither of these was fitted to the review transceiver. Another untested option is a single crystal-controlled fixed channel in each amateur band except the new 30m band.

Microphone and headphone connectors are provided on the front panel, while at the rear there are a.f. outputs for a tape recorder, etc., and an external loudspeaker; Morse key jack; r.f. output for driving a transverter; accessory socket for remote microphone, etc.; external v.f.o. jack for connecting the FV-707DM; 8V d.c. output for the panel lamps in the FC-707; 13.5V d.c. supply input connector and antenna and earth connectors.

The FV-707DM external v.f.o. provides 12 memory channels plus scanning in 10Hz steps and offset from the memory channels. The latter functions are controlled from the scanning microphone.







The FC-707 antenna coupler (not shown in our photographs) will match an antenna with a feedpoint impedance of 10-250 $\Omega$  to the 50 $\Omega$  required by the FT-707. It also incorporates s.w.r. and power output metering, and a 50 $\Omega$  dummy load.

## Results

On-air tests, using a variety of antennas: long wire, trapped dipole and trapped vertical, all produced very good results. The receiver is sensitive and stable, with no apparent vices of any kind, and reports of transmitted quality are good. The transceiver is small enough for sensible mobile use (a mounting bracket is available) or, as the instruction

Inside view of the FP-707 power supply incorporating an extension loudspeaker ▶

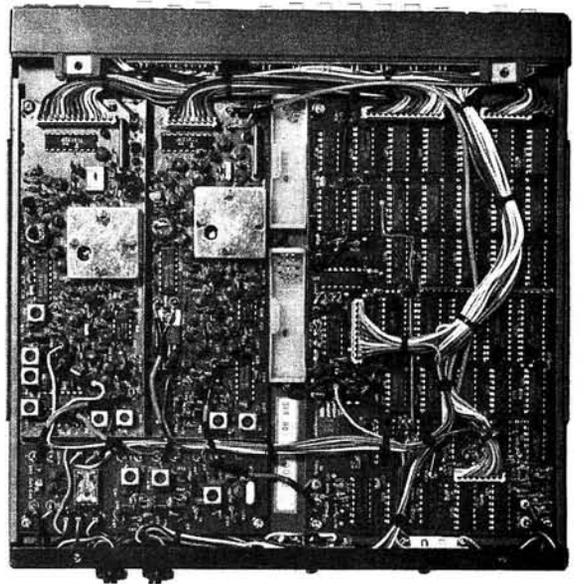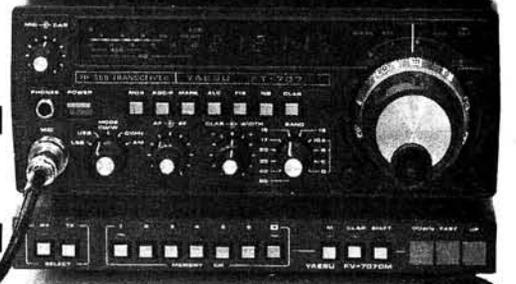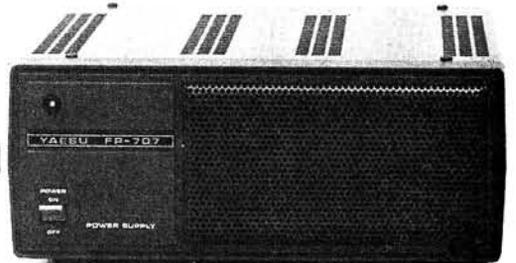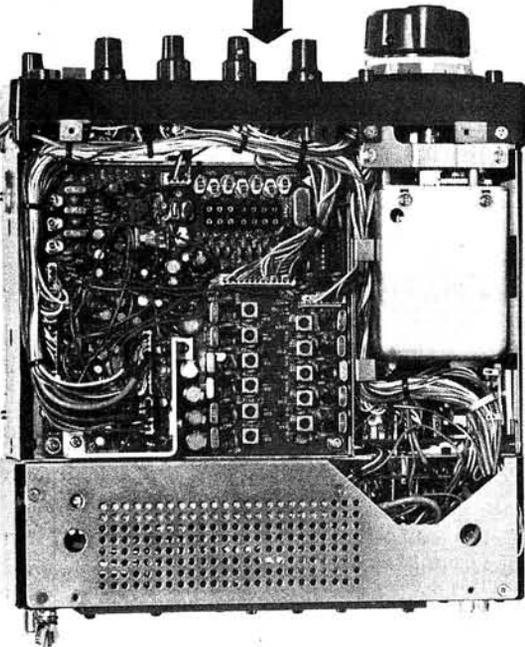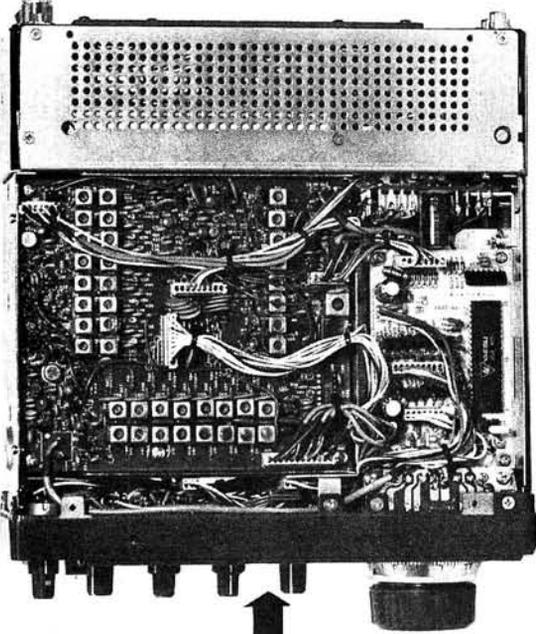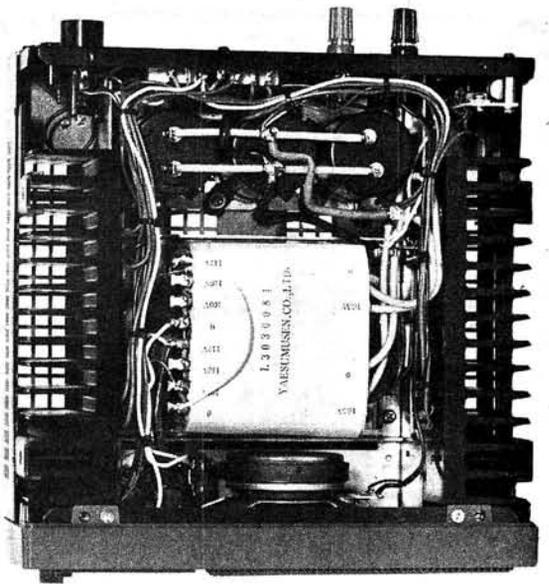Top and bottom views of the FT-707S. Accessibility for servicing appears good, considering the very compact construction ▶



The FV-707DM. The battery holders in the centre are for a memory back-up supply ▶

## ★ specifications

**Frequency coverage:** 3.5–4.0MHz (80m)  
 7.0–7.5MHz (40m)  
 10.0–10.5MHz (30m)  
 14.0–14.5MHz (20m)  
 18.0–18.5MHz (17m)  
 21.0–21.5MHz (15m)  
 24.5–25.0MHz (12m)  
 28.0–29.9MHz (10m)

**Types of emission:** A1 (c.w.), A3 (d.s.b.) and A3J (u.s.b./l.s.b.)

**Power input:** A1/A3J 240W d.c.  
 A3 80W d.c.

**Carrier suppression:** Better than 40dB

**Sideband suppression:** Better than 50dB at 14MHz, 1kHz mod.

**Spurious emissions:** At least 50dB down

**Third order distortion products:** At least 31dB down

**Frequency response:** 350–2700Hz (–6dB)

**Frequency stability:** Less than 300Hz drift over 30 minutes after 10 minutes warm-up; less than 100Hz drift after 30 minutes warm-up

**Microphone impedance:** 500–600Ω

**Antenna impedance:** 50Ω unbalanced

**Receiver sensitivity:** A1/A3J 0.25μV for 10dB S/N  
 A3 1.0μV for 10dB S/N

**Selectivity:** A1/A3J 2.4kHz (–6dB)  
 4.0kHz (–60dB) plus variable bandwidth control  
 A3 3.6kHz (–6dB)  
 6.8kHz (–60dB)

**Image rejection:** 60dB (80–12m), 50dB (10m)

**Audio output:** 3W into 4Ω at 10% t.h.d. (permissible load range, 4–16Ω)

**Power requirements:** 13.5V d.c., negative earth 1.5A receive, 20A (peak) transmit

**Case size (FT-707):** 93 × 240 × 295mm

**Weight (FT-707):** 6.5kg approx.

## ★ Test measurements

### TRANSMITTER

**Power output:** A3 75W carrier  
 A3J 212W p.e.p.

**Carrier suppression:** On u.s.b. –43dB  
 On l.s.b. –42dB

**Sideband suppression:** Output u.s.b. –53dB  
 Output l.s.b. –56dB

**Two-tone intermodulation:** –29dB relative to either tone

### Harmonic and spurious outputs:

Band (m)	Spurious outputs	Harmonic outputs
80	All better than –70dB	2nd –60dB
40	All better than –70dB	2nd –53dB
30	No transmit	
20	All better than –70dB	2nd –52dB
17	No transmit	
15	All better than –70dB	2nd –50dB
12	No transmit	
10	Spurious output at ±1.6MHz at –60dB	2nd –60dB

### RECEIVER

#### Sensitivity:

Band (m)	Input for 12dB SINAD (μV)		Input for S9 (μV)
	A3J	A3	
80	0.3	1.1	16
40	0.19	0.75	15
30	0.23	0.95	15
20	0.2	0.95	15
17	0.17	0.75	15
15	0.18	0.85	15
12	0.18	0.8	15
10	0.18	0.9	17.5

**Image rejection:** From 72.5dB on 80m, to 52.5dB on 10m

**Intermodulation:** Input level of two equal signals at  $f + 10\text{kHz}$  and  $f + 20\text{kHz}$  which produce a 12dB SINAD signal at  $f$ , relative to that required at  $f$  to produce 12dB SINAD=71dB

**Blocking:** Input signal level (relative to 12dB SINAD level), 10kHz away from wanted signal, to degrade SINAD by 6dB=80dB

**Audio output:** 2.5W into 4Ω for onset of clipping  
 3.9W into 4Ω for 10% t.h.d.

manual suggests, to take away on holiday. It seems to incorporate all the really necessary features, without any gimmicks, and it's going to break my heart to send the review model back.

The four units mentioned in the review are so sized that they will stack (as shown in our heading photograph) or sit side by side along a desk top (see pages 50/51 in our March 1981 issue). There is also available a special mounting rack, while looks like a small version of the adjustable steel shelving used in warehouses. It certainly doesn't match the equipment in appearance or quality, and I personally wouldn't give it house-room. Please, Yaesu, bring out something more suitable, if you feel a rack is really necessary.

The instruction manual for the FT-707 is quite comprehensive, with information on controls, connections and installation, and operation. There are circuit diagrams, a block diagram and detailed circuit description, quite a lot of maintenance and alignment information, major component

location pictures and a fairly detailed parts list. Similar manuals are provided with the external v.f.o. and antenna coupler, but that for the mains power supply is more basic.


The manufacturer's specification and our measurements are shown in the tables. The test equipment we used was: TF2002 signal generator, TF2370 spectrum analyser, TF2000 audio signal generator and TF893A audio power meter (all by Marconi Instruments), Hewlett Packard 1707B oscilloscope and Sinadder automatic signal-to-noise meter.

The FT-707 is currently available at around £500 including VAT, approximate prices for the associated items being: FP-707 £110, FC-707 £80 and FV-707DM £180, all including VAT. A range of microphones cost between £6 and £23, according to facilities offered. We are indebted to **South Midlands Communications Limited, SM House, Osborne Road, Totton, Southampton SO4 4DN, telephone Totton (0703) 867333**, for the loan of the review equipment. ●


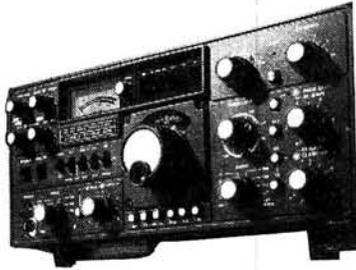
# BUY ONE ~ TAKE ONE


A YAESU SPECTACULAR FROM THEIR NUMBER ONE UK RETAIL OUTLET WITH FULL FACTORY BACKED SERVICE.



Buy this FT902 DM at £799.00

AND TAKE  
1 Skymaster 4000 Rotor Worth £85.00  
or  
1 Astatic Silver Eagle Mic Worth £50.00

**Free**

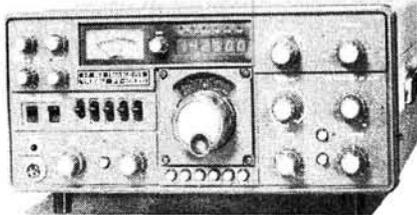

Buy this FT101ZD at £569.00

AND TAKE  
1 Shure 526T Mic Worth £40.00  
or  
1 Oskerbloc or 200B SWR/PWR Meter Worth £40.00


**Free**



Buy this FT707 at £529.00

AND TAKE  
1 Shure 526T Mic Worth £40.00  
or  
1 Killowatt Dummy Load Worth £35.00


**Free**

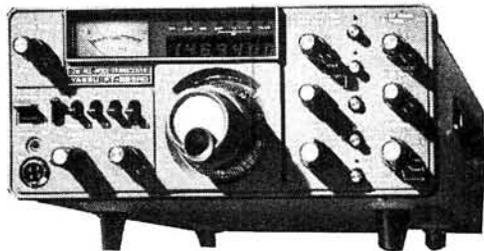

Buy this FT225 RD at £565.00

AND TAKE  
1 AR40 Rotor Worth 59.00  
or  
1 Shure 526T Worth £40

**Free**

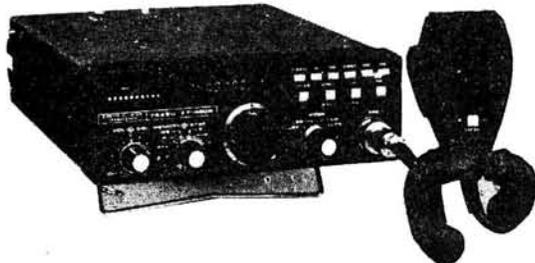

Buy this FT480 at £359.00.

AND TAKE  
1 Jaybeam 4 Element Quad Worth £23.69  
or  
1 Jaybeam 8 x y/2m Antenna Worth £28.40

**Free**

## AMCOMM SERVICES

194 NORTHOLT ROAD, SOUTH HARROW, MIDDX.  
Telephone: 01-864 1166, 01-422 9585

Opposite South Harrow Tube Station on Piccadilly Line

ALL ITEMS INCLUDE VAT + CARRIAGE

### Showroom Opening Hours:

Tuesday to Saturday 9.00 - 5.30 Sunday by Appointment

Please send me \_\_\_\_\_

at \_\_\_\_\_ enclosed cheque/P.O. for \_\_\_\_\_

\_\_\_\_\_ or charge my VISA/ACCESS

Nr. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_ Post Code \_\_\_\_\_

Amcomm Services  
194 Northolt Road,  
South Harrow,  
Middx HA2 0RN.

# Lee Electronics Ltd



LONDON'S LEADING SUPPLIER OF—STANDARD ★ ICOM ★ YAESU ★ FDK ★ MICROWAVE  
MODULES ★ J-BEAM ★ LUNAR ★ HI-MOUND ★ TELECOMM ANTENNAS ★ COMMUNI-  
QUE PRODUCTS ★ OSCAR METERS ★ AND MANY MORE TOO NUMEROUS TO MENTION ★



## TELECOMM

### TOP QUALITY MOBILE ANTENNAS

TA-301 2m  $\frac{1}{4}$  wave with snap-in mount and cutting chart £3.99

TA-309 2m  $\frac{5}{8}$  wave 3dB gain with snap-in mount and cutting chart £9.95

TA-330 UHF 3dB gain with snap-in mount and cutting chart £10.50

TA-3MM Magnetic mount for the above supplied with coax cable and PL259 fitted £9.75

TA-3GC Gutter clip for above supplied with coax cable and PL259 fitted £9.75

POSTAGE FREE

## YAESU MUSEN

THE LARGEST RANGE IN LONDON!

PHONE FOR PRICES!



FULL RANGE IN STOCK



SWR200B swr/power meter covering 3-200MHz 50/75 Ohm power range 3-30MHz, 20/200/2kW, VHF 2/20/200W £39.95 inc. VAT, P&P 50p.

### HI-MOUND KEYERS

KH707 Straight UP/Down keyer £10.06  
BK100 Semi auto/mechanical bug £17.88  
HK702 Up/Down keyer on marble base £22.43  
MK702 Manipulator £22.43  
MK704 Squeeze paddle £14.38  
MK705 Squeeze paddle on marble base £22.43  
ALL PRICES INC. VAT, P&P 50p

### ADONIS MICS

AM802 Desk mic £59.95  
AM502 Desk mic £29.95  
202S Boom mic £20.98  
202HD Headset £28.17  
202FX Swan neck £30.48  
ALL PRICES INCLUDE VAT  
P&P 50p


### C78 Special Offer

C78+  
CL8+  
CPB78

Normally £299.90




NOW ONLY £289.00

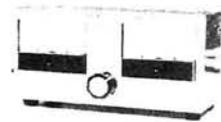

T-435: VHF/UHF swr and power meter with 2/20/120 watt through line power measurement £34.95 inc. VAT, P&P 75p.



UH74 SWR and power meter switchable HF, 2m and 432MHz with remote head at £16.39 inc. VAT, P&P 75p.

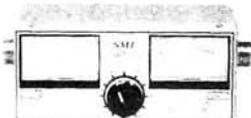

SWR25: This ever-popular twin SWR and Power meter covers 3.5-150MHz at £12.00 inc. VAT, P&P 50p.



DL-30 Dummy load 25W DC-150MHz £6.35 inc. VAT, P&P 25p.  
T-100 100W Dummy load DC-500MHz £20.12 inc. VAT, P&P 25p.  
T-200 150W Dummy load DC-500MHz £35.60 inc. VAT, P&P 25p.

### HELICAL ANTENNAS

2m with BNC plug £4.50  
2m with P1259 plug £4.50  
2m with IC215/Standard/Trio screw £4.25  
2m with AR240 screw £4.25

ALL PRICES INCLUDE VAT, P&P 25p

### COAX SWITCHES

#### ★ NEW SA-450 ★

High quality coax switch housed in a diecast box with SO239s  
Frequency 3.5-500MHz  
Loss 0.02dB  
Weight 450gms  
Max power 2.5kW  
Impedance 50ohm



CT-1 Coax toggle, 3 SO239s £6.85 inc. VAT, P&P 25p.

CT-2 Coax toggle, 2 SO239s, 1 PL259 £6.85 inc. VAT, P&P 25p.



TS-120 Coax slide switch, 3 SO239s £6.75 inc. VAT, P&P 25p.

### POWER SUPPLIES

PM103 4.5/6/7.5/9/12V dc 500mA fully stabilised £13.50 inc. VAT, P&P £1.00  
PX402 13.8V dc 3A max fully stabilised power supply with overload protection £21.95 inc. VAT, P&P £2.00  
PH5000 13.8V dc 5A continuous 7A max. Fully stabilised £46.00 inc. VAT, P&P £2.00.



PX402

### C8800 ONLY £251



C7800 still available at £274.85

### FRG 7700



Basic Unit £309 – Memory £83.95  
– With Memory Fitted £389

### R1000



ONLY £289

All MICROWAVE MODULES products available

## LEE ELECTRONICS LTD

400 EDGWARE ROAD, LONDON W2  
Tel: 01-723 5521. Telex: 298765  
9.30-5.30 Mon. to Fri. 10.00-4.30 Sat.

## HF & PART EXCHANGES WELCOME

SAE FOR FULL DETAILS



# SUPPRESSING & PROTECTING THYRISTORS

Ben J. DUNCAN

Part 1

Thyristors have gained a notorious reputation for being fragile devices electrically speaking, and this series of articles shows how thyristors and triacs may be confidently applied in power control circuits.

The word "thyristor" is derived from the Greek for "a door" and is the generic name for a large family of semiconductor devices. However, in the UK, the term "thyristor" is usually limited to the unidirectional device (also known as the silicon controlled rectifier or s.c.r.), whilst the bi-directional device is commonly known as the triac. There are many other members of the thyristor family, but for power applications we shall only need to consider the s.c.r. and the triac. Both of these devices are used primarily as switches, though thyristor amplifiers have been built.

Figs. 1 and 2 depict the differences between the thyristor and the triac. In Fig. 1, the thyristor is turned on or "triggered" by applying a small positive voltage to the gate. The device will then pass a large current at high voltage in one direction only, thus acting as a rectifier if the current being controlled is a.c. Once a thyristor is triggered, the gate current can be turned off and the device will continue to conduct between anode and cathode until the current flowing across these terminals drops below a certain level, typically 30 to 60mA. This is the "holding" current.

When a thyristor is used to control d.c., once triggered, it latches on and another switch is needed to reduce the anode to cathode current to below the holding current. For a.c. or pulsed d.c. control, the thyristor will, of course, turn off after the first positive half cycle unless it is triggered again.

The triac is rather like two thyristors connected back-to-front and in parallel with a common gate terminal, though this analogy is not entirely accurate. The triac will conduct in both directions and the triggering voltage at the gate can be either positive or negative.

In the thyristor, the gate current flows out of the cathode and this terminal is the reference point for voltage ratings. Because the triac is bi-directional, it does not have a cathode; the equivalent reference point is "main terminal one" ( $Mt_1$ ) and the equivalent of the thyristor's anode is "main terminal two" ( $Mt_2$ ) in the triac.

In mains supply applications, it is normal to connect  $Mt_2$  to the live terminal via the load, whilst  $Mt_1$  goes to neutral.

There are four triggering modes for a triac since it will conduct when  $Mt_2$  is positive or negative, regardless of the polarity of the gate signal. Fig. 2 shows the triac in its four triggering modes. Note that a lot more gate current is required to trigger it in the III+ mode. Some triacs are also slightly insensitive in the I- mode.

Table 1 shows how thyristors and triacs perform as switches in comparison to other common devices. Note that they far outperform the power transistor in these duties; a thyristor gate current of 150mA can switch 2500A whilst the same current flowing into the base of a power transistor would scarcely control more than a few amps!

Moreover, the thyristor is inherently a high voltage device and doesn't have the secondary breakdown limitations of the power transistor, thus it can control very high currents and voltages simultaneously. For instance, whilst a transistor might be able to control either 500V at 5A or 50A at 7V, but not 500V at 50A, thyristors are readily available which can handle 2500A at 1300V!

## Device Ratings

Before considering how to protect a triac or thyristor it is helpful to understand the significance of the manufacturer's data, notably the special voltage and current ratings which allow thyristors and triacs temporarily to accommodate special circuit conditions.

**Average current**  $I_{T(AV)}$  applies to thyristors only. This is the maximum *average* current that can be passed through the device on a recurrent basis without overheating and destroying the junction. This figure usually assumes a

Fig. 1:


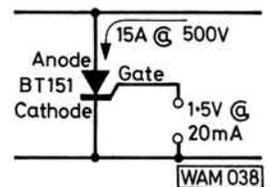


Fig. 2:

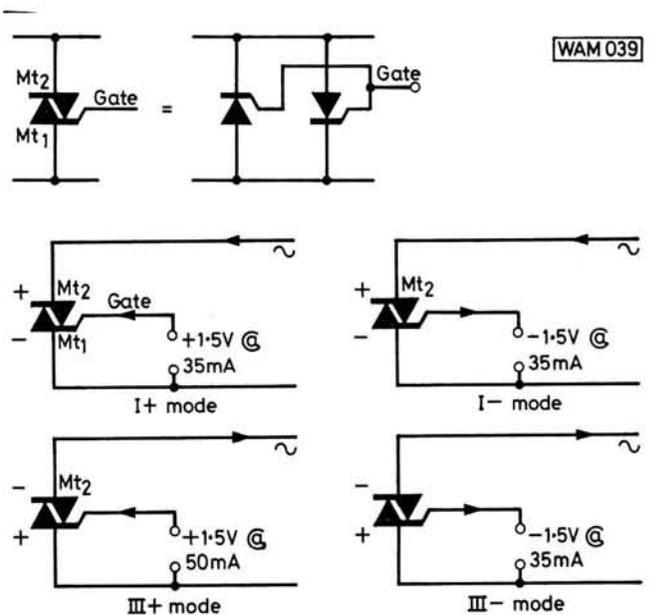

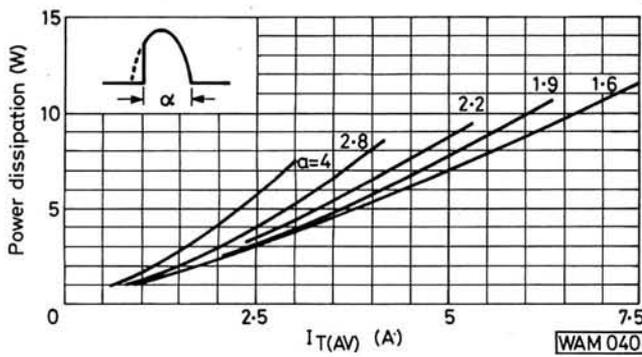


Fig. 3:

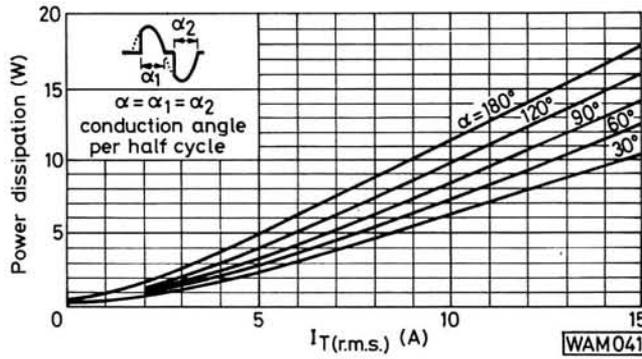


Fig. 4:

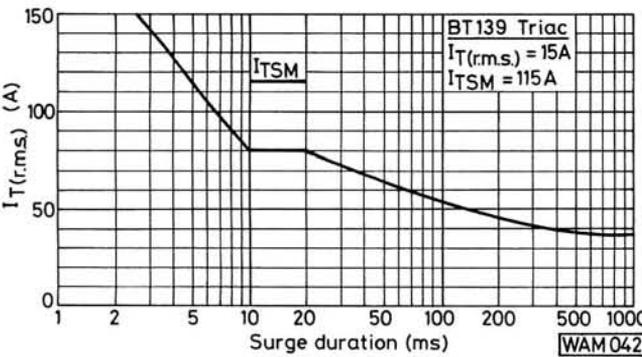


Fig. 5:

Table 1

	Triac Thyristor or Solid State Relay	Power Transistor	Electro- mechanical Relay	Contactors or Switch
Power Handling	Very high	Very low	Medium	Very high
Turn-off Time	Very fast	Fast	Medium	Slow
Current to Hold Switch ON	Low	High	Medium	Low or zero
Power Dissipation	Low	High	Very low	Very low
Switching Speed	Very high	Medium	Low	Very low
Electrical Robustness	High	Low	High	High

180° conduction angle, that is, the thyristor conducts throughout the whole of a half cycle. Fig. 3 is a typical graph showing  $I_{T(AV)}$  against power dissipation for various conduction angles. Note that as the conduction angle decreases, the power dissipated increases or the  $I_{T(AV)}$  rating falls.

**RMS current,  $I_{T(RMS)}$ .** This rating applies both to thyristors and triacs. For thyristors, however, this rating is usually only of significance if the waveform being switched is not sinusoidal, in invertors for instance. In this case the current could exceed the r.m.s. ratings yet be within the average rating. This is especially true when high peak currents are applied at low duty cycles. If you have to switch such a waveform, it's necessary to find out its shape and value and then to calculate the equivalent r.m.s. value of the pulse. For triacs,  $I_{T(RMS)}$  is the general current rating and a graph of this parameter against power dissipation is often given (Fig. 4). This graph differs from the preceding one in that a smaller conduction angle allows more current to be safely passed or reduces the power dissipation. If a thyristor data sheet doesn't give the  $I_{T(RMS)}$  value, it can be found from the expression:— $I_{T(RMS)} = (1.55 \times I_{T(AV)})$ .

**Non-repetitive peak current,  $I_{TS}$ .** is usually shown as a graph (Fig. 5). It may be either an average or a peak rating, and varies according to the duration of the current surge. Closely related is the  $I_{TSM}$  rating. This is the *absolute maximum* current a device can withstand over a half cycle at mains frequency, therefore 8.3ms for American devices (60Hz) and 10ms for British devices (50Hz). The  $I_{TSM}$  rating is particularly useful for fuse selection. A current which approaches the  $I_{TS}$  or  $I_{TSM}$  values will cause the junction temperature to rise close to its limits and until the device has cooled down many of its ratings will be invalid. Furthermore, a thyristor's characteristics may be permanently degraded or the device may fail if this catastrophic condition occurs regularly. Thus the  $I_{TS}$  and  $I_{TSM}$  ratings should only be used to accommodate unusual circuit conditions, such as short circuits. *The interval between surges does not change the  $I_{TS}$  rating.*

The thyristor has a forward blocking and a reverse breakdown voltage. The triac, on the other hand, because it conducts in both directions, can only have a forward blocking breakdown voltage. For thyristors only, the reverse voltage ratings are:

**Continuous peak reverse voltage,  $V_{WRM}$ .** is the maximum *continuous* peak reverse voltage allowable across a thyristor, for 240V mains, for example, the  $V_{WRM}$  must be  $240\sqrt{2}$  or 340V; 400V is the nearest standard value here.

**Repetitive peak reverse voltage,  $V_{RRM}$ .** is the rating that takes into account any regular, but not *continuous*, transient voltage peaks that occur across a thyristor. In an inverter, for example, a small amount of ringing may cause the peak voltage to rise by 20 per cent for a few milliseconds in each cycle. Provided this voltage does not exceed the  $V_{RRM}$  rating, the device will not be harmed.

**Non-repetitive peak reverse voltage,  $V_{RSM}$ .** is the *absolute maximum* voltage ratings which a thyristor can withstand for short time periods, usually 10ms. It shows a thyristor's ability to withstand occasional transient voltages which are *not regular and inherent in the equipment*, for example, those originating in the mains supply.

These ratings have corresponding forward equivalents which also apply to triacs using the subscript "D". The forward equivalent of  $V_{WRM}$  is  $V_{DWM}$ , likewise  $V_{RRM}$  becomes  $V_{DRM}$  in the forward direction and  $V_{RSM}$  becomes  $V_{DSM}$ . Sometimes these ratings are equal, e.g.:— $V_{WRM} = 400V = V_{DWM}$  and sometimes continuous and repetitive voltage ratings are equal, for instance,  $V_{WRM} = V_{RRM}$ . Reverse breakdown in a thyristor will at best cause

degradation of the device's characteristics and at worst failure will result. Forward breakdown in a thyristor or triac need not cause failure if the current is limited. Nevertheless, it is advisable to prevent forward breakdown whenever possible.

The multiplicity of voltage and current ratings for these devices need not cause confusion. It will be seen later that a  $V_{RSM}$  of 800V is often needed when mains operated thyristors are fused. These will also need a 400V  $V_{RWM}$  rating, and we simply need to look for the cheapest device which satisfies both conditions. To meet the  $V_{DSM}$  rating will often entail using a device with a 600 or 700V  $V_{RWM}$  rating, but this is quite in order. In a similar fashion, with current ratings, we may need an  $I_{TSM}$  of only 100A and an  $I_{TS}$  of over 20A; the fact that a 25A triac will have a 250A  $I_{TSM}$  rating is pure generosity!

## Miscellaneous Ratings

**Rate of rise of off-state voltage,  $dv/dt$**  shows how fast a waveform a device can handle without turning on accidentally. Apart from applying a signal to the gate, a thyristor or triac can also be turned on by applying a rapidly rising voltage to the anode. A typical maximum  $dv/dt$  for a 25A triac is 100V/ $\mu$ s. The application of a waveform which rises more quickly than this may turn the triac on. Like forward breakdown, this effect is undesirable solely because the device loses control and may be damaged by suddenly conducting large currents. The circuit in Fig. 6 may be used to demonstrate  $dv/dt$  turn-on. If the switch is

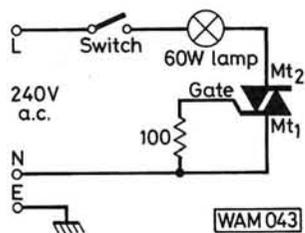


Fig. 6:

flicked rapidly, the lamp will light occasionally, even though there is no gate signal. Contact bounce in relays, contactors and other switches frequently cause this effect if switch-on happens to occur at the peak mains voltage. Thyristors invariably have better  $dv/dt$  ratings than triacs and are often connected back-to-back to provide bi-directional power control when high  $dv/dt$  ratings are required. Thyristors and triacs have other  $dv/dt$  ratings which concern commutation but these need not worry us here.

**Rate of rise of on-state current,  $di/dt$** , concerns the inability of a triac or thyristor to turn on instantaneously. Initially, only a very small area of silicon is conductive, though within a few microseconds the whole area of the device conducts. A current which rises to its maximum value very rapidly and reaches a high value before the whole area of the device is conductive will pass through the very small area of silicon which conducts initially. This results in overheating which can destroy the device. A typical maximum  $di/dt$  rating for a 25A triac is 50A/ $\mu$ s. Although turning on a device by exceeding its  $dv/dt$  rating is not in itself harmful, some circuit faults can cause  $dv/dt$  breakdown in a device, which in turn causes sudden conduction of rapidly rising currents. Thus  $dv/dt$  breakdown can precipitate  $di/dt$  breakdown and the result is a dead triac.

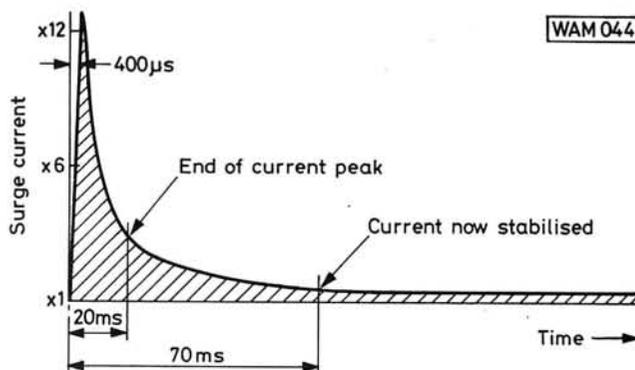


Fig. 7:

## Surge Currents

These occur when motors, incandescent lamps and capacitors are initially energised. Starting surges in motors are due to the initial lack of back e.m.f. — only the inductance and resistance of the motor windings limit the current when a motor starts from rest. The filament of an incandescent lamp runs at some 2600°C. At this temperature the resistance of the tungsten filament is 9–20 times higher than at 20°C. The current in lamps and capacitors stabilises quite quickly, usually within a few tens of milliseconds in the case of a lamp.

Motor surges, however, can have a duration of hundreds of milliseconds or longer. Table 2 shows the duration and magnitude of typical current surges in lamps and motors. Fig. 7 is a graph of a typical lamp surge current. Note that the current does not rise to its maximum value instantaneously because of circuit and lamp inductance. A similar graph for a motor can usually be obtained from the manufacturer. The main difference is that motors usually have high inductance, therefore the surge current rises quite sluggishly. A peak motor surge current is also lower than that arising from lamps, but the surge duration is 10 to 100 times greater.

Table 2

Component	Typical peak current magnitude	Typical duration of surge
100W incandescent lamp	$\times 13$	70ms
1000W incandescent projection lamp	$\times 18$	100ms
Shaded pole motor	$\times 1.5$	2 seconds
Series a.c.-d.c. motor	$\times 2.5$	100–400ms
Split-phase motor	$\times 4-6$	100–500ms
Capacitor start motor	$\times 4$	100–600ms
Induction motor	$\times 7$	750ms
Three-phase motor	$\times 3.5$	170ms

Because these surges are *inherent and normal* in any circuit controlling lamps or motors, the surge current must not exceed the  $I_{TRM}$  rating of the device. This rating refers to surges of short duration only, however, and it is advisable in addition to check the  $I_{TS}$  rating of the device (Fig. 5). Sometimes a surge current graph is given in the data sheet; this is intended specifically for these conditions. The  $I_{TS}$  curve shows the maximum *non-repetitive* current against the duration of the current. In Fig. 8, the  $I_{TS}$  curve has been plotted for a 15A plastic triac. The  $I_{TRM}$  rating is also shown, together with the surge curves for 3 sets of 100W lamp arrays, consisting of ten, twenty and thirty lamps respectively. The thirty lamp (3000W) load exceeds the  $I_{TRM}$  and a triac controlling these lamps would rapidly fail. The 2000W lamp surge is below the  $I_{TRM}$  limit, but goes above the  $I_{TS}$  curve for 1ms (point A). This is not really satisfactory. The 1000W lamp load is well below both the  $I_{TS}$  curve and the  $I_{TRM}$  rating, thus the triac would handle this load quite happily. An examination of the graph will show that the maximum lamp load the triac can handle without the lamp surge curve encroaching on the  $I_{TS}$  curve is around 1500W, or 6.25A. This is approx-

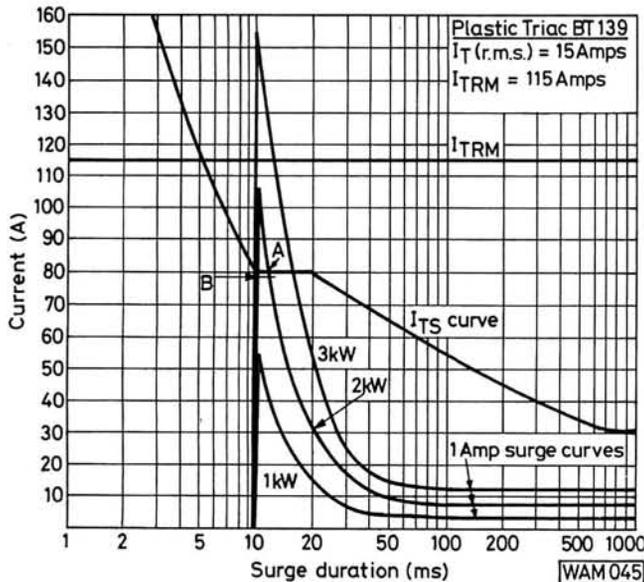


Fig. 8:

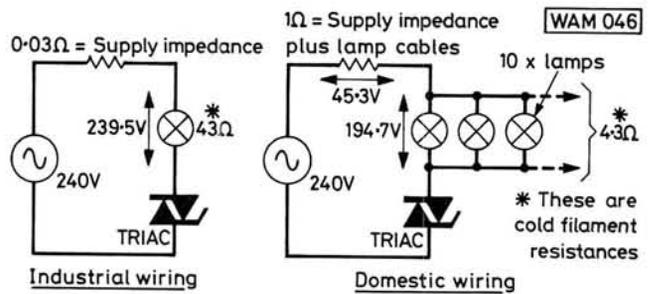


Fig. 9:

imately 50 per cent of the triac's  $I_{T(RMS)}$  rating (15A).

Thus we arrive at the rule of the thumb "derate triacs or thyristors by 55 per cent for lamp loads." However, it is always a good idea to check a triac's suitability by drawing a graph of the form shown in Fig. 8, especially when high-power incandescent lamps are to be handled.

The lamp surge curves in Fig. 8 give a conservative idea of the triac's capacity in many domestic applications. Fig. 9 shows why this is so. In industrial wiring systems, the supply impedance seen by the lamp is often very low because the control circuitry is likely to be wired directly into the mains, possibly close to a 100 or 300A distribution point. In this case, the impedance of the mains cables will be mainly resistive and will be possibly as low as 0.03Ω. The cold resistance of a 100W lamp filament is 43Ω. The total resistance is then  $43 + 0.03 = 43.03Ω$ . Here the supply impedance will have a negligible effect on the surge current. However, domestic wiring may have an impedance of 1Ω and the effect on the lamp surge current can be significant, particularly when large currents are drawn.

If we connect ten 100W lamps in parallel, the total (cold) filament resistance will be 4.3Ω and the 1Ω supply impedance will then reduce the peak lamp surge current by around 20 per cent or 10A! If we take the impedance of connecting cables into account, the surge current will be reduced even more.

So far we have circumvented lamp surges by selecting triacs with suitable  $I_{TRM}$  and  $I_{TS}$  ratings. We can also use a thermistor to limit the lamp surge; this approach is com-

continued on page 52 ▶▶▶

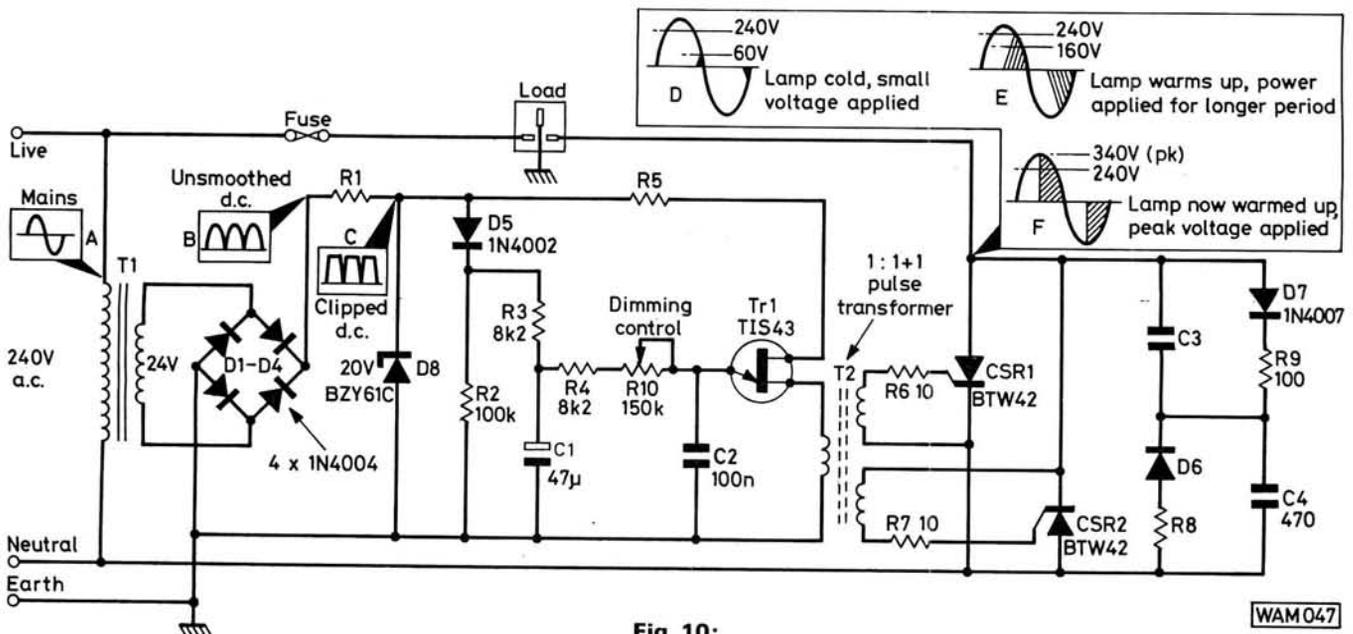


Fig. 10:

# AMATEUR ELECTRONICS UK



Your number one source  
for **YAESU MUSEN**



## FT-707 All solid-state HF mobile transceiver

The definitive HF mobile rig, digital, variable IF bandwidth, 100 watts PEP SSB. Latest WARC bands, AM, CW (Optional 12 channel memory VFO).

**£529<sup>00</sup>**



As factory appointed distributors we offer you - widest choice, largest stocks, quickest deal and fast sure service right through-

### FT-707 In base station format



FC-707 £80<sup>50</sup>    FP-707 £109<sup>25</sup>  
FV-707DM £186<sup>30</sup>

Here we show the 707 together with the matching FP-707 PSU, FC-707 ATU and FV-707DM VFO memory.

### FRG-7 General coverage receiver



A precision built high performance Wadley Loop receiver, rugged and reliable - proved by the tens of thousands in use around the globe.

**£199<sup>00</sup>**

### FRG-7700 Synthesized general coverage receiver



The very latest in receiver technology from YAESU. Receives AM (3 band widths), USB, LSB, CW and FM - memory option with 12 channels and automatic band selection.

(With Memory £389) **£309<sup>00</sup>**

ALL PRICES INCLUDE V.A.T.

## Amateur Electronics UK

508-516 Alum Rock Road - Birmingham 8

Telephone: 021-327 1497 or 021-327 6313

Telex: 337045

As from March 1st, our new opening hours are 9.30-5.30 Tues. to Sat. continuous and CLOSED all day Monday.

### AGENTS

NORTH WEST - THANET ELECTRONICS LTD, GORDON, G3LEQ, KNUITSFORD (0566) 4040.  
WALES & WEST - ROSS CLARE, GW3NWS, "GLENVIEW" NEWPORT ROAD, MAGOR, GWENT (0633) 880 146.  
EAST ANGLIA - AMATEUR ELECTRONICS UK - EAST ANGLIA, DR T. THIRST (TIM) G4CTT, NORWICH 06925 865  
NORTH EAST - NORTH EAST AMATEUR RADIO, DARLINGTON 0325 55969  
SOUTH EAST - AMATEUR ELECTRONICS, UK - COASTAL, CLIFTONVILLE, KENY KEN McINNIS, G3FTE, THANET (0843) 291297, 9 a.m. - 10.30 p.m.

### Drake R-7 Synthesized, General Coverage Receiver



#### Model 1240

Full general coverage reception, 0-30 MHz, with no gaps or range crystals required.

Continuous tuning all the way from vlf thru hf. Superb state-of-the-art performance on a-m, ssb, RTTY, and cw - and it transceives with the Drake TR-7.

**Price £879.75**



#### R1000 £285.20 inc VAT

The R-1000 is a high class general coverage receiver covering 30 bands between 200KHz and 30MHz with a PLL synthesizer that incorporates all of Trio's sophisticated electronic technology developed over recent years.

Both digital display readout (1KHz resolution) and analog display (10KHz resolution) are provided for easy and accurate tuning.

The R-1000 also includes a quartz digital clock with timer, three IF filters, RF ATT and tone control, etc. to ensure the best receiving conditions for each mode.

Due consideration has been given to innovative design and compactness, making the R-1000 an incomparable station receiver for amateur radio operators, professionals, BCL's and SWL's, etc.

## THE 2 METRE FM MOBILE TRANSCEIVER

### TR7800 £268 inc VAT



The new TR7800 is the only 2 metre FM mobile transceiver. Its performance both in your car and shack has to be experienced to be believed. Power output is 25 watts, a needle bending signal. The rig has keyboard entry for fixed station use and for programming the 15 memories. When used with the up/down shift switch on the mike the 15 memories, each having a repeater shift facility, make mobile operation a sheer pleasure. The scan facility, both on memory and 25/5Kc on keyboard means no missed contacts. Five second hold on each occupied channel gives you time to identify the station before the rig moves on to the next QSO, press the mike switch and the scan instruction is cancelled. Add the priority facility and you have it, the only 2 metre FM mobile rig.


#### Bearcat® 220FB

*With 4m, 2m & 70cm FM Amateur Bands*

FREQUENCY COVERAGE . . . 66-88MHz FM; 118-136MHz AM (Aircraft Band); 144-174MHz FM; 420.45-512MHz FM. This coverage includes the 70cm; 2m; 4m FM AMATEUR BANDS. To programme this Receiver you simply punch in the frequencies you wish to monitor. To AUTOMATICALLY SEARCH MARINE FREQUENCIES YOU JUST PRESS ONE BUTTON. The Bearcat 220FB will also AUTOMATICALLY SEARCH the AIRCRAFT BAND.

Power requirements: 240v AC/12v DC. Accessories included in the price are Mounting bracket and hardware, DC cord and telescoping antenna.

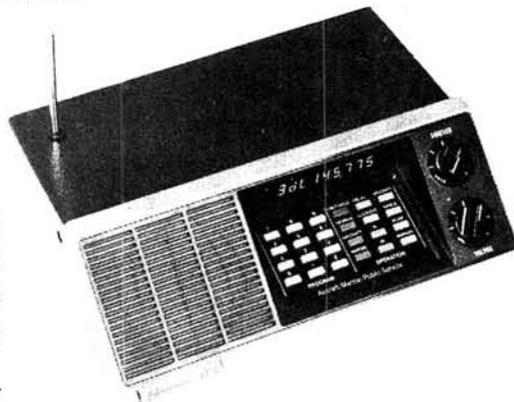
**£258.75 inc VAT. Delivery by Securicor**



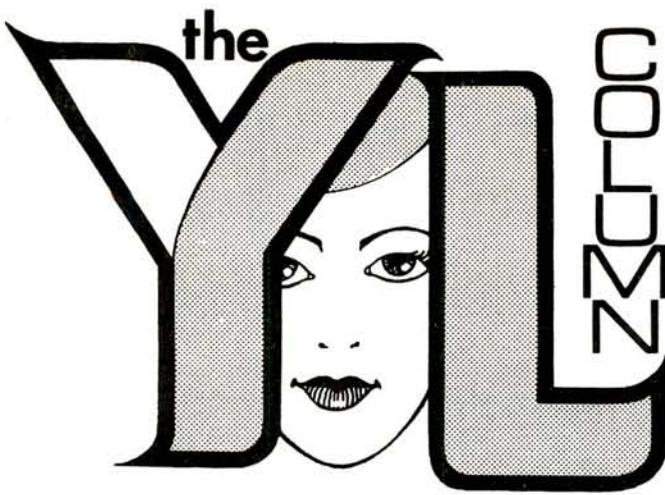**Importers & Distributors for Hy-Gain, CDE, Rockwell-Collins, Macrotronics Bencher, R. L. Drake, Ten-Tec, A E A, Bearcat, stockists of all Amateur & Computer Products**

**RADIO SHACK LIMITED**  
TELEX 23718

188 BROADHURST GARDENS, LONDON, NW6 3AY  
**TELEPHONE 01-624 7174**



Elaine HOWARD G4LFM



At least I can start this month's column with some good news (for me anyway). The result of the December RAE was favourable and I am now the proud owner of the call G4LFM, and a new 2m rig.

I was pleased to hear via Eric in "On the Air" in the April issue that the last YL Column was read by at least one other YL, so thanks for the encouragement. Writing the first column was easy, it's filling up the space the second time that proves difficult.

My call sign arrived the morning of writing this and whilst I was ripping open the envelope with the awaited news I was switching on my rig with the other hand. Not that I was eager to get on the air! It was just that over the past few weeks, since I bought the rig, everyone else has been trying it for me, to see that it operates properly. I wasn't sure whether anyone would be listening, it was rather early in the morning for most people, and if they were listening would I get things right. Fortunately all went well and my first contact was established.

Getting used to my own callsign is quite difficult, I can always think of everyone else's and not my own. Imagine

being half way through a QSO and forgetting my callsign, I'd never be allowed to live it down in the office. So if I keep repeating it to myself eventually it should sink in. The fact that I passed the exam is only now beginning to register, it is hard to adjust to the idea that I actually passed, not the miserable failure that I was convinced would be the result.

After spending some time being unable to transmit, due to the lack of a licence, now it is perfectly legal I feel very guilty as soon as I start transmitting. Perhaps it will wear off in time, as I get more at ease on the practical side of the hobby.

I have heard of one new YL with a nice call sign, it is G8ZYL, I haven't actually worked her yet, I didn't have my callsign at the time. I would like to hear from any others who have new callsigns, interesting or otherwise. I am gradually compiling a list of YLs but the 1981 call book only goes as far as the G8Ws, so I would be grateful to hear from any others.

## PW "WINTON" TUNER

As announced in our April issue, we have run into difficulties with this project due to the a.m. tuner module being discontinued by the manufacturer.

In drawing up the specification for this tuner, the aim was to provide a design with a similar high standard of performance and facilities to the PW "Winton" amplifier, yet capable of being put together by a home constructor without access to sophisticated test equipment. This meant that pre-aligned tuner modules were essential, but unfortunately the result is that we were of course dependant on the continued availability of the chosen modules.


The a.m. tuner head selected seemed to provide the best combination of performance and facilities of all

those available. Enquiries have been made on a world-wide basis to try to locate any remaining stocks, but without success. The question of a suitable substitute has been investigated, but there is nothing else which could be used without a complete redesign of a large part of the PW "Winton" tuner. We have reluctantly come to the conclusion that this is not economically viable, but we are continuing to look for some other solution.

We apologise for the disappointment this delay will cause our readers. It is no less disappointing and frustrating for the author and ourselves, especially in view of the large amount of time and money which had already been devoted to the project.



# COMPUTERS IN RADIO

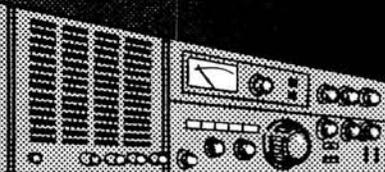

## INTRODUCING THE MICROCOMPUTER — 1

by Mervyn J. Axson BA G8WHG

From conversations heard over the air, a lot of radio amateurs are becoming interested in microcomputers. This is not surprising because they have a lot in common with radio and they can go together very well. No doubt there are a lot more people who would be interested if only they could penetrate the jargon. A lot of published material is not very helpful in this respect, for all too often you become enmeshed in binary arithmetic in the second paragraph and Boolean Algebra soon follows. This is not necessary at all. It is like starting a learner driver off by giving a talk on the theory of heat engines. You don't have to know what is happening inside a computer in order to use it. So we will adopt the "Black Box" approach and just accept that certain actions produce certain results.

There are three essential components in any computer system. These are: a means of getting information into it (input peripheral or i.p.), something to perform operations on the information (central processing unit or CPU) and some way of getting details out (output peripheral or o.p.). With microcomputers the i.p. is invariably a keyboard of some type and the o.p. is usually a c.r.t. screen known as a Visual Display Unit or VDU. These and the CPU may come in separate cases or they may all be packaged in one unit, it makes no difference. There can be other types of i.p. and o.p. devices in a complete system, but these are the essentials. We can deal with the others as the need arises.

How do we use a computer to solve a problem? You are sitting in front of the keyboard watching a little symbol flashing on the VDU. This is known as the cursor. Before you can solve any problem the computer must be programmed. Now there is more mystique about that simple word than almost any other. And yet there need not be, for a program is simply a list of instructions telling the computer what to do. The trouble arose because you have to use a very special language, known as machine code, to talk to the CPU. This varies from machine to machine and is always a very precise and complex code. It does take a great deal of experience and a lot of time to write successful programs in machine code.

Fortunately, the very clever people who made the first computers soon realised how this would limit their use, so they made good use of the power of the computer. They wrote a program which is stored inside the CPU which lets you type instructions in a recognisable form and which then translates these into the machine code. I said that they were clever! There are so many different ways that you can express instructions in English that some rules had to be made if these interpreters were to work properly. These rules form the basis of what is called a high-level language, and there are a number of these such as COBOL, ALGOL, FORTRAN, PASCAL, etc., but the most popular for microcomputers is BASIC. Some professionals criticise BASIC but for our purpose it is very good. Programs written in it are fairly easy to read, and it

is an easy language to learn. By the time you have finished reading this article you will be able to write simple programs in BASIC.

Rather than just giving a list of the rules making up BASIC, we will write some simple programs so learning as we go. We have said that a program is a list of instructions, which are called Statements. BASIC requires that the Statements shall be numbered in ascending order, and they will be carried out or executed in that order. Note that the numbering does not have to be consecutive. It does not matter whether they are numbered 1, 2, 3 or 100, 200, 300. This is very useful in developing a program because if we want to add a Statement between two existing ones we simply give a number between and BASIC will put it between. For example, a later Statement numbered 150 will be inserted between 100 and 200.

## Writing Programs

So to start writing. Let us make a simple program to carry out the calculations for Ohm's Law,  $V = IR$ . We need to tell the CPU what the values of  $I$  and  $R$  are, so the first two lines of the program are INPUT Statements.

```
400 INPUT I
410 INPUT R
```

Now we have to tell it to multiply  $I$  by  $R$  to get the value of  $V$ . Note that the sign for multiply in BASIC is "\*" and not "x". This uses the LET Statement.

```
420 LET V = I * R
```

Now we want it to give us the answer. Output is made with the PRINT Statement.

```
430 PRINT V
```

And that is the program completed! Type each line on the keyboard and you will see it displayed on the VDU. As you finish the line press the RETURN key. This tells the CPU that you have finished that line, which it then stores in its memory. When this has been done, the cursor moves down to the next line.

Having completed the entry of the program, we now have to tell the CPU to act on it and for this we use a COMMAND Statement. These are not numbered, and are not stored in the machine, but are acted on at once. So type RUN followed by the RETURN key, and the CPU will immediately ask for the input of  $I$ . It indicates this by printing a question mark on the screen. As soon as you have typed in a value, say 2, it will ask for  $R$  by printing another "?". Type in this value, say 4, and the CPU immediately prints the answer, 8, on the screen. So the program works. Alright, it is not really very useful at this stage, but we can do a lot to improve it. Any program that is of real use is made up of two parts. One that solves the problem and one that makes the program versatile and

easy to use. For example, it is not very informative just to flash "?" on the screen. What input is required? INPUT Statements allow us to say what is expected, simply type the details between quote marks.

```
400 INPUT "CURRENT IN AMPS"; I
```

Similarly for line 410 and also for the output

```
430 PRINT "VOLTAGE IS"; V; "VOLTS"
```

We can improve the clarity by spacing. A simple PRINT Statement will give a line space between the questions.

```
405 PRINT
```

We may want to carry out another calculation. We could of course type RUN again, but a GOTO Statement will send the CPU back to the start automatically. Of course it would then be neater to clear the screen. PRINT CHR\$(147) will achieve this, and as we don't want it to happen before we have read the previous answer we put line 535 in to temporarily stop execution of the program.

It would also be nice to say what the program does and to start with a clear screen, so we add lines 100 and 110.

```
100 PRINT CHR$(147)
110 PRINT "OHM'S LAW"
535 INPUT "TYPE 1 TO CONTINUE"; A
540 PRINT CHR$(147)
```

We now have quite a tidy program, but a glaring omission is that although called Ohm's Law it only deals with  $V = IR$ , what about  $I = V/R$  and  $R = V/I$ ? Obviously we can add more lines to cater for these, but we must also allow the user to select the desired formula. A neat way of doing this is to present a "menu" from which the user can make his choice. We can easily do this with a series of PRINT Statements.

```
200 PRINT "MENU"
210 PRINT
220 PRINT "OPTIONS AVAILABLE"
230 PRINT
240 PRINT "1. GIVEN I & R FIND V"
250 PRINT
260 PRINT "2. GIVEN I & V FIND R"
270 PRINT
280 PRINT "3. GIVEN R & V FIND I"
290 PRINT
300 PRINT "4. FINISHED WITH PROGRAM"
```

This is fairly straightforward, but we now have to decide how to tell the CPU what the answer is.

Fortunately our clever friends thought of all kinds of problems, and provided Statements which can be adapted to all needs. In this case it is an extension to the GOTO and is the ON -- GOTO ----. Firmly believing that an ounce of practice is worth a ton of theory, and that by now you are getting to grips with the way things work, let us do the necessary coding. After setting up the "menu" we proceed.

```
310 PRINT
320 INPUT "TYPE NUMBER OF YOUR CHOICE"; I
330 ON I GOTO 400, 500, 600, 700
```

We know we have the formula for case 1 starting in line 400, so we put the formula for case 2 starting in line 500, case 3 in line 600 and case 4 in line 700. Depending on the number chosen, the program will proceed directly to the appropriate formula.

We now have a simple program but it does have quite a sophisticated looking output. Exactly the same methods could be adapted to other types of problems involving the use of formula. Simply change the parameters and equations as required. Of course, programming can be more complicated, but the methods of solution are the same. A bit of logical thinking about the problem will reveal a

```
Listing of Ohm's Law program.
Mervyn J. Axson BA 68WHG. 02.10.80.
100 PRINTCHR$(147)
110 PRINT"OHM'S LAW"
120 PRINT
200 PRINT"MENU"
210 PRINT
220 PRINT"OPTIONS AVAILABLE"
230 PRINT
240 PRINT"1. GIVEN I & R FIND V"
250 PRINT
260 PRINT"2. GIVEN I & V FIND R"
270 PRINT
280 PRINT"3. GIVEN R & V FIND I"
290 PRINT
300 PRINT"4. FINISHED WITH PROGRAM"
310 PRINT
320 INPUT"TYPE NUMBER OF YOUR CHOICE";J
330 PRINTCHR$(147)
340 ON J GOTO 400,500,600,700
400 INPUT"CURRENT IN AMPS";I
405 PRINT
410 INPUT"RESISTANCE IN OHMS";R
415 PRINT
420 LET V=I*R
430 PRINT"VOLTAGE IS";V;"VOLTS"
440 INPUT"TYPE 1 TO CONTINUE";A
450 PRINTCHR$(147)
460 GOTO 200
500 INPUT"CURRENT IN AMPS";I
505 PRINT
510 INPUT"VOLTAGE IN VOLTS";V
515 PRINT
520 LET R=V/I
530 PRINT"RESISTANCE IS";R;"OHMS"
540 INPUT"TYPE 1 TO CONTINUE";A
550 PRINTCHR$(147)
560 GOTO 200
600 INPUT"RESISTANCE IN OHMS";R
605 PRINT
610 INPUT"VOLTAGE IN VOLTS";V
615 PRINT
620 LET I=V/R
630 PRINT"CURRENT IS";I;"AMPS"
640 INPUT"TYPE 1 TO CONTINUE";A
650 PRINTCHR$(147)
660 GOTO 200
700 PRINT"FINISHED"
710 END
READY.
```

possible solution. Flow charts are often a great help. Once this stage has been reached it is a fairly straightforward procedure to code the instructions in BASIC. With very little practice quite considerable skill is acquired. One warning, though, the process is addictive and may divert from all sorts of other things including Amateur Radio!

*to be continued*

# PW 'STOUR' TOP-BAND TRANSCEIVER

## PART 1

David G. BARRELL G4BMC



Now that 160m has been confirmed as an amateur band at the 1979 WARC there seems to be an upsurge in activity using this band. The author required an s.s.b. transceiver for 160m to use in a caravan when on holiday in Wales. The commercial transceiver, which had been used for this purpose until recently, had several shortcomings.

Firstly, when in a farmer's field with very little man-made noise and a large  $\frac{1}{2}\lambda$  antenna, it did not cope with strong signals as well as one would have liked. Secondly, the current drain was alarming. Although there are now commercially available solid state units that cover 160m it was decided to "have a go" at building a rig which was more economical on current consumption during receive, and possessing a larger dynamic range with good signal handling capabilities.

It must be stated at the outset that the author is not professionally qualified and neither is he weighed down by superb test equipment. A g.d.o., d.c. meter and test oscillator (not a commercial signal generator) represented all that was available.

As several other people had shown more than a passing interest in the project it was decided that the various circuits should be as repeatable as possible.

To this end, and after many preliminary trials with various circuits, it became clear that one of the problems was the varying gains between different transistors of the same type number. A standard broad-band amplifier is used in many situations with a large amount of feedback, including an un-bypassed emitter resistor. This was used throughout the transceiver designs and the results after this method of approach was adopted proved extremely effective. The un-bypassed emitter resistor in each stage was found to be an easy method of setting the various gains in each stage and it is strongly advised that they are strictly adhered to.

Initial tests of the PW Stour prototype were carried out by using a Yaesu FT101B as the main piece of "test gear", but grateful thanks go to G4CEN who performed the rather more stringent tests and whose figures are quoted at the end of this article.

Because of the limited test equipment, modular construction was decided on. All sections were built and tested in such an order that simple functional tests could be performed without additional test gear.

The original front end of the receiver consisted of a

40673 r.f. amplifier feeding a diode mixer. After two months and about six printed circuit boards, this idea was given up. The cross-mod performance was, at its best, only as good as the commercial transceiver.

A design was then found using a pair of v.h.f. transistors in a broad-band push-pull circuit. This was quickly knocked up, and the results obtained were greatly improved. Similarly, the original p.a. used tuned circuits and worked quite well using a single 2N5591. However, being converted to broad-band techniques by the receiver front end success, a much more stable p.a. was evolved by adopting a similar approach.

Diode switching was used wherever possible to save the inevitable bulk of wiring associated with relay switching. Pin diodes were used for this purpose and although various articles have suggested the use of silicon switching diodes as a cheaper alternative, the author cannot comment on their effectiveness as they have not been tried.

## CONSTRUCTION RATING **Advanced**

### BUYING GUIDE

All components required for the construction of this project should be available from suppliers advertising in the magazine. Buying information will be provided in subsequent issues as appropriate.

APPROXIMATE  
COST **£185**

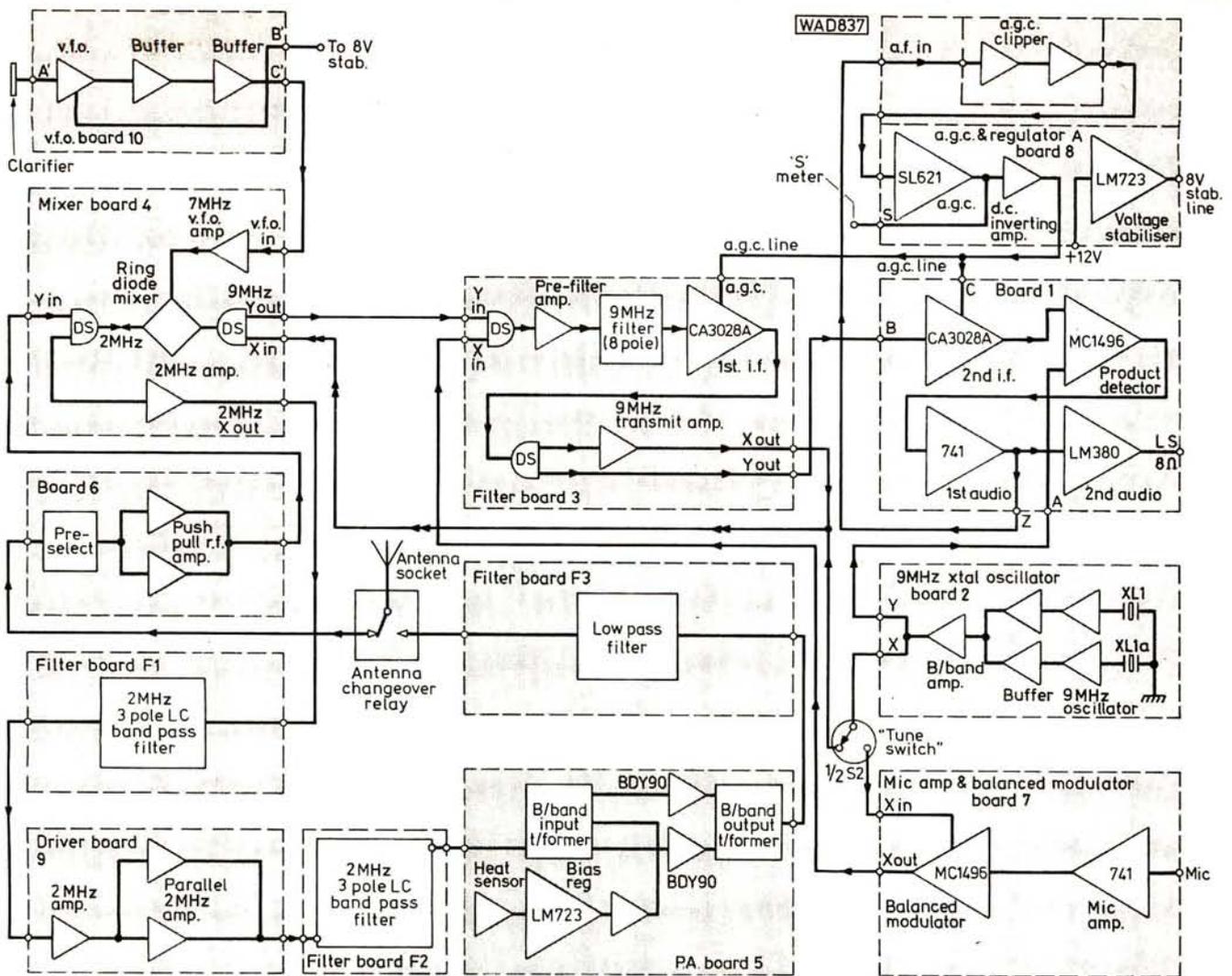


Fig. 1: The full block diagram of the PW Stour transceiver

## Circuit Description—Receiver

(Refer to the functional block diagram of the transceiver shown in Fig. 1.)

The v.f.o. frequency is variable in the range 7–7.500MHz, with separate control of the receiver frequency available over a plus or minus range of 2–3kHz. The v.f.o. obtains its supply from an eight volt stabiliser.

Signals from the antenna are passed through a 2MHz filter and are then amplified by the push-pull front end before being fed to the mixer.

The v.f.o. output is fed to the mixer board where it is amplified by a broad-band amplifier before being fed to the doubly balanced diode mixer. This mixer uses HP2800 hot carrier diodes.

Mixed v.f.o. and amplified signals produce a 9MHz i.f. output from the mixer. The importance of terminating the mixer output correctly is paramount. The circuitry L5, C23 forms a parallel tuned circuit providing high impedance at the resonant frequency of 9MHz. At other frequencies a 50Ω terminating impedance is effected by means of the resistor R20. C24 and L6 are also series resonant at 9MHz. The mixer input and output are diode switched for transmit and receive functions.

The 9MHz i.f. signals are then passed to the filter board where a single stage of amplification is introduced before the filter. This amplifier is run at a fairly high current to minimise the effects of cross-modulation. Signals then pass through the 9MHz filter and on through a CA3028A 1st i.f. amplifier. Transmit and receive selection on this board is also accomplished by diode switching.

The 9MHz i.f. undergoes a second stage of amplification, again a CA3028A, located on board 1. From here, signals pass to the product detector which uses an MC1496. This receives its carrier insertion from the 9MHz oscillator board (board 2).

Readers who intend to operate the Stour should be in possession of the appropriate licence issued by the Home Office to those who have passed the City and Guilds Radio Amateurs' Examination. Details may be obtained from: The Home Office, Radio Regulatory Department, Amateur Licensing Section, Waterloo Bridge House, Waterloo Road, London SE1 8UA.

The audio so produced is amplified by a 741 op. amp. and then by an LM380 to give adequate loudspeaker volume.

Automatic gain control is accomplished by the use of an SL621 a.g.c. system preceded by a clipper.

A relay is at present used to switch the antenna, the 12V/0V supplies required for the diode switching and the d.c. switching. Transistor switches could be used for the latter, but it was felt that as a relay was required for the antenna the spare contacts might as well be used to switch the necessary d.c.

Although not yet tried the only requirement on receive to produce a receiver on any amateur band between 160m and 10m is a change in v.f.o. frequency and one filter, with possibly more r.f. amplification on the high frequencies.

## ★ specifications

### GENERAL

Single conversion with 9MHz i.f.  
 Frequency Range: Transmit 1.8–2.00MHz.  
                           Receive 1.5–2.00MHz.  
 Modulation: A3J, upper and lower sideband (selectable). CW facility available.  
 Supply Voltage: 11.5–14V, 13.8V nominal.  
 Current Consumption: 500mA receive, 6A nominal peak transmit.  
 Frequency Stability: Less than 100Hz drift in any 30 minute period. (After initial warm up period at normal room temperature.)  
 Size: Case measurements 240mm deep x 190mm wide x 140mm high.

### TRANSMITTER

Input Power: 45–55 watts }  
 Output Power: 20–25 watts } 12–13.5V  
 Output Impedance: 50Ω  
 Microphone: High impedance, dynamic type  
 Out of Band  
 Spurious Radiation: 50dB down, on wanted signal at rated output. (80m output 50dB down, all other spurious >60dB down.)  
 Carrier Suppression: 45dB down relative to wanted signal.  
 In Band Ripple: 1.80–2.00MHz ±0.66dB.

### RECEIVER

Input Impedance: 50Ω  
 RIT: ±2.5kHz  
 Preselector Range: 1.50–2.00MHz  
 Filter: Centre frequency 9MHz.  
 Specifications: 8 Pole.  
                           Passband: 2.4kHz @ –6dB.  
   4.3kHz @ –60dB.  
 Audio Output: 1.5–2.00W (dependent upon supply voltage.)  
 Sensitivity: 0.3μV for 10dB S + N/N.  
 3rd Order Intercept: –14dBm.  
 Loudspeaker  
 Impedance: 8Ω

## Circuit Description—Transmitter

Audio signals from the microphone are amplified by a 741 operational amplifier which feeds into the MC1496 balanced modulator. The microphone gain is controlled by means of a potentiometer located on the printed circuit board. Carrier injection, at 9MHz, is obtained from the carrier oscillator board and the output from the MC1496 modulator (double sideband suppressed carrier) is passed to the filter board.

The filter board acts in the same manner on transmit as it does on receive, with one exception. After the output from the CA3028A, and via the diode switch, the 9MHz single sideband undergoes a further stage of amplification through the broadband amplifier 3T2. The resultant signal is then fed to the mixer board.

9MHz s.s.b. signals are mixed and converted to 2MHz by means of the doubly balanced mixer. Switching required during transmit and receive is again accomplished by the use of a pin diode switch. The mixer board also contains one stage of 2MHz amplification via 4T2, a standard broad-band amplifier. This amplifier is the first in the 2MHz amplifier chain and the gain of the whole chain may be adjusted by altering the value of the un-bypassed emitter resistor. At the level at which it has been set however, no instability has been encountered and it is recommended that this resistor remains unaltered unless full output cannot be obtained. The low level s.s.b. at the output of 4T2 is then passed to the drive board via a band-pass filter F1.

The driver board uses three stages: first stage being in Class A and the other two being in parallel, operating in Class A. The output from this board is at approximately 1 watt, which is then transferred to a second band-pass filter F2 and finally to the p.a.

The p.a. consists of a pair of BDY90 switching transistors which operate satisfactorily at 2MHz. (They should, in fact, be OK to above 9MHz as they have an Ft of about 90MHz.)


These transistors are operated in class B at an input of approximately 50 watts. The broad-band transformers were wound using partly trial and error techniques to obtain the turns ratios eventually used. The BDY90s seemed fairly rugged devices and have sustained both short and open circuit loads under full output on more than one occasion without coming to grief. However, it is not recommended that this procedure is adopted too often! The output from the p.a. is fed through a low-pass filter and then to the antenna changeover relay.

## General Constructional Notes


Due to the component density required for this project, the p.c.b. layouts must be rigidly followed. Most boards employ ground plane, double-sided techniques. Ensure adequate clearance for component leads as they pass through the copper ground plane layer. Countersinking of the holes is recommended, but do not countersink holes that are earth connections.

## Components

Before purchasing the required components the lead-out spacings should be checked. The values of components should be exactly as shown: avoid using inferior quality types. The size of the 0.1μF capacitors must be reasonably small and the author had difficulty in obtaining the same size on a second purchase of both these and the silver mica capacitors.

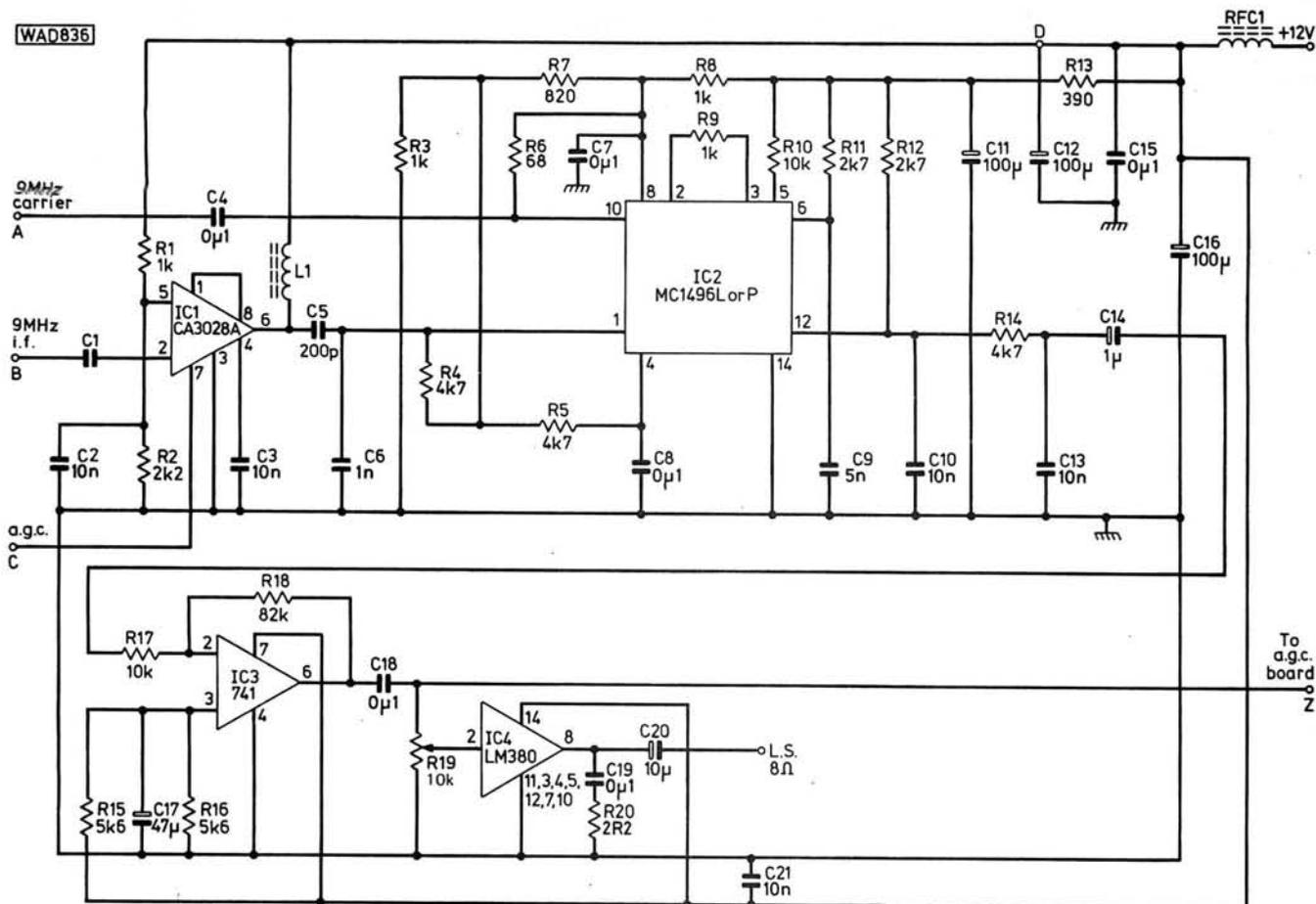

**Fig. 2: Circuit diagram of board 1; i.f., product detector and audio stages. Below: Board 1 is located in the bottom right-hand corner of the prototype**

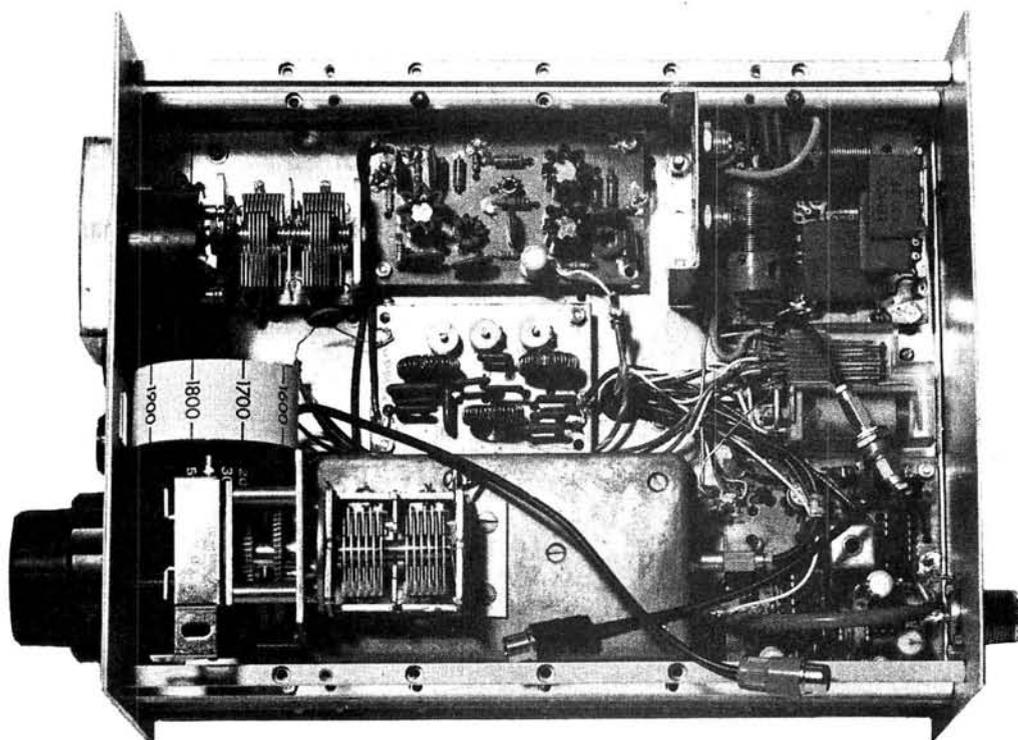

The toroids in the broad-band circuits did not seem at all critical and other types would obviously work quite well. A high  $\mu$  is however essential. The toroids associated with the filters however should not be substituted unless the filter is to be re-designed. The individual component lists will specify the correct grades, etc.

## Wiring

It is essential that 50 $\Omega$  screened cable is used where shown between boards. The miniature p.t.f.e. type of coax is ideal, but any cable with the correct impedance will suffice. The filters in particular will not be terminated correctly if other impedances are encountered.

## Board 1—IF Product Detector and Audio Stages

Board 1 contains the following circuitry:

1. IC1, a CA3028A, 2nd i.f. amplifier.
2. IC2, an MC1496, product detector.
3. IC3, a 741, 1st audio amplifier.
4. IC4, an LM380, audio amplifier to provide loudspeaker drive level.

## Circuit Description

A full circuit diagram of board 1 is shown in Fig. 2. Point B receives the 9MHz i.f. from the filter board (board 3). It is routed to pin 2 of IC1 via C1. This stage is operated in its cascode mode and has a typical power gain of 39dB at 10.7MHz. In conjunction with the preceding i.f. amplifier this would give a post filter gain of approximately 80dB. The output load to the CA3028 consists of the tuned circuit L1, C5 resonant at 9MHz, this inductor being slug tuned. The output is capacitively tapped into pin 1 of IC2 via C5 and C6.

IC2, an MC1496, makes an excellent s.s.b. product detector. According to the application notes on this device it has a sensitivity of 3 $\mu$ V and a dynamic range of 90dB when operating at an i.f. of 9MHz. The resistor between pins 2 and 3 controls circuit gain, sensitivity and dynamic range. Extra decoupling was found to be necessary which consisted of C11, R13. This cured any tendency towards audio instability and did not seem to reduce the overall gain of the device. The circuitry around IC2 is similar to that of the balanced modulator but has no facility for carrier null, this not being necessary on receive. The audio output appears at pin 12 and is routed to pin 2 of IC3 via R14, C14 and R17.

IC3, a 741 operational amplifier, is used here as the first audio amplifier with its gain set by the ratio of R18 to R17. Increasing R18 will increase the available gain. The audio output at pin 6 is fed via C18 and R19 to pin 2 of IC4. R19 is the volume control and is located on the front panel.

IC4, an LM380, is used as the audio power amplifier. This amplifier was chosen as it needed a minimum of components around it, is short circuit proof (essential at the author's QTH) and has internal thermal limiting. The voltage gain of this device is fixed internally at 50. The output power of 2 watts, appearing at pin 8, is fed to the 8 $\Omega$  loudspeaker via C20. R19 used in the prototype was a 100k log potentiometer, but a value of 10k $\Omega$  was found to be a better proposition as IC4 had a tendency to latch on switch on. C19 and R20 were included to prevent any instability in the LM380.



Fig. 3 (above): Full size track pattern of the underside of board 1


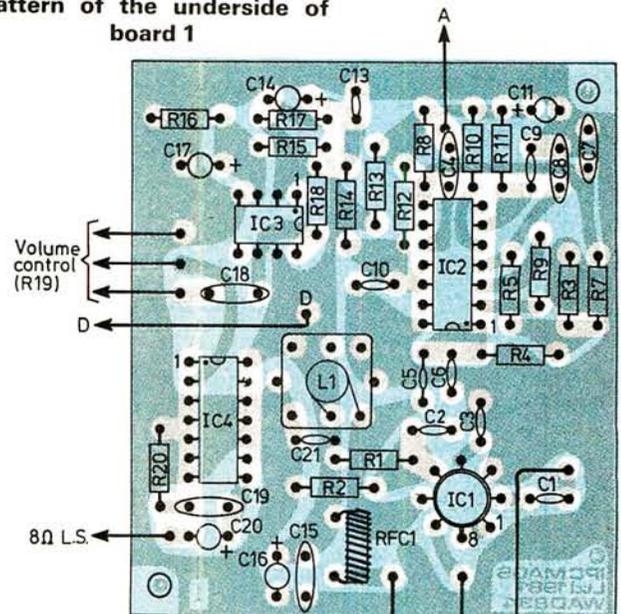


Fig. 4: Component overlay  
Fig. 5 (below): Component side p.c.b. ground plane pattern

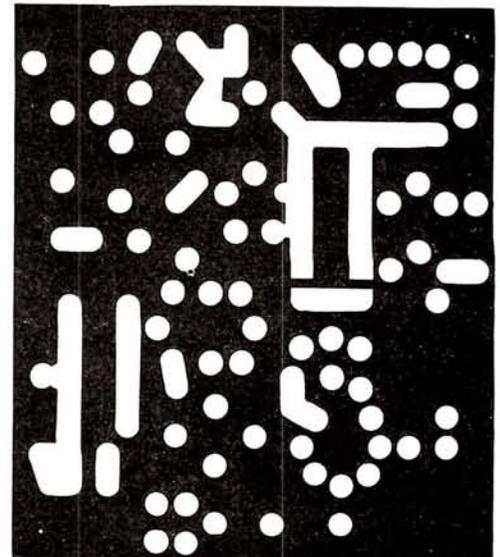

**BOARD 1**

**Resistors**

$\frac{1}{4}$ W 5% Carbon Film

2.2Ω	1	R20
68Ω	1	R6
390Ω	1	R13
820Ω	1	R7
1kΩ	4	R1,3,8,9
2.2kΩ	1	R2
2.7kΩ	2	R11,12
4.7kΩ	3	R4,5,14
5.6kΩ	2	R15,16
10kΩ	2	R10,17
82kΩ	1	R18

**Potentiometer**

Panel Mounting

10kΩ log.	1	R19
-----------	---	-----

**Semiconductors**

Integrated Circuits

CA3028A	1	IC1
MC1496 LP	1	IC2
741	1	IC3
LM380	1	IC4

**Capacitors**

Resin Dipped Ceramic

1nF	2	C1,6
5nF	1	C9
10nF	5	C2, 3, 10, 13, 21

Sub-min Ceramic

200pF	1	C5
-------	---	----

Disc Ceramic

0.1μF	6	C4,7,8,15,18,19
-------	---	-----------------

Tantalum Electrolytic

1μF	1	C14
10μF	1	C20
47μF	1	C17
100μF	3	C11,12,16

**Miscellaneous**

RFC1 20 to 30 turns of 32 to 38 s.w.g. wire on 28-002-27 toroid; L1 15 turns of 38 s.w.g. wire on Neosid inductance assembly type A6; printed circuit board.

The radio frequency choke and C15 provide r.f. decoupling to the board. This was found to be necessary when hooking the various boards together on the bench during preliminary tests on the receiver section.

The 9MHz carrier insertion enters at point A and, via C4, is routed to pin 10 of the MC1496. The a.g.c. voltage is applied to pin 7 of the CA3028 at point C. Point B is the 9MHz i.f. input to pin 2 of IC1.

To prevent any r.f. breakthrough during transmit the 12V supply is connected to this board during receive only via relay connections.

**Constructional Details**

The board is constructed on a double sided glass fibre p.c.b. and Vero pins are used for all external connections. It is important that the d.i.l. package is obtained for IC2 (this is also available in other forms). Similarly, the TO5 style package for IC1 and 14 pin d.i.l. package for IC4 are used.

R6, a 68Ω resistor, is connected between pins 10 and 8 of IC2 on the underside of the board.

A 100μF decoupling capacitor, C12, is included to ensure adequate audio decoupling. This capacitor is joined between point D (see component layout) and the earth plane on the top of the board.

Two holes between C13 and R8 are not used. A resistor was originally used between the input (point B) and earth, consequently there are two spare holes at this point also.

**Connections to Board 1**


Point A connects to the 9MHz oscillator on board 2, point Y. Point B connects to filter board 3, Y out. Point C connects to a.g.c. voltage, board 8 a.g.c. 0/9V. The +12V line connects to the +12V rail via relay contacts, during receive only. Point Z, the top of R19, volume control, connects to the a.g.c. board 8.

**NEXT MONTH**

The second part of this article will cover the construction of the 9MHz oscillators, filter and mixer boards.

**BI-PHASE COMPARATOR**

▶▶ continued from page 21

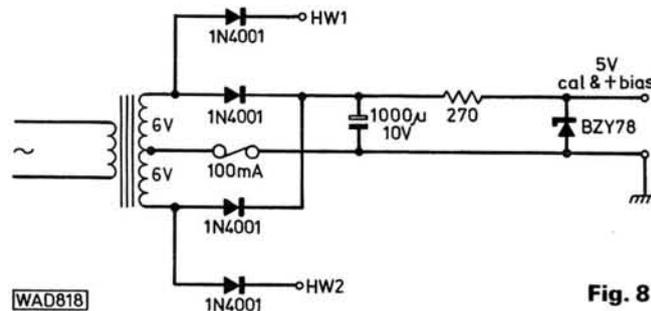

**Fig. 8**

For convenience, the bias controls are calibrated during construction using a multimeter temporarily wired for reference. Volts for valves, microamperes for transistors.

**Practical Circuits**

The valve versions of the bi-phase power supply and comparator are shown in Figs. 5 and 7 and that for transistors in Fig. 6. The valve power supply, Fig. 7, has provision for 6.3 volt heaters, negative bias and a stabilised voltage of 105 volts for the screen grids and calibration source. The transistor power supply in Fig. 8 has a 5.2 volt stabilised voltage for calibration and current bias source.

The two additional diodes in Fig. 6 are needed in the transistor comparator so that current in R1 or R2 is not diverted through the non-conducting transistor. ●

# PRODUCTION LINES

ALAN MARTIN G8ZPW

## Electronic Music

Over the last few years, Casio have entered the electronic musical instruments market and the latest additions to their range are real beauties.

I will describe the model in the middle of their electronic organ range, the Casiotone 301 which compares very favourably with similar products on the market.

The CT-301 keyboard covers four octaves (49 keys) which allows up to an eight note polyphonic sound combination to be played. Fourteen separate voices are available; they are organ, flute, oboe, clarinet, trumpet, violin, cello, piano, harpsichord, celesta, accordion, electric piano, funny and frog. Each of these voices can be effected by a vibrato and vibrato delay function, the vibrato delay being particularly applicable to creating the sensitive sounds of wind and stringed instrument voices.

The rhythm section features eight built-in rhythms from Rock to Mambo.

Each rhythm has two variations and a Synchro Start function that can add that professional touch to performances. Also included in this section is an override Start/Stop switch, rhythm tempo control and rhythm-only volume control.

The CT-301 is housed in a woodgrain finished case, measures 796 x 326 x 116mm and weighs 12.3kg (27lbs). A built-in speaker is fitted, as is a preset Pitch Control ( $\pm\frac{1}{4}$  tone).

External connections can be made via four rear panel jacks for headphones, output (line out), foot volume and sustain. Optional accessories for these functions are available.


The discounted price of the CT-301 is £245 and is obtainable, as are details of other instruments in the range, from: *Tempus, The Beaumont Suite, 164-167 East Road, Cambridge CB1 1DB. Tel: (0223) 312866/67503.*


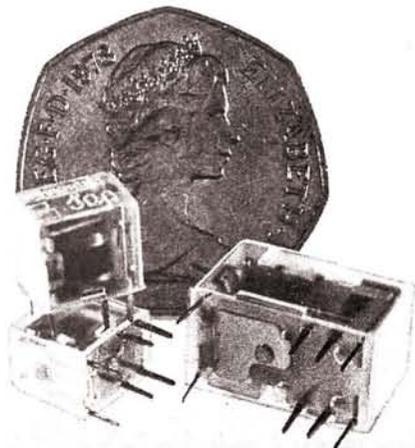
## Miniature PCB Relays

Ambit have recently introduced two p.c.b. mounting relays. The RBU series is a flux resistant relay with two-pole changeover contacts, each capable of handling 2A at 24V d.c. Stock types are provided with 10-12V d.c. 320 ohm coils, although any value from 3V to 24V can be accommodated to order. Life expectancy is a minimum of 10 million mechanical cycles, with 100 000 cycles for the contacts when run at maximum capacity.

The RCU relay is one of the smallest changeover relays available (excluding



## New DFM

Holdings Photo Audio Centre consider that a unit they are importing will prove to be a real winner. It is the FC-841 digital frequency meter which covers the range 10Hz to 50MHz and up to 500MHz using a suitable prescaler.

Measuring only 120 x 100 x 32mm the unit is powered by internal batteries or external d.c. supply (8 to 11V). Sensitivity is claimed to be better than 30mV over most of the range (60mV on int. batteries), with accuracy of  $\pm 10$ Hz and resolution 10Hz/10kHz.



The basic price of the FC-841 is £39.99 including VAT and the total price which includes batteries, input lead, carriage and insurance is £43.58. Other optional accessories and further details are available from: *Holdings Photo Audio Centre, Mincing Lane, Darwen Street, Blackburn BB2 2AF. Tel: (0254) 59595.*

## Useful Mini Drill

The "Reliant" 12V mini drill is available from TRI-tronic Marketing Ltd., together with a range of accessories which includes a versatile drill stand, mains to 12V d.c. power supply unit, drill bits and diamond burrs.

Measuring only 75mm long x 34mm diameter, the drill is powerful enough to drill up to 3mm holes in p.c.b. materials or sheet metal.

The basic price of the drill is £6.98 and further details are available from: *TRI-tronic Marketing Ltd., 9 Badby Leys, Rugby, Warwickshire CV22 5RB. Tel: (0788) 812895.*

TO5 types). It is a single-pole unit, capable of switching 2A at 24V d.c. (or 2A at 100V a.c.). The "stock" coil is a 10-12V d.c. 320 ohm winding, although 3-24V is available to order. Life expectancy is the same as for the RBU relay.

Applications of both these relays include antenna switchover, remote control systems etc.

The RBU costs £1.85 and the RCU £1.65. Both are available from: *Ambit International, 200 North Service Road, Brentwood, Essex CM14 4SG. Tel: (0277) 230909.*


## Low-cost Desolder Pump

Industrial performance at an economy price is claimed for OK Machine and Tool (UK) Ltd.'s DSP-1 desolder pump.

Suitable for general purpose industrial use and the hobbyist, the hand operated tool costs about £6 and is all metal with an easy to replace teflon tip.

Solder can be removed precisely from delicate circuitry without causing damage and the tool is self cleaning on each stroke.

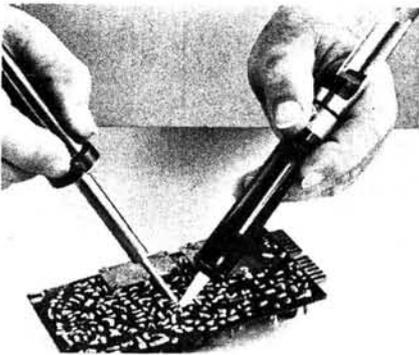
Further details from: *OK Machine and Tool (UK) Ltd., Dutton Lane, Eastleigh, Hants SO5 4AA. Tel: (0703) 610944.*


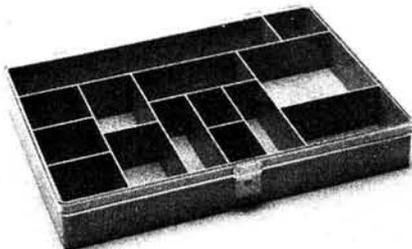
## Clear-up

Probably one of the most efficient ways of storing small electronic components is multi-compartment storage cases, two which would seem to fit the bill are available from Edward Roland Ltd.

Called "Space Misers", the largest is a 14, various sized, compartment case, measuring 349 x 241 x 51mm. The case is beige in colour and fitted with a crystal-clear hinged lid with a strong snap-shut clasp. This unit costs £5.75 which includes VAT.



The smaller unit has 10, equally sized, compartments and measures 267 x 140 x 32mm. Similarly, this case is beige coloured has a crystal-clear hinged lid and costs only £2.40 which includes VAT.

Both items are available by post (p&p free within the UK) from: *Edward Roland Ltd., 215 Putney Bridge Road, London SW15 2NY.*

## Noise Suppressor

A new noise suppressor for car audio systems has been introduced by Hitachi to minimise the interference created by a vehicle's electrical equipment which may be transmitted along the power supply cable.

The Hitachi NF2 is a dual suppressor and choke filter unit which fits simply between the power lead and the car radio or cassette player. It was designed and developed by Hitachi's own in-car audio specialists in the UK. This small device comprises an iron core choke and electrolytic decoupling capacitor, sealed-for-life in an epoxy resin encapsulation.

Costing £3.45 which includes VAT,



the NF2 suppressor is supplied complete with detailed fitting instructions and is available through Hitachi's extensive UK network of car audio dealers. Alternatively, full information can be obtained from: *The Sales Manager, In-Car Equipment Division, Hitachi Sales (UK) Ltd., Hitachi House, Station Road, Hayes, Middlesex UB3 4DR. Tel: 01-848 8787.*


## Small Desk Consoles

Recently introduced by Boss Industrial Mouldings Ltd., is a range of small desk consoles manufactured in ABS and fitted with a 1mm thick grey aluminium panel which sits recessed into the sloping front.

Available in two sizes measuring 161 x 96 x 58mm deep and 215 x 130 x 75mm deep, these Bimconsoles are moulded in orange, blue, black and grey and incorporate, not only slots on all four sides into which 1.5mm thick p.c.b.s can be fitted, but also 5mm diameter stand-off bosses for supporting small sub-assemblies, etc.

The front panel is supported on four corner pillars which also carry the brass bushes into which the panel fixing screws run.

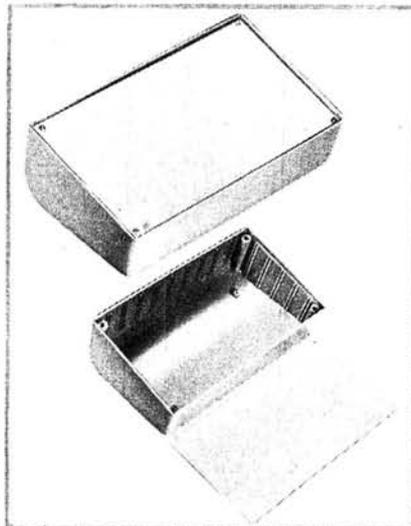Prices, which include VAT and p&p, are £2.48 for the smaller Bimconsole and £3.48 for the larger one. The enclosures are obtainable from: *Boss Industrial Mouldings Ltd., 2 Herne Hill Road, London SE24 0AU. Tel: 01-737 2383.*



## Useful Receiver

Grundig's Party Boy 700 radio should prove very popular with people who do not possess the full use of their hands.

Without any conventional control knobs, the Party Boy 700 has a slide volume control and a roller tuner which suits people with handling difficulties.

It can be powered by mains or batteries and is capable of receiving l.w., m.w. and v.h.f. wavebands, with a built-in a.m. aerial and a telescopic antenna for f.m. (v.h.f.). It has an output of 1.5 watts.



The radio has a tone control, earphone socket and carrying handle.

Measuring 29 x 16 x 7cm, the Grundig Party Boy 700 weighs approximately 1.3kg and is available from Grundig dealers, in Black or Walnut finish at a typical selling price of £36 including VAT.

## If you please

Please mention "Production Lines", when applying to manufacturers or suppliers featured on this page.

# Assessing the new RAE

## THE FIRST TWO YEARS

\*Arthur HARADA M.Ed, Dip.SP.Ed, ACP, G4INX

In the light of much ill-informed and often heated argument heard on the airwaves nowadays concerning the new RAE, it is time to offer a sequel to my last article (*Practical Wireless*, Jan. 1980) on this important examination. By and large people don't enjoy taking exams, simply because we naturally avoid those experiences in life which will not only discover our weaknesses, but also point them out to others. However, if we can gain sufficient familiarity with the RAE, namely, what the questions seek to measure, how they are constructed and marked, etc., this new-found insight might prevent an apoplectic fit by some readers when reading the now famous slip from the City and Guilds of London Institute (CGLI) pushed through the letterbox in late August or January. From all accounts, there are as many complaints over not being awarded distinctions as there are about failing.

Each part of the two-part RAE consists of multiple-choice questions, some of which make a regular and generally unchanged appearance and endeavour to tap knowledge of specific basic facts. Coupled with them are newcomers constructed to measure more complex learning outcomes, and supplied by technical college staff amongst others, many of whom are licensed amateurs. All the questions are vetted by a small examinations committee reporting to the CGLI and not, as is popularly believed, to the RSGB. Theoretically, every question presents candidates with a task that is both important and understood, and can be answered correctly only by candidates who have mastered the desired learning.

A multiple-choice item in the RAE is sometimes in the form of a question or more often an incomplete statement (called a **stem**) followed by four suggested answers or completions (called **alternatives** or **responses**). Only one of these is correct (called the **key**), the wrong responses (called **distracters**) being plausible. It can happen that the alternatives are very similar to one another, and the candidate has to exercise considerable care, e.g.

Q.5 The spelling of the word MEXICO using the recommended phonetic alphabet is:

- Mike Echo X-ray India Charlie Oscar
  - Mike Easy X-ray India Charlie Oscar
  - Mike Easy X-ray India Charlie Oboe
  - Mike Echo X-ray Ireland Charlie Oboe
- (Paper 2, May 1980)

\*Department of Professional Studies, Chester College of Higher Education

Not very often, but nevertheless candidates should be aware of the fact, the stem of an item can be expressed in a negative form, e.g.


- Q.5 Entries in the Station log book need not include:
- date
  - time of commencement of operation
  - signature of the licensee
  - time of closing down the Station
- (Sample items, 1979)

Using negatively-stated item stems can be a convenient way of overcoming the test constructor's frustrations and inability to generate a sufficient number of plausible distracters. This state of affairs is being quickly reached in Paper 1 where the scope for fresh items on Licensing Conditions and Transmitter Interference is somewhat limited, and might result in future papers containing what some might call very difficult items, e.g.

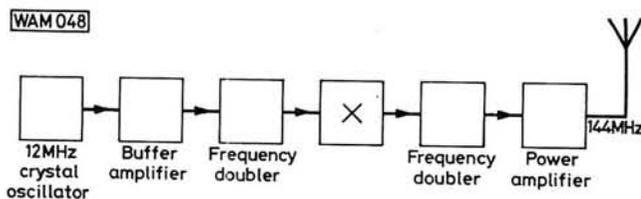- Q.4. The holder of a Class B licence may use which of the following modes of operation in the frequency band 144-146MHz?
- A3, A3A, A3H, F3, P3E
  - P3D, A3J, A1, F3, A3H
  - F3, A1, A3J, A3, A3A
  - A3, A3A, A3H, A3J, F3
- (Paper 1, May 1979)

If nothing else, this type of item warns you to learn every detail on the facsimile of the Licence printed in the majority of examination preparation manuals.

Despite every reasonable precaution, examiners can make mistakes and provide a list of alternatives none of which is correct, e.g.



Q.37 The above figure shows a block schematic diagram of a c.w. transmitter for the 144MHz band. What is the purpose of the box marked X?

- linear amplifier
  - frequency modulator
  - frequency doubler
  - buffer amplifier
- (Paper 2, Dec. 1980)

Correct answers in triplicate to the Editor, please!

Another version of the multiple-choice item is known as the best-answer form, in which more than one alternative is correct, but one is better than the rest, e.g.

Q.8 Ohm's Law states that:

- a current of one ampere flows in a circuit having a resistance of one ohm when one volt is applied to it
  - $I = \frac{E}{R}$
  - when one coulomb of electricity passes between two points there is a potential difference of one volt then one joule of work is done
  - the current flowing in a circuit is directly proportional to the applied e.m.f. and inversely proportional to the resistance of the circuit
- (Paper 2, May 1979)

In this last example it could well be argued that the choice between (a) and (b) is minimal, although neither are accurate on reading Ohm's Law in the original which states "The ratio of the p.d. (V) between the ends of a conductor, to the current (I) flowing in it, is always a constant provided the physical condition of the conductor is unaltered."

Yet another example of examiner error, or to put it another way, an illustration of the difficulty of avoiding the pitfalls of writing poor items may be seen in:

- Q.3 An amateur licence may be revoked by:
- a notice cancelling all amateur licences appearing in a newspaper published in London
  - a general notice cancelling all amateur licences being broadcast by the British Broadcasting Corporation
  - the Licensee transferring the Licence to another person without informing the Secretary of State for the Home Department
  - a letter from the local Chief Constable (Paper 1, Dec. 1979)

Both (a) and (b) are equally valid if one takes the relevant clauses in the Licence separately.

In theory, it is by guesswork possible to stand a 1-in-4 chance of obtaining the correct answer in the RAE, but this technique is not advised as the right answer is randomly placed and, as a general rule, appears in each alternative position approximately an equal number of times throughout both papers. It could be strongly argued that the CGLI should use what is known as a "correction formula"—designed to penalise the candidate who guesses the answers, since the scoring system provides no larger penalty for guessing wrong than for omitting an item. Hence, the more daring and less conscientious class of examinee may enjoy an added advantage deriving from their personality type and not from their grasp of the subject matter being questioned. The CGLI's standpoint on this is:

"It is Institute policy not to apply a correction score for guessing. In theory, the expected guessing score is 25 per cent for a set of "1-from-4" items. However, in practice this score is not of great significance as:

- Pure guessing is a last resort, and likely to be confined to the poorest students, who are in any case likely to fail (the pass mark is well above the expected guessing score).
- Part-guesswork is a valid activity, as on average a student will gain a score reflecting his partial knowledge."

There are still some inaccurate claims made about the pass rate, not to be confused with the pass mark. It still remains at approximately 70 per cent in Paper 1 and 60 per cent in Paper 2. Clearly, this is because the RAE is standardised using a statistical technique known as item analysis, whereby poor items can be identified, rejected or re-drafted, and acceptable ones banked for future use. So, don't skimp in either initial study or revision; abstain from unreasoned guesswork as it might prevent your dredging the deep recesses of your mind for the right answer; tackle the items you're sure of first; and if you change your mind about an answer be sure to rub out the first mark. Finally, count yourself lucky if you aren't an overseas candidate—about 50 per cent of them fail. Without doubt this is because home candidates have excellent support from patient teachers of the RAE, and easy access to first-rate technical journals that pitch their contents so as to encourage practical experimentation in the reader's home. Good luck!

*Practical Wireless, May 1981*

# Kindly note!

## PW Sherborne, October 1980

In the circuit diagram Fig. 3, D41 adjacent to Tr15 should read D42. D42-47 then become D43-48 inclusive.

C29+ should be connected to the other side of S19b.

In the components list for the synthesiser the yellow l.e.d.s are D41, D44 and D45.

## Mods. No. 5 Standard C 8800, April 1981

The new wire, shown in orange in Fig. 3, should connect pin 4 to pin 1, and not as shown. The additional resistor, R1, should be 10kΩ **not** as specified in the text.

## PW Helford April 1981

In Fig. 30, page 39, R902 and R903 are not, in fact, resistors but the two regulated bias supplies as detailed in Part 4.

The transistors (Tr501-504) in the component placement diagram Fig. 23 Page 43 are shown with the collectors and bases transposed. These transistors should be fitted so that the tabs with the cut-away corners are towards T504 and T505.



## Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with the PRACTICAL WIRELESS logo. Gold Letra-set supplied for self blocking of volume numbers and years.

Price £4.30 including postage, packing and VAT. Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

it's easy with **EASIBIND**

### Order form PRACTICAL WIRELESS

I enclose P.O./cheque value .....  
for.....binders

Years required .....  
(BLOCK LETTERS PLEASE)

Name .....

Address .....

Date .....

# MODS

**IMPORTANT**—The ideas presented here are suggestions only, and as they are untried by this magazine, we cannot accept responsibility for any resultant damage, however caused. Before alterations are attempted, care should be taken to ensure that any guarantee is not invalidated, and it should also be borne in mind that modifications usually have an adverse effect on resale prices. In cases where specialist skills or equipment are needed, most dealers will undertake the work for a reasonable fee.

## Roger Hall G8TNT (Sam)

No. 6

### Trio TR-2300

This month's column is devoted to the ever popular TR-2300. Bill, G8UNN, wrote to ask me if I knew of a reverse repeater mod for this set and so I contacted Steve, G8VEF, at Lowe Electronics, and he has supplied the following information.

First, take off the cover of the set on the loudspeaker side and locate the Aux switch, it has a brown wire and a white wire attached to its rear tags (Fig. 1). The original mod suggested removing these wires and tucking them back into the loom, and then adding new wires as in Fig. 1. Steve has pointed out that if the wires are cut approximately 25mm back from the switch at the points marked "X" in Fig. 1, they can then be used instead of two new pieces of wire. As Steve said, this means that you only have to make two soldered joints and not four, which in this instance is a good idea because there is not much room on this switch as there are many other wires attached to it, although for the sake of clarity they have not been shown in the diagram. When the set is operating on the REPEATER position of the bandswitch, this mod gives instant reverse repeater operation whenever the Aux switch is pressed.

Following on from this, Gareth, GW4KJW, has written in with what he calls a mod of a mod, and he says, although it does not contribute anything to the performance of the set, it does make use of something that is otherwise left unused.

When the set has been modified for reverse repeater, there is a small l.e.d. to the left of the Aux button that remains permanently off because it was originally designed to show that a crystal controlled channel had been selected,

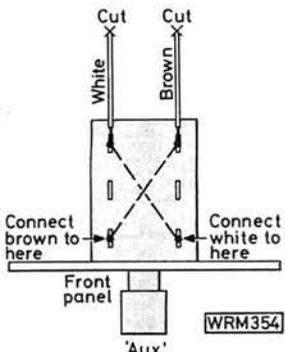


Fig. 1

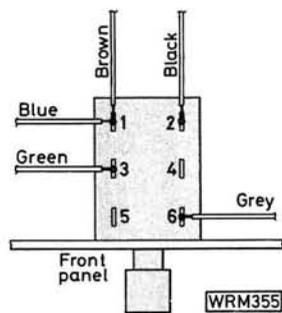


Fig. 2

but now that the Aux button has a different function, the l.e.d. has nothing to do. Gareth suggests using it as a toneburst indicator to give a visual indication that the toneburst is switched on.

To do this, the top cover should be removed and the blue wire unsoldered from the three-position dial light slider switch. This wire should then be fed back through the wiring loom and soldered to Pin 1, the rear left-hand pin of the toneburst switch (Fig. 2).

This mod lights the l.e.d. for as long as the toneburst is switched on, except on transmit, when the l.e.d. is off while the p.t.t. is depressed.

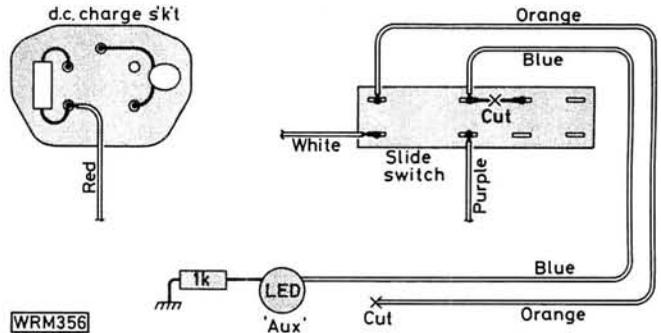


Fig. 3

The last mod this month was devised by G8JLE, but was given to me by Lowe Electronics. This mod makes use of the same l.e.d. as the last one but this time it is used to give a visual indication of battery charge, and needless to say, it is not possible to carry out both of these mods on the same set! Fig. 3 shows the original charge socket, and the original three-position dial light slider switch. Fig. 4 shows how the two have to be modified and interconnected. The orange wire has to be removed from the top left-hand pin and attached to the top right-hand pin and then cut some way away from the switch and that end soldered to the side of the l.e.d. that has a 1kΩ resistor soldered to it. The resistor is then cut off and not used.

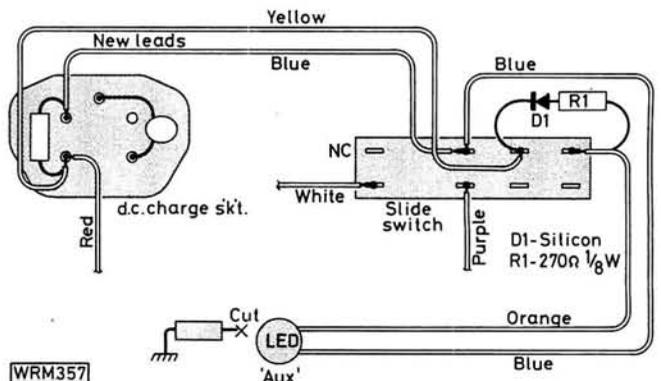


Fig. 4

Two new wires, blue and yellow, are run from the switch to the socket, as in the diagram, and the link on the switch is then cut. A silicon diode and a 270kΩ resistor are then connected as in Fig. 4.

When completed, this mod gives a visual indication that the batteries are receiving charging current when the charger is plugged in. If you have any mods, or requests for mods, please write to: R. S. Hall, *Practical Wireless*, King's Reach Tower (Hatfield House), Stamford Street, London SE1 9LS.

73's  
Sam G8TNT

# Next month in *Your All Radio*

*Your All Radio*  
**Pw**

★ **Britain's No.1 Magazine for the Radio Enthusiast**

Licensed Amateur Radio • Short-Wave Listening  
DX Listening and Viewing • Radio Control  
plus The Latest Developments on the CB Scene

## GETTING INTO MICROWAVES

with our



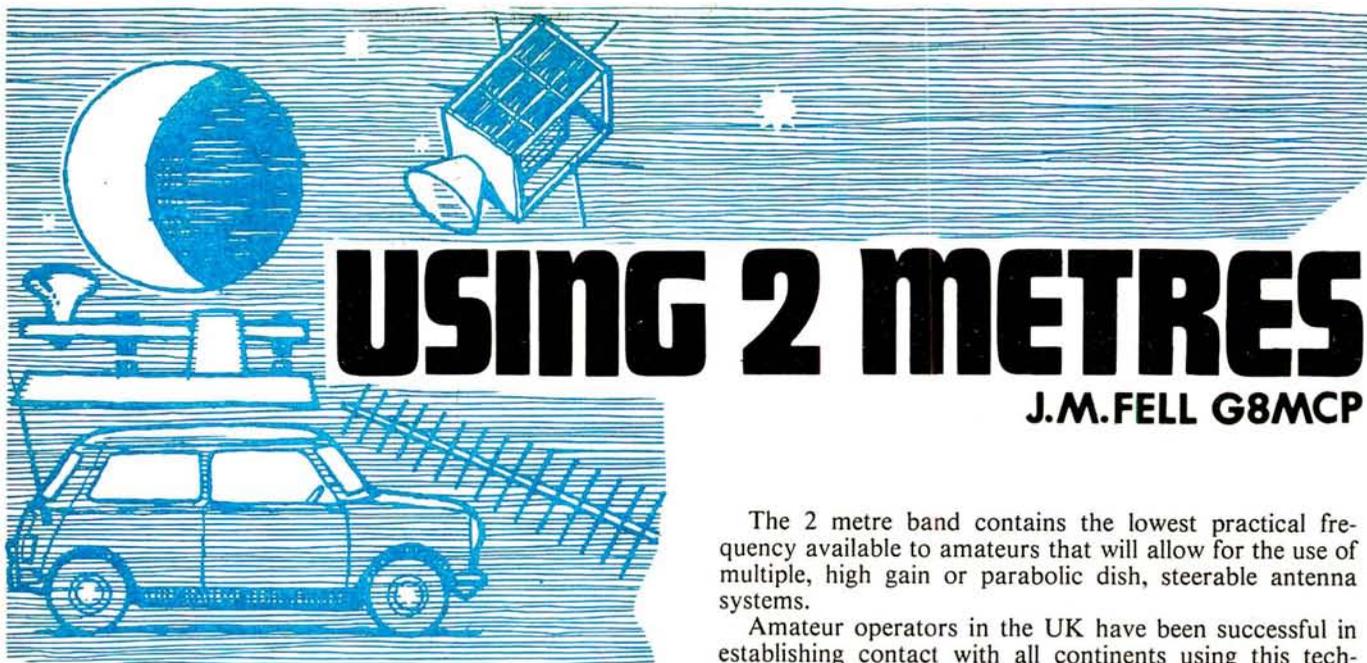
# EXE

With this 10GHz wide-band f.m. transceiver you can enter the wonderful world of microwaves. Contacts over line-of-sight paths of 150km should be possible with this project, which has been designed with the beginner to microwaves in mind. Look out also for news of our parabolic dish offer

also  
**Band II VHF Pre-Amp**  
and  
**USING REPEATERS**





# USING 2 METRES

J.M.FELL G8MCP

The 2 metre amateur band, since its availability to Class B licensed radio amateurs in the mid-60s has seen a continuous increase in activity and operating modes.

Readily available commercially designed and produced equipment, together with the readily manageable wavelength at this frequency, has encouraged many people into licensed amateur operation. Whilst the 2 metre band is used extensively by the newly licensed amateur, the band has much more to offer to all user levels, licence holders or s.w.l.s.

This article has been written to provide an indication of the extensive variety of modes available for operation and observation of this v.h.f. waveband.

## The 2m Band Plan

In order to make the best possible use of the 2 metre band it is useful to be able to refer to a nominated band plan. Fig. 1 is a reproduction of the International Amateur Radio Union (IARU) Region 1 band plan, showing the current UK usage notations.

The band plan has been formulated between the Region 1 member countries. The interests of all UK amateurs are represented on the Region 1 sitting committee by the Radio Society of Great Britain.

Whilst, with the exception of the two spot frequencies, the band plan is a *recommended* guide to band use, by following this course of self-regulation the maximum use of the frequencies between 144-146MHz can be obtained by all.

A study of the band plan will reveal the variety of operations taking place, and a brief guide to these follows.

## Moonbounce

Moonbounce, Earth Moon Earth or e.m.e. for short, is the name given to encompass the increasing number of experiments being conducted by radio amateurs, utilising the face of our natural satellite for the reflection of radio signals.

The 2 metre band contains the lowest practical frequency available to amateurs that will allow for the use of multiple, high gain or parabolic dish, steerable antenna systems.

Amateur operators in the UK have been successful in establishing contact with all continents using this technique, primarily using very narrow c.w. bandwidths, but in increasing instances via single sideband telephony.

Because of the large path losses introduced by the distances involved and the surface absorption of the transmitted signals on the face of the Moon, e.m.e. equipment represents the current state-of-the-art. Great attention must be paid to achieving very low noise figures in the receiver front ends in addition to high passive antenna gain. For this kind of operation to succeed it is vital that the allocated link frequencies remain free of other conventional forms of earthbound communications.

## CW

Morse coded transmissions are permissible on 2 metres, as with all other amateur bands, but the use of this highly efficient narrow bandwidth means of communication is restricted to use by holders of the full Class A licence.

Valuable information can, however, be obtained by the s.w.l. and Class B licence holder from observations on the c.w. frequencies. The sheer scale of distances that are being worked on a daily basis has inspired many to the attainment of a full licence.

## Meteor Scatter (MS)

This exacting mode of operation utilises the reflective nature of ionised patches of the upper atmosphere produced by the decomposition of meteorite debris. Due to the height above the surface of the Earth that this ionisation occurs, approximately 110km, signals may be propagated over paths of 2000km in length.

Main activity periods are coincident with known meteorite storms or showers, but several amateur operators maintain activity to enable contacts to be made via random meteorite action. All the information obtained is also of interest to the many space observatories and is eagerly sought out to enhance our knowledge of this phenomenon.

Once again, it is of vital importance to establish frequencies for this method of operation. Single sideband (s.s.b.) and c.w. modes are utilised, with separate sub-bands provided. A study of the band plan will show 5 minute and 1 minute time periods allocated for the random

**Fig. 1: IARU 144MHz Band Plan with UK usage**

CW only	144-000 144-000 —144-010 144-050 144-100 —144-110 144-145 —144-150	Spot frequency (UK use forbidden) Moonbounce c.w. calling frequency Random c.w. m.s. (5 min) Random c.w. m.s. (1 min)	FM repeater inputs	145-000 145-025 145-050 145-075 145-100 145-125 145-150 145-175	R0 R1 R2 R3 R4 R5 R6 R7
SSB and c.w. only	144-200 —144-210 144-250  144-260± 144-300	Random s.s.b. m.s. Used for GB2RS and slow Morse transmissions Used by Raynet SSB calling frequency	FM simplex channels	145-200 145-225 145-250  145-275 145-300 145-325 145-350 145-375 145-400 145-425 145-450 145-475 145-500  145-525  145-550  145-575	S8 Raynet S9 used by Raynet S10 used for slow Morse tone modulated transmissions S11 S12 RTTY—a.f.s.k. S13 S14 S15 S16 S17 S18 S19 S20 f.m. calling channel S21 used for GB2RS f.m. newscasts S22 used for rally/ exhibition talk-in S23
All modes non-channelised	144-500 144-540  144-550 144-600 144-600± 144-650 144-700 144-750  144-800 144-825 144-850 144-875	SSTV calling frequency Spot frequency (UK use forbidden) Data RTTY calling frequency RTTY working (f.s.k.) AM calling frequency FAX calling frequency ATV calling and talkback Raynet Raynet Raynet Raynet	FM repeater outputs	145-600 145-625 145-650 145-675 145-700 145-725 145-750 145-775	R0 R1 R2 R3 R4 R5 R6 R7
UK beacons	144-900—144-990	UK beacons	Satellite service	145-800 —146-000	Satellite service

operation. These times refer to the pre-arranged methods of calling and listening, essential in order to allow the flow of information to accumulate from the very short duration bursts of reflected signals.

Comprehensive details of m.s. operating procedure may be found in the RSGB *Amateur Radio Operating Manual*.

## Amateur Television

Since the earliest pioneering days of commercial television, radio amateurs have paralleled with their own experimental services.

Several modes of TV operation occur on the 2 metre band with slow scan (SSTV) probably the most prevalent. The ability to transmit and receive audio and video information adds considerably to the enjoyment of stations equipped with the necessary hardware.

## Facsimile—FAX

Facsimile transmissions utilise a process that converts graphic information into electrical signals. Initially, the equipment used relied heavily on ex-commercial, electro-mechanical devices, utilising the effects of passing current from a tracking stylus through electrolytic paper. By suitably decoding the variations in received signal level, corresponding density variations are produced on the paper in the form of the original material.


### NOTES

Operation on the two spot frequencies is not permitted in the UK by the terms of the Home Office licence. See licence footnote No. 4.

The beacon and satellite service bands must be kept free of normal communication transmissions to prevent interference with these services.

The use of the f.m. mode within the s.s.b./c.w. section and c.w. or s.s.b. in the f.m.-only sector is not recommended. Repeater stations are primarily intended as an aid for mobile working and they should never be used for DX communication. FM stations wishing to work DX should use the all-mode section, taking care to avoid frequencies allocated for specific purposes.

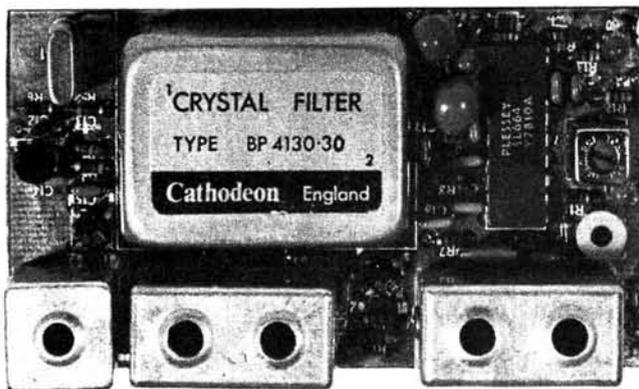GB2RS is the callsign of the RSGB weekly news bulletin, broadcast on 144.250MHz u.s.b. and S21 f.m. For further details of times and coverage contact the RSGB.



**Constructional projects for 2 metres are popular with our readers. This 2m Monitor Receiver was featured in *Practical Wireless* April 1979**

Interest in this form of communication has been stimulated recently by the advent of all solid-state devices that provide an output suitable for display on a v.d.u. The techniques used in this latest equipment are the same as those employed for the retrieval of weather satellite information.

## Radio Tele Type—RTTY

The use of RTTY also represents a current growth area amongst radio amateurs, with plenty of activity on the 2m band.

Traditional electro-mechanical devices, still well established commercially, are being superseded by the latest electronic processing methods, again utilising v.d.u.s for the silent display of received information. There can be no doubt that a request to the XYL for permission to install the earlier oil-guzzling, all-singing-and-clanking, mechanical printers, has proved to be the proverbial last straw!

Separate frequencies are listed in the band plan to cater for audio frequency shift keying (a.f.s.k.), associated with a.m. and f.m. modes and frequency shift keying (f.s.k.), transmitted via single sideband.

**The Trio TR-7800 is a versatile m.p.u. controlled f.m. transceiver suitable for use mobile or as a base station. Power output is 25W and programming is by key-pad**



**Fig. 2: A Selection of IARU Region 1 2m Beacons**

Callsign	Frequency	QRA Locator	Location
GB3CTC	144.915MHz	XK64a	Redruth, Cornwall
GB3VHF	144.925MHz	AL52j	Wrotham, Kent
GB3NEE	144.935MHz	ZO12a	Burnhope, Tyne and Wear
GB3GI	144.945MHz	XO41j	Nr. Ballynahinch, N. Ireland
GB3LER	144.965MHz	ZU65f	Lerwick, Shetland Islands
GB3ANG	144.975MHz	YQ35c	Dundee
HB9HB	144.125MHz	DH66f	Switzerland
DLOUB	144.807MHz	GM47b	West Germany
PAOJTA	144.820MHz	CL03g	Netherlands
LA1VHF	144.860MHz	ET13c	Norway
LA2VHF	144.870MHz	FX43g	Norway
LA3VHF	144.880MHz	DS78f	Norway
OY6VHF	144.885MHz	WW76d	Faroe Islands
LA4VHF	144.890MHz	CU47a	Norway
EA3VHF	144.897MHz	BB41c	Spain
OH6VHF	144.900MHz	KW59f	Finland
DLOPR	144.910MHz	EO54c	West Germany
SK7VHF	144.920MHz	GP38c	Sweden
OE5XBL	144.920MHz	GI77b	Austria
OZ7IGY	144.930MHz	GP23c	Denmark
DM2ACM	144.935MHz	GL53g	East Germany
DLOUH	144.940MHz	EL68f	West Germany
SK1VHF	144.950MHz	JR41d	Sweden
DM0VHF	144.990MHz	FN29f	East Germany
ON4VHF	145.985MHz	CK23e	Belgium

## Beacon Service

Within the frequency range 144.900–144.990MHz can be found the amateur 2m beacon service. These devices operate continuously transmitting c.w. Morse identification information from fixed locations, often employing directional antennas on a fixed beam heading.

An invaluable wealth of information can be obtained by both the licensed amateur and s.w.l. from the observation of signal propagation over these fixed paths. By maintaining a careful record of the received signal strength and variations in audible characteristics, detailed propagation profiles can be built up. The licensed amateur can also obtain information on the suitability of a given path before commencing transmissions, by locating a beacon on the same nominal beam heading and comparing this with the known path capability.

For the constructionally minded person, the presence of a continuously available signal source on a fixed frequency is invaluable for alignment purposes.

The amateur beacon service probably represents one of the few areas of activity for which there is no readily available commercial parallel offered to the general public, and it is known that their facilities are also utilised by many professional bodies. A selection of operational 2m beacons, within IARU Region 1, is given in Fig. 2. A complete list of Region 1 beacons is available from the RSGB headquarters.

## Amateur Satellites

Two amateur satellites are currently operational in Earth orbit, financed and built by radio amateurs worldwide.

Both these satellites, code named OSCAR-7 and OSCAR-8 are equipped for linear talk-through operation, allowing the possibility of intercontinental communication between amateur stations. In addition to the transponder function, the satellites are equipped with beacons, operating in the same manner as their terrestrial counterparts. As the satellites are not geostationary, valuable information can be derived from observation of the Doppler effect frequency shifts, and also the effects on signal transmission due to the ionosphere layers.

A third experimental satellite project, code named UOSAT, is being constructed by the University of Surrey, and currently scheduled for launch on a NASA vehicle during September 1981. This device will provide a wide variety of beacon and data mode transmissions, not the least of which will be a narrow-band frequency modulated speech synthesised beacon on 145.825MHz.

In the case of the two operational AMSAT OSCAR series satellites, the 2m band contains either the uplink (transmit) or downlink (receive) frequency. As both these transponders employ highly sensitive receivers, the overall gain of which is controlled by the relative input levels, it is vital to avoid the use of frequencies within their input passbands.

## Telephony

Most of the "specialist" modes of communication already covered rely on the use of a.m., f.m. and s.s.b. Telephony on 2 metres utilises all of these modes, specific frequencies being designated to prevent interaction.

Amplitude modulation (a.m.), initially the dominant mode for 2 metre telephony, is now the least used method. Several factors have contributed to this situation, the main ones being the higher possibility of TVI and the lack of available equipment, although several multi-mode transceivers are once again providing this facility.

Single sideband, A3J, telephony is the premier mode for DX working, allowing the maximum utilisation of available bandwidth.

**The hand-held 2 metre portable transceiver is very popular with amateurs. The IC-2E from Icom is compact and convenient with an output of 1.5W**

Frequency modulation, F3, is currently by far the most often used mode and this fact is reflected in the amount of bandwidth allocated for this system.


A study of the band plan will show that a "multi-mode" section exists between 144.500MHz and 144.875MHz. Within this sub-band, excluding the specifically designated frequencies, it is possible to use any of the licensable modes of transmission. It is this section of the band that should carry any spill-over activity during crowded "lift" conditions. Regrettably, either through ignorance or deliberate lack of consideration, operation using inappropriate modes or frequencies, still takes place.


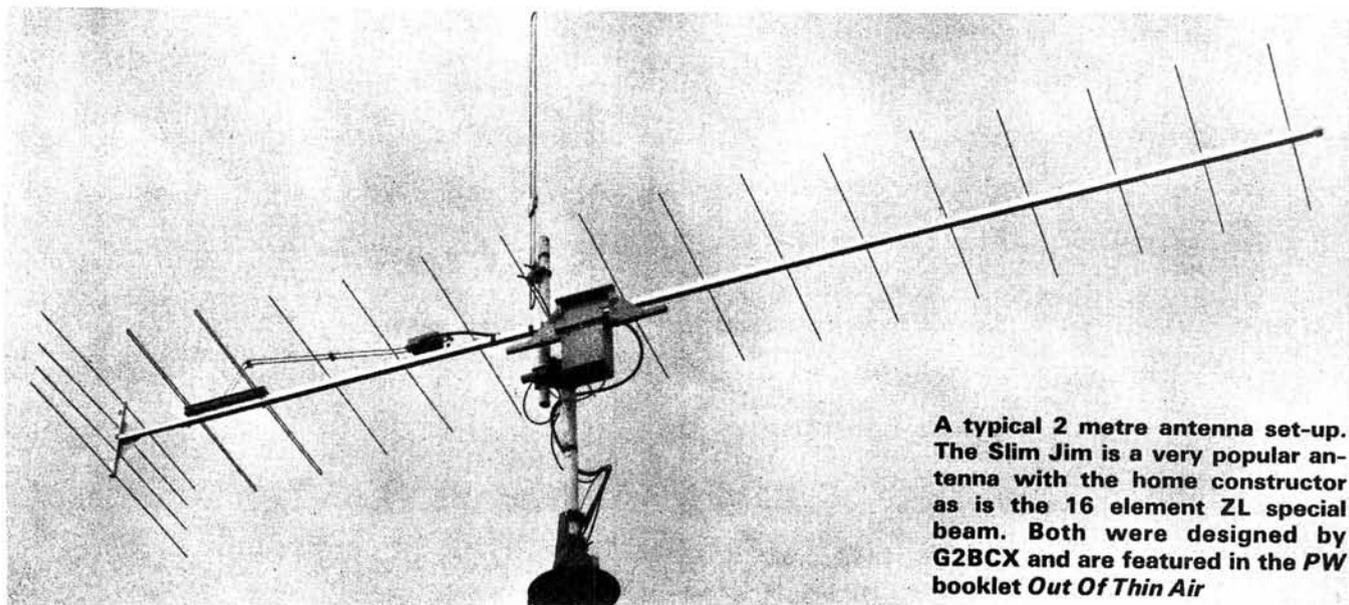
## Channelisation

Unlike the lower portion of the 2 metre band, the sub-band between 145.000MHz to 145.800MHz is divided into discrete 25kHz divisions, referred to as channels.

The amateur band specification for f.m. telephony on 2 metres restricts the maximum frequency deviation to  $\pm 5$ kHz from the nominal carrier frequency. In order to prevent adjacent channel breakthrough, the use of a 25kHz channelised system was introduced, providing a



**A typical 2 metre antenna set-up. The Slim Jim is a very popular antenna with the home constructor as is the 16 element ZL special beam. Both were designed by G2BCX and are featured in the PW booklet *Out Of Thin Air***



**Yaesu's 2 metre multi-mode transceiver—the FT480R enables the amateur to cover the whole of the 2 metre band including c.w., s.s.b. and f.m. modes. With 10W output interesting DX contacts can be made**

theoretical 15kHz of isolation between adjacent channels. In order to readily identify those channels, they are designated code numbers with letter prefixes. Channels used for single frequency transmission and reception (SIMPLEX) are designated prefix "S" and those used for repeater operation, with the necessity for separate transmission and reception frequencies (SEMI-DUPLEX) are designated prefix "R".

### Simplex Operation

This single-channel working mode for f.m. transmissions normally occurs between 145-200MHz (S8) and 145-575MHz (S23). As mentioned previously, f.m. equipped stations may use the sub-band 144-500MHz-144-875MHz, with the exception of notated frequencies.

By agreement the UK f.m. calling frequency is located at 145-500MHz (S20) and should be used only for the initial establishment of contact. To maintain the calling channel for its primary use, stations should shift to an agreed working channel, or all-mode frequency.

### Repeaters

No account of the 2 metre band could be complete without reference to the extensive amateur repeater system.

The 2m Repeater Datacard presented free with this issue indicates the extent of the network in the UK, up to February 1981. Two changes have occurred since the map was printed—GB3KR has become GB3KS and changed to channel R1, and the RSGB have found a hiccup in their computer program—GB3SB is on R0 not R2.

A repeater is a device designed, constructed, financed, and maintained by individual groups of radio amateurs primarily to assist with communication between mobile and portable amateur stations. The advent of repeater installations in the UK during the early 1970s heralded an enormous expansion in the number of licensed amateurs.

In the next article in this series, a full account of the history and operation of repeaters will be given.

## PROTECTING THYRISTORS—1

▶▶ continued from page 30



mon when large and expensive lamps must be protected from the stress of their own surge, in projection gear for instance. However, thermistors which can handle projection lamp currents are expensive and unreliable components. A control circuit which can limit lamp surge current without using a thermistor is shown in Fig. 10. This is the "soft start" dimmer. In this circuit, an unsmoothed d.c. supply is provided by T1 and the bridge rectifier, D1-4 (Waveform B). D8 clips this (Waveform C), but note that the voltage still drops to zero at the end of every half cycle. When power is applied to the circuit, C1 will begin to charge. C2 will also charge, but more slowly, and will only have enough voltage on it to trigger the unijunction transistor (Tr1) towards the end of the first half cycle. The unijunction in turn triggers CSR1 and CSR2. The lamp surge will be very small, however, because triggering occurs towards the end of the mains cycle and the mains voltage is low and rapidly decreasing at this point (Waveform D). As the voltage on C1 rises, C2 is able to trigger Tr1 earlier in successive mains cycles. Simultaneously the lamp filament is heating up and with every cycle its resistance is increasing (Waveform E). By the time the peak voltage is applied (Waveform F), the lamp filament has attained its normal resistance. Thereafter R10 can be used to dim the lamp in the normal fashion.

If the circuit is switched on when the mains voltage is at its peak, the voltage across the thyristors rises from 0 to 340V very rapidly. It is possible that a triac's dv/dt rating would be exceeded in this circumstance. The triac would then turn on and the full lamp surge current would flow, which defeats the purpose of the circuit. Therefore thyristors have been used to give a high dv/dt capability. Also, RC networks with steering diodes C3, R8, D6 and C4, R9, D7 act to limit the dv/dt. The action of these RC 'snubber' networks will be considered later in the series.

# AMATEUR RADIO EXCHANGE



## SERVICE WITH A SMILE

It's all very well offering special deals to customers, like free credit for twelve months, or big discounts for cash, but what most people really want is courtesy and helpfulness before they buy, and the prospect of good service afterwards. This is something we have always endeavoured to provide, but the growth of our business has put space at a premium in our well-known corner emporium . . . the only shop in London where you can see and try under one roof ALL the leading makes of Amateur Radio equipment . . . and have a cup of Brenda's coffee too.

## NEW SERVICING CENTRE NOW OPEN


So we have now opened separate premises across the road where, with first-class test equipment to hand in light and spacious quarters, we are confident that our engineers can offer really quick turn-round on guarantee work in particular, and on other servicing too. What's more, the new premises will also carry a wide range of components for the enthusiast who wants to build his own gear . . . just another service – with a smile! – from Brenda (G8SXY) and Bernie (G4AOG) at the shop with a smile.

**NOW WITH FM**

## ARE YOU A G8 ABOUT TO TAKE YOUR 'A' LICENCE? OR ARE YOU TAKING YOUR G4 STRAIGHT AWAY?

Either way, why not start listening right now on a Yaesu FT-101 transceiver? It really knocks spots off the average general coverage receiver, with better selectivity, better sensitivity, better stability . . . And remember, cooling fans and microphones come FREE with 101s from ARE!! So, buy your rig now, and claim your mic and fan when you get your G4.

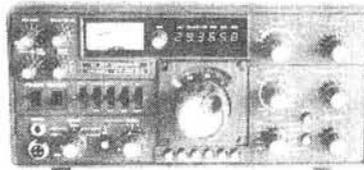**FT-101Z £488 inc. VAT FT-101ZD £569 inc. VAT**



### FRG-7

Still the finest value-for-money communications receiver on the market at only **£185 inc. VAT** and free Heliscan aerial worth **£15**.

### FRG-7700

Yaesu's latest receiver with FM right across the band and optional memory facility plus excellent filtering. **£299 inc. VAT** and free Heliscan aerial worth **£15** (Memory extra).



### BEARCAT 220FB

The super scanner which brings you all the excitement of the VHF and UHF frequencies . . . aircraft, marine, amateur, plus so much more. **£258.75 inc. VAT.**

### SX-200

Another of our sophisticated scanning receivers. Similar functions to the BEARCAT, but even wider frequency coverage, and with AM and FM right across its range. **£240 inc. VAT.**



## THE FANTASTIC NEW SONY ICF-2001

At last, from one of the world's electronics giants, not just a new HF communications receiver, but a whole new breed of radio which supplants the conventional multi-band concept and replaces tuning knob and dial with a direct-access tuning keyboard and Liquid Crystal Display. LCD digital frequency readout confirms exact, drift-free reception right across its range, AM/SSB/CW 150kc to 30 MHz and FM 76MHz to 108MHz, and LCD also provides memory indication for its six station pre-sets plus two auxiliary pre-sets giving instant reception of selected stations. As easy to use as a calculator, and so compact you can slip it into your briefcase . . . **. . . and all for the amazingly low price of just £149 inc VAT.**



Closed Wednesday, but use our 24-hour Ansafone service. LICENSED CREDIT BROKERS. \*Ask for written quotation. INSTANT HP AND 6 MONTHS NO INTEREST HP TERMS AVAILABLE FOR LICENSED AMATEURS AND BANK/CREDIT CARD HOLDERS.



Credit Card Sales by telephone.

**2 NORTHFIELD ROAD, EALING, LONDON, W13 9SY. TEL: 01-579 5311**

*So easy for Overseas visitors – Northfields is just seven stops from Heathrow on the Piccadilly Line.*



# Multicore makes for a better job...


The biggest name in solder worldwide



**Tool Box Reels**  
3 flux-cored solders that cover a range of electrical and non-electrical applications. ARAX 40/60 tin/lead size 11 £3.91 each. ALU-SOL size 4 £6.90 each. ERSIN 40/60 tin/lead size 3 £3.91 each.



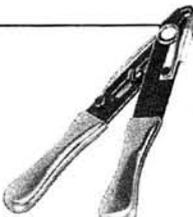**Solder Cream**  
For precision soldering. Solder Cream is a mixture of solder powder and flux. Electrical/electronic ("Ersin" flux) size BCR10 £1.38. Metal joining ("Arax" flux) size BCA14 £1.38. Stainless steel and jewellery ("Arax" flux) size BCA16 £3.22.



**Wire Strippers & Cutters**  
No tool box is complete without this handy wire stripper which will adjust to most sizes of flex and cable. Easy grip plastic coated handles. Automatic opening. Handle locking device. Ref 9 £2.69.



5-CORE SOLDER, PC, EXTRA THIN FAST FLOW, ARAX, ALU-SOL, 96S

**Handy Dispensers**  
Size 19A 5-core solder Ersin flux 1.22mm dia for electrical work £0.97.  
Size PC115 extra thin gauge for small electrical components £1.15  
Size SV130 5-core Savbit specially for copper bits and wires £1.61  
Size AR140 Arax solder for all metal repairs except aluminium £1.38.  
Size AL150 Alu-sol for most metals especially aluminium £1.93.  
Size SS160 for stainless steel and silver jewellery £2.53.

**Soldering Flux Paste - Ersin**  
A fast, non corrosive rosin flux for general and electrical soldering applications. Use with Ersin Multicore solder. Size RF10 £0.69.  
Arax soldering flux paste also available for general metal working. Size AF14 £0.69.




**Ersin 5-core Dispenser**  
Handy dispenser for all electrical and electronic applications. Size 6 £0.58.




**Savbit Dispenser**  
Handy dispenser ideal for radio, TV and similar work. Reduces copper erosion. Size 5 £0.90.
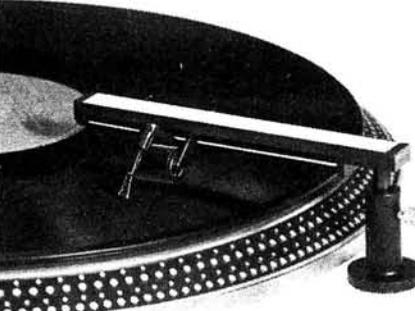
# ... Bib makes for a better sound



**Electronic Cassette Head Demagnetizer**  
Demagnetizes the tape heads to improve performance and reduce background noise. Audible tone indicates demagnetizing action.  
Works on all cassette machines including in-car. No external power needed. Ref 23 £10.49.



**Bib Groove-Kleen**  
For single play turntables. Velvet pad and tracking brush track across the record as it plays picking up harmful dust to improve sound performance.  
Ref. 101B £4.69 British Patent Number 1519881



**Cassette Tape Hand Winder**  
Winds a C90 cassette in 60 seconds - faster than most cassette machines. Especially ideal for battery powered recorders to save consumption when used on fast wind.  
Ref 78 £1.66. British Patent Number 1443628



**Bib Groove-Guard-XL-2**  
Unique formula liquid, when applied to record, gives anti-static protection and helps reduce friction between stylus tip and groove. Complete with pump spray dispenser and special cleaning pad. Treats up to 12 LPs. Ref 27 £2.60.



**Record Valet and Liquid**  
Handy kit contains special anti-static fluid and velvet record cleaning pad. Ideal to remove dust and other particles from records and provides an anti-static effect to help keep your records clean.  
Ref 47 £3.45.




**Tape Head Cleaning Kit**  
Contains everything needed to clean and maintain the heads, capstan and pinch wheel on all types of cassette and tape machines. Kit includes cleaning and polishing pad, special liquid and handy inspection mirror. Ref 25 £2.48.  
British Patent Number 1485069.



**Bib Hi-Fi Accessories Ltd.**  
Kelsey House, Wood Lane End,  
Hemel Hempstead,  
Hertfordshire HP2 4RQ.  
Telephone: (0442) 61291.

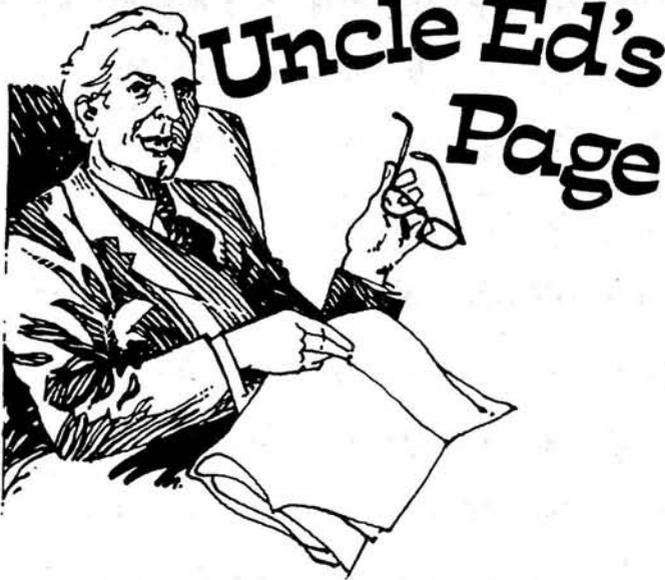All prices given are recommended retail including VAT. If you have difficulty in purchasing your Multicore solder product or Bib Hi-Fi accessory, send direct to the address above quoting the reference number and including your remittance plus 40p P&P. Send SAE for free colour catalogue showing complete range.



**A monthly look at some aspect of the radio/electronics hobby that seems to bug the beginner, or occasionally a more advanced topic seen from an unusual angle.**

Mention the words "equivalent circuit" to a newcomer to radio or electronics, and you'll get either a blank look or a comment along the lines of: "A way of explaining a simple component by turning it into something more complicated." I think that's often an understandable attitude—in the case of a transformer, for example, the equivalent circuit adds nine components ( $L$ ,  $C$  and  $R$ ) to explain the various losses in the windings and core. An equivalent circuit which is very much simpler, and which is very, very useful is one worked out many years ago by a gentleman called Thevenin. It will help you to understand power supply regulation, "voltage" and "current" sources, and also attenuators.

Any-one who has played around with batteries and torch bulbs will have found that connecting a second bulb across a small battery will cause the first one to glow less brightly, especially if the battery isn't particularly fresh. If you were lucky enough to have a voltmeter or a multimeter, you would have discovered that the voltage across the battery terminals dropped when you connected the second bulb. On the other hand, if you left the voltmeter connected across the battery and removed **both** bulbs, the voltage went up. See Figs. 1 and 2.

If we ignore the current taken by the meter itself, which should be pretty small, the voltage reading across the battery terminals with no bulbs connected is the open-circuit voltage, also called the no-load voltage or the e.m.f. (electromotive force).

The reason the voltage at the battery terminals drops when a load is connected (a load is anything that consumes power, like our torch bulbs), is that any source of electrical power has some losses in it. The battery terminal voltage you measure when the load is connected is called the on-load voltage or the p.d. (potential difference). In fact, p.d. is a general term for the voltage difference between any two points in a circuit.

The difference between the off-load and on-load voltages is called the regulation of the supply, which you will often see quoted in the specifications for mains transformers or stabilised power units. It's usually expressed as a percentage. If, for example, you had a supply which measured 10

volts off-load, but dropped to 9 volts on full load, the regulation would be 10 per cent. (Just for completeness, I should mention that some people do the calculation the other way round, taking the rise in voltage from full-load to no-load, which produces slightly different figures.) If you connected a load which took only half the supply's rated current, the voltage would drop to 9.5 volts, illustrating that regulation is a linear relationship, in other words, doubling the current drawn will double the voltage drop.

If you go on trying to draw a bigger and bigger current, you will eventually reach a state where the supply voltage drops rapidly. This may be due to a component going up in smoke, or (hopefully) to a fuse or other overload protective device operating to safeguard the whole circuit. This applies regardless of whether you're talking about a battery, a power unit, or even the mains supply in your house.

If our 10 volt supply had a maximum rated load of 1 amp, and that was the current which we drew to cause the output to drop by 1 volt, then from Ohm's Law ( $R = V/I$ ) we might guess that somewhere in the supply circuit there was a 1 ohm resistance scuffling about. This takes us back to the beginning of this article, and to Mr Thevenin (you thought I'd forgotten about him, didn't you?), because this was exactly what he proposed in his theorem, on which he based his equivalent circuit.

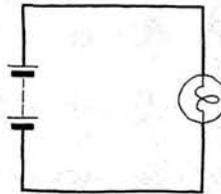


Fig. 1

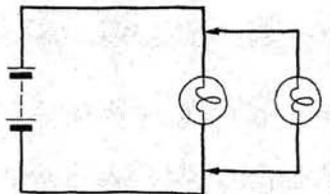


Fig. 2

WRM353


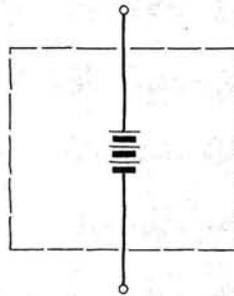


Fig. 3

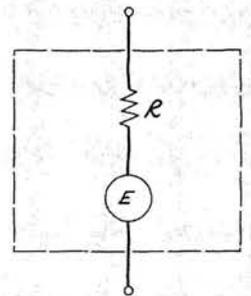

In Fig. 3, I show the Thevenin equivalent of a practical power source, which is made up of a "perfect" electrical generator  $E$  (having zero internal resistance), in series with a fictitious resistor  $R$ , whose value defines the regulation of the supply in the way I described above. Of course, there isn't really a resistor there—it's just the equivalent of the various losses in supply, but it makes it less complicated to think of just one thing at a time.

When we use a power supply to drive something like an audio power amplifier, the current drawn is varying constantly, in sympathy with the audio signals passing through the amplifier. The regulation of the supply for rapid variations like these is not necessarily the same as for a "once-off" change, say from no-load to full-load. For rapidly-varying loads, we would replace the resistance  $R$  by an impedance ( $Z$ ), which in simple terms is the a.c. equivalent of resistance. For simplicity, I shall treat them as being identical in value.

continued on page 64 ▶▶▶

# ULTRA FAST

# STEREO PEAK INDICATOR

G.S.MACAULEY

One of the most frustrating things about tape-recording is knowing whether one has the correct recording level or not. True, most tape decks these days are equipped with VU meters, but in some cases these are unreliable in the extreme. The reason being that they are mechanical devices and cannot respond very rapidly to musical transients, which are often of high amplitude compared to the mean signal level and of extremely short duration. Even very high quality meter movements have a response time to changes in signal amplitude usually found to be tens of milliseconds.


In recent years i.e.d. VU meters have been constructed which feature very fast response times. To cope with such extremely short transients the electronics required need to be fairly complex and such devices are expensive to construct. An alternative circuit, that is fairly simple and inexpensive to construct, is a peak level indicator. This device will give an indication only when a preset level is exceeded. It can be adjusted to any convenient point (within reason) by a simple preset control.

The circuit shown features an attack time of ten microseconds and holds the indicator on for a second each time the preset level is exceeded. A block diagram of the device is shown in Fig. 1.

The level detector comprises a fast comparator, whose non-inverting input is supplied with a constant voltage by means of a simple series regulator. This regulator is formed by R8 and D1 and the potential divider R1, R2 and R3. Input signals are fed into the inverting input via C1 and R4. When a large enough positive going input signal is fed into the circuit the inverting input becomes more positive than the non-inverting input. At this point the output of the comparator goes abruptly negative, triggering the monostable whose output goes positive for an externally set period of time—allowing current through to the i.e.d., which illuminates indicating the passage of the transient.

## Circuit Description

Fig. 2 shows the circuit diagram of the peak indicator. The comparators are contained in a quad package, the LM339, and the monostables in a NE555 which is a dual version of the well-known 555 timer. Two 555s could be used instead of the 556 in this circuit, but the layout would have to be altered and in all probability more space would be required. The comparators have a very fast rise and fall time, typically one microsecond. In common with most in-

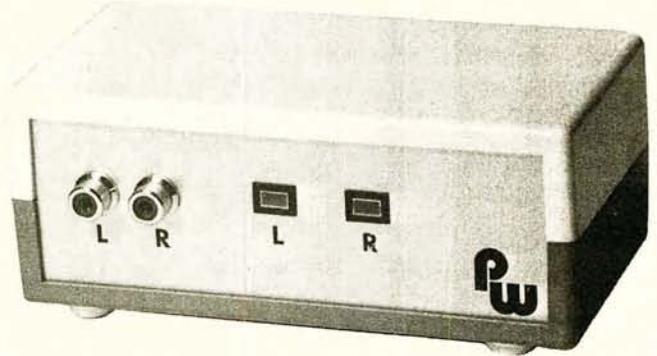

tegrated comparators the output stage is an *npn* transistor with an uncommitted collector. In order for these to operate properly it is necessary to refer the collector to the positive supply line. This is done here by R9 and R10, these two resistors also fulfil a second function in that they refer the trigger inputs of IC2 to the positive line.

Like the 555 timer, with which most readers will be familiar, the trigger inputs of the 556 have to be taken low to produce a monostable period. The actual length of the pulse obtained from this i.c. is dependent upon the time constant of the timing components. In this circuit the time constant has been set at one second, this allows all transients to be easily observed. The major factor that determines the attack time constant of the circuit is the high

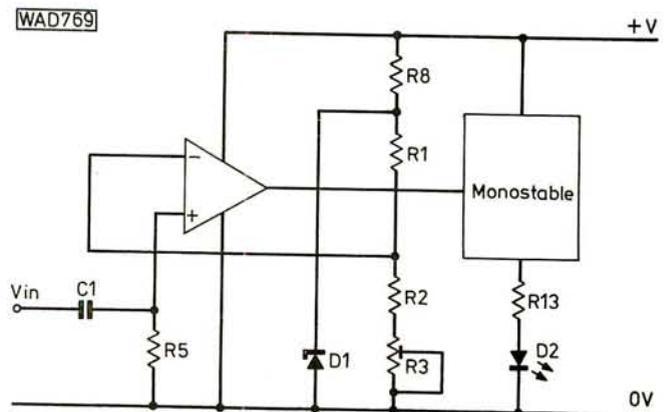


Fig. 1: Block diagram of one channel of the peak indicator

frequency response of the monostable. In other words the shortest negative going transient that will reliably trigger it. With this i.c. it is less than 10µs.


Since the output stage of each of the monostables will source 200mA, the limit of the current supplied is set by the available power supply and the maximum rating of the l.e.d.s employed. For practical purposes the current supply to the l.e.d.s has been fixed at 10mA, as this was found to give a sufficiently bright display.

## Construction

Construction is quite straightforward, with all of the components being mounted upon the Veroboard panel shown in Fig. 3. Care should be taken when mounting the i.c.s and electrolytics to ensure that the correct orientation is observed. Also, the board should be checked to ensure that no bridges of solder have spilled across the tracks.

To check the operation of the circuit it should first be connected to a 9V battery. At switch-on both l.e.d.s should be extinguished. If not, switch off and check the wiring to and from the comparators. If, and when all is well, a piece of wire should be connected to the positive terminal of the battery and the other end touched onto both inputs in turn. When connected by the wire the l.e.d.s should illuminate for approximately one second and then extinguish.

With the components specified the sensitivity can be varied by the preset from 100mV to 2V, thus catering for the line input sensitivities of almost all available tape-

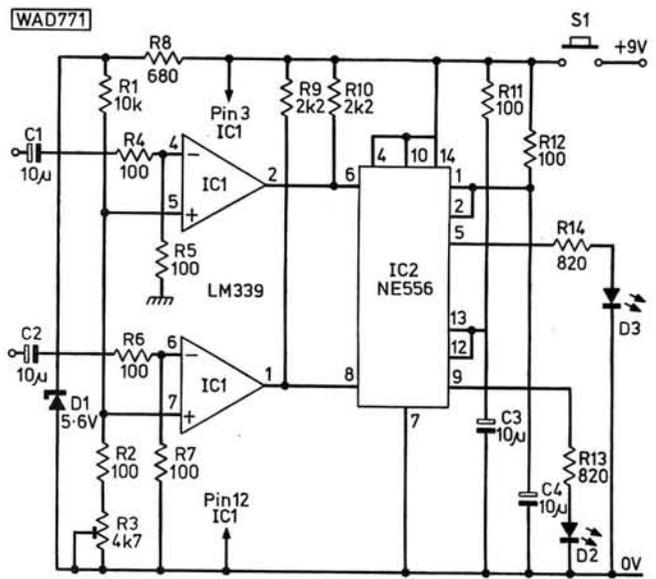

**Fig. 2: Complete circuit diagram of the unit. Note that resistors R4,5,6,7,11 and 12 should be 100kΩ**

recorders. This range can be extended by increasing the value of R4 and R6 so that the circuit can be used to monitor the output power across a loudspeaker system. A better method of increasing the range is to precede the cir-

*continued on page 64* ▶▶▶

## ★ components

### Resistors

¼W 5% Carbon

100Ω	1	R2
680Ω	1	R8
820Ω	2	R13,14
2.2kΩ	2	R9,10
10kΩ	1	R1
100kΩ	6	R4,5,6,7,11,12

Sub-Miniature Skeleton Preset

4.7kΩ	1	R3
-------	---	----

### Capacitors

Axial Electrolytics 25V

10µF	4	C1,2,3,4
------	---	----------

### Semiconductors

Diodes

5.6V 400mW	1	D1
Red l.e.d.	2	D2,3

Integrated Circuits

LM339	1	IC1
NE556	1	IC2

### Miscellaneous



Veroboard; PP3 battery; Battery clips.

Track breaks


at:-

A4  
B4  
C4  
D12,15,23  
E12,15,23  
F12,15,23  
G12,15,23  
H12,15,23  
I12,15,23  
J12,15,23  
N8,14  
O14  
P26  
Q26  
R26

WAD770

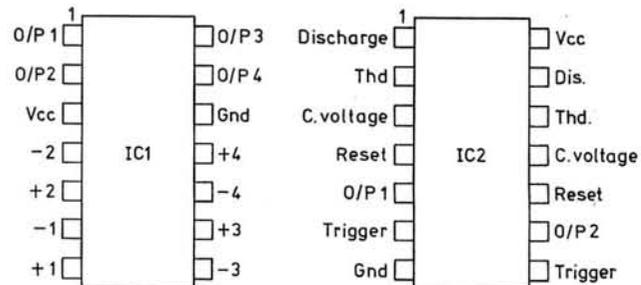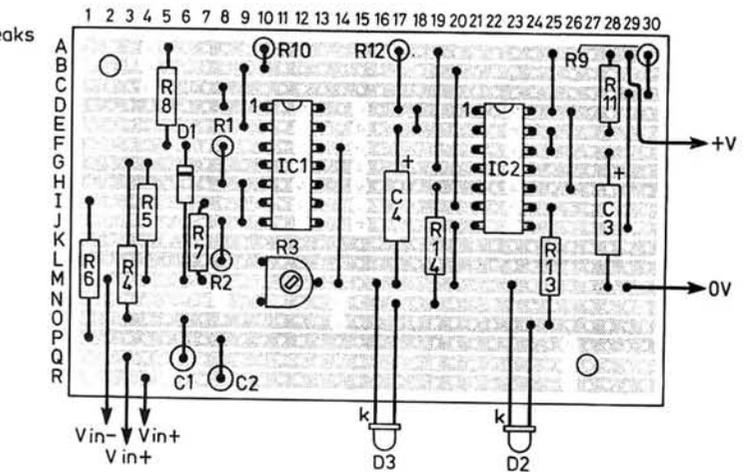

**Fig. 3: Veroboard layout and integrated circuit pin connections**

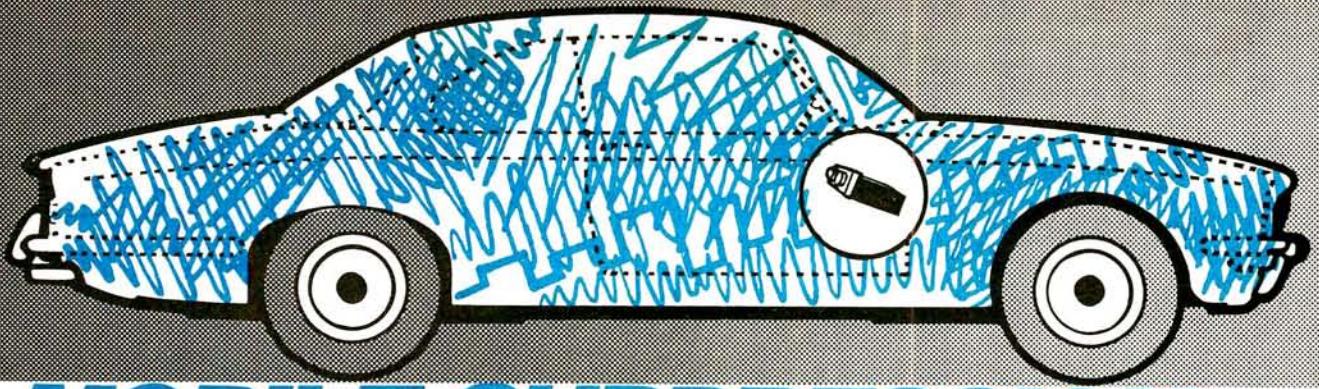

# MOBILE SUPPRESSION TECHNIQUES

## PART 2

John M. FELL G8MCP

The first part of this article dealt with the suppression requirements of vehicle h.t. systems. This concluding part details the suppression requirements of standard electrical equipment and accessories.

### Voltage Regulator

Associated with the charging system, the voltage regulator may be incorporated within the alternator body or contained in a separate module. The noise effect is a whine or crackle, only apparent some moments after starting the engine and generally not apparent at idling speed. Unlike ignition noise the level of interference stays constant with increase in engine revolutions. A test for this form of interference breakthrough consists of applying a load to the generating system, such as the headlamps and rear windscreen heater. If the regulator is the culprit the noise will diminish or stop. With Lucas ACR alternators, the cure is to connect a  $1\mu\text{F}$  capacitor type LS627 from the warning light (IND) terminal to earth. Other types of alternator, with separate control box, require a  $1\mu\text{F}$  capacitor fitting between the positive terminal of the control box and earth. **Never connect a capacitor to the field terminal.** With a d.c. (dynamo) system it is necessary to connect a  $1\mu\text{F}$  capacitor between the control box "D" terminal and earth.

### Instrument Stabiliser

Intermittent bursts of crackle, sounding like the tearing of paper or frying of eggs, are usually caused by the instrument stabiliser. This is an electro-mechanical device and is affected by vibration. A sharp "thump" on the instrument panel should provoke the noise, if this device is at fault. A  $1\mu\text{F}$  capacitor connected from the feed terminal "B" to earth, and an in-line 3A choke in the feed and instrument supply leads, should clear the problem. In extreme cases, replacement with a purpose-built electronic version will be necessary.

### Ancillary Equipment

Because the items within this category of equipment are used occasionally, interference from these sources will be apparent only when the specific devices are switched on.

This makes the assessment of the suppression effectiveness relatively easy, unlike h.t. and generator system noise which is usually mixed together.

### Windscreen Wiper Motor


Characterised by an oscillating crackling noise, the wiper motor is a frequent source of interference in wet weather. The initial cure is to bond the metallic body to earth, as most devices "float" on rubber mountings. If the noise persists it will be necessary to fit 7A in-line chokes to all the supply leads, positioned close to the connector plug. In the case of two-speed motors, a total of five chokes are required, one in each lead.


### Screen Washer Motor

Becoming a more popular fitting in modern vehicles this device can produce a high-pitched whine when activated. A  $1\mu\text{F}$  capacitor from the positive supply terminal to earth should remove the noise, but in persistent cases, insert 7A in-line chokes in both supply leads.
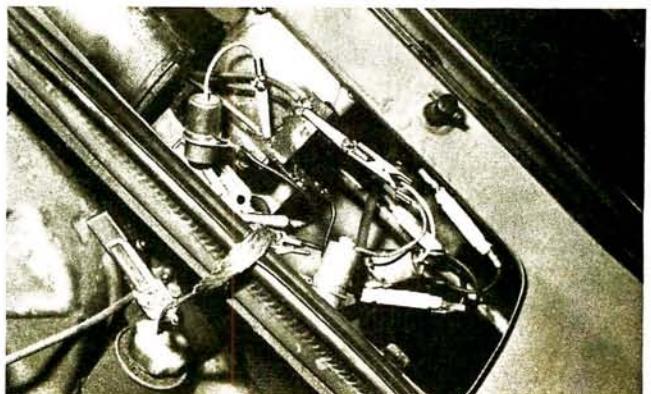
### Stop Lights

Operation of the brake pedal can produce "clicking". The switch element is either mounted in the brake pipe circuit and activated hydraulically or fitted behind the pedal and mechanically actuated. A  $1\mu\text{F}$  capacitor from the supply lead to earth will stop interference from this source.



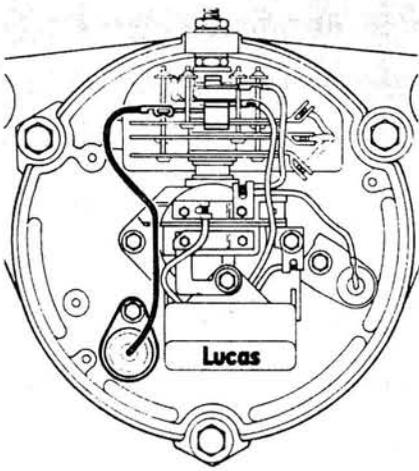

◀ Fig. 10: Generator output; whine varying with engine speed. Fit capacitor between output terminal and earth. Lucas 15-16-17-18 ACR alternators—LS629. 20ACR—LS682. 23-25ACR—LS673. Dynamos—LS628.


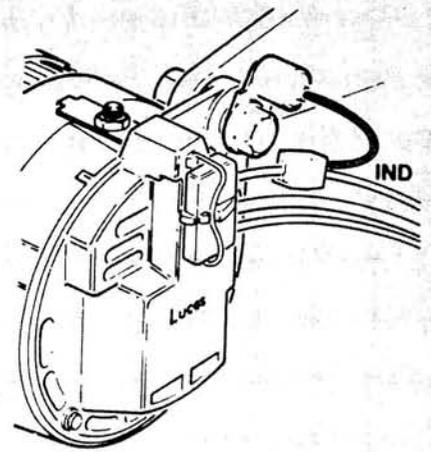


Fig. 11: Other alternators including Lucas, Delco, Bosch and Femsu equivalents. Fit  $1\mu\text{F}$  capacitor between IND (warning lamp) terminal and earth. ▶

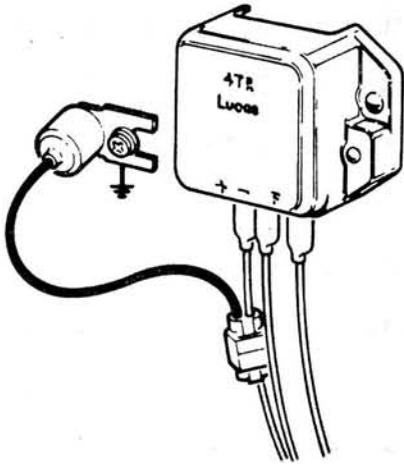

◀ Fig. 12: Voltage regulator; whine or crackle only apparent some moments after starting; disappears when headlamps and heated rear screen are switched on. Generally not apparent at idling speed. Fit  $1\mu\text{F}$  capacitor between + terminal and earth.


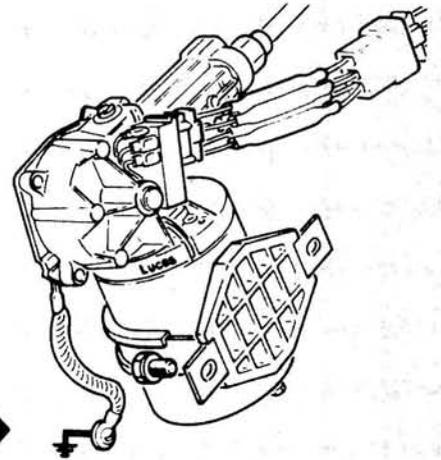


Fig. 13: Wiper motor; crackling when wipers operated. Bond body to earth with strap. If necessary connect LS639 chokes in each supply lead. For permanent magnet versions use LS641 choke assembly. ▶

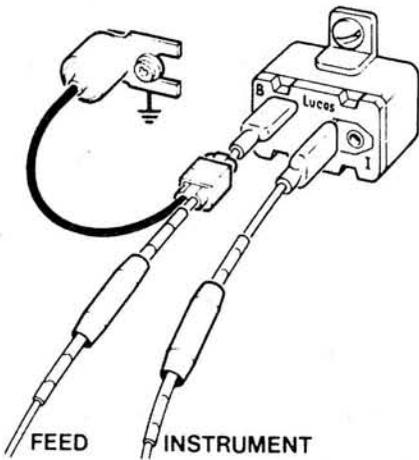

◀ Fig. 14: Instrument stabiliser; intermittent bursts of crackle, provoked by tapping dashboard. Fit LS640 choke in feed, if necessary connect LS637 capacitor across B and E terminals (or B and earth) and LS640 in instrument supply lead.

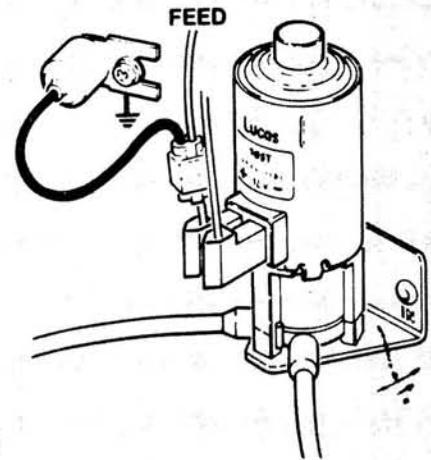


Fig. 15: Screenwasher motor; whine when washers operated. Connect LS637 capacitor between washer feed terminal and earth. Occasionally it is necessary to fit LS639 chokes to supply leads. ▶

## Electric Fuel Pump

Regaining popularity, the solenoid actuated, electric fuel pump is the cause of crackle or "ticking" when the ignition is switched on. The repetition rate will depend on the fuel demands made by the engine. The greater the demand, the higher the repetition rate. Once again, fit a  $1\mu\text{F}$  capacitor between the feed input terminal and earth, including a 7A in-line choke if noise is not completely eliminated.


Motor-driven pumps may be suppressed by a  $1\mu\text{F}$  capacitor between positive supply and earth, adding a 7A in-line choke to both leads if not completely cleared.

## Heater Motor

Whines and crackles when in use are the typical effects produced by the heater motor. To cure, fit 7A in-line chokes in all the supply leads and, if necessary, a  $1\mu\text{F}$  capacitor between each supply lead and earth.
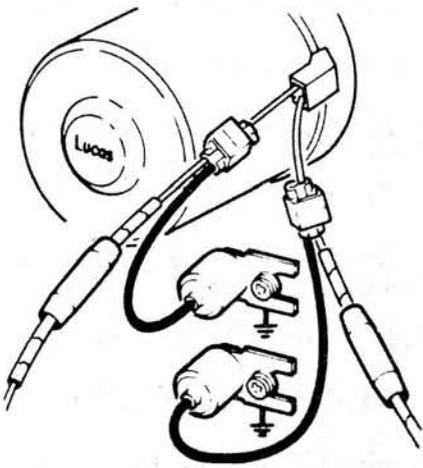
## Direction Indicator Flashers

The bi-metallic switching element can cause distinct "clicks" in the received audio when the indicators are in use. The cure is simple and requires the insertion of a  $1\mu\text{F}$  capacitor between the "B" terminal and earth.



◀ Fig. 16: Heater motor; whine or crackle when heater motor operated. Connect LS639 choke in series with supply leads. In persistent cases fit LS627 capacitor between each feed and earth.


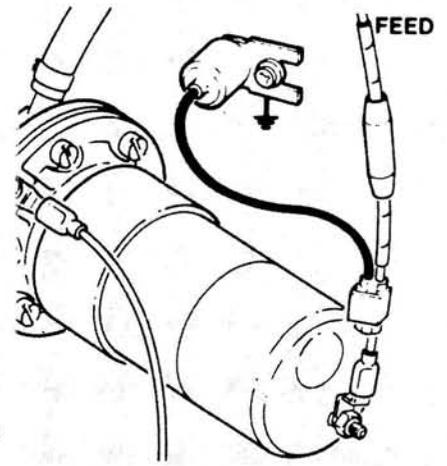


Fig. 17: Fuel pump; whine, crackle or ticking when ignition is on. Connect LS627 capacitor between supply lead and earth. If necessary fit LS639 choke in feed lead. ▶

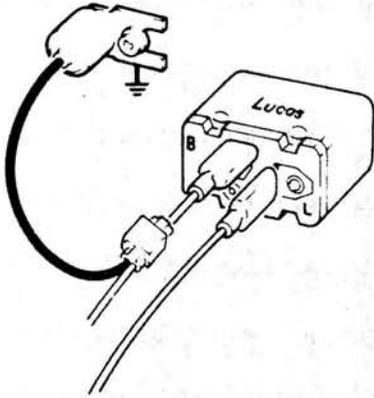

◀ Fig. 18: Indicator flashers; clicking when flashers are operated. Connect LS627 capacitor between B terminal and earth.


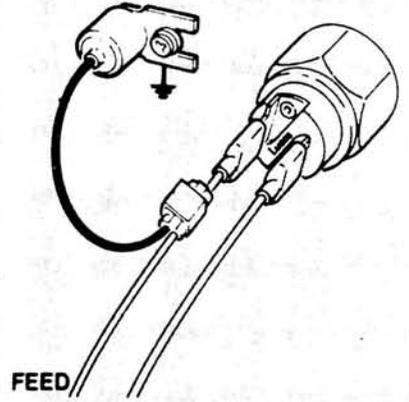


Fig. 19: Stop lamp switch; clicking when brakes are operated. Connect LS627 capacitor between feed terminal and earth. ▶

FEED

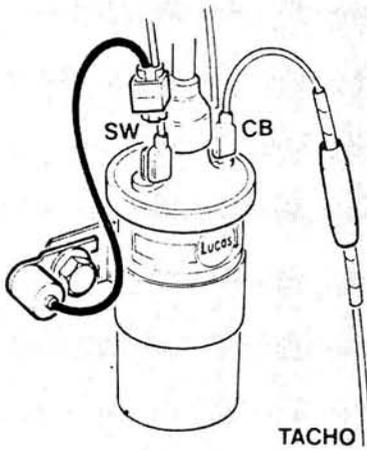

◀ Fig. 20: Electronic tachometer feed; ignition crackle still present after normal h.t. suppression—confirmed by disconnecting tacho lead. Connect LS640 choke in take-off wire at coil/distributor end.

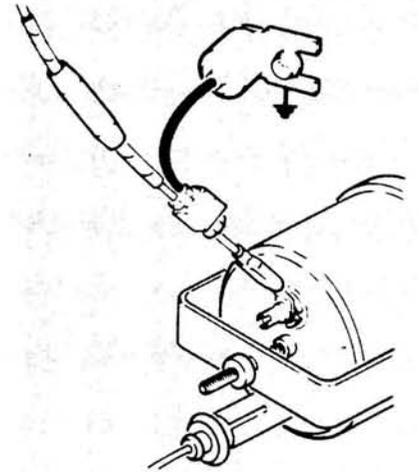


Fig. 21: Electric clock; regular ticking with ignition off. Connect LS627 capacitor between clock feed and earth. If necessary, fit an LS640 choke in supply lead. ▶

## Electric Clock

Analogue format electric clocks can produce a “regular ticking!”, mainly noticeable when the ignition is switched off. A  $1\mu\text{F}$  capacitor between the positive input terminal and earth should restore the silence. Again the insertion of an in-line choke will be necessary in persistent cases.

## General Notes on Fitting

The sequence of suppression methods detailed in this article represent tried and tested approaches. When a single suppressor does not appear to make a worthwhile improvement **do not remove it** before trying a further device; their **combined** effort may be required.

The depth of suppression complexity can vary to a large degree and is related to the individual vehicle, signal strengths available, receiver design and operating frequencies. Whilst manufacturers will often recommend a list of items to be suppressed, large variations can even occur between examples of the same model.

Successful diagnosis and cure of interference can be time consuming and frustrating. However, it has been the writer's experience that a group approach to the problem is best. “Quick-fit” suppression items can be made up and fitted, the required items having been established you can then order the necessary parts and install permanently.

It is well worth repeating that optimum effects will be obtained by utilising the shortest possible lead lengths and locating suppression items close to the items being suppressed.

Lucas deliberately do not fit terminals to their general-purpose capacitors for this reason. From the financial point of view, try capacitors first, they are cheaper than chokes.

On certain vehicles, notably Italian and French, the gear box and steering column can radiate interference within the vehicle interior. All parts of the offending components must be bonded to earth using heavy braided cable, being careful to allow for normal movements.

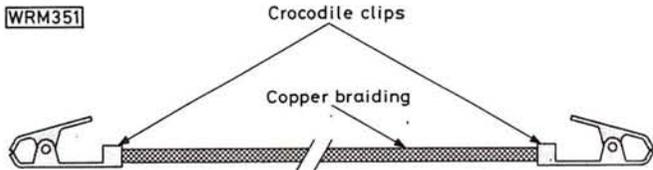



Fig. 22: Quick fit bonding strap.

## Equipment Supply

The supply leads of transceiving equipment may be further filtered by the use of a suitably rated "pi" network line filter to prevent the entry of interference by this route. The current rating of the components will depend on the current consumption of the equipment to be used. Wherever possible, run separate supply leads directly from the vehicle battery to the equipment. Do not forget to use an additional, suitably rated, in-line fuse at the battery terminal.
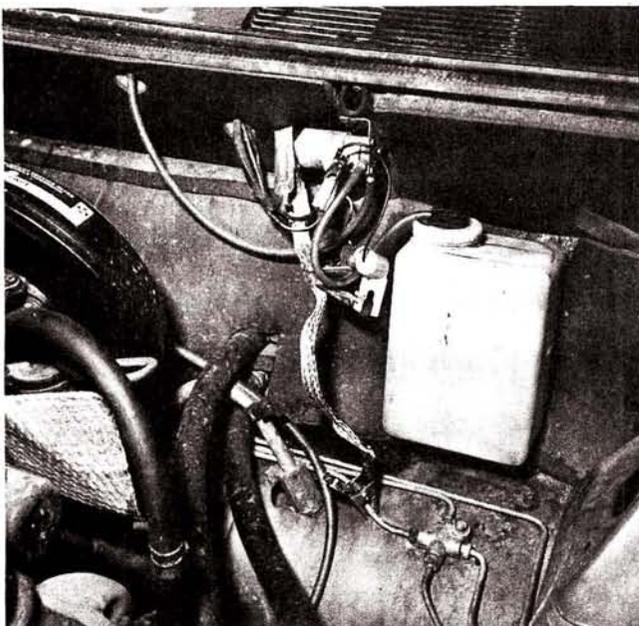
## Fibre-Glass Bodied Vehicles

The steel bodywork of conventional vehicles plays a large part in suppressing r.f. interference. With vehicles having a bodywork made from fibre-glass the suppression requirements become greater. Even these vehicles can be satisfactorily dealt with, usually involving the bonding of aluminium building foil or light gauge wire-mesh to the underside of all the bodywork. In this case frequent bonding of the foil to the main metallic frame and earth is required. Further improvements can also be made by spiral wrapping the wiring loom with foil and earthing. Carbon fibre reinforced bodysells usually offer similar suppression characteristics to those with metallic bodywork.




## Antenna Positioning

Although not part of the suppression system, the antenna and its location, is of prime importance to a vehicle installation. In general terms the antenna should be mounted at a point on the vehicle that provides the greatest practical distance between it and the engine compartment.

For l.w. and m.w. installations mounting the antenna onto the front wing or roof is recommended. This has the combined advantage of bodywork screening and maintenance of minimal feeder length. Losses introduced by the use of extension cables often reduce the available signal to very low levels and thus makes the receiver more prone to local interference pick-up. Vertical antennas for the h.f. bands tend to be physically large and usually need to be mounted at the rear of the vehicle for mechanical stability. This location will also afford the lowest levels of direct emission but attention must be paid to secondary emissions from non-earthed items such as the exhaust pipe.

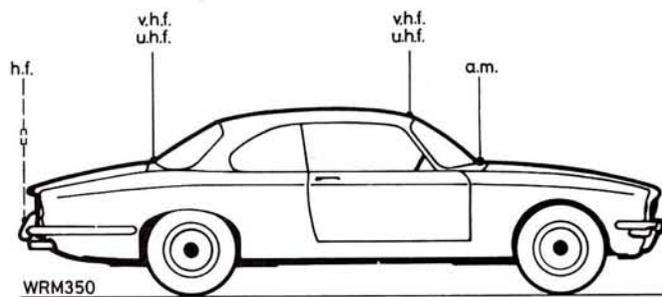The smaller antennas used for v.h.f. and u.h.f. are ideally located on the roof of the vehicle, allowing the utilisation of the natural ground plane. Boot lid mounting is also a preferred method but ensure that the mounting base is provided with a good earth. (One Japanese car actually uses the boot lid as an antenna.)



## Sources of Components

The largest manufactured range of specialist suppression components in the UK is marketed by the Audio Systems Division of Lucas Electrical Ltd. Items from their range are available from most reputable motor factors. If difficulty is experienced in obtaining items, Lucas has a network of 300 distribution centres throughout the UK, listed under "Garage Services" in *Yellow Pages*, who are able to provide any items from stock within four days.

The Sparkrite h.t. leads shown in the illustrations are manufactured by Electronic Design Associates and are also available through all normal sources.

When ordering parts the part number and description of the device should always be quoted to avoid confusion between similar items.

## Acknowledgments

The author is indebted to Lucas Electrical Limited and to Electronic Design Associates, for their permission to allow publication of details from their suppression range. Personal thanks for their invaluable technical advice and assistance go to Mr D. W. Morris, C.Eng, MIEE, G3AYJ, Mr John S. Davenport G8SOO and Mr Barrie Orme G8OFE.

Further information about the Lucas range of suppression components and recommendations for specific vehicles may be obtained from Mr J. S. Davenport, Audio Service Manager, Lucas Electrical (Parts & Service Division) Limited, Great Hampton Street, Birmingham B18 6AU. ●



# TONO

## θ-7000E

# COMMUNICATIONS COMPUTER

The Tono θ-7000E is a communications computer which will transmit and receive in c.w. (Morse), RTTY (Baudot) and ASCII, and display the messages on the screen of a v.d.u. or u.h.f. TV set, or as hard copy on a dot matrix printer.



Your reviewer is competent in c.w. operation and typing, but has had no previous experience of the RTTY mode. Therefore, the manufacturer's instruction manual, in conjunction with the RSGB *Amateur Radio Operating Manual* and the recent *PW series Introducing RTTY*, had to form a primer in RTTY operation generally.

As will be seen from the specification table, the θ-7000E incorporates a very comprehensive range of features indeed. The instruction manual advises practice with a TV set before using with a transceiver, and this proved very necessary. In fact, most of the test periods were spent that way, and even after a couple of months of intermittent use, new features were still being discovered and explored. The instruction manual is written in "Oriental English" which although adequate in straightforward items, does get rather lost in the more sophisticated features, of which there are quite a few.



The most frustrating feature at first was that after following instructions for, say, entering copy into one of the memories, the machine would just sit there, defying all attempts to make it do what it was supposed to do, until it was eventually discovered quite by accident, that the Space bar acted as an "Execute" key, and caused the beast to spring into action when depressed. So far as I am aware this is not a normal feature of RTTY nor computer operation, but perhaps my lack of previous experience is letting me down here. Certainly there is no mention of it anywhere in the instruction manual.

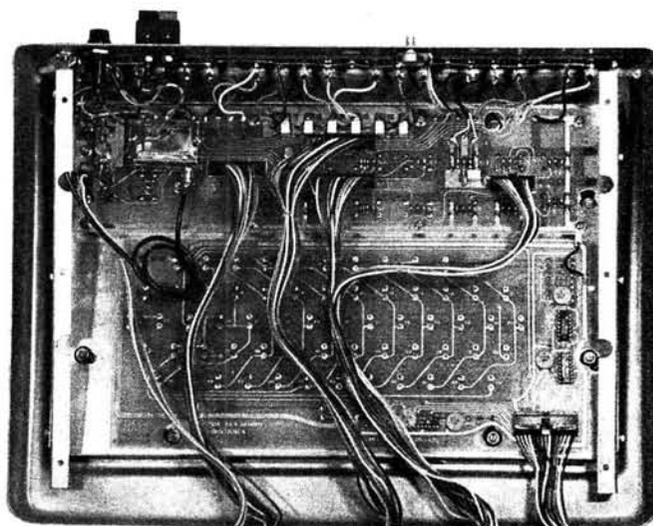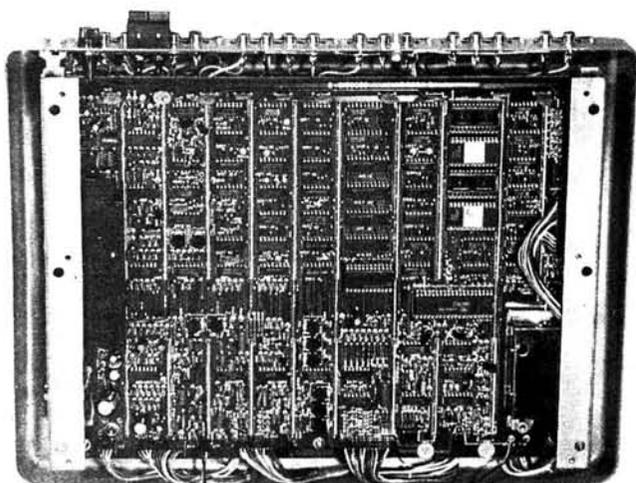The θ-7000E is housed in an attractive sheet steel cabinet which provides adequate screening so far as our tests showed, both **from** an adjacent 100W h.f. transmitter, and



The computer/control circuitry is housed on one large printed circuit board (left), while the switches and keyboard are mounted on two more (right)

to an adjacent h.f. communications receiver. All input and output connections are at the rear of the unit: spring terminals for the nominal 12V d.c. supply,  $\frac{1}{4}$ in jack for headphones, multi-way connector for the printer, and "phono" sockets for the rest.

Within the brief space of this review, I cannot hope to describe all the features of this very versatile unit. The Instruction Manual takes 30 pages to do so, regrettably somewhat inadequately. The Specification table summarises the main points, and the following notes add some detail:

**Characters:** "QBF" (Quick Brown Fox) and "RY" test messages are pre-programmed. The keyboard follows the standard typewriter layout.

**Input:** The required a.f. input level from a receiver is 50mV-1V. An anti-noise circuit eliminates garbled display in no-signal conditions.

**AF Input Frequency:** Accurate tuning of the incoming signals to the a.f. filters is aided by i.e.d. indicators.

**Remote Control Keyer:** Provides Transmit/Receive control of associated radio equipment, and can be automatic or manual.

**Number of Characters and Pages:** The first page can be divided in two. The lower half displays received signals, the upper half messages to be transmitted. These can be edited whilst receiving. A word-wrap-around function prevents the last word on a line being split in two in receive mode.

**Battery Backed-up Memory:** The messages put into Channels 1-6 can be repeated from 1-9 times at will. The message put into Channel 7 can be subdivided into four parts.

**Buffer Memory:** For composing and editing messages for transmission. Can be used whilst simultaneously receiving.

**Output for Oscilloscope:** Provides "cross" tuning pattern. Output level 1.2V p-p into 1M $\Omega$  minimum.

**AF Output:** The internal loudspeaker is muted when headphones are plugged in.

For anyone trying to learn or improve their Morse Code, the  $\theta$ -7000E can also form a useful tutor/exercise aid. It will produce individual characters at various speeds at the press of a key. It will decode Morse from a receiver or tape to provide a simultaneous visual readout. It will act as a "listener/decoder" to Morse which you send to it by means of a key plugged into the back of the unit, producing clean copy on the TV screen if you have a good "fist", or gibberish if you don't (well—I never did think my sending with a mechanical bug-key was very good!). It will even play back to you, in perfect Morse, what it thinks you just sent to it. I don't suggest you go out and buy one just for this purpose, but if you want it for RTTY, then you get that lot thrown in, as it were.

Note that under the terms of the current UK Amateur Transmitting Licence, Morse (c.w.) operation is not permit-

## ★ specifications

### Code:

CW (Morse), RTTY (Baudot Code), ASCII

### Characters:

Alphabet, Figures, Symbols, Special characters

### Communication Speed:

CW receiving: 25-250 Characters/Min. (Automatic follow)

CW transmitting: 25-250 Characters/Min.

Weight: 1:3-1:6

RTTY and ASCII: 45.45, 50, 56.88, 74.2, 100, 110, 150, 200, 300 Baud (Fine adjustment available)

### Input:

AF Input: CW, RTTY, Input Impedance 500 $\Omega$   
ASCII, Input Impedance 100 $\Omega$

TTL Level Input (common to CW, RTTY, ASCII)

### AF Input Frequency:

CW: 830Hz

RTTY: Mark: 1275Hz (Low Tone), 2125Hz (High Tone); Shift: 170Hz, 425 Hz, 850Hz and Fine Tuning (or reverse)

ASCII: Mark: 2400Hz, Space: 1200Hz (or reverse)

### Output:

Keying: CW Keying (positive) 100mA, 300V

CW Keying (negative) 100mA, 300V

FSK Keying 100mA, 300V

FSK Keying (ID) 100mA, 300V

AFSK Output Impedance 500 $\Omega$  (common to CW, RTTY, ASCII)

TTL Level Output (common to CW, RTTY, ASCII)

### AFSK Output Frequency:

CW: 830Hz

RTTY: Mark: 1275Hz (Low Tone), 2125Hz (High Tone); Shift: 170Hz, 425Hz, 850Hz (or reverse)

ASCII: Mark: 2400Hz, Space: 1200Hz (or reverse)

### Display Output:

UHF, Output Impedance 75 $\Omega$

Composite video signals, Output Impedance 75 $\Omega$

### Interface for a Printer:

Centronics parallel compatible

### Remote Control Keyer:

Capacity: 300mA, 50V

### Number of Characters and Number of Pages to be displayed:

512 characters (32 characters  $\times$  16 lines)/page  $\times$  2 pages (Total 1024 Characters)

### Battery backed-up Memory:

64 characters  $\times$  7 channels

### Buffer Memory:

53 characters

### Output for Oscilloscope:

Output Impedance 200k $\Omega$

### AF Output:

150mW, Output Impedance 8 $\Omega$

### Power Supply:

DC +12V, 1A

### Dimensions:

400  $\times$  300  $\times$  120-57mm

ted by Class B licence-holders, and this restriction applies even to the use of a device such as this.

## Results

Stability and reliability proved excellent, and we used the review unit for the somewhat unusual task of decoding and displaying a message for visitors to our stand at Breadboard '80 Exhibition. The message was recorded in Morse on a standard Compact Cassette, and replayed more or less continuously for over nine hours a day for five days, without a hiccup by the computer. Tests on the air proved highly successful once the basics had been mastered. My appreciation to several amateurs, especially G4GTH, who bore with me so patiently in my tests. The unit's ability to extract and decode a signal beset with QRM on the h.f. bands was at times quite amazing. Similar results were obtained with weak signals on 2m f.m. We understand that the  $\theta$ -7000E is widely used on commercial h.f. links, which obviously says much for it.

The  $\theta$ -7000E provides, in conjunction with a v.d.u. or TV receiver, a versatile telegraphy terminal unit, with dedicated programming for operation in the three modes, with auxiliary symbols and functions, and some user-programmable memory for brief standard messages. A similar range of functions could probably be obtained from a micro-computer plus a range of software and interface hardware at a comparable overall cost. Which solution is most attractive will depend very much upon the circumstances and requirements of the individual user.

The Tono  $\theta$ -7000E is available, price £640 including VAT, from **Thanet Electronics, 143 Reculver Road, Beltinge, Herne Bay, Kent, telephone Herne Bay (02273) 63859**, to whom we offer our thanks for the loan of the review unit. ●

## UNCLE ED'S PAGE

▶▶▶ continued from page 55


In most circuits, we want a supply whose **voltage** stays as steady as possible with variations in current drawn. This implies a power supply impedance as low as possible. Such a supply is termed a voltage source, which is short for constant voltage source. Sometimes we need a supply whose **current** stays as steady as possible when the resistance of the load connected to it varies. Such a supply is termed a current source (short for constant current source), and its terminal voltage will vary according to the resistance of the load.

I know that these shorthand terms often baffle beginners, who argue that a power supply has both voltage and current, and you can't separate the two. I hope it will become a little clearer when they realise that the word "constant" has been left out in each case. One other point that may help the beginner. We say that a *load* (our bulbs, for example) *puts a load* on the supply (in other words, draws a current from it). When we say we are going to put a lighter or smaller load on, we mean one that takes a smaller current. It will therefore have a higher resistance value. On the other hand, a load with a lower resistance will take more current, and is called a heavier or bigger load. Confusing, isn't it?

Next month, I shall talk some more about voltage and current sources, and simple ways in which we can make them. For now, I leave you to puzzle over the following, and see if you can work out why it should be. For a (constant) current source, the internal impedance of the supply must be as high as possible.

## STEREO PEAK INDICATOR

▶▶▶ continued from page 57

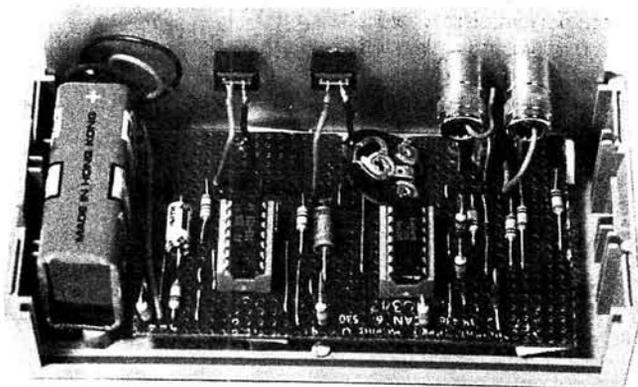

Internal view of the completed unit, fitted into a Verobox Cat. 202-21049A

**CONSTRUCTION  
RATING** **Beginner**

### BUYING GUIDE

All components for this project are widely available from our advertisers. The cost quoted includes the Verobox shown in the photographs

**APPROXIMATE  
COST** **£8**

cuit with a stereo linear potentiometer with a value of 100k $\Omega$  wired as a volume control.

To set up the circuit one requires a source of alternating voltage and an a.c. voltmeter. The most convenient source of a.c. is from the secondary of a low voltage mains transformer, with a potentiometer of around 10k $\Omega$  across it. The output at the slider of the potentiometer is monitored by an a.c. voltmeter and R3 adjusted until the l.e.d. just extinguishes. This procedure is then repeated for the other channel and the circuit is then ready for use.

The power source for the circuit should not exceed 15V, and this must be regarded as the absolute maximum. For this reason the prototype is powered from a 9V battery and housed in a small plastic box. Since the board is small the circuit can be mounted by means of the l.e.d. clips. Maximum current consumption is some 25mA and for this reason a PP3 is used to power the prototype, this will last for several months with normal use. ●

# H. LEXTON LIMITED

HARVEY G4JDT

RADIO AND ELECTRONIC ENGINEERS

DAVE G8SYG

YOUR EAST LONDON HAM STORE

We are the main UK Service Contractors to Hitachi Sales UK and we have fully trained engineers on the premises. We have been in the service industry for 15 years and we know what we are doing.

## THE STANDARD TRIPLETS!!

**C7800**  
**£270**

**C8800**  
**£250**

**C78**  
**£209.50**

ALL STANDARD ACCESSORIES IN STOCK

## SOMMERKAMP/YAESU

FT767Dx	H.F. W.A.R.C. (complete with mike, C.W. filter)	FT2772D	H.F. W.A.R.C. (complete with AM+CW filters, AM facility, YE7 mike and fan)	£617.00
	£525.00	FT227RB	2M synthesised transceiver	£225.00
TS280FM	50W 2M mobile transceiver	FT207	2M handheld transceiver	£196.00
TS280LP	10W 2M mobile transceiver	YM24	Microphone	£16.27
FRG7	HF Receiver	N9C	Charger	£7.50
FT480RE	2M multimode transceiver	FT101Z	HF transceiver	£488.75
	£359.00	FT101ZD	HF transceiver	£569.00

## NOW IN STOCK

### ICOM

IC2E	£159
IC251	£479
IC202S	£169
IC240	£169

### TRIO

TR7800	£268
TR8400	£275
TR2400	£198
TR2300	£166

## ACCESSORIES

ICHM9	Speaker Mic	£12
ICBP5	Battery Pack	£30
ICCP1	Mobile Charging Cord	£2.75
ICBP4	Battery Case	£5
LC3	Leather Case	£3
210 TRX	Mobile mounting bracket for TR2300 with built in IOW linear	£59.95
MMB10	Mobile mounting bracket for FT207	£6.95
DAIWA SR11	2m Scanner	£55

## SWAN

100MX	235W P.E.P. Analogue mobile	£365.00	1500ZA	1500W Linear Amp	P.O.A.
Astro 150	(Including mounting bracket)	£551.00	103BX	235W P.E.P. W.A.R.C.	£810.00
			PSU6	(102BX)	£140.00
			PSU5	(100MX) 13.8V DC, 20 amp	£132.00

## CUSHCRAFT AMATEUR ANTENNAS

### H.F.

A3	20/15/10 3ele Beam 8dB gain	£147.00
ATV5	80-10 Trapped Vertical	£74.40
ATV3	20/15/10 Trapped Vertical	£34.00
ATV4	40/20/15/10 Trapped Vertical	£68.00

### VHF (144 MHz)

144	10TWIST complete with phasing harness!	£34.75
214B	14ele Jnr 'Boomer' Yagi 15.2dB gain	£49.50
ARX2	Ringo Ranger 6dB gain vertical	£24.75
A144-4	4ele Yagi 9.0dB gain	£16.25

A144-7	7ele Yagi 10.0dB gain	£20.31
A144-11	11ele Yagi 11.3dB gain	£25.72
DX120	20ele Array 13.2dB gain	£47.20
ARX2B	Ringo Ranger II	£28.75
ARB2K	Conversion Kit for Ringo to Mk II version	£12.75
CS100	Communication Speakers	£11.50
TAP3009	5/8 Side Mount and snap in 2MTR.- 144-174 MHz	T.B.A.
TAP677		£18.50
K220	Mag Mounts Base 17' Cable & PL259	£8.67
TAP/432 MHz	Snap in for K220	TBA

## EXCLUSIVE TO US

1KW VHF linear - 600WSSB - 350W FM	£449
200S 1KW Input VHF Linear	Due in soon
200C 1KW Input 70cms Linear	Due in soon



Also available:- Video - Hi-Fi - T.V. - Music Centres, e.g. Hitachi SDT 300 auto-reverse music centre with pre-set FM, Dolby, strobe turntable, 25 + 25W per channel, including speakers only **£269.95** - These are either Sample or Demonstration units. Many other Hitachi Demonstration models available, Hi-Fi, Portable Stereo Radio Cassettes etc.



Telephone 01-558 0854

191 FRANCIS ROAD, LEYTON, LONDON E10

Telex 8953609

Opening Times: 9-5.30 Mon.-Fri.

10.00-1.00 pm Sat.


or any time by appointment.



# AMATEUR RADIO EXCHANGE



B. MR-1000A

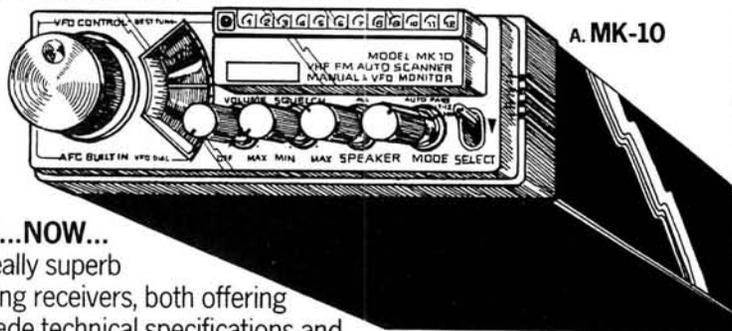

A. MK-10

## HERE...NOW...

Two really superb scanning receivers, both offering top-grade technical specifications and unbelievable value for money. Come and try them in the shop, or phone your orders and enquiries. (24-hour answer service when we're closed.)

**A MK-10** VHF FM scanning receiver, covering 144-152MHz. Scanning or manual tuning through up to 12 crystal-controlled frequencies, **OR** VFO control on main dial. Automatic lock-out facility. Sensitivity  $\mu\text{v}$  (25 db S/N). 12v or mains. **BASIC PRICE £69.**

**B MR-1000A** The finest-value pocket receiver ever offered. VHF FM scanner, 10 channels, and allowing scan or manual tuning across selected crystal-controlled channels. Complete with Nicads and charger. **BASIC PRICE £39.**

**CRYSTALS: AMATEUR BAND 145-145.775MHz £2 EACH. ALL OTHER FREQUENCIES £4 EACH. PRICES ARE POST-FREE AND INCLUDE VAT.**

INC. MARINE

**AMATEUR RADIO EXCHANGE,**  
2 Northfield Road, Ealing, London, W13 9SY.  
Telephone: 01-579 5311.

CREDIT CARD



SALES BY  
TELEPHONE.

## MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.

- ★ Practise anywhere, anytime at your convenience.
- ★ Generates a random stream of perfect Morse in five character groups.
- ★ D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- ★ Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.



Price **£49.45**

## ACTIVE RECEIVING ANTENNAS

Datong active antennas are ideal for modern broadband communications receivers - especially where space is limited.

- ★ highly sensitive (comparable to full-size dipoles).
- ★ Broadband coverage (below 200 kHz to over 30 MHz).
- ★ needs no tuning, matching or other adjustments.
- ★ two versions AD170 for indoor mounting or AD370 (illustrated) for outdoor use.
- ★ very compact, only 3 metres overall length.
- ★ professional performance standards.



Prices: Model AD170 (indoor use only) **£42.55**  
Model AD370 (for outdoor use) **£56.35**  
Both prices include mains power unit.

## VERY LOW FREQUENCY CONVERTER

If your communications receiver gives poor results below 500 kHz Model VLF is the answer.

- ★ Connects between antenna and receiver input.
- ★ Converts signals between DC and 500 kHz to the range 28 to 28.5 MHz with low noise and high sensitivity.
- ★ Crystal controlled for high stability.
- ★ Quality construction in diecast aluminium box (size 112 x 62 x 31mm), SO239 connectors, LED indicator, in/out switch.
- ★ Operates from internal 9 volt battery or external supply (5-15 volts DC).

Price: only **£25.30**

Our full catalogue plus further details of any product are available free on request.  
All prices include VAT and postage and packing.

**DATONG ELECTRONICS LIMITED**

Spence Mills, Mill Lane,  
Bramley, Leeds LS13 3HE  
England.  
Tel: (0532) 552461

## STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA

ENGLAND  
Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers—transceivers. Mobile equipment pre-selectors—filters—antennas. Stabilised power supplies from 2 to 20 Amp. Antenna switches—converters. Aluminium masts—clamps. Antenna rotators.

**Trio R1000 Receiver**  
Digital readout general coverage receiver covering 200KHz to 30MHz with a P.L.L. synthesiser. Also incorporating quartz digital clock. £285.20.

**Trio R820**  
Amateur Band Receiver £690.00.

Send for full specifications of our full range of receivers covering from 200KHz to 520MHz. Our secondhand equipment changes daily. Send SAE for up to date lists. Part exchange welcome. Good clean Equipment bought for cash.

**Drake**  
R7 Solid state receiver digital readout 1.5 to 30MHz. £989.  
**J.R.C.**  
NRD515 Solid state synthesised digital receiver 100KHz to 30MHz. £948.

**Bearcat 220FB Receiver**  
Scanning Receiver. 66-88MHz-118-136MHz. 144-148MHz-144-148MHz. 420-450MHz-450-470MHz. 470-512MHz £258.75.  
Send S.A.E. for details of our range Aircraft Band Receivers.

## FIT A DIGITAL DISPLAY TO YOUR FRG7 OR SRX30.

These units come complete, with only three wires to connect. The FDU7 for the Yeasu FRG7 can be fitted in place of the KHz dial, or can be supplied for external use. (Please state when ordering) The FDU3 for the SRX30 is supplied for top of the set use only.

(Full Fitting Instructions are supplied.)


(FDU7) for FRG7 @ **£44.77**  
(FDU3) for SRX30 @ **£44.77**

We also manufacture an R.T.T.Y. Converter. The MB6R (Receive only) and MB6R/T (Receive/Transmit). We supply these units with single or double current loops for connection to teleprinter To Order. T.T.L./C.MOS Logic Levels and Oscilloscope Outputs are provided. Dimensions (84x304x210).

(MB6R Double or single current) @ **£77.96**  
(MB6R/T Double or single current) @ **£83.25**

(All Units are fully Guaranteed, and come complete)  
(No extras needed)  
(All prices inclusive of postage and V.A.T.)  
(Payment by P.O., Cheque or Access)

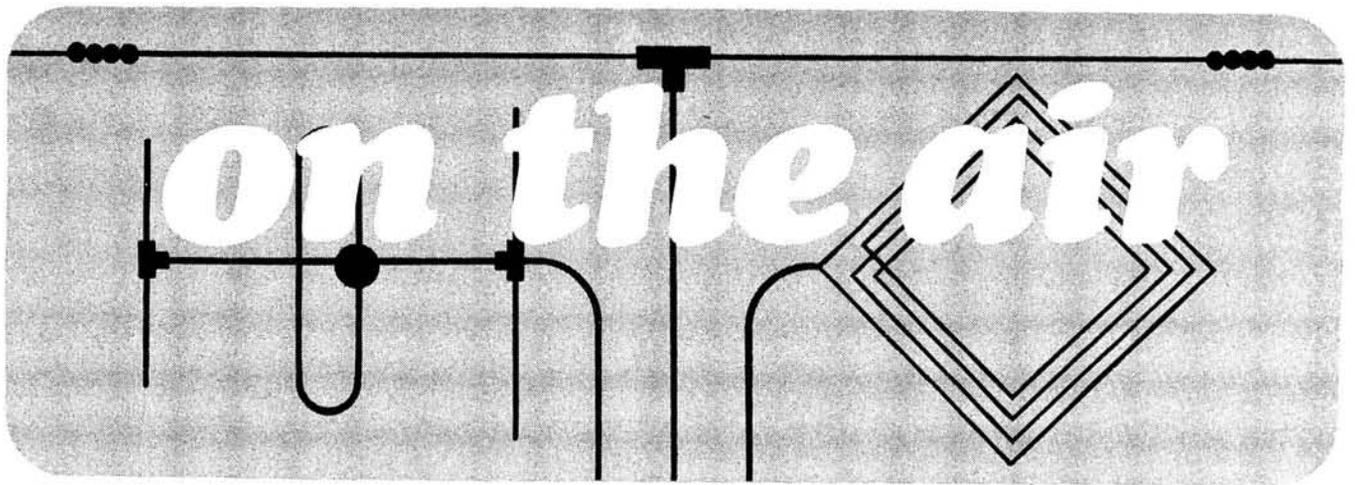**B. BROOKES ELECTRONICS, 69 Leicester Street,  
NORWICH NR2 2DZ, ENGLAND.  
Tel: 0603-24573.**



## Amateur Bands

by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR  
Silver Firs, Leatherhead Road,  
Ashted, Surrey KT21 2TW.  
Logs by bands in alphabetical order.

I am frequently asked by readers of this column for my views on this or that piece of equipment being advertised, which is calculated to remove or reduce the interference (QRM) that afflicts most amateur bands today, or seems to. At first sight this may seem to be a relatively easy way of getting rid of a very difficult and persistent problem. In the event the audio filters, for that is what most of these devices are, often prove ineffective or are disappointing, especially as some of them are far from being cheap.

It is sometimes like fitting twin carburettors and a head conversion kit to a clapped-out old banger and expecting a major improvement in performance from it. In other words, the receiver must be a reasonable performer in its own right before any added gadget can hope to work properly. I am in no way condemning the many filters on the market, as I'm sure they will all work as claimed, but only when given a chance by being connected to a decent receiver.

Where most communication receivers fall down in performance is in the r.f. and mixer stages, and, strangely enough, the price tag doesn't necessarily mean a better set in this respect. When two or more powerful signals are passed through the r.f. tuned circuits to a transistor amplifying stage, then the device by its very nature will operate in a non-linear manner and that means one thing, intermodulation. The two signals may be many kilohertz apart, or even outside the amateur bands, but if they both appear at the transistor then there will be trouble.

Nothing, but nothing, is going to improve matters once those signals have passed the r.f. circuitry, least of all any form of audio filter. Receiver manufacturers today fit all kinds of gadgets to the r.f. stages, with an equally bewildering variety of names, in order to reduce the signal input to the transistors themselves. All of them, in the end, are what we have always called them, r.f. gain controls. A

simple  $1k\Omega$  carbon potentiometer across the antenna and earth terminals will do the job just as well.

All kinds of solid-state devices have been developed, particularly the f.c.t. series, in an effort to prevent this intermodulation effect, without a great deal of improvement. The same effect and the same problems arise with large signal levels in audio equipment and it is significant that some hi-fi manufacturers are turning to the old-fashioned thermionic valve. And why not? Valves have virtually no problems with non-linearity at high signal levels and if they can do a better job in this particular application why not use them?

The usual excuse of heavy heater consumption and heat problems is really nonsense as far as receivers are concerned. Long before transistors were thought of miniature valves were common, with 1.4V filaments run from a single cell if necessary, and, indeed are still advertised for sale in our radio magazines. Some had wire leadouts making them ideal today for p.c.b. mounting, while others had the standard 7-pin glass base.

The first communications receiver manufacturer that decides to forget solid-state devices in the front end of his sets, and uses or develops valves for the purpose, will find his product performing better than even the most expensive solid-state set available to the amateur today.

It is very shortsighted to decry the valve just because it came before the transistor. As someone reputedly remarked not long ago: "If the valve had come after the transistor it would have been hailed as a great new development," or something like that.

So, before fitting that filter to sort out the signals, make sure the QRM is really being caused externally and not being generated inside the receiver itself.

## On the Air

Not much doubt this month as to which of the bands has sent the blood racing through the veins of the ardent DXers. Take a look at this lot: AP2ZR, DA8BE/TA1, FG0FOK, FK8CR, HI8EJH, HP3FL, H44SH, KL7Y, KP4AAQ, OA4AWP, YB0UR, ZL1JC and ZL4AP and many others logged by **Mike Howard** BRS44755 of Chadderton, Oldham, on the 80m band with his DX160 and loaded ground-plane for 40, 80 and 160m. Mostly after midnight although the H44SH was caught at 0950 GMT. Only catch of import on 40m was VK9NS, but the 20m dipole found FR7OY, HS1AMM, JW5IJ, ZE1EK and 9Q5NB, while 15m produced A22ZM, D4CBS, 5H3KS, 5N9GM and 5Z4CH. Mike suggests that anyone wanting a 3X station should look for VK3NIC/3X on 15m around

2200 GMT, and QSL via K4FRU. Some of the comparatively new prefixes on 160m s.s.b. copied by Mike included UA9RYN, UA0ACW, UL7ECW and UL7MNA.

Unusual one for **Basil Woodcock** BRS44266 of Leeds was LA1EKO on 80m from the Ekofisk oil rig in the North Sea. Others have also been reported so it's time there was a Worked All Oil Rigs award! Also on 80m Basil logged KP4AAQ, OA4AWD and PY5RR, with FG0FOK, 6W8IJ on the 10m range of his SRX-30. Two nice ones for 15m were HP1XRK and VP1CBT with 20m showing up with DU9RG, VK9GC, ZD7SD and ZD8TC. An a.t.u. has been added to the 40 metre-long wire to help Basil log 186 countries in his first year of listening.

"Phew! What a month" was **David Coggins'** reaction from Knutsford, Cheshire, not surprising with a pair of phased verticals on 20m also used on other bands like 10m for FG0FOL/FS. YS1ECB reputed to be using old-fashioned a.m., and 5N6RED with catches like TG4NX, UK0QAA (rare Zone 19), VE8YQ and VK9NS on Norfolk Is. Catch of the month must be ZL3NR/C on 80m s.s.b. working into Europe, plus OA4AWD, VK7AE, and 7X4MD. For 160m a loop or 5 metre-tall vertical was used to find the usual Europeans on c.w. (a pleasant change!) noting UK2KDX, OZ7YY and UA3ALO in particular. On s.s.b. it was several VEs and lots of Ws all around 0600-0700 GMT.

**Bill Rendell**, down in Truro, comments on the very sudden disappearance of stations on 10m at the beginning of February with VP8PP going from 57 to zero in three minutes, while on the 8th he heard a 59 signal from VU2USE working G3IIY in Bedford, who was 55 and far beyond the normal ground-wave and sounding like a long-path signal. Bill surmises it was a round-the-world echo and I imagine he is right. Bill was suitably aghast hearing that KL7EBK had a 53 metre-tall steel tower with friend KL7EBK boasting a 46 metre tiltover job!

Down to the nitty-gritty from Bill and his HRO with FK8CR, HI8EJH and ZL4QE on 80m, VK2WC, ZL1AMO and ZL4AV on 40m, C5AR (two-letter suffix unusual, says Bill), J6LOU, PY0ZZ on Fernando de Noronha Is., VP8PP, ZD7SS, ZD8RH, 1A0KM (de Bill, where's that?) but as he said QSL I0MGM it doesn't seem worth worrying about, 5T5AY, 6W8AR and 9X5PP all on 20m. The 15m band revealed C5ACO, DU7RLG, TA2AK, VK4NIC/3X, VP1WP, VP2SAM, VP5GT on Grand Turk and ZD8RH who'd like cards via G4DBW. Finally on 10m C5ADS, J3AH, KG4ET and KG4WM (QSL WB1COR), PY0ZZ, TR8CN (QSL to W5RU), VP5TCI also on G. Turk, ZD7BW, 3B8AE/3B9 and 5N6RED.

Towards the end of January a very fine catch was made by **Allan Stevens** (Crowthorne, Berks) with his Trio 9R59DS and just a TV downlead as an antenna, namely JT0YFU on the 7MHz band who was audible most of the night. Others heard in the same session were EA8AK, UK0SAW and YV4BMV. On the 3.5MHz band or to be more precise around the top end at 3900kHz or so, EA8XS, HI8AL, KP4R, OD5MR, VP2AZG, YL6LV (seems to be a new prefix) and 4Z4ZB. At the moment Allan is getting the parts together for the *PW* Active Antenna project. Code practice is another interest when time permits.

From Birmingham **Dennis Court** reports on the findings of his Collins R390A receiver fed with a 40 metre-long wire on the 80m band like AP2ZR, VO2CC, XE2AX, N2BV/LX, CT2FL and a nice one in 5T5JD of Box 477, Nouakchott, Mauritania, with 7X5AL to end with. In Earl Shilton, Leics, **Dennis Sheppard** is still clearing the muddle resulting from his move of QTH but at least he has his RTTY gear going well judging by 4X4MR, 5N0DOG, and 5Z4RT on 10m, 1A0KM said to be in Malta (Bill

Rendell please note!), JA1ACB, LU3EQ, VK2SG and XE1VV on the 15m band. Not neglecting the s.s.b. mode Dennis logged HI8PGG on 10, JE6QUJ, YZ9CRM and 6W8AR on 15 with a good catch in VP2SAV on 40m. A later note from Dennis mentioned that 10m was wide open in mid-February with 28080 to 28100kHz full of RTTY stuff. A Siemens T100 printer is being commissioned as soon as the necessary gears are to hand.

Another 9R59DS, in the hands of **David Warr** (Weymouth), helped by a G5RV antenna and a ZL Special on the 21MHz band brought good DX on all bands, with 7MHz in particular shining with such as TG9AL, FK8CR, H44DX and 6W8AR in the log. David heard stations working the FK8 on the 80m band but was unable to copy him for sure so didn't count it. However OA4AWD, OHONE, XE2AY and ZL4AP did show up on that band, with well-reported FG0FOK on 10m plus JW5IJ and FR0FLO. The FG0 and HK0FBF came up on 15m for a couple of good ones. David is busy with CSE and "O" level problems, so wisely is not worrying about the RAE for the time being.

## In General

**Barry McCarthy**, a welcome new correspondent from Croydon, Surrey, never believes in rushing things! He decided to sit the RAE when he was just 14 and finally got down to it 22 years later! However he did manage a distinction and a credit and is now after the code test. Dare I quote his comment: "No second-class licence for me"! His view on the RAE? "Nothing less than a comprehensive crib sheet"! I may be a bit slow but I have never heard of a satisfactory explanation of why there are "Pass", "Credit" and "Distinction" with the RAE since any are good enough to get a licence. It might be a good idea if these varying permutations were linked to different grades of licence with, say, two passes earning a limited novice licence and so on, with another exam for a higher class or grade.

**A. M. Chapman** BRS43503 of Grimsby wrote about a Beverage antenna some 152 metres long that he intends to erect, and recommends the book on *80m DXing* by ON4UN as an invaluable guide to the subject, although I have not yet acquired a copy myself. Judging by the few photostat pages sent to me I feel I have missed out on something good.

Another to pass the RAE and awaiting his call is **John Everingham** of Bristol, also a newcomer to this column, who has spent some time modifying and, hopefully, improving a present received in the shape of a Heathkit CG-1U Mohican receiver. Anyone interested should write to me in the first instance.

Yet another writing in for the first time is **Barry Harper** from Wednesbury in the W. Midlands, who started in amateur radio about five years ago and is at last "knuckling down" to studying for the RAE. At the moment an ex-Army 19 set is in use after various missing bits and pieces had been replaced. Antennas being played with include a helical one on a broomstick (no, OM, we won't laugh! We've all tried something like that at one time or another) and a 18 metre-long wire. Logs are threatened in the near future.

A writer who wishes to remain anonymous would like to see some praise for Ernie Burke G3VOZ who runs RAE classes at the Dacorum College, Hemel Hempstead, whose six pupils sitting the December RAE all passed as did no less than 18 at the May 1980 exam. Just hope this little appreciation doesn't result in the classes being overwhelmed!

## Club Time Again

Looking at the pile of newsletters and the like it seems just about every club in the land has reported in this month! So entries may be a bit brief, but, hopefully, adequate.

**Chiltern ARC.** New secretary Peter Stears, 127 Hughenden Avenue, High Wycombe, Bucks, says club meets last Wed of month at the factory of John Hawkins & Sons, Victoria Street, High Wycombe at 8pm with visitors and prospective members assured of a warm welcome.

**Hull & District ARS.** A note concerning the rally at the University of Hull at midday on Sunday May 31, with trade stands, XYL stalls, films and cartoons for the kids and a bar and refreshments. Talk-in facilities will be operating, says Heather Cunliffe, club sec, at 12 Pearson Avenue, Hull.

**West of Scotland ARS.** Weekly Morse classes at 7pm on Fridays at 22 Robertson Street, Glasgow run by Willie Goldie GM4GIH and George Allan GM4HYF has meant 15 members qualifying for their "A" tickets in recent times (the QRM!) after which the regular meetings get going. Nightly meetings on 28400kHz cater for SWLs and GM8s with c.w. sessions, but Ian McGarvie GM4JDU at 3 Kelso Avenue, Paisley will tell you more.

**Yeovil ARC.** Every Thursday, 7.30pm, Building 101, Houndstone Camp, Yeovil with activity from club stations G3CMH and G8YEO plus lectures and amateur radio library facilities. May sees start of RAE course for December exam, run by G3MYM. Club sec is D. L. McLean G3NOF, 9 Cedar Grove, Yeovil or Yeovil (0935) 24956.

**St Helens & District ARC.** Change of meeting place! Now every Thursday, 7.45pm, at the Conservative Rooms, Boundary Road, St Helens, instead of the YMCA. The larger premises should offer better facilities for club activities as well as being more attractive to prospective members and visitors. It is Paul Gaskell G8PQD, 131 Greenfield Road, St Helens, Merseyside, or St Helens 25472.

**Stevenage & District ARS.** Some 16 candidates should be taking the May RAE, with five out of the seven making it last time. These classes are "blamed" for the increase in membership in a year from 35 to 72 which includes 39 licensees! Try the first and third Thursdays at 8pm at the staff canteen, British Aerospace Dynamics, Plant B, Gunnels Wood Road, Stevenage. Respectful silence please on April 16 when club chairman Stephen Clarke G8LXY will address the assembled multitude. Might also mention Mike Barraclough talking on s.w. broadcast DXing (ugh!) on May 7, in case your June *PW* does not arrive on time. Trevor Tugwell G8KMV, 11 The Dell, Stevenage, Herts, will fill in with anything I've missed.

**Sutton & Cheam RS.** Meetings held at both the Sutton College of Liberal Arts, Cheam Road, Sutton, Surrey and the Banstead Institute, High Road, Banstead, so contact G. Brind G4CMU, 26 Grange Meadow, Banstead for more precise details. The second venue sees the AGM on Friday April 24 if you like that sort of thing. You are more likely to meet just about everybody from the club on that occasion.

**Cheshunt & District RC.** Every Wed at 8pm in the Church Rooms, Church Lane, Wormley, near Cheshunt, Herts, says Jim Sleight G3OJI, 18 Coltsfoot Road, Ware, Herts, also (0920) 4316. New code course starts soon for potential "A" licence candidates with a class for complete beginners in the art in April, lasting 12 weeks.

**Braintree RC.** Janet Storey, publicity officer, sent me the club's monthly communication, consisting of several pages of very well produced information to suit all in-

terests in amateur radio. Meetings first and third Mondays at the Braintree Community Centre, Victoria Street, Braintree, next to the bus station. 7.45pm would be about right. Contact Janet at 33 Redwood Close, Witham, Essex.

**Exmoor RC.** Patricia Jemison says notes on club have resulted in several enquiries from the area, obviously interested in the special projects organised for the younger members. Meetings 7.30pm every Thursday at Loughrigg, East Street, South Molton. If interested contact Pat at Homedale, Brayford, near Barnstaple, N. Devon which is Brayford 327.

**Grafton RS.** Don't forget the club now has a new QTH at the Five Bells, East End Road, Finchley, London N2 at 8pm second and fourth Fridays with new members and visitors threatened with a warm welcome. John Thomson G8SYD, 70A Deans Lane, Edgware, Middx.

**Chesham & District ARS.** Possible change in club venue in the wind for the near future so first of all contact Andy G8PUC, 8 Lynton Road, Chesham, Bucks. Otherwise normal meetings on second Wed with informal gatherings on remaining Weds.

**Wirral ARS.** First and third Weds at 7.45pm, at the Sports Centre, Grange Road West, Birkenhead. April 1 welcomes G8VPF on "navigating in a car rally" at which I'm assured the speaker is very experienced, as well as being the club's Hon. Sec. April 15 is another jolly jape, namely a sale of surplus equipment. So says the excellent newsletter but more details from the aforesaid Hon. Sec. G. O'Keeffe-Wilson G8VPF, 20 South Drive, Upton, which is 677 1531.

**Ipswich RC.** Note, again, new QTH at Rose & Crown, 77 Norwich Road, Ipswich, second and last Weds at 8pm. RAE and code classes and many other items for your delectation plus first-class club magazine *QUA* to read when away from the club. Jack Toothill G4IFF, 76 Fircroft Road, Ipswich, is the man to contact for more info.

**Crawley ARC.** Has decided to carry on calling its newsletter *The ARC Newsletter* in spite of other suggestions. Well done! Informal meetings are held at various members' homes with the next on April 8, so contact Dave Hill G4IQM on Crawley, Sussex 882641 for details. Otherwise meetings are held at the Trinity United Reformed Church, Ifield, on the last Wed of the month.

Newsletter editors please ensure magazine has **full QTH** of Hon. Sec. or other contact and times and place of regular meetings.

All letters, newsletters, etc., by the 15th of the month please.



"It wasn't a very good QSO. I couldn't hear him and he couldn't hear me."

... Brighton & District RS Newsletter

"I should be stronger now. I have a power meter in the antenna."

... heard by G4BYV

# Medium Wave Broadcast Band DX

by Charles Molloy G8BUS

Reports to: Charles Molloy G8BUS  
132 Segars Lane, Southport PR8 3JG.

Last month we looked at the advantages of tuning a loop, and how interference between two stations on the same frequency (co-channel QRM) can be reduced or eliminated. This time we will have a look at other problems that a loop may help to solve.

## Static

Static (QRN), sometimes called atmospheric, is caused by thunderstorms often some considerable distance from the DXer's QTH. When severe, static produces a "frying" type noise in the loudspeaker. If it comes from all directions then there will be a reduction in the total amount picked up if you use a directional antenna such as a loop, as nothing will be picked up from the directions of the nulls. If static comes from one direction only, as may occur in summer from tropical thunderstorms to the south, then the static can be nulled-out by the loop just like an unwanted station, leaving DX from other directions such as North America in a static-free background. A loop is invaluable for summer DXing.

## Adjacent Channel Interference

If you are trying to listen to a weak station close to a strong one, then peak-up the loop on the wanted one and rotate the loop until the interference is reduced or it disappears. Used in this way the loop is a substitute for additional receiver selectivity, but of course it only works if the wanted station and the QRM are in different directions.

There are several undesirable effects that occur as a result of adjacent channel QRM. One is overloading. A very strong signal applied to a receiver can produce spurious responses, cross-modulation, etc. A loop will often bring about an improvement, leading to a cleaner, better-quality audio signal. There is also the advantage that the wanted signal will not be weakened along with the QRM, which would occur with an aerial attenuator.

Sideband splatter occurs when a strong station spreads out to swamp nearby weak stations. Monkey chatter is another name for the inverted speech produced when one of the sidebands of the unwanted signal modulates the carrier of the wanted one. Receiver selectivity cannot cure these problems as the QRM is spread over the wanted station, but a loop will often bring about an improvement.

When two stations are separated by only a few kilohertz then there will be an audio tone (heterodyne) equal to the frequency difference between them. If you are


listening to DX from North America or from other parts of Region 2 where the channel spacing is 10kHz, then a heterodyne of 1kHz, 2kHz or 3kHz can occur from broadcasts on a Geneva Plan channel which will spoil your DX signal. A tuneable audio notch filter will remove the heterodyne but so will a loop if it can null-out the unwanted station. You can try this out on 981kHz where there is a 1kHz heterodyne between Radio Sweden and Algiers on 980kHz which has not (yet) moved from its pre-Geneva channel. It is quite easy to separate the two with a loop and remove the heterodyne.

Next time we will look at the limitations of a loop antenna. What it cannot do and why it will not work with a portable receiver.

## Iberia

Spain and Portugal between them provide interesting though contrasting DX. Spain has several chains of low-power local radios spread right across the country, many sharing the same frequency, rather like local radio in the UK but on a larger scale. In Portugal there are a number of low-power outlets that offer a challenge to the DXer. Both countries allocate callsigns to privately-owned stations, the Spanish prefix being E while the Portuguese is CSB. The two countries lie to the south of the UK so a loop is very useful for reducing interference from the remainder of Europe, QRM that comes mainly from an easterly direction.

A pennant from Madrid

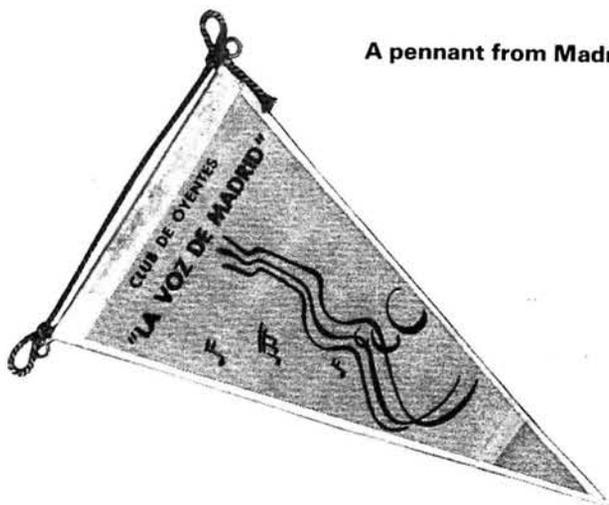

A QSL card from Barcelona



# WATERS & STANTON ELECTRONICS

18/20 MAIN ROAD, HOCKLEY, ESSEX. TEL (0702) 206835

4,000 SQ FT  
DEVOTED TO  
RADIO COMMUNICATION

24 HOUR TURN ROUND  
ON ALL ORDERS!

"SUCH NICE PEOPLE"

EVERY ITEM TESTED  
BEFORE DESPATCH



**SR9 VHF  
RECEIVER  
AMATEUR/  
MARINE  
£46 inc. VAT**

The SR9 must be one of the most popular monitors for 2 metre amateur radio enthusiasts. (Also available as a marine version at the same price). It is fully tuneable across the band with the option of also installing up to 11 xtal controlled channels. Power requirements are 12v DC negative earth at 200ma approx. The unit comes complete with mobile mounting kit and built-in speaker.

**PROFESSIONAL AIRCRAFT MONITOR  
R517 £49.50**  
(as supplied to pilots, ground crew etc.)



The R517 is a professional aircraft monitor receiver, having superb sensitivity and capable of tuning across the entire aircraft band 118-143MHz. For easy tuning there is both a coarse and fine tuning control. In addition there is a 3 position switch for selecting xtal controlled channels (xtals £3.00 extra) for your local airport. The unit is completely portable running off self-contained batteries.

**AR22 VHF FM MONITOR  
OUR PRICE £83 inc. VAT**



Truly amazing! The AR22 tunes across the 2 metre FM band 142-148MHz (also includes Police and Fire Brigade) in 5kHz steps. So small it will fit into a shirt pocket and yet nothing is sacrificed in terms of performance. Price includes rechargeable batteries, mains charger, fly aerial etc. You won't find a smaller monitor anywhere.



**TRIO R1000  
COMMUNICATIONS RECEIVER  
OUR PRICE £285 (Free Securicor  
Delivery)**

The R1000 has really caused a stir in the receiver market! Its performance matches professional receivers costing many times more and with our new competitive price of £285 it must be the best value on the market today. Full digital readout from 200kHz (actually it operates right down to 20kHz but with reduced sensitivity) means accurate tuning and the 30 position band selector switch means really good bandspread for easy operation. Other features include noise blander (a really good one!) built-in speaker, digital clock/timer and both 230v AC/12v DC operation. (Yes we include the 12v DC kit free!) Each model is fully checked and delivered anywhere in the U.K. within 24 hours of receipt of payment!



**YAESU COMMUNICATIONS  
RECEIVER  
FRG7700 £309  
FRG7700MEM £380  
PLUS FREE GLOBAL 3-30MHz Aerial**

Free Securicor  
Delivery

The FR7700 is a new model from Yaesu that replaces the FRG7000. Full coverage is provided between 200kHz and 30MHz with bright digital readout that also doubles as a clock. Features include noise blander, FM detector, internal speaker, 230 volt AC operation and built-in timer. As an optional extra there is also a memory unit which enables up to 12 selected frequencies to be stored and selected.

## SHORT WAVE LISTENER ATU



**AT1000  
£31.95  
carriage £1.00**

### SUPER NEW DESIGN 200kHz-30MHz

Here's a brand new ATU specially manufactured for us in Japan. Primarily designed for the Trio R1000 and Yaesu FRG7700, it will match most other current models.

Most modern receivers have very poor front end performance because of their very wide frequency coverage. This results in cross modulation etc. which sounds like a general background jumble of stations obscuring the signals you are trying to receive. If you are feeding your receiver with a random length of wire then matters will be even worse! This unit provides the missing selectivity and the correct match to your receiver. The result, ... A lot of extra stations you have never before heard and the remainder a lot of clearer.



**SWR/POWER/FIELD  
STRENGTH MEASURING  
METER  
SPECIAL  
OFFER  
£11.95 +60p p&p**

As used by CB and Amateur radio operators.

The YW3 is used by amateur radio and CB operators around the World. It's offered to you at a really low price because we import them direct from Japan. It tells you the VSWR, power output and field strength and covers 3.5 to 150MHz. If you want the strongest signal in town - you'll find the YW3 the sure answer.

## STOP TRANSMITTER INTERFERENCE



**HP3A £3.50 each  
Ferrite Filters £1.00 for 2**

If you are suffering from or causing transmitter interference to TV or audio equipment, then these are the items for you. Our HP3A TV filter simply plugs into the TV lead and cuts out transmitter interference (ideal for 27MHz). Our ferrite ring filters are ideal for cases of interference to hi-fi systems.

## 28MHz FM!

**NEW AZDEN  
PCS2800**



**£179 inc. VAT**

Here's an exciting new 20 watt input (10 watts output) transceiver with a host of features to put it head and shoulders above the competition. Compare its features:- 200 channels, high/low power switch, computer control touch pad, 6 programmable memory channels, automatic band searching, automatic memory scanning, microphone frequency control button, priority channel, digital frequency readout, removable control panel (permits main transceiver to be mounted remotely), slide in mobile bracket, built in speaker and a host of other features. Its high power and very sensitive receiver gives it better coverage than its competitors. Send for details today or come and see our demonstration model.

STOP PRESS:- SEND 14p STAMP FOR NEW 1981 CATALOGUE ON RADIO COMMUNICATIONS

MAIL ORDER SLIP to: Waters & Stanton Electronics, Warren House, Main Road, Hockley, Essex.

Name..... Goods required .....

Address.....

Please rush me the above. Cheque enclosed for £...../Please charge to credit card No.....

# NORTHERN COMMUNICATIONS

AMATEUR • COMMERCIAL • MARINE


## AND NOW FOR SOMETHING REALLY NEW!



-12V DC earth  
144-146 MHz or  
MARINE

15 x 19 x 5 cms.  
Mobile bracket  
+ Int speaker inc.

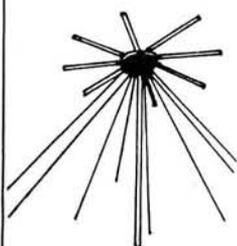A VHF monitor receiver with **VFO** plus **12** optional scanning channels for **£46.00** inc. VAT. Carriage free.



### NORCONE 512 (66-512 MHz)

It's here! A no compromise, precision made full 16 element disccone antenna made in Britain. Standard SO239 connector, with cover. Supplied with 1" diameter, 30" mounting support mast and complete instructions.

An ideal partner for the SX200A, "Bearcat" and other scanning receivers. It may also be used for transmission and in particular where antenna space is limited.

Full coverage of 70.144.432MHz Amateur bands plus Aircraft, Marine and Commercial bands.

**£24.95** p.p. £1.50

NCMK-1. In line vertical mounting kit for 1" to 2" mast. **£2.45** p.p. £0.50

NCMK-2.

Chimney lashing kit, including hardware and lashing wire. **£2.95** p.p. £1.00

NCKK-1. Low loss coaxial cable kit, 10 metres, with connectors and fixing clips. **£3.75** p.p. 50p

### ZL-12 COMPACT YAGI

13db gain, compact 2 metre Yagi. 10'6" boom, lightweight rugged design. Hundreds of this award winning antenna already in use. Send for details.

**£28.75** p.p. £1.50

### ZL-8 SUPER COMPACT YAGI

9db gain, super compact 2 metre Yagi. 6'0" boom, lightweight rugged design. Ideal for limited spaces and portable operation. Send for details.

**£17.25** p.p. £1.50

## SX200N HOT NEWS!

### Scanning Receiver NEW MODEL!

New model of this superb unit now with:

Plug in modules - for easy service.

Increased AF Output - for better reception.

Improved Image Rejection - to cut out unwanted signals.

Increased Selectivity - to cut out adjacent channels.

Plus many more interesting features.

**£264.00** inc. VAT.  
Carriage £1.50

## SPECIAL OFFER!

SX200N + Norcone 512. Complete inc. VAT. and delivery.

**£285.00**

## YAESU FT707 TRANSCEIVER

This most popular of compact HF rigs is currently the number one selling station amongst our extensive range of amateur radio equipment which includes such names as: CUSHCRAFT, JAYBEAM, FDK, STANDARD, SWAN, AZDEN, MICROWAVE MODULES, NAG, SEM and many more. Don't just take our word for it come and try the FT707 or better still order yours now!

FT707 100W

**£500.00**

FP707 PSU

**£109.00**

FC707 ATU

**£72.00**

FV707 VFO

**£178.00**

Customer satisfaction and good service is our trademark!

Prices include VAT @ 15%

299-303, Clarendon Road, Halifax HX3 6AW,

West Yorkshire. G3UGF.

Tues-Sat. 9.45am-5.30pm.

Telephone (0422) 40792.

24 hour Ansafone Service.



# Western

THE COMMUNICATIONS SPECIALISTS  
EVERYTHING FOR THE RADIO AMATEUR

## ANTENNAS . . . FOR THE HF BANDS

BRITISH MADE BY **Western**

### TRAP DIPOLES (3 types)

TD1/10-80 10, 40 and 80m **£34.44**

TD1/15-80 15, 20, 40 and 80m **£34.44**

TD-P Portable type with winding spools **£30.48**

(TD1 are of 14 gauge copper; TD-P is copper/terylene braid)

### VERTICAL

DX-5V 10-80 metres; approx 26ft high; slimline **£89.00**

### BEAM ANTENNAS (and Rotary Dipole)

DX-31 Rotary dipole for 10, 15, 20m **£46.00**

DX-32 2-element beam for 10, 15, 20m **£80.50**

DX-33 3- " " " " " " **£121.90**

DX-34 4- " " " " " " **£161.00**

DX-103 3-element monoband beam for 10m **£74.75**

DX-105 5- " " " " " " **£97.75**

★ Other Antenna Accessories available - see our Price List ★

ALL PRICES INCLUDE VAT (15%) AND FREE DELIVERY UK.

Send large SAE for further details of this and other equipment - or use our Answerphone after hours.

## Western Electronics (UK) Ltd

HEAD OFFICE (All Mail/Enquiries)

FAIRFIELD ESTATE

LOUTH, Lincs, LN11 0JH

Tel: Louth (0507) 604955/6/7

ACCESS

VISA

H.P.



## YOUR SOMMERKAMP IMPORTER

1 Railway Road,

Blackburn, Lancs. Telephone: 51842.

(Telephone Evenings: Bolton 592929 G4GHE)

### SOMMERKAMP FT767DX

— Same as the FT707 reviewed this month, but includes CW Filter and a YM35 microphone. Full coverage from 80-10 meters, plus of course, the new WRAC bands.

**£559** inc. VAT.

### OTHER SOMMERKAMP H.F. RIGS

FT277ZD. 80-10 metres, AM, SSB and CW. Inc. mic. CW filter, cooling fan, DC converter. **£659**

FT7B. 80-10 metres, complete coverage, inc. mic and mobile bracket. **£429**

FT902DM. 160-10 metres, AM, FM, SSB, CW and FSK. Inc. mic, filters, DC converter and cooling fan. **£959**

### SOMMERKAMP 2m TRANSCEIVERS

TS280. 80 channel synthesised mobile rig, complete with mic and fixing brackets.

50W O/P version. **£199**

10W O/P version. **£159**

FT480R. Multimode mobile, complete with scanning microphone and slip-in bracket. **£359**

We stock genuine Sommerkamp accessories - power units, SWR meters, aerials, etc.

ACCESS and BARCLAYCARD. Send SAE for further details of the Sommerkamp range.

## Spain

In Spain the official Radio Nacional Espana (RNE) high-power broadcasts are at the l.f. end of the band, the most conspicuous being Madrid 585kHz, Seville 684kHz, Oviedo 727kHz and San Sebastian 774kHz. It is the low-power locals that provide the interest for the DXer, and these broadcasters are distinguished by the slogan "La Voz de—" with the call letters ECS or EFE, "Radio Juventud —" with EFJ, "Radio Popular —" with EAK and "Radio —" which uses EAJ.

Listen for EAK14 Radio Popular Pamplona on 1134kHz, EAJ17 R. Murcia on 1179kHz, EAJ10 San Sebastian 1260, ECS10 R. Centro Madrid 1314, EAJ34 R. Gijon 1359, EFJ15 R. Juventud Barcelona 1395, EFE22 La Voz de Asturias 1413, EFE57 LV de Navarra 1503, EAJ40 R. Pontevedra 1521, EAJ47 R. Valladolid 1539, EAJ35 R. Panades 1584, EAJ20 R. Sabadell 1602 and many others on the same channels. Also conspicuous are EAJ5 R. Sevilla on 792kHz and EAJ7 R. Madrid on 810kHz.

It is at sign-off time between midnight and 0100 that the real catches are made. As a dominant station goes off, its place on the channel is taken by a less conspicuous occupant, which may in turn be replaced by a third as the night progresses.

## Portugal

The official Radiodifusão Portuguesa (RDP) outlets carry three separate programmes on the medium waves and a fourth on v.h.f. only. RDP1 comes from Lisbon on 666kHz and from Norte on 719kHz; RDP2 Lisbon is on 756kHz and Norte on 1062kHz while RDP3 is transmitted from Porto on 782kHz and Porto Alto on 1035kHz. All come in well after 2300 but can be heard earlier with a loop. These programmes are also carried by a number of low-power local stations. Look for Castell Branco on 828kHz, Covilha 1562kHz and Lisboa/Canidelo 1579kHz all with 1kW.

Listen for Radio Club Beiras which transmits on 1485kHz with the call CSB20, for Radio Renascenca which has CSB30 on 1170kHz located at Porto and a new outlet CSB5 on 594kHz located in Lisbon to replace CSB3 on 1287kHz.

## QSLs

Spanish and Portuguese stations are good verifiers even to a report in English but do not forget to send an Inter-



This one is from Porto Alto on 1035kHz

HAVING TROUBLE GETTING  
YOUR COPY OF

**PRACTICAL WIRELESS?**

PLACE A REGULAR ORDER  
WITH YOUR NEWSAGENT

national Reply Coupon or unused stamps of the country concerned. A comprehensive list of station addresses is given in the *World Radio and TV Handbook* but a letter sent to El Gerente (manager) followed by the station name (La Voz de Asturias, for example) and the town or city should reach stations in Spain.

## Readers' Letters

"Q Radio" which is CJYQ on 930kHz located at St John's in Newfoundland was monitored regularly in St Andrews by **Dr Eric Duncan** between November 7 and December 30 last year. The receiver is a home-brew superhet with long wire and a.t.u. Reception was never later than 0100 and the only blank night was on November 24 when the Post Office removed the antenna along with some old telephone wires. I wonder where the long wire was fixed?

The Director of Q Radio was surprised to learn that his station was being heard regularly in Scotland, but if you look at a Great Circle map you will see why it should be. Newfoundland is no farther away than Cairo, with the advantage that the path is over water, and it is only QRM that prevents regular reception of broadcasts from this area. Listeners in favourable locations in the British Isles, in parts of Scotland or on the west coast of Ireland ought to be able to pick up the maritime provinces of Canada easily. Can anyone confirm this?

Congratulations to **Mark Hattam** who is now G4KGA. He is still active on the medium waves and uses a Realistic DX160. Best DX recently includes WGY Schenectady NY on 810kHz and KDKA Pittsburg on 1020kHz. Mark connected his loop to the A1 terminal of the DX160 leaving A2 floating, and joined the other lead from the loop to the GND terminal. The DX160 has an internal antenna for m.w. reception.

## DX Heard

"Radio Bilbao 990kHz relayed by R. San Sebastian 1260kHz are broadcasting an international programme Sundays 0000 to 0100, with music and information about the Basque country in Spanish, English, French and German," writes **Roy Patrick** from Derby, who goes on to say that: "San Sebastian gives a nice clean signal, Bilbao is hopeless with QRM from Beacon Radio and Berlin." Roy also heard Radio Globo Brazil on 1220kHz at 0100.

Reader **David Hyams** (Finchley) reports hearing the Faroe Islands on 531kHz some two hours before sunset (in winter), before high-power Europeans and North Africa come in. A nice catch David. Other DX logged included the BBC relays on Cyprus 639kHz and Oman 1413kHz plus Saudi Arabia on 1521kHz.

# Short Wave Broadcast Bands

by Charles Molloy G8BUS

Reports: as for medium wave DX,  
but please keep separate.

Back to antennas again with a query from **Dr P. W. Allen** of Harpenden concerning the impedance and directional pattern of the dipole. This can be a confusing subject, but it need not be so if it is remembered that a half-wave dipole is cut for one band only, and the impedance and directional pattern only apply when the antenna is used on this band.

## Half-wave Dipole

The half-wave dipole antenna consists of a length of wire slightly shorter than half a wavelength, which is cut in the middle and terminated there with an insulator. The impedance at this point is about 70 ohms but only at the resonant frequency (i.e. the frequency to which it is cut). If 70 ohm feeder is used to connect the antenna to the low-impedance antenna input of a receiver, then an antenna tuning unit is not required, since there is already a good match and maximum transfer of signal will occur. This only happens at the resonant frequency.

The half-wave dipole is also directional. At the resonant frequency the direction of minimum pick-up is along the wire and the maximum is broadside-on. At other frequencies the pattern may be different.

The formula for calculating the overall length in metres, of a half-wave dipole for the 49m band, taking 6.075MHz as the mid-band frequency, is  $142.6 \div 6.075 = 23.47\text{m}$ , which is the resonant length for the 49m band.

Since the impedance of 70 ohms and the standard directional pattern are valid only at the resonant frequency, the dipole is a single-band antenna. The impedance is also 70 ohms at multiples of the resonant frequency but the international s.w. bands, unlike the amateur bands, are not harmonically related. This feature is therefore not relevant for broadcast band DXing, except that a 49m dipole should perform reasonably well on 16 metres.

## Practical Considerations

So much for theory: how about the practical side of it? The Aerial Data Chart presented with the November 1979 *PW* gives constructional details for dipoles and the only problem left is that you have a centre-fed antenna. All right if you live in a house with space all around. You can put up a mast on either side in any direction you like and take the lead-in from directly overhead. In my case a half-wave dipole for the 49m band would have to be in a SW/NE direction, with a lead-in from a point some 11.6

metres from the house. Not convenient and the direction would give poor reception from South America and the Far East.

## Inverted V Antenna

You could have the mid-point of the dipole at the chimney and terminate the ends at ground level, making the antenna into an inverted "V" which performs like a half-wave dipole. Not every XYL though will be happy with an antenna fixed to the front fence!

My personal preference is for the end-fed antenna, usually called the long wire by DXers. It is non-directional and need not even be in a straight line. Since it is non-resonant you need an antenna tuning unit to match it to the receiver. This type of antenna performs well and is easy to erect. If, however, you are particularly interested in one band and if the direction permitted by available space is right, then put up a half-wave dipole or inverted "V". You can use it as a "T" antenna on other bands by joining the two wires of the lead in together at the receiving end, using an a.t.u. for matching the "T", and you can do the changeover quickly and easily by means of a switch.

## CBC Northern Service

The Northern Canada Service which broadcasts in English/French/Eskimo/Cree Indian has attracted some attention recently. **Colin Watson** (Cumbernauld) has been listening to the programme on 11 720kHz in the 25m band at 2300 hours. Unfortunately this service no longer QSLs, but a programme schedule is obtainable from Radio Canada International, PO Box 6000, Montreal, Quebec, Canada H3C 3A8.

Reader **Trevor Corns** of Sheffield also picked up the Northern Service on the same channel from 2200 to 2300 with his FRG 7700, 9 metre-long inverted "L" and a.t.u. He says the programming is aimed at Northern Quebec and Labrador via a Canadian domestic satellite link and part of the programme is in local languages.

## Radio Free Grenada

This broadcaster has been heard with a fairly good signal on 15 102kHz in the 19m band by **Adrian Childs** of Dorchester, using his Murphy MS3200 stereo music centre (which has short-wave bands) and the rooftop two-element antenna used for v.h.f. reception. The signal faded



Card marking the 35th Anniversary of Radio Canada International

in at 2030 with a relay of the domestic service. Fourteen-year-old **Andrew Chadwick** (Bury), who is a newcomer to DXing, also picked up R.F. Grenada at 2040, and he wonders what address to write to for a QSL. **Anthony Cross** (Bath) picked up the station at 2030 using his FRG-7000, long wire and a.t.u., and he wonders if the station will QSL. Try PO Box 34, Morne Rouge, St George's, Grenada.

This station was heard by **Steve Browne** in Birmingham using a home-brew receiver with Q Multiplier, Crystal Filter and Audio Notch Filter, along with an a.t.u. and 24 metre-long wire. Where could you buy a receiver like that?

## Tropical Bands

"A Trio R-1000 used with a Mizuho Sky Coupler (a.t.u.) and 30 metre-long wire performs especially well on the Tropical Bands," writes **Stephan Rogalson** of Birmingham who pulled in Radio Anhangueara Brazil on 4915kHz at 0130, R. Sutatenza Colombia on 5095kHz at 0152, the domestic service of Radio Nigeria on 4770kHz at 2142 and Radio Diffusion de Mauritanie on 4845kHz at 2215. From Natal in South Africa comes a note from **Robert Mowrey** regarding the report in the December issue about the station on 3250kHz in the 90m band, which is not Radio RSA but a local commercial broadcaster called Radio 5. It is on 3250kHz between 0300 and 0545, and again from 1535 to midnight, also on 9620kHz in the 31m band between 0550 and 1530.

A 30 metre-long wire and AR88LF are in use at St Leonards-on-Sea by **Harold Brodribb**. His 60m DX covers Radio Uganda 5026kHz, Radio Kabul 4760kHz, Tirana 5057kHz (with 5th harmonic at 25 285kHz), Yerevan 4990kHz at 1855, Kiev 4940kHz and, on 3277kHz in the 90m band, faint Indian music at 1600. **David Hyams** (Finchley) used his DX160 and long wire to pull in Benin on 4870kHz at 0600, Cameroon 5010kHz at 2130, three from Colombia: R. Super 4875kHz at 0500,

R. Colosal 4945kHz at 0620, R. Santa Fe 4965kHz at 0630, La Voz de Nicaragua 5948kHz (49m band) at 0435, South Africa 4880kHz at 2000, Yemen 4853kHz at 1845 and from Venezuela, Ecos del Torbes 4980kHz at 2320, R. Lara 4800kHz at 2335, R. Juventus 4900kHz at 0340 and R. Reloj 5030kHz at 0400.

## Radio Algiers

Reader **Paul McKee** of Belfast would like to know the frequency and times of English broadcasts from Algeria. They are on the air daily in English at 2100 on 254kHz long waves plus frequencies in the 13, 19 and 25m bands though they do move around a bit. Try 11 740, 15 365 or 21 632kHz. The address for an up-to-date schedule is Radiodiffusion Television Algerienne, 21 Boulevard des Martyrs, Algiers.

## DX Heard

Radio Bras (Brasilia) is reported on 15 125kHz in the 19m band by Steve Browne at 1900, by Adrian Childs also at 1900, and by **Andrew Byte** (Holywell) who gives the mailing address as Radio Nacional do Brasil, PO Box 04-0340, Brasilia, Federal District of Brazil.

Eleven-year-old **Peter Manson** of Glasgow, who must be our youngest reporter, has a Grundig Melody Boy 1000 with which he logged the Voice of Greece at 1245 and Radio Sweden at 1240 both in the 25m band. **John A Walker** (Birmingham) used a Selena portable with telescopic antenna to pick up Radio Korea at 1605 on approx 44 metres (6580kHz), Radio Turkey with DX programme at 2320 on 30.5m (9515kHz).

Havana in Cuba on 7135kHz was heard in English at 2200 by **Roy Patrick** of Derby, plus Radio Clarin in Santo Domingo on 11 700kHz with station identification and jingles music at 2330, which means that this 5kW outlet is active again.



**VHF Bands**  
by Ron Ham BRS15744  
Reports to: Ron Ham BRS15744  
Faraday, Greyfriars, Storrington,  
Sussex RH20 4HE.

storm on the 5th to the 8th (Fig. 1) and small ones on the 9th to the 11th. A variety of bursts were again recorded during a mild noise storm on the 12th (Fig. 2), and several strong, short-duration bursts were recorded on the 15th and 16th. The solar noise was so extensive on the 7th that **Harold Brodribb** heard it in the 10m band. No doubt this solar activity was responsible for the 10m band being dead when I checked it at 0845 on the 7th and 0920 on the 9th. **Ted Waring**, Bristol, counted 14 sunspots on January 25, 24 on the 30th, 35 on February 1, 34 on the 10th and 23 on the 13th.

## Aurora

With all that solar activity recorded I was not surprised when **John Branegan** GM4IHJ, Saline, Fife, told me that he logged GMs and LAs during an aurora between 1640 and 1910 on February 5. During another aurora between 1640 and 2030 on the 6th, John said that the 2m band was full of "wall to wall" signals from DK, EI, F, G, GI, GJ, GW, LA, ON, OZ, PA and SM. He also received strong tone-A signals from the 2m beacons in Cornwall GB3CTC, Northern Ireland GB3GI, Wrotham GB3VHF and Germany DL0PR. Although John could hear some amateur signals on 4m there was very little European f.m. heard around the band at the time. During the event, **George Grzebieniak** RS41733, London, heard GM3WOJ

While my radio telescope was recording signals from the active sun, and the trace on my barograph was high and steady, there was little doubt in my mind that this month's postbag would be as fascinating as ever.

## Solar

Both **Cmdr. Henry Hatfield**, Sevenoaks, and I recorded a variety of small bursts of solar radio noise, at 136MHz and 143MHz respectively, on January 22, 25, 27, 28 and a mild noise storm on the 29th. A prolonged solar event began on February 5 and lasted until the 16th, during which time we recorded several large bursts amid a noise


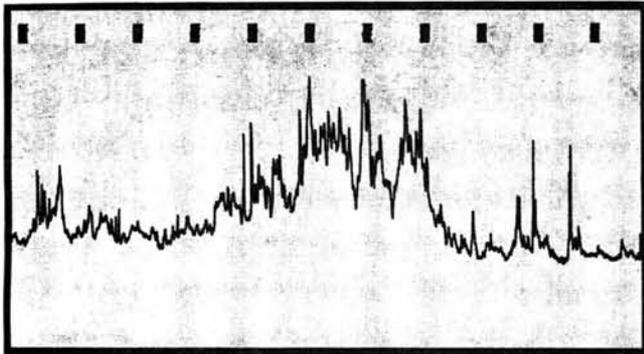


Fig. 1: A solar burst within a noise storm recorded by the author at 143MHz on February 6

Fig. 2: A typical individual solar burst recorded by the author on February 12

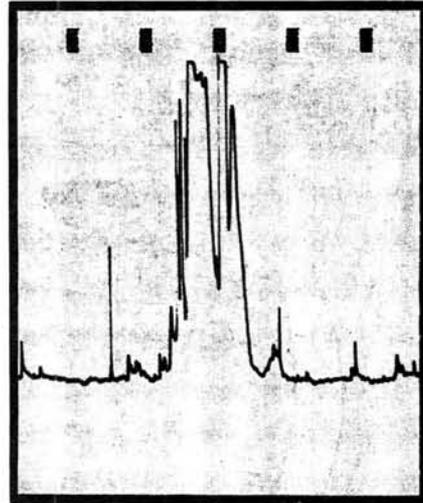

on 4m, and **Roy Banister** G4GPX, Lancing, and G4JGJ/MA (Maritime Anchored), Brighton, heard auroral c.w. on 2m. "I have been in telephone contact with GM4ILS who regularly monitors for aurorae and have arranged to be a link in the warning chain," writes **Phil Hodson** G8RBY, Melton Mowbray, who is prepared in turn to telephone up to five people. Anyone who wants to be included in this should write to Phil, QTHR, and include their phone number and an s.a.e.

## The 6m Band

Congratulations to **Peter Turner**, Brighton, using the callsign GW4IIL/A, on receiving an Americam 6m award for his cross-band work. For the 10m band, Pete uses an FT-200, and to receive on the 6m band he has a Microwave Modules converter into a TS-120V receiver. So far he has worked some 50 stations with this set-up. John Branegan had a cross-band QSO with VE1AVX on January 14 and writes: "GB3SIX, Anglesey, is excellent strength here by meteor scatter, pity they have to switch it off during TV hours."

## The 10m Band

Generally speaking, propagation on 10m has followed the same pattern as in previous months, with Russian signals predominant in the early morning and North Americans at midday. There were of course exceptions. At 0930 on January 27, I received a very strong signal from a VK4 while he was working an SM, and around 0850 on the 28th I heard strong JAs and a VK working SM and HK. Signals from Japan were also heard between 0800 and 0900 on February 1, 3, 4, 5, 6, 8, 11, 12, 16 and 17. Among the more interesting QSOs was a very strong signal from a JA near Tokyo airport working many European stations around 1000 on the 6th, and at 0947 on the 12th I received an "armchair copy" QSO between JA2APA and LX1SI. At 0930 on the 10th I received a 58 signal from ZL2BFU when he was working OH2TI, a club station at the Technical Institution in Helsinki.

**Steve Bowler** RS46105, Newton Bar, has been listening on 10m with a Trio R-1000, a Mizuho a.t.u. and a long wire antenna. Everything is DX when you are new at the

game Steve, keep it up, ten is a fascinating band. "It has been 'VE DAYS' again here," writes Ted Waring from Bristol, who continues to monitor the Canadian beacon VE2TEN and has received a QSL card (Fig. 3) and a log sheet from the beacon-keeper Serge Freve for his efforts. During the 29-day period between January 20 and February 17, I received signals from the beacons in Bahrain A9XC on 26 days, Bermuda VP9BA 10 days, Cyprus 5B4CY 24 days, Germany DL0IGI 27 days and DK0TE 7 days. In addition to the Canadian beacon, Ted often receives signals from the beacons in Florida W4ESY, Mauritius 3B8MS and South Africa ZS6DN and ZS6PW.

## RTTY

Until I purchased my MM2000 and fed the signals into an Ultra 12in TV, I did not realise just how much enjoyment there is in reading amateur RTTY signals. There is a lot of activity around 14 090kHz and I have so far logged signals from stations in Austria, France, Germany, Italy, Poland, Spain, Switzerland and Sweden. The MM2000 almost operates itself once its tuning lights are responding to the twittering RTTY signals coming from my FR-101. At 0912 on January 24 I received good copy, both ways, from SM7EVV working DL0CI. The SM was using a Yaesu FT-707 and a PET CBM3008 for RTTY, and the DL was operating from a club station. My best DX so far

**PLEASE MENTION  
PRACTICAL WIRELESS  
WHEN REPLYING  
TO ADVERTISEMENTS**

Whether you are: just starting, taking an R.A.E. course, just licensed, or an old timer, SMC has something for you. . . . And at the right price.

**PRICES** on this page **INCLUDE VAT** at 15%, **INCLUDE SECURICOR** speedy delivery and **INCLUDE A TWO YEAR WARRANTY** (remember as Yaesu Musen UK distributors our guarantee is **FACTORY BACKED**).

We take **ACCESS AND BARCLAYCARD OVER THE PHONE**, offer attractive **HP** (including a **FREE FINANCE SCHEME** on many regular priced items) on application. We have branches and agents conveniently situated across the country plus the biggest mail order department here in Totton. What ever your requirements SMC is your single stop.

## FRG7700



### COMMUNICATIONS RECEIVER

From 30MHz to 150KHz (lower at reduced spec.) in 1MHz bands. SSB, CW, AM, FM. On 10m and with a convertor the NBFM detector with squelch (plus a noise blanker) opens new horizons.

4 filters fitted as standard! SSB, 2.7KHz and FM 15KHz. For AM, 3 positions! Narrow 2.7KHz, Medium 6KHz and Wide 12KHz, with tone control, and switchable AGC.

- ★ 150kHz-30MHz no gaps
- ★ SSB-CW-AM and FM
- ★ Up-conversion no preselector
- ★ 12 channel memory option
- ★ Mains and 12 volts dc option
- ★ Clock/timer built-in

No preselectors! Up conversion with a 48MHz crystal filtered IF plus dual PLL system provides automatic selection of the input bandpass filter direct from the band selector or memory. The inbuilt quartz clock/programmable timer has battery back-up.

12 frequencies anywhere within the range may be stored by simply touching the M button, no preselector adjustment, no range switch adjustment. The memory is tunable by  $\pm 1$ KHz and is kept alive year long by 3'AA' dry cells.

**FRG7700 £309 FRG7700M £389**



**GaAs FET R.F. stage!!**

**FT780R £409**

70cms Synthesized. 100, 25, 1kHz stops on FM. 1kHz, 100Hz, 10Hz stops on SSB. 10W PEP. E&EO



**FT480R £359**

2m. Synthesized. 25, 12.5, 1kHz steps FM 1kHz, 100, 10Hz, steps SSB, 10W PEP.



**FT/FP200 £335**

10-80m. SSB, CW, 240W PIP. Premix VFO. C/W FP200 AC PSU/Speaker.



**FRG7 £199**

0.5-30MHz General Coverage Receiver. 230V AC. 12V DC. + Battery pack. AM/SSB.

PRICES INCLUDE VAT @ 15%



**FRG7000 £259**

0.25-30MHz General Coverage Receiver. 230V AC. AM/SSB Timer.

FREE SECURICOR DELIVERY



**FT902DM £799**

10-160m. SSB, CW, AM, FM, 9 bands (DE version E713 D version E724)

2 YEAR DISTRIBUTOR WARRANTY



## SOUTH MIDLANDS COMMUNICATIONS LIMITED

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND  
Tel: Totton (0703) 867333, Telex: 477351 SMCOMM G, Telegram: "Aerial" Southampton

### S.M.C. Agents

G3ZUL Stourbridge (03843) 5917  
GM8GEC Edinburgh (031665) 2420  
G13WVY Tandraee (0762) 840656  
G13KDR Bangor (0247) 55162  
GW3TMP Pontyboodin (035287) 846/324  
GW8EBB Swansea (0792) 872575  
GJ41CD Jersey (0534) 26788

### S.M.C. (Leeds) BRANCH

LEEDS,  
Colin Thomas, G3PSM  
257 Otley Road,  
Leeds 16, Yorkshire.  
Leeds (0532) 782326  
9-5.30 Monday-Saturday

### ★ S.M.C. (Jack Tweedy) LTD

CHESTERFIELD,  
Roger Baines, G3YBO  
102 High Street,  
New Whittington, Chesterfield.  
Chesterfield (0246) 453340  
★ 9-5 Tuesday-Saturday

### ★ S.M.C. (Jack Tweedy) LTD

WOODHALL-SPA,  
Jack Tweedy, G3ZY  
150 Horncastle Road,  
Woodhall Spa, Lincolnshire  
Woodhall Spa (0526) 52793  
★ 9-5: Tues-Sat (- appointments)

# GAREX (G3ZV1)

**RESISTOR KITS** a top-selling line for many years. E12 series, 5% carbon film, 10Ω to 1M, 61 values, general purpose ratings  $\frac{1}{4}$ W or  $\frac{1}{2}$ W (state which)

Starter pack 5 each value (305 pieces) **£3.10**

Standard pack 10 each value (610 pieces) **£5.55**

Mixed pack, 5 each  $\frac{1}{4}$ W +  $\frac{1}{2}$ W (610 pieces) **£5.55**

Giant pack, 25 each value (1525 pieces) **£13.60**

**NICAD RECHARGEABLES** physically as dry cell: AA(U7) **£1.30**; C(U11) **£3.35**; PP3 **£5.55**. Any 5+: less 10%, any 10+: less 20%.

**AMPLIFIER MODULE** new, fully assembled 6W IC unit, 12V DC. Low impedance (4-8Ω) input and output for extrn. speaker amplification, with circuit **£2.75**

**CRYSTALS FOR 28.5MHZ** 3rd. overtone, suit most 'CB' rigs. 28.5MHz Tx and 28.045MHz Rx. HC18U **£4.60 per pair**

**CRYSTAL FILTER** 10.7MHz, 12 $\frac{1}{2}$ kHz channel spacing, ITT type 901C **£6.90**

**CO-AXIAL CONNECTORS & ADAPTORS** see full list.

**PL259** UHF plug with reducer **75p**; S0239 UHF socket, panel mtd. **60p**; 2 x S0239 inline coupler **£1**; 2 x PL259 inline coupler **£1**. Any 5+ connectors: less 10%

**HT TRANSFORMER** multi-tap pri.: 5 secs.: 35v 200mA, 115v 150mA, 50v 500mA, 150v 300mA, 220v 300mA **£5**

**HT CHOKE** top grade type, 9H 240mA **£3.50**

**PYE CAMBRIDGE SPARES** (our speciality, see full list). Ex. equip., fully guaranteed. Rx RF board 68-88MHz **£5.95**. 10.7MHz I.F. **£3.65**. 2nd mixer 10.7MHz to 455kHz **£3**. 455kHz block filter 12 $\frac{1}{2}$ kHz **£9.40**, ditto 25kHz **£3**. 455kHz AM I.F. **£3.65**. Audio bd. **£1.95**, and many more. Vanguard & Westminster spares also.

## MONITOR RECEIVERS

### SX-200 VHF-UHF AM-FM SCANNER

Covers 26-88MHz, 108-180MHz and 380-514MHz, AM + FM, it scans, seeks, memorises and beats all the others. See full details.

**HF-12 POCKET SIZE FM** 12 channel xtal controlled. 4MHz bandwidth in range 130-174MHz. With nicad and charger **£57.95** Xtals extra, see below.

**SOUNDRAIR 008 PORTABLE FM SCANNER** 8 channel xtal controlled 140-170MHz. With nicad and charger. **£59** Xtals extra.

**SR-9** top-selling monitor: 2m FM with 144-146MHz full coverage VFO + 11 xtal controlled channels; ideal for fixed, /M, /P use. 12V DC operation **£47.50**

**Marine band SR-9**, 156-162MHz, same spec. and price.

**CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B** All 2m channels from 0 (145.00) to 32 (145.80) incl. at **£2.46** (+15p post per order). Over 40 popular marine channels at **£2.85** (+15p post). Non-stock xtals made-to-order in 3 weeks at **£4.30** each. See list.

**'SCAN-X' VHF/UHF BROADBAND FIXED STATION AERIAL** **£19.90** Ideal for SX-200 and other VHF/UHF receivers.

We also stock the:

**KDK 2025 2m SYNTHESISED TRANSCEIVER** Full band coverage 25 or 12 $\frac{1}{2}$ kHz steps/10 channel memory/scans memories or selected band portion/3W or 25W Tx/all the features you need at **£225**

**YAESU FRG 7700 GENERAL COVERAGE RECEIVER** 150kHz - 30MHz AM/USB/LSB/CW and FM **£309**

**MAINS PSU** British made by GAREX 12 volt 1 Amp regulated, adjustable 10-16v **£15.95**

**MAIN DISTRIBUTOR OF REVCO AERIALS & SPECIAL PRODUCTS** (trade enquiries welcome)

PRICES INCLUDE UK POST & PACKING & 15% VAT.

## GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH, TRING, HERTS HP23 4LS.

Phone 0296 668684. Callers by appointment only.



Bedford 0234 854133

# AUDIOCOMM

76 BEDFORD ROAD,  
KEMPSTON, BEDS

AUTHORISED DEALERS FOR:

- YAESU ● FDK ● JAYBEAM
- MICROWAVE MODULES
- BANTEX
- RSGB PUBLICATIONS, ETC

SCANNERS, RECEIVERS, AERIALS,  
PLUGS, SOCKETS & CABLE AT  
COMPETITIVE PRICES - SEND FOR  
FREE LIST

CREDIT SALE, ACCESS, BARCLAYCARD  
AND OUR OWN CREDIT CHARGE CARD

OPEN TUES-SAT  
COME AND VISIT OUR 'SHACK' SOON  
G8XIE

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories which have been up-dated to suit the novice and the expert.

**£14.50 INCLUSIVE** - the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

**AT LAST** - a battery eliminator kit, which will last you a lifetime - for use in all H.A.C. valve receivers. H.T. batteries are now unobtainable, this will solve your problems for only £9.60.

**T TWIN TRANSISTOR RECEIVER**, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £17.50 this receiver is outstanding value, and will give you hours of interest and entertainment.

**NEW - TRIPLE-T RECEIVER**, a more advanced super three transistor receiver, loud, clear reception, value unequalled at bargain price of £24.00.

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

**SORRY, NO CATALOGUES WITHOUT S.A.E.**

**'H.A.C.' SHORT-WAVE PRODUCTS**  
P.O. Box No. 16, 10 Windmill Lane  
Lewes Road, East Grinstead, West  
Sussex RH19 3SZ

## Helpford components:-

PT9795	per pair	£17.90
Monolithic R/D Ceramic 100NF	each	£0.20
VFO P.C.B.		£1.15
Buffer P.C.B.		£1.15
G4CLF P.C.B.		£4.24
Preselector P.C.B.		£1.48
Pre-Amp P.C.B.		£1.42
Ist-Amp P.C.B.		£1.36
SL1612	f..	56
SL1621		£2.07
SL6270		£2.51
SL1640		£2.07
SL6310		£2.51
2N5771		£0.31
SL560C		£4.97
BA182		£0.36
78L06		£0.59
J304		£0.54
J310		£0.87
FX2249	per pair	£0.60
SBL-1 = (MD108)		£4.90
SL560C		£4.97

+ Postage & Packing £0.35.

VFO/CAP 4170/75/023 incl. 12		£8.84
VFO ADJ/TORO. Ball Drive 5620		£4.41
4 Gang (Preselect) CAP.		
5318/4/102		£7.73
Preselector (Reduction Drive)		
5870/3		£1.76

+ Postage & Packing £0.50

## HELTFORD

(Troubleshooting by the designers.)  
Any problems send S.A.E. + Invoice  
Number.

## HOME BRU RADIO

(Mail order only)

55 Ashley Road, Parkstone,  
Poole BH14 9BT.

Delivery on Jackson Capacitors  
4/6 weeks.

came at 0934 on February 9 when I received good copy from VK2ZN, Sydney, who was working F6EXG. On February 10 a German station was type-testing with "the quick brown fox jumps over the lazy dogs back".

My first RTTY signal on v.h.f. came during the tropo opening, near midnight on January 29, when I received good copy from Phil Hodson G8RBY on 144.6MHz. At 1318 on the 30th, Phil, who has a solid-state message recorder on his VDU, replayed the message he received from the station he was working in Cologne. Phil's biggest bit of pleasure from the opening came when he worked G4ABM, Cleveland, in ZO square at 2128 on the 27th, and at 0049 on the 28th he was called by GD3YEO and had an enjoyable natter. At 1307 on the 30th Phil had a 45-minute QSO with DD3KM/A who was making his first RTTY contact with G, and later in the afternoon Phil worked ON1APE, ON7MQ and PA0SQE. During the lift at the end of January, **Tony Phillpott** G4IMP, Folkestone, tuned his FT-221R to 144.6MHz and, running just 10W to a 10-ele Yagi, had an hour or so RTTY contact with DB8EB. Tony uses an old Creed 7B teleprinter and an ST5 terminal unit.

Anyone wishing to become a member of the British Amateur Radio Teleprinter Group should write to Mrs I. D. Double, 89 Linden Gardens, Enfield, Middx. Ted Double G8CDW would like to remind readers about the BARTG 2nd Spring VHF-UHF Contest which takes place from 1800 on the 18th to 1200 on the 19th of April (GMT). Further details and log sheets from Chris Plummer, G8APB and G8CDW, QTHR.

## Tropospheric

At midday on January 20 the atmospheric pressure rose sharply from 29.9in (1012mb) to 30.3 (1026) by midnight, rising a little more to 30.4 (1029) by noon on the 22nd, and reaching 30.6 (1036) by midday on the 28th. It hovered there until noon on February 2 and then fell rapidly to 29.9 in less than 24 hours. As expected, this long period of high pressure increased the range of v.h.f. and u.h.f. signals, and true to form, a few days before the pressure fell, an extensive tropospheric opening occurred. Band II was badly affected and a major victim of this event was the EBU concert to commemorate Mozart's bi-centenary, during the evening of January 29. This programme was so important that the BBC re-arranged their schedule and many people I spoke to during the previous week were looking forward to it. This could have killed the layman's confidence in stereo v.h.f.

"I believe the EBU concert over BBC Radio 3 was somewhat a shambles and I can imagine how disappointed listeners were," writes **Simon Hamer**, Presteigne, who heard a variety of programmes from France, BBC Radios London, Manchester, Sheffield and Solent, and ILR Capital between 1955 and 2100 on January 20. He also heard many French stations during the evening of the 21st and 22nd, and BBC London, Medway and Solent and ILR Capital, LBC and Thames Valley on the 23rd. During the evenings of the 25th, 26th and 29th he added pop music and adverts from Italy, football results from Belgium, and opera and rugby results from France. **Reg Moores**, Brighton, heard strong French stations in Band II during the evening of the 25th, and **Eric Arnold** G4JDJ, Brighton, found continentals interfering with the BBC stations on the 27th. "The high atmospheric pressure produced a very long period of exceptional French reception," writes Harold Brodribb, St Leonards-on-Sea, Sussex. On most days he logged 18 French stations and 5 editions of BBC Radios 2, 3 and 4, and on February 2 he heard 16 French and 5 Dutch stations.

VE2TEN				
Serge Frève				
1505 des Martinets				
Chicoutimi - Québec				
Canada - G7H 5X9				
Time for report				
GSO via radio	Date			
Ted Waring				
GMT	MHz	Band	R ST	Mode
				SSB
				CW
Pst OSL INX TO Serge				

Fig. 3: A QSL card for the Canadian 10m beacon, received by Ted Waring

Needless to say, the amateur bands were full of DX and while the repeater channels were stacking up several deep some operators were not sure which one they were working through. While listening to the Buxton repeater GB3HH R4, predominant in Sussex, I heard one operator say it was Bedlam, which just about summed the situation up. "Some of the 2m signals were colossal strength," said **Cyril Fairchild** G3YY, Brighton, who heard several EAs on 2m f.m. During the evening of the 30th both **Alan Baker** G4GNX, Newhaven and first-timer **Deryck Arnold** G8OUK worked G8URE/A in Plymouth via the Brighton repeater, GB3SR R3. At 1300 on the 30th, Alan worked G8SEE/M Redruth, both using 10W, via GB3SR and followed this with a simplex contact. During the evening of the 29th Alan worked G3XDY, Ipswich and a DJ on s.s.b. and a PA0 on c.w., on the 30th four French stations on s.s.b. and one on c.w., and on the 31st he had c.w. contacts with three PA0s, an ON and a DJ. "There were many continental repeaters up," said Alan, who at times was receiving signals from the Cornish beacon, GB3CTC, at 559 and the Paris beacon, FX0THF was sending his meter over the stop.

**Mark Evans** G8CTN, Burgess Hill, using 10W from a Trio TR-9000 to a 4-ele quad, worked stations in Northern G. Cornwall, Somerset, PE, F and ON, heard a GM on s.s.b., and worked an ON using horizontal f.m. **Bob Hodge** G8TYW, in nearby Hurstpierpoint, Sussex, using a home-brew rig giving 5W to a 5-ele Yagi, worked stations in France and Holland, and both Mark and Bob worked their fellow Mid-Sussex club member, Jonathan Wymer G8URE/A in Plymouth. Outside the main event Mark has worked G4FRZ in Abbots Langley, who uses 500mW to a dipole. At 1243 on February 2, **Adrian Boyd** G8NNY/M, Horsham, using a TR-2300 giving 1W to a Microwave Modules 25W linear and a  $\frac{7}{8}\lambda$  gutter-mount aerial on his car in Eastbourne town centre, worked PA3BFB/M in the town centre of Rotterdam. Later, from Beachy Head, Adrian worked PE1FBR, near Rotterdam.

At 2217 on January 31 **John Parry** GJ8RRP, St Saviour, was mobile on the north coast of Jersey and had a QSO with G8OQT, Wembley. Between January 24 and February 1, George Grzebieniak heard stations in Northern G. GM, France and Holland on 2m, Devon, GW, DJ and PA on 70cm, and ON and PA on 23cm. George also keeps a daily record of atmospheric pressure, temperature and the weather charts from his newspaper to compare with his 2m and 70cm log. For most of the 30th and 31st I was receiving signals from the Sutton Coldfield beacon, GB3SUT, at 569-599 with only a dipole feeding

my 70cm receiver. "My most enjoyable moment on 2m s.s.b.," writes Phil Hodson, "was hearing Bill, G8YYO in Ilfracombe calling CQ. I gave him a call and we got chatting. Bill was 650ft a.s.l. near Ilfracombe, running 100W, and we were colossal signals with each other. For a laugh, I asked Bill to give me a report on 5W and he came back, 10 over 9! He then dropped to 6W and likewise was 59 plus with me. I dropped to 1W and still got 59, then down to 100mW and received 45, and on 40mW a report of 33." I congratulate the pair of you on a most interesting v.h.f. experiment over a 175-mile path.

During the 70cm contest on February 8, George Grzebieniak heard G3XMG, Lancs, GD2HDZ and GW8AAP/P. The atmospheric pressure was again doing the right things on the 8th, because at 1900 I heard that an EA was worked from London on 2m, **John Cooper** G8NGO, Cowfold worked 12 French stations, Alan Baker worked F6GDX and George Grzebieniak heard F6GDX at 630km.

## News Items

Congratulations to Deryck Arnold, Hove, on passing the December RAE and getting Dad's (now G4JDJ) old call-sign G8OUK. Deryck uses an ICOM IC-2E and is often heard working through the Crawley repeater GB3BP R6. At times, under Dad's supervision, he has worked VK5ARZ on 20m.

Now that the BBC World Service programme *World Radio Club* has finished, **Ian Galpin**, Poole, reminds us that another BBC programme, *Waveguide*, is of similar interest and is transmitted at 1709 GMT Thursdays and 0439 and 2154 on Fridays.

For those of my readers who are interested in vintage radio I can recommend a new book called *Early Wireless* by Anthony Constable, published by Midas Books. Many readers will know Anthony as the founder of the British Vintage Wireless Society.

We regret to report the sudden death of **Ern Hoare** G3RZD. Throughout his life, Ern made a great contribution to many aspects of amateur radio and was one of the partners in the famous "Two Ern's" microwave team. We extend our deepest sympathy to his family and his many friends.

**TV**

by Ron Ham BRS15744

Reports: as for VHF Bands,  
but please keep separate.

"I set the five spare tuners on our Mitsubishi receiver to Crystal Palace for BBC1, BBC2 and ITV, and Sandy Heath for Anglia ITV and BBC1 East. Past experience has shown that they appear every time the atmospheric pressure is high and then a wider range of programmes is available for the family," writes **Simon Hamer**, Presteigne, Wales. This is a marvellous idea Simon, you now have your own DX detector and I bet it paid off during the last week in January.

## Tropospheric

Obviously the big tropospheric opening, described in *VHF Bands*, must take pride of place in this month's column. On January 30, **Steve White**, Huntingdon, Cambs, received full u.h.f. colour pictures from a Dutch station showing English adverts with sub-titles. This was followed by a quiz game where a car was won, and an announcer with the station ID AVRO above his right shoulder. This is a very interesting report, Steve, especially as you are using a standard Philips CTV with a set-top antenna in a location surrounded by trees.

One French station that **Cyril Fairchild** G3YY worked on 2m, told him that he was receiving perfect pictures from BBC u.h.f. television for several hours. At around the same time, **Adrian Boyd** was receiving French TV in Horsham, on Channels 21 and 30 using the loop antenna on the back of his set. Further north in London, **George Grzebieniak**, using a 91-ele Yagi, received pictures from Germany on Chs. 27 and 35 on January 30 and Holland on Chs. 28 and 55 on the 31st. One of the German programmes George saw was about Africans, followed by an adventure programme called *DEREK*. **George Garden**, using a 10in Sanyo CTV at the top of a block of flats in Bracknell, watched the close-down of Tyne Tees TV from Bisdale, Ch. 29, on the 29th, and the German station ZDF giving details of the week's programmes and a clock from the Belgian station RTB F1 on the 31st. I received pictures throughout the event from the IBA transmitter at Lichfield on Ch. 8. **John Thompson**, Gillingham, Kent, using a JVC 3040 plus an Antiference XG14 antenna and rotator, also checked Band III and on January 30 saw a Charles Bronson film, in English, from BRT-1 Belgium on Ch. E10. For most of the time between the 27th and 29th, **Sam Faulkner**, Burton-on-Trent, received test cards and programmes from Ireland, RTE1 Ch. 1H and RTE2 Ch. 1G, in Band III. Sam also saw Southern Television's *Day-by-Day* programme, on Ch. 42, being interfered with by a French station. Like Steve White, Sam saw the Tele Bingo Quiz from Holland in addition to an English film with Dutch sub-titles. During the event he saw a discussion programme, the American series *Vegas* and *Televieze Magazine* from Holland on Ch. 29, and on Ch. 35 a YL announcer appeared with the station ID, ZDF. "Unidentifiable pictures occupied Ch. 48, and generally the whole of the lower u.h.f. spectrum, which under normal conditions is crowded here, was simply chaotic," said Sam.

During January 29, 30 and February 1, John Thompson received pictures from Anglia TV on Ch. 59, Tyne Tees TV on Ch. 29, Nederlands 2 on Ch. 31, and test cards from the German u.h.f. stations NDR, WDR and ZDF. On January 26, Simon Hamer, using his own TV176 and the family Mitsubishi CTV, watched *Nationwide* from Crystal Palace on Ch. 26, *About Anglia* from Sandy Heath on Ch. 24, and *Look East* from Sandy Heath on Ch. 31. Although on this occasion the signals were only fair, it was the start of the event and as time went on these signals were soon bumping in. On the 29th he added pictures from France on Chs. 27 and 29, and on the 30th he saw the closing programme from Thames TV, London, in good colour.

Down in Folkestone, **Nicholas Wythe** is getting very good results from a modified Bush TV183D dual-standard receiver incorporating switching for the French system, supplied by Hugh Cocks, and can normally receive FR3 (Fig. 1) from Dunkirk. During the opening Nicholas received many Belgian, Dutch and German signals (Figs. 2, 3, 4) and saw test cards, a documentary and programmes about rock music and Dr. Snuggles. Another very important observation Nicholas made was to try for DX on his parents' Baird Teletext receiver, and although

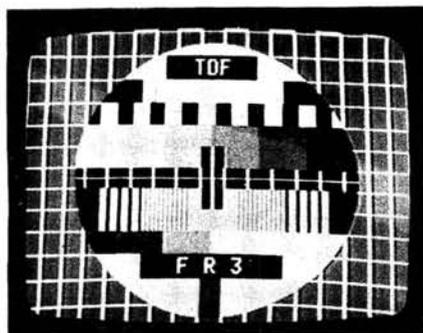


Fig. 1: A test card signal received from Dunkirk

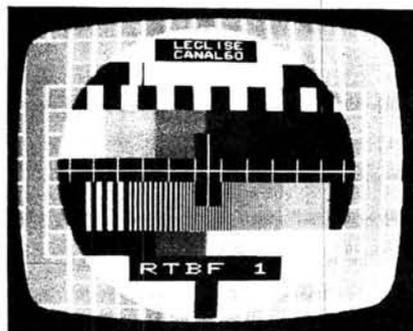


Fig. 2: A test card from Belgium received on Ch. 60 on January 29

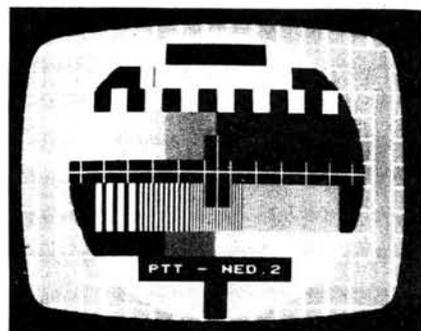


Fig. 3: A test card from Holland received on Ch. 32 on January 29



Fig. 4: Programme details from ZDF received on February 1



Figs. 5 and 6: Two Teletext pages received from Belgium BRT Egem on Ch. 43 on January 30



The pictures shown above were all received by Nicholas Wythe in Folkestone, Kent

the antenna was pointing in the wrong direction he received Teletext pictures from Belgium BRT Egem on Chs. 43 and 46 (Figs. 5, 6) in excellent colour on the 30th. Like the others, T. Amp RS46056, London, enjoyed the event, and among the many u.h.f. pictures he received from Belgium, Germany and Holland, he saw a Schools programme from Holland *Russian for Beginners*, Sport from Germany and a variety of announcers at work. His real prize came some days later, at 1230 on February 9, when he received pictures for the first time from RTL Luxembourg on Ch. 21.

At 1810 on January 30, S. A. Spiller, Sutton, Surrey, watched a cartoon programme, *Scooby Doo*, with Dutch sub-titles, and was among those who saw the Tele-Bingo quiz from Holland on Ch. 28. During the event, Mr Spiller used his VCR to record some of the DX in good colour.

## Aurora

"Both sporadic E and auroral conditions seemed present on January 21," writes Sam Faulkner. "I heard an SM station on 6m, 4m/10m crossband say he was copying auroral signals on Ch. R1 49.75MHz. I immediately tuned and logged TSS Russia with BPEMR news and other programmes between 1720 and 1830." Sam also received flickering pictures during that time on Chs. E2 48.25MHz, E3 55.25MHz and R2 59.25MHz. John Branegan, Saline, Fife, received pictures from Arctic TV on Chs. E2 and E4 during an aurora between 1400 and 1600 on January 26, again between 1640 and 1910 on February 5, and from Norge Melhus on Ch. E2 during the aurora on the 6th.

## SSTV

"Despite poorer SSTV conditions on 10m, east coast USA activity has been seen here almost daily," wrote Sam Faulkner on February 9. On January 24 he logged pictures from WA0PQD, WB0QCD, WD0ADZ and KOLSW, at 1300 on the 25th VOIBL, at 0900 on February 1 17PQD and at 1745 on February 3 HK3DBQ.

## F2

Although, like John Branegan, I had not received pictures via F2 since early in January, there was an event between 0845 and 1045 on February 17. It began as usual with weak sync pulses, audible on Ch. R1, gradually getting stronger until smeary pictures filled the screen. Although mainly unidentifiable, the outline shapes of announcers were periodically seen and there was evidence of a news programme.

## BATC

The British Amateur Television Club has been going now since 1949, and its members are involved with all aspects of DXTV. The club is affiliated to the RSGB and has a representative on the Society's VHF Committee. Readers who wish to join or require further information should write to: B. Summers, 13 Church Street, Gainsborough, Lincs.



```

10 FOR I=N THEN GO TO 6
20 I=1 TO N
30 X=I*(X)
40 X
50 I=0
60 I=J+1
70 N OR J=N THEN GO TO 48
80 I=J+1
90 AT A(J)>A(I) THEN GO TO
100 J=A(J)
110 A(J)=A(I)
120 A(I)=J
130 I=J-1
140 I THEN GO TO 15

```

### New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer (not available yet – but coming soon!)
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.

# sinclair ZX81

**Sinclair Research Ltd,**  
6 Kings Parade, Cambridge, Cambs.,  
CB2 1SN. Tel: 0276 66104.  
Reg. no: 214 4630 00

*Practical Wireless, May 1981*


## If you own a Sinclair ZX80...

The new 8K BASIC ROM used in the Sinclair ZX81 is available to ZX80 owners as a drop-in replacement chip. (Complete with new keyboard template and operating manual.)

With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 – including the ability to drive the Sinclair ZX Printer.
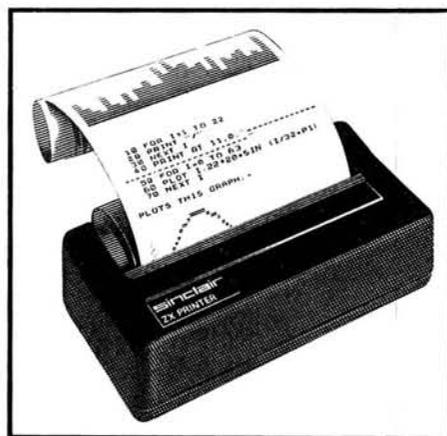
## Coming soon – the ZX Printer.

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumerics across 32 columns, and highly sophisticated graphics. Special features include COPY, which prints out exactly what is on the whole TV screen without the need for further instructions. The ZX Printer will be available in Summer 1981, at around £50 – watch this space!



## 16K-BYTE RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.



### How to order your ZX81

**BY PHONE** – Access or Barclaycard holders can call 01-200 0200 for personal attention 24 hours a day, every day.  
**BY FREEPOST** – use the no-stamp-needed coupon below. You can pay by cheque, postal order, Access or Barclaycard.  
**EITHER WAY** – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack(s).	18	49.95	
	8K BASICROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95
				<b>TOTAL £</b> _____

Please tick if you require a VAT receipt

\*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ \_\_\_\_\_

\*Please charge to my Access/Barclaycard account no. \_\_\_\_\_

\*Please delete/complete as applicable. \_\_\_\_\_ Please print.

Name: Mr/Mrs/Miss \_\_\_\_\_

Address \_\_\_\_\_

**FREEPOST – no stamp needed.**

PRW05

## FAMOUS LOUDSPEAKERS

Post £2

MAKE	model	size	watts	ohms	price
Seas	Tweeter	4in	50	8	£7.50
Goodmans	Tweeter	3in	25	8	£4.00
Audax	Tweeter	3in	60	8	£10.50
Seas	Mid-Range	4in	50	8	£7.50
Seas	Mid-Range	5in	80	8	£10.50
Seas	Mid-Range	4in	100	8	£12.50
Goodmans	Full-Range	5in	15	8	£6.50
Goodmans	Full-Range	8in	20	8	£5.50
Seas	Woofers	8in	30	8	£14.00
Rigonda	Full-Range	10in	20	8	£5.50
Goodmans	Audiom	12P	60	8	£20.00
Goodmans	Di12	12in	90	8/15	£27.50
Goodmans	Audiom	12P	50	8/15	£20.00

## BATTERY ELIMINATOR MAINS TO 9 VOLT DC

Stabilised output, 9 volt 400 m.a. UK made with terminals. Overload cut out. 5 x 3 1/2 x 2 1/2 in. Transformer Rectifier Unit. Suitable Radios. Cassettes, models, £4.50

## E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. £9.95

10W. State 3 or 8 ohm. Post £1

15W model £10.95

8 ohms Post £1

GOODMANS 20 Watt Woofer

Size 8in. 4 ohms. £6.00

Rubber cone surround. Post £1


GOODMANS TWIN AXIOM 8

8in. 8 ohm Hi-Fi Twin Cone Post £8.00

Special unit 15 watts Post £1



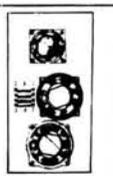**EMI MINI MODULE KIT 3-way Loudspeaker System, EMI 5in Bass, 5in Middle, 3in Tweeter, with 3-way Crossover and Ready Cut Baffle. 15 x 8 1/2 in. Full assembly instructions. Response = 60 to 20,000 cps 12 watt RMS. 8 ohm. £10 ea. £18-50 pair. Postage £1-50.**



## R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 8 x 5in. £3-00. 6 1/2 in. £3-00. 8in. £3-50. 10in. £4-00. 12in. £4-50.

6 ohm. 2 1/2 in. £1-50. 3in. £1-50. 5in. £1-50. 8in. £3-50. 12in. £4-50. 16 ohm. 6 x 4in. £1-50. 5in. £1-50. 8in. £3-50. 12in. £4-50. 10 x 6in. £3-50. 25 ohm 3 1/2 in. 35 ohm 3in. £1-50.

## LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 12V 20p; 25V 20p; 50V 30p;  
1000mF 12V 20p; 25V 35p; 50V 50p; 1200mF/76V 80p.  
2200mF 6V 25p; 25V 42p; 40V 60p; 2000mF/100V £1-20.  
2500mF 50V 70p; 3000mF 25V 50p; 50V 65p.  
3300mF 63V £1-20; 4700mF 63V £1-20; 2700mF/76V £1.  
5000mF 35V 85p; 50V 95p; 5600mF 76V £1-75.

## HIGH VOLTAGE ELECTROLYTICS

8/450V 45p 8-8/450V 75p 50+50/300V 50p  
16/350V 45p 8+16/450V 75p 32+32/325V 75p  
32/350V 75p 20+20/450V 75p 100+100/275V 85p  
50/350V 90p 32-32/350V 90p 150+150/275V 70p  
50/500V £1-20 32-32/500V £1-80 220/450V 95p

## MANY OTHER ELECTROLYTICS IN STOCK

**TRIMMERS** 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.  
**CONDENSERS VARIOUS**, 1pF to 0.01mF, 3p.  
**PAPER** 350V-0.1 7p; 0.5 13p; 1mF 150V 20p; 2mF 150V 20p  
400V-0.001 to 0.05 5p; 0.1 15p; 0.25 25p; 0.47 35p.  
**MICRO SWITCH SINGLE POLE CHANGE OVER 20p.**  
**SUB-MIN MICRO SWITCH £1.25.** Single pole change over.  
**TWIN GANGS** 120pF 50p; 500pF £1.  
**GEARED TWIN GANGS** 25pF 95p; 365pF £1;  
365 - 365 - 25 + 25pF £1.  
**NEON PANEL INDICATORS** 250V. Red 1 1/2 x 3/4 45p.  
**ILLUMINATED ROCKER SWITCH.** Single pole. Red 85p.  
**RESISTORS.** 10Ω to 10M. 1/2W, 1/4W, 1W, 20% 2p; 2W, 10p.  
**HIGH STABILITY.** 1/2W 2% 10 ohms to 1 meg., 8p.  
Ditto 5%. Preferred values 10 ohms to 10 meg., 3p.  
**ALUMINIUM CHASSIS** 18 s.w.g. Undrilled, 4 sides, riveted corners: 6 x 4 x 2 1/2 in.—£1-20; 8 x 6 x 2 1/2 in.—£1-50; 10 x 7 x 2 1/2 in.—£1-90; 14 x 9 x 2 1/2 in.—£2-50; 16 x 8 x 2 1/2 in.—£2-40; 12 x 3 x 2 1/2 in.—£1-50; 12 x 8 x 2 1/2 in.—£2-20; 15 x 10 x 2 1/2 in.—£2-70. **ANGLE BRACKET** 6 x 1/2 x 1 1/2 in.—25p.  
**ALUMINIUM PANELS** 18 s.w.g. 12 x 12 in.—£1-30; 14 x 9 in.—£1-20; 6 x 4 in.—36p; 12 x 8 in.—90p; 10 x 7 in.—80p; 8 x 6 in.—60p; 14 x 3 in.—60p; 12 x 3 in.—60p; 16 x 10 in.—£1-40; 16 x 6 in.—90p.  
**BLACK PLASTIC** construction box with brushed aluminium fascia size 6 1/2 x 4 1/2 x 2 1/2 in. Many other sizes.  
**BRIDGE RECTIFIER** 200V PIV 1/2 amp. 50p. Post £1-00.  
4 amp £1-50. 8 amp £2-50.  
**TOGGLE SWITCHES** SP 30p. DPST 40p. DPDT 50p.  
**MANY OTHER TOGGLES IN STOCK. Please enquire.**

**BSR 172 BUDGET SINGLE PLAYER** ideal for disco or small three-speed Hi-Fi system with stereo cartridge cueing device and bias compensator. Post £2 £20

**BSR STEREO CARTRIDGES** SC7 medium SC8 High output £2. Sonotone 9TA-HC £2-50. V.100 Magnetic £7.  
**WIRE-WOUND RESISTORS** 5 watt, 10 watt, 15 watt 15p.  
**CASSETTE MOTOR.** 6 volt £1-00.

## MAINS TRANSFORMERS

Post	Post
6V, 500mA.....£2.00	6-0-6V 100mA.....£1.80
12V, 100mA.....£1.30	8-0-8V 50mA.....£1.50
12V, 750A.....£1.75	10-0-10V 2A.....£3.00
10-0-10V 2A.....£3.00	10V, 30V, 40V, 2A.....£3.50
30V, 5 amp and	20V, 0-20V, 1A.....£3.00
17V-0-17V, 2A.....£4.00	2 of 18V, 2A.....£11.00
0.5, 10, 16V, 3A.....£2.50	1 1/2-0-1 1/2V, 2A.....£2.50
9V, 3 amp.....£3.50	1 1/2-0-1 1/2V, 2A.....£2.50
15-0-15V 2A.....£3.00	1 1/2-0-1 1/2V, 2A.....£2.50
35V, 2A.....£3.50	1 1/2-0-1 1/2V, 2A.....£2.50
30V, 1 1/2A.....£3.30	1 1/2-0-1 1/2V, 2A.....£2.50
20V, 40V, 60V, 1A.....£4.00	32-0-32V 6.5A.....£11.00

**Radio Component Specialists**  
337, WHITEHORSE ROAD  
CROYDON, SURREY, U.K. TEL: 01-684 1665  
Post 50p Minimum. Callers Welcome.  
Access-Barclay-Visa. Lists 20p. Closed Wed.

**COMMUNICATIONS RX** made by Murphy for R.N. covers 60/560Kc & 1.5 to 30Mc/s in 5 bands uses 13 type B7g valves, requires ext power supply, supplied tested with H/Bk see back P.W. or write for full spec £115.

**RADIOSONE UNITS** these measure Temp, Press & RH these are transmitted in the form of slow morse by a MCW Tx working on 27Mc/s require only 3v battery to operate, the signals are sent in turn by motor driven swt new unused. £12.50.

**RADIO SET** 128 small dry battery operated unit comprising Tx & Rx covers 2 to 8Mc/s tunable Rx & xtal Tx about 1 watt CW supplied with accessories in haversack with circ req 135 & 1.5v with circ. £27. Batteries £4.50.

**COAX CABLE** type UR57 HD 75 ohm 10mm OSD suitable HF Tx & Video use new £3.50 10 metres 25p metre over this.

**METER T.S.** contains meter 2.5Ma FSD scale 0 to 25. 3x yax swts 2p 8w, 3p 11w, 4x neon ind, 3x insul term, approx 20 close tol resistors etc in case size 8 x 12 x 4". £6.50.

**PAN & TILT HEADS** for use with CCTV cameras outdoor type two types both 240v full spec on list £35 & £55.

**MIKES** fist type by SGB Mill type 25 ohm with press to talk swt & short ext cord noise cancelling type £3.80.

**UHF Rx** Ass single chan xtal controlled with xtal for 243Mc/s uses 11 min valves in dull conversion circ with 100 ohm O/P new cond. £16.50.

**INDICATOR UNIT** with CRT 3WP1 3" green trace okay scope use 13 min valves inc case size 10 x 8 x 2 1/2" American surplus as int PU but 400c/s with circ. £30.

**DRIVE UNIT** with precision DC motor 0 to 60v with 24va DC field this as built in DC Tacho Gen O/P 0 to 60v the O/P drives 2 resolvers etc motor size 4 1/2" long 2 1/2" dia. £15.

**MAINS TRANS** 240v HT type Sec 450-400-350-0-350-400-450v at 380Ma Chk or 240Ma Cnd filter. £11.50.

**AUTO TYPE** 200/250v to 115v 560 watts fully enclosed £14.50.

**CCTV Cameras** Philips type PM1001 these are less outer weather proof case & lense but are complete with Vidicon & have int mains P.U. no gen on these but thought to be self contained with video O/P & req ext control unit, size 12 x 10 x 14" all transistor. £35.

Above prices include carriage post & VAT  
SAE with enquiry or 2 x 14p stamps for list 26.

# A.H. SUPPLIES

122, Handsworth Rd.,  
Sheffield S9 4AE.  
Phone: 444278 (0742).

## OSMABET LTD

We make transformers amongst other things.

**TRANSFORMERS TO ORDER**  
We have capacity for the supply of transformers to specification, either one off, or production runs, your enquiries please.

**LOW VOLTAGE TRANSFORMERS: Prim 240V ac.**  
6.3V 1.5A £3-00; 3A £4-15; 6A CT £7-90; 12V 1.5A £3-75; 3A CT £7-90; 6A CT £9-75; 15V 0.5A £3-00; 18V 1.5A CT £7-90; 24V 1.5A CT £7-90; 3A CT £9-75; 5A CT £18-00; 8A CT £29-25; 12A CT £37-50.

**MIDTIE RECTIFIER TRANSFORMERS: Prim 240V ac.**  
6.0-6V 1.5A or 9.0-9V 1A £3-40 each; 12-0-12V 1A or 20-0-20V 0.75A £4-15 each; 9-0-9V 0.3A or 12V-0-12V 0.25A or 20V-0-20V 0.15A £3-00 each.

**LT TRANSFORMERS TAPPED SEC: Prim 240V ac.**  
0-10-12-14-16-18V 2A £7-50; 4A £9-40; 0-12-15-20-24-30V 2A £8-25; 4A £12-00; 0-20-0-60V 1A £9-00; 2A £12-00; 0-40-50-60-80-100-110V 1A £12-00.

**AUTO & ISOLATION TRANSFORMERS 240/110V ac.**  
30 to 4000 watts, many types ex stock. Lists.

**MAINS TRANSFORMERS. SPECIAL OFFER. Prim 240V ac.**  
300-0-300V 80 Ma; 6.3V 1A CT; 6.3V 1A £5-50; 250-0-250V 60 Ma; 6.3V 1A £3-00; 9V 3A £2-50; 25V 300 Ma 90p; 15-0-15V 0.5A £2-50. 12V 4A £4-00.

**LOUDSPEAKERS**  
1 1/2", 1 3/4", 2 1/4", 2 1/2", 3", 3 1/2", 8Ω £1.50 each; 3" 35Ω 3p; 3" 8; 16; 80Ω £1.75 each; Goodman mid range 5" Hi Fi speaker 8Ω for 25W systems, £6-50; Do Tweeter 3p C/M 8Ω for 25W systems £2-50; F/Range Hi Fi speakers 4" 10W, 8Ω £3-50; 5" do 25W 8Ω £5-00.

**"INSTANT" BULK CASSETTE/TAPE ERASER**  
Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V ac. leaflet £8-00. Cassette/Tape Head Demagnetiser, £3-50.

**"BIB" Video Tape Eraser £20.**  
**EDGWISE LEVEL METER FSD 200/μA**  
Size 19 x 18 x 20mm 800Ω £1-50.

**CHARGING METERS 1 1/2 in diameter**  
2A or 3A £1-25 each; A or 10A £1-50 each.

**MINI FLEX CABLE**  
4 core, for Intercom, telephone, burglar alarm extensions, etc, white pvc, 10 metres £2, 100 metres £15.

**POWER SUPPLY, TWIN OUTPUT Prim 240V ac:**  
New, British manufacturer, smoothed d.c. output 20V, 1.5A, plus STABILISED output of 15V 100 Ma, plus further 12V ac 0.5A, complete with diagram, £4-50.

**O/P TRANSFORMERS FOR VALVE AMPLIFIERS**  
P.P. sec tapped 3-8-150 A-A 6K, 30V £17-50; A-A 3K 50V £26-00; 100W (EL31, KT88) etc £35-00.

**G.E.C. MANUAL OF POWER AMPLIFIERS**  
Covers valve amplifiers 30W to 400W £1-25.

**MULTIWAY SCREENED CABLE, PVC COVERED**  
36 way £1, 25/75p; 14/50p; 6/25p; 4/20p.

**CONDENSERS A 50Hz, 350-20V; 6/30V, £1-50.**  
Electrolytic 400 mfd 400V 75p; 2000/30V 30p; 2200/40V 40p; Paper tubular, W/E, 4/160V 6/160V 30p each.

**CARRIAGE EXTRA ON ALL ORDERS**  
**ALL PRICES INCLUDE V.A.T.**

Callers by appointment only. S.A.E. Enquiries, Lists.  
46, Kenilworth Road, Edgware, Middx.  
HA8 8YG. Tel: 01-958 9314

## MAINS INTERCOM



**NO BATTERIES NO WIRES ONLY**  
**£37.99**  
PER PAIR  
+ VAT £5-70  
+ P & P £2-15

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1/2 mile on the same mains phase. On/off switch. Volume control, with 'buzzer' call and light indicator. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. Also F.M. 2 channel "touch" model £55-95 a pair + VAT £8-40 + P & P £2-15.

## NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



**£18.95**  
+ VAT £2-85  
+ P & P £1-65

Latest transistorised Telephone Amplifier, with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording, model at £20-95 + VAT £3-15. P & P £1-65.

## DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged, and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock); mains power unit, cable (4 pairs) 50ft and wiring diagram. Price £95-95 + VAT £9-00 + P & P £2-25. Kit with two Telephones £69-95 + VAT £10-50 + P & P £2-45.  
10-day price refund guarantee on all items.

**WEST LONDON DIRECT SUPPLIES (PWS)**  
169 KENSINGTON HIGH STREET,  
LONDON, W8.



TTLS BY TEXAS		74221		74LS192		74C157		LINEAR I.C.s		MC1496		TRANSISTORS		TIP41C		2N3866		DIODES	
7400	11p	7497	180p	74225	140p	74C160	155p	AY1-0212	60p	MC3340	120p	AC127/8	22p	TIP42A	70p	2N3903/4	80p	BY127	12p
7401	12p	74100	130p	74259	250p	74C161	155p	AY1-1313	68p	MC3360	120p	AD161/2	45p	TIP295	70p	2N4036	65p	OA47	9p
7402	14p	74104	65p	74265	90p	74C162	155p	AY1-5050	212p	MC3380	120p	BC107/8	11p	TIP305	70p	2N4058/9	12p	OA81	15p
7403	14p	74105	65p	74278	290p	74LS220	100p	AY5-1224A	225p	MC3508	150p	BC109	11p	TIS43	34p	2N4060	12p	OA85	15p
7404	14p	74107	34p	74279	140p	74LS241	175p	AY5-1315	780p	NE531	75p	BSX19/20	20p	TIS93	30p	2N4061/2	18p	OA90	9p
7405	18p	74109	55p	74283	190p	74LS242	175p	AY5-1317	780p	NE543K	225p	BU105	190p	ZTX108	12p	2N4123/4	22p	OA95	9p
7406	32p	74110	55p	74284	400p	74LS243	175p	AY5-1320	320p	NE555	225p	BU108	190p	ZTX300	11p	2N4125/6	22p	OA200	9p
7407	32p	74111	70p	74285	400p	74LS244	180p	CA3046	70p	NE561B	425p	BU208	240p	ZTX500	15p	2N4289	20p	OA202	10p
7408	19p	74115	200p	74293	150p	74LS245	180p	CA3048	725p	NE562B	425p	BU406	145p	ZTX502	18p	2N4401/3	27p	1N914	4p
7409	19p	74119	130p	74294	200p	74LS246	180p	CA3080E	725p	NE565	130p	MJ2501	225p	ZTX504	30p	2N4427	90p	1N916	4p
7410	15p	74119	210p	74298	200p	74LS257	200p	CA3080E	725p	NE566	130p	MJ2595	35p	2N457A	250p	2N4471	60p	1N4148	4p
7411	24p	74120	110p	74365	150p	74LS258	200p	CA3089E	725p	NE567	175p	MJ3001	225p	2N5087	27p	1N4401/2	5p	1N4401/3	6p
7412	20p	74121	28p	74366	150p	74LS259	200p	CA3090A	Q375p	NE568	175p	MJ3040	225p	2N5172	27p	1N4405	6p	1N4406/7	7p
7413	30p	74122	48p	74367	150p	74LS267	200p	CA3100E	100p	NE569	175p	MJE340	65p	2N5179	27p	1N4501/3	14p	1N5404/7	19p
7414	50p	74123	88p	74368	150p	74LS268	200p	CA3100E	100p	NE570	175p	MJE355	100p	2N706A	20p	ZENERS			
7415	27p	74125	55p	74369	150p	74LS274	195p	CA3160E	75p	TBA641B11	225p	2N708A	20p	2N7519	83p	2-7V-33V			
7416	27p	74126	60p	74390	200p	81LS95	140p	FX209	75p	TBA800	90p	2N7520	83p	2N5245	40p	400 mW	9p		
7417	40p	74128	75p	74393	200p	81LS96	140p	ICL7106	925p	TBA810	90p	2N7521	83p	2N5246	55p	400 mW	9p		
7421	40p	74132	75p	74490	225p	81LS97	140p	ICL8038	25p	TBA820	90p	2N7522	83p	2N5457/8	40p	1 W	15p		
7422	22p	74136	90p	SERIES		81LS98	140p	LM301A	36p	TBA820	90p	2N7523	83p	2N5459	40p	SPECIAL			
7423	34p	74141	70p	74LS00	140p	81LS99	140p	LM311	190p	TC4181	175p	2N7524	83p	2N5460	40p	OFFERS			
7425	30p	74142	200p	74LS01	140p	81LS99	140p	LM312	190p	TC4500	200p	2N7525	83p	2N5465	44p	100+ 741			
7426	40p	74145	90p	74LS02	18p	81LS99	140p	LM324	70p	TD100A	325p	2N7526	83p	2N5466	40p	RC2	2N3055		
7427	34p	74147	190p	74LS04	14p	81LS99	140p	LM339	90p	TD1008	300p	2N7527	83p	2N5467	40p	RC3	2N3055		
7428	36p	74148	150p	74LS08	22p	81LS99	140p	LM349	95p	TD1022	600p	2N7528	83p	2N5468	40p	RC4	2N3055		
7430	17p	74150	100p	74LS10	29p	81LS99	140p	LM377	175p	XR2205	400p	2N7529	83p	2N5469	40p	RC5	2N3055		
7432	30p	74151	70p	74LS12	30p	81LS99	140p	LM380	75p	XR2207	400p	2N7530	83p	2N5470	40p	RC6	2N3055		
7433	40p	74153	70p	74LS14	75p	81LS99	140p	LM389AN	140p	XR2216	675p	2N7531	83p	2N5471	40p	RC7	2N3055		
7437	35p	74154	100p	74LS20	22p	81LS99	140p	LM399	130p	XR240	400p	2N7532	83p	2N5472	40p	RC8	2N3055		
7438	35p	74155	90p	74LS22	28p	81LS99	140p	LM399	130p	ZN414	30p	2N7533	83p	2N5473	40p	RC9	2N3055		
7440	17p	74156	90p	74LS27	38p	81LS99	140p	LM399	130p	ZN424E	135p	2N7534	83p	2N5474	40p	RC10	2N3055		
7441	70p	74157	70p	74LS30	22p	81LS99	140p	LM399	130p	ZN425E	135p	2N7535	83p	2N5475	40p	RC11	2N3055		
7442A	80p	74159	190p	74LS34	90p	81LS99	140p	LM399	130p	ZN103AE	200p	2N7536	83p	2N5476	40p	RC12	2N3055		
7443	112p	74160	100p	74LS35	30p	81LS99	140p	LM399	130p	95H90	800p	2N7537	83p	2N5477	40p	RC13	2N3055		
7444	112p	74161	100p	74LS37	50p	81LS99	140p	LM399	130p			2N7538	83p	2N5478	40p	RC14	2N3055		
7445	100p	74162	100p	74LS37A	40p	81LS99	140p	LM399	130p			2N7539	83p	2N5479	40p	RC15	2N3055		
7445A	93p	74163	100p	74LS37B	40p	81LS99	140p	LM399	130p			2N7540	83p	2N5480	40p	RC16	2N3055		
7447A	70p	74164	100p	74LS38	110p	81LS99	140p	LM399	130p			2N7541	83p	2N5481	40p	RC17	2N3055		
7448	80p	74165	130p	74LS38	100p	81LS99	140p	LM399	130p			2N7542	83p	2N5482	40p	RC18	2N3055		
7450	17p	74166	100p	74LS38	100p	81LS99	140p	LM399	130p			2N7543	83p	2N5483	40p	RC19	2N3055		
7451	17p	74167	200p	74LS39	60p	81LS99	140p	LM399	130p			2N7544	83p	2N5484	40p	RC20	2N3055		
7453	17p	74170	240p	74LS39	60p	81LS99	140p	LM399	130p			2N7545	83p	2N5485	40p	RC21	2N3055		
7454	17p	74172	720p	74LS107	45p	81LS99	140p	LM399	130p			2N7546	83p	2N5486	40p	RC22	2N3055		
7460	17p	74173	120p	74LS112	100p	81LS99	140p	LM399	130p			2N7547	83p	2N5487	40p	RC23	2N3055		
7470	30p	74174	93p	74LS12	75p	81LS99	140p	LM399	130p			2N7548	83p	2N5488	40p	RC24	2N3055		
7472	30p	74175	85p	74LS132	900p	81LS99	140p	LM399	130p			2N7549	83p	2N5489	40p	RC25	2N3055		
7473	34p	74176	90p	74LS133	80p	81LS99	140p	LM399	130p			2N7550	83p	2N5490	40p	RC26	2N3055		
7474	30p	74177	90p	74LS138	60p	81LS99	140p	LM399	130p			2N7551	83p	2N5491	40p	RC27	2N3055		
7475	30p	74178	160p	74LS139	60p	81LS99	140p	LM399	130p			2N7552	83p	2N5492	40p	RC28	2N3055		
7476	35p	74180	90p	74LS151	100p	81LS99	140p	LM399	130p			2N7553	83p	2N5493	40p	RC29	2N3055		
7480	50p	74181	200p	74LS153	60p	81LS99	140p	LM399	130p			2N7554	83p	2N5494	40p	RC30	2N3055		
7481	100p	74182	90p	74LS157	60p	81LS99	140p	LM399	130p			2N7555	83p	2N5495	40p	RC31	2N3055		
7482	84p	74184A	150p	74LS158	120p	81LS99	140p	LM399	130p			2N7556	83p	2N5496	40p	RC32	2N3055		
7483A	90p	74185	150p	74LS160	100p	81LS99	140p	LM399	130p			2N7557	83p	2N5497	40p	RC33	2N3055		
7484	100p	74186	800p	74LS161	100p	81LS99	140p	LM399	130p			2N7558	83p	2N5498	40p	RC34	2N3055		
7485	110p	74190	100p	74LS162	140p	81LS99	140p	LM399	130p			2N7559	83p	2N5499	40p	RC35	2N3055		
7486	34p	74191	100p	74LS163	100p	81LS99	140p	LM399	130p			2N7560	83p	2N5500	40p	RC36	2N3055		
7489	175p	74192	100p	74LS164	120p	81LS99	140p	LM399	130p			2N7561	83p	2N5501	40p	RC37	2N3055		
7490A	30p	74193	100p	74LS165	80p	81LS99	140p	LM399	130p			2N7562	83p	2N5502	40p	RC38	2N3055		
7491	38p	74194	100p	74LS173	110p	81LS99	140p	LM399	130p			2N7563	83p	2N5503	40p	RC39	2N3055		
7492A	45p	74195	95p	74LS174	110p	81LS99	140p	LM399	130p			2N7564	83p	2N5504	40p	RC40	2N3055		
7493A	36p	74196	95p	74LS175	110p	81LS99	140p	LM399	130p			2N7565	83p	2N5505	40p	RC41	2N3055		
7494	36p	74197	30p	74LS181	320p	81LS99	140p	LM399	130p			2N7566	83p	2N5506	40p	RC42	2N3055		
7495A	70p	74198	150p	74LS190	100p	81LS99	140p	LM399	130p			2N7567	83p	2N5507	40p	RC43	2N3055		
7496	85p	74199	150p	74LS191	100p	81LS99	140p	LM399	130p			2N7568	83p	2N5508	40p	RC44	2N		

# HIGH POWER MODULE KITS

## SPECIFICATIONS

Max. Output power ..... 125 watt RMS  
 Operating voltage (DC) ..... 50-80 Max.  
 Loads ..... 4-16 ohms  
 Frequency response Measured at 100 watts ..... 25Hz-20KHz  
 Sensitivity for 100 watts ..... 400mV @ 47K  
 Typical T.H.D. @ 50 watts 4 ohms load ..... 0.1%  
 Dimensions ..... 205 x 90 and 190 x 36mm.  
 The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

## ACCESSORIES

Suitable LS coupling electrolytic for 125W, model £1.00 plus 25p p&p.  
 Suitable LS coupling electrolytic for 200W, model £1.25 plus 25p p&p.  
 Suitable Mains Power Supply Unit for 125W, model £7.50 plus £3.15 p&p.  
 Suitable Twin Transformer Power Supply for 200W, model £13.95 plus £4.00 p&p.

## 125 WATT MODEL

**£10.50**  
 plus £1.15 p&p. (Illustrated)


## 200 WATT MODEL

**£14.95**  
 plus £1.15 p&p

**FREE!**
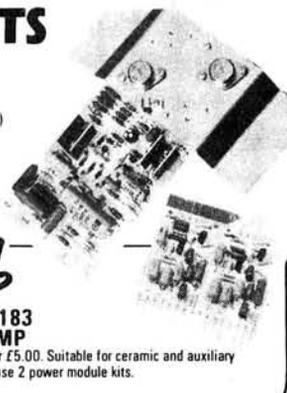
## MULLARD LP1183 STEREO PREAMP

Original listed price over £5.00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.




## STEREO DISCO PREAMPLIFIER

Matching other modules, suitable for twin deck mixing with P.F.L. output and Mic/Tape input. Ready built, ready to play with circuit diagram and application notes to suit our power module kits.



**£21.95**  
 plus £1.72 p&p

## 10+10 WATT STEREO HI-FI AMPLIFIER KIT

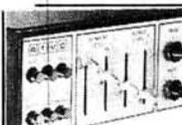

**£14.95**

● Featuring latest SGS/ATES/TOA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.  
 ● Mullard Stereo Preamplifier module plus £2.90 p&p  
 ● Attractive ready made black vinyl finish cabinet  
 ● Converts to a 20 Watt Disco amplifier  
 To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or turner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9" x 8 1/4" x 3 1/4" approx.


**SPECIFICATIONS** Suitable for 4 to 8 ohms speakers. Frequency response - 40Hz-20KHz; Input Sensitivity - P.U. 150mV Aux; 200mV Mic. 1.5mV; Tone controls - Bass ± 12db @ 60Hz; Treble ± 12db @ 10KHz; Distortion - 1% typically @ 4 watts; Mains supply - 220-250 volts 50Hz.

**BSR** chassis record deck with manual set down and return, complete with stereo ceramic cartridge; £8.50 plus £3.15 p&p when purchased with amplifier. Available separately £10.50 plus £3.15 p&p.

**8" SPEAKER KIT**, 2 8" approx. twin cone domestic use speakers £4.75 per pair plus £1.70 p&p when purchased with amplifier. Available separately £6.75 plus £1.70 p&p.
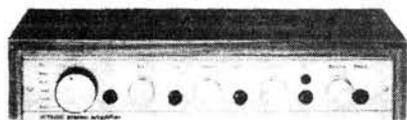
## STEREO MAGNETIC PRE-AMP CONVERSION KIT

All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. £2.00 when purchased with kit featured above. £4.00 separately inc. p&p.



## 30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/4" x 10" approx.

**READY TO PLAY £32.90** plus £3.80 p&p

## PRACTICAL ELECTRONICS CAR RADIO KIT


**£10.50** plus £2.00 p&p

### 2 WAVE BAND MW LW

- \*Easy to build "5 push button tuning"
- \*Modern styling design "All new unused components"
- \*6 watt output "Ready etched & punched P.C.B."
- \*Incorporates suppression circuits "Now with tape input socket"

All components and instructions to build the radio, you supply only the wire and solder. Pre-set tuning with five push button options, black illuminated tuning scale, matching control knobs, one combining on/off volume and tone-control, the other for manual tuning. The P.E. Traveller has a 6 watts output, neg ground and an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. Fits easily in or under dashboards.

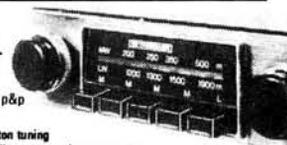Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete. **£1.95** p&p £1.15



323 EDGWARE ROAD, LONDON W2 Mail Order 21c HIGH ST. ACTON W3 6NG

ALL PRICES INCLUDE VAT AT 15%. All items subject to availability. Price correct at 1.3.81 and subject to change without notice. For further information send for instructions 20p plus stamped addressed envelope. Goods despatched to mainland and N. Ireland only. NOTE: Persons under 16 years not served without parent's authorisation. Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432 9.30am-5.30pm. Closed all day Thursday. ACTON: Mail Order only. No callers.

## NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5Ahr	SUB 'C' 1.2Ahr	'C' (HP11) 1.65Ahr	'C' (HP11) 2.0Ahr	'D' (HP2) 4.0Ahr	PP3 0.1Ahr
1-24	£0.85	£1.38	£1.69	£2.25	£2.97	£3.79
25-49	£0.82	£1.28	£1.58	£2.10	£2.77	
50-99	£0.80	£1.24	£1.52	£2.02	£2.67	
100 up	£0.70	£1.15	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are 'VENTED' devices suitable for fast charge.

**CHARGERS** - single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type **must** be specified for each required O/P when ordering.

SINGLE O/P CHARGER **£5.04**

DUAL O/P CHARGER **£5.72**

**TRANSFORMERS** - as used in chargers, 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections **£1.57** each.

Data and charging circuits free with orders over £10 otherwise 30p post. P&P 10% if order less than £10, 5% if order over £10. Prices **DO NOT INCLUDE VAT** and this should be added to the total order.

Cheques, P.O.'s Mail Order to:-  
**SOLID STATE SECURITY,**  
 Dept. (PW), Bradshaw Lane,  
 Parbold, Wigan, Lancs.  
 Telephone 02576-3018.

## A CAREER IN PRODUCT MARKETING?

YOUR KNOWLEDGE OF ELECTRONIC COMPONENTS COULD BE THE KEY TO A SECURE AND FINANCIALLY REWARDING CAREER IN ELECTRONIC COMPONENT DISTRIBUTION. PREFERRED AGE BETWEEN 20-26 YEARS.

We are the U.K.'s largest semiconductor distributor and we are looking for people with an interest and/or knowledge of up-to-date electronic components to become product marketing engineers at our head office, here in Slough.

The job develops commercial skills and offers prospects for very rapid advancement for people who are prepared to work hard and are ambitious.

We offer an attractive starting salary plus salary reviews twice-yearly plus a company car to the successful candidates.

Call or write to:  
**Julian Barnard or John Evans,**  
**Macro-Marketing Ltd., Burnham Lane, Slough, Berks.**  
**Burnham (06286) 61266**

# RADIATION DETECTORS

BE PREPARED WITH THIS DETECTOR

Recommended for General use. CIVIL DEFENCE ● FIRE SERVICES ● MEDICAL

VIEW THRU LENS

R

■ THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS.

■ UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.

■ PRECISION INSTRUMENT, METAL CASED, WEIGHT 2oz.

■ CONTAINS 3 LENSES. ■ RUGGED CONSTRUCTION.

■ MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.


Be prepared, buy whilst available.

**HENRY'S**

404 EDGWARE ROAD, LONDON W2 1ED

Standard model 0-5 or 0-50R ONLY

**£6.95** inc. VAT  
 Post & Packing 60p

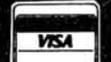



When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## Receivers and Components

**BOURNEMOUTH/BOSCOMBE.** Electronic components specialists for 33 years. Forresters (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

## BRAND NEW COMPONENTS BY RETURN

### HIGH STABILITY RESISTORS.

1W Carbon Film E12 Series 1R-10M. (E24 2R-6M2)—1p  
1W 1/2W & 1W Metal Film E12 Series 10R-2M2—2p

### CAPACITORS.

MULLARD Min. Ceramic E12 100V 2% 1.8pf. to 47pf.—3p  
2% 56pf. to 330pf.—4p. 10% 390pf. to 4700pf.—4p

### Plate Ceramic 50V Wkg. Vertical Mounting.

E12 22pf. to 1000pf. & E5 1K5pf. to 47Kpf.—2p  
Miniature Polyester 250V Wkg. Vertical Mounting.  
01 .015 .022 .033 .047 & 068 mfd.—4p  
0.1—5p. 0.15 & 0.22—6p. 0.33 & 0.47—8p  
0.68—11p. 1.0—15p. 1.5—20p. 2.2—22p

### ELECTROLYTIC. Wire Ended (Mfda/Volts).

0.47/50	5p	22/25	5p	100/25	7p	470/25	11p
1/50	5p	22/50	8p	100/50	8p	470/40	16p
22/50	5p	47/16	6p	220/16	8p	1000/15	15p
47/50	5p	47/25	6p	220/25	8p	1000/25	18p
10/50	5p	47/50	6p	220/50	10p	1000/40	35p
12/50	6p	100/16	7p	470/16	11p	2200/16	20p

### TANTALUM BEAD SUBMINIATURE ELECTROLYTICS.

0.1, 0.22, 0.47, 1.0, 2.2 + 35V & 4.7 + 6.3V—14p  
4.7/16V & 25V—15p. 10/16 & 22/16—20p. 10/25—25p  
10/35V. 22/16V. 47/16. 68/3V. 100/3V—30p  
15/25. 22/25. 47/10—35p. 47/16—80p. 220/16—£1.20  
Polystyrene 63V Wkg. E12 Series Long Axial Wires.  
10 pf. to 820 pf.—3p. 1000 pf. to 10,000pf.—4p

### TRANSISTORS.

BC107/8/9	10p	BC182L	8p	BF197	10p
BC147/8/9	10p	BC184L	8p	BFY50/51/52	18p
BC157/8/9	10p	BC212L	8p	BFX88	25p
BC547/8C/9C7p	BCY70	15p	2N2926	7p	
BC557C/8C/9C7p	BF194	10p	2N3055	50p	

8 Pin D.I.L. i.c.'s 741 Op/amp.—18p. 555 Timer.—24p  
Holders 8 pin.—9p. 14 Pin.—12p. 16 Pin.—14p. 28 Pin.—25p  
40 Pin.—30p.

### DIODES (p.i.v./amps).

75/25mA	1N4148	2p	1200/1A	BY127	10p
100/1A	1N4002	4p	400/3A	1N5404	14p
800/1A	1N4006	6p	60/1.5A	S1M1	5p
1000/1A	1N4007	7p	30/150mA	AAV32	12p

### ZENER DIODES.

E24 Series 3V3 to 33V 400mW.—8p. 1W—14p  
L.E.D.'s 3 mm. & 5 mm. Red—10p. Green, Yellow—14p  
Grommets for 3 mm.—11p. Holders for 5 mm.—2p  
FUSES. 20 mm. Glass. 100mA to 5A. O.B.—3p. A/S.—5p  
VOLTAGE REGULATORS+. 5V, 8V, 12V, 15V 100mA.—35p  
5V. 8V. 12V. 15V. 18V & 24V 0.5A.—60p. 1A.—65p  
PRESET POTENTIOMETERS  
50mW & 1W 100R to 1M0.—6p

## THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN.  
V.A.T. Inclusive Prices, Postage 15p  
(FREE over £5.00)

**TVDX.** Vhf-Uhf converter (upconverter). Ideal way to monitor sporadic E signals on Band 1 using UHF TV. £10.50 inc p.p. SAE data. lists. H. Cocks, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

# SMALL ADS

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £9.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

**PREWAR ONWARD VALVES, WIRELESS, SAE.** Sole Electronics, 37 Stanley Street, Ormskirk, Lancs.

## VALVES

Radio—T.V.—Industrial—Transmitting  
Projector Lamps and Semiconductors  
We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 50p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

### COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering,  
Sussex PO20 8BN  
West Wittering 2023 (STD Code 024366)

**BALLARD'S OF TUNBRIDGE WELLS** have moved to 54 Grosvenor Road, no lists. S.A.E. all enquiries phone Tunbridge Wells 31803.

## Southern Valve Co., 2nd Floor, 6 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked, SAE Lists, Cash with order, Same Day Postal Despatch, Telephone afternoons preferred. Not Thursday.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.  
Philip Bearman, 6 Potters Road, New Barnet, Herts.  
Tel: 01-449 1934/5 (1934 Recording Machine).  
Closed Thursday, Telephone for Shop Hours.

**WE REPAIR/RESTORE** valve type communication receivers with a one year guarantee. For a free quote telephone Corby 61697. Vintage British Radio Components Co., 22, Thurso Walk, Corby, Northants.

## £1 BARGAIN PACKS

All packs £1 each; any 12 for £10. Post 25p. All top-grade new components — no rubbish.

PC1 12 BC107	PC9 10 T03 sockets
PC2 14 BC108	PC10 15 0-1/35V tants
PC3 12 BC109	PC11 14 3mm red LEDs
PC4 3 2N3055	PC12 12 5mm red LEDs
PC5 7 BFY51	PC13 8 741
PC6 16 BC182	PC14 6 555
PC7 60 1N4148	PC15 15 12V zeners
PC8 25 1N4003	PC16 200 1k 1W 5% Rs

## PC ELECTRONICS,

5 Thornhill, Romsey Road  
Whiteparish, Salisbury, SP5 2SD

**CRYSTALS MADE TO ORDER** within 6 weeks. 4-105MHz, wire or pins. £3.90 each inclusive. HARTLEY CRYSTALS, Green Lane, Milford, Godalming, Surrey GU8 5BG.

**CRYSTALS** Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc: HC33/U: 1-0, £3.75. 2-5625 MHz. £3.50. HC18/U: 4-0, 5-0, 6-0, 7-0, 8-0, 9-0, 10-0, 10-7, 12-0, 15-0, 16-0, 18-0, 20-0, 38-6667 MHz, £3.35. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 8 weeks from £4-10. 2-3 week service available.  
**FILTERS** Your best source for 6 and 8 pole and monolithics for AM, CW, SSB, FM, on 455 kHz, 1-8, 9-0, 10-7, 21-4 MHz, etc.  
Prices inc. VAT and UK post. SAE lists.

## P. R. GOLLEDGE ELECTRONICS

G3EDW, Marriot, Somerset, TA16 5NS.  
Tel: 0460 73718

## V.L.F. DETECTOR KITS

"PROFESSIONAL AUTOMATIC METAL LOCATORS"

The printed circuit board and search head are ready built and aligned for easy assembly. Discrimination is by a rising tone for non-ferrous and falling tone for ferrous.

Complete Kit, inc. meter £27  
Discriminating pulse induction £48

**CDI SYSTEMS LTD., Storrington 4830**  
(Anytime)

## NOTICE TO READERS

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.*

## Aerials

**COPPER AERIAL WIRE** 14swg hard drawn 70' £5.34, 140' £8.84 inc. VAT. Postage £1.75 T.M.P. Electronics Supplies, Britannia Stores, Leeswood, Nr. Mold, N. Wales.

## ANTI-TVI TRAP DIPOLES

1981 Range: Shortwave Listener Aerials

Indoor models £14.50 & £27.50  
Outdoor models £30.00 & £36.00  
Lists 10 x 8 in 17p SAE, Aerial Guide 50p  
Indoor and Invisible Aerials £3.50

Callers Welcome Tel: 03986-215  
**G2DYM, Uplowman, Tiverton, Devon.**

**TONNA (F9FT) AMATEUR ANTENNAS** for 2m, 70cm, and 23cm bands, send 30p for full catalogue. Randam Electronics, (PW) 12 Conduit Road, Abingdon, Oxon OX14 1DB.

## TV-DX

FM-DX and all domestic reception requirements — Fringe or 'Local'. Aerials, Amplifiers, Boosters, Filters, Hardware — and the knowledge. Our new 1981 Catalogue costs 45p. SAE all enquiries, please.

## SOUTH WEST AERIAL SYSTEMS (PW)

10, Old Boundary Road, Shaftesbury, Dorset.  
Tel. (0747) 4370.

**ALMAG INDOOR T.V. AERIAL.** New design. All groups £2.50 + 50p p+p refundable. Murphy, 6, London Road, Dalkeith, Midlothian.

## Books and Publications

### Build your own

## P.A., GROUP & DISCO SPEAKERS

by R. F. C. Stephens  
Save money with this practical guide. Plans for 17 different designs, line source, i.B., Horn and Reflex types, for 8"-18" drive units. £3-95 post free (£8 overseas).

## THE INFRA-BASS LOUDSPEAKER

by G. Holliman  
(full constructional details for systems using 15", 12" and 10" drive units.) £2-95 post free (£6 overseas)

## THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens  
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for i.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2-20 post free (£5 overseas).

## VAN KAREN PUBLISHING

5 SWAN STREET, WILMSLOW, CHESHIRE

**WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS.** A genuine opportunity to success. LARGE PROFITS. You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. NO PREVIOUS KNOWLEDGE IS REQUIRED, as the manual covers in 13 chapters, where to obtain all the work you need, materials required, all instructions, rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. £4.50 inclusive of P&P. UK. CWO to: INDUSTRIAL SUPPLIES, 102 Parrswood Rd., Withington, Manchester 20. Dept. PW.

**Service Sheets**

**G.T. TECHNICAL INFORMATION SERVICE**  
76 CHURCH ST., LARKHALL, LANARKS.

**Any full size service sheet – still only £1 + s.a.e.**

Thousands of different sheets & manuals in stock (many of these only obtainable from us)

**Repair data your named T.V. £6 (with circuits £8)**

**Domestic Equipment Manual Vol. 1 £13.50 (updatings free for 1 year)**

S.A.E. for free newsletter, price lists, any quotation, bargain offers, unique T.V. publications. 2 big catalogues listing thousands of service sheets and manuals with £4 worth of vouchers – special offer £2 + large s.a.e.

**Phone: 0698 883334 anytime. Callers 4–6 pm weekdays, Sat. after 10.**

**30,000 SERVICE SHEETS IN STOCK**  
**COLOUR MANUALS ALSO AVAILABLE**

TV Monos, Radios £1.25 – Tuners £1.25 – Tape Recorders, Record Players, Transistors from £1.25 – Car Radios, Stereograms, Radiograms from £1.25 – Except Colour TV Circuits from £2. – State, if circuit will do, if sheets are not in stock. All TV sheets are full length 24 x 12", not in Bits & Pieces. All other Data full lengths. Free Fault Finding Chart or TV Catalogue with order. Crossed P.O.s returned, if sheets not in stock. S.A.E. please.

**C. CARANNA**  
71, Beaufort Park, London NW11 6BX  
01-458 4882 (Mail Order)

**For Sale**

"PRACTICAL WIRELESS", "Practical Television", "Hi-Fi Sound", "Amateur Tape Recording". Several hundred issues, all good condition, most as new. 1948-1976. S.A.E. details Box 85 or phone 0579-62804.

**NEW BACK ISSUES OF "PRACTICAL WIRELESS"** available 90p each, post free. Cheque or uncrossed P.O. returned if not in stock. **BELL'S TELEVISION SERVICE**, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

**EDDYSTONE MODEL 770R** Receiver. 1st class condition. £125 o.n.o. Telephone WARE 822135.

**YAESU MUSEN FRG-7 BRAND NEW!** Working abroad, must sell £155 o.n.o. Malcolm 01-898-0769.

**BEARCRAFT 220FB** Scanner. Purchased new 9.1.81. Cost £258. Will accept £200. Tel: EDWARDS. KIDDERMINSTER 700447.

**BACK COPIES** 1971-1980. Offers (not single copies). Chelmsford 62907.

**L.E.D. CHASING BADGE** 2 1/2" diameter runs from P.P.3. Kit £3.75, built £4.90. Phone 01-441 5032.

**Record Accessories**

**STYLE**, cartridges for Music Centres, etc. Free list no. 30 for S.a.e. includes Leads, Mikes, Phones etc. Felstead Electronics, Longley Lane, Gatley, Cheadle, Ches., SK8 4EE. Please note closed from March 19th to April 12th, 1981.

**SERVICE SHEETS** from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, TV etc., £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, W. Yorkshire. Tel. (0423) 55885.

**SERVICE SHEETS**, Radio, TV etc., 10,000 models. Catalogue 25p. plus S.A.E. with orders, enquiries, TELRAY, 5 Henderson Street, Preston PR1 7XP.

**Wanted**

**ELECTRONIC COMPONENTS PURCHASED.** All types considered – Must be new. Send detailed list – Offer by return – WALTONS, 55A Worcester Street, Wolverhampton.

**COLLECTOR** requires 1920/39 wireless crystal T.V. set also interesting wireless items of the period. Tel. Sevenoaks 62811.

**Courses**

**COURSES – RADIO AMATEURS EXAMINATION.** City & Guilds. Pass this important examination and obtain your G8 licence, with an RRC Home Study Course. For details of this and other courses (GCE, professional examinations etc) write or phone – **THE RAPID RESULTS COLLEGE**, DEPT. JX1, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service) or for prospectus requests ring 01-946 1102 (24hr Recordacall).

**Educational**

**CAREERS** in Marine Electronics, Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JS. Tel. 03917 79123.

**TECHNICAL TRAINING**

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. 277G Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

**COLOUR TV SERVICING**

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. 277G Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

**CITY & GUILDS EXAMS**

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs, Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. 277G Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

**Miscellaneous**

**KEEP ONE HANDY IN THE WORKSHOP**



The unique aerosol treatment for minor burns and scalds. From Boots and other Chemists.

**EX GOVT BATTERIES HT AND LT.** Send SAE for list. A. Messom, 22, Oakwood Close, Warsash, Southampton, Hants.

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer – now greatly improved and very much faster. Aerosol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass. Board approx. 1mm thick £1.70 sq. ft. Post/Packing 75p. **WHITE HOUSE ELECTRONICS**, P.O. BOX 19, Castle Drive, Penzance, Cornwall.

**ORDER FORM PLEASE WRITE IN BLOCK CAPITALS**

Please insert the advertisement below in the next available issue of Practical Wireless for ..... insertions

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

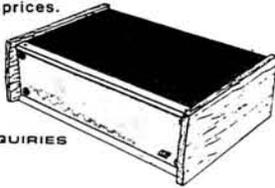

NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager  
**PRACTICAL WIRELESS,**  
GMG, Classified Advertisement Dept., Rm. 2337,  
King's Reach Tower, Stamford Street,  
London SE1 9LS Telephone 01-261 5846  
Rate  
28p per word, minimum 12 words. Box No. 60p extra.

If it's a case of making your project look good, then use one of ours.

Simply send a S.A.E. for Details and prices.




TRADE ENQUIRIES INVITED.

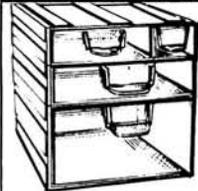H. M. ELECTRONICS P.W.

271a/275a Fulwood Road.  
Broomhill  
Sheffield S10 3BD

NEAT TIDY! HANDY!  
**INTERLOCKING PLASTIC STORAGE DRAWERS**



AS SUPPLIED TO POST OFFICE & GOVT DEPTS

Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (1D) (5in-2 1/2in-2 1/2in) £4.90 DOZEN  
DOUBLE UNITS (2D) (5in-4 1/2in-2 1/2in) £7.50 DOZEN  
TREBLE (3D) £7.50 for 8

DOUBLE TREBLE 2 drawers, in one outer case (6D2): £10.90 for 8

Extra large size (6D1) £8.50 for 8

Orders over £60, less 5% Packing/Postage/Carriage. Add £1.30 to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES

Please add 15% V.A.T. to total remittance.

All prices correct at time of going to press.

**FLAIRLINE SUPPLIES**

(PWS) 124 Cricklewood  
Broadway, London  
N.W.2. Tel: 01-450  
4844.

**KEEP IT CLEAN!** Large can of tape head cleaner £2.75. PCB lacquer £2.55. 14 pin 709 Op AMPS 30p. Prices include VAT. Postage 40p extra. Apex Enterprises, 329 Welford Road, Leicester.

**MORSE CODE TUITION AIDS**

Cassette A: 1-12 w.p.m. for amateur radio examination.  
Cassette B: 12-24 w.p.m. for professional examination preparation. Each Cassette are type C90.  
Morse Key and Buzzer unit for sending practice.  
Price each Cassette (including booklets) £4.75. Morse Key and Buzzer £4.75.  
Prices include postage etc. Overseas Airmail £1.50 extra.

**MHEL ELECTRONICS (Dept 2), 12 Longshore Way, Milton, Portsmouth PO4 8LS.**

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry and the Trade. BAZELLI. (Dept No. 25), St. Wilfrid's, Foundry Lane, Halton, Lancaster LA1 6LT.

**THE SCIENTIFIC WIRE COMPANY**

PO Box 30, London E.4  
Telephone 01 531 1588

**ENAMELLED COPPER WIRE**

SWG	1 lb	8 oz	4 oz	2 oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

**SILVER PLATED COPPER WIRE**

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

**TINNED COPPER WIRE**

14 to 30	3.85	2.36	1.34	0.90
----------	------	------	------	------

Prices include P&P, VAT and Wire Data.  
Orders under £2 please add 20p. SAE for list.  
Dealer enquiries welcome.  
Reg. Office 22, Coningsby Gardens.

**PSYCHOTRONIC GENERATORS**, gravity lasers, electrokinesis, electropotography, skinvision. SAE 4 x 9" Paralab, Downton, Wilts.

**RECHARGEABLE BATTERIES**

**TRADE ENQUIRIES WELCOME**  
FULL RANGE AVAILABLE. SAE FOR LISTS. £1.45 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call. Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764  
NEW SEALED LEAD RANGE AVAILABLE

**UK AIRCRAFT FREQUENCIES** list spot HF, VHF, UHF, frequencies, airports, air traffic control, etc. £1. UK Marine Frequencies list spot MF, HF, VHF, frequencies, coast stations, ship to shore, etc. £1. International Distress Frequencies chart 75p. PLH Electronics, 20 Vallis Road, Frome, Somerset BA11 3EH.

**LOSING DX?**

**RARE DX UNDER QRM?** DIG it OUT with a Tunable Audio Notch Filter, between your receiver and speaker. BOOST your DX/QRM ratio, 40dB notch, hear WEAK DX. £10.90.

**TIME WRONG?** MSF CLOCK is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, can expand to Years, Months and Milliseconds, auto GMT/BST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000KHz range, ABSOLUTE ACCURACY. £54.80.

**V.L.F.7 EXPLORE 10-150KHz Receiver £13.70.**  
**MISSING DX?** Get SPOT-ON with a Crystal calibrator, between your antenna and receiver, 1MHz, 100, 25KHz markers to vhf. £19.80.

**SIG. GEN.,** 10Hz-200KHz, logic and 0-1V sine and square wave outputs, harmonics for r. £12.80.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc. money back assurance so GET yours NOW.

**CAMBRIDGE KITS**

45 (PS) Old School Lane, Milton, Cambridge.

**C.W.A.S. ALARM.** Send now for the latest discount catalogue of Professional Burglar Alarm Equipment. C.W.A.S. Alarm, 11 Denbrook Walk, Bradford BD4 0QS, W. Yorks. Phone 0274 682674.

**PM COMPONENTS LTD**

VALVE & COMPONENT SPECIALISTS  
CONINGSBY HOUSE, WROTHAM RD.,  
MEOPHAM, KENT.

VALVES	PL508	1.48	6080	4.20	BC213L	0.09	BU108	1.69
DY86	0.55	PL509	2.30	6C214	0.09	BU205	1.30	
DY802	0.60	PL802	2.50	7025	1.50	BU208	1.39	
E180F	5.65	PY88	0.72	7360	7.50	BU208A	1.52	
EAB8C80	0.56	PV500A	1.35	7591	2.35	MJE340	0.40	
EBF89	0.70	PY801	0.65			OC71	0.22	
ECC81	0.55	QV02/6	10.50	AC175	0.22	R2008B	1.70	
ECC82	0.60	QV03-20A		AC176	0.22	BC337	1.70	
ECC83	0.60			BC461	0.30	R2540	2.48	
ECC85	0.60	QV06-40A	12.25	AC126	0.22	TIP29	0.40	
ECC88	0.65		13.95	AC127	0.22	TIP29C	0.42	
ECC807	1.30	QV03-12	3.50	AC128	0.28	TIP30C	0.43	
ECF80	0.65	TY2-125A	45.00	AC129	0.34	TIP31C	0.42	
ECF82	0.65		11.95	AC141K	0.22	TIP32C	0.42	
ECH81	0.58	UCH81	0.70	AC176K	0.31	TIP41C	0.45	
ECL82	0.58	UCL82	0.76	AC187	0.26	TIP42C	0.47	
ECL83	1.13	UL84	0.78	AC187K	0.28	TIP47	0.65	
ECL86	0.74	UY85	0.70	AC188	0.22	TIP2955	0.84	
EF37A	3.00	Z759	9.00	AD149	0.70	TIP3055	0.60	
EF80	0.48	2D21	1.60	AD161	0.39	TIS91	0.20	
EF86	0.70	2K25	10.00	AD161/2	1.04	2N3078	0.12	
EF89	0.65	4CX250B	26.60	AD162	0.39	2N3055	0.59	
EF91	1.22	5U4G	0.90	AF127	0.32	2N3702	0.12	
EF93	0.65	6CD6GA	4.00	AF139	0.42	2N3703	0.12	
EF94	0.65	6GK6	2.50	AF239	0.42	2N3704	0.12	
EF95	0.78	6J6	0.65	BC107	0.10	2N3705	0.12	
EF183	0.56	6JS6C	5.00	BC107B	0.10	2N3706	0.12	
EF184	0.56	6KD6	3.95	BC108	0.10	2N3708	0.12	
EL34	1.54	6L6GC	1.75	BC108C	0.10	2N5294	0.38	
EL84	0.60	6LD20	0.60	BC109B	0.10	2N5296	0.48	
EM84	0.65	6SN7GT	0.90	BC140	0.31	2N5298	0.38	
EZ80	0.48	6V6GT	0.90	BC141	0.25	1C-9	0.11	
EZ81	0.56	7S7	2.00	BC142	0.21	MC1307	1.00	
GZ32	0.76	12AT7	0.55	BC143	0.24	MC1350	1.00	
GZ33	1.85	12AU7	0.60	BC147	0.09	MC1495	3.00	
GZ34	2.00	12AX7	0.55	BC148	0.09	SN76003N	1.65	
KT61	3.50	12BA6	0.80	BC149	0.09	SN76013N	1.50	
KT66	4.85	12BE6	1.05	BC157	0.10	SN76013ND	1.50	
KT77	5.00	12BH7	0.95	BC158	0.09			
KT88	6.00	12HG7	3.50	BC159	0.09			
N78	8.90	30FL2	0.95	BC160	0.28			
OA2	0.78	85A2	1.20	BC170B	0.10			
PCF80	0.72	90C1	1.65	BC171	0.08			
PCF802	0.72	807	0.95	BC172	0.05			
PCF808	1.48	811A	9.00	BC173B	0.10			
PCL82	0.74	813	11.30	BC182	0.09			
PCL84	0.76	833A	47.85	BC183	0.09			
PCL86	0.76	866A	2.50	BC184LA	0.09			
PCL805	0.80	2050A	3.90	BC212	0.09			
PL200	1.13	5753	3.20	BC212L	0.09			
PL504	1.20	5814A	2.75	BC213	0.09			

Prices exclude VAT  
Please add 15%  
P&P 50p per order

Many other types available  
including vintage valves.  
**PHONE 0474 813225**



**Wilmslow Audio**

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ●
- BOWER & WILKINS ● CASTLE ● CELESTION ●
- CHARTWELL ● COLES ● DALESFORD ●
- DECCA ● EAGLE ● ELAC ● EMI ● FANE ●
- GAUSS ● GOODMAN'S ● HARBETH ●
- ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ●
- KEF ● LOWTHER ● MCKENZIE ● MISSION ●
- MONITOR AUDIO ● MOTOROLA ● PEERLESS ●
- RADFORD ● RAM ● ROGERS ● RICHARD ●
- ALLAN ● SEAS ● SHACKMAN ● TANGENT ●
- TANNOY ● VIDEOTONE ● WHARFEDALE ●

**WILMSLOW AUDIO LTD. (Dept. P.W.)**

35/39 CHURCH STREET, WILMSLOW,  
CHESHIRE SK9 1AS

Tel: 0625 529599

FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.

Tel: 0625 526213

(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

# TRANSFORMERS +VAT 15%

**30 VOLT RANGE (Split Sec)**  
Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref.	Amps	Price	P&P
112	5 1	2.90	1.00
79	1 2	3.93	1.00
3	2 4	6.35	1.20
20	3 6	7.39	1.44
21	4 8	8.79	1.60
51	5 10	10.86	1.60
117	6 12	12.29	1.72
88	8 16	16.45	1.96
89	10 20	18.98	1.84
90	12 24	21.09	O.A.
91	15 30	24.18	O.A.
92	20 40	32.40	O.A.

UK postage only  
Overseas extra  
Voltages stated are on full load  
**Continuous Ratings**

**60 VOLT RANGE (Split Sec)**  
Pri 120/240V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref.	Amps	Price	P&P
124	5 1	4.27	1.20
126	1 2	6.50	1.20
127	2 4	8.36	1.60
125	3 6	12.10	1.72
123	4 8	13.77	1.96
40	5 10	17.42	1.84
120	6 12	19.87	2.04
121	8 16	27.92	O.A.
122	10 20	32.51	O.A.
189	12 24	37.47	O.A.

**50 VOLT RANGE (Split Sec)** Pri 120/240V  
Sec 50V Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V.

Ref.	Amps	Price	P&P
102	5 1	3.75	1.20
103	1 2	4.57	1.20
104	2 4	7.88	1.44
105	3 6	9.42	1.60
106	4 8	12.82	1.72
107	6 12	16.37	1.84
118	8 16	22.29	2.20
119	10 20	27.48	O.A.
109	12 24	32.88	O.A.

**12 OR 24V OR 12-0-12V**  
Pri 220-240 volts

Ref.	12V	24V	Price	P&P
111	0 5	0 25	2-42	0.95
213	1 0	0 5	2-90	1.00
71	2 1	0 2	3-86	1.20
18	4	2	4-46	1.20
85	0 5	2 5	6-16	1.20
70	6	3	6-99	1.20
108	8	4	8-16	1.44
72	10	5	8-93	1.60
116	12	6	9-89	1.60
17	16	8	11-75	1.72
115	20	10	15-87	1.84
187	30	15	19-72	2.04
226	60	30	40-41	O.A.

**MAINS ISOLATORS (SCREENED)**  
Pri 0-120; 0-100-120V (120, 220, 240V) Sec 60-55-0-55-60 twice to give 55, 60, 110, 115, 120, 125, 175, 180, 220, 225, 230, 235, 240.

Ref.	VA	Price	P & F
107	20	4.84	1.20
149	60	7.37	1.20
154	100	8.38	1.44
151	200	12.28	1.72
152	250	14.61	2.04
154	500	22.52	2.20
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

\*Pri 0-240V Sec 115 or 240V  
State sec. volts required.

**SCREENED MINIATURES**

Ref.	mA	Volts	Price	P&P
238	200	3-0-3	2-83	0.50
212	1A, 1A	0-6-0-6	3-14	1.00
13	100	9-0-9	2-35	0.50
235	330	330 0-9-0-9	2-19	0.60
207	500	500 0-8-9-0-8-9	3-05	0.95
208	1A, 1A	0-8-9-0-8-9	3-88	1.20
236	200	200 0-15-0-15	2-19	0.60
214	300	300 0-20-0-20	3-08	1.00
221	700	700 20-12-0-12-20	3-75	1.00
206	1A, 1A	0-15-0-15	5-09	1.20
203	500	500 0-15-27	4-39	1.20
204	1A, 1A	0-15-27	6-84	1.20
239	50	12-0-12	2-88	0.50
234	500	6-0-6	2-19	0-44

**CASED AUTO TRANSFORMERS**  
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref.
20	6-55	0.95	56W
75	8-50	1.20	64W
150	11-00	1.44	4V
250	13-39	1.44	69W
500	20-13	2.04	67W
1000	30-67	2.20	84W
2000	54-97	O.A.	95W

Send 20p stamps for Catalogue. Prices correct 1/1/81.

**AUTO TRANSFORMERS**  
Voltages available: 105, 115, 190, 200, 210, 220, 230, 240, for step up and step down.

Ref.	VA	Price	P&P
113*	15	2.73	1.00
64	80	4.41	1.20
4	150	5.89	1.20
53	350	10.00	1.44
67	500	12.09	1.84
84	1000	20.64	2.20
93	1500	25.81	O.A.
95	2000	35.31	O.A.
73	3000	68.13	O.A.
80S	4000	94.55	O.A.
57S	5000	98.45	O.A.

\*0, 115, 220, 240.

**END OF LINE OFFERS**

87 - 110-240V 7.1A **£1.80** 70p  
M616 - 0-240V Screen **£1.90** 80p  
11 13-0-13 1A 21 12V 150mA **£1.50** £1.20

M708 - 6k to 3Ω match trans. 5 watt **90p** 95p  
M679 - 240V, 36V 1.6A **£3.00** 80p  
M865 - 100V Line to 4Ω 10 watt **£1.90** £1.00

M1020 - 0-240V 12-0-12V = 50mA **75p** 50p  
M1126 - 120/240V: 9-0-9V = 1A **£1.79** 60p  
M9 - 0, 12, 15, 20, 24, 30V 1A **£2.89** P&P £1.10

**15V CT Range (7.5V-0-7.5V)**

Ref.	mA	Price	P & P
171	500	2-30	0.60
172	1A	3-26	1.00
173	2A	3-95	1.00
174	3A	4-13	1.20
175	4A	6-30	1.20

**NEW RANGE TRANSFORMERS**  
Pri 120/240V

2 windings 0-36V-48V/36V-0-36V or 48V-0-48V 72V or 96V.

Amps	Ref.	Price	P&P
1.0	431	8.12	1.44
2.0	432	13.35	1.22
3.0	433	16.17	1.96
4.0	434	20.65	2.04
5.0	435	29.30	2.20
6.0	436	36.69	O.A.
8.0	437	40.03	O.A.

**Split Bobbin Type.** Pri 0-115, 0-115. Sec 0-12-15-20-24-30 to give 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24, 30V.

## OTHER PRODUCTS

**AVO TEST METERS**

AVO 8 MK5. Latest Model **£106.40**  
AVO 71 Electronic & TV Service **£43.10**  
AVO 73 **£58.60**  
AVO MMS minor **£36.90**  
AVO Wee Megger **£87.00**  
Megger 70143 500V **£87.00**  
AVO EM272 316K -Volts **£63.40**  
AVO DA116 L.C.D. Digital **£108.90**  
DA211 L.C.D. Digital **£67.00**  
DA212 L.C.D. Digital **£67.00**

All Avos Meggers and accessories available.  
**P&P £1.32 VAT 15%**

**SPECIAL OFFER**  
Multimeter 20KΩ B/V with combined audio/F test oscillator at 1 KHz and 465 KHz AC/DC to 1000 volts DC current to 500mA resistance to 1M. Size 160x97x40mm **£8-50 P & P £1.00 VAT 15%.**

**EDUCATIONAL METERS (Moving Coil)**  
0-10A, 0-15V, 0-30V. Freestanding large scale easily read meters with top screw terminals for quick connections. **£4.50** P&P 66p+VAT. Size 75x78mm scale.

**Burglar Alarm:** Ultra sonic 20ft range, no installation costs, key operated; built in siren (external can be added). Looks like a speaker. **£98.00** P&P £2.00 + VAT.

**Antex Soldering Irons** CCN240 15W & 25W **£4.58** each. Safety Stand **£1.75** P&P 52p each.

**P.W. Purbeck** oscilloscope transformer 250-0-250; 6-3V; 12-9V (author approved) **£9.42** £1-04

**Soldering Iron** - 25W to BS spec. **£1.75** P&P 30p+VAT  
**Precision De-Solder Pumps** - Spring loaded with quick action button release for one handed working. Large **£5.10** P&P 35p+VAT Small **£4.75** P&P 30p+VAT. Replacement tips Small **65p**+VAT. Large **86p**+VAT.

**Telephones** - Latest model, brand new, boxed, 2 tone grey **£11.50** P&P £1-20+VAT.

**Metal Oxide Resistors** - 1/2W 5% **£1.00** 100, 30p P&P+VAT. 390Ω/470Ω/510Ω/560Ω/620Ω/1K/1K1/1K2/1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K/110K/120/120K/130K/180K/220K/270K/300K Electro. Now available - Cable inc. Co-ax (BNC plugs) multi and single core. Also wide range of hand tools.

**PANEL METERS**

33mm x 43mm	82mm x 78mm
0 50mA <b>6-20</b>	0 50mA <b>6-70</b>
0 500mA <b>5-95</b>	0 500mA <b>6-70</b>
0 1mA <b>5-95</b>	0 1mA <b>6-70</b>
0 30V <b>5-95</b>	0 30V <b>6-70</b>


**MAINS ELIMINATORS**  
Plugs into 13A socket or 6, 9, 12V - 300mA **£4.60**, P&P 60p - VAT.

**BRIDGE RECTIFIERS**

100V 25A <b>£1.80</b>	500V
100V 50A <b>£2.20</b>	PM7A6
200V 2A <b>£0.52</b>	12A
200V 4A <b>£0.75</b>	<b>£3-75</b>
400V 1A <b>£0.25</b>	
400V 4A <b>£0.98</b>	P&P 20p
400V 6A <b>£1.44</b>	+VAT.

**UA315** - Budget Meter 20KΩ/V Ranges to 1000V 2.5A, AC/DC 500K Res., in steel case **£15.85** P&P £1.32+VAT.

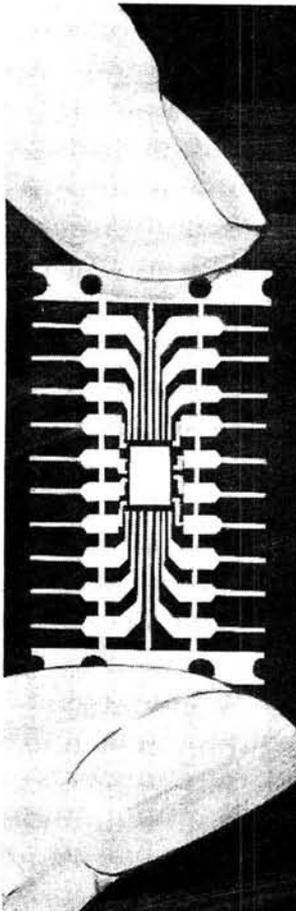**Barrie Electronics Ltd.**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST



# ELECTRONICS POCKET BOOK

Fourth Edition by E. A. Parr

Chips with everything! - Semiconductor technology has progressed at a startling rate and microprocessor chips have caused an information revolution that will be as significant as the Industrial Revolution proved to be. This fourth edition of *Electronics Pocket Book* is completely new and covers the latest developments in areas such as optoelectronics and microprocessors as well as the basic principles.

The book gives a non-mathematical presentation of the many topics in electronics and is designed to provide the designer, student or enthusiast with a readily accessible source of information.

186 x 120mm 360 pages **£5-60**  
0 408 00481 9 Illustrated Paperback

## Companion Books

by R. G. Hibberd

**Transistor Pocket Book**  
A comprehensive guide to the principles, characteristics and uses of the various types of transistors, practical circuits being given for the major transistor applications. Related devices, conductor diodes, thyristors, etc. are also covered.

186 x 120mm 312 pages  
0 408 00254 9  
Illustrated Paperback **£5-60**

**Integrated Circuit Pocket Book**  
The book covers both unipolar and bipolar i.c.s. and their applications in linear and digital circuits. It is intended primarily for technicians, students and all who are concerned with integrated circuits and their applications.

186 x 120mm 282 pages  
0 408 00255 7  
Illustrated Paperback **£5-60**

Available from your local Bookseiler or in case of difficulty from the Publisher.



### ORDER NOW

Cut out this coupon and return it to Patricia Davies Marketing Manager at the address below

- Please send me
- Electronics Pocket Book - 4th Edition (Parr) 0 408 00481 9 £5.60 Paperback
  - Transistor Pocket Book (Hibberd) 0 408 00254 9 £5.60 Paperback
  - Integrated Circuit Pocket Book (Hibberd) 0 408 00255 7 £5.60 Paperback

I enclose a cheque/PO for £ \_\_\_\_\_ in total payment

From \_\_\_\_\_

Address \_\_\_\_\_

(PW 5/81)

**Newnes Technical Books**  
Borough Green, Sevenoaks, Kent TN15 8PH



OFF THE SHELF  
DELIVERY ON THESE <sup>®</sup>



**BRAND NEW FROM FLUKE ...  
NOW AVAILABLE  
THE 8024A HAND HELD DMM**

This model incorporates all the features of the 8020A but in addition has:  
A peak hold switch which can be used in AC or DC for volts and current functions.  
Audible continuity testing and level detection for sensing logic levels.  
A temperature (°C) range for use with a thermocouple.

£149  
Carriage and Insurance £3

The following accessories are in stock now

Y8008 Touch and Hold Probe.....	£18.00
80K-40 High Voltage Probe.....	£45.00
81RF RF Probe to 100 MHZ.....	£32.00
80T-150C Temperature Probe (C).....	£55.00
801-600 Clamp-on AC Current Probe	£55.00



**HERE IT IS ...  
THE EVER POPULAR  
8022A HAND-HELD DMM**

Consider the following features:  
6 resistance ranges from 200 ohm-20 ohms.  
8 current ranges from 2mA-2A AC/DC.  
10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC.  
Pocket size - weighing only 370 gms.  
Full overload protection - will withstand 6kv spikes.  
Rugged construction - virtually indestructible.  
Meets tough military specs. - drop proof.  
In line, pushbutton operation for single-handed useage.  
Incorporates low power CMOS chip for low power consumption.  
All this plus a 2-year full guarantee.



**NOW only £75**  
Carriage and Insurance £3

**Soft carrying case  
£7 extra**


**Even more sophisticated the Fluke 8020A.**  
Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

**Price £125**

Carriage and Insurance £3.00

A handsome soft carrying case is included (this model only)

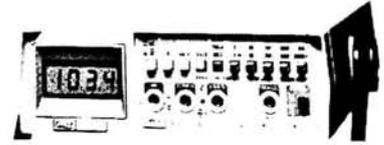OFF THE SHELF  
DELIVERY ON THESE <sup>®</sup>



**8010A AND 8012A  
BENCH MODEL D.M.M.s**

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.  
The 8010A and 8012A feature:  
10 voltage ranges from 200mv-1000v dc, 200mv-75v ac.  
3 conductance ranges from 2mS-200nS.  
6 resistance ranges from 200Ω-20mΩ - the 8012A has two additional resistance ranges 2Ω and 20Ω.  
10 current ranges from 200μA-2A AC/DC - the 8010A has two additional current ranges 10A AC and 10A DC.

**8010A £159 8012A £199**

Carriage and Insurance £3.

The 8010A is also available with two rechargeable Nicad size C batteries installed in option -01 a + £179.00.

**PLEASE ADD 15% VAT TO ALL ORDERS except where items marked "VAT Included". CALLERS WELCOME.**

We are open 9 a.m.-6 p.m. Monday-Saturdays. We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities.

**ELECTRO-TECH COMPONENTS LTD.**  
364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

**INDEX TO ADVERTISERS**

A.H. Supplies ... ..	84	Flairline Supplies ... ..	90	P.C. Electronics ... ..	88
A.J.H. Electronics ... ..	8	Garex Electronics ... ..	78	P.M. Components ... ..	90
Amateur Electronics ... ..	31	Gemini Electronic Components ... ..	12	Partridge Electronics ... ..	8
Amateur Radio Exchange ... ..	53, 66	Gemini Communications ... ..	72	Precision Petite ... ..	6
Ambit International ... ..	6, 7	Golledge Electronics PR ... ..	88	Progressive Radio ... ..	10
Amcomm Services ... ..	25	GT Technical Information Service ... ..	89	RST Valve Mail Order ... ..	94
Barrie Electronics ... ..	91	G2 Dym Aerials ... ..	88	Radio Component Specialists ... ..	84
Bedford Audio ... ..	78	H.M. Electronics ... ..	90	Radio Shack ... ..	32
Bib Hi-Fi Accessories Ltd ... ..	54	H.A.C. Shortwave ... ..	78	Rapid Results College ... ..	89
Bi-Pak ... ..	9	Harversons Surplus Co ... ..	10	R & TV Components ... ..	87
Birkett J ... ..	4	Henry's Radio ... ..	87	S.E.M. ... ..	5
Bowes Electronics C ... ..	4	Homebru Radio ... ..	78	Sandwell Plant Ltd ... ..	90
Bredhurst Electronics ... ..	Cover II	I.C.S. Intertext ... ..	11, 89	Science of Cambridge ... ..	82, 83
British Institute of Engineering Technology ... ..	86	I.L.P. Electronics Ltd ... ..	5, 14, 15	Scientific Wire Company ... ..	90
British National Radio & Electronics School ... ..	94	Intel ... ..	12	Solid State Security ... ..	87
Brookes B ... ..	66	Lee Electronics ... ..	26	Southern Valve ... ..	88
Bull J ... ..	13	Leeds Amateur Radio ... ..	16	South West Aerial Systems ... ..	88
Burneze ... ..	89	Lexton Harvey ... ..	65	South Midlands Communications ... ..	77
Cambridge Kits ... ..	90	Low Electronics ... ..	2, 3	Stephens-James Ltd ... ..	66
CDI Systems Ltd ... ..	88	Macro Marketing ... ..	87	Sunmit Electronics ... ..	10
Caranna C ... ..	89	Manor Supplies ... ..	8	Swanley Electronics ... ..	86
Catronics Ltd ... ..	11	Maplin Electronic Supplies ... ..	Cover IV	Technomatic Ltd ... ..	86
Chordgate Ltd ... ..	8	Marco Trading ... ..	7	Tempus ... ..	85
Chromatronics ... ..	7	Marshall A (London) Ltd ... ..	4	Thanet Electronics ... ..	95, 96, Cover III
Colomor (Electronics) Ltd ... ..	85	Mhel Electronics ... ..	90	V & F Smallcraft ... ..	6
Cox Radio (Sussex) Ltd ... ..	88	Microwave Modules ... ..	12	Van Karen Publishing ... ..	88
C.R. Supply Co ... ..	88	Modular Electronics ... ..	85	Waters & Stanton ... ..	71
Datong Electronics ... ..	66	Munro W ... ..	7	Watford Electronics ... ..	92
Electrovalve Ltd ... ..	11	Newnes Butterworths ... ..	91	Western Electronics ... ..	72
Electro-Tech Components Ltd ... ..	93	Northern Communications ... ..	72	West London Direct Supplies ... ..	84
Electronics Mail Order ... ..	86	Orion Scientific Products ... ..	6	Wilmslow Audio ... ..	90
		Osmabet ... ..	84	Wood & Douglas ... ..	94
				Wye Valley Electronics ... ..	10

# Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

## MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


## MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.
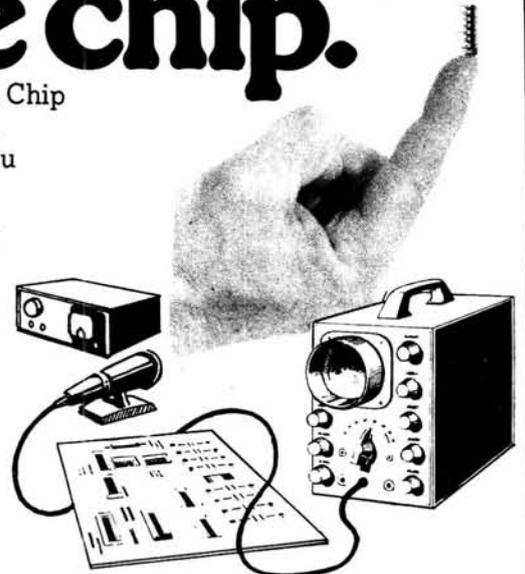
## MASTER THE REST

- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



Please send your **FREE** brochure without obligation to -

Name: \_\_\_\_\_

Address: \_\_\_\_\_

I am interested in -

PRACTICAL ELECTRONICS \_\_\_\_\_

COMPUTER TECHNOLOGY \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_  
(please state your interest)

BLOCK CAPS PLEASE PW/5/813

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL  
4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

# RST

VALVE MAIL ORDER CO.  
Climax House  
159 Fallsbrook Road, London SW16 6ED  
SPECIAL EXPRESS MAIL ORDER SERVICE

AZ31	1.10	EM87	1.50	PY81	0.84	6AN5	4.74	6Q7	2.20
CL33	2.00	EN91	3.50	PY82	0.80	6AN8A	3.45	6SA7	1.45
DY86/7	0.84	EY51	1.75	PY83	0.70	6A05	0.96	6SC7	1.50
EY80/8	0.84	EY88	0.84	PY88	0.88	6AR5	1.98	6SJ7	1.60
E88CC	3.36	EY500A	1.94	PY80A	1.80	6AS6	4.98	6SK7	1.30
E180F	8.40	EZ80	0.84	PY801	0.84	6AS7GA	6.75	6SL7GT	2.68
E810F	14.47	EZ81	0.84	QQV02-6	12.56	6AT6	0.85	6SN7GT	1.60
EABC80	1.20	GY501	2.75	QQV03-10	17.50	6AU5GT	4.32	6SS7	1.80
EB91	0.82	GZ32	1.25	6AW8A	3.39	6AU6	1.08	6SG7M	2.50
EBF80	0.50	GZ33	4.00	QQV03-20A	5.80	6B8	1.75	6X4	1.20
EBF89	0.85	GZ34	2.50	6B7	1.90	6BA5	1.00	6X5GT	0.85
EC91	7.56	GZ37	4.00	QQV06-40A	36.34	6BA7	5.12	7C5	2.95
ECC33	3.50	KT61	3.50	QV03-12	4.46	6BE6	1.08	7C6	2.25
ECC35	3.50	KT66	10.00	R18	4.25	6BH6	1.52	7S7	2.25
ECC81	0.88	KT77	8.00	R19	1.20	6BJ6	1.08	12A7E	1.20
ECC82	0.72	KT88	12.00	SP41	6.00	6BN6	1.65	12A7T	0.88
ECC83	0.88	N78	9.00	SP61	2.00	6BQ7A	3.72	12AU7	0.72
ECC85	1.20	OA2	1.92	SP61	2.00	6BR7	4.00	12AX7	0.88
ECC88	1.90	OB2	2.55	U19	13.75	6BR8	1.75	12BA6	2.19
ECC91	8.93	OC3	1.92	U25	1.16	6BR8	1.75	12BE6	2.43
ECF80	1.08	OD3	1.92	U26	1.44	6BS7	4.00	12BY7	2.70
ECH35E	2.00	PC86	1.40	U37	9.00	6BW6	1.52	12BY7A	2.70
ECH42	1.15	PC88	1.40	UABC80	1.25	6BW7	8.50	30P11/2	1.12
ECH81	1.20	PC92	1.28	UBF89	1.20	6BZ6	2.37	12HG7	4.17
ECL80	1.00	PC97	1.20	UCH42	1.20	6C4	0.88	30FL1/2	1.12
ECL82	1.00	PC900	1.20	UCH81	2.32	6C6	1.75	30P4	1.20
ECL83	1.50	PCF80	1.00	UCL82	1.04	6CB6A	2.49	30P19	1.20
ECL86	1.20	PCF82	1.00	UCL83	1.44	6CDB6A	5.07	30P113	1.80
EF37A	3.50	PCF86	1.60	UF89	1.44	6CH6	8.50	30P114	1.88
EF39	2.75	PCF801	1.60	UL41	2.50	6CL6	3.72	75C1	2.35
EF41	2.00	PCF802	1.90	UL84	1.20	6CV4	7.68	85A2	2.39
EF42	2.00	PCF805	1.60	UY41	1.25	6D6	1.75	90C1	2.44
EF50	1.50	PCF808	1.60	UY85	1.04	6D05	5.94	15082	3.02
EF54	5.00	PCH200	1.50	VR105/30	1.92	6EAB	2.94	150C2	1.92
EF55	2.50	PCL82	1.00	VR150/30	1.92	6E45	1.85	150C4	2.39
EF80	0.80	PCL83	2.00	Z759	16.80	6F8	1.75	5Y2B	27.50
EF86	1.52	PCL84	1.00	Z803U	7.90	6GK6	2.67	805	20.00
EF91	1.80	PCL85	1.08	2D21	3.50	6H6	1.50	807	3.75
EF92	5.81	PCL86	1.08	3B28	16.80	6HS6	3.77	811A	15.93
EF183	0.80	PCL905	1.08	4CX250B	27.50	6J5	2.52	812A	15.88
EF184	0.84	PD500	3.60	5R4Y2	2.00	6J7	3.50	813	74.67
EH90	1.40	PFL200	1.80	5U4G	1.52	6J8	1.50	866A	8.85
EL32	1.50	PL36	1.20	5V4G	1.52	6JB6A	4.56	872A	18.67
EL33	3.50	PL81	1.20	5V4G	1.52	6JS6C	5.58	931A	14.76
EL34	2.20	PL82	1.20	5Y3GT	0.85	6K4N	1.25	2050	6.96
EL36	1.60	PL83	1.20	5Z3	1.50	6K5GT	1.30	5763	3.75
EL81	2.50	PL84	1.08	5Z4GT	1.50	6K7	1.50	5814A	3.72
EL84	1.00	PL504	1.40	6/3DL2	1.56	6K8	1.75	5842	12.09
EL86	2.50	PL508	1.80	6A87	1.50	6KD6	6.36	6080	6.85
EL91	7.14	PL509	3.20	6AH6	4.71	6L6G	2.50	6146A	8.96
EL95	1.32	PL519	3.20	6AK5	3.60	6L6GC	2.50	6146B	7.06
EL360	8.50	PL802	2.96	6AL5	0.82	6L7	2.00	6883B	11.19
EM81	1.00	PY33	1.10	6AM6	1.80	6LQ6	6.72	6973	3.87
								7360	9.96
								7586	10.14
								7587	17.49

Open daily to callers: Mon-Fri 9 a.m.-5 p.m.  
Valves, Tubes and Transistors. Closed Saturday  
Terms C.W.O. only Tel. 01-677 2424-7.  
Quotations for any types not listed S.A.E.  
Post and packing 35p per order

Telex  
946708

Prices correct  
when going  
to press

## WOOD & DOUGLAS

With the winter evenings approaching, the constructional season for radio amateurs is about to begin. If you are undecided on your winter project perhaps you can find something in our range of over 30 kits and modules to suit you.

**70FM05TR** In case you missed October's review of this single channel FM transceiver for 70 cms here are a few details. The receiver sensitivity is typically 0.4µV and uses dual gate MOSFETS and a high quality crystal filter. The audio output drives an 8Ω speaker. The transmitter gives 500mW of RF and has a modulator on the pcb. Both boards use readily available crystals and measure a very compact 6" by less than 1 1/4".

Kit RX £38.50 Assembled RX £47.25  
TX £17.80 TX £25.95

**70MC06TR** When one channel is not enough then by adding this two pcb set you will have 6 channels on tx/rx. This includes a toneburst for repeaters and a scanner to ease monitoring.

Kit RX £18.60 Assembled RX £26.05  
TX £11.30 TX £18.10

**144SY25B** An FM synthesiser for 25KHz steps at 144-146MHz. The output frequencies are 5.5, 11, 22 or 45MHz on receive and 6, 12 or 24MHz on transmit. This will feed most commercial radio telephones and also the PW NIMBUS. So for the cost of ten crystal channels you get full band coverage, crystal controlled toneburst, repeater ±600KHz offset, out of lock inhibit and channel selection by channel number.

Kit £50.95 Assembled £69.70

**INTERESTED?** If you would like further details of these and our many other products then send a large SAE (please!) for the latest lists. The above prices include VAT at the current rate but please add 60p p&p on the total order. The prices include all items to make a working pcb module. We do not supply external hardware such as boxes or switches etc. This leaves you free to use the modules in whatever configuration you wish and yet have confidence that the electronics will perform well. We will gladly service any of our products providing it has been built as directed. We make a small charge for this facility depending on complexity. Kits when in stock are return of post otherwise 10-14 days. Assembled items 10-20 days.

9 HILLCREST, TADLEY  
BASINGSTOKE, HANTS RG26 6JB



# "NEW" IC24G



The Famous IC240 has finally been replaced. Many thousands are in use and its popularity was due in part to simplicity of operation, sensitivity and superb audio on TX and RX. The new IC24G has these and other features:—

Full 80 channels selected by easy to operate press button thumbwheel switches. Readout is by channel numbers. ie: S21 = 521, S16 = 516 and for the lower part of the band 144.5 = 420. This readout can be clearly seen in the brightest of sunlight. Duplex and reverse duplex is provided along with a crystal controlled tone call. Hi-10w and Lo-1w RF output is available, along with a 12½KHz upshift, should the new channel spacing be necessary. The old IC240 proved to be the most reliable rig we have ever sold – the IC24G, because it is so similar, looks like following the same pattern.

Remember, for mobile use a rig MUST be easy to operate to be safe.

## £199.00

# TONO

FOR ONLY  
**£640.00**  
INCL.



## Tono Theta 7000E A great computer on offer from Thanet

The new THETA 7000E means that every Amateur can enjoy the visual display of CW, RTTY and ASCII in both transmit and receive modes. Just connect the TONO to any TV set via the antenna terminals or to a page printer from the parallel port provided. Bring up your CW speed in receiving or sending by either watching receiver sent or from recorded cassettes. Connection to the transceiver is via the key, phone and mic sockets.


Some of the Outstanding Features  
COMMUNICATIONS COMPUTER THETA 0-7000E

UHF and Composite Video Output \* Printer interface \* Wide range of transmitting and receiving speeds – 10CW speeds + 8RTTY \* Built-in demodulator for high performance for 170, 425 and 820 Hz shift \* Crystal controlled modulator for ASFK – Hi or Lo tone \* Convenient ASCII key arrangement \* Large capacity display memory

– 2 pages 32chr x 16 lines split screen for Rx & Tx if required \* Automatic transmit/receive switch \* Anti-noise circuit \* Battery backed-up memory 7 channels of 64chrs \* Send function \* Buffer memory – 53 character type ahead, rub out function \* Simultaneous access of the memory – 53 character type ah LF (line feed) cancel function \* Cursor control function \* Word mode operation \* Automatic CR/LF (72, 60 or 80 chrs per line) \* Echo function

\* Word Wrap around function \* Transmit/receive in ASCII mode or RTTY \* CW identification function \* Mark and break (space and break) system \* Monitor circuit & CW practice function \* Variable CW weights \* Cross pattern checking output terminal \* Log computer output provided \* Test message function (Ry and QBF).

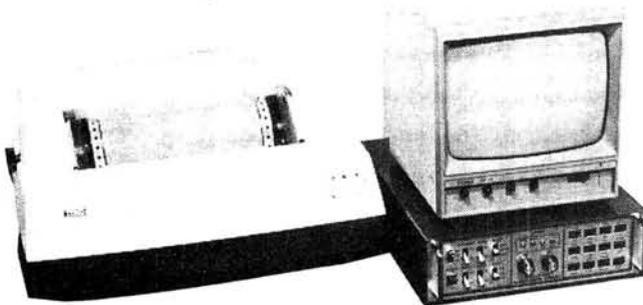Phone or write for the price list of accessories for this unit.



### RETAIL PRICE LIST

MODEL	DESCRIPTION	TOTAL inc VAT
Theta-7000E	Communications Computer (Send and Receive)	640.00
Theta-350	Communications Computer (Receive only)	325.00
CRT-12	12" Data Display Monitor (80 char/1 max, B/W) (Video bandwidth = 18 MHz)	121.00
CRT-12G	12" Data Display Monitor (80" char/1 max, Green) (Video bandwidth = 18 MHz)	131.00
CRT-10	10" Data Display Monitor (64 char/1 max, B/W) (Video bandwidth = 18 MHz)	109.50
HC-800	Impact Dot Printer (9 x 7 Dots, 132 char/1 max)	590.00
SK-7	Printer Socket for Theta-7000E	18.32
RX-144	144MHz RF Pre-Amplifier – mast head – very low noise complete with station controller	68.70
RX-430	430 MHz RF Pre-Amplifier – mast head – low noise complete with station controller	75.10
ASW-430	430 MHz SWR and Power Meter (200W max.)	49.50
ASW-180	1.8-160 MHz SWR and Power Meter (200W max.)	45.80

# Thanet for




# ICOM



# As Versatile As An Egg!

SO GET CRACKING WITH ONE

## IC-2E Handy Talky £159 INCL.

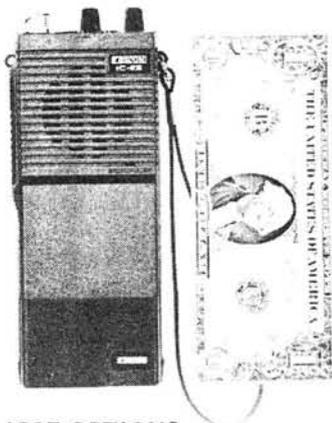

### CHECK THE FEATURES

FULLY SYNTHESIZED – covering 144-145.995 in 400 5kHz steps.  
 POWER OUTPUT – 1.5W with the 9V rechargeable battery pack as supplied – but lower or higher output available with the optional 6V or 12V packs.  
 BNC ANTENNA OUTPUT SOCKET – 50 ohms for connecting to another antenna or use the Rubber Duck supplied.


SEND/BATTERY INDICATOR – Lights during transmit, but when battery power falls below 6V it doesn't light indicating the need for a recharge.  
 FREQUENCY SELECTION – by thumbwheel switches, indicating the frequency.

+5kHz SWITCH – adds 5kHz to the indicated frequency.  
 DUPLEX SIMPLEX SWITCH – gives simplex or plus 600kHz or minus 600 kHz Transmit.  
 HI-LOW SWITCH – reduces power output from 1.5W to 150mW reducing battery drain.  
 EXTERNAL MICROPHONE JACK – If you do not wish to use the built-in electret condenser mic an optional microphone/speaker with PTT control can be used. Useful for pocket operation.  
 EXTERNAL SPEAKER JACK – for speaker or earphone.  
 This little beauty is supplied ready to go complete with nicad battery pack, charger, rubber duck.

### IC2E OPTIONS

BATTERY PACKS		CHARGERS ETC		
ICBP3	9 VOLT PACK (AS FITTED) REPLACEMENT	£15.50	IC-DC1 9 VOLT REGULATOR PACK	£7.50
ICBP2	(7.2 VOLT) (1 WATT)	£22.00	IC-CP1 CAR CHARGER LEAD WITH CIGAR PLUG	£2.75
ICBP4	EMPTY CASE (WILL TAKE SIX 'AA' SIZE NI-CADS)	£5.00	IC-BC25 CHARGER FOR BP3 AS SUPPLIED	£3.70
ICBP5	11 VOLT PACK (2-3 WATTS)	£30.50	IC-BC30 DESK CHARGER FOR ALL NI-CAD PACKS FAST FOR IC-BP5 + BP2 (1½ hours)	£34.00
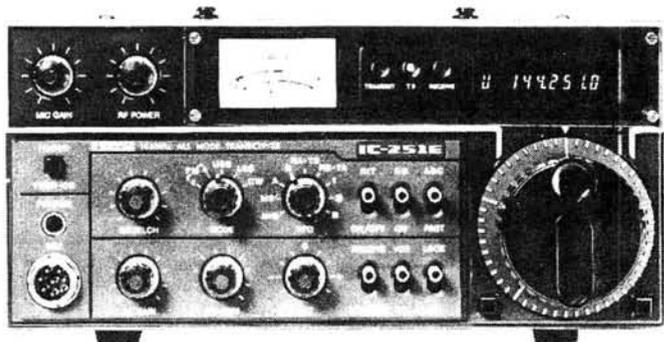
## THE LATEST 2M MULTIMODE BASE STATION the ICOM IC 251E



**Facilities Include:**  
 Fm, USB, LSB & CW.  
 Built in scanner and memories.  
 Bright Green Digital Readout.

**only  
£479 INCL.**

SEND FOR TECHNICAL DETAILS

### AGENTS (PHONE FIRST – evenings and weekends only)

Scotland Jack GM8GEC (031-665-2420)  
 North West Gordon G3LEQ (Knutsford (0565) 4040)



# IC-255E- An experts mobile choice

for only  
**£255**  
INCL.

NOW WITH  
IMPROVED  
FRONT-END



**25 Watts – 5 Memories – Scanning – 600kHz  
AND User Selectable Repeater Shift – Full Coverage in 5kHz or 25kHz Steps.**

- Crystal controlled Tone Burst
- Full band coverage – extendable to 148MHz if required
- Four digit LED display
- 25 Watts output or 1W low power
- A superb receiver using grounded gate FET front end
- Scanning over a user programmable range
- Memory scan
- Stop on empty or busy channels
- Tuning in 25kHz or 5kHz steps
- 5 Memories – retained while the power is connected to the rig
- Built-in 600kHz Repeater Shift
- Alternative programmable shift
- Reverse Repeater facilities
- RIT (± 3kHz for those off channel stations)
- Scan control from the microphone (optional mic available)
- Good loud audio
- Optically coupled tuning between control knob and CPU
- Multiway 24 pin socket on back for touchpad, computer, or external control
- Rugged modular PA (Guaranteed of course!)
- Mobile mount which can be padlocked
- Up-down scanning microphone available

**CAN YOU RESIST SUCH A TEMPTATION**

## Enjoy VHF mobile at it's best-IC-260E

The IC-260E offers such extras as full frequency read out, upper and lower sideband, and scanning as well as FM and CW. Thus, it makes an ideal base station, when used with a DC power supply, as well as a mobile. Now supplied with up-down scanning mic.



**£339** INCL.

**144MHz ALL-MODE TRANSCEIVER INCORPORATING A MICRO-COMPUTER** – CPU control with Icom's original programs provides various operating capabilities. No backlash dial controlled by Icom's unique photo-chopper circuit. Band edge detector and Endless System provides out-of-band protection. No variable capacitors or dial gear, giving problem-free use. The IC-260E provides FM, USB, LSB, CW coverage in the 144-146MHz frequency range. Thus the IC-260E can be used for mobile, DX, local calls and satellite work. Easily extendable to 144-148.

**MULTI PURPOSE SCANNING** – Memory scan allows you to monitor three different memory channels. Program Scan provides scanning between two programmed frequencies. Adjustable scanning speed. Auto-stop stops scanning when a signal is received, in all modes.

**DUAL VFO'S** – Two separate VFO's can be used either independently or together for simplex operation, and any desired frequency split in duplex operation.

**CONTINUOUS TUNING SYSTEM** – Icom's new continuous tuning system features an LED display that follows the tuning knob movement and provides an extremely accurate readout.

Frequencies are displayed in 7 LED digits representing 100MHz to 100Hz digits. When in Duplex and using the tuning-knob the two VFO's track together. Automatic recycling restarts tuning at the top of the band, i.e. 145.999.9 MHz when the dial goes below 144.000.0MHz. Recycling changes 145.999MHz to 144.000.0MHz as well. Quick tuning in 1kHz steps is available, and fine tuning in 100Hz steps in the FM mode, is provided for trouble-free QSO.

**OUTSTANDING PERFORMANCE** – The RF amplifier and first mixer circuits using MOS FET's and other circuits provide excellent Cross Modulation and Two Signal Selectivity characteristics. The IC-260E has excellent sensitivity demanded especially for mobile operation, high stability and with Crystal Filters having high shape factors and exceptional selectivity. The transmitter uses a balanced mixer in a single conversion system, a band pass filter and a high performance low pass filter. This system provides distortion free signals with a minimum spurious radiation level for an output of 10W or more.

**ADDITIONAL CIRCUITS** – The IC-260E has a built-in Noise Blanker, CW Break-in CW Monitor, APC and many other circuits for your convenience. The IC-260E has everything you need to really enjoy VHF operation, in an extremely compact rugged transceiver.

**Thanet for**



**ICOM**

143 RECVLVER RD.,  
BELTINGE,  
HERNE BAY, KENT.  
Tel: 02273/63859



