
DECEMBER 1960

W Inuth

Wireless World


ELECTRONICS Radio · Television

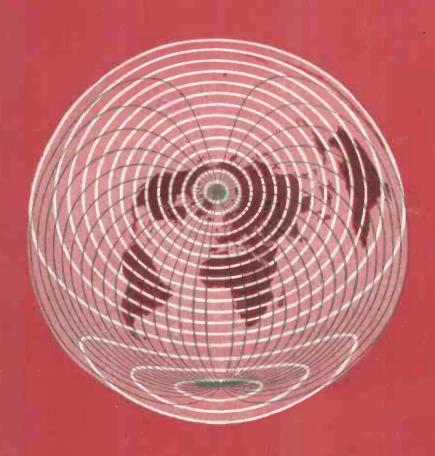

FIFTIETH YEAR OF PUBLICATION





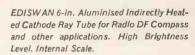

This Ediswan Radio DF Compass Tube ends parallax errors for the simple reason that the scale is printed on the inside face in actual contact with the phosphor screen. The scale pigment used is completely inert and unaffected by the electron beam. It is a dense black and does not fade after prolonged use.

Contrast is further improved by the aluminised screen which greatly intensifies the brilliance of the trace.

Anti-Dazzle Face All CRTs in this range have a flat face, treated on the outside with a robust process which eliminates distracting specular reflections and gives the impression of a soft matt ground glass finish.

Scale Applications The tube is available with an octantally corrected scale (31C1) or a uniformly graduated scale (31C2). Other versions can be supplied printed with selected portions of the Smith's Impedance Diagram.

Invitation We should welcome discussions with designers and manufacturers who have specific requirements involving special scales.

BRIEF SPECIFICATION					
Heater voltage (volts)	Vh	4-0 - 6-3			
Heater current (amps)	Ib.	0-72-0-8			
Anode voltage, rating (kV)	Va (max)	10-0			
Anode voltage, typical operation (kV)	Va (IIIax)	9·5			

EDISWAN

INDUSTRIAL VALVES & CATHODE RAY TUBES
Associated Electrical Industries Limited

Radio & Electronic Components Division
155 CHARING CROSS ROAD, LONDON W.C.2. TELEPHONE: GERrard 8660
[RC16/13

Wireless World

ELECTRONICS, RADIO, TELEVISION

DECEMBER 1960

Managing Editor:	579	Editorial Comment			
HUGH S. POCOCK, M.I.E.E.	580	Practical Aerial Measurements	By F. C. Judd		
	585	100-kc/s Crystal Marker	By F. G. Rayer		
Editor:	587	Amateurs' National Convention			
F. L. DEVEREUX, B.Sc.	588	Interkama 1960			
	590	World of Wireless			
	592	Personalities			
Assistant Editor:	594	News from Industry			
H. W. BARNARD	595	Ceramic Permanent Magnets By	J. W. Bunn and J. Harrison		
	599	Nodal Analysis—2	By F. R. B. Jones		
	605	Camera Remote Control	By G. W. H. Larkby		
	607	Short-wave Conditions			
	608	Letters to the Editor			
	613	Technical Notebook			
	615	Manufacturers' Products			
	617	Principles of Digital Computers—2	By D. S. Wilde		
	622	High-power Loudspeaker System	By Michael Lorant		
VOLUME 66 No 12.	623	Valve Noise	By " Cathode Ray"		
PRICE: TWO SHILLINGS	627	Elements of Electronic Circuits-20	By J. M. Peters		
TRICE. TWO SITELINGS	629	December Meetings			
FIFTIETH YEAR	630	Random Radiations	By " Diallist "		
OF PUBLICATION	632	Unbiased	By " Free Grid"		

Offices: Dorset House, Stamford Street, London, S.E.1

Please address to Editor, Advertisement Manager,
or Publisher, as appropriate

© Iliffe & Sons Ltd. 1960. Permission in writing from the Editor must first be obtained before letterpress or illustrations are reproduced from this journal. Brief abstracts or comments are allowed provided acknowledgment to the journal is given.


PUBLISHED MONTHLY (4th Monday of preceding month) by ILIFFE & SONS, LTD., Dorset House, Stamford Street, London, S.E.1.

Telephone: Waterloo 3333 (65 lines). Telegrams: "Ethaworld, Sedist, London." Annual Subscriptions. Home and Overseas, £1 15s. 0d.

Canada and U.S.A., \$5.00. Second-class mail privileges authorised at New York, N.Y. BRANCH OFFICES: BIRMINGHAM: King Edward House, New Street, 2. Telephone: Midland 7191. COVENTRY: 8-10, Corporation Street. Telephone: Coventry 25210. GLASGOW: 62, Buchanan Street, C.1. Telephone: Central 1265-6. MANCHESTER: 200, Deansgate, 3. Telephone: Blackfrlars 4412. NEW YORK

OFFICE: U.S.A.: 111, Broadway, 6. Telephone: Digby 9-1197.

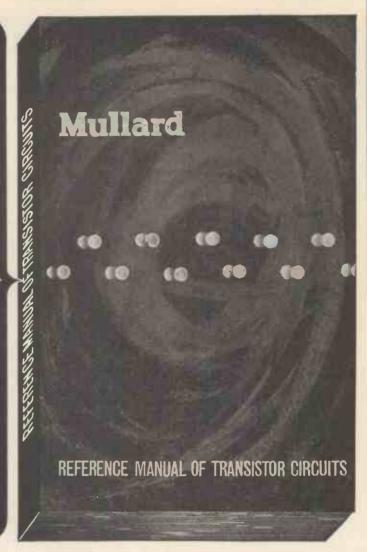over 30 new circuits are in the Mullard REFERENCE MANUAL OF TRANSISTOR CIRCUITS



This new manual of transistor circuitry has been prepared by Mullard engineers, as an up-to-date and readable volume which will be of use and interest to technicians, service engineers, junior designers and electronics students.

It has a page size of $8\frac{1}{2}^{11} \times 5\frac{1}{2}^{11}$ and describes more than 60 circuits—over 30 are made generally available for the first time—including both domestic and industrial applications.

308 PAGES · 241 DIAGRAMS · U.K. PRICE 12s. 6d.

PUBLISHED BY MULLARD LTD.

Get your copy of the Mullard "Reference Manual of Transistor Circuits" today from your radio dealer, or order direct from Mullard Ltd. (postage and packing 1s. Od. extra in U.K.).

MULLARD LIMITED . MULLARD HOUSE . TORRINGTON PLACE . LONDON . W.C.1.

Overseas readers should enquire of their local Mullard Agents.

Wireless World

Radiation at Very Low Frequencies

IN the present state of the art there are often times when the study and practice of radio may seem to be a hard grind. "Under the sun there's nothing new" and work consists of mastering known principles and taking advantage of improved materials to refine existing designs. But our subject is never dull for long. The field is wide, the labourers are many and new finds in old workings are constantly turning up to fire the imagination and shift the centres of interest. Hertz worked with centimetre waves, and electromagnetic waves at frequencies which would be audible if air were the propagating medium were widely used in the early days.

From these extremes of frequency interest tended later to converge to the intermediate values which gave greater bandwidth and traffic-handling capacity, lower capital cost for transmitters and greater running economy. In recent years the interest, as far as frequencies are concerned, has again become divergent; to centimetric waves for narrower beams and higher discrimination in radar, and to very long waves for special navigation and communication

systems and for geophysical research.

In passing, it is of interest to recall the criticism which was levelled at the Post Office for continuing in their policy of building a high-power long-wave station at Rugby, when the new short-wave beam stations were showing every promise of making it obsolete. A similar situation is now arising between the fact of the Commonwealth telecommunications project and the promise of satellite communications.

Although the bulk of the world's communication traffic took to the new short-wave bypass, we have reason to be grateful, now more than ever before, that the Post Office, and authorities in other countries, did not allow the old low-frequency roads to fall into disrepair. The services of Rugby GBR (16kc/s) and Criggion GBZ (19.6kc/s) are much in demand all over the world not only for communication but for time and frequency comparison and, because of their wide dissemination and high stability, for navigational purposes. New stations, working on similar frequencies with powers of IMW, have been built in the U.S. for communication with

At "extremely low," frequencies1 there is worldwide interest and much international co-operation in the investigation of electromagnetic phenomena of terrestrial and extra-terrestrial origin. Lightning flashes produce transients with e.l.f. components of considerable magnitude, and correlation has been established with perturbations of the geomagnetic field. But by far the most interesting development in the e.l.f. and v.l.f. ranges has, in our opinion, been the investigation of "whistlers," which can be heard under favourable conditions and in high latitudes by connecting an aerial directly to the input of an audio amplifier. These have been

shown to have their origin in lightning flashes and to owe their peculiar sound to the different rates of propagation with frequency of the components of the original pulse waveform in following the lines of force of the earth's field through a dispersive medium. This gave the first intimation, later confirmed by rocket exploration, of the existence of belts of ionized particles extending to heights of

many earth radii.

While much new knowledge has been collected by patient observation and analysis of natural phenomena, more rapid progress would be made if controlled impulses and burst of radiation at specific frequencies could be launched, particularly from the polar regions. But the resources of conventional radio engineering find themselves hard pressed in trying to emulate lightning as far as power and radiator dimensions are concerned. Many ingenious suggestions have been put forward, for example, that v.l.f. signals might be superimposed on the electricity grid system. Unfortunately, grid systems are seldom to be found where the scientists want them. An experiment, reported on page 614 of this issue, makes use of a 10,000 ft. aerial wire suspended from a helicopter in what must surely be the biggest mobile-marine transmitting station ever devised. Even so, the aerial is no longer than that used at the Marconi transatlantic receiving station at Towyn in the early 1920s.

To our way of thinking, the most ingenious suggestion put forward so far is that due to M. G. Morgan², of the Thayer School of Engineering, Dartmouth College, Hanover, New Hampshire, U.S.A. This is to use the whole of Deception Island in the South Shetland Islands as a slot aerial, using the surrounding sea as the ground plane conductor. The island is the rim of a submerged volcano and has one gap leading to an inner lagoon. An expedition of the Falkland Islands Dependencies Survey is now on its way with equipment to check that the rock formation is a good enough insulator and to measure the impedance of the "slot," which has a calculated resonant frequency of 5kc/s. If the answers are favourable it is hoped to try to energize the "aerial" at points opposite to the lagoon entrance by current entering the sea on each side of the saddle, and thus to launch waves upwards

into space.

We wish every success to this enterprise, which has shown that the older arts of radio are still as capable of stirring the pulse as those of its younger offspring, electronics.

¹ Designated as the range from 1c/s to 3kc/s at the January 1960 Conference on Propagation of E.L.F. Electromagnetic Waves, Boulder, Colorado, U.S.A., and reported in the National Bureau of Standards Technical News Bulletin, Vol. 44, No. 5, May 1960.

² I.R.E. Trans. on Antennas and Propagation, Sept. 1960.

INVESTIGATING PERFORMANCE OF AERIALS BY MEANS OF SCALE MODELS

CALCULATING the radiating and/or pick-up properties of any aerial is a tedious process and does not take into account its environment once in situ. For this reason alone many engineers and organizations who specialize in aerials use scale models operated at very high frequencies for determining performance under working conditions. Practical experiments of this nature are fascinating to say the least, and may be carried out by anyone with a few simple items of equipment plus a little knowledge of basic principles of radiation.

The aerial "table" described in this article was constructed mainly for investigating the performance of aerials used for amateur radio transmitting and for live demonstrations during lectures.

For this article the reader is asked to assume that all reference to the performance of an aerial is in the radiating sense. The characteristics and performance of an aerial during reception are for all practical purposes reciprocal and identical. It is easier to think and talk in terms of radiation.

In general the object of the aerial designer is to produce standing waves on the radiating elements of an aerial so that radiation takes place in a known manner and where required. For example, resonance may be obtained with a quarter wavelength of wire if one end is on a theoretically infinite conducting sheet (e.g. copper) placed perpendicular to the wire. The reflection from the sheet then produces an image of the quarter-wave wire, as, say, a pencil standing on a mirror appears to be carried on into the mirror. The system resonates as freely as a half-wave length of wire but with halved radiation resistance.

The diagram of Fig. 1 shows how reflection from the earth takes place and how the angle of reflection

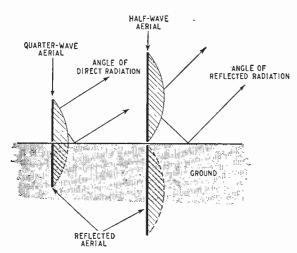


Fig. 1. Direct and reflected radiation from aerials adjacent to earth.

is determined by either the height or the length of the aerial above ground. As the height or length is increased the relative phase angle between the direct and reflected wave will vary, thus modifying the strength of radiation in different directions.

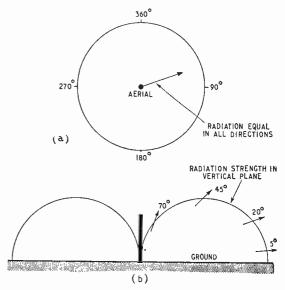


Fig. 2. Radiation field from vertical aerial; (a) in horizontal plane, (b) in vertical plane.

Radiation from any aerial system is determined by resonant length, or by the physical assembly of a number of radiating and/or reflecting and directing elements (beam aerials). For example, the radiation from a single vertical $\lambda/4$ radiating element is uniform for all directions around the aerial (horizontal plane). In the vertical plane the field strength varies as the angle from the ground increases, being maximum at ground level and zero in the true vertical direction as shown in Fig. 2.

In free space, clear of any conducting or semiconducting obstacles, an aerial generally behaves according to accepted theories, but in the presence of other conductors and earth, the true radiation pattern may become very much modified. Since the height of an aerial above ground will never be very great (compared with an imaginery position in free space) the earth and its conductivity always play a great part in forming the actual radiation pattern. The term "earth" or "ground" applies also to aerials on aircraft since the body of an aircraft may be regarded as "earth" and usually has considerable effect on radiation.

The Theory of Similar Aerials.—The difficulties involved in plotting, other than the ground radiation


^{*} Amateur Radio Station G2BCX

field of aerials operating in the lower portion of the radio frequency spectrum, make it almost impracticable to attack the problem. It becomes necessary, therefore, to devise some other system, other than calculation, for investigating true radiation patterns. The use of scale models is not an entirely new idea, for the method was used before the war by the B.B.C. and others, although the scale reduction of the models was limited owing to lack of suitable sources of r.f. power for very high frequencies'.

From a practical point of view a half-wavelength aerial resonant at say 10 centimetres (3,000Mc/s) would behave in the same way as an aerial of similar type operating at 10 metres (30Mc/s) or even at 100 metres (3Mc/s), provided all other conditions were maintained, i.e. height above ground, conductivity of ground, dielectric constants and/or conductivity of materials used for the manufacture of the aerial and the effects of surrounding objects. Most of these can be simulated in scale models and the results of small differences ignored, although at certain very high frequencies the construction of an accurate model does become more difficult.

The problem of suitable methods of feeding the aerial also arises and at frequencies above about 200Mc/s the radiation field, particularly from balanced aerials such as the dipole, may become asymmetrical owing to inaccurate matching of aerial to feed system. (Some asymmetry may be noticed in the dipole pattern of Fig. 9.)

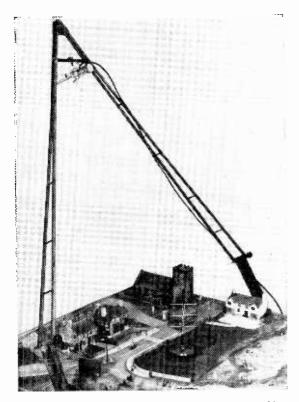The method does, however, provide a means of establishing the pattern of the radiation strength in



The 3,000-Mc/s model aerial testing table (scale 4mm/ft) used by the author. The aerial shown in lower centre is a scaled-down 6-element, stacked array for a normal frequency of 30Mc/s.

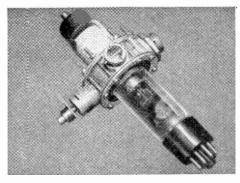


Fig. 4. Typical 3,000-Mc/s Klystron oscillator, the Type CV67.

both the vertical and horizontal planes, as well as the effect of surrounding buildings and similar structures. Measurement of gain in beam aerials may be carried out and the effect of physical modifications rapidly ascertained. Many commercial concerns use the scale model method for determining radiation patterns, etc., the U.S.A. Bureau of Standards for example have a "Model Antenna Testing Range many aircraft companies use scale model aerials in conjunction with model aircraft to the same scale^{2, 3}.

Suitable Frequencies.—The writer's earliest experiments were carried out with an operating (model) frequency of 144Mc/s and many types of aerials commonly used for the radio amateur bands of 1.8, 3.5, 7 and 14Mc/s were scaled down for measurement of gain and radiation. More than 30 model aerials were constructed, most of the tests being carried out over normal earth. Attempts were later made to construct a "table" which could be used indoors but even at a frequency of 800Mc/s reflection from walls, etc., was found to be troublesome and imposed considerable restriction on accuracy.

A Practical 3,000-Mc/s Model Aerial Table.—To avoid inaccuracies due to unwanted reflection and to allow time for the complete formation of the electric field from a radiating aerial, the field strength meter and its aerial should be at least five wavelengths distant from a radiating aerial under test. higher the frequency the shorter becomes the free space wavelength and at 3,000Mc/s it becomes possible to construct equipment suitable for indoor demonstration, as well as for reliable estimation of field patterns.

The aerial table shown in Fig. 3 was constructed in three sections to form a total area 4ft 6in square. Plywood, backed with thin aluminium sheet was used for this and forms an effective ground plane or artificial earth. The table contains a section of a typical residential area modelled at 4mm/ft and is constructed mainly from materials that simulate as near as possible those normally used for full-size

structures.

Mounted directly under the centre of the table is a 3,000-Mc/s Klystron oscillator (CV67), complete with power supplies and modulator, which provides r.f. power for the model aerials, the r.f. output being taken to an aerial via a specially designed rotating coupling flush with the top of the table. The Klystron and its associated assembly can be turned through 360° by means of a slow-

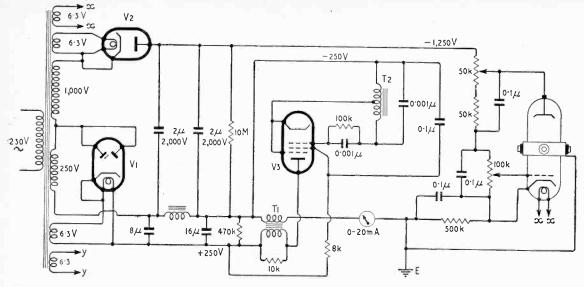


Fig. 5. Klystron oscillator, power supply and modulator used by the author. VI = 250V rectifier; V2 = 1,250V rectifier; V3 = EF91; Klystron (see text); T1 = modulation transformer, ratio 1 to 1; T2 = tapped a.f. transformer.

motion drive and hand wheel located at the side of the table.

Klystron oscillators, such as the CV67 shown in the photograph of Fig. 4, may be obtained from Government surplus supply sources. Other Klystrons suitable for this work include the CV36 (2,850Mc/s), CV116 (3,540Mc/s), CV23 (3,300Mc/s) and the CV238 (3,050Mc/s). The latter two are low voltage types and require 250 volts between anode and cathode and 100 to 200 volts for grid bias and the target anode. The others operate with up to 1,500 volts on the target anode and take an average current of 5m/A. These Klystrons have fine and coarse tuning adjustment plugs fitted around the resonant cavity and provide an r.f. output of 100 to 150 milliwatts.

The Klystron oscillator and modulator circuit used by the writer is shown as Fig. 5. Component values may have to be modified slightly, although those given should be close enough to enable the circuit to function reasonably efficiently.

On either side of the table and on a line through the axis of the rotating coupling, two supports carry an inverted "V" frame. This is based on an arrangement used by the U.S.A. Bureau of Standards, which permits the field-strength meter and its associated receiving aerial, which are mounted at the apex of the frame, to move through an arc of 180°. This arc extends from ground level on one side of the aerial to ground level on the other.

The frame may be locked in any position so

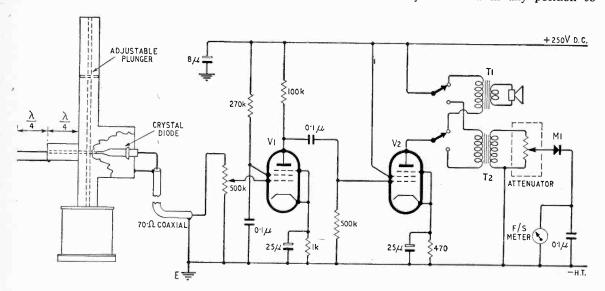


Fig. 6. Receiver and field-strength meter used for aerial measurements at 3,000Mc/s. VI = EF91, V2 = EL91; T1 = loud-speaker transformer; T2 = 1 to 1 ratio a.f. transformer; M1 meter rectifier or diode.

that a horizontal radiation pattern can be plotted for any vertical angle with respect to earth.


The Receiver and Field Strength Meter.—The 3,000-Mc/s receiver consists of a tunable resonant cavity and a crystal diode from which the demodulated signal is fed via an audio amplifier to a variable attenuator. Various surplus 3,000-Mc/s radar tuning units may be adapted for this purpose and 120 used in conjunction with an amplifier circuit similar to that of Fig. 6. The audio signal level is indicated by a sensitive meter calibrated in 15 equal divisions, this being equivalent to the ruling of Chartwell Polar Co-ordinate paper, Sheet No. 4001. The attenuator is directly calibrated in decibels. The Klystron modulating signal is about 1,000c/s so that a loud-speaker may be connected in place of the meter for practical demonstration purposes.

As an alternative to the Klystron for a source of r.f. power there are many conventional valves that will oscillate at a 1,000Mc/s or more. If lower frequencies are used, however, the model aerials will be correspondingly larger but still suitable for openair operations. Only a few milliwatts are needed to drive the aerials and ensure full-scale meter readings, so that radiation will be quickly absorbed and will not travel very far if experiments have to

be made out of doors.

Plotting Radiation Patterns.—Clear surroundings are very necessary and the equipment should be carefully sited several wavelengths (at operating frequency) away from other conductors such as electrical wiring, metal window frames and pipes. Gain measurements may be made with respect to a "standard dipole," the radiated power from this being taken as a reference and regarded as 0dB. The importance of clear surroundings will be appreciated when attempts are made to simulate by means of models the conditions imposed by the presence of buildings and other structures. Two-dimensional "solid" patterns of a radiation field are more interesting than the conventional polar diagrams, especially for demonstration and from these a very clear conception of radiation directivity may be obtained. These two-dimensional shapes are produced by taking patterns from an aerial every few degrees in the vertical or horizontal plane, whichever is applicable, each pattern being drawn on thin cardboard, cut out and glued together in the correct order as shown by the example of Fig. 7. A selection of patterns taken from model aerials on the testing table described in this article are shown in Figs. 8, 9, 10 and 11. The model aerials are shown in the photograph of Fig. 12.

Fig 7. Solid radiation pattern of two vertical half-wave aerials spaced one wavelength apart and fed in phase.

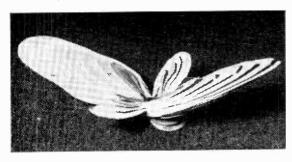

Wireless World, December 1960

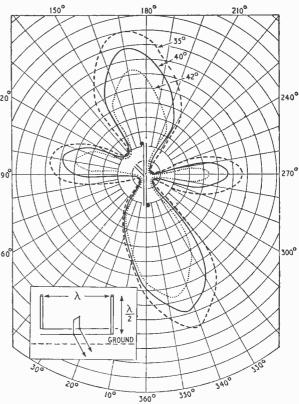


Fig. 8. Radiation patterns of two vertical half-wave aerials as described in Fig. 7 and measured at three different vertical angles.

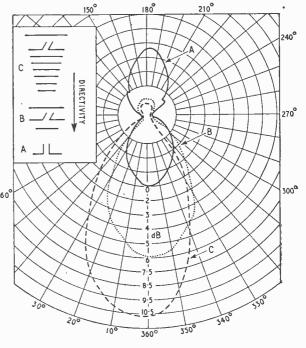


Fig. 9. Gains of 3- and 8-element Yagi aerials compared with a half-wave dipole measured at 3,000Mc/s.

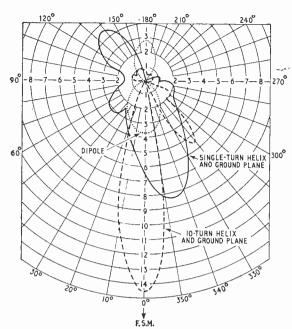


Fig. 10. Radiation patterns and gains compared with halfwave dipole of single-turn helix with ground plane and ten-turn helix with ground plane.

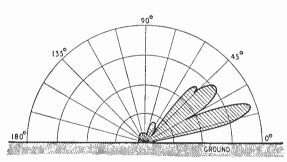


Fig. 11. Vertical radiation pattern of a scale model 2-element "Quad" aerial.

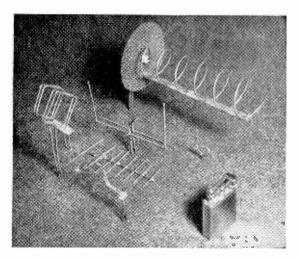


Fig. 12. Some of the scale model aerials used for the measurements described in the text.

Models provide a unique system for testing and estimating the performance of aerials for all the lower radio frequencies up to at least 30Mc/s and offer an excellent method of demonstration during lectures. The writer has used over 100 different models and several aerials suitable for amateur radio transmitting have been developed with the aid of the testing table. Using scale models, a number of enlightening experiments were recently carried out to determine the radiating properties of "loaded aerials" suitable for mobile operation on the 1.8- and 3.5-Mc/s amateur radio bands and for certain applications at frequencies around 30Mc/s.

REFERENCES

- ¹ The Admiralty Wireless Handbook, H.M.S.O.
- ² G. H. Brown and R. King. "High Frequency Models in Antenna Investigation." *Proc.I.R.E.*—April, 1934.
- F. Charman, B.E.M. "High Frequency Model Aerials," *Proc.R.S.G.B.*—Spring, 1949.

Additional Sources of Information

- L. E. Radburn, Tele Tech-September/51.
- R. D. Rhodes, Electronics-March/49.
- J. T. Tiley, Electronics—February/52.
- F. C. Judd, Short Wave Magazine-January/50.
- J. D. Kraus, Electronics—April/47.

BOOKS RECEIVED

The Radio Amateur's Handbook, 1960 edition, compiled by the American Radio Relay League, West Hartford, Connecticut, U.S.A. First published in 1926 and now widely recognized as the standard manual of amateur radio communication. Chapters devoted to construction of equipment have been extensively revised to include the latest s.s.b. and radio-teleprinter techniques for amateur use. Several chapters are devoted to basic principles clearly explained. Pp. 584 plus 32 pp. of tabulated data on valves and semiconductors with over 1,300 illustrations. Obtainable from leading technical booksellers, also from Radio Society of Great Britain, New Ruskin House, Little Russell Street, London, W.C.1; price 32s 6d (34s by post).

Mullard Reference Manual of Transistor Circuits. More than 60 circuits of audio amplifiers (including p.a.), hearing aids, simple radio receivers, oscillators, switching circuits, stabilized power supplies, etc., with component values, coil winding data and constructional hints. Prepared by the staffs of Mullard Research Laboratories, Applications Research Laboratory and Semiconductor Measurement and Application Laboratory. There are nine introductory chapters on transistor characteristics, equivalent circuits, bias and stabilization and limiting values. Pp. 308; Figs. 241. Mullard, Ltd., Torrington Place, London, W.C.1. Price 12s 6d (13s 6d by post).

British Semiconductor Guide—1960. Characteristics of 963 semiconductor devices including transistors, diodes and rectifiers and photosensitive devices, with introductory articles on considerations determining the use of valves and transistors, and on transistor parameters and specifications. Pp. 66. Heywood & Co., Ltd., Drury House, Russell Street, London, W.C.2.

Einführung in die Microwellen-Electronik. Teil II Lauffeld-röhren by Drs. Kerner Kleen and Klaus Pöschl. Mathematical treatise on the principles and operation of travelling-wave tubes in general and special types, including backward-wave oscillators and amplifiers. Pp. 192; Figs. 125. S. Hirzel Verlag, Birkenwaldstrasse 185, Stuttgart N.

100-kc/s Crystal Marker


EMBODYING A NEON MODULATOR FOR HARMONIC RECOGNITION

By F. G. RAYER*

*Amateur Radio Station G3OGR.

HE use of a 100 kc/s crystal marker, to provide frequency checking harmonics at 100 kc/s intervals, is quite well known. Such a marker is most often employed in conjunction with a communicationstype receiver to give exact calibration, or check points at 100-kc/s intervals. Amateur transmitters can employ a marker of this kind to locate the band edges, or for calibrating or adjusting a transmitter VFO. When used with a reasonably accurately calibrated receiver, this method is an acceptable one for frequency determination with amateur transmitting equipment.

The usual simple type of crystal marker has the disadvantage that it is not always possible to distinguish its signal from other signals, especially when tuning to higher harmonics. Even with the receiver aerial removed, other carriers are heard on the crowded short wave bands, so that the crystal marker's signal cannot always be located immediately and without possibility of error. To avoid this, the circuit shown in Fig. 1 is provided with a

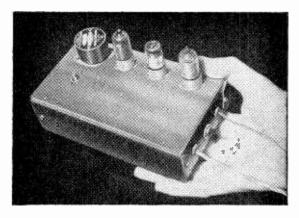

The completed crystal marker showing the top plate screwed to the chassis box.

neon "modulator." This strikes two or three times a second, pulsing the 6BA6 control grid negative, so that the marker signal can always be identified at once. Such a "modulator" does not produce sidebands which would confuse tuning. In addition, the 6BA6 acts as an harmonic amplifier, so that the marker can be used up to about 30Mc/s.

The crystal oscillator stage consists of a 6AM6, with a 100-pF pre-set capacitor for frequency adjustment. The degree of adjustment is quite small, but it allows the crystal frequency to be checked against the B.B.C. 200kc/s Light Programme, or the National Physical Laboratory standard frequency transmissions on 2.5Mc/s, 5Mc/s, and 10Mc/s. Other valves, such as the CV138 or EF91, etc., may be used in this stage. The type of neon is of little importance, provided it will operate with about 150V to 250V. Various other valves could also be utilized instead of the 6BA6.

The unit illustrated was built into a universal chassis $4in \times 7in \times 2in$, with back plate, obtainable from Home Radio (Mitcham) Ltd. The layout employed is shown in Fig. 2. To simplify work the

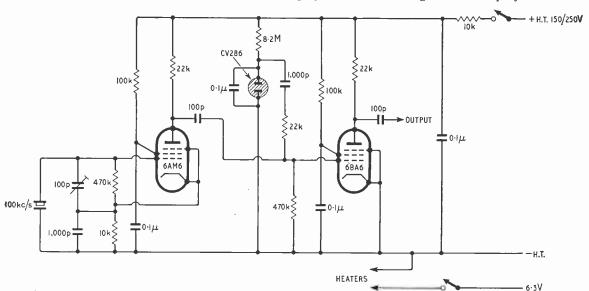


Fig. 1. Circuit diagram for the 100-kc/s crystal marker.

marker was built on the 4in×7in back plate and when completed it was fitted on to the chassis box. For lining up with other equipment it was most convenient to have the heater switch, supply leads, and output at one end of the chassis box. If the marker is connected to its supply only when used, no switch is required, but if it is permanently connected, the h.t. circuit has to be switched, as in Fig. 1, to stop the neon striking.

It is essential that the 100-pF pre-set capacitor is isolated from the chassis. It is also necessary that the 0.1-µF capacitor, in parallel with the neon, should be without appreciable internal leakage, or the neon will not strike. For the same reason the associated 1,000-pF capacitor should be a mica type.

The crystal connections shown in Fig. 2 are for a Quartz Crystal Co's. octal-based Q5/100 crystal unit. This has so low a temperature coefficient that for normal purposes no temperature control is needed, and the crystal stage of the marker is a modified Colpitts intended for use with this crystal. With the component values given, the accuracy of the marker would usually be sufficient even without

checking the frequency against the B.B.C. or MSF (Rugby) transmissions.

Power for the unit can often be drawn from the receiver; if not current may be available from a small power pack, or from some other item of equipment. Coupling between the marker and receiver will be sufficient, for lower frequencies, if the marker output lead is placed near the receiver aerial terminal. For the high harmonics, the output lead is connected directly to the receiver.

To check against the B.B.C. or MSF transmissions, tune in the signal, and adjust the marker coupling to the receiver so that its signal is of similar strength to that of the station. In some parts of the country this may mean that no aerial, or a very short length of wire, will suffice. The receiver BFO should not be used, and if the MSF transmissions are chosen they should be at those periods (of the hour) when no modulation is present.

When the 100-pF capacitor is far from its correct setting, the difference in frequency between the crystal marker and the station transmission will be audible as a low pitched flutter. As the capacitor


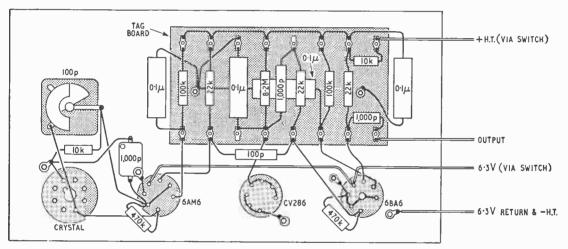


Fig. 2. Layout of components and wiring on the underside of the "top" plate of the chassis box.

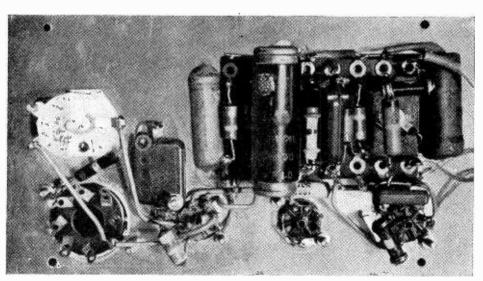

This underside view of the top plate should be studied in conjunction with Fig. 2 for identification of the components.

is adjusted towards correct capacity, the rapidity of flutter will decrease. If a tuning meter or indicator is fitted to the receiver, this will rise and fall as the marker and station signals fall in and out of step, and the best setting for the capacitor can easily be located. The B.B.C. 200-kc/s transmissions are easily received in many areas, frequency is maintained to a very high order of accuracy, and adjusting the marker against this frequency is particularly simple.

For checking receiver calibration, the receiver

BFO should be switched on, and the aerial removed. The gain controls will need to be quite low for harmonics such as those used to mark the edges of the 1.8Mc/s to 2Mc/s or 3.5Mc/s to 3.8Mc/s bands. For higher harmonics, such as are required to indicate the edges of the 28Mc/s to 30Mc/s band, the receiver gain controls will need to be near maximum.

For signal generator or VFO calibration or adjusting, the BFO should be off, so that the generator or VFO signal can beat with the crystal marker's

signal.

Amateurs' National Convention

VARIED R.S.G.B. PROGRAMME AT CAMBRIDGE

HE fourth post-war National Convention of the Radio Society of Great Britain—held at Cambridge from September 15th-17th and attended by some 200 members and guests—was notable for the very full programme of technical lectures and discussions, in addition to visits to places of technical interest and those social functions which are traditional at amateur radio conventions.

The links between radio amateurs and radio astronomers have always been close; indeed the first steerable radio telescope was built by an American amateur and a British amateur played an important rôle in establishing the radiation of radio signals by the sun. The Cambridge convention fittingly included talks by Prof. Martin Ryle (who holds the call G3CY) and Dr. F. G. Smith, of the Mullard Radio Astronomy Observatory. The programme also included visits to the Observatory to see the unique development of aperture synthesis and EDSAC II, the University's computer on which the observations are analysed. One of the radio telescopes now records signals automatically in digital numbers for feeding direct to EDSAC.

Prof. Ryle described the two main aerial arrays which would be capable of detecting a one milliwatt transmitter on the moon and which in June identified radio sources 4,500,000,000 light-years distant—the world's one-way DX record! Present investigations are concentrated on 38 and 178 Mc/s, though work is also being carried out on 81.5 and 408 Mc/s. By aperture synthesis, the 3,200ft, 38 Mc/s fixed array used in conjunction with the relatively small moving section gives results equivalent to a paraboloidal reflector of 1,500ft diameter.

The low-noise maser, parametric amplifier and electron beam amplifier are not exactly standard amateur practice yet (though some interesting work on parametric amplifiers has been carried out by amateurs in the United States and also, on a more limited scale, in this country) but A. H. W. Beck and Dr. F. G. Smith graphically summarised recent research in these developing fields. The Adler tube, with its remarkable ability to separate signal from noise and then to lose the noise, appears particularly promising in view of its relative simplicity of adjustment, wide bandwidth and 25dB or so gain to 3,000 Mc/s—if only prices fall to suit amateur pockets. At the other end of the radio spectrum, Dr. B. H. Briggs, of the Cavendish Laboratory (formerly

G2FJD) described investigations into the strange phenomena of the "whistling atmospherics."

The rapidly increasing interest in single-sideband transmission ensured a lively audience for a survey of modern amateur practice by G. C. Bagley (G3FHL)—one of the few British amateurs who can already claim more than ten years' experience of this type of operation. Another topic attracting increasing attention stems from the results now being achieved by members of the British Amateur Radio Teleprinting Group which sprung into being after the first British amateur teleprinter contacts were made last year in the 3.5 Mc/s band.

A most effective demonstration of the present advanced state of amateur television transmission in the U.K.—which appears to lead the world in this specialized branch of amateur radio—was presented by members of the British Amateur Television Club. Two 27in receivers displayed the 405-line transmissions from G3NOX/T at Duddenhoe End, some 15 miles from Cambridge. This station, one of an active network of stations reaching well down into Essex, transmits on 436.3 Mc/s with an e.r.p. of 5.7 kW.

The pictures were of impressively high standard; so incidentally was the programme technique displayed by the team of operators who had pooled resources to provide three camera chains. Transmissions from this group of stations are made regularly on Saturday evenings and can be received over distances of up to about 30 miles on standard television receivers fitted with 70-cm converters. At the end of the demonstration, viewers at Cambridge were able to question the operator (I. M. Waters, G3KKD) at the television transmitter via a duplex radio link on 70cm and 2 metres.

radio link on 70cm and 2 metres.

Throughout the Convention transmissions were made on amateur bands from 1.8 Mc/s to 144 Mc/s

under the special call-sign GB2CAM.

The convention was rounded off by a dinner at the Guildhall with guests including the Mayor of Cambridge, who had assisted the event in many ways, Dr. F. G. Smith, Brigadier E. J. H. Moppett and Major-General E. S. Cole, now Director of Telecommunications at the War Office, but formerly better known to amateurs as G2EC, SU1EC and SV1EC. General Cole spoke of the effective work of the R.S.G.B. in preserving amateur frequency allocations and of the value of radio communication in encouraging international friendships.—J. P. H.





DUSSELDORF EXHIBITION OF AUTOMATION AND INSTRUMENTS


OCCUPYING thirteen exhibition halls of various sizes having a total floor area of nearly 10 acres, the Interkama exhibition and congress was held from 19 to 26 October. 470 exhibitors, 188 from countries other than Germany, displayed equipment for test, measurement, process control, data logging and the myriad other functions required by industry today. There were sections devoted to French, East German and British firms (this latter arranged by S.I.M.A.), but these were not the only displays because many "foreigners" showed their products on the stands of their German agents, or had stands of their own elsewhere in the exhibition.

Industrial Control and Automation

The simplest type of control system uses a man, who makes adjustments by reference to a continuous-reading instrument, as part of a servo loop. The next step is, naturally, the closing of the loop without the man, so that automatic control is achieved. A practical illustration of a closed-loop control system was given by Eckhardt, with a liquid-flow meter and control valve. The sensor uses the Faraday effect of the generation of a potential on a conductor moving in a magnetic field: an electromagnet energized from the mains creates a field across the pipe carrying the liquid. Two electrodes pick out the potential generated by the flow, and this potential is "bucked" or backed off by a servodriven potentiometer whose motor is energized, via amplifiers, by the difference of potential between the potentiometer and electrodes.

For quality control of a product the recording of the many parameters of a plant must be carried out constantly. The registering, collating and working out of results from these readings can, in a complex plant, consume much time and effort, but this "watchdog" facility can be provided by a central data-processing machine, for instance, the Beckman "123" system. This can accept up to 100 electrical inputs representing plant parameters, scanning each one by a stepping switch in 60sec, processing each input as selected by the position of plugs in a peg board—a zero offset might be required for one input, say, whilst another channel may require a logarithmic amplifier characteristic. The measurements taken can be written out on an electric typewriter or punched-tape system at preset intervals or on demand, and a digital electrical output is available.

"Automation" of processes using small closed loops can have the disadvantage of inflexibility when, say, a chemical process using raw materials of variable quality or where fairly frequent changes in output are required. Each control loop must be reset to a new value each time a change is required, and all the possible combinations must have been worked out beforehand. With more than a very small number of variables it can be seen that the amount of work required could be uneconomical. However, the necessary flexibility can be achieved by opening the individual closed loops and interposing a "communal" computer. Then, by giving the computer the reaction equation and data on raw

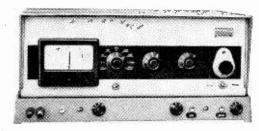

Macq Electronique drift meter for stabilized power supplies

material purity and price changes the programme can be set to operate the plant automatically for maximum profit.

A system of this type using a Ramo-Wooldridge RW 300 computer to control the manufacture of dodecylbenzene was illustrated on part of the French stand by the Compagnie Européenne d'Automatisme Electronique.

Another point noticed was the widespread use of small-package solid-state logic (such as "and," "or," "not") and instrumentation (timers, amplifiers, etc.) units. There would seem to be a good case here for the various manufacturers to standardise practical details such as mounting, connections and power supplies so that a Siemens "Simatic," say, is directly interchangeable with an Ateliers des Constructions Electronique de Charleroi "Logacec," a Telefunken "Logistat," or a Mullard "Norbit" or "Combi-element."

Instruments

A major feature of the exhibition was the display of instruments for test and measurement, as distinct from automatic control, in the laboratory or the production line. A complete floor of one exhibition hall was divided into "classrooms" in which 56 instrument manufac-

588

WIRELESS WORLD, DECEMBER 1960

The Wandel and Goltermann WZL-181 test set is designed for the testing of transformer windings. Basically the instrument itself consists of a bridge which can be preset to check coil resistance, turns ratio, etc., a "good" coil returning a zero or "in balance" reading. In the case of unbalance an indication of direction, i.e.,

turers gave 249 courses of instruction on their products.


In the case of unbalance an indication of direction, i.e., high or low, is given. The coil undergoing test is placed in a test jig and connected up; a standard coil induces power, and the tests (including a phase-reverse facility in case the leads have been reversed on connection) can be carried out by the use of push buttons on the jig.

On the General Radio stand small variable delay lines were found. These, having maximum delays of 0.5 and 1µsec are made rather after the fashion of a wirewound potentiometer, but the winding is skewed on the former to enable a greater length of wire to be in close proximity to a "screen" which forms the capacitive element of the line. This type of variable line is used in the GR 1392A delay generator which can be used for measurements of time intervals as short as 1/100 µsec. Another instrument seen here was a transfer-function and immittance (impedance and admittance) bridge for the range 25 to 1500Mc/s, enabling measurements to be made on two, three and "four" (one input and one output earthed) terminal networks. Two calibrated indicator heads are supplied with this bridge, one for each use, and these have small rotatable loops as variable coupling elements to the lines connected to the network under test. The loops are energized from an external generator and a null detector is connected to the junction of the output from the network, a known susceptance and a known conductance. By adjustment of the couplings from the generator to the network input and the resistive and reactive arms, a null can be achieved, when the parameters of the tested object can be read from the calibrated scales of the indicator heads.

For the testing of many circuits frequency-sweep techniques have immense advantages but until the Carcinotron*, whose frequency can be varied widely electrically, was produced by the C.S.F. the widest sweep available in the s.h.f. bands was somewhat limited. Several manufacturers have produced swept signal generators using Carcinotrons, notably Ferisol (Geffroy et Cie). A generator making its debut at the exhibition was the Rhode and Schwarz Type ZWC. This has a choice of plug-in Carcinotron modules covering the range 1 to 18 Gc/s in (roughly) octave sweeps and constant output is achieved by sampling the signal at a directional coupler at the entry to the test piece so that any anomolous effects due to the cable or waveguide coupling and the three "marker-producing" wavemeters are neutralized. These wavemeters are mounted below the display unit for ease of use, and the display itself offers double-trace working on a 20-cm (≈ 7¾-in) square cathode-ray tube.


The short-term drift, or random variations, of a stabilized power supply are usually so small that they are insignificant. However, if it is desired to know what is happening to one's "stable" supply, the difficulty of measurement has to be overcome. Macq Electronique had on display a drift-meter for this purpose; accepting inputs in the range IV to 2.5kV, a resistive network is used to drop the applied potential to that of a standard Weston cell contained within the instrument. A mechancial chopper switches between the cell and applied potential, and the resulting a.c. is amplified detected and applied to a centre-zero meter. The sensitivity of the amplifier can be adjusted so that variations of 1/100,000 or 1/10,000 of the input produce half-scale deflection; also sense (i.e., fall or rise) is indicated

*P.476, Wireless World, November 1959.

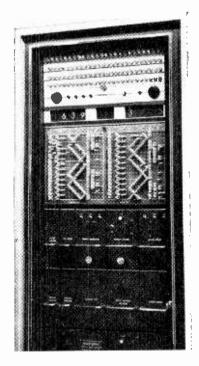


Beckman Instruments "123" datalogging system. "Peg board" is used for setting up.

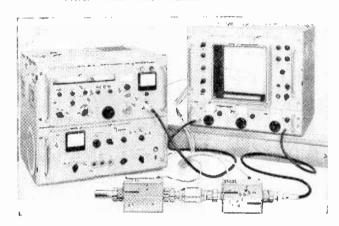Wandel u. Golterman transformer test set showing the test jigs.



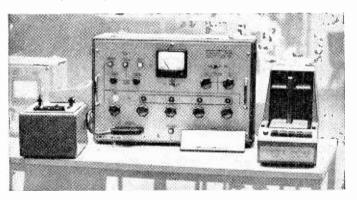Swept signal generator using Carcinotron (Rhode u. Schwarz).



WORLD OF WIRELESS

Commonwealth Telecoms

WITHIN the 62 pages of the 9th General Report of the Commonwealth Telecommunications Board, covering 1959, are reports on the activities in each of the eight partner countries which have nationalized telecommunications systems. The report as a whole is concerned mainly with traffic statistics but there are also some interesting items covering

research and developments.

In this country experimental tropospheric scatter transmissions from a transmitter near Bodmin, Cornwall, to receivers near Leafield, Oxon (173 miles) and at West Beckham, Norfolk (300 miles) continued with the aim of obtaining a year's cycle of measurements for analysis of fading characteristics. The tests have included comparisons between multi-channel telephony with f.m. and narrow-band s.s.b. with a.m. and also television with f.m. Tropospheric scatter transmissions from Holland to West Beckham (150 miles) are also being conducted. The C.T.B., of which Sir Ben Barnett is chair-

man, consists of a representative from each of the partner governments. Its primary function is the formulation of joint telecommunications policies.

For C.A.R.A.C. read C.C.E.C.A.

WHAT was originally known as the Civil Aviation Radio Advisory Committee has been renamed the Consultative Committee on Electronics for Civil Aviation. Broadly its terms of reference are to provide a forum for discussing U.K. policy in the field of electronics for civil aviation in relation to industrial research and development.

The representatives of the Electronic Engineering Association on the committee are Dr. B. J. O'Kane (Marconi's), K. E. Harris (Cossor) and Air Comdre. C. A. Bell (G.E.C.). The Ministry of Aviation, Admiralty, Air Ministry, B.O.A.C., B.E.A., Post Office, Society of British Aircraft Constructors and the British Independent Air Transport Association are also represented.

Student Exchange

SINCE the scheme for the international exchange of students for technical experience was introduced in 1947, over 52,000 students have participated. During the past year 6,430 took advantage of the scheme, which is operated by 24 countries. The 1960 report of the International Association for the Exchange of Students for Technical Experience records that Germany received the largest number of students (1,195) and also sent abroad the largest number (1,105), with the U.K. second, receiving 909 and sending 883.

The report issued by the U.K. branch shows the distribution by country of the students sent from and received in this country and also by the subjects which they were studying. About 20% (178) of U.K. students went to Sweden, from which the largest number of students (171) came to this country. The address of the London office is 178 Queen's Gate, S.W.7.

B.B.C. Plans

CONTRACTS have recently been placed by the B.B.C. for the building of a number of low-power transmitters to extend and improve its television and v.h.f. sound services. Combined stations are to be erected at Oxford, Llandrindod Wells (Radnor) and Redruth (Cornwall) and a TV station at Manningtree (Essex). Also the site has been chosen for a combined station near Galashiels (Selkirk).

Approval in principle has been given by the P.M.G. for a low-power station near Ballachulish (Argyll). This station is additional to those originally planned for Western Scotland. A point-to-point link was originally to be installed for this part of the route feeding two new stations. It has been decided, however, to build a small auxiliary station which will serve the dual purpose of linking the two stations and providing direct television reception for the people in the area.

Technical Writing

AUTHORS of technical articles on British electronic developments, published during 1960, who wish to compete for the six premiums of 25 guineas each awarded by the E.E.A. and R.I.C., must submit their entries by December 31st. They should be sent to the Electronic Engineering Association, 11 Green Street, London, W.1, and should consist of a copy of the journal* and the relevant pages, proof or reprint. Entries must be accompanied by a signed declaration of eligibility, showing that the entrant is not paid a salary solely for writing and not earning 25% or more of his income from articles or book royalties.

* Wireless World is sent by arrangement to each of the judges

Receiver Despatches.—Figures issued by B.R.E.M.A. show that manufacturers' despatches of television re-ceivers during the first nine months of this year were 30% below the same period last year (1,257,000 compared with 1,787,000). Domestic sound receivers and (1,346,000 against 1,091,000). Radiogramophones, too. rose from 114,000 to 130,000.

Recording Studios.—The revised topographical list of members of the Association of Professional Recording Studios shows that the Association now has a membership of nearly 100 "private professional studios" in this country. It operates a scheme under licence from the Mechanical-Copyright Protection Society, permitting its members to make recordings for private customers of works controlled by the M.P.S.

CHRISTMAS PRESENTS

Why not give your technical friends a copy of the Wireless World Diary as a Christmas present? It has an 80-page reference section and costs 6s 9d (leather) or 4s 9d (Rexine). Friends who seem quite incapable of adjusting correctly the controls of their television sets might appreciate a copy of "Improve Your Television Reception" (5s) or "Correcting Television Picture Faults" (4s). Satellite Communications.—Technical discussions between American and British officials on matters associated with the possible use of communications systems via earth satellites are being held in the U.S.A. The U.K. team is headed by Major General L. de M. Thuillier, of the Cabinet Office, and includes Captain C. F. Booth, W. J. Bray, H. Leigh and F. J. D. Taylor, of the Post Office; J. R. U. Page, of the Office of the Minister for Science; F. E. J. Girling, A. G. Earl and C. Williams (Ministry of Aviation); F. A. Kitchen (Admiralty) and Group Captain A. Foden and C. F. Sutton (Ministry of Defence).

B.C.A.C.—When the British Conference on Automation and Computation, which is a consortium of associations and institutes interested in the field of computation, was formed in 1957 it was divided into three autonomous groups. One dealt with engineering, another control and the third sociological interests. It has now been decided to reconstitute the association with a central council. There are now about 30 societies in the reconstituted B.C.A.C. of which Sir Walter Puckey is chairman with L. T. Blakeman, J. F. Coales and H. G. Conway as vice-chairmen. The honorary secretary is W. K. Brasher, secretary of the I.E.E. which is providing secretarial services.

Local Broadcasting.—A detailed survey of their plans for 100 or more local broadcasting stations in this country has been issued as a 13-page brochure by Pye Ltd. Comparisons are drawn with the situation in the U.S.A. where extensive use is made during daylight of common medium-frequencies by a large number of stations with geographical spacing of 90 miles or less.

Fleming Memorial Lecture of the Television Society will be given by Professor D. M. MacKay on January 26th at the Royal Institution, Albemarle Street, London, W.1. His subject will be "Behind the Eye". Admission is by ticket obtainable from the society, 166 Shaftesbury Avenue, London, W.C.2. Dr. MacKay was recently appointed to the research chair in communication founded by Granada Television at the University College of North Staffordshire.



MARY E. CHAMBERS, of the E.M.I. Research Laboratories, is the first woman to be awarded the Dip.Tech. with first class honours. She has taken a four-year sandwich course at the Brunel College of Technology and E.M.I., where she has been concerned with the preparation of photo-conductors for television camera tubes and phosphors for c.r. tubes.

Publication date. — Owing to the Christmas Holidays our January issue will not be published until December 31st.

The National Radio Show, 1961, will be held at Earls Court from August 23rd to September 2nd with a preview for overseas and invited guests on August 22nd. This, the 28th National Radio Exhibition, will again be organized by Radio Industry Exhibitions Ltd., 59 Russell Square, London, W.C.1.

Aeronautical Electrics and Electronics.—A joint committee, with Professor G. A. Whitfield, of the College of Aeronautics, Cranfield, as chairman, was recently formed by the I.E.E. and the Royal Aeronautical Society to consider ways and means of stimulating discussion of problems of common interest. As a result, joint meetings of the two organizations are to be held in London and plans are being made for the formation of joint groups in the provinces. At the inaugural meeting in London on November 11th, Viscount Caldecote spoke on the future of "electrics" and "electronics" in aircraft and guided missiles.

Transducers.—The Electronic Engineering Association is seeking the help of manufacturers and users in compiling a list of transducers. It is collating information not only on current types but also on those under development. Those interested in helping the association in compiling this list, which will be available to nonmembers, are invited to send for the questionnaire obtainable from J. F. Richardson, Technical Secretary, E.E.A., 11 Green Street, London, W.1.

Gramophone records produced during the third quarter of the year totalled just over 16M, about 5% more than in the corresponding period last year. There were 59% fewer 78 r.p.m. records produced (688,000 compared with 1,691,000) and 2% fewer 33\frac{1}{2} r.p.m. discs (3,488,000 against 3,546,000) but 18% more 45's and medium-play (11,860,000 against 10,092,000).

Vacation Courses.—"Introduction to Industry" training courses are again available at the Chippenham Works of Westinghouse Brake and Signal Co. Ltd., for boys who are taking G.C.E. "A" level scientific subjects. Two courses are arranged during the Christmas vacation, January 2nd to 6th, and 9th to 13th. Applications should be made before December 1st.

Engineering aspects of the plastics industry will be covered by a new monthly journal, *International Plastics Engineering*, to be published in association with *British Plastics*. The first issue will appear on February 1st.

INDUSTRIAL GROUPS - 3

E.M.I.—Since going to press with the section of this issue in which the third of our series of surveys of industrial groups appears (p. 611), E.M.I. has supplied additional information which brings the total number of companies within the group to nearly 80. The additional companies are:—

80. The additional companies are:—
E.M.I. (Australia) and its subsidiaries, Television Patents, Marconiphone Co., E.M.I. Finance Corp., Hayes Properties, and Castle Music; the following subsidiaries of Capitol Records Inc.: Ardmore Music Corp., Beechwood Music Corp., Capitol Records International Corp., Capitol Patents, Capitol Records International Corp., Capitol Publications Inc., Electric & Musical Industries (U.S.), Electric & Musical Industries (Canada), Capitol Records of Canada, Ardmore & Beechwood (U.K.), and Capitol Records of Canada, Ardmore & Beechwood (U.K.), and Capitol Reyal Club of Canada; Edition Accord, Kristall Schallp, alten, and Odeon Musikhaus, subsidiaries of Carl Lindstroem; and these ten additional subsidiaries of Morphy-Richards, Morphy-Richards (Canada), Morphy-Richards, S. Africa, Morphy-Richards (Canada), Morphy-Richards, S. Africa, Morphy-Richards Inc., U.S.A., Morphy-Richards (Nederland), M-R Salgsorganisation A/S, Denmark, Eureka Electric, Astral Equipment, and Yelsen.

Personalities

Major-General E. S. Cole, C.B., C.B.E., has accepted the invitation to become president of the Radio Society of Great Britain for 1961. He has been a member of the society for nearly thirty years and is well known among amateurs by his call G2EC. General Cole was commissioned in the Royal Signals in 1925 and from 1941 to 1946 was Corps Chief Signal Officer. In 1952 he became Chief Signal Officer, Headquarters, Southern Command, and in 1954 was appointed Deputy Chief Signal Officer, Signals Division, S.H.A.P.E. Since 1958 he has been Director of Telecommunications, War Office. General Cole was at one time chairman of the British Joint Communications Board.





Maj. Gen. E. S. Cole

J. K. Laughton

- J. K. Laughton, who joined Plessey's Telecommunications Division in 1958 as sales engineer, has been appointed manager of that division. He went to Plessey after 20 years' service in the Royal Navy. He was promoted to Commander in 1954 and was for the last year of his naval career Assistant Director of Radio Equipment (Communications) in the Admiralty.
- J. H. H. Merriman, O.B.E., M.Sc., A.Inst.P., M.I.E.E., was recently appointed staff engineer of the Overseas Radio Planning and Provision Branch of the Post Office. For the past four years he has been seconded to the Treasury as the assistant secretary responsible for computer work and policy in all Government Departments. A physics graduate of King's College, London, where he later worked under Professor Appleton on non-linear oscillators for his M.Sc. degree, he joined the Research Station staff at Dollis Hill in 1936. He was closely associated with the development of MUSA—the steerable aerial system.
- N. T. Atkinson, formerly head of television development in Ekco, has been appointed to the post of chief of television and radio development. He has been concerned with the development of Ekco television receivers since 1938 and in his new position he will be directly responsible to A. J. Brunker, executive director and chief engineer. E. W. Maynard, who has been in charge of export television development, succeeds Mr. Atkinson as head of television development.
- Dr. J. L. Pawsey, F.R.S., assistant chief of the Division of Radiophysics of the Commonwealth Scientific and Industrial Research Organization, Australia, has been awarded the Hughes Medal of the Royal Society for his distinguished contributions to radio astronomy both in the study of solar and of cosmic radio emission.

Terence B. Tomlinson, Ph.D., B.Sc., A.M.I.E.E., A.M.Brit.I.R.E., joined Southern Instruments earlier this year as chief engineer. He is responsible for design and development for the newly formed company, Drayton-Southern, Ltd. After graduating from London University he became a laboratory demonstrator in electronics at the Cavendish Laboratory, Cambridge. He spent two years with Sobell Industries, returning to the university to take a higher degree—his research being concerned with low-frequency fluctuations of emission from oxide-coated cathodes. Dr. Tomlinson subsequently became a lecturer in electronics at Southampton University, where he stayed for six years before joining the G.E.C. Research Laboratories for work on solid-state physics. He transferred to the G.E.C./I.C.T. subsidiary, Computer Developments, Ltd., where he stayed until joining Southern Instruments.

Dudley Saward, O.B.E., who joined Texas Instruments Ltd. on its formation in 1956, has resigned from the managing directorship in order to devote more time to other activities, but will remain a director of the company. Mr. Saward was chief radar officer, Bomber Command, from 1942 to 1945 and was for some time after the war controller of navigation and telecommunications with British European Airways. He is succeeded as managing director by A. N. Provost, a former U.S. naval officer and an engineering graduate of Tufts and New York Universities. Mr. Provost was for some time with Sylvania Electric Products before joining the semiconductor components division of Texas Instruments, Inc., in Dallas, U.S.A.

J. D. Dale-Lace, A.M.I.E.E., D.F.H., the new sales manager of the radio components and special products department of A.E.I.'s Radio and Electronic Components Division, was a technical officer in the Royal Navy from 1940 until 1946 when he joined Pye, where he worked on the development of television transmission equipment. A year later he went to South Africa as technical representative of Sperry's South African agents. He rejoined Pye in 1951 as a telecommunications sales engineer, and since 1956 has been with de Havilland Propellers as guided weapons service manager at Hatfield.





J. D. Dale-Lace

T. J. Murphy

T. J. Murphy, A.M.I.E.E., A.M.Brit.I.R.E., of the engineering division of Radio Eireann, has been given the City and Guilds Insignia Award in Technology (C.G.I.A.) for "his competence in the field of electrical industries (broadcasting—sound and television) and in respect of a thesis on the design of modern sound broadcasting studios." Mr. Murphy had been three years in Pye's final test department before joining the Engineering Division of the B.B.C. in 1943. He left the Corporation in 1951 to join Radio Eireann, Dublin, and for the past five years has been in charge of the studio department of the engineering division.

- Colonel H. A. Lewis, O.B.E., T.D., B.Sc.(Eng.), M.I.E.E., A.C.G.I., has relinquished his appointment as managing director of E.M.I. Sales and Service, Ltd., to become managing director of Newmark (London) Distributors, Ltd., precision instrument manufacturers, of Great Portland Street, London, W.I. Col. Lewis has been with E.M.I. since 1956. For the previous six years he was in the Broadcasting Division of Marconi's. From 1933 to 1948, except for the war years when he was in R.E.M.E., Col. Lewis was in the Engineering Division of the B.B.C.
- F. W. Perks, sales director of British Radio Corporation Ltd., is retiring. His career in the radio industry extends from 1914 when he joined Marconi's W/T Co. Freddie Perks, as he is affectionately known in the industry, has held many important appointments including the chairmanship of B.R.E.M.A. and B.R.V.M.A. and is at present chairman of Radio Industry Exhibitions Ltd. (organizers of the National Radio Exhibition) and president of the Radio Industries Club. He is succeeded as B.R.C. sales director by T. B. (Jock) Henderson, general sales manager of Philco (Great Britain) Ltd., an associate company.
- P. A. M. Curry, M.A., B.Sc., has been appointed deputy to H. St. A. Malleson, head of Mullard's Government and Industrial Valve Division. After graduating with a first in engineering science at Oxford, Mr. Curry studied for a research degree and was awarded a Henry Fellowship providing a two-year course at Harvard where he obtained the degree of Master of Business Administration.
- L. J. M. Knotts has joined Mullard Equipment Ltd. as technical adviser on the application of electronics to railway signalling and communication systems. He was formerly signal engineer to the Scottish Region of British Railways.
- F. S. Barton, C.B.E., M.A., B.Sc., M.I.E.E., who, as announced in October, has retired from the Civil Service, has joined the board of Painton & Co., Ltd., of Northampton.
- Keith Lockyer, B.Sc., A.M.I.E.E., A.M.Brit.I.R.E., has been appointed general manager of Donvin Instruments Ltd., and Dumar Optics Ltd., the instrument, camera and tape recorder repair firms which are part of the R. B. Pullin group.
- **Dr. T. W. Straker** is deputy manager of Marconi's Radar Division and not manager as was inadvertently announced in our last issue. The manager of the division is **E. N. Elford**, O.B.E., A.M.I.E.E.
- H. M. Palmer has retired from Marconi International Marine after nearly 50 years' service. He has been in charge of the company's Fleetwood service depot for the past 25 years. He is succeeded by J. E. Dallaston who joined the company in 1931 as a sea-going radio officer, as did Mr. Palmer.
- G. H. W. Johnson, Assoc.Brit.I.R.E., for the past three years marine director of Marconi (South Africa) Ltd., has relinquished his seat on the board and has joined Norsk Marconikompani A/S in a similar capacity. Mr. Johnson joined the Marconi organization as a radio officer in 1938.
- G. A. Dwyer, manager of the Marconi Marine Co.'s Bombay depot from 1952 to 1954, has been appointed the company's representative in India and Ceylon. He joined Marconi's sea-going staff in 1929. In 1941 he was appointed to the shore technical staff at Glasgow and three years later was seconded to the Naval base at Ardrossan.

Angela M. Lane has been appointed administrative secretary of the Television Society. She joined the secretariat of the Society in 1955 and has been assistant secretary for some time. Geoffrey Parr, the honorary secretary of the Society since 1945, who recently entered hospital for heart trouble, is now convalescing.

OUR AUTHORS

- G. W. H. Larkby, author of the article describing a remotely controlled TV camera designed by the B.B.C., has been with the Corporation since 1936, except for the war period when he served with the R.A.F. in 60 Group (Radar). On his return to the B.B.C., Mr. Larkby was attached to the outside broadcast department of the Television Service. He later transferred to the Designs Department where he has been chiefly concerned with the many complex electro-mechanical and optical problems in the television field.
- J. W. Bunn, joint author of the article on ceramic permanent magnets, is powder metallurgist with Swift Levick and Sons, with whom he has been associated for 13 years. In 1954 he gained the associateship in metallurgy from the University of Sheffield where he had undertaken part-time study. He is a licentiate of the Institute of Metallurgists. J. Harrison, his co-author, is magnet design engineer with Swift Levick. He was previously assistant metallurgist at the central research laboratory of the Permanent Magnet Association.
- F. C. Judd, contributor of the article on aerial measurements, is a free-lance technical writer. Until making writing his full-time occupation, he was in the radar research laboratory of Kelvin & Hughes.

OBITUARY

Dr. G. W. O. Howe, Emeritus Professor of Electrical Engineering of Glasgow University, died on November 7th, aged 84. Professor Howe was successively technical editor of and consultant to our sister journal Wireless Engineer (now Electronic Technology) for over 30 years. In 1956 he was awarded the Faraday Medal of the I.E.E. for "his pioneering work in the study and analysis of high-frequency oscillations and on the theory of radio propagation; and for his outstanding contributions to engineering education." Dr. Howe, who was apprenticed to Siemens at Woolwich, went to Imperial College as a lecturer in 1905 and in 1921 was appointed James Watt Professor of Electrical Engineering at Glasgow University, the position he held until his retirement in 1946 when he was appointed an Emeritus Professor. Dr. Howe was a great teacher and his editorials in Wireless Engineer over very many years were an outstanding contribution to electrical and radio theory. In recognition of "his contributions to the advancement of radio science and in particular for his long series of notable editorial articles in Wireless Engineer", he was, in 1956, elected an honorary member of the Brit.I.R.E.

Professor Bernard Hague, D.Sc., Ph.D., F.C.G.I., D.I.C., M.I.E.E., who had occupied the James Watt Chair of Electrical Engineering at Glasgow University since 1946, has died aged 67. His academic career began in 1920 when he became a lecturer at the City and Guilds College, prior to which he was for four years at R.A.E., Farnborough. Dr. Hague was a lecturer at Glasgow University from 1923 until 1929 when he went to the Brooklyn Polytechnic Institute, N.Y. He returned to Glasgow as senior lecturer in 1930.

Reginald Lawler, manager of the Electronics Division of Ferguson Radio Corporation, which he joined in 1938 as a radio development engineer, died on November 2nd, aged 59. He was at one time in charge of the company's factory at Hirwaun, Glamorganshire, but returned to Enfield in 1952.

News from Industry

Pye-Ekco Merger.—The boards of Pye Ltd. and E. K. Cole Ltd. have recommended to their share-holders a merger of the two companies through a holding company, as yet unnamed. C. O. Stanley would be chairman and E. K. Cole deputy chairman. Pye will have a 75% holding in the new company and Ekco 25%. Their combined assets are nearly £25M.

Plessey-Garrard.—Agreement has been reached in principle under which the Plessey Company would acquire all the issued share capital of the Garrard Engineering and Manufacturing Co. If the offer is accepted Garrard will continue as a separate entity under its own board of directors with Hector V. Slade as managing director.

Cossor.—Major-General Sir Miles Graham, who succeeded the Marquess of Exeter as chairman of A. C. Cossor Ltd. last March, reported at the annual general meeting that for the year 1959/60 the group trading profit was £127,699, compared with £534,260 the previous year. There was, however, a net loss of £97,977. The group includes Cossor Radar & Electronics, Sterling Cable Co., Cossor Communications, Cossor Instruments, Lea Bridge Cabinet Works and Best Products.

Baird.—Radio Rentals Ltd. have entered into an agreement to purchase Baird Television Ltd., and will market television and sound receivers bearing the name "Baird." All the company's sets are made in Bradford by its Bradford manufacturing subsidiary, Mains Radio Gramophones, and will in future carry the new trade name.

BMEWS.—R.C.A. Great Britain Ltd., the U.K. associate of the Radio Corporation of America, is "weapon system contractor" for the Fylingdales, Yorks., base for the American ballistic missile early warning system. It is estimated that the cost of the whole Fylingdales project will be \$115M. Work has already begun on this, the third site for the BMEWS chain (see Wireless World, July, 1960, p. 335).

Eimac.—In association with the development of new Eimac klystron valves for high-power radar and communications, Eitel-McCullough are building a "superpower" supply unit drawing 12 amps at 282kV (approximately 3MW). Agents for Eimac products in the U.K. are Walmore Electronics Ltd., Phænix House, 19/23 Oxford Street, London, W.1.

Trav-ler Tape Recorder.—This transistor battery/mains portable tape recorder introduced at the National Radio Show by Casian Ltd., is being produced by Aerialite Ltd., of Hargreaves Works, Congleton, Cheshire, who have acquired the manufacturing and distributing rights.

Balzers High Vacuum Ltd. has been formed, with offices at 1 Mornington Terrace, Regent's Park, London, N.W.1, to handle in this country the products of Balzers A.G., of Liechtenstein, including equipment for high-vacuum metallurgy and coating, vacuum pumping gear and measuring instruments.

Grundig.—To mark the sale of the 100,000th Grundig TK20 tape recorder in the U.K., G. S. Taylor, managing director, presented the 100,001st model to the Royal National Institute for the Blind at a recent ceremony in London. It is understood that it has already been assigned to the Chorley Wood College for Girls.

Air-to-Ground Telemetry.—A consortium of five British manufacturers has been formed on the recommendation of the Ministry of Aviation to exploit the overseas and U.K. markets for a major air-to-ground multi-channel telemetry system. This has been developed by the member companies in collaboration with the Royal Aircraft Establishment, Farnborough. The members are: Elliot Brothers (London) Ltd., McMichael Radio Ltd., Rank Cintel Ltd., Southern Instruments (Contracts) Ltd., and W. S. Electronics Ltd., who have been appointed to act on behalf of the consortium.

Thermionic Products (Electronics) Ltd., of Hythe, Southampton, have ceased manufacturing domestic tape recorders and dictating machines. A limited supply of spares will be available until the end of next year. The company is concentrating on the production of multichannel recorders for airport communications logging and other fields of data logging.

Marconi's have received a further order valued at over £93,000 for the supply of translators, amplifiers and associated equipment for the B.B.C. The equipment will be used in the first stage of the Corporation's programme for the extension of its television and v.h.f. sound services by satellite stations.

Vactric (Precision Tools) Ltd., and Vactric (Control Equipment) Ltd., subsidiary companies of Vactric Ltd., which was recently put in the hands of a receiver, are continuing to operate as separate entities.

Texas Instruments France, with headquarters in Nice, has been set up by the Dallas company to manufacture semiconductor devices and components for the European Common Market.

EXPORTS

I.L.S.—Through their Canadian associates, Pye Telecommunications Ltd. have received a contract from the Royal Canadian Air Force for the supply of an instrument landing system for installation at the R.C.A.F. Airfield, Trenton, Ontario. This is said to be the first installation of British I.L.S. in the western hemisphere.

Montreal's two new commercial television stations are to be equipped by Marconi's with duplicate 18-kW vision and 9-kW sound transmitters. Each station will transmit a bilingual service (English and French).

Broadcasting Transmitters.—British Sarozal, of 22 Berners Street, London, W.1, have recently supplied a number of short-wave and medium-wave broadcasting transmitters to Africa. They include a 5-kW transmitter for Radio Pax, in Beira, Mozambique, which will radiate on 3.952 and 7.205Mc/s and another for Praia, Cape Verde Islands, for operation on 3.960Mc/s.

Communications Equipment.—Racal, of Bracknell, Berks., have received through their agents, Instronics Ltd., of Stittsville, Ontario, three major orders for communications equipment from the Canadian Department of Defence Production. They have a total value of £560,000.

Multi-lingual Catalogue.—Alfred Imhof Ltd., of 112/116 New Oxford Street, London, W.C.I. have produced an international version of their catalogue of racks, cases, consoles and accessories, every item being described in ten languages (English, French, German, Spanish, Italian, Portuguese, Dutch, Swedish, Norwegian and Danish).

Ceram'c Permanent Magnets

By J. W. BUNN*, A.Met., L.I.M., and J. HARRISON*

A relatively recent addition to the range of magnetic materials is the barium ferrite ceramic permanent magnet¹. This material, commercially available under a variety of trade names, e.g. Feroba, Magnadur, Caslox, Indox, Oxit, etc., is basically an oxide compound having the formula BaFe₁₁O₁₉. It is non-metallic and, in common with other ceramics, is hard, brittle, a non-conductor, and relatively light in weight when compared with alloy magnets. These properties together with its unique magnetic characteristics have opened up a new field in magnet applications.

Barium ferrite, although of similar appearance to the more commonly known "soft" magnetic

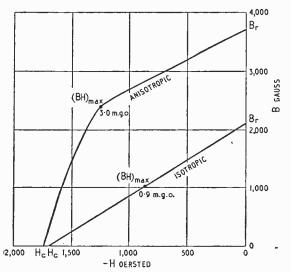


Fig. 1. Demagnetization curves for barium ferrite.

core materials, is distinct from this class inasmuch as magnetically soft materials are characterized by high permeability and low losses when used in an a.c. circuit, whereas barium ferrite is a magnetically hard material possessing a high coercivity, remanence and energy product $(BH)_{max}$. The compound $BaFe_{12}O_{19}$ has a hexagonal crystal structure with one axis of easy magnetization parallel to the hexagonal axis. This uniaxial crystal anisotropy together with a small crystal size (approximately 1 micron) is largely responsible for the high coercivity of this material compared with a "soft" magnetic ferrite which has a cubic crystal structure, i.e. three easy directions of magnetization, resulting in low coercivity. Magnetic Properties.—An essential feature of a permanent magnet is its ability to withstand demagnetization, and this is directly related to the coercivity of the material. Barium ferrite has an

exceptionally high coercivity of the order of 1600 oersted, compared with 600-650 oersted for Alcomax alloys, which is responsible for its ability to withstand high demagnetization effects such as a.c. fields, repulsion by other magnets, and excessive mishandling. Its high coercivity coupled with low permeability makes it possible to use ceramic magnets to minimize magnetic leakage fields of magnetic circuits and so increase the overall efficiency of the assembly.

Of the two further properties, remanence B_r and energy product $(BH)_{m,n}$ the former is a measure of the magnetization remaining in a material when the applied field is reduced to zero, and the latter is the maximum product of $B \times H$ on the demagnetization curve, shown in Fig. 1.

The low saturation magnetization² of barium ferrite leads to comparatively low B_r and $(BH)_{max}$, typical values for the isotropic variety being shown in Table 1.

Additional properties of permanent magnets which are sometimes required are the incremental or reversible permeability, and the maximum useful recoil energy³. In isotropic barium ferrite these values are 1.2 and 0.7 m.g.o. (mega gauss-oersted) respectively, from which it is seen that the recoil

TABLE 1

PROPERTIES OF BARIUM FERRITE COMPARED WITH ALCOMAX III						
Paragrapa P	Isotropic BaFe ₁₂ O ₁₉	Anisotropic BaFe ₁₂ O ₁₉	Alcomax III			
Remanence B _r (gauss)	2100	3700	12,800			
Coercivity H _c (oersted)	1700	1750	675			
Maximum energy product (BH) _{max} (m.g.o.)	0.9	3.0	5.5			
B_w at $(BH)_{max}$ (gauss)	1000	2400	10,200			
H_w at $(BH)_{max}$ (oersted)	900	1250	540			
Recoil permea- bility	1.25	1.15	3.5			
Maximum useful recoil energy (m.g.o.) Temperature coefficient of mag-	0.7	1.0	1.5			
netization (%/°C)	-0.2	-0.19	-0.02			
Curie tempera- ture (°C)	450	450	860			
Resistivity (ohm- cm) Density (gm/cc) Magnetizing field	1×10 ⁶ 4.8	1 × 10 ⁶ 5.0	55×10 ⁻⁶ 7.35			
for saturation (oersted)	10,000	8,000	3,000			

^{*}Swift, Levick & Sons, Ltd.

energy is 47% of that of Alcomax III alloy magnet material, whereas the total energy $(BH)_{max}$ is only 18% of that of Alcomax III. In view of the comparatively low cost of barium ferrite a definite economic advantage is gained by using this material under recoil conditions. Other features of the recoil properties are dealt with in the section on design and applications.

The Curie point of this material, i.e. the temperature at which for practical purposes the material ceases to be magnetic, is 450°C, so that all traces of magnetism can be removed by heating to above this temperature. For barium ferrite, this is the best method of demagnetizing, but this method cannot be used for normal alloy magnet materials.

A serious disadvantage of barium ferrite is its high temperature coefficient of magnetization which

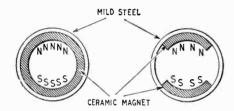


Fig. 2. Isotropic ceramic magnets for d.c. motor stators. Continuous cylinder (left) segments (right).

at -0.2% °C is some ten times greater than that of normal alloy magnets. This excludes the use of barium ferrite for, say, measuring instruments, unless elaborate temperature compensating devices are included.

The resistivity of barium ferrite is of the order of 106 ohm-cm, and this is of great importance in h.f. applications.

A density of 4.8 gm/cc is usual, which can be advantageous where weight considerations are paramount.

In 1952, Rathenau and others4 found that by aligning the crystallites of this material when in powder form by means of a strong magnetic field, an anisotropic effect was observed in the direction of the aligning field. Following this, intensive work by different workers5 in various parts of the world has led to the anisotropic variety which has a higher remanence and a (BH) max some three times greater than isotropic barium ferrite.

At the time of writing, only the isotropic form is commercially available in large quantities in this country. Table 1 gives typical properties of both isotropic and anisotropic barium ferrite, together with the more commonly known alloy material Alcomax III. Demagnetization curves for both varieties of barium ferrite are shown in Fig. 1. Manufacture.—The basic ingredients are iron oxide Fe₂O₃ and barium carbonate BaCO₃ which are mixed in the correct proportions and then heated in air at 1000°C approximately to form the required compound BaFe₁₂O₁₉. This is followed by ball-milling to a very small particle size, after which a binder is added and the powder pressed to the required shape by normal powder metallurgy techniques. The compacts so formed are then fired by heating to approximately 1200°C in an oxidizing atmosphere. The density of the fired compact is about 90% of its solid density, and volume

shrinkage occurs, the final compact being approximately five-eighths by volume of the pressed

The anisotropic differs mainly from the above isotropic variety in that the ball-milled powder is magnetically aligned in the required direction during the pressing process. This alignment is achieved by applying a high magnetic field to the powder, which can be either dry or in the form of a slurry, whilst the powder is in the die. To obtain precise dimensions, the finished magnet may be ground, but normal drilling and machining methods are impracticable due to the brittle nature of the ceramic material.

After mechanical inspection and magnetic testing for quality, final magnetizing is carried out, when a force of 7000 ampere-turns per centimetre length of material must be applied to achieve saturation. Design.—In the design of permanent magnets or magnetic circuits incorporating permanent magnets, the aim is to produce the required performance in the most economical manner. In other words, the most efficient use of the magnetic material must be obtained.

Reference has already been made to the demagnetization curve and the three properties B_r, H_e, and (BH)_{max} of a magnetic material, and these are the main features of the material used by the design engineer.

In the majority of permanent magnet applications it is desired to achieve a given magnetic field strength within the confines of a finite gap. In a gap of length l_g and area a_g , where \mathbf{H}_g is the field required in the

$$H_{w}l_{g}k = H_{w}L_{m}...................................(1)$$
where $L_{m} = \text{length of magnet material}$
 $H_{w} = \text{demagnetizing force}$
 $k = \text{reluctance factor.}$

The demagnetizing force H_w is the value at the particular operating point selected for the design on the demagnetization curve, and k is a factor to allow for the total reluctance of the magnetic circuit and usually has a value of between 1.1 and 1.3.

If B_w is the simultaneous induction value at point H_w on the demagnetization curve, then the total flux required in the gap is:-

$$H_{y}a_{y}K = B_{w}A_{m} \qquad (2)$$
where A_{m} = magnet cross-sectional area
$$K = \text{leakage factor}$$
Combining (1) and (2) we have:—

$$V_m = \frac{H_g^2 v_g K k}{B_w H_w} \qquad (3)$$

where $V_{\it m}=$ volume of magnet material $v_g = gap \ volume$

from which it is seen that the minimum volume of magnet material required to produce a given gap energy is obtained when the product B_wH_w is a maximum. Hence it follows that the most efficient design will be obtained when the magnet geometry is constructed so that the point B_wH_w coincides with the $(BH)_{max}$ point of the particular magnet material used in the design. For isotropic barium ferrite operating at $(BH)_{m\, n\, x}$ the value of B_w is 1000 gauss and H_w is 900 oersted. The above holds for all designs and magnet

materials used, but in the use of ceramic barium ferrite the high value of H_w makes practical much shorter lengths than is normal for other materials,

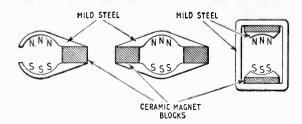


Fig. 3. Three typical methods of using anisotropic ceramic magnets as d.c. motor stators.

although greater magnet areas are required due to the lower value of B_w .

Applications - Generators and Dynamic Motors.—Despite the low value of B_w, the high coercivity of barium ferrite makes it greatly superior to other commercial permanent magnet materials in its ability to reproduce substantially the same flux after being subjected to adverse conditions. Demagnetizing fields of the order of the coercive force of the material may be applied and, upon removal, approximately 97% of the flux is recovered. Subsequently applied demagnetizing fields equal to or less than the coercive force will have no further effect on the resultant flux after removal of the demagnetizing field. From this it is seen that a magnet working at any point on the demagnetization curve after having been subjected to a demagnetizing force will return to its original working point. This unique recoil property opens up new fields in permanent magnet applications.

As outlined above, the most efficient design is achieved by operating the magnet at $(BH)_{max}$. With conventional alloys this is in the main achieved by incorporating the magnet in a flux carrying or mild steel assembly and to obtain optimum efficiency magnetization must be carried out after assembly. Owing to the favourable recoil properties of isotropic barium ferrite, magnetization may be carried out prior to assembly. This obviates the necessity for complicated and often costly magnetizing jigs

and fixtures.

In bicycle dynamos and generators using a permanent magnet rotor, it is common practice to magnetize an alloy magnet before assembly in a jig, from which it is pushed directly into a mild steel ring to act as a keeper to maintain a closed magnetic circuit. It has then to be transferred in a similar manner into the stator. When barium ferrite is used, none of these precautions is necessary as the rotor may be open-circuited after magnetization without impairing the performance of the generator. Furthermore, the rotor of such a generator or any barium ferrite magnet in any assembly may be totally removed from the circuit and replaced without the necessity to remagnetize the magnet to maintain the performance after reassembly. This allows for the assembly to be dismantled and reassembled if required.

A further property of barium ferrite arises from the combination of high coercivity and low permeability which makes it possible to place poles of opposite polarity in close proximity without progressive self-demagnetization effects occurring. As many as 24 poles can be impressed on the outer surfaces of a plain cylinder of 1in diameter. limiting factor to the number of possible poles is the difficulty of producing a magnetizing fixture to provide sufficient field to obtain magnetic saturation.

Ceramic permanent magnets may also be used in the construction of d.c. motors to provide direct current fields. Here again the high coercivity and low recoil permeability play an important part. Owing to the low flux density of this material it is necessary to provide the maximum possible magnet area in the stator, and at the same time the high coercivity enables short radial lengths to be employed. In all magnetic circuits greater efficiency is obtained by placing the magnet material as close as possible to the gap. With these considerations in mind, the simplest and most efficient method of using isotropic barium ferrite for d.c. motor fields is to have the magnet in the form of plain cylinders or segments which in themselves constitute the pole pieces (Fig. 2). In view of the low permeability of this material it is necessary to provide a low reluctance return path to complete the magnetic circuit, conveniently in the form of a mild steel ring which also serves as the motor housing. The magnetic characteristics of the material allow air gaps between three and four times those used in normal motor construction, and also allow for variations in air gap. This means that magnets in the "as fired" condition may be used, so obviating a costly internal grinding operation. For larger motors where the flux provided by isotropic barium ferrite would be insufficient, the anisotropic variety can be employed, but in this case pole pieces would normally be required in order to provide a radial Three typical constructions are shown in Fig. 3 using anisotropic magnet b ocks. Similarly, isotropic and anisotropic ceramic magnets can be

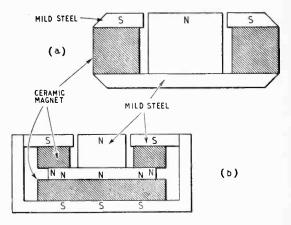


Fig. 4. (a) Ring type loudspeaker assembly (b) Pot type assembly.

used to provide the field energy for flywheel magnetos such as are commonly used in small two-stroke

Radio and Television Applications.—In the domestic radio and TV receiver field, the main use of permanent magnet is in moving coil loudspeaker assemblies. The main advantage of the ceramic magnet over the alloy magnet in this field is an economic one due to the very low cost of the raw materials used. In loudspeaker design, only the anisotropic variety is considered because the lower B_w of the isotropic material leads to designs having unwieldy and bulky dimensions.

The magnetic properties of anisotropic ceramic material lead to designs which, although having large magnet area, have exceptionally short axial length (Fig. 4(a)). This is important where space considerations are vital, as in midget portable receivers, tape recorders, etc. Two main constructions are used for loudspeaker magnet assemblies incorporating anisotropic barium ferrite, namely ring type and pot type, as shown in Fig. 4. The latter may only be used for low gap field strength assemblies, but has the advantage of having little or no external field. This factor assumes importance in television receivers where stray magnetic fields adversely affect the c.r.t. performance. This pot assembly requires a dual magnet construction in order to utilize barium ferrite to its best advantage dimensionally6. A similar magnet construction to loudspeaker assemblies is used for vibrators, moving-coil microphones, and for punch card actuators.

Extensive use has been made of ceramic magnets for television tube focusing units, the high coercivity enabling two isotropic rings axially mag-Changing the netized to be used in opposition.

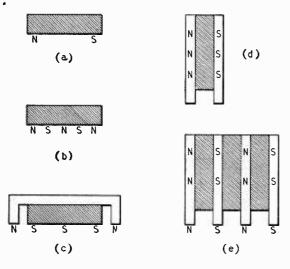


Fig. 5. Holding assemblies using ceramic magnets.

axial distance between the two rings alters the axial field strength distribution and also the working points of the two magnets, thereby changing the field strength of the magnetic lens.

Ceramic magnets are also used in conjunction with television picture tubes as ion trap and picture shift devices and as correction magnets for wide

Holding Applications.—Magnetic holding force is proportional to B2A, where B is the flux density at the contact faces, and A is the contact area. Taking for example a thin rectangular block of isotropic barium ferrite, there are several methods of utilizing this as a holding device, as shown in Fig. 5. The simplest method of magnetizing is shown in Fig. 5(a), where two poles are impressed on one contact face. Since the pull of a magnetic device is proportional to the product B2A, a greater pull is obtained by

impressing a number of poles on one face, as in Fig. 5(b). This is possible with barium ferrite due to the high coercivity which reduces the effects of selfdemagnetization. In order to achieve a higher B, advantage can be taken of the possible high magnetic saturation values of soft iron or mild steel. Typical arrangements are shown in Fig. 5(c), (d), and (e). Here it is seen that the mild steel is suitably proportioned to collect and concentrate the low density flux from a large area of magnet to provide a high flux density at the contact areas. Using a construction similar to Fig. 5(c), with an isotropic disc magnet inside a mild steel cup, an assembly 3in diameter and 7/16in deep would lift approximately 70lb, i.e. over one hundred times the assembly weight. Using an anisotropic magnet, the assembly would be 3in diameter and 3/4in deep, and should lift over 100lb. Construction Fig. 5(d) is widely used for applications like magnetic door catches as it has the advantage of occupying very little space. When used for such applications as magnetic separators, chucks and jigs, multi-assemblies as in Fig. 5(e) have the advantage of providing a greater number of poles in any given area than can be obtained using any other magnet material.

Magnets in the Presence of A.C. Fields.—The high resistance to demagnetization combined with a high resistivity allow ceramic magnets to be used in conjunction with fairly strong a.c. fields. Typical applications are vibrating armatures where the armature consists solely of ceramic magnet material. Alternatively, a mild steel armature inside an a.c. actuated coil may be used. This is made a close fit inside a ceramic magnet ring having mild steel pole pieces which polarize the central armature, so imparting a vibrationary motion. This principle is made use of in bells, small pumps, etc.

A similar principle applies to polarized relays. Other Applications.—There are many other uses for which ceramic magnets may be used with advantage due to their unusual magnetic characteristics, low weight, or for economic considerations. Amongst these may be cited: remote control services, magnetomechanical coupling possibly operating through gas-tight seals, are blowouts, snap contact switches, travelling wave tubes, synchronized artificial eyes, toys and novelties. Barium ferrite may be embodied in plastic or rubber to form a flexible magnet material for such purposes as magnetic seals, etc.

Conclusion.—From the foregoing, it is seen that the advent of barium ferrite magnets has broadened the field of applications of permanent magnets in addition to providing an economically advantageous alternative, in some cases, to conventional alloy magnets. The unique properties of this material provide a stimulus for further investigation of its many and varied possibilities.

REFERENCES

- ¹ J. J. Went, G. W. Rathenau, E. W. Gorter and G. W. van Oosterhout, *Phil. Tech. Rev.*, Vol. 13, pp.194-208, 1952.
- ² J. Smith and H. P. J. Wign, "Ferrites", Philips
- Tech. Library, Chap. IX, p.193.

 3 A. Edwards and K. Hoselitz, Electrical Review, August 4, 1944.
- ⁴ G. W. Rathenau, J. Smit and A. L. Stuijts, Zs. für Phys., Vol. 133, pp.250-260, 1952.
 - ⁵ British Patents 808,211, 726,462 and 747,724.
 - ⁶ E. Schwabe, Radio Mentor, Jan. 1958, p.32.

2.—ACTIVE NETWORKS: VALVES AND TRANSISTORS

N the first part of this article we introduced nodal analysis to new students, showing how it is complementary to mesh analysis. In mesh analysis we use constant-voltage generators and equate known voltages to find unknown current magnitudes. In nodal analysis we employ constant-current generators and equate known currents to find unknown voltage magnitudes.

In this second part we propose to indicate a method by which "active" networks (i.e. those which contain a generator such as a thermionic valve or transistor) may be solved. The method will be identical with that used for passive networks, except for one additional convention.

Network Theory with Valves.—Every student knows that although the anode characteristics of a valve are far from straight, it is still possible to work the valve in a linear mode by avoiding the lowest parts of these curves, where the curvature is worst, and by carefully selecting the position of the load line, so as to work in Class A1. If, in addition, the part of the characteristic worked over is small, we can almost certainly assume linearity with negligible error. Idealized triode and pentode characteristics are shown in Fig. 1(a) and (b).

Valve Admittance Parameters.—The primal equation for a valve is

$$i_a = f(v_g, v_a)$$
This may be immediately developed into $\delta i_a = rac{\partial i_a}{\partial v_g} \, \delta v_g + rac{\partial i_a}{\partial v_a} \, \delta v_a$

Both the partial differential coefficients have the dimensions of an admittance, hence the equation may be written

where the currents and voltages are all incremental: for our case we may say they represent the instantaneous values of the sinusoidal currents and voltages.

Conventional Development.—It is usual to develop the primal equation by specifying that a signal voltage be applied between the grid and cathode only, and that a load be placed in the anode circuit. The equation then becomes

 $g_m v_g - g_a (i_a R_l) = i_a$ where $-i_a R_l$ is the back e.m.f. across the load. g_a is then inverted and expressed as a resistance $(r_a = 1/g_a)$ and the equation easily resolves to

$$i_a = \frac{e_g g_m r_a}{r_a + R_l} = \frac{\mu e_g}{r_a + R_l}$$

where μ may or may not have a positive sign, according to the convention adopted.

The next step shows how this equation may be represented by the circuit shown in Fig. 2(a), where i_a is obviously the current flowing through the generator and load.

This, however, is only one way of interpreting the equation. Suppose we apply Norton's Theorem,

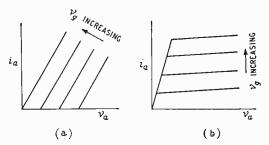


Fig. 1. Idealized triode (a) and pentode (b) characteristics.

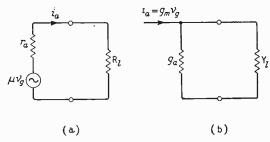


Fig. 2. Voltage (a) and current (b) generator equivalent circuits of the valve amplifier.

as we did in the first half of this article, and transform the valve from a "constant-voltage generator" to a constant-current generator. We obtain the circuit shown in Fig. 2 (b).

In this circuit i_a is the current flowing in from the generator; it has a constant value for all loads from short circuit to open circuit; in the latter case it all flows out through g_a .

Nodal Development.—Returning now to the primal valve equation, we see that it has a nodal form since it gives current in terms of voltage multiplied by admittance. Since there are two voltages there must be two significant nodes and hence two equations, one for the input and one for the output. We may immediately write down the general set of nodal equations:—

$$Y_{11}$$
 $V_1 + Y_{12}$ $V_2 = I_1$ (node 1, input)
 Y_{21} $V_1 + Y_{22}$ $V_2 = I_2$ (node 2, output)
Now a valve is an active network: it extracts

Now a valve is an active network: it extracts unidirectional energy from the power supply unit and transforms it into alternating energy. Thus we would hardly expect its nodal equations to fall out exactly as for a passive network. The differences, however, are not large.

Fig. 3 shows the basic ideal valve amplifier (no load resistor and no grid resistor) with the input and output nodes N_1 and N_2 marked in. A cursory glance at this figure will show us that $V_1 = v_g$ and $V_2 = v_a$, but I hope we will not now fall into the trap of writing $I_2 = i_a$. I_2 is the current supplied from an external generator to node 2. In this case

^{*}R.E.M.E. Electronic Engineering School, Arborfield.

there is no such generator since we have specified one generator only, feeding a signal to the grid. I_2 is therefore zero. However, it is important to note that although I_2 is zero, this does *not* mean that no current flows into node 2 at all. Actually the anode current, i_a , flows from node 1 (the grid) to node 2 (the anode) and then to earth again wing

(the anode) and then to earth again, via g_{a} .

Now what of the coefficients Y_{21} and Y_{22} in the second nodal equation? Y_{21} corresponds to current flowing into node 2 (the anode) due to a voltage at node 1 (the grid). This, by definition, is g_m . Y_{22} is the admittance in the output circuit. For the case we are considering this, by definition, is g_a . In a practical amplifier Y_{22} would include all the admittances in the output circuit, i.e. the load resistor, stray capacities etc. The second nodal equation for a valve is thus

 $g_m V_1 + g_a V_2 = 0 \text{ (node 2)}$

This is our primal equation in nodal form. We might have expected the current flowing into node 2, $g_m V_1$, to have a negative sign, so as to agree with our selected conventions. It must be remembered, however, that this current is itself negative, since increasing V_1 positively increases the flow of electrons or negative current, and a negative current flowing in a negative direction will have a positive sign.

What of the equation for node 1? The derivation of this will be quite straightforward. For the case where we have no grid resistor, and when we work in Class A1 (no grid current), I_1 must be zero. Hence, if I_1 is to be expressed in terms of V_1 and V_2 , these must both be prefixed with a nought, which gives us

 $0V_1 + 0V_2 = I_1$

This just means that the valve itself draws no current from the generator driving it. Looking in detail at the coefficients Y_{11} and Y_{12} in this equation, Y_{11} is the admittance in the input circuit. With no grid resistor this will be zero. In a practical amplifier, however, the grid admittance Y_g will appear in Y_{11} and then I_1 will have a definite value. Y_{12} corresponds to current flowing into node 1 (the grid) due to a voltage at node 2 (the anode). For the perfect valve we are considering Y_{12} must thus also be zero. (We will consider the practical case—"Miller Effect"—later.)

If we assemble our results for the ideal valve we obtain

 $0V_1 + 0V_2 = I_1 \text{ (node 1)}$ $g_m V_1 + g_a V_2 = 0 \text{ (node 2)}$

These equations show clearly the differences between active and passive networks.

(1) In a passive network Y_{12} always has the same magnitude and sign as Y_{21} . In an active network this is not so. (Here $Y_{12} = 0$ and $Y_{21} = g_m$.)

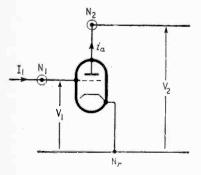


Fig. 3. Basic ideal valve amplifier.

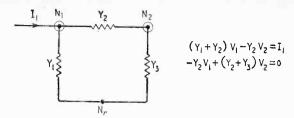


Fig. 4. Simple two-node passive network with its associated nodal equations.

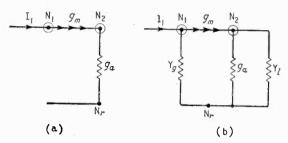


Fig. 5. Equivalent nodal circuits of a valve amplifier (a) in the ideal form of Fig. 3 and (b) with the addition of a grid admittance Y_g and load admittance Y_L

(2) In a passive network the linking admittance joining nodes 1 and 2 appears in Y_{12} and Y_{21} prefixed with a negative sign, and also in Y_{11} and Y_{22} with its normal sign. (An easy example of this is shown in Fig. 4, together with its set of equations.) In the active network this is not so. (g_m appears in Y_{21} only, and is not included in the other three parameters.)

Hence a separate sign is necessary to indicate the unilateral admittances of an active network. We could make use of the appropriate arrow symbol for a one-way street, pointing from N_1 to N_2 say for Y_{21} and from N_2 to N_1 for Y_{12} in cases where it has a value other than zero (as in a transistor). The convention would be that where a unilateral admittance appears it is only shown once, in either Y_{12} or Y_{21} , according to the arrows, and with the sign shown. For example, the equivalent diagram of a valve only, in the ideal condition, would be as shown in Fig. 5(a). The valve with a grid admittance Y_{g} and a load admittance Y_{l} would have an equivalent circuit as in Fig. 5(b).

It only remains to state that any passive elements added to an active network behave as they normally do in a passive network, even if connected across nodes one and two, when they appear in all four parameters.


We can now proceed to apply these equations, and I think you will find this much easier than the derivation of the equations!

General Case of an Active Network.—We can now obtain some standard formulae for gain, input admittance and output admittance, which will apply to all such networks, passive or active, valve or transistor.

The general nodal equations for the case when there is no external generator connected to the output (node 2), i.e. with $L_{i} = 0$, are

(node 2), i.e. with
$$I_2 = 0$$
, are $Y_{11} V_1 + Y_{12} V_2 = I_1 Y_{21} V_1 + Y_{22} V_2 = 0$

WIRELESS WORLD, DECEMBER 1960

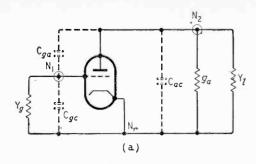

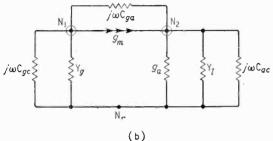


Fig. 6. Valve with interelectrode capacities (a) and its nodal equivalent circuit (b).

It can immediately be seen from the second equation that the voltage gain

$$\frac{V_2}{V_1} = -\frac{Y_{21}}{Y_{22}} = M_v$$

 $rac{V_2}{V_1} = -rac{Y_{21}}{Y_{22}} = M_v$ Similarly the short-circuited (output) current gain

$$\frac{\overline{I_2}}{V_1} \times \frac{V_1}{I_1} = \frac{Y_{21}}{Y_{11}} = M_i$$

The input admittance of the network, which can include the load, may be found from the equations as follows. From the second equation $V_2 = -Y_{21} V_1$

Y₂₂ and substituting this into the first equation gives
$$Y_{11} V_1 - \frac{Y_{12} Y_{21}}{Y_{22}} V_1 = I_1$$
Thus $Y_{in} = \frac{I_1}{V_1} = Y_{11} - \frac{Y_{12} Y_{21}}{Y_{22}} = Y_{11} + M_v Y_{12}$
Conversely, the "looking-back" admittance at the output will be

Conversely, the "looking-back" admittar output will be
$$Y_0 = Y_{22} - \frac{Y_{12} Y_{21}}{Y_{11}} = Y_{22} - M_i Y_{12}$$

From these equations we can see that the load only affects the source admittance, and vice versa, if both Y_{12} and Y_{21} have values (i.e. neither are zero).

Simple Valve Amplifier.—The nodal equations for the valve under ideal conditions are

$$\begin{array}{ll} 0 \ V_1 + 0 \ V_2 = I_1 \ g_m \ V_1 + g_a \ V_2 = 0 \ & \text{The voltage gain} = -g_m/g_a = -g_m \ r_a = -\mu. \end{array}$$

The nodal equation brings out clearly to the new student the fact that the valve amplification factor is merely the ratio of two admittances.

Now take a simple amplifier, with anode load Y_l . Since the valve is being treated as a current generator the load will appear in parallel with the generator admittance. If we include the grid resistor $(1/Y_g)$ our equivalent diagram will be as in Fig. 5(b), and our equations will become

$$Y_g V_1 + 0 V_2 = I_1$$

$$g_m V_1 + (g_a + Y_l) V_2 = 0$$
The voltage gain
$$M_v = -\frac{Y_{21}}{Y_{22}} = \frac{-g_m}{g_a + Y_l}$$
Unformitian Characteristics

$$M_v = -\frac{Y_{21}}{Y_{22}} = \frac{-g_m}{g_a + Y}$$

Unfamiliar? Change the admittances to impedances and

$$M_v = \frac{-g_m}{\frac{1}{r_a} + \frac{1}{R_l}} = \frac{-g_m}{\frac{R_l + r_a}{R_l + r_a}}$$

$$= \frac{-g_m r_a R_l}{R_l + r_a} = \frac{-\mu R_l}{R_l + r_a}$$
which is familiar to everyone—yet not as simple.

If Y_i should be complex, say $g_i + jB_i$, then

If
$$Y_l$$
 should be complex, say $g_l + jB_l$, then
$$M_v = \left| \frac{g_m}{\sqrt{(g_a + g_l)^2 + B_l^2}} \right| / 180^\circ - \theta$$
where $\theta = \arctan \frac{B_l}{g_a + g_l}$

Calculation of Miller Effect .- Due to interelectrode capacitance a valve, particularly a triode, is not truly unilateral at high frequencies, but does transfer some energy from the output to the input, and so modify the input admittance of the valve. The basic circuit and its equivalent are shown in Fig. 6(a) and (b) and the pair of nodal equations will be

$$\begin{array}{l} \left[\mathbf{Y}_{g} + \mathrm{j}\omega \left(\mathbf{C}_{g\,c} + \mathbf{C}_{ga} \right) \right] \mathbf{V}_{1} - \mathrm{j}\omega \mathbf{C}_{g\,a} \, \mathbf{V}_{2} = \mathbf{I}_{1} \\ \left[\mathbf{g}_{m} - \mathrm{j}\omega \mathbf{C}_{g\,a} \right] \mathbf{V}_{1} + \\ \left[\mathbf{g}_{a} + \mathbf{Y}_{l} + \mathrm{j}\omega \left(\mathbf{C}_{a\,c} + \mathbf{C}_{g\,a} \right) \right] \mathbf{V}_{2} = 0 \end{array}$$

The voltage gain

$$M_{v} = -\frac{Y_{21}}{Y_{22}} = -\frac{g_{m} - j\omega C_{ga}}{g_{a} + Y_{l} + j\omega (C_{ac} + C_{ga})}$$

The input admittance
$$Y_{in} = Y_{11} + M_v Y_{12}$$

$$= Y_g + j\omega(C_{gc} + C_{ga}) - j\omega C_{ga}|M_v|$$

$$- 180° + \phi$$

$$= Y_g + j\omega C_{gc} + \omega C_{ga}(1/90° + |M_v|$$

$$- 90° + \phi$$

This is the normal equation for the input admittance of a triode amplifier at radio frequencies; we have found it, together with the gain, in a few lines of working. Other examples of valves working with grounded cathode can be solved in the same manner.

Grounded-Anode Stage (Cathode Follower).-

Let us now examine the grounded-anode stage. Here, due to the valve being inverted, the nodal equations must be modified. The primal equation, $i_a =$ $g_m v_g + g_a v_a$ always applies, whatever the configuration. Referring to Fig. 7 we see that $v_a = -V_2$, and since $v_{ac} = v_{ag} + v_{gc}$, then $v_{gc} = v_{ac} - v_{ag} = -V_2 - (-V_1)$. Hence $i_a = -g_m (V_2 - V_1) - v_2 - (-V_1)$ g_aV₂. Allowing for the reversed direction of i_a, the nodal equations then become

$$\begin{array}{l} 0 \text{ V}_1 + 0 \text{ V}_2 = \text{I}_1 \\ -g_m \text{ V}_1 + (g_m + g_a) \text{ V}_2 = 0 \end{array}$$

These equations are easily remembered, whilst the procedure for finding the gain etc., is exactly as before. Let us draw the circuit of a typical cathode follower and its equivalent, and then write down the nodal equations. The circuits are shown in Fig. 8(a) and (b) and the nodal equations are

$$\mathbf{Y}_{g}\mathbf{V}_{1}+\mathbf{0}\ \mathbf{V}_{2}=\mathbf{I}_{1} \ -\mathbf{g}_{m}\mathbf{V}_{1}+(\mathbf{g}_{m}+\mathbf{g}_{a}+\mathbf{Y}_{k})\ \mathbf{V}_{2}=\mathbf{0}$$

WIRELESS WORLD, DECEMBER 1960

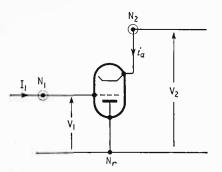


Fig. 7. Basic ideal grounded-anode valve (cathode follower).

$$M_v = -\frac{Y_{21}}{Y_{22}} = \frac{g_m}{g_m + g_a + Y_k}$$

This is obviously less than one. Typical values may be, $g_m = 2.5$ milliamps per volt, $g_a = 100$ micromhos and $Y_k = 100$ micromhos. The gain is then 0.925.

If the gain equation is transformed into impedances we obtain for the voltage gain

$$M_v = \frac{\left(\frac{\mu}{1+\mu}\right) R_k}{\left(\frac{r_a}{1+\mu}\right) + R_k}$$

This is the familiar equation, which shows voltage

negative feedback.

Since Y_{12} is zero, the input admittance is just Y_g and the output admittance $g_m + g_a + Y_k$. However, things become quite different if Y_g is connected between grid and cathode (i.e. between nodes 1 and 2). The input admittance then falls to about one-tenth of Y_g and the output admittance is now no longer independent of the input admittance. Why not work it out for yourself? There are some good notes by J. McG. Sowerby in the Wireless World for September, 1948.

The behaviour of the cathode follower at high frequencies can be studied by including the inter-

electrode and other capacitances.

Grounded-Grid Amplifier.—Since the procedure followed is identical with that for the cathode follower, the explanation will be curtailed. Referring to Fig. 9 we see that $v_g = -V_1$ and $v_a = V_2 - V_1$. Substituting we find that $i_a = -(g_m + g_a)V_1 + g_aV_2$. Now I_1 must have the same magnitude as i_a (there being no grid current). Therefore it should have the same coefficients as i_a , but with the signs changed, since current flowing out of node 1 is positive, whereas the same current flowing into node 2 is negative. Hence our nodal equations are

$$(g_m + g_a) V_1 - g_a V_2 = I_1$$

 $-(g_m + g_a) V_1 + g_a V_2 = 0$
A simple circuit and its equivalent are shown in

$$\mathbf{1}_{k} + g_{m} + g_{a} \mathbf{1}_{1} - g_{a} \mathbf{1}_{2} = \mathbf{1}_{1} - (g_{m} + g_{a}) \mathbf{1}_{1} + (g_{a} + \mathbf{1}_{1}) \mathbf{1}_{2} = 0$$

$$\mathbf{1}_{k} + g_{m} + g_{a} \mathbf{1}_{1} + (g_{a} + \mathbf{1}_{1}) \mathbf{1}_{2} = \mathbf{1}_{1}$$

$$\mathbf{1}_{k} + g_{m} + g_{a} \mathbf{1}_{2} + (g_{a} + \mathbf{1}_{1}) \mathbf{1}_{2} = \mathbf{1}_{1}$$

A simple circuit and its equivalent and its Fig. 10(a) and (b). Its equations are $(Y_k + g_m + g_a) V_1 - g_a V_2 = I_1 \\ -(g_m + g_a) V_1 + (g_a + Y_l) V_2 = 0$ The voltage gain $-\frac{Y_{21}}{Y_{22}} = \frac{g_m + g_a}{g_a + Y_l}$

If Y_l and g_m are much larger than g_a , this gain approximates to g_m/Y_l or g_mZ_l .

The input admittance will be $Y_{11} + M_v Y_{12}$ or approximately $Y_k + g_m$, for the same conditions as the gain

the gain.

Indefinite Admittance Matrix.—All the basic valve configurations have now been dealt with. We will conclude this section by giving a mnemonic to enable you to remember the three sets of equations.

First write down the admittance parameters of the common-cathode valve configuration in the position they normally occupy in the equations. We get

Now add a third column (on the right) and a third row (underneath) in such a way as to make the sum of every column or row zero. Lastly mark the rows and columns G, A and C, as shown.

G G $\begin{array}{ccc}
g_a & -(g_m + g_a) \\
-g_a & (g_m + g_a)
\end{array}$ A Ĉ

C $|-g_m| - g_a$ $(g_m + g_a)$ For grounded-cathode working strike out the third (C) row and column. This brings us back to where we started, viz.

 g_m

For grounded-anode working strike out the second (A) column and row, which gives

This agrees with the values already found.

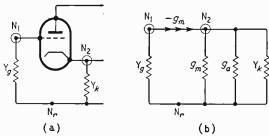


Fig. 8. Typical cathode-follower (a) and its nodal equivalent circuit (b).

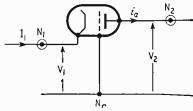


Fig. 9. Basic ideal grounded-grid valve.

Lastly, for grounded grid, we cross out the first (G) row and column to obtain

This places the anode in the top left-hand corner, which is input, and the cathode in the bottom righthand corner, or output. We therefore make a diagonal changeover of all four parameters to get

$$\begin{array}{ccc}
(g_m + g_a) & -g_a \\
-(g_m + g_a) & g_a
\end{array}$$

This again agrees with the values previously found. You may protest that these equations are easy enough to remember without this mnemonic; if so I would agree. The real reason they were brought in here was to show that the method gave the right (Continued on page 603)

602

Wireless World, December 1960

answers with a valve. We will soon use the same method to convert a common-emitter configuration transistor to common collector or common base. The real justification for this method lies in matrix theory, and is due to J. Shekel1. This subject, however, is outside the scope of the present article.

Transistor as an Active Network.—The transistor, like the thermionic valve, is an active two-node network and as such its manipulation and basic equations for gain and input and output admittance are the same as the valve. Once we have obtained the nodal equations for the transistor the rest is merely a repetition of what we did with the valve.

Derivation of Transistor Parameters.-Following common practice, we will first consider the transistor in common base. The transistor collector curves, shown in Fig. 11(a) strongly resemble the pentode anode characteristics shown in Fig. 1(b), with one subtle difference. Whereas each separate curve on the valve characteristic represents a certain grid voltage, on the transistor collector characteristic each curve represents a certain emitter current. This makes quite a difference to the resulting equations. We must now say

 $i_c = f(i_e, v_c)$

Our other parameter, the emitter voltage, must then also be expressed in terms of the same variables. Once again we get equations of the form

$$\begin{array}{l} \delta v_e = \frac{\partial v_e}{\partial i_e} \quad \delta i_e + \frac{\partial v_e}{\partial v_c} \quad \delta v_c \\ \delta i_c = \frac{\partial i_c}{\partial i_e} \quad \delta i_e + \frac{\partial i_c}{\partial v_c} \quad \delta v_c \end{array}$$

 $\partial v_e/\partial i_e$ is dimensionally an impedance and we may replace it with r_{11} . Similarly $\partial i_e/\partial v_e$ is dimensionally a conductance and may be replaced by g_{22} . On the other hand $\partial v_e/\partial v_c$ is a mere ratio between two voltages, let us use μ_r for this, where the subscript means "reverse" (voltage fed back to input). In the same way $\partial i_c/\partial i_e$ is the forward current gain and its symbol is usually α .

Our set of equations thus becomes

$$egin{aligned} \mathbf{r_{11}} i_e + \mu_r v_e &= v_e \ lpha i_e + \mathbf{g_{22}} v_c &= i_c \end{aligned}$$

with the signs depending on the convention employed. By the reasoning employed in the first article, r_{11} and α are measured with the output short circuited to a.c. whereas μ_r and g_{22} are measured with the input open circuited to a.c.

Now it happens that in matrix theory there is a set of equations of the form

$$H_{11} I_1 + H_{12} V_2 = V_1$$

H₁₁ $I_1 + H_{12} V_2 = V_1$ H₂₁ $I_1 + H_{22} V_2 = I_2$ which is of the same basic form as those we have just derived. Thus the next step was to substitute H_{11} for r_{11} , H_{12} for μ_r , H_{21} for α and H_{22} for g_{22} . It wasn't really necessary, but you must admit it looks good and is calculated to baffle the most pertinacious student. Indeed we have now reached a dead end and will have to transform these " hybrid " parameters (from the H and the mixed dimensions) into admittances, similar to the valve, if we wish to attack transistor problems without the aid of a course in memory training.

We can easily transform the H parameters into Y by the aid of simple algebra, but if the transistor manufacturers would quote these values it would save us the trouble.

Wireless Engineer, Jan. 1954, p. 6.

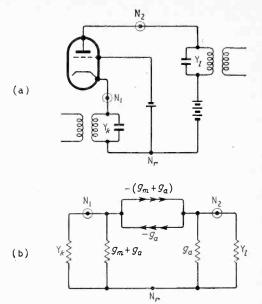


Fig. 10. Simple grounded-grid amplifier (a) and its nodal equivalent circuit (b).

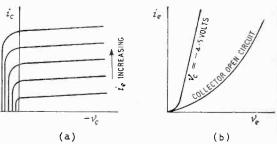


Fig. 11. Common-base characteristics of the transistor (a) at its output and (b) at its input.

From the first equation we can quickly obtain

$$I_1 = \frac{1}{H_{11}} \, V_1 - \frac{H_{12}}{H_{11}} \, V_2$$


Substituting this into the second equation we get
$$I_2 = \frac{H_{21}}{H_{11}} V_1 + \frac{|H|}{H_{11}} V_2$$

Where $|H| = H_{11} H_{22} - H_{12} H_{21}$

$$Y_{11} = \frac{I}{H_{11}}, Y_{12} = -\frac{H_{12}}{H_{11}}, Y_{21} = \frac{H_{21}}{H_{11}}, Y_{22} = \frac{|H|}{H_{11}}$$

Transistor manufacturers usually publish a set of H parameters for common-emitter, common-collector and common-base working-three sets-for each transistor.

It is common for teachers and lecturers to approach transistors from the common-base viewpoint, but in practice the common-emitter configuration is far more common. We will therefore give our example on the common-emitter configuration. Commonemitter parameters may be found in the same way as common base, and they are always given by transistor manufacturers. In any case it is always possible to transform from one configuration to another.

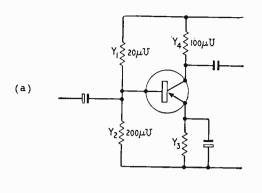

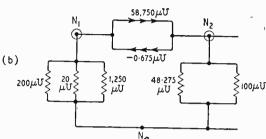


Fig. 12. Common-emitter transistor current amplifier (a) and its nodal equivalent circuit (b) ($\sigma \equiv mho$).

Common-Emitter Transistor Amplifier.— Mullards give the hybrid parameters of their OC 71 transistor in common emitter as

 $H_{11} = 800 \text{ ohms}, H_{12} = 5.4 \times 10^{-4} \ H_{21} = 47, \qquad H_{22} = 80 \times 10^{-6} \text{ mhos}$ The admittance parameters work out to $Y_{11} = 1,250, Y_{12} = -0.675$ all figures in $Y_{21} = 58,750, Y_{22} = 48.275$ micromhos Consider the amplifier shown in Fig. 12(a). A little consideration will show that both Y_1 and Y_2

are in parallel across the input, whilst Y4 is obviously across the output. The equivalent circuit is then as in Fig. 12(b).

The voltage gain is still

$$M_v = -\frac{Y_{21}}{Y_{22}} = -\frac{58,750}{148.275} = -396$$

The current gain, with output short circuited to a.c.

$$M_i = \frac{Y_{21}}{Y_{11}} = \frac{58,750}{1,470} = 40$$

The input admittance

$${
m Y}_{in} = {
m Y}_{11} - rac{{
m Y}_{12} {
m Y}_{21}}{{
m Y}_{22}} = {
m Y}_{11} + {
m M}_{m v} {
m Y}_{12} = 1{,}737~\mu {
m mhos}$$

The "looking-back" admittance at the output

$$Y_o = Y_{22} - \frac{Y_{12}Y_{21}}{Y_{11}} = Y_{22} - M_iY_{12} = 175.3 \,\mu \text{ mhos}$$

Perhaps you will agree that once the admittance parameters have been worked out, or obtained from manufacturer's data, the actual work involved in finding the gain, etc., is small.

Transistor in Common Collector and Common Base.-If one wishes to obtain the performance of a transistor in common collector (near equivalent to the cathode follower) or common base (equivalent of grounded grid), the admittance parameters for these configurations can easily be obtained from those

of the grounded-emitter admittances, without recourse to the hybrid parameters again. We employ the indefinite admittance matrix, as we did for the valve, using a modification of the method devised by Shekel².

First write down the admittance parameters of the common-emitter configuration, in the positions which they normally occupy in the equations. Now add a third column (on the right) and a third row (underneath) in such a way as to make the sum of every column or row zero. Lastly mark the rows and columns, B, C and E. I have done it for the OC 71.

To obtain common-emitter parameters strike out the E row and column. (This brings us back to our starting point, of course.)

To obtain the common-collector parameters strike

out the C row and column. This leaves 1,250 -1,249.325 all is all in all in micromhos -60,000 60,047.6 which are the admittance parameters for the OC 71 when used in grounded collector. They are used exactly as were the valve admittance parameters in the cathode follower.

For the common-base configuration we strike out the first (B) row and column. This gives the collector in the top left-hand corner, which is input, and the emitter in the bottom right corner, or output: our transistor is connected the wrong way round. It is therefore necessary to make a diagonal switch of all four parameters which gives

Again, these common-base parameters may be used to find gain, input admittance and output admittance exactly as shown for the common emitter, or for that matter, the valve.

Conclusion and the Shape of Things to Come.— This then is nodal analysis as applied to passive and active networks. The basic procedure is the same for passive, valve or transistor circuits, which should be of considerable help to students. Only a few examples of its use are shown, it really is a powerful method: however, it does not supersede

mesh analysis, but is complementary to it.

And where do we go from here? The next step would be a study of four-terminal networks, using matrices, assisted by determinants. If you should be interested in the transient case, nodal analysis may still be very helpful, in conjunction with Laplace transforms, and will tell you whether a network is stable or unstable, and what sort of response (current) will occur as a result of an externally applied stimulus (which is commonly non-sinusoidal)3.

However, leave these latest methods until you are quite familiar with mesh and nodal analysis: between them they will take you a long way, especially the latter!

This article is published with the permission of Lt. Col. J. Harris, C.O., 3 Trg. Bn., R.E.M.E. Arborfield.

² Proc. I.R.E., Nov. 1952, p. 1493.

See, for example, "Linear Feedback Analysis", by J. G. Thomason (Pergamon Press).

Camera Remote Control

USED IN B.B.C. REPORTING STUDIOS

By G. W. H. LARKBY*

N recent years the stability of vidicon cameras has improved to the degree that it is now possible to use them without the attention of technical operators. The first example of the use of an unattended camera in this fashion was, in fact, in the B.B.C.'s Parliamentary Reporting Studio at Westminster which was put into service about a year ago.

This studio is as simple as it is possible to conceive a television studio to be, consisting of a small room furnished with a table and chair, lights, microphone and a single television camera in a fixed position. The studio is brought into action by remote control from the Television News Studio at Alexandra Palace where the received signal is "mixed" into the programme. The operational success of this facility, simple as it is, stimulated a demand to be able to control the main positional functions of the remote camera in order to give variety to the In turn, the development of the presentation. apparatus for this positional control has led to the provision of a facility whereby the camera can be made to take up any one of a number of pre-set "shots" by the operation of a push-button switch, which may, if desired, be operated by the "subiect" himself.

The camera functions which require to be controlled are horizontal angle (pan), vertical angle (tilt), angle of view (focal length of lens), camera focus and lens aperture. In order to avoid a hiatus in the picture while changing the focal length of the lens, advantage can be taken of a zoom lens.

As a field experiment, a vidicon camera has been fitted with a zoom lens and is installed in the B.B.C.'s studio in All Souls Hall, near Broadcasting House, and the camera can be controlled in all its main functions, either from the local control room or from the control room at

Alexandra Palace, some seven REMOTE STATION miles away.

The camera is a standard vidicon, of a type in general use in interview studios where it is normally fitted with a four-lens turret. For the purpose of this experiment, the turret was removed and replaced by a cast plate on which is mounted the zoom lens together with the motor mechanisms for the zoom, focus and iris movements.

The servo system employed is shown in Fig. 1. The two potentiometers, A and B, form a bridge circuit of which the potential difference, at d.c.,

between points A and B, is fed to a modulator, which detects the potential difference between these two points and provides a correcting signal which, in turn, operates a motor so that the two points are brought as nearly as possible to the same potential. The modulator circuit employed is the well-known "ring" connection of four diodes to which, in addition to the d.c. control voltage, a constant 50 c/s e.m.f. is also connected. In order to keep harmonics in the output voltage to a reasonably low level the amplitude of the 50 c,'s applied to the modulator is relatively low. It can be seen from the symmetry of the circuit that at balance, i.e., when A and B are at the same potential, there will be no 50 c/s output from the bridge into the control amplifier. On the other hand, when potentiometer A is moved, say to give a current flowing in the direction from B to A, diodes M1 and M3 conduct, causing the 50 c/s e.m.f. in transformer T1 to send a current through the centre-tapped winding of the transformer T2, producing an output in a particular phase. Movement of potentiometer A in the other direction, so as to cause a current to flow from A to B, makes diodes M2 and M4 conduct and, as compared with the previous condition, reverses the connection of the e.m.f. in transformer T1 to the terminals of transformer T2. Thus the phase of the output of the voltage from T2 changes by 180° as the direction of current between A and B reverses. Accordingly, the motor can run in either direction, depending upon the position of potentiometer B relative to potentiometer A. The a.c. output from the bridge is amplified and drives the servo control motor, which will always attempt to keep the bridge

^{*} B.B.C. Designs Department.

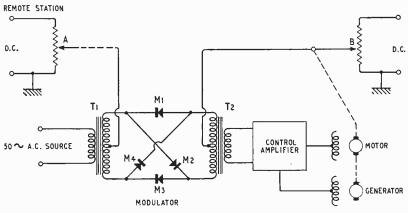


Fig. 1. Servo system schematic used for the remote control of a television camera.

Wireless World, December 1960



Fig. 2. Servo motors, zoom lens, etc., mounted in place of the normal four-lens turret. These are enclosed in a cover which also forms a lens hood.

in balance. Thus, any movement of the control knob results in an equal movement of the controlled potentiometers as the motor drives the bridge into balance. Coupled to the motor shaft is a generator which produces an output of voltage proportional

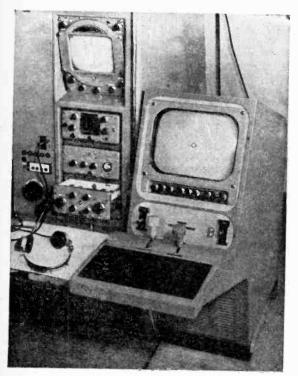


Fig. 3. Remote control console. The two large knobs control focus and zoom (left) and tilt and pan (right).

to the speed which is fed into the servo amplifier and so adjusted as to make the whole system critically damped. The action is very nearly dead beat giving the operator the impression that the knob is directly coupled to the mechanism which it operates and he has little or no feeling that it may well be many miles away.

The use of d.c. for the control current has the advantage that for short distances, say of the order of 10 miles, low quality circuits may be used. The system as installed between Alexandra Palace and All Souls Studio makes use of phantom circuits superimposed on existing speech and music circuits. For longer distances on which a d.c. loop is not available, it would be necessary to translate the control signals to audio frequencies, at which they can

be conveniently transmitted.

The control amplifiers are four identical transistorized units capable of giving a continuous output of 20 watts each. They are driven from a stabilized 24-volt power supply. The amplifiers are straightforward audio amplifiers with emitter follower driven Class B output stages, the transistors being OC71, OC71, OC72+OC72 driving 2N268+2N268. There are two controls, i.e., gain and velocity feedback, thus allowing the performance of any function to be varied at will.

The lens fitted has a minimum focus of 4 feet with a maximum aperture of f/2.8. The movement of the knurled operating rings required to go from minimum to maximum of all three functions of the lens is approximately 180°, and the preliminary design called for an operational time of 5 seconds end to end. This sets the reduction gear ratio for the servo motor, the stalled torque necessary at motor shaft being sufficient to overcome the friction of the mechanism. In view of the experimental nature of this camera only two positional servos were used on the lens, i.e., focus and zoom. The iris is controlled by a non-servo type of small reversible motor of low torque, end stops being used to limit travel. The servo balance potentiometers are mounted on the penultimate drive shaft; the final drive to the lens is by neoprene toothed timing belts. These belts have built-in flexible steel wires which prevent stretch, the teeth giving positive drive so that a minimum of side loading is required and they are silent in operation.

All the connections to the motors, etc., are brought out to a multi-way plug on the side of the plate. A cover with acoustic damping fits over the whole assembly and also operates as a lens hood.

The camera and lens assembly is mounted on a panning tilt head which has a tilting centre above the camera mounting platform so that the centre of gravity of the camera can be placed at this point, thereby making the whole assembly inherently balanced. The camera tilt mechanism consists of a sector of a circle whose centre is above the camera mounting surface. Gear teeth are cut in the curved underside of this sector and mesh with a transverse This mechanism can be seen in driving shaft. Fig. 2.

A servo motor is fitted to both pan and tilt mechanisms. The error detector in the tilt servo is a carbon track potentiometer geared to the transverse shaft, but that in the pan is a three-turn potentiometer to give adequate resolution. Velocity feedback is achieved by using a generator on the same shaft as the motor, as in the focus and zoom unit.

The pan motion uses an 8mm roller chain with a spring-loaded jockey pulley. In this case the driven chain wheel is fixed to the tripod head and the motor and driving pulley drive themselves round the head carrying the camera with them. The use of this method permits a change of gear ratio to be used without the use of large, expensive, special

For continuous operation of the camera controls at the remote point, the operator sits at a console on the front of which are two knobs; each of these is moved in two modes: (a) rotation, (b) fore and aft like a lever. On the right-hand knob the rotation corresponds to pan and the fore and aft motion to tilt; on the left-hand knob the rotation corresponds to focus and the fore and aft to zoom (see Fig. 3). With a little practice, by the use of both hands the operator can control all four functions of the camera smoothly and comfortably.

It was soon apparent that to give smooth control, some form of damping on the motion is required, and this is provided by discs immersed in a silicone fluid rotating in a close-fitting chamber. The physical operation of each of these controls turns a potentiometer which forms part of the bridge of

the appropriate servo mechanism.

Because the setting of any of the camera functions can be represented by the position of a potentiometer, by arranging to switch to groups of potentiometers, it is possible to give the camera a number of pre-set "shots." For example, Shot No. 1 might consist of a general view showing two people in conversation, Shot No. 2 would then be a close-up of the interviewer and Shot No. 3, perhaps, a close-up of the person being interviewed. On the operation of a push button, the camera can

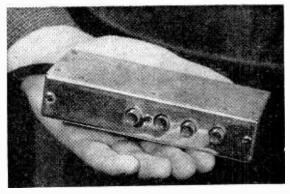



Fig. 4. "Shot-box" for the control of a camera by an interviewer.

be made to take up any of these shots at will. This leads to the possibility in studios where the programme is of a pre-set nature of using say, two remotely controlled cameras which look in turn at the appropriate "shots" under the control of the vision operators in the control room without having to have studio cameramen at all.

To pre-set any particular shot, it is only necessary to adjust the corresponding potentiometers for pan, tilt, focus and zoom, there being a group of four such potentiometers for each shot required. On the experimental camera the four positions on the "shot-box" control have proved adequate and useful. Visitors to one of the B.B.C. stands at the Earls Court Radio Show had the opportunity of manipulating a camera in this manner.

SHORT-WAVE CONDITIONS

Prediction for December

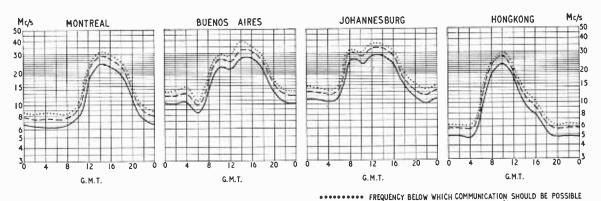

THE full-line curves indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during December.

Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.

FOR 25% OF THE TOTAL TIME

FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

Transistorized Wien Bridge Oscillator

ON PAGE 390 of the August issue Mr. Butler says, "There is little point in using RC oscillators at frequencies much higher than 100kc/s, since it is simpler

and cheaper to use switched tuned circuits.'

Perhaps Mr. Butler would care to expand on this statement, since (1) there is some merit in being able to have sweep or continuous tuning. The usual Wien network oscillator has a continuous 10:1 frequency sweep, and this is not normally achieved in an LC tuned system and, (2) there are several RC oscillators commercially available extending beyond 100 kc/s.

Dorking, Surrey.

D. J. COLLINS

The author replies:

I AGREE with Mr. D. J. Collins that a normal LC oscillator will not cover the 10:1 frequency range of an RC oscillator and that there are occasions when this wide coverage is of value in experimental work. Nevertheless the chief merit of the RC oscillator lies in the lower frequency part of the spectrum where LC oscillators require large and inconvenient tuning elements. At higher frequencies LC oscillators with continuously variable tuning elements have these advantages:

(a) Low distortion due to the use of high Q com-

ponents

(b) High efficiency as compared with RC oscillators. (c) Satisfactory operation from low voltage unregu-

lated power supplies.
(d) High stability of frequency can be obtained in a simple way, e.g., by the use of capacitors having a negative temperature coefficient to offset the positive coefficient of the associated inductance.

(e) Distortionless amplitude control is easy to apply.

(f) Pulsed or modulated operation is possible.

(g) For a given scale length, the frequency of an LC oscillator covering a 3:1 range can be read more accurately than that of an RC oscillator covering a 10:1

As stated in my paper, there is no difficulty in adding an extra range covering up to 200 kc/s if this is required. For distortionless operation at such high frequencies it is desirable to use v.h.f. transistors. This is because of difficulties due to hole-storage effects in transistors which have relatively low alpha cut-off frequencies. Moreover, v.h.f. transistors have a much lower collector capacitance. This parameter is dependent on temperature and on the collector voltage and is responsible for a variable amplifier phase shift which affects the frequency.

Mr. Alan Carpenter's fixed frequency 100 c/s oscillator (October issue) embodies some interesting design features and is outstandingly good in respect of frequency stability. At this low frequency, variation of transistor characteristics (like input and output capacitance) can be swamped by the much larger capacitances in the bridge elements. Even so, to achieve a stability better than I part in 1,000 is an excellent result.

My only criticism of the circuit is perhaps a trivial one. It concerns the method used for amplitude stabilization. As Mr. Carpenter states, the low heater resistance of the indirectly-heated thermistor shunts the emitter load of V3 and absorbs considerable signal power, at the same time introducing a rather long time constant into the control circuit operation. Although a 100 µF capacitor is used in the feedback circuit there

is a phase shift of about 10 degrees in the feedback voltage due to the associated 100-ohm heater element. In my experience, the actual capacitance of large electrolytics is sometimes well below the nominal value and it tends to vary with time and temperature. This would cause minor frequency fluctuations in the oscillator output of the kind Mr. Carpenter has mentioned. I am almost certain that the use of an R₅₃ or, perhaps, better, an R₁₄, directly heated thermistor would cure this trouble and also give a more effective control of amplitude.

There is, however, an entirely different way of using an indirectly heated thermistor for control purposes if the long time constant is acceptable. It involves the use of an extra transistor stage as a Class B amplifier in which the thermistor heater forms the collector load. A suggested circuit is shown in Fig. 1 in which V3 is the last stage of Mr. Carpenter's amplifier and V4 is the power amplifier stage used to energize the thermistor heater. The virtue of this arrangement is that V4 is completely outside the main amplifier and feedback

The function of V4 is merely to supply heater power proportional to the main oscillator output power. A Class B amplifier is suggested because in this case there is no initial heating of the thermistor by a standing collector current in V4. Use of a Class C connection might be still better, for then there would be no thermistor heating until the oscillator output reached a definite threshold level sufficient to overcome the initial reverse base bias of V4. Where low distortion is important it is just possible that the non-linear input impedance of V4 might prove objectionable but this effect could be minimized by including a moderately high series resistance in the base circuit of V4.

When fixed frequency operation of an oscillator is required there is a great deal to be said in favour of


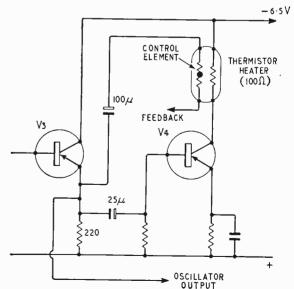


Fig. 1. Use of separate power amplifier for thermistor

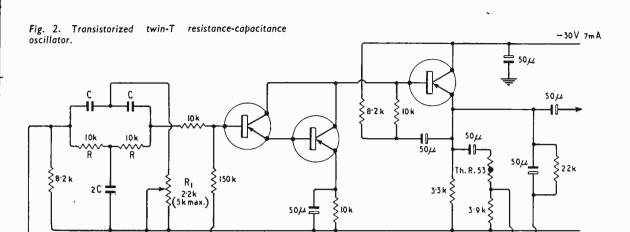

the twin-T RC circuit. This is in effect an equivalent of the Wien bridge which has a common input and output terminal. Reference (2) of my original article concerns a valve oscillator of this type, described by A. R. Bailey. The writer has developed a transistor version of Bailey's circuit, shown in Fig. 2. Space limitations preclude a full description of this arrangement but its salient features are the same as for the valve-operated version. Due to the use of high amplifier gain and a large amount of negative feedback the performance is outstanding in respect of low distortion and high frequency stability. For variable frequency operation the circuit is less attractive since it calls for the use of three ganged variable resistances one of which differs in value from the other two. Coarse changes of frequency are made by changing the capacitors C, C and 2C shown on the diagram. Mr. Carpenter may find the circuit useful for his timing standard. Regarding the super-alpha circuit used in my two designs, readers may care to note a brief reference to this compound-connected pair in the book "Transistor Circuit Engineering," (pp. 131-133), edited by R. F. Shea and published by Wiley.

In conclusion it may be of interest to mention a few points concerning the performance of the original Wien bridge oscillator. As regards its output level, measurements made on a version using a Standard Telephones Type R₁₄ thermistor as TH.2 and a Type A as TH.1 show that the output is exactly the same over the two low-frequency ranges. On the highest frequency range this remains so up to a frequency of 13 kc/s. Between 13 and 20 kc/s the output falls slowly, dropping by 4 per cent (about one third of a decibel) at the highest frequency. Harmonic distortion is 1.2 per cent for 1

volt output at 1000 c/s.

There is a small change of frequency if a reactive load is connected across the output terminals. To remove this it would be necessary to use an emitter follower as a final output stage. Another OC 72 would be

suitable for use in this position.


Finally, an earlier letter from Messrs. Evans and Williams, to which I replied in the October issue of Wireless World, cast some doubt on the performance of the super-alpha circuit at temperatures in excess of 30°C. This point has been checked by the crude expedient of holding a hot soldering iron near the casing of the first transistor VI until it became uncomfortably hot to touch. Under these circumstances the total supply current dropped by about 10 per cent (due to the use of three d.c. coupled stages) but there was no noticeable change in the output level of waveform and only an insignificant change in frequency. No trouble from this source need be anticipated, using germanium transistors, at normal room temperatures. For use at very high temperatures it might be desirable to use silicon devices in this or any other comparable circuit.

Cheltenham. F. BUTLER

THERE is an alternative method of using RC tuning networks which avoids the difficulties arising from the low input impedance of a transistor which were pointed out by Mr. Butler in the August issue. It is to connect the networks as current attenuators rather than voltage attenuators. (See D. E. Hooper and H. E. Jackets, "Current Derived Resistance Capacitance Oscillators using Junction Transistors," Electronic Engineering, August 1956.)


To operate a Wien type network in this way, an input current is applied to what are normally the output terminals, and an output current is taken from what are normally the input terminals. The frequency at which there is no phase shift is unaltered, and the current attenuation is the same as the voltage attenuation of

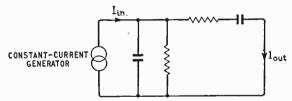the usual connection. When the network is used in this way, the input



current must be supplied by a high-impedance source, such as a common-base transistor, and the output current must be supplied to a low-impedance load: again, a common-base transistor is indicated, though a common-emitter stage can be made to serve. Under these conditions, the effect of the maintaining amplifier on the frequency of oscillation is small, just as it is in voltage-operated circuits when the input voltage source has a low impedance and the output voltage is supplied to a high-impedance load.

A difficulty of current operation is that the resistance element of the parallel arm forms the d.c. collector load of a transistor. The value of resistance which can be used is then limited by considerations of supply voltage. This problem can, however, be avoided by using an RL network instead of an RC network. The collector current then flows through an inductor, as shown in the diagram, and there is only a small voltage drop. With resistances and inductances of equal value the frequency of oscillation is $R/2\pi L$. A danger in RL circuits is that the self-resonance of the chokes might provoke oscilla-

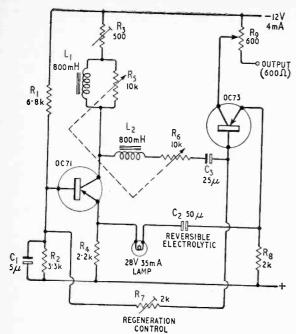

tion at the wrong frequency. In general, the risk can be reduced by making R as small as possible. When this is done, the resistance of the load, which comes in series with one of the R's, may not be negligible at the low-frequency end of a tuning range. It will affect both the frequency and the attenuation. One method of compensation is to add an extra resistance to the parallel arm (R, in the diagram). This trick is particularly useful in lamp-stabilized circuits, where variations in network attenuation are apt to have a bigger effect on the amplitude of oscillation than in thermistor-stabilized circuits.

The circuit shown is that of a "lash-up" constructed to see how and RL oscillator behaves in practice. It is not put forward as a proper design though, in fact, it exhibited reasonably good waveform and amplitude stability over the tuning range 100c/s—2kc/s.

Croydon.

G. W. SHORT

FURTHER to the recent correspondence on transistorized Wien bridge oscillators, the accompanying circuit may be of interest.

By the use of n-p-n and p-n-p transistors in the

amplifier it is possible to maintain correct bias conditions very easily, merely by biasing the first stage directly and the last stage by means of negative feedback.

The optimum bias voltage at the point A is clearly half the supply potential and that at point B one-sixth, since the attenuation through the bridge is three times. R, and R_s bias point B; R_1 and R_s supply one-third of the amplifier output d.c. potential (i.e., one-sixth of the supply potential) as negative feedback to the emitter of the first transistor. The small potentials developed across R_s and R_s do not materially affect the biasing arrangements. With this arrangement R_s and R_s can be $100 \mathrm{k}\Omega$ if desired


The association of a p-n-p and a n-p-n transistor for the second pair provides for handling a wide variation in load impedance without output amplitude variation.

As shown the circuit will oscillate from 2 to 20kc/s. For supply potential variation from 13 to 22 volts, or with the load impedance varying from ∞ to 100 ohms, there is negligible waveform distortion, or variation in output amplitude and frequency.

Chertsey.

W. R. NAYLAND, A. V. Roe and Co., Ltd.

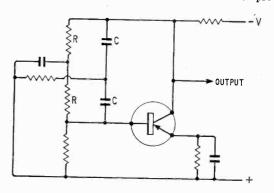I FEEL that Mr. Carpenter (October issue) has chosen a circuit which is not really suitable for a time standard. In the first place three active elements are used to pro-




duce the necessary loop gain and phase shift to maintain oscillation; these are three items of variation and trouble. Secondly, the symmetrical case of the Wien bridge has poor selectivity and a strong dislike to a shunt impedance across the parallel RC in the network. However, the effect of this shunt impedance and the changing


circuit parameters may be considerably offset by the introduction of the virtual earth system shown in the block diagram.

This refinement is still insufficient if a constant amplitude of output is required. Of course, this is due in the main to the thermistor.

With the preceding arguments I have been endeavouring to pave the way for a simple oscillating circuit briefly outlined in a paper in the section of the Proceedings of the I.E.E., at the Convention held on 25th May, 1959, and entitled "Discussion on Application: Linear Amplification and Oscillators." This oscillator consists of only one transistor and a selective network taking the form of the well-known parallel-T network.

(Continued on page 611)

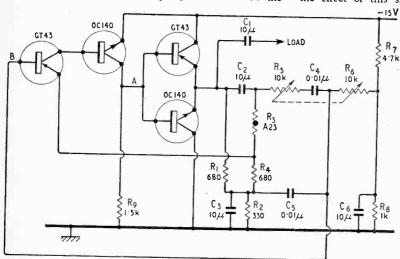

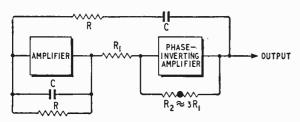

When this oscillator was subjected to temperature variation of 20°-80°C, it is stated that the frequency shifted by less than 0.1% and the output change was less than 1%.


From these details it will be realized that the circuit has at least equalled the performance of the Wien bridge oscillator with considerable saving in component cost and greater reliability. W. WOODMAN,

Tolworth, Surrey.

Nash & Thompson, Ltd.

Standing Wave Ratio

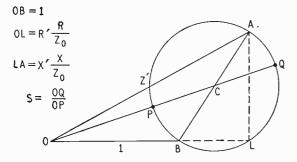IN your June issue Mr. J. E. Robson describes a method of calculating the s.w.r. with the help of a quadratic



equation which on the face of it, appears to be frightening. Technicians possessing a pair of compass and a foot rule may find the following geometrical method much more instructional and useful in practical problems.

After normalizing the terminating impedance to $Z' = (R + jX)/Z_0$ a line OB equal to a unity is drawn to represent the normalized characteristic impedance. The line OA is then drawn to represent the normalized terminating impedance Z' with OB as the unity of scale. With AB as diameter the "reflection" circle is drawn as shown. Finally, O is joined to the centre of C of this circle, cutting the latter at P and Q. The s.w.r. is then given by

$$S = \frac{OQ}{OP}$$

This can easily be proved and, if required, Mr. Robson's equation for S obtained from the above construction without resort to complex variables and coordinate geometry.

Calcutta.

O. C. GUPTA

Signal-flow Diagrams

IN the November issue S. R. Deards asks Thomas Roddam to try to justify the use of "signal-flow method" diagrams as superior to other methods. Thomas Roddam gracefully declines.

I would like to draw their attention to a book called "Introduction to Electronic Analog Computers" (Prentice Hall), signal-flow methods are described in application to computers, but it states that this method is useful not so much for analysis, as S. R. Deards thinks is its prime function, but for synthesis. It goes on to state that usually there is just not one good way, but several and this method allows one to decide which will suit the requirements. Where in the previous sentence I have used the word way, this applies to design, not s.f. methods.

Liverpool. •

H. BAYLISS

PLEASE get it in your noddle That matrix was nodal, not model.

THOMAS RODDAM [We apologize to Thomas Roddam for the unlucky misspelling in line 13, right-hand column of page 562 of the previous issue. -Ep.1

INDUSTRIAL GROUPS - 3

TWO or three times within the last few months the initials E.M.I. have been in the news because of takeovers or rumours of takeovers by the Group, whose latest acquisition is Ardente and its subsidiary Ardente Acoustic Laboratories for the sum of over £600,000.

Electric and Musical Industries, Ltd., was formed in 1931 to merge the interests of the Gramophone Co. and Columbia Graphophone Co., and today the Group embraces nearly 50 companies in this country and abroad. Among the trade names used by the Group are His Master's Voice and Marconiphone (both also used under licence for certain products by the Thorn Group),

Alpha Accessories Ardente Ardente Acoustic Laboratories Capitol Records Inc. Columbia Graphophone Co. Columbia Graphophone Co. of Comercial del Gramofono Odeon, S.A., Spain Compania del Gramofono Odeon, S.A.E., Spain Davey & Moore Electric & Musical Industries Electric & Musical Industries (China) Electric & Musical Industries (Ireland) Electrola G.m.b.H., Germany

E.M.I.-Cossor Electronics
E.M.I. Electronics
E.M.I. Records
E.M.I. Sales & Service
E.M.I. (South Africa)
E.M.I. Suppliers (Sud America)
E.M.I. Switzerland
Grampfon Limiter Sirkeri Turkey Gramofon Limitet Sirketi, Turkey Gramophone Co.
Gramophone Co., Pakistan
His Master's Voice (N.Z.)
Home Maintenance Home Maintenance Imudico AJS, Denmark Industrias Electricas y Musicales Odeon, S.A., Argentine Industrias Electricas y Musicales Odeon, S.A., Chile Industrias Electricas e Fabrica Odeon, S.A., Brazil

Capitol, Columbia, Parlophone, M.G.M., Mercury, Emarcy and, of course, many beginning with "Emi."

The Group's interests in the radio and electronics

field range from sound and television broadcasting transmitters and ancillary equipment and electronic computers to domestic receivers and sound-reproducing equipment. In the latter field the Group markets the Emisonic Orthotone products jointly with Clarke & Smith, of Wallington, Surrey.

The following companies are within the group which during the last financial year made a profit of £5,348,000 -some £400,000 more than the previous year's figure:-


La Voce del Padrone-Columbia-Marconiphone S.p.A., Italy
Felicions et Productions Les Editions et Productions Musicales Pathe-Marconi, S.A., France Lindstroem, Carl, G.m.b.H., Germany Marconiphone Co. Morphy-Richards Morphy-Richards (Astral) Morphy-Richards (Sales & Services) Musica Argentina e Internacional, S.R.L. Nordisk Beka Record A/S, Denmark Oesterreichische Columbia Graphophone G.m.b.H.,

Parlophone Co. S.A. Gramophone N.V., Belgium Skandinavisk Grammophon A/S, Denmark Skandinaviska Grammophon A/B, Sweden Skandinavisk Odeon A/S,

Denmark Skandinaviska Odeon A/B, Sweden Ardmore Beechwood (Belgique) S.A. Ardmore A(rica) & Beechwood (S.

Les Industries Musicales Electriques Pathe-Marconi,

Austria

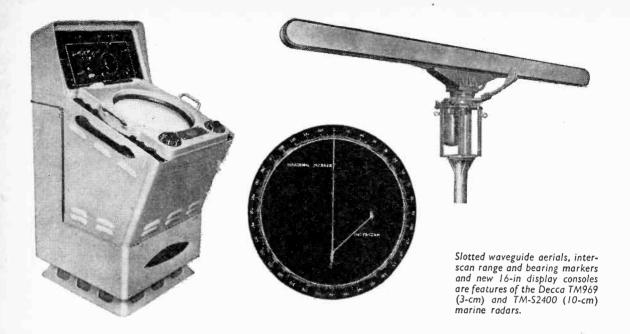

NEW DECCA RADARS

ANALYSIS by Decca of more than 350 cases of collision at sea during the past five years has shown that more than 95% occur in congested shipping lanes and in pilotage waters, and the conclusion is drawn that the possession of radar is not in itself a guarantee of safety. Simple radar systems must be supplemented by facilities which will reduce the time and effort necessary for the interpretation of target movements on the p.p.i. display. A major step forward was taken with the introduction by Decca in 1956 of True Motion displays in which returns from buoys and coastlines remained stationary while "own ship" and other vessels under way were shown by moving spots leaving persistence trails to show their true motion. Even so the officers of the watch are often hard pressed in keeping under observation the changes of range and bearing of all the vessels in the vicinity which at any time might change to potential collision courses.

A most useful additional feature is now incorporated in the new Decca TM969 and TM-S2400 in the form of an interscan marker originating from "own ship" and variable in length and inclination, with direct reading of range and bearing from scales coupled to the controls. Any number of targets can be checked in rapid succession, and the use of a longer-persistence screen helps in showing change or—more important—lack of change of bearing with the minimum of effort.


In all, four new models have been added to the Decca range giving a choice of 12 types for varying requirements. One of these operates on 10cm (S-band) giving a high target/clutter ratio and better performance in the presence of precipitation. Two models have 16-in displays, and in all the new consoles particular attention has been given to the grouping of controls according to function and frequency of use. The display units hinge forward,

giving instant access to circuits for ease of maintenance.

All the sets make use of narrow-beam slotted waveguide scanners with lower top weight and windage. The rotation rate has been increased to 20 r.p.m.

All-Transistor Car Radio

The new Murphy "Voxson" fully-transitorized, long-and medium-wave, twelve-volt car radio is made up of two separate units. One of these consists of a small cabinet cum rear-view car mirror (see illustration) which is attached via an adjustable ball and socket joint and suction cup to the car windscreen. This unit contains the volume, tuning and wave-change controls, the internal ferrite aerial, and the mixer, two i.f. and audio driver transistors. The $2\frac{1}{2}$ -watt audio output transistor, together with its associated heat sink, input and output transformers and 5-in loudspeaker form the other unit. This may be sited in any convenient position in the car, for example, under the dashboard. The total cost of both units is 20 guineas (including purchase tax).

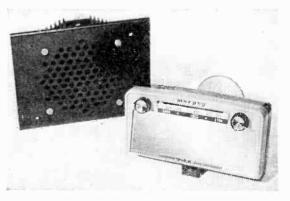


WIRELESS WORLD, DECEMBER 1960

Transformer with a number of secondaries wound on separate parallel limbs is being developed by the G.P.O. With this arrangement, which is electrically equivalent to a number of ordinary two-winding transformers with their primaries connected in series, the parallel magnetomotive forces across each secondary are equal. The ampere turns are thus equal for each secondary so that the number of winding turns determines the secondary current rather than, as in a normal transformer, the secondary voltage. This new type of transformer is thus useful for feeding a number of current-operated devices such as transistors.

Peak Voltmeter in which the peak voltage storage capacitor is not, as is usual, charged directly from the input but rather from a flip-flop which is triggered from the input is described by R. P. MacKenzie in the June 17, 1960, issue of *Electronics*. In conventional peak voltmeters the indicated voltage may be too low at low input duty cycles because insufficient input current is available to charge up the storage capacitor to the full input voltage. In the circuit described by MacKenzie, as long as the voltage on the storage capacitor is less than the input voltage, their difference triggers a flip-flop which then for its unstable period charges the storage capacitor. Input voltage peaks thus continue to trigger the flip-flop to charge up the storage capacitor until the voltage on this capacitor reaches the input voltage and their difference is no longer capable of triggering the flip-flop.

Speed Control and (TASC) units introduced by the Lowestoft Division of Pye Electric, Ltd., utilize inductive coupling to produce the control torque. The two cross-sectional diagrams show the construction of a typical unit. This consists of two independently rotating shafts and a stationary magnetizing control coil. The control input shaft is driven at a fixed speed and carries a poled rotor. This rotor is surrounded by an aluminium or copper torque tube attached to the control output shaft. (The larger

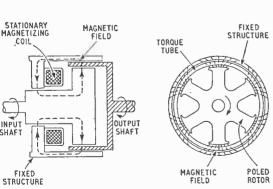



units are driven in reverse, i.e. the input shaft carries the torque tube and the output shaft the rotor.) A fixed magnetizing coil concentric with the rotor is energized from a d.c. supply. This sets up a d.c. magnetic field (see diagrams) which streams out from the pole faces of the rotor and rotates with these poles. This induces currents in the torque tube and thus a magnetic The torque-tube and magfield netizing-coil magnetic fields interact to produce a torque on the output shaft in the direction of rotation of the poled rotor. The magnitude of this torque is directly proportional to the value of the magnetizing coil current and is thus easily controllable. This torque is almost com-pletely independent of the shaft speed. Three other advantages of this system of torque control are that no slip rings or brushes are used, that there is no physical contact between the input and output shafts except via the shaft bearings, and that the units may be stalled down without overheating. Applications of such units range over almost as wide a field as for electric motors.

"Change-of-State" Crystal Oven was described by D. J. Fewings (of Marconi's Wireless Telegraph Co., Ltd.) at the Brit.I.R.E. symposium on "Stable Frequency Generation" held last May. This type of oven utilizes the constancy of the melting point temperature of a substance to produce the required constant crystal temperature. Ideally such an oven would consist of the crystal imbedded at the centre of a sphere of a suitable solid substance which is in turn surrounded by a uniformly

thick layer of the same substance in liquid form. The crystal and inner solid portion of sphere will the then eventually take up the melting-point temperature of the substance, and ex-ternal temperature changes will then merely increase or decrease the amount of melted material, leaving the temperature nearly unchanged.

The action of the oven depends on there being both solid and liquid layers of material present. simplest practical way of ensuring this is to use a substance whose volume changes substantially on melting, together with an expansible closed container for the whole oven. The change in the volume of the container as the substance melts can then be used to operate the on/off switch for the oven heater, and this must uniformly heat the whole outer surface of the sphere. In practice the temperature control cannot be perfect because the necessary supports and connections to the crystal through the sphere provide paths along which heat can flow. However, a similar limitation applies to any type of temperature control. A suitable material to use is naphthalene, which has a melting point of 79.5°C and expands by rather more than 10% in volume on melting. In a practical case using such an oven an external temperature change of 14.5°C produced a crystal tem-perature change of only 0.084°C. For maximum crystal frequency stability it may be desirable to operate the crystal at the temperature at which its rate of change of frequency with temperature is zero. Crystals can be cut so that this temperature is within ±3°C of the melting point temperature of the substance used. Any remaining temperature difference could then be taken up by altering the melting point temperature by adding a suitable impurity to the substance. In the case of naphthalene anthracene is a suitable impurity: by adding up to 10% by weight of anthracene to naphthalene the melting point of the resultant mixture can be varied from 79.5°C to 76.4°C.

Low-frequency Noise can be obtained from high-frequency noise by sampling it at regular intervals and storing each sample until the next is obtained so as to produce a stepped noise output in which the step heights are equal to the sample amplitudes and in which steps occur whenever a sample is made. It can be shown that, if T is the time interval between successive samples, then 90% of the total power in the stepped noise output lies in the frequency range from 0 to 1/T. Although in this frequency range the

noise output decreases as the frequency increases from zero, the noise spectrum shape can be calculated and allowed for. A description of a low-frequency noise generator based on these principles is given by N. T. Slater in the August 1960 issue of Electronic Engineering.


Very-Low Frequency Propagation over long distances is being studied with the aid of a ship-borne 30MW (peak) pulse generator and 3,000-metre long helicopter-supported aerial according to an article by M. M. Newman et al in the July 22 issue of the American journal Electronics. With a transmission frequency of 20kc/s a signal strength of the order of 100µV/metre can be produced at a distance of 10,000km (6,200 miles) by means of this generator and aerial.

Optical Maser oscillator utilizing the fluorescence of synthetic ruby has been developed by the Bell Telephone Laboratories. The ruby is "pumped" with green light to produce "stimulated emission" at the frequency of the fluorescent colour (red). The ruby, which is the form of a rod 11 in long with a diameter of gin, is held in the centre of a spiral photoflash lamp. The green com-ponent of the light from this lamp excites the chromium impurity atoms in the ruby. The excited chromium atoms at first rapidly relax from the excited quantum energy level to a metastable intermediate quantum energy level without emitting any radiation. The chromium atoms then rather more slowly relax from this metastable level to their original level,

emitting red fluorescent light in the The fluorescent light first process. emitted stimulates the chromium atoms still in the metastable state to radiate at the fluores-cent frequency, provided that the fluorescent light stays long enough in the ruby rod to provide sufficient stimulation. This proviso is satisfied by polishing the ends of the rod until they are exactly flat and parallel, and then partially silvering them. Some of the fluorescent light which is emitted within a small angle about the rod's axis is then reflected back and forth between the silvered rod ends for long enough to stimulate emission. It is this stimulated emission which distinguishes the action of this maser from ordinary spontaneous fluorescence. This stimulation process ensures both that the stimulated radiation is all emitted within a small angle about the rod's axis (an angle of about one-tenth of a degree was actually measured), and that the stimulated radiation is coherent (i.e. has the same phase at all points on either end of the rod). Coherence was proved by observing interference between the light from two fine parallel slits in the silver. Coherence has not hitherto been achievable with a light source. As with radio waves, it makes possible the communication processes of modulation, amplification and detection. Another property of the emitted light resulting from stimulation is that its bandwidth is only about one-sixtieth of that of normal fluorescent light, and it is hoped to achieve an even narrower bandwidth. This narrow-bandwidth property, as well as the fact that the light is all emitted within a very

narrow angle, gives rise to a very bright source, in fact more than a million times brighter than the sun. This brightness should also be useful for communication purposes. The light from this maser has in fact been seen twenty-five miles away. With the present device, maser action can be sustained for about a millisecond at a time. During this time several hundred bursts of radiation spaced a few microseconds apart are produced, each lasting for about a microsecond. The stimulated emission is produced in pulses probably because, when stimulated emission occurs, it de-creases the number of atoms in the metastable state so rapidly that the flash lamp is not bright enough to maintain a sufficient number of atoms in the metastable state to allow maser action to continue. Maser action then ceases, but commences again when the flash lamp has had time to produce a sufficient number of atoms in the metastable state. This alternate decrease and increase in the number of atoms in the metastable state then produces pulses of light.

Crystal-Frequency Variation with temperature can be compensated for (according to a letter from E. A. Gerber in the February, 1960 issue of Proc. I.R.E.) by applying a temperature-dependent force to the crystal so as to produce an opposite frequency change. A bimetal strip bearing on the crystal can be made to provide a suitable temperature-dependent force and, according to the direction of this force, a positive or negative compensating change in the crystal frequency can be produced.

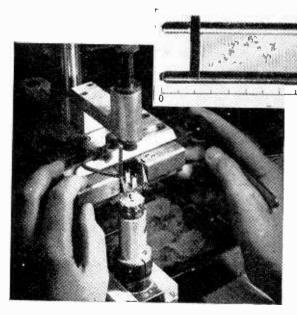

Frame Grid Valve Manufacture


THE mechanical precision necessary for the handling of the fine wires (10 microns in diameter) and the assembly of frame grids with grid-cathode spacings of the order of 50 microns has called for the development of a completely new range of electrode winding and welding machines, and of assembly methods comparable with those in the watch-making industry. The accompanying photographs show a typical frame grid, and the assembly jig for the two grids of the PCC89 cascode r.f. amplifier, one of the four new high-slope television valves now in quantity production at the Mitcham Works of Mullard Ltd.

Manufacturers' Products

ACCESSORIES NEW ELECTRONIC EQUIPMENT AND

Precision V.II.F. Frequency Standard

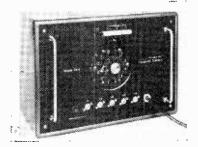A COMPACT and portable (but mains-operated) frequency standard for accurately checking the operating frequencies of mobile, as well as of fixed, v.h.f. radio transmitters has been introduced by Wayne Kerr Laboratories, Ltd., Chessington, Surrey. Known as Model FS100 it consists of a crystal-controlled oscillator, three



Wayne Kerr Model FS100 crystal-controlled frequency standard for testing mobile v.h.f. transmitters.

frequency multiplier units, wide-band detector and a.c. mains power unit for 110-130V or 190-240V, 40-60c/s.

The oscillator can be switched to operate with any one of 12 quartz crystals mounted in thermostatically controlled, plug-in ovens, two crystals being mounted in a single oven. Crystals for operation on fundamental frequencies within the range 7.5 to 9.7Mc/s can be used and each multiplier unit covers a specific part only of the total frequency coverage. For example, the Band I multiplier covers crystal frequencies of 7.5 to 8.17Mc/s giving final outputs on 3, 9 and 18 times as required of the frequency of the crystal selected. Between them the 3 multipliers will provide spot output frequencies of from 22.5 to 175Mc/s with an accuracy of 3 parts in 10°.

Crystals are selected by a rotary switch mounted in the centre of the instrument panel, while multipliers are

selected by means of push-buttons.

Signals from the transmitter to be tested are fed into the test set and the crystal and multiplier switches set to the transmitter's operating frequency and the out-put then checked for zero beat. The test set measures 1314in wide, 9in high and 814in deep and weighs 161b complete.

New Plessey $2\frac{1}{4}$ in Loudspeaker

A NEW 24 in diameter loudspeaker for use in modern miniature transistorized receivers has been introduced by The Plessey Company Ltd., Ilford, Essex.

The magnetic circuit uses a new constructional technique to enable the overall depth to be reduced to a

Plessey 21 in loudspeaker has а depth of only 0.83in.



minimum-a rod magnet being inserted into a split aluminium ring which is fitted into an accurately machined yoke. This design arrangement gives a compact, robust motor unit without the use of magnet assembly

The 21/4 in diameter loudspeaker is available with a low impedance voice coil (8/10 ohms) for use with a matching transformer or alternatively with high impedance coils for direct connection into transistor circuits.

20W Transistor Amplifier

THE Type TR/2 transistor amplifier is a compact unit measuring 8in \times 6in \times 3in (high) and capable of delivering 20W peak a.f. output to 3.5- Ω or 15- Ω loudspeakers. It is intended primarily for portable and mobile PA applications and operates from a 12V d.c. supply, imposing a no-speech load of 0.25A and a mean working load of 1A.

It employs 5 transistors, one protective diode and a lightweight moving-coil microphone fitted with a pressto-talk switch, thereby ensuring maximum economy in l.t. consumption during intervals in operation. price is £31 10s 0d including microphone.

Although a non-reversible l.t. input socket is fitted, a safety circuit to prevent damage to the transistors,



R.E.E. 20W transistor PA amplifier. The key gives a good indication of its size

should the battery polarity be reversed, can be included at a small extra charge.

Further details can be obtained from R.E.E. Telecommunications Ltd., Telecomm Works, Market Square, Crewkerne, Somerset.


V.H.F. Marine Radio-telephone

SHOWN in the illustration is the latest Pye marine v.h.f. radio-telephone for shipborne use. It is suitable for use in large or small vessels having 100-150V or 190-240V, 40-60c/s a.c. supplies and operates on the frequencies allocated for inter-ship, ship-to-shore, harbour and docking telephone communications.

The equipment allows for operation on 28 channels in the international marine v.h.f. band, 9 channels being for single frequency simplex and 17 for duplex working. The 28 channels are provided by 18 crystals.

Frequency modulation is employed and the transmitter power output is 20W. The Type PTC8306 equipment complies with the Hague and British G.P.O.

Wireless World, December 1960

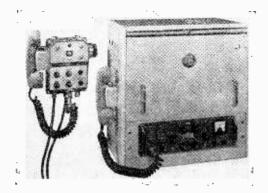

Pye marine V.H.F./F.M. radio-telephone Type PTC8306. The remote control unit is on the left.

specifications for this type of equipment so it is suitable for international use as well as for use in home waters. Provision is made for full remote control over lines up to 200ft in length.

The makers are Pye Telecommunications Ltd., Newmarket Road, Cambridge, from whom further details can

be obtained.


Oscilloscope Kit

THE Heathkit Model OS-1 enables an oscilloscope to be built with a Y-amplifier sensitivity of 14mV/cm and a response within ±3dB from 10c/s to 2.5Mc/s. The X-amplifier sensitivity is 1.4V/cm and its response within ±3dB from 15c/s to 500kc/s: the time-base range is from 15c/s to 150kc/s approximately. A 50c/s calibration source provides a peak-to-peak potential of 1, 10 or 50V to an accuracy of ±10%. A printed circuit board helps to ensure that all kits are wired exactly as required. The manual provided includes step-by-step wiring instructions, pictorial diagrams, and a circuit description and diagram. Operating voltages are also given. The Kit costs £18 19s 6d and is available from Daystrom Ltd., of Gloucester.

Transistor Oscillators

WITH the new Levell Electronics Types TG150 and TG150M battery oscillators sine waves can be produced

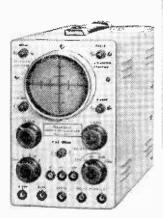Right,—Levell Flectronics Transi cr Ba tery Oscillator. Type TG15_M.





Left. Assembled Heathkit Model OS-I oscilloscope

at any frequency between 1.5c/s and 150kc/s and with any amplitude up to 2.5V into 600Ω . The harmonic distortion is <0.3% between 50c/s and 15kc/s and <1.5% below 50c/s and above 15kc/s. The frequency changes by <0.3% at 1kc/s for a 30% fall in the supply voltage and by <0.05% per °C temperature change. The output level varies by <0.1dB over the whole frequency range, by <0.05dB for a 30% fall in the supply voltage, and by about -0.02dB per °C temperature change. A thermistor stabilized Wien bridge circuit is used in these oscillators. The Type TG150M is fitted with a calibrated output meter and costs £36, a version of this oscillator without the output meter—the TG150—costs £27. These instruments are manufactured by Levell Electronics Ltd., of 10-12 St. Albans Road, Barnet, Herts.

New Plastic Foil Capacitors

TROPYFOL capacitor is the name given to a new type of miniature capacitor which utilizes an aluminium-coated polyester foil dielectric rolled and impregnated in a plastic resin with axial end wires. They are available in 125V and in 400V types, the former with capacitance ranging from $0.01\mu F$ to $1\mu F$ and the latter



Tropyfol 0.1 µF, 40CV miniature capacitor.

from $0.001\mu F$ to $1\mu F$. A $0.001\mu F$ capacitor in the 125V type measures 4.5mm in diameter and 12mm long and a $1\mu F$ size for 400V working is 13mm in diameter and 24mm long $(0.5 \text{in} \times 0.9 \text{in approx.})$.

Insulation resistance is said to be not less than 2,500 sec $(M\Omega_X\mu F)$ while in some cases it may reach 50,000

sec

Supplies are available to the radio and electronics industries and further details can be obtained from Waycom Ltd., Empire Buildings, Duke Street Hill, London, S.E.1.

Very Low Temperature Coefficient Resistors

BY combining two wires of different temperature characteristics Alma Components have produced a range of precision wire-wound resistors with the remarkably low temperature coefficient of less than 4 parts per million per degree C. The wires are wound on non-hygroscopic ceramic formers encapsulated in a sealing resin. Three sizes are available rated at Iw (Type C), $\frac{1}{2}$ w (Type C2) and $\frac{1}{4}$ w (Type C4) with resistance values of 100Ω to $300k\Omega$, 100Ω to $120k\Omega$ and 100Ω to $80k\Omega$ respectively. The winding is sectionalized with adjacent sections wound in opposite directions. Standard tolerances are 0.1%, 0.25%, 0.5% and 1%.

Further details can be obtained from Alma Components Ltd., 551, Holloway Road, London, N.19.

Digital Computers

By D. S. WILDE, B.Sc., A.M.I.E.E., Grad. Inst. P.

2.—ARITHMETIC AND CONTROL CIRCUITS

N the previous article methods of storing binary information in a digital computer were outlined. These digit patterns represent numbers and instructions and the function of the arithmetic unit (sometimes called the accumulator—Babbage called it the "mill") is to perform additions, subtractions etc. with these numbers, as dictated by the instructions.

A group of digits may be delivered from a store one after the other on a single channel (serially) or simultaneously with a separate channel for each digit (in parallel) and the choice must be made in the design of the computer between increased

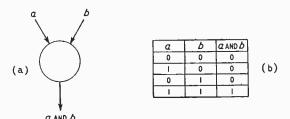


Fig. 3 (a) Symbolic AND gate. (b) Truth table for the AND gate.

speed and economy of equipment. For example, a serial adder will take nt + t periods to add two n-digit binary numbers occurring as pulse trains of period t (the final t is for the last carry). Parallel addition will only take 2t periods but there must be one adder per channel i.e. n adders.

It is possible to effect a compromise between both extremes and the Ferranti Mercury computer is an example of this. Access to the storage elements is parallel, the parallel digits are turned into serial form

and dealt with by fast serial circuits.

machines, it is possible that with new types of storage operating extremely rapidly—perhaps up to 100 Mc/s—we may see a return to serial techniques and consequently smaller computers.

It has already been shown that the fundamental

Whilst the present tendency is for fully parallel

It has already been shown that the fundamental arithmetic operation is subtraction and that all the other common functions can be derived from it. Subtractions only occur about one-third as frequently as addition in most programmes, and since an addition operation performed in a subtracter would require two stages [0-b, a-(0-b)] a subtracter is an uneconomical component. An adder is always provided and a complementer then enables subtractions to be performed by complement addition.


Binary addition can be reduced to a set of logical (or Boolean) operations and these operations are performed by extremely simple electronic circuits. Given the necessary reduction details a binary adder can be easily synthesized, so can other functional units.


There are a variety of logical operations although only two are essential and the others can be derived from them. It is much more convenient however to use three basic logical functions, these are AND, OR, and NOT, and they are almost self explanatory.


and NOT, and they are almost self explanatory. The AND gate is shown symbolically in Fig. 3(a) and both input a AND input b must be present⁹ to cause an output from the gate. There are four possible combinations for the conditions of a and b and these are shown in the "truth table" of Fig. 3(b) (1 signifies presence, 0 signifies absence). Only when a = b = 1 do a and b = 1 and hence the AND operation is equivalent to the algebraic product ab.


The circuit for such an AND gate is shown in Fig. 4(a) and in this case the inputs must be positive going and the supply rail is a positive rail. Suppose, in a practical case, that the supply is 100 volts and a and b

Fig. 4 (a) Circuit of an AND gate for positive-going inputs. (b) Input and output pulses for the AND gate for positive-going inputs of Fig. 4(a). (c) Circuit of an AND gate for negative-going inputs.

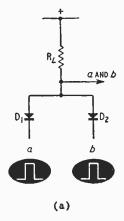


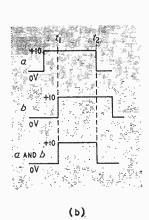


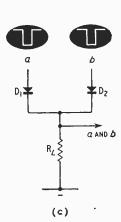

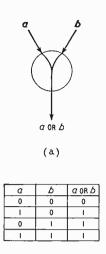

(b)

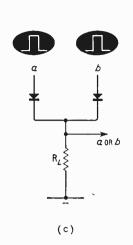

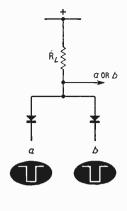

(d)

Fig. 5 (a) Symbolic OR gate. (b) Truth table for the OR gate. (c) Circuit of an OR gate for positive-going inputs. (d) Circuit of an OR gate for negative-going inputs.

inputs are normally at earth potential. Both diodes will be conducting and if R_L is considerably higher than the forward resistance of the diode then the voltage drop across the diode will be negligible compared with that across the resistor. The output is therefore also at earth potential. If input a moves 10 volts positively then diode D₁ will become cut off. The diode D₂ remains conducting and hence its anode (and thus the anode of D1) stays at earth potential. Thus although input a moves positively the output remains at earth. Only when a and b inputs move 10 volts positively together will the output rise by 10 volts. Fig. 4(b) makes this clear. For $t < t_1$ only input a moves positive and the output does not change. For t_1 $< t < t_2$ both a and b are positive and there is an output. After t_2 only b is now positive and there is no output.

A second type of AND gate is shown in Fig. 4(c) and this gate operates when inputs a and b are negative-going pulses, and the supply rail is negative. Only when both inputs move negatively together will the output move negatively.

Fig. 5(a) shows an OR gate symbolically. Its name suggests that input a OR input b being present will operate the gate and cause an output. The "truth table" is in Fig. 5(b) and the algebraic equivalent of a OR b is a+b-ab and this can be checked by substitution of possible values from the "truth table". The OR operation is inclusive since both a and b being present together operate the gate.

The electronic OR gate for positive-going pulses is shown in Fig. 5(c) but in this case R_L is taken to a negative rail. Either input moving positive will cause the output to move positive. An OR gate circuit for negative-going pulses is shown in Fig. 5(d). An OR gate for positive-going pulses is identical to an AND gate for negative-going pulses; similarly an AND gate for positive pulses is the same as an OR gate for negative-going pulses.

NOT a is a very simple logical function and is algebraically equivalent to 1 - a since if a = 1, NOT a = 0 and if a = 0, NOT a = 1.

Electronically this corresponds to a voltage inversion and a simple valve circuit is shown in Fig. 6. If a is a negative-going pulse from earth potential then the pentode will be bottomed when its grid is at

earth and will be cut-off when the grid goes negative. The anode potential will be low when the valve is bottomed and high when cut off. The anode excursions are applied to the potentiometer chain R_1 and R_2 which can be chosen in conjunction with V_2 to ensure that as the input a moves from earth negatively the output NOT a moves from a negative potential to earth. D_1 merely serves to prevent the output going above earth potential.

In early computers the diodes in AND or OR gates were thermionic and valves were used for inversion circuits. The diodes are now semi-conductor types and the inversion circuits are transistors.

Using only these three circuits, AND, OR and NOT, it is possible to construct a binary adder. There is an additional circuit required for a serial adder however, this is a delay.

First it is necessary to establish the "truth table"

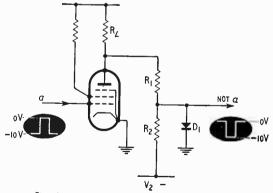


Fig. 6 Voltage inverter circuit of a NOT gate.

1	<u>a</u>	0	_ 0	0	0	1			ı
1	b	_0	_ 0	1	_ 1	0	0		
ļ	c	0	L	0		0	ı	0	ı
ļ	ANSWER	0	I	I	0	T	0	0	- 1
ļ	CARRY	0	0	0	- 1	0		-	-
L	a or b or c	0	1	1		- 1	ı	ı	1

ig. 7 Truth table for binary addition.

for binary addition (Fig. 7). There will be three digits to add; these will be from the addend, the augend and the carry digit resulting from the addition of the previous digits. With three inputs, each of which can be either 1 or 0, there are eight possible combinations of inputs to the adder. These are shown in the "truth table" together with the answer (1 or 0) and carry (1 or 0) which must result.


Suppose that the three inputs are applied to an OR gate. Whenever there is a 1 among the inputs there must be a 1 in the output. If all eight combinations are tried the output agrees with the required answer except when two of the inputs are 1's together. (The output will be 1, the correct answer should be 0.) There must be an additional set of circuits to inhibit the output of the OR gates under these conditions. In other words the required answer is $(a \text{ OR } b \text{ OR } c) \text{ AND NOT } [(a \text{ AND } \hat{b}) \text{ OR } (b \text{ AND } c)]$ OR (a AND c)]. The logical diagram now looks like Fig. 8.

The circuit combination responsible for inhibiting the output when only two 1's occur can also be used to generate the carry pulse since there must be a carry developed when two (or three) ones are present. Unfortunately the inhibit gates will inhibit the output when three 1's are present at the input and no answer digit will appear though one is required. A three-input AND gate is included therefore and its output is applied to a two-input OR gate whose second input is the previous output.

This logical configuration now satisfies all eight conditions of input giving the correct answer digit and the correct carry (Fig. 9). The carry digit is applied to a delay of one digit period and is fed back to the input, arriving in the next most sig-

nificant place.

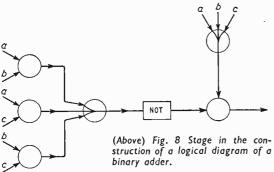The same logical considerations apply to adders for a computer working in the parallel mode. The carry digits in this case are not delayed to a more significant time period but are applied as third inputs to a more significant adder.



(Right) Fig. 9 Logical diagram of a binary adder giving both answer and carry digits.

There are other forms of binary adders and a binary subtracter can be developed in a similar The final step in the design is the substitution of circuit elements for logical symbols, and these have already been shown.

Whatever alternative solutions are found to the design of a specific logical circuit, Boolean algebra can provide a simple check that the circuit per-forms the function required. In the example chosen of the adder circuit the logical function is written

Answer = (a OR b OR c) AND NOT [(a ANDb) OR (a AND c) OR (b AND c)] OR(a AND b AND c)

= (a AND b) OR (b AND c) OR (aAND c


Previously it has been shown that a AND b =ab, $a ext{ OR } b = a + b - ab ext{ and NOT } a = 1 - a$. Algebraic substitutions can thus be made. Working the final expressions is rather tedious but a glorious simplification is available because $a^n = \bar{a}$ (since a = 1 or a = 0). If the above substitutions are made then

Answer = (a + b + c) - 2(ab + ac + bc) +

= ab + ac + bc - 2 abcCarry

and any binary adder must satisfy these conditions. Control Unit.—The control part of the computer is responsible for reading and sequentially obeying instructions which are held in the stores. Generally an instruction is divided into two parts, a function section (add, subtract, multiply, input, output, etc.) and address section (locating in the store the number that the function is to be performed on).

In the case of a serial computer the instruction will emerge from the storage as a series of pulses. The pulse pattern is a code and must be decoded to operate various gates in the computer which allow numbers to be routed to the various parts of the computer (the arithmetic units, the output units, another store location, etc.). Since only one pulse occurs at a time a pulse pattern can only be decoded if the individual pulses are staticised ("remembered") and all compared together after the last one has occurred. The staticisor most commonly used is the well-known bi-stable element (other names used are Kipp Relay, flip-flop, multivibrator, Eccles-Jordan circuit, and toggle). circuit consists of a pair of valves (or transistors) cross connected from anode to grid (or collector to base). A pulse input applied to one grid causes one of the valves to conduct, the second to cut

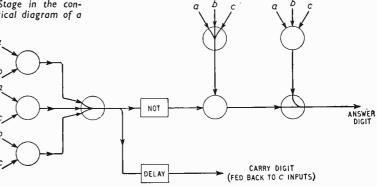

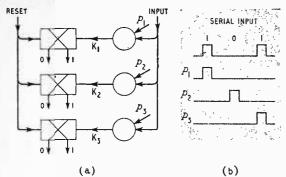


Fig. 10 (a) Staticisor (store) for serial input train of three binary pulses. (b) Serial input train and clock pulses for storing 101 in the staticisor of Fig. 10 (a).

off and this state is maintained until a trigger pulse is applied to the other grid when the circuit changes state.

A set of three bistable elements is shown symbolically in Fig. 10 and the serial pulse train is applied to them via two-input AND gates. second inputs to the gates are single clock pulses; they behave in the manner of a strobe pulse and p_1 is coincident in time with the first pulse of the pulse train, p_2 with the second, and p_3 with the third¹⁰. In the case of a pulse train of 101 the first bi-stable element will receive a trigger since p_1 and the first 1 of the pulse train coincide and there will be an output from the AND gate. p_2 coincides with a 0 (no pulse) and there is no output from the gate, hence the second bi-stable element is not triggered. The third one is triggered, p_3 coinciding with the third place. The pulse pattern 101 has now been stored (or staticised) and the bi-stable elements are said to be in the 1, 0, and 1 state respectively.

With three bi-stable elements there are eight

possible combinations in which they can be set. These are, of course, determined by the input pulse train and could represent eight possible functions.

It is necessary to decode these eight possible states to uniquely define each of them. Fortunately this is an easy matter for a decoder is merely an AND gate; eight three-input AND gates are necessary to decode three binary digits. These are shown in Fig. The first digit has its inputs connected to the 0 side of the bistable elements. For this type of AND gate, positive inputs are required and the 0 side of a bi-stable element is defined as that side being at a positive potential when no input trigger has been received. The 1

output must therefore be at a negative potential under these conditions. Thus if the 0 side of the three bi-stable elements are connected to the first decoding AND gate and no input triggers have been received the output of the decoder will be positive. For the second gate the 0 sides of two of the bi-stables are inputs and the 1 side of the third bi-stable is the third input. If the pulse pattern 001 is now staticised the second decoder has an output, since both 0 inputs are positive (the bistables have not been triggered) and the 1 input is positive (the third bi-stable has been triggered and now the 1 output is positive, the 0 output negative). This method of decoding can be extended to the remaining six combinations of digits and whatever the input pulse train may be one, and only one, of the eight decoders will register an output.

Simple Computer.—With storage, an arithmetic unit, and a control unit we have enough components to construct a simple digital computer. In addition to its logical circuits there must be a timing cycle generated to ensure sequential operation.

Associated with the store are its address decoders. These behave exactly in the manner of function decoders but select the location of a number or instruction in the store, and in this example the store may be of the electrostatic or magnetic core type, not the delay-line type.

The control unit has a two-line store and an adder in its read/write loop. Associated with it are function and address staticisors.

The arithmetic unit consists of a store acting in conjunction with adders and subtracters.

There are six instructions in the simple programme to be performed and the computer can perform four functions. These are defined by 00 (ADD), 01 (SUBTRACT), 10 (RETURN TO STORE), and 11 (STOP). The store has eight lines in it and the eight addresses require three digits to specify them.

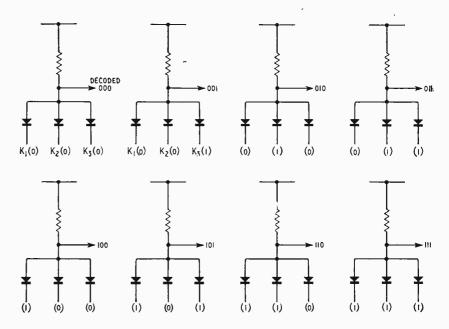


Fig. 11 Set of eight AND gate decoders for the eight possible states of three bi-stable elements.

Instructions are therefore five digits long.

The cycle of operations can be defined by four time periods T₁, T₂, T₃, T₄ and one instruction is selected and obeyed during each cycle of four periods. What happens in each time period is detailed below.

T1: add unity to the top line of the control store. This control address initially has zero stored in it and its job is to read instructions from the main store one by one. During T₁ the top line is read from the control store into the control adder through the STOP gate, which is open unless a STOP instruction is being obeyed. The number which emerges from the adder is used to set up the address and function staticisors and it also replaces the old number in the control store top line.

 T_2 : in this period the contents of the store address specified by the control unit in T_1 will be read out and transferred to the second line in the control store.

This is the instruction which is to be obeyed.

 T_3 : the instruction in the second line of control is now read out to the function and address staticisors which are set up.

T₄: the number specified by the setting of the address staticisors is read out of the main store and is operated on in the manner determined by the function staticisors.

To show how this sequence of operations works in practice the simple programme shown in Fig. 12 will be followed through. The computer, which has four functions and an 8-address store, initially starts with the programme in the main store and the control store and arithmetic unit store empty. In the first T₁ period 00000 is read from the control store, 1 is added to it, and the address staticisors are set to 001. The first two (function) digits (00) are not set up since the function staticisors are only set in period T₃. During T₂ line 001 is read from the store; its contents (00,101) pass through the gate marked T₂ into the control store. This is the first instruction and the code 00,101 is interpreted by the computer as "take the number stored in line 5 (101) and add it (00) to the arithmetic store contents".

This instruction is staticised on the function and address staticisors in T_3 and the function staticisor decoders open the gate marked + and the address staticisor decoders select line 5.

The contents of line 5 (the number 11111)* is routed to the arithmetic unit adder and arrives simultaneously with the read-out contents of the

Fig. 12 Simple computer.

store. Addition is performed and the answer is stored. The first instruction has now been completed and the cycle repeats for the second instruction (01, 110). This can be interpreted as "subtract from the arithmetic unit total (01) the number stored on line 6 (110)". In T₄ of the second cycle the number on line 6 (01111) is fed to one input of the subtracter through the gate marked—. The number in the arithmetic store (11111) is read into the subtracter at the same time and the answer (10000) is returned to the arithmetic store.

(10000) is returned to the arithmetic store.

The third instruction (10111) reads "transfer the number in the arithmetic store (10) to line 7 (111) of the store".

The fourth instruction merely says STOP. The decoded stop instruction closes the stop gate and no further adding of unity takes place in the top control line. Hence no subsequent instructions can be read and the programme has been finished with the final answer (10000) now in the main store in line 7.

This programme is an extremely simple one but it does show the way in which the basic elements work in conjunction with one another in doing a simple calculation. It illustrates also an important point from von Neumann's researches. This is that numbers and instructions were of exactly the same form. They both had five binary digits and were differentiated by the layout in the store which would be decided by the programmer. There is considerable flexibility to be gained since some programmes use few instructions but have a very large amount of numbers stored, whilst others use few numbers but a considerable number of instructions. The computer is therefore much more compact than if sepa-

STORE 00000 00101 110 ADDRESS DECODERS 0 1 CONTROL STORE 3 10 000 4 5 6 7 1.1 11 111 01 INPUT FUNCTION DECODERS ARITHMETIC UNIT STORE STOP STORE OUTPUT

^{*} This is not intended to be a negative number in this example.

rate stores were provided for numbers and instruc-

An additional and extremely important consequence is that instructions can be modified in the course of the programme by using them as if they were numbers and processing them in the arithmetic

units to give new instructions.

The simple programme did not exploit the "decision facility" which was recognized by Babbage as essential to an automatic computer. A short series of instructions will illustrate the importance of this "decision facility". Suppose it is required to divide 9 by 3. This can be done by simple subtraction, counting the number of subtractions performed before the answer goes negative, and this is the required quotient. The programme would

(1) Subtract 3 from the number in the arithmetic

store (9).
(2) Test the answer to see if it is positive. If it is, proceed to instruction (3), if it is not, STOP. (For this purpose 0 is a positive number.)

(3) Count 1 and store it.

(4) Repeat from instruction (1).


The test facility is not difficult to achieve in practice since it has been shown that negative binary numbers are recognized by having a 1 in the most significant place. Detection of this 1 is the deciding factor in whether the computer carries on its programme or whether it stops. Far more sophisticated uses are made of this property but they cannot be dealt with here.

The principles of digital computers are simple, but a full scale computer is obviously a much larger collection of elements than those discussed in this article. There are many additional circuits necessary which are concentrated on connecting the computer to the outside world, but the aim of these articles has been to emphasise the basic simplicity at the heart of even the most mighty machines.

REFERENCES

⁹ "Electronic Computers" (2nd edition.) T. E. Ivall, Iliffe, 1960, p. 100.

10 Ibid. p. 120.

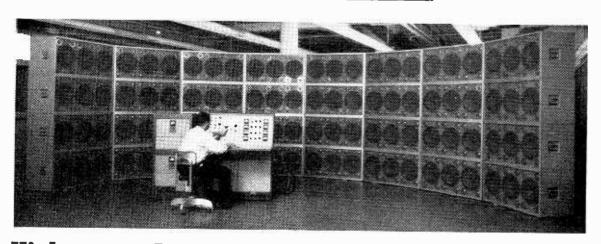

High-power Loudspeaker System

By MICHAEL LORANT

FOR STUDYING THE PHYSIOLOGICAL EFFECTS OF HIGH-INTENSITY SOUND

RESEARCH technicians of the Acoustical Engineering section of Stromberg-Carlson have recently developed for the Aerospace Medical Division of the Wright Air Development Centre, Ohio, a new highintensity acoustic system for studies of the physiological effects of high-intensity sound.

The most unusual feature of the new system is the "high-fidelity" quality of its performance—the generation of undistorted sound throughout the full

10-octave range of normal audibility.

The "business end" of this system is a huge assembly of loudspeakers-480 in all. These are mounted in 32 separate baffles for maximum flexibility in arrangement and control. Each baffle contains three low-frequency "woofers" and twelve high-frequency "tweeters". All the loudspeakers are especially designed to deliver "high-fidelity" sound

at high acoustic powers for sustained periods. The system is controlled from a console providing four possible inputs—sine wave, electronic "white noise", tape recordings (of jet engine, missile, etc.), or an external source.

The main audio power equipment consists of two pairs of audio amplifiers. One pair of these is for "low-power" use only, with each amplifier providing an output of 200 watts. Each of the pair of highpower amplifiers has an output of 7,000 watts. The frequency response of the system is "flat" over the entire audible range, from 20 to 20,000 c/s.

To avoid unintentional exposure of subjects to high-intensity sound, a safety precaution makes it necessary for the operator to put the controls first into the low-power position before energy can be

supplied to the high-power amplifiers.

MAIN ambition of power engineers is to generate electricity direct from heat, instead of going through the tiresome sequence of using the heat to boil water and making the steam impinge against blades in a turbine, causing it to move an array of conductors in a strong magnetic field. They may or may not be encouraged by the fact that direct conversion of heat into electrical energy does take place in absolutely every circuit. The evidence is before our very eyes—and ears—in every TV screen and loudspeaker receiving weak transmissions. The annoying thing is that this electricity is random, and therefore not only useless but detrimental.

Last month we considered the constant factor connecting temperature with random electrical power ("noise"): Boltzmann's constant, denoted by k. Since this form of electrical power is worse than useless, the fact that we get a very poor rate of exchange is a point in favour rather than otherwise. In our ordinary units, k is only 1.38 imes 10- 23 joule per °K. The resulting noise voltage across a resistor or tuned circuit is of the order of one or two microvolts. But of course that is enough to be a serious nuisance if the signal we are trying to receive is of the same order. When amplified 120dB, microvolts become volts. The most significant source of this universal circuit noise (called thermal or Johnson noise) is obviously the circuit followed by the greatest amplification. In fact, if the first stage of amplification is doing well, the contributions from circuits other than its input circuit may be neglected. But Johnson noise is not the only kind that causes the escaping-steam sound in the loudspeaker and the animated graininess on the screen.

If the subject of valves is not too passé, démodé, suramé, vieux jeu, radio à la vapeur, or any of the other contemptuous French epithets we may choose to bestow on it in these transistorizing days, let us consider how they too contribute their quota of noise. Even the transistor hounds may find it worth their valuable time to do so, for at bottom the

principles of transistor noise are similar.


One thing had probably better be made clear at the start: so far as the end product is concerned, valve noise is the same as Johnson noise. There is nothing to give a clue as to how much is due to valves and how much to circuits. (To cover myself against argumentative readers I had better declare a possible exception: two ingredients of valve noise to be mentioned might be recognizable by their tendency to occur increasingly at one end or other of the frequency scale.)

As has just been ninted, valve noise can be subdivided. The basic ingredient is what is usually called shot noise or shot effect. Sometimes writers (for the sake of effect?) name it in German, as Schroteffekt, which sounds even more penetrating. The air of mystery and confusion is further heightened by others who call it (wrongly, as it happens) Schottky effect, because it was first described by one Schottky. All these names are even more than usually subject to individual variations in spelling.

The thing was called shot noise (to come back to plain English), so we are told, because of its supposed resemblance to the sound of shot peppering a target. Since the sound in question, even after enormous amplification, is much more like a gentle hiss of steam, I prefer to think that the reference to shot is more to remind us (or even inform us, if we are beginners) that the flow of electric current through a valve is not perfectly smooth like the flow of treacle from spoon to plate, but more like the flow of water from cloud to earth, as rain.

The merit of likening it to shot or even rain is, I think, confined to the simple idea of current being made up of discrete particles and therefore subject to random variations from an average rate of flow. In

Fig. 1. A negative charge Q is moving towards the positive plate under the influence of the electric field between the plates. The work thus done on it by the battery necessitates a current through the battery.

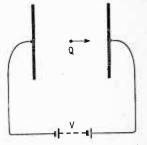

other ways it is misleading. A fairly obvious discrepancy is that what we get is not the magnified sound of electrons striking the anode, but a result due to random fluctuations of current in the anode circuit. A less obvious but most important difference is that shot has no effect on the target before actual impact. To be quite correct I suppose we must say that the first effect is produced by the extra pressure of air pushed against the target by the shot, but by that time the shot is virtually home. With electrons in a valve it is quite different. Electrically, they affect the anode circuit all the time they are travelling there from the cathode, and arrival marks the end of this influence, not the beginning. The fact that the movement of an electric charge near a conductor induces a current in the conductor used to be demonstrated by one of the stock gold-leaf-electroscope experiments of the nineteenth century. Nowadays I suppose one relies on Conservation of Energy. Q in Fig. 1 is the negative charge on a particle moving in response to the constant electric field between a pair of electrodes having a difference of potential V. (The field strength is V divided by the distance between the electrodes.) As its potential is being raised, work is being done on it, and the requisite energy can come only from the battery, through which a corresponding charge must therefore pass. The faster Q moves, the greater the rate of charge flow through the circuit; i.e., the greater the current. Assuming an electron starts from rest at the cathode, and the field is uniform, its acceleration is constant, so its velocity steadily increases, and the current waveform is as in Fig. 2.

For the sake of a nice round number, let us suppose

the anode current in a valve is 16mA. The rate at which electrons cross the vacuum must then be 1017 per second. If they were released at exactly equal intervals the anode current would therefore be modulated at a fundamental frequency of 1017 c/s. That is in the X-ray band, so we are safe in assuming that it would be smoothed out into imperceptibility in any practical anode circuit. But although the average rate of flight is 1017 per second, owing to the nature of thermionic emission this rate fluctuates in a random manner around its average, rather like the day-to-day fluctuation in actual births compared with a steady long-term average. At the foot of Fig. 3 the ideal waveform of Fig. 2 is repeated at intervals representing an average of eight electrons in flight at any one instant, but varying irregularly. Above is the result of adding all these pulses, and we see that it is mostly d.c., with a very high-frequency ripple—the one we are assuming is smoothed out, like the residual r.f. in a detector circuit—and a comparatively slow and quite irregular variation of the d.c. from its average. This last is the shot noise current.

It should be clear by now that the name "shot noise" is misleading in another respect: any idea that we are hearing even an indirect effect of the separate electrons pattering on the anode is completely unfounded; their frequency is far too high.

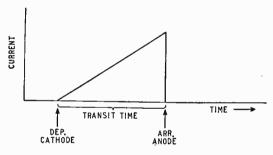


Fig. 2. Assuming a uniform field in Fig. 1, the charge is accelerated uniformly, and since the current in the circuit is proportional to the charge's velocity it increases steadily throughout the flight.

Just to make sure, and for the fun of the thing, I calculated what sort of a current Fig. 3 really represented, assuming the fairly typical transit time of 10-9 sec. The average rate of arrival of electrons is than 8 × 109 per sec., and as the frequency of the sawtooth ripple is the same—8 \times 10° c/s or 8 Gc/s it is actually a microwave frequency, with a wavelength of $3\frac{3}{4}$ cm. We may perhaps be surprised to find the electron frequency inside a commercially used radio waveband. But lest we imagine a great peak of noise at this particular frequency, let us remember two things. The first is that in this case one cycle is only one-eighth of the transit time, so is right outside the working frequency of the kind of valves we are considering. The second is that the anode current is only 0.001 µA, which wouldn't do much anyway. But it is easily measurable, even though as few as eight electrons at a time are in transit between cathode and anode; which makes one

In practical valves the anode current is millions of times larger, and the sawtooth ripple (which is

"shot noise" in the most literal sense) is correspondingly higher in frequency and can be left right out of account. But the slower ups and downs, due entirely to the fact that electrons are not emitted at regular intervals, are only too evident in high-gain amplifiers. Their power is distributed evenly over the frequency band. While this fact may seem natural for a purely random effect, so that we might have guessed it, it does need to be proved. Anyone sufficiently interested can wade through (e.g.) 15 pages of difficult mathematics in Davenport and Roots "Random Signals and Noise." Don't ask me to put it into a few lines of elementary algebra. I have to be content that the authorities agree on


 $I_N{}^2=2eI_AB$ where I_N is the r.m.s. shot noise current, I_a the anode current, e the electric charge of one electron (1.6 \times 10⁻¹⁹ coulomb), and B the frequency bandwidth. We may note in passing that I_N is proportional to the square root of I_a , so it doesn't do to starve the first valve in a high-gain amplifier. When the anode current is on the small side the gain is almost directly proportional to I_a , so signal/noise ratio would get worse if I_a were reduced too much.

Actually it is rather too soon to start drawing such conclusions, for the formula just quoted is limited to such exceptional cases that we are unlikely to find any use for it. One of the rare exceptions is a brightemitter diode run with such low filament voltage and such high anode voltage that every electron emitted is immediately pulled across the vacuum. In other words, the anode current depends entirely on cathode temperature, not anode voltage. Its technical description is a temperature-limited diode. Another exception is a photoemissive cell.

Valves as normally used are run at a cathode temperature that emits more electrons than are required. Imagine a great crowd of delegates to a conference moving out after the first session into a room with a buffet at the far end. The first arrivals spot it and stream across, but the main body can't even see it for the crush, and mill around just inside the entrance. They form a "space charge" screening the attractions of the buffet from the late entrants. This is roughly what happens in a valve (Fig. 4). Suppose the emission is at the rate of 1 amp. That is 6.4 billion (American trillion) electrons per microsecond. Even before the cathode is fully hot after switching on, enough electrons have emerged to build up a negative charge near the cathode that more than counterbalances the positive attraction of the comparatively distant anode. So nearly all the electrons emitted from then on are repelled back to the cathode. Only the few within sight, as it were, of the anode feel its attraction and stream across, forming a current of perhaps a few milliamps. If none at all left the cathode permanently, the space charge would soon be used up, but of course the slightest reduction in its numbers reduces its repelling power and allows some of the emitted electrons to join. And so a balance is reached between the attraction of the anode and the repulsion of the space charge, resulting in a certain rate of anode current, depending on the anode voltage.

A space-charge-limited diode (for that is what we are talking about) is therefore like a triode in which the part of the negative grid, controlling the flow of electrons to the anode, is played by the space charge. It is really like automatic grid bias, as produced by a cathode resistor. Any increase in cathode current

Fig. 3. Here there are, on the average, 8 electrons in flight all the time, but they start at irregular intervals. The resulting total current therefore has a slow irregular fluctuation as well as the fast saw-tooth ripple.

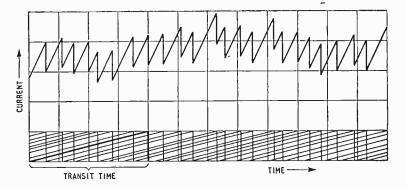

increases such bias and checks the increase in current. Similarly an increase in emission, due perhaps to mains voltage rising, increases the space charge and repels more electrons back to the cathode, so the

current remains fairly constant.

The purpose of the negative grid in a triode is to supplement the space charge, reducing the anode current as required, even down to cutting it off altogether. So long as the potential of the grid is not allowed to rise high enough to attract electrons to itself, a triode behaves similarly to a diode as regards

And how is that? Well, suppose the delegates were released from the conference room at short irregular intervals at such a rate that no crowd could form; the rate of flow across to the buffet would be equally irregular, as in a temperaturelimited valve. A crowd, on the other hand, would tend to even out such irregularities and ensure a relatively steady flow. This is much more certain with electrons, which, being free from individualities such as varying degrees of hunger, politeness or sociability, work according to simple and predictable laws. That is not to say that the quantitative working out is not even more difficult than in the temperaturelimited case. But having just seen that the space charge works rather like automatic grid bias, counteracting changes in anode current, we should not find it hard to understand that it has a cushioning effect on irregular emission, as indeed experience confirms.

In our ignorance of the extent of this noise-reducing or smoothing effect it can be brought into the formula for the temperature-limited valve as a factor, say S:

 $I_N^2 = 2 SeI_aB$

It is found that S can be as small as 1/50, signifying a 50-fold reduction in noise, but something like 1/5 is more usual. Note that this is in a formula for I_N squared, which is proportional to noise power; don't confuse it with an equivalent factor (= \sqrt{S}) that is sometimes used in the formula for I_N.

The question of noise in diodes seldom arises except when they are used as frequency changers in microwave receivers—so we pass on to amplifying valves, especially those that might be considered for first-stage positions. One of the things designers want to do is compare valve noise with circuit noise. As we have seen, the only circuit that matters very much, usually, is the grid circuit of the first stage. The amount of effort worth expending on reducing this depends on how much noise the valve contributes. If circuit noise is given in microvolts at the grid, and valve noise in microamps in the anode circuit, one has to do calculations to find out which is greater,

and by how much. It is of course possible to find how many microvolts at the grid would cause that number of microamps of noise, but direct comparison with circuit noise microamps would be vitiated by the fact that both figures depend on the respective frequency bandwidths, and it would be a coincidence if they were equal.

So the convenient custom is to express valve noise in terms of the resistance which, if included in the grid circuit of a noiseless but otherwise similar valve, would cause the same amount of noise. Let us call this imaginary resistance R_N. According to the formula we already have for the noise voltage at the terminals of a resistor,

$$V_N^2 = 4kTBR_N$$

 I_N is related to V_N by the mutual conductance, g_m :

$$I_{N} = g_{m}V_{N}$$

So substituting $2SeI_aB/g_m^2$ for V_h^2 in the previous equation we get

$$\frac{2SeI_{,B}}{g_{m}^{2}}=4kTBR_{N}$$

$$\therefore R_{N} = \frac{SeI_{a}}{2g_{m}^{2}kT}$$

This doesn't get us where we want, unless we know S. The rather difficult working-out I mentioned gives

$$S = \frac{1.28 \text{ k T}_c \text{ g}_m}{\text{e I}_a}$$

where T is the temperature of the cathode. Substituting this in the equation for R_N we get

$$R_{N} = \frac{0.64 T_{c}}{g_{m} T}$$

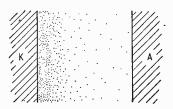


Fig. 4. The many electrons emerging from the cathode, on the left, form a negative space charge that neutralizes the distant positive charge on the anode and restricts further movement towards it. The surplus electrons are forced back to the cathode.

The cathode temperature T_c is usually about $1130^{\circ}K$ and the room temperature T about $290^{\circ}K$,

$$R_{N} = \frac{2.5}{g_{m}}$$

Because of the various assumptions in the smoothing theory, as well as the temperatures, this conveniently simple formula is far from precise, but it does at least give a rough idea. A moderate $g_{\rm m}$ for a triode is 2.5 mA, which makes $R_{\rm N}=1 {\rm k}\Omega$.

At frequencies less than say 30 Mc/s, noise resistance of this order is hardly worth bothering about as a noise source, compared with the usual grid-circuit resistance, to say nothing of manmade noise and atmospherics, both of which are worse at the lower frequencies. At very high frequencies, however, all these other noises are so much reduced that shot noise is appreciable and choice of first valve is correspondingly important. And at these same frequencies another effect adds to random noise. It concerns the electrons streaming through the grid.

We are still assuming that the grid is kept sufficiently negative to prevent any electrons landing on

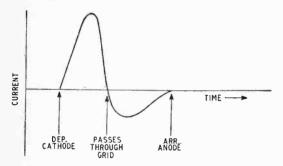


Fig. 5. An electron flying from cathode to anode through a control grid induces a grid current as shown.

it. But during the first step of an electron's journey to the anode it is moving towards the grid, so it induces a small current in the grid circuit, just as was explained in connection with Fig. 2 for the anode circuit-though the waveform is unlikely to be quite the same. After it has passed through the grid it induces a current of opposite polarity; see Fig. 5. The duration of this cycle is of course the transit time, which we have already noted is usually of the order of 10 -9 sec. At moderate signal frequencies this is too quick for the grid potential to change appreciably, so the positive and negative portions of Fig. 5 represent equal amounts of work, and cancel out. But at very high signal frequencies the grid potential changes appreciably during the transit time and the resulting inequality of positive and negative work causes a loss in the grid circuit. This loss can be represented by a resistance. Being in parallel with the grid circuit, it is one of the things that make the net resistance low at very high frequencies. At the moment, we are not directly concerned with that; what does concern us is that this resistance depends on the rate at which electrons pass the grid, and as that varies randomly the resistance varies and causes noise.

Even at low radio frequencies one naturally

uses a pentode rather than a triode, mainly for the sake of the screening it provides between grid and anode. The need for this is even greater at v.h.f. But it was soon found that at v.h.f., where noise is the limiting factor, a pentode is much noisier than a triode. This was traced to the fact that the second grid intercepts a fraction of the anode current. A row of waitresses with trays, widely spaced across the conference refreshment room, would waylay some of the delegates; each one thus intercepted would reduce the number arriving at the buffet, and thereby modulate that stream in a random manner.

It is easy to see that any current-taking grid introduces an additional random element and hence noise; but since the grid current is seldom as much as one-fifth of the whole, we might expect its noise contribution to be in that proportion and therefore not enough to worry about. But whereas the shot noise due to random emission, common to triodes and pentodes, is reduced by space charge to perhaps a tenth, there is no such luck with partition noise (as it is called). So it is usually at least double the emission noise.

I haven't left myself space to go into details about its derivation, but the rough formula for pentodes, corresponding to $2.5/g_{\rm m}$ for triodes, is

$$R_{_{N}} = \frac{I_{_{a}}}{I_{_{a}} + I_{_{g2}}} \left(\frac{2.5}{g_{_{m}}} + \frac{20 \; I_{_{g2}}}{{g_{_{m}}}^{^{2}}} \right)$$

Here the first term in the bracket is obviously the emission noise—the triode term reduced to the extent that the space current is diverted from the anode—and the second is the partition noise. Filling in values taken from data for a pentode designed for v.h.f. amplification:

$$\begin{split} R_{N} &= \frac{10}{10+2.5} \Big(\frac{2.5}{7.4} + \frac{20\times2.5}{7.4^2} \Big) \\ &= 0.8 \ (0.34+0.92) \ k\Omega \\ &= 270\Omega + 730\Omega = 1000\Omega \end{split}$$

So the total is about 3 times what it would be as a triode (340Ω) . That accounts for the urge to use triodes for the first stages of sensitive v.h.f. receivers, however unsuitable they appeared for the task. The first expedient to make them work there was to arrange them with earthed grid as a screen between input and output. This method has now been generally superseded by the cascode arrangement, in which a double triode secures the advantages of a pentode without its disadvantages.

At the lower frequencies it is common practice to make the first valve the frequency changer. The higher the frequency, the greater the temptation to do so, since it becomes difficult to coax amplification at the original frequency. But the signal/noise ratio of frequency changers is several times worse than that of amplifiers, so even a little r.f. amplification is not to be despised. The reason is that the effective amplification of a frequency changer is related to g_e , the conversion conductance, which is only about $\frac{1}{3}$ of g_m , whereas the noise is at least

(Continued on page 627)

as great; in fact, slightly greater, owing to the oscillator. The rough formula for a triode is

$$R_{\scriptscriptstyle N}=rac{4}{g_{\scriptscriptstyle c}}$$

and for a pentode

$$R_{N} = \frac{I_{a}}{I_{a} + I_{g2}} \left(\frac{4}{g_{c}} + \frac{20 I_{g2}}{g_{c}^{2}} \right)$$

These speak for themselves, which is just as well,

for the closing bell may sound any minute.

Lastly, there are the heptodes, hexodes, etc., which can be lumped together as multi-grid frequency changers. The more current-carrying electrodes, the more noise is introduced by random partition; so valves in this class are the worst of all, and would never be chosen for the first stage of a sensitive v.h.f. receiver. The formula is

$$R_{N} = \frac{20 I_{a} (Ik - I_{a})}{Ik g_{c}^{2}}$$

where Ik is the cathode current. I suggest you look up a valve data list and work out a few values of R_N in the various classes. Remember, of course, to use consistent units—mA and $k\Omega$, or A and Ω .

We have been concentrating rather heavily on the high end of the frequency scale, because that is where random noise is the thing that limits reception, and also the transit-time ingredient increases with frequency. For the sake of completeness mention should be made of flicker effect,

which seems to be due to comparatively slow changes at the cathode surface causing random variations in emission. At any rate, it is important only at low a.f. and below, where it increases steeply. In badly made valves there is yet another cause of random noise: ionization, due to inadequate vacuum. Of course it inevitably occurs in gas-filled valves even when (in fact, because) they are properly made, and such valves are sometimes used as sources of random noise for testing. In case any reader is not up in the jargon, perhaps I had better mention that random noise, in so far as it is distributed equally over the whole frequency spectrum, like white light in the visible band, is often called white noise.

In brief: all valves are subject to shot noise because of random emission. In nearly all, this effect is considerably muffled by the space charge. So diodes and triodes on the whole are relatively quiet. Current carrying grids introduce further noise (partition), which is not muffled. So pentodes are usually several times worse than triodes. Valves used as frequency changers are relatively noisier than as amplifiers, because they amplify the signal about \(\frac{3}{2}\) less. The order of preference of the different classes of valve in this role is the same as in the straight amplifying role. Beside shot and partition noise, which are very "white," there are gridadmittance noise which increases steeply at the v.h.f. end, and flicker noise which increases steeply at the a.f. end.


Elements of Electronic Circuits

20.—ADDITION AND SUBTRACTION CIRCUITS.

By J. M. PETERS, B.Sc. (Eng.), A.M.I.E.E., A.M.Brit.I.R.E.

MATHEMATICAL operations can be performed on waveforms, especially the square wave, with reasonably accurate results and use is made of this in the field of computation.

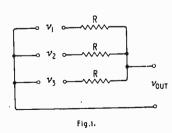It is possible to carry out the operations of addition, subtraction, differentiation and integration without having to resort to valves or other non-linear devices, but accuracy is increased with the aid of the feedback amplifier. The operations of multiplication,



as of multiplication, division, squaring and the extraction of square roots (which will be dealt with later) are very difficult to perform using only linear elements such as resistor networks. Depending on whether accuracy or speed is the govern-

ing factor a choice can be made from several different methods. For example, in multiplication, electromechanical methods may give a high degree of

accuracy, but if speed is desired it will be necessary to use circuits with multi-electrode valves.

Addition and Subtraction


Addition can take a number of forms and the process is met for example in (i) heterodyning in radio receivers, (ii) feedback, where a portion of the output of an amplifier is "added" to the input, (iii) a.g.c. in radio receivers, where the a.g.c. voltage is added to the bias of the earlier variable- μ stages. The simplest form of adding circuit involves linear passive elements such as the parallel-resistor adding circuit of Fig. 1.

$$v_{out} = (v_1/R + v_2/R + v_3/R) (R/3)$$

$$\therefore v_{out} = (v_1 + v_2 + v_3)/3$$

Inductors and capacitors can also be used in simple adding networks of this sort.

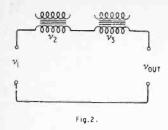The simplest form of subtraction circuit involves a phase-reversing device such as a valve or a transformer. One of the principal drawbacks to the simple addition circuit of Fig. 1 is that at high frequencies stray capacitance effects may distort



the waveforms. This is overcome by inserting a small capacitor in parallel with each resistive branch and a resistor in parallel with the stray capacitances. The time constants (CR) are arranged to be the same. Series


addition circuits are also used for the addition of voltage, e.g. Fig. 2 where transformers are used.

$$v_{out} = v_1 + v_2 + v_3$$

A balanced equal-arm bridge is a useful method of eliminating mutual coupling between the inputs. An example is shown in Fig. 3. Solving the mesh equations by Kirchhoff's laws it can be shown that

$$v_{out} = (Z/2) [v_1/(Z + Z_1) + v_2/(Z + Z_2)]$$

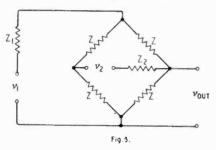
Difficulties are often encountered when it is desired to add voltages with short rise times such as rectangular pulses; but the method of overcoming the stray-capacitance effect described above is usually successful. Transients which produce overshooting and shock-excited oscillations can be minimized by damping and compensating networks. Waveform



shaping (described in an earlier instalment) can also be performed at the same time as addition and helps in compensating for waveform slow rise times.

Use of Valves

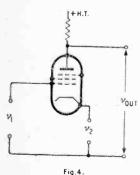
The use of valves in addition and subtraction circuits provides a means of isolating the network from the source voltages and for changing the



impedance levels between network and source. Reasonable accuracy can be obtained by using multi-grid valves as shown in the subtraction circuit of Fig. 4.

 $v_{out} = v_1 - v_2$ Note that the low input impedance at the cathode ($\approx 1/g_m$) makes it necessary to supply the cathode from a low-impedance waveform source.

Alternatively the application of signals to control and screen grids results in the output being the sum of these voltages. Sum and difference voltages

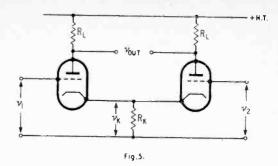

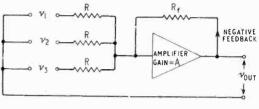


Fig.6

may be obtained from the cathode-coupled paraphase amplifier or long-tailed pair (described in No. 5, September, 1959) (Fig. 5). The difference in voltages appearing at the anodes (v_{out}) is proportional to the difference between the inputs at the grids $(v_2 - v_1)$. On the other hand, the cathode voltage, $v_{\rm K}$, is proportional to the sum of the inputs to the grids $(v_2 + v_1)$.

One of the most useful addition circuits is perhaps the parallel-addition circuit of Fig. 1 followed by stages of amplification with negative feedback (Fig. 6). This gives an output of inverted polarity, compared with the passive network. The advantages are that the amplitude of the output can exceed the input, also that with this circuit only one amplifier is necessary regardless of the number of inputs to be added.

$$v_{out} = (R_{t}/R) (v_{1} + v_{2} + v_{3}),$$

as long as the gain within the feedback loop is high. This presupposes a high value for A, the amplifier gain, and a fairly low numerical value for R₁/R, which is the overall gain of the circuit with feedback.

Commercial Literature

Thirty Transistor Circuits, covering a range of functions including a.f. amplifiers, regulated power supplies, d.c. to d.c. and d.c. to a.c. converters, oscillators and a photographic electronic-flash unit are contained in "Newmarket Transistors—Application Notes" from Newmarket Transistors Ltd., Exning Road, Newmarket, Suffolk.

Molybdenum Disulphide as a lubricant and additive to lubricating solutions can bring about reductions in wear. Booklet on molybdenum disulphide, giving data on applications, from Rocol, Ltd., Rocol House, Swillington, near Leeds.

Silvered-Mica Capacitors made by Johnson Matthey have the electrodes screen-printed, instead of sprayed, on to the mica. The makers call these "Silver Star" and claim that the sharply defined edges of the electrodes aid stability. Booklet describing the process and listing the capacitors from the manufacturers at 73-83, Hatton Garden, London, E.C.1.

Radio and Television Interference. Advice on the tracing and suppression of interference is given in a booklet called "Everyman's Guide to Electrical Interference" published by Belling and Lee, Ltd., Gt. Cambridge Road, Enfield, Middlesex.

DECEMBER MEETINGS

Tickets are required for some meetings; readers are advised, therefore, to communicate with the secretary of the society concerned.

LONDON

2nd. I.E.E.—Discussion on "Telemetering biological data" opened by Dr. G. H. Byford and Dr. K. G. Williams at 6.0 at Savoy Place, W.C.2. 2nd. Brit.I.R.E.—"Progress in

microminiature circuit techniques for digital computers" by D. Roberts, Dr. D. S. Campbell and P. M. Thompson at 6.30 at the London School of Hygiene, Keppel Street, W.C.1.

7th. Institute of Physics and Physical

7th. Institute of Physics and Physical Society.—"The international conference on physics education" by N. Clarke at 6.0 at 47 Belgrave Square, S.W.1.
7th. Brit.I.R.E.—"Flight evaluation of airborne electronic equipment" by H. G. Hinckley at 6.30 at the Longian Keppel Street.

tion of airborne electronic equipment "by H. G. Hinckley at 6.30 at the London School of Hygiene, Keppel Street, W.C.1.

8th. Television Society.—"The all transistor receiver: where do we stand?" by A. Landman (Plessey) at 7.0 at the Cinematograph Exhibitors' Association, 164 Shaftesbury Avenue, W.C.2.

8th. Radar & Electronics Association.—"True motion radar" by J. H. Beattie at 7.30 at the Royal Society of Arts, John Adam Street, W.C.2.

12th. I.E.E.—"Topology concepts in network theory" by Dr. P. R. Bryant at 5.30 at Savoy Place, W.C.2.

13th. Brit.I.R.E.—"Objective and subjective requirements for loud-speakers" by F. H. Brittain at 6.30 at the London School of Hygiene, Keppel Street, W.C.1.

13th. I.E.E. Graduate and Student Section.—"Electrical engineering in the Naval Service" by Sir Hamish MacLaren at 6.30 at Savoy Place, W.C.2.

16th. B.S.R.A.—"Magnetic recording in the home cinema" by D. O'C. Roe at 7.15 at the Royal Society of Arts, John Adam Street, W.C.2.

20th. I.E.E.—Discussion on "Digital transducers" opened by L. Airey at 5.30 at Savoy Place, W.C.2.

21st. I.E.E.—"Microminiaturization" by L. J. Ward at 5.30 at Savoy Place, W.C.2.

13th. I.E.E.—"Wave guides" by Dr. P. J. B. Clarricoats at 6.30 at the Civil Engineering Department, Queen's University, Stranmillis Road.

5th. I.E.E.—"Radiocommunication in the power industry" by E. H. Cox and R. E. Martin at 6.30 at the College of Technology.

6th. I.E.E.—"Thermistors—their theory, manufacture and application" by Dr. R. W. A. Scarr and R. A. Setterington at 6.30 at the College of Technology.

BRISTOL
13th. Television Society.—"Ferrites in television receivers and aerials" by E. C. Snelling at 7.30 at the Hawthorns Hotel, Woodland Road, Clifton.

CHESTER

12th. I.E.E.—"The potentialities of artificial earth satellites for radiocommunication" by W. J. Bray at 6.30 at the Town Hall.

EDINBURGH

5th. Institute of Physics and Physical Society.—" Low noise amplifiers" by

Dr. R. A. Smith at 7.15 at the Univer-

GLASGOW

6th. Institute of Physics and Physical Society.—"Low noise amplifiers" by Dr. R. A. Smith at 7.15 at the Univer-

HOVE

7th. I.E.E.—"Radiocommunication in the power industry" by E. H. Cox and R. E. Martin at 6.30 at 10 Queens Gardens.

LIVERPOOL

14th. Brit.I.R.E.—"V.H.F. sound broadcasting" by L. G. Dive at 7.0 at the Adelphi Hotel.

5th. I.E.E.—"Parametric amplifiers" by R. V. R. Carter and I. A. Bagnall at 7.30 at the Winter Gardens.

MANCHESTER

MANCHESTER
1st. Brit.I.R.E.—"Industrial television" by I. M. Waters at 7.0 at the Reynolds Hall, College of Technology.
7th. I.E.E.—Discussion on "New semiconductor devices" opened by A. A. Shepherd at 6.15 at the Engineers'

21st. I.P.R.E.—"Control systems" by J. Pyke at 7.30 at Central Hall, Old-

ham Street.

NEWCASTLE-UPON-TYNE
5th. I.E.E.—"Radar observations of birds and 'angels'" by Dr. E. Eastwood at 6.15 at the Rutherford College

wood at 6.15 at the Rutherford College of Technology, Northumberland Road. 7th. Brit.I.R.E.—"Human engin-eering" by S. G. Ramsay at 6.0 at the Institution of Mining and Mechanical Engineers, Neville Hall, Westgate Road.

NEWPORT, I.O.W. 9th. I.E.E.—Discussion and demonstration of stereophonic sound at 6.30 at S.E.B. Showrooms.

NORWICH

6th. I.E.E.—"Engineering aspects of commercial television programme presentation" by T. C. Macnamara at 7.30 at the Assembly House.

READING

15th. Institution of Production Engineers.—" Electronic data processing allied to production engineering" by F. W. Purchall at 7.30 at the George Hotel, King Street.

SOUTHAMPTON
6th. I.E.E.—"F.M./A.M. v.h.f. portable transistor receivers" by L. E. Jansson at 6.30 at the University.
14th. Brit.I.R.E.—"Some new piezoelectric devices" by A. E. Crawford at 7.0 at the University

at 7.0 at the University.

STONE
12th. I.E.E.—"Recent developments in colour television" by I. J. P. James at 7.0 at Duncan Hall.

SWANSEA


13th. I.E.E.—Faraday Lecture on "Transistors and all that" by L. J. Davies at 6.30 at the Brangwyn Hall.

WORKINGTON
13th. I.E.E.—"The transmission of news film over the transatlantic cable" by C. B. B. Wood and I. J. Shelley at 7.0 at the College of Further Education.



Model B100

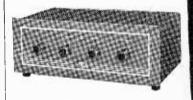Transistorised Amplifier for 12 volt operation. Output 12 watts. Inputs for microphone and music. Minimum battery consumption-maximum effici-



Model GP100

AC operated general purpose high quality Amplifier. 4-way Input Selector-Bass and Treble controls. 10/12 watts output.

> Full details available on request



WIRELESS WORLD, DECEMBER 1960

RANDOM RADIATIONS

By "DIALLIST"

Far-East Colour TV

SO Japan, or at least Tokyo and Osaka, has a colour television service. The man who after a threevear struggle forced a reluctant government to make up its mind on the subject is said to be Mr. Matsutaro Shoriki, president of Nippon Television (NTV), who got the country's 525-line black-and-white service started in 1953. Ordinary television has become so popular in Japan that all but the very poorest now have receivers and the total is over six million. Mr. Shoriki is firmly convinced that there will be a similar boom in colour TV. To get things going he put up colour receivers in various public places. The system used is the N.T.S.C. and it is reported that the Japanese have improved upon the results obtained in the United States. They have apparently not succeeded in developing low-priced domestic receivers; but even though the earnings of factory and other workers are much less than they are in America, Mr. Shoriki is convinced that colour sets will sell. Japan, it appears, is well provided with "never-never" facilities.

What About Us?

After five years of experimental colour transmissions the B.B.C. has announced that, technically at any

rate, it is ready to start a regular service, if and when permission is given. The radio industry doesn't feel that the time is yet ripe, for no manufacturer in his senses—and ours are very much in theirs—wants to go into the production of colour receivers unless there is likely to be a good demand for his wares. The big snag is the cost of the receiver, governed largely by the cost of the three-colour tube, and, frankly, I don't think that our people would go for them in a big way unless this can be greatly reduced.

DX Printing

THE setting of the type of the New York and Paris editions of the New York Times simultaneously is a very remarkable feat. The Paris edition now goes to press at the same time as the early edition in New York. The setting is done by a tape perforated by means of wireless signalsthe transatlantic cable will be used if radio conditions are bad-which is fed into linotype machines. Naturally some of the type-setting will be done in the ordinary way in Paris, for purely local American news won't be carried in the French edition, the space being devoted to happenings on this side of the Atlantic. Many of the advertisements will be different. Owing to the time difference-Paris is six hours ahead of New York-the

Paris issue must derive from a very early American edition. But, of course, the U.S.A. is a large country and very early editions are needed if the paper is to appear on distant breakfast tables.

Anti-mortar Radar

IN collaboration with the Royal Radar Establishment, E.M.I. have developed a new type of radar equipment for which substantial contracts have been placed by the War Office and by the Swedish army. This equipment enables mortar shells or bombs to be tracked in flight and makes it possible to calculate accurately and quickly the exact position from which they were fired. It is small and highly mobile and is said to be very easy to operate. Something of the kind was done towards the end of the last war with ordinary radar sets. They were used to spot shells as they left an enemy battery and proved very useful in Italy for pin-pointing hostile battery positions with considerable accuracy.

I.G.Y. No. 2

THERE are plans afoot, I see, for holding a second International Geophysical Year on a smaller scale at the time of the next sunspot minimum, which is due to come along in about four years' time. The idea is that we can get to know a good deal more if we compare the happenings recorded during a period of maximum solar activity with those which occur when such activity is at a minimum. An excellent scheme and may it have the success it deserves. Completely satisfactory explanations of some of the phenomena of I.G.Y. No. I haven't so far been found and the second series of observations may help to clear things up.

TV Progress in France

AT long last television seems to be really getting into its stride in France. At the end of June this year the total of "declared" sets had risen to 1,700,000. And there's pretty sure to be a largish number of undeclared, or pirate receivers, as undoubtedly there is in this country. The French transmitter, booster and relay net-

"WIRELESS WORLD" PUBLICATIONS ASSOCIATED LIFFE By Post Price CORRECTING TELEVISION PICTURE FAULTS John Cura and Leonard Stanley. 4th Edition 4/-4/6 26/-INTRODUCTION TO LAPLACE TRANSFORMS for radio and electronic engineers. W. D. Day, Grad.I.E.E., A.M.Brit.I.R.E. 32/6 33/6 MICROWAVE DATA TABLES. A. E. Booth, M.I.R.E., Graduate I.E.E. . . 27/6 28/8 FOUNDATIONS OF WIRELESS M. G. Scroggie, B.Sc., M.I.E.E. 16/-17/4 30/-31/9 18/-19/~ WIRELESS SERVICING MANUAL, 9th Edition. W. T. Cocking, M.I.E.E. 17/6 18/8 A complete list of books is available o application. Obtainable from all leading booksellers or from ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1

work is not yet complete and where transmissions have only recently begun the increase in the number of viewers has so far proved surprisingly slow. And that is unfortunately true of certain other regions which have had a service for some time. Alsace, for instance, can boast only 28,900 receivers, though the Strasbourg transmitter has been at work ever since TV began in France.

Bigger and Bigger

THEY like big things in the U.S.A. and whatever sized TV screen comes along there's always a demand for something a bit larger. Having introduced 27-inch sets comparatively recently some of the manufacturers now have plans for 29-inch sets. I'd have thought that the best way of getting a really big picture would be to make use of projection techniques. But that doesn't seem to have caught on over there any better than it has done here. Talking of screen sizes reminds me of a conversation between two fishermen that I overheard on a boat not long ago:

"How big's your TV set?"

"Fourteen inches."

"Oh, you want something bigger than that."

"Does me all right."

"But don't you see you're missing a lot of the picture."

"How do you mean?"

"Stands to reason. A screen of that size isn't big enough to take the whole picture that's sent out. The same sized picture is sent to everyone; but if your screen is small, some of it laps over the edges and you can't see those bits."

"Oh, I hadn't thought of that." Frankly, I hadn't either!



Roger and Out, Sir.





A. F. BULGIN & CO. LTD., BYE-PASS RD., BARKING, ESSEX.

Telephone RIPpleway 5588 (12 Lines)

Unlicensed Sets

HOW many unlicensed sets are there in this country? I am told that a recent industrial survey covering car radio showed that only about 50% of the sets were licensed. It does not surprise me in the least to hear this opinion, and I think the proportion in the case of domestic sets is fully as had sets is fully as bad.

Look for example, at the numerous houses which are let out in what are euphemistically called one-room flats. In these days of miniaturized transistor sets, I wonder how many of the tenants—some of whom are very transient—bother about a licence? I would go even further and say that in a great many cases the owners of these sets think that the licence—if any—of the landlord

covers them.

When a householder changes his address he can fill in a form for letters to be redirected and one of the questions asked on the form is for particulars of his wireless licence. if any. If he has no licence he is asked to write "None." The non-licence holder can write "None" with a perfectly clear conscience; at any rate that part of his conscience which deals with truth-telling will be clear, if, indeed, a conscience can be compartmented, as so many people obviously think, judging by their behaviour. It would seem to be more useful to ask if the form-filler had a receiver, but there would, of course, be little point in it unless it were made an offence to give a false

But all the same, the very fact of a person having to fill in particulars of his licence or else write "None" might have the same psychological effect on a guilty conscience as does the presence of a G.P.O. wireless detector van in the neighbourhood.

Even so, only the householder is affected because it is clearly stated in the Post Office Guide (July, 1960 edition, page 67) that the P.M.G. will not undertake to re-direct the correspondence of those in lodgings, etc., and therefore, the people whom I regard as the real offenders, namely sub-tenants or lodgers, do not receive even the psychological stimulus of answering the questions about licences on the mail redirection form.

I am quite aware a G.P.O. inspector has authority to call at any time and inspect the wireless installation of a licence holder. But he certainly can't demand entrance to the home of a non-licence holder but must apply to a Justice of the Peace for a search warrant, after first satisfying the I.P. that he has reasonable grounds for suspicion. But Section 15 of the Wireless Telegraphy Act of

1959 only mentions a search warrant for premises. It makes no mention of a search of the person of a suspect which would, therefore, be ultra vires. In these days of tiny transistor sets, a radio receiver can easily be concealed in a man's pocket, or even in the corsage of a lady's dress. If an over-zealous Post Office official dared to search in the latter place, he would find himself on very dangerous ground indeed. Supposing the lady in her haste to conceal the set had inadvertently knocked the switch to the "on" position, it would be very galling but singularly apt if, as the perspiring official searched the room, the strains of "Music While you Work" burst forth from the depths of her person. He could only gaze at her in baffled impotence, knowing full well that he dared not search her. It would be truly an apoplectogenic situation.

At one time the outdoor aerial made it obvious when a TV set was installed but in these days more and more indoor aerials are in use, and before many years have gone by, we shall all be using sets with built-in

aerials.

Could not a question about wire-less licences be included in the census form which we shall all have to fill in on April 23rd next, or better still, could not such a question be put in the form which we all receive annually for the compilation of the electoral roll.

In my opinion, if every person who ought to have a licence did, in fact, have one, the B.B.C.'s revenue would be increased considerably.

Cymatology

RECENTLY, when reading an interesting article by a learned professor who is also a Fellow of the Royal Society, I was a little surprised to find that when he mentioned electromagnetic waves, he appended in parentheses the explanatory words, light waves or radar waves." was at once clear to me that he was not writing for his peers, who would naturally not need to be told what electromagnetic waves do for a living; nor, I realized, could he be writing for people having a slightly lesser standard of knowledge, pos-sessed, for instance, by those who have only just matriculated in Wireless World readership.

It was only after further thought that it suddenly dawned on me that the writer (Professor J. L. Synge) had chosen the words "radar waves" with that careful and precise thought which one associates with an F.R.S., and that he may have intended it as an indirect rebuke to all those of us who use the vague and unsatisfactory

word "radio" in such phrases as "radio receiver" and "r.f. amplifier."

When all is said and done, the true definition of a radio wave is one which is radiated in any medium. There is nothing to restrict the word radiation (and, therefore, radio) to the electromagnetic spectrum except customary usage or, more correctly, misusage; if that be allowed to influence us we cannot cavil at the great majority of our fellow citizens who misuse the lovely old English abbreviation "ain't," and pervert it from its true meaning.

It is clear that electromagnetic waves are merely a subdivision of radiated waves (or, in other words, of radio waves). Sound waves also are undoubtedly radiated and, in like manner, if we drop a stone into a pond, do we not bring about the radiation of surface waves in the water in ever-widening circles? The O.E.D. lends support to my views as it tells me, inter alia, that radiation is "the manner in which the energy of a vibrating body is transmitted in all directions by a surrounding medium"; it does not

define the medium. The word "radar" which the pro-fessor uses has a very clear and precise meaning, for it was synthesized



Searching for my stud with e.m. waves.

from the initial letters of words defining a particular application of e.m. waves, and has nothing to do with the altosonic or supersonic waves which bats use for a similar

We ought, therefore, to rename our radio receivers, and also cease to talk of an r.f. amplifier. But we must be careful not to adopt the name e.m.w. receivers for, obviously, that could equally well mean a camera, and it would certainly lead to confusion if we spoke of an e.m.f. amplifier even though the set-up which we call an r.f. amplifier is, in fact, a voltage amplifier. I do feel that only a person with the precise mind of an F.R.S. could help us straighten out our nomenclature; but probably some of you may have some good ideas?

AVO INSTRUMENTS

Made within the shadow of Big Ben, AVO instruments enjoy a reputation for reliability which, like the chimes of this famous Tower, reaches the farthest corners of the world.

D.C. Amplifiers **Radiation Monitors** Valve Voltmeters **Multi-range Testmeters Valve Testers** and other electronic and nucleonic instruments

ALYO LTD

AVOCET HOUSE

92-96 VAUXHALL BRIDGE ROAD

LONDON

Cables: Avocet, Sowest, London

RANGE.


Fastest service

... consistent quality . . . this is the triumvirate which induces so many premier organizations to rest their resistor needs in our hands. Post a card for our illustrated stock book issued alternate months. Indicate your particular interests - once you are on our mailing list you will be automatically notified of new resistor developments.


P.S. Our prices are very competitive too!

CARBON	WATTS	OHMIC RANGE	TOLERANCES ±
I. Solid	1/10—1/2 I and 2	10—10M	5% 10% 20%
2. Cracked	1/30	IΩ-10M	5% and 10%
5. V. High Resistance	1/4-3	50M — 1013	5% — 25%
6. * High Stability	$\frac{1}{10} - 2$	I — 50M	0.5% 1% 2% 5%
7. High Stability encapsulated in Epoxy Resin	1/4, 1/2,	10Ω — 4·7M	1% 2% 5%
4. Metal Oxide Precision	1/4-2	100 — 4·2M	1% 2% 5%
WIREWOUND		,	
8. Vitreous	1-500	I — 150K	1% 2% 5%
3. Cemented	1/2-15	I — 25K	5% and 10%

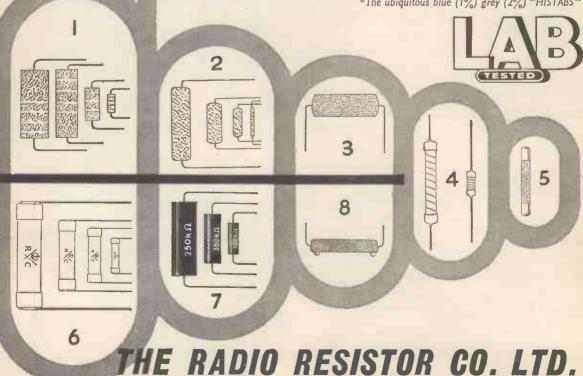*The ubiquitous blue (1%) grey (2%) "HISTABS"



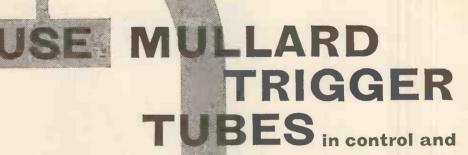9-11 PALMERSTON ROAD, WEALDSTONE, HARROW, MIDDX. Tel: HARrow 6347



Life and Reliability

Mullard cold cathode tubes offer a life expectancy and reliability comparable with the highest quality components used in electronic equipment.

switching circuits for...

High Sensitivity

Only a small energy pulse is required to "trigger" the main discharge. A gain of 100,000 may be achieved.

Instantaneous Operation

Cold cathode tubes are always ready for instantaneous operation. They are ideal for stand-by and intermittent duty applications.

The Mullard range at a glance

- **Z700U** Low cost subminiature tube for use in computing/switching circuits.
- **Z700W** Subminiature tube with two trigger electrodes for use in reversible ring counters.
- **Z701U** Subminiature tube particularly suited for speech passing in electronic telephone exchanges.
- **Z803U** Extremely stable, close tolerance miniature tube.
- **Z900T** Miniature tube intended primarily for intermittent operation from d.c. or 115 volt a.c. supplies.

Full information on the range of Mullard trigger tubes is available—please write or telephone Mullard House.

MULLARD LIMITED


Mullard House • Torrington Place London W.C.1 · Tel: LANgham 6633



GOVERNMENT AND
INDUSTRIAL VALVE DIVISION





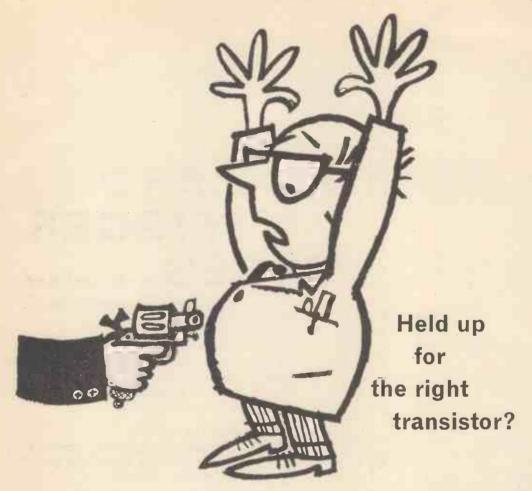

When you find yourself in the sort of situation where you have to come across with the right transistor or else—when either you've got it or you've had it—give us a shout. We have developed many special types of transistor for a number of unusual applications. A request from you will bring full particulars.

EDISWAN

SEMICONDUCTORS

THIS COULD BE IT!

DID YOU SAY A GERMANIUM JUNCTION TYPE

NPN SWITCHING TRANSISTOR

WITH A MINIMUM

FREQUENCY CUT OFF OF 3, 5 or 10 Mc/s.

Then the transistor to get you out of trouble is either the

EDISWAN MAZDA XA701 · XA702 or XA703

Associated Electrical Industries Limited


Radio & Electronic Components Division

Semiconductor Department, 155 Charling Cross Road, London W.C.2

Tel: GERrard 8660 • Telegrams: Sieswan Westcent London

CRC 15/80

Transistorized UNIVERSAL COUNTER TIMER

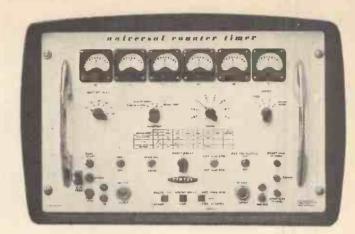

Frequency Measurement

Random Counting

Frequency Division

Time Measurement

Frequency Standard

This fully transistorized portable equipment provides for a wide range of time and frequency measurement as well as facilities for counting, frequency division and the provision of standard frequencies. The facilities available are briefly listed below:

TIME/UNIT EVENT (1 LINE): For the measurement of the time interval between two occurrences in a continuously varying electrical function in the range 3μ sec to 1sec. The time for 1, 10 or 100 such events can be measured.

TIME/UNIT EVENT (2 LINE): For time measurement in range 1 μ sec to 2777hrs. of any interval defined by a positive or negative going pulse in any combination.

EVENTS/UNIT TIME: For frequency measurement in range 30c/s to 1 Mc/s over period of 0.001, 0.01, 0.1, 1 or 10 secs. Crystal accuracy ± 2 parts in 10°/week. For mains or 12Vd.c. operation.

Full technical specification available on request.



RANK CINTEL LIMITED

WORSLEY BRIDGE ROAD · LONDON · SE26

HITHER GREEN 4600

advanced Microwave Sub-Units for special applications

The accumulated knowledge and experience of Mullard Equipment Limited are demonstrated in their ability to produce microwave units which are both advanced in design and dependable in operation. Typical of recent developments is the L324 isolator described here. Other current developments include X-band isolators, circulators, co-axial mixers, switches and folded tees.

If you have a microwave problem just write to the address below. A wealth of experience will be at your disposal to provide the answer.




L324 X-band Isolator

This isolator is a ferrite loaded waveguide component with unidirectional characteristics designed to isolate an X-band microwave source from reflections caused by mismatch. It is suitable for incorporation in equipment or for use as a laboratory aid and is tunable for peak performance over X-band.

MULLARD EQUIPMENT LIMITED

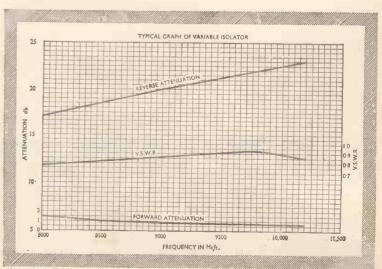Mullard House • Torrington Place • London WC1 Telephone: Langham 6633



...again!

first again

now with 23" teletubes

BRIMAR exhibited the first British-made 23" teletube in this

110° with tripotential electrostatic focus

country....it is now in production!

- Virtually right-angled corners
- Flat faced
- Nominal overall length of 13%




Brimar Limited



3 STAR

AK 5



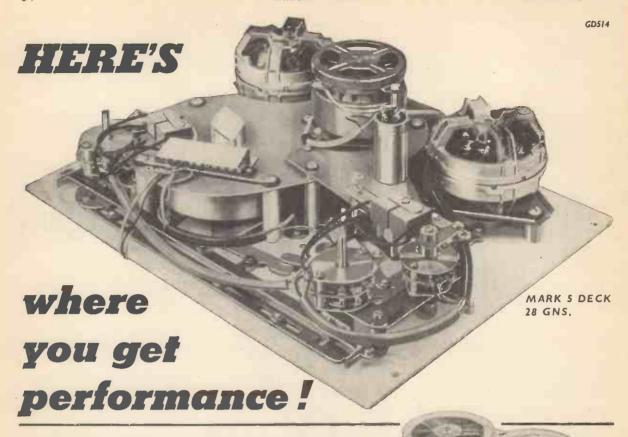

A tape recorder is only as good as its deck. This is where precision in manufacture and assembly is vital for professional standards of recording and reproduction. In the Brenell Mark 5 deck there's a rare combination of advanced technology and an almost-forgotten kind of craftsmanship.

The Mark 5 deck has a remarkable, new main motor of a type widely regarded as the most effi-cient to be used in tape recording. The HYSTE-RESIS SYNCHRONOUS MOTOR, with a balanced outer rotor and a heavy, statically and dynamically balanced flywheel. It brings 'wow and flutter' down to below .1% at 7½ ips!

This and the other components providing the specifica-tion shown below are assembled with fanatical care. Brenell Mark 5 (and all other equipment) production is an individual task which is repeatedly checked and tested. Nothing less than mechanical and electrical perfection will do.

At 28 gns., you'd be missing a great deal to pay less and there's no need to pay more.

Abridged specification
3 INDEPENDENT MOTORS
4 RECORDING SPEEDS
FAST REWIND in either direction. 1,200ft. reel rewound in 45 seconds.
WOW AND FLUTTER

FREQUENCY RANGE: Below .05% at 25 ips | 15 ips: $50/16,000 \text{ c/s} \pm 3\text{db}$ Below .1% at $7\frac{1}{2}$ ips | $7\frac{1}{2}$ ips: $60/12,000 \text{ c/s} \pm 3\text{db}$ Below .15% at $3\frac{3}{4}$ ips | $3\frac{3}{4}$ ips: $60/7,000 \text{ c/s} \pm 3\text{db}$ Below .25% at $1\frac{1}{4}$ ips | $1\frac{7}{4}$ ips: $60/4,000 \text{ c/s} \pm 3\text{db}$

SELECTIVE FREQUENCY CORRECTION at 15, 7½ and 3½ ips.
ACCEPTS 8½in, REELS, PAUSE CONTROL, DIGITAL REV. COUNTER,
PROVISION FOR EXTRA HEADS.

Brenell

TAPE RECORDERS: 3 STAR. 58 GNS. MK. 5. 64 GNS. 3 STAR. RIP STEREO. 89 GNS.

MK. 5 R/P STEREO £99 . 12 . 0

* I track available with 3 Star models

ss of your nearest stockist from the Sole Manufacturers BRENELL ENGINEERING CO. LTD. · 1a DOUGHTY STREET · LONDON · WC1 CHANCERY 5809 & HOLBORN 7358



The 4300 range of carbon film resistors is available where a reliable high stability close tolerance resistor is required for use in critical circuits.

The range comprises five main groups— $\frac{1}{10}$ W., $\frac{1}{4}$ W., $\frac{1}{4}$ W., and 1 W. Within the limits listed below resistors are available in all preferred values. Other values can be supplied to Order.

- 4302 1 WATT-RESISTANCE 10 Ω to 10M $\Omega \pm 1\%$
- 4303 $\frac{1}{4}$ WATT-RESISTANCE 10 Ω to 7.5M Ω ± 1% (approved to RC2.C of RCS.112 from 10 Ω to 1M Ω)
- 4304 $\frac{1}{2}$ WATT-RESISTANCE 10 Ω to 5·1M Ω ± 1% (approved to RC2.D of RCS.112 issue 2 from 10 Ω to 1M Ω)
- 4305 $\frac{1}{4}$ WATT-RESISTANCE 4-3 Ω to 4-7M Ω ± 1% (approved to RC2.E of RCS.112 issue 2 from 10 Ω to 1M Ω)
- 4307 1/10 WATT-RESISTANCE 10 Ω to 470K $\Omega \pm$ 5% Send for Data Sheets CFR



Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

RECTIFIER DIVISION: EDINBURGH WAY . HARLOW . ESSEX




PYE T.V.T. LIMITED - INDUSTRIAL DIVISION 9, Upper Berkeley Street, London W.I. Telephone: AMBassador 3044



magnetic materials

from STC

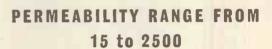

'Stanferite' is the latest magnetic material to be added to the already well known STC range of Permalloy powder, strip and Permendur products.

'Stanferite' is a non-metallic material having high resistivity with consequent low eddy-current losses. This characteristic enables it to be used at much higher frequencies than was previously possible with metallic materials of similar permeability.

'Stanferite' can be supplied in the form of pot cores, cylinders, rings and "U"-shaped pieces to meet most applications.

Material	Initial Permeability	Frequency range of application	Typical applications	Typical Core Shapes	
S.F.1 S.F.15	2 000 to 3 000 1 100 to 1 900	Up to I Mc/s Up to I Mc/s	(Manganese Zinc Ferrites) — both of which have high permeability and low-loss at frequencies up to 1 Mc/s. Wide band and Miscellaneous Types of Transformers High quality Inductors, Communication Transformers, Delay Lines and Recording Heads.	··U" Pot	
S.F.3 S.F.11 S.F.14	100	Pulse	(Mixed Ferrites)—having substantially rectangular hysteresis loops and therefore eminently suitable for data-processing applications. Memory Arrays and Switching for Data Processing.	Small Toroid and Magnetic Cell	
S.F.4 S.F.5 S.F.6	650 250 100	50 kc/s to 2 Mc/s 200 kc/s to 5 Mc/s 500 kc/s to 15 Mc/s	(Nickel Zinc Ferrices) — having extremely low eddy-current and dielectric losses rendering them useful over a very wide frequency range up to 150 Mc/s. H.F. Transformers and Inductors, Tuning Coils, Saturable Reactors.	Toroid, "U" Pot and	
S.F.7 S.F.8	30 15	I Mc/s to 50 Mc/s IO Mc/s to 150 Mc/s		Cylinder	

Write or telephone for Technical Data Sheets to:-




Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

MAGNETIC MATERIALS SALES DEPT : EDINBURGH WAY . HARLOW . ESSEX

Where great things are done

with Microwaves

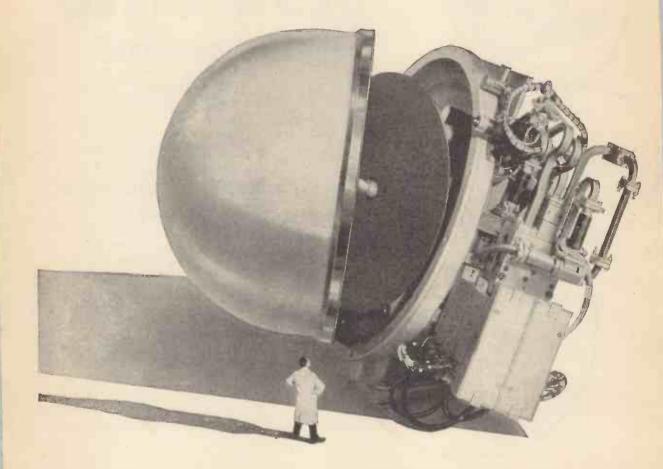

RADAR: Fire Control · Navigation of Aircraft and Small Ships · Automatic Landing · Missile Guidance · Transponders · COMMUNICATIONS: Multichannel Radio Links for telemetering Data and Speech • VALVES: Klystrons and Magnetrons for 35 Gc/s and 75 Gc/s bands • Monitor Diodes for I Gc/s to 35 Gc/s • INSTRUMENTS: Comprehensive Waveguide measuring circuits covering 6 to 75 Gc/s • RESEARCH: Outstanding Research and Development of the latest techniques.



COMMUNICATIONS DIVISION . RADAR DIVISION . VALVE DIVISION MICROWAVE & ELECTRONIC INSTRUMENTS DIVISION . RADAR RESEARCH LABORATORY

ELLIOTT BROTHERS (LONDON) LTD

Elstree Way, Borehamwood, Hertfordshire · Elstree 2040 Airport Works, Rochester, Kent · Chatham 4/4400



EA A MEMBER OF THE ELLIOTT-AUTOMATION GROUP



the name to remember for

INDUSTRIAL TYPE TRANSISTORS

BIDIRECTIONAL GERMANIUM TRANSISTORS

(Effectively symmetrical in significant parameters)

TYPES TK 20 C, TK 25 C

For high frequency switching circuits (cut-off frequency greater than 8 Mc/s with the TK 25 C), or small signal amplification.

ASYMMETRICAL GERMANIUM TRANSISTORS

TYPES TK 30 C, TK 31 C

For high frequency switching circuits (cut-off frequency greater than 8 Mc/s with the TK 31 C), these are asymmetrical versions of the TK 20 C and TK 25 C respectively.

TYPE TK 23 C

For general purpose low and intermediate frequency applications and telephone and telegraph carrier systems.


TYPES TK 40 C, TK 41 C, TK 42 C

For audio and intermediate frequency oscillators and amplifiers requiring high gain and a power output of several hundred milliwatts.

SILICON TRANSISTORS

TYPES TK 71 C, TK 72 C

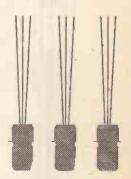For amplification, switching and control in extremes of ambient temperature; and having excellent saturation characteristics at high collector currents, unusual in silicon transistors.






Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

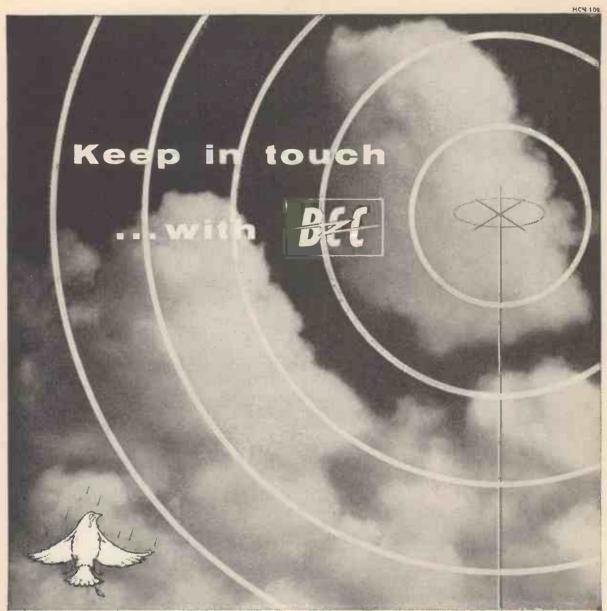TRANSISTOR DIVISION: FOOTSCRAY . SIDCUP . KENT



Keep in touch-with BCC and the latest in communications techniques.

BCC's Type 400/100 VHF 15-watt Fixed Station makes other means of communication look a little old fashioned. It's designed for the control of mobile systems, point-to-point links, ground/air communications and similar uses. Two-way, single or dual frequency simplex, or duplex operation. Auxiliary units are available for extended or remote simplex or duplex operation. A fully-descriptive leaflet is available.

Consult our Systems Planning Service for full Information and guidance on communications systems planning

BRITISH COMMUNICATIONS CORPORATION LIMITED


High Wycombe, Bucks

Tel: High Wycombe 2501


Cables: BeeCeeCee High Wycombe

And at Wembley



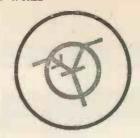




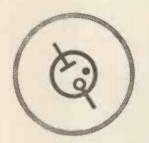

RELIABLE PERFORMANCE demands

TC COMPONENTS

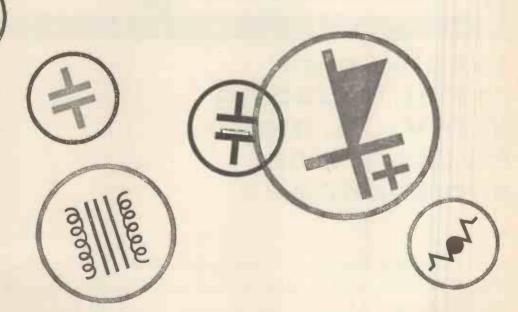The standard of reliability of STC components is set by the vital roles of the navigation and communications equipments in which many of them are used. The consequent employment of top grade materials and high degrees of skill and care in manufacture ensures that all users of STC components may have the fullest confidence in them.



YOU CAN RELY ON STC COMPONENTS

Brimistors

Capacitors · Contact Cooled

Rectifiers **Ferrites**

Germanium Diodes

Germanium Photocells

Hermetic Seals . High

Stability Resistors · Magnetic

Materials Quartz Crystals

Relays · Special Valves

Selenium Rectifiers · Silicon

Rectifiers - Silistors

Suppressors · Transistors

Thermistors Transformers

Zener Diodes

Get to know the range of STC Components—write for booklet M103 which lists all components and their relevant technical literature.



Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London W.C.2.


COMPONENTS GROUP

FOOTSCRAY

SIDCUP

KENT

meters made to measure

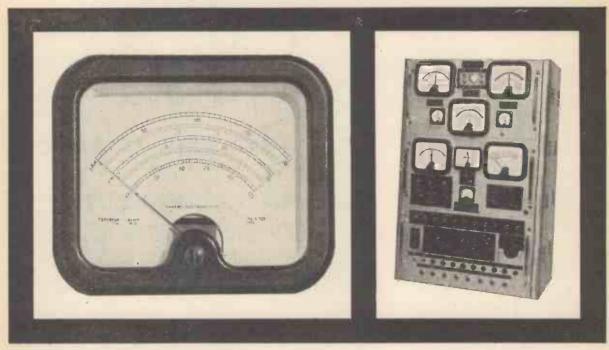

seven-range meter, including V, mV, µA, made for Elliott's at short notice

This seven-range meter, using Ernest Turner Model 605 was calibrated with special ranges by Anders at short notice for Elliott Brothers Ltd for the special-purpose test gear shown above. All the meters in this complex installation were supplied by Anders, who have the pleasure of carrying out similar work for a number of famous manufacturers. Anders are indebted to Elliott Brothers for kind permission to illustrate this equipment.


DECEMBER, 1960

The Anders Instrument Centre commands the largest stocks of meters in the country, unique calibrating facilities, and detailed knowledge of metering problems. Most standard meters are supplied immediately. Non-standard meters of all kinds, shapes and sizes, for special voltage and current ranges, are accurately calibrated, tested and normally ready within 10-14 days. Makes include Avo, Crompton Parkinson, EAC, Elliott, Pullin, Taylor, Turner, Weir, Weston. Types include moving coil, moving iron, thermocouples, electrostatic, dynamometers, from $1\frac{1}{2}$ to large switchboard instruments, and complete range of accessories. Please write or 'phone for details of the Anders meter service.



ELECTRONICS LIMITED

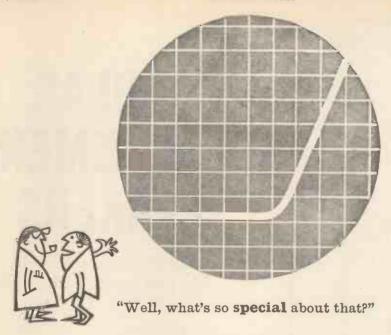103 Hampstead Road, London NW1. Tel: EUSton 1639
Contractors to GPO and Government Departments.
Ministry of Aviation approved.



"O.K.—it's an ordinary characteristic but what isn't so ordinary is that we have got definition of this valve's performance. Definition in a special way that is. For instance, we know just what 'spread' we can expect in every batch that is delivered, and we have an indication of the spreads that we can expect over life.

This information is a tremendous help when you're designing equipment that's got to be reliable and you get it on Mullard Special Quality valves. You get this information because of the work they put in at their quality and test laboratories; with it you can design circuits that allow for possible valve variations and so achieve standards of equipment dependability that might otherwise not be possible.

Closely controlled characteristics are a feature of some Mullard Special Quality valces—others have a particularly long life expectation and some are designed for application where physical shock and vibration are likely to be experienced; some

even have a combination of these features."

"When it comes to selecting the right valve for the right job, you know, the people at Mullard House are very helpfulthey can give you all the facts you need and what's more they're always happy to discuss problems with you."

SPECIAL QUALITY

Government and Industrial Valve Division, Mullard Limited Mullard House, Torrington Place, London, W.C.1. Telephone: LANgham 6633.




MODEL 5G-5"

MODEL 6G-6;

10DEL 58C-8x5"

MODEL 8C-8"

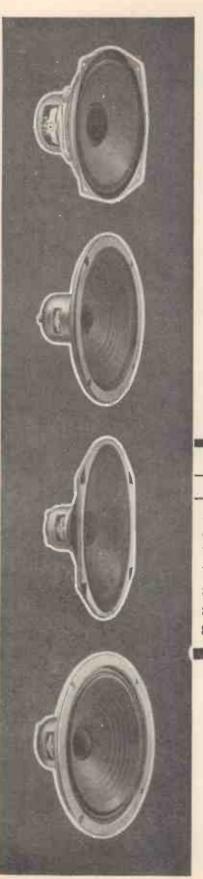

POPULAR REPLACEMENT SPEAKERS

For the guidance of the trade and public we publish below a list of the most popular ELAC replacement loudspeakers.

We have made this selection from our wide range of speakers as they cover practically all the requirements of the replacement trade.

The new prices are now operative.

POPULAR REPLACEMENT MODELS

Туре	Ref	Flux	Retail Price	Purchase Tax
5in.	5G	6500 g	20/6	6/7
6 <u>1</u> in.	6G	65 00 g	21/6	6/11
7 x 4in.	47G	6500 g	20/6	6/7
7 x 3in.	37G	6500 g	20/6	6/7
8 x 3in.	38G	6500 g	20/6	6/7
8 x 5in.	58C	8500 g	24/6	7/10
8in.	8C	7000 g	25/6	8/2


All loudspeakers have Standard 3 Ohm impedance. Higher impedances can be supplied at an extra cost of 31- plus 11- Purchase Tax.

Please write for leaflets and further details.



ELECTRO ACOUSTIC INDUSTRIES LIMITED

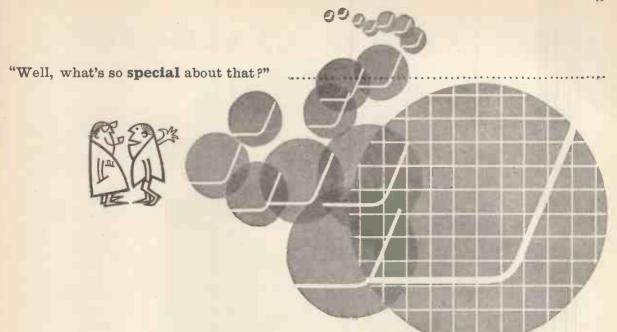Stamford Works, Broad Lane, Tottenham, N.15 Tel: TOTtenham 0505



"It's a valve characteristic that looks no different from many others—what is special is that it will be maintained for a much greater period than you would normally expect.

This feature of long consistent performance is typical of many of the Special Quality valves they make at Mullard. They achieve these standards by combining sound design with first class materials and, of course, thorough testing. In a single year, Mullard carry out something like 30 million valve hours of life testing on these types. Obviously, the many valves used are subsequently destroyed.

You can see that with this kind of background, equipment manufacturers—and users—can specify Mullard long life Special Quality types and be pretty sure that they won's be caught out by valve failures. And that's important nowadays when so much equipment serves vital functions where failure can mean real trouble.

Long life is only one feature of the Mullard Special Quality range; there are types

available with closely controlled characteristics and others are particularly rugged, some even have a combination of these features."

SPECIAL QUALIT

"Mullard, as you probably know, are most helpful when it comes to selecting the right valve for a particular job—the data they can let you have really is comprehensive and the people at Mullard House are always happy to discuss problems with you."

Government & Industrial Valve Division Mullard Limited Mullard House, Torrington Place, London, W.C.1. Tel: LANgham 6633



The R.F. SIGNAL GENERATOR



TYPE B4 MODEL A

100 kc/s to 80 M/cs in 6 bands

MODEL B

30 kc/s to 30 Mc/s in 6 bands.

Calibration accuracy of both models is ± 1%

by

Advance

to be sure!

NETT PRICE IN U.K.

£72

Full technical details in Leaflet W38 available on request.

Advance COMPONENTS LIMITED

INSTRUMENTS DIVISION

ROEBUCK ROAD . HAINAULT . ILFORD . ESSEX TELEPHONE : HAINAULT 444

OUTPUT IMPEDANCE: 75 ohm unterminated; (50 ohm model available on request) termination pad supplied to provide output impedances of 37 and 10 ohms and a dummy aerial facility.

The "Advance" B4 Signal Generator is a well tried and proven instrument which incorporates special features consisting of a monitored r.f. output

and variable modulation depth (which is also monitored); an 80 dB attenuator of special design provides exceptional accuracy of attenuation throughout the frequency range and an unusually low leakage factor is achieved by triple screening of the r.f. oscillator, and by mounting the calibrated dial

INTERNAL MODULATION: 400 c/s ±10%. Modulation depth 0 to 80% ±10%. EXTERNAL MODULATION: Model A: 10 :/s to 30 kc/s; modulation depth 0 to 80%.

Model B: 10 c/s to 10 kc/s; modulation depth 0 to 80%.

AUDIO OUTPUT: 0 to 10 volts into 600 ohms at 400 c/s.

R.F. LEAKAGE: Less than I microvolt.

on the outside of the case,

RUGGONNO

"Yes it's a straightforward enough valve characteristic, but it is special because it will be maintained in spite of the punishment-shock and vibration-it will get in the equipment where it is installed.

You see, right the way through Mullard Special Quality rugged types are designed and built to the tightest specifications-tolerances are finely controlled, assembly methods are extremely accurate and welding techniques are of the highest standards. Indeed all the staff who work on them are carefully selected and specially trained—even completely new manufacturing techniques have been devised to make sure that the end product is as rugged as possible.

When it comes to equipment that must stand up to a certain amount of shock and vibration these Mullard Special Quality valves are just the job-a worthwhile insurance against valve failure and resulting




equipment breakdown, with the high servicing costs that go with it. Ruggedness is only one feature of the Mullard Special Quality range; there are types available with extra long life expectation and others with closely controlled characteristics, some even have a combination of these features." "So far as information is concerned, Mullard can let you have all you need on any particular valve type. What's more, the people at Mullard House, who are pretty knowledgeable on these things, will always help in selecting the best valve for a particular job."

Government & Industrial Valve Division, Mullard Limited Mullard House, Torrington Place, London, W.C.1 Telephone: LANgham 6633

979

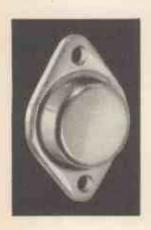A NEW TRANSISTOR DESIGNED FOR D.C. CONVERTER APPLICATIONS



Progress in one of the most promising fields of transistor application—d.c. converters—has been delayed not by a shortage of power transistors, but by transistor avalanche breakdown caused by the simultaneous heavy currents and high voltages encountered in inductive circuits.

Now, after extensive application work and customer consultation, Mullard introduce the OC28—a transistor designed and tested for use in 28-volt d.c. converter and similar applications where inductive loads are employed.

The OC28 is dynamically tested to withstand 60 volts at 0.5 amp and 60 volts at 6 amps. This testing is additional to the normal static voltage ratings of 80 volts collector to base and 60 volts collector to emitter under cut-off conditions.

The assurance of specially controlled and specified avalanche breakdown characteristics broadens scope for the design of nominal 24 volt power converters, even where the actual supply voltage rises on occasions to 30 volts or more. For operation in self-oscillating circuits a tight control on current gain is exercised.

In static and mobile equipments—in road, rail, sea and air-borne applications—the generation of high voltage for lighting, instrumentation, communication and control is now possible. The performance and small size attainable are exemplified by a pair of OC28's mounted on a folded blackened $\frac{1}{8}$ in. thick copper plate of area $3\frac{3}{4}$ in. x 14 in. Operated from a 28 volt supply in a push-pull circuit utilising two small transformers, they will deliver 100 watts at 195 volts d.c. with an overall efficiency of 86% in ambient temperatures up to 80°C.

Please write on your company letterhead for data sheets and any further information on the OC28.

OG28

Abridged Data




V _{cb} max. (I _e =0)	8oV
V _{ce} max. (cut-off)	6oV
V_{oe} max. $(I_c = 0.5A)$	6oV
V_{ce} max. $(I_c=6A)$	6oV
I. max.	6A
p _{sot} max. at 45°C mounting base	
p _{tot} max. at 45°C mounting base temperature	30W
T ₁ max. (continuous rating)	90°C
Ti max. (intermittent rating, 200 hours	
max.)	100°C
$\bar{\alpha}'$ (at $V_c = -iV$, $I_c = iA$)	20 to 55
α' (at $V_c = -iV$, $I_c = 6A$)	15 to 30

Mullard

industrial semiconductors


SEMICONDUCTOR DIVISION · MULLARD LIMITED · MULLARD HOUSE TORRINGTON PLACE · LONDON · W.C.1 · TEL: LANGHAM 6633

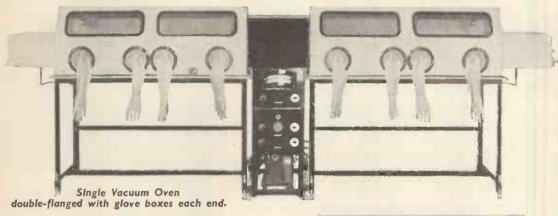DOUBLE ENDED STAINLESS STEEL VACUUM OVENS



- * Made throughout in polished stainless steel.
- * Single action door openings.
- * Rectangular with shelf spacings to suit.
- * Double ended controls.
- * Electrical interlocking of air inlet and isolation valves.
- * Outer cover hermetically sealed.
- ★ Temperature range 0°-300°C or equivalent F.
- * Temperature Control: Normal ±71°C. Special ±1C.
- ★ Internal Spacing 7In. x 8in. x 18in. (can be altered to special requirements).
- ★ Vacuum Range: To 10-4.
- * Respective Vacuum Gauges incorporated.
- * Automatic air inlet valve on Backing Pump.
- * Visual indicators and fuses on all switches.
- * Flanged for fitting into Dry Box.



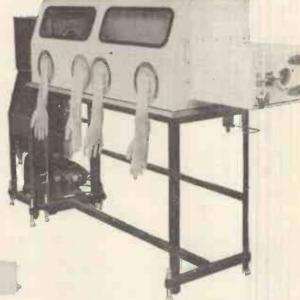

View showing automatic interlocking of unloading compartment on glove box.

We design and manufacture Ovens to Customers' special requirements. Should you have any problems in this field our Technical Department is always willing to help you solve them.

Vacuum Ovens with temperatures of up to 600°C are also manufactured by us on similar lines but with Sectional Heating and Water-Cooled Ends.



VACWELL ENGINEERING CO. LTD.

WILLOW LANE, MITCHAM, SURREY

Phone: MITcham 8211 (3 lines)

QUICKER SERVICING AND MORE PROFIT WITH NEWNES RADIO AND TELEVISION SERVICING

1954 - 1960) (Pre 2.300 Models IN SIX PACKED VOLUMES

This is Newnes Complete Library of Servicing Data. Here are all the circuits, component and layout diagrams you must have for speedy, efficient repair work, tuning and general maintenance—over 2,300 models pre-1954 right up to 1960 including those contained in the separate volumes offered below. Everything you want for profitable servicing and satisfied customers is in this comprehensive library.





TELEVISION, RADIO, RECORD REPRODUCERS. TAPE RECORDERS—

Servicing Data for Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K.-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philoo, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radlomobile, Rainbow, Raymond, Regentone, R.G.D., Robert's Radio, Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.

3,800 Circuit and Component **Diagrams**

RADIO AND

TELEVISION

SERVICING

RADIO AND

TELEVISION

SERVICING

RADIO AND

TELEVISION

SERVICING

RADIO AND

TELEVISION

SERVICING

Over 3,750 Pages

In addition—every purchaser receives 2 years' Free Radio and TV Postal Advisory Service

OR YOU CAN HAVE INSTEAD-

Data for 1958/59 and 1959/60 750 POPULAR MODELS IN TWO HANDY VOLUMES

In these two volumes you have at your fingertips all the data you need to keep the newer sets working efficiently.

The 1958-59 Volume contains 672 pages of data, circuits, components and chassis layout diagrams for over 300 popular models. TV, Radio, Tape recorders and Record Reproducers.

The 1959-60 Volume provides all the wanted servicing data for 350 popular models. 656 pages. Includes recent developments, servicing hints, etc.

We urge you to act to-day. It costs you nothing to examine these valuable servicing aids and there is no obligation to buy!


TICK YOUR CHOICE BELOW	George Newnes Ltd., 15-17 Long Acre, London, W.C.2		
RADIO & TV SERVICING 6 VOLUMES (1954/60 Models) 11/- Deposit. 20 monthly payments of 11/-, paying £11/11s. Cash in 8 days £11. 2 VOLUMES (1958/60 Models)	Please send me the book or books I have selected, without obligation to purchase. I will either return the book or books in 8 days or send the deposit 8 days after delivery, then the monthly subscriptions as set out on left, until the total subscription price of the book or books I have selected has been paid. Mr., Mrs., Miss		
15/- Deposit. 9 monthly payments of 10/-, paying £5/5/ Cash in 8 days £5.			
(1958/59 Volume) 12/6 Dep. 4 mthly, paymts. 10 -, pay- ing 52/6 in all. Cash 50 (1959/60 Volume) 12/6 Dep. 4 mthly, pymts. 10 -, pay- ing 52/6 in all. Cash 50	Occupation. Tick (I) where applicable Your Signature. HouseOWNER Householder Living with Parents Lodging Address Lodging Address		

ACT NOW

FOR 7 DAYS' FREE **EXAMINATION**

No Obligation to Purchase

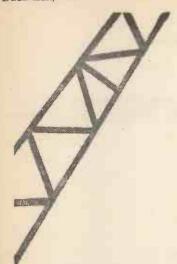Special Extra Service. -Owners are notified year by year of publication of new volumes. This service guarantees you will always be up-to-date.



Once again HALTRON is in the forefront with additional latest types making their stock still more comprehensive.

Our prices are most competitive and can be had on



Your specific enquiries for special types to CV. JAN and MIL specifications are invited.

Our organisation is Air Registration Board approved.



application.

HALL ELECTRIC LTD

HALTRON HOUSE, ANGLERS LANE, LONDON N.W.5.

Tel.: Gulliver 8531 (10 lines) Telex 2-2573 Cables: "Hallectric London"



well connected with ...

Superspeed

Superspeed Cored Solder, incorporating Enthoven's unique 6-channel stellate core, is unchallenged as the most efficient cored solder wire for general assembly work on radio, television, electronic and telecommunication equipment. It speeds production, reduces costs and makes a vital contribution to the dependability of your products.

Not only Superspeed. The knowledge that you rely on Enthoven for all your solder requirements cannot fail to enhance your prestige and increase confidence in your products. It is a name that represents 150 years experience in non-ferrous metals and an incomparable record in research and development.

SUPERSPEED CORED SOLDER for normal electrical assembly work

SUPERSPEED 'XX' CORED SOLDER
specially developed to solder tarnished, plated, and/or
oxidised surfaces easily

ENTHOVEN


SOLDER PRODUCTS

ENTHOVEN SOLDERS LIMITED

Sales Office & Works: Upper Ordnance Wharf, Rotherhithe Street, London, S.E.16. Telephone: BERmondsey 2014

Head Office: Dominion Buildings, South Place, London, E.C.2.

Telephone: MONarch 0391

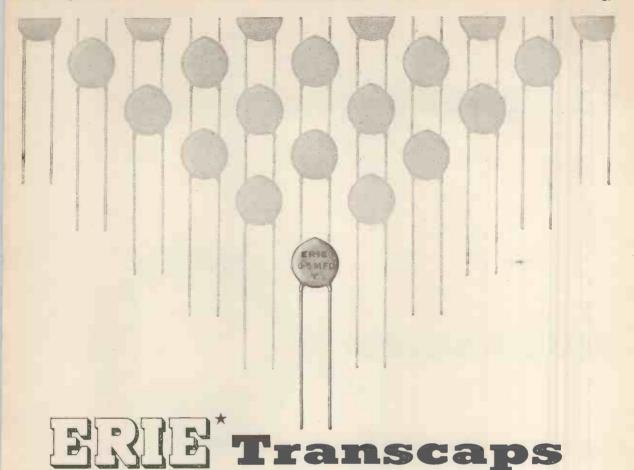

for all Transistor Circuits

SPECIFICATION

Diameter: 0.594 inches maximum

Thickness: 0.156 inches maximum

Capacitance: 0.5 mfd

Tolerance: -20% +50%

Working voltage: 3 volts d.c.

Power factor: Not greater than 5%, when measured at 1 kc/s, and less than 0.5 volts Leakage resistance: Not less than 100,000 ohms, when measured at 3 volts

S 0 E

In line with the Erie policy of anticipating the component requirements of the future, the Erie Transcap capacitor is now added to our ever-increasing range of components for use with transistors.

Designed specifically as a small, reliable, high capacitance, low voltage, coupling, and by-pass capacitor, the Erie developed Transcap is manufactured entirely at our Great Yarmouth factory.


Style T, shown here in its actual physical size, is but a forerunner of the wide range, in differing values and voltages, which will ultimately emerge.


HEDDON STREET, LONDON, W.I Telephone: REGent 6432

FACTORIES

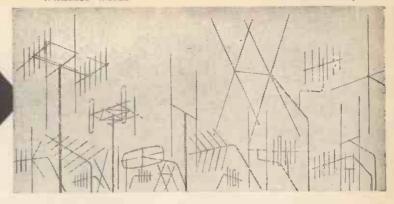Great Yarmouth and Tunbridge Wells, England: Trenton, Ont., Canada: Erie, Pa., Holly Springs, Miss., and Hawthorne, Cal., U.S.A.





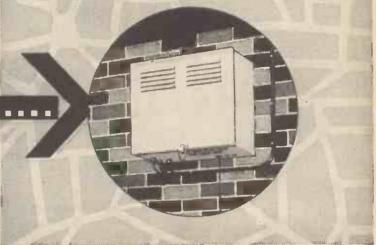

because of THIS....

- GOOD STRONG SIGNALS
- CLEAN PICTURES
- ELIMINATION OF AERIALS

An occasional intermediate amplifier and neat house-to-house wiring are the only visible evidence that, in this area, for the first time T.V. is being enjoyed at its best, with clean pictures, no interference and no aerial replacement and repair costs.

Built with the future in mind, the installations of to-day are capable of handling a third or fourth channel—or more, colour, "coin-in-the-slot" T.V. or any foreseeable development in television and sound techniques.

E MI COMMUNITY TELEVISION SYSTEM

Full technical particulars together with any planning assistance that may be required can be obtained from THE GRAMOPHONE COMPANY LIMITED.

Recording and Relay Equipment Division,

HAYES, MIDDLESEX, ENGLAND. - Telephone: Southall 2468 (One of the E.M.I. Group of Companies)

GC/CTV/1

Easy - to - build kit - sets of -----------



highest quality at lower cost

++++++

"GLOUCESTER" STEREO CABINET
KIT. Specially designed to meet the varying needs
of different homes. Mk. I houses Record Player,
F.M. Tuner, Stereo Ampliffer, records, etc. Mk. II
will house a Tape Deck in addition. 46½in. long,
30in. high, 21in. deep. "In the white " for finish
to personal taste. to personal t Mk. I £15.18.6

Mk II £17.8.6

"COTSWOLD" HI-FI SPEAKER SYSTEM "COTSWOLD" HI-FI SPEAKER SYSTEM KIT. Acoustically designed enclosure "in the white "26in. x 23in. x 15½in. housing a 12in. bass speaker with 2in. speech coil, elliptical middle speaker together with pressure unit to cover the full frequency range of 30-20,000 c/s. Complete with speakers, cross-over unit, lever control, etc. €19.18.6

"CHEPSTOW" EQUIPMENT CABINET KIT. Occupies minimum floor space. Will house Record Player, F.M. Tuner, Stereo Amplifier and additional power amplifiers where needed. Dim. 35 x 18 x 33in. high.

HI-FI SINGLE CHANNEL AMPLIFIER KIT Model MA-12. 12 W. output, wide freq. range, Low discortion. £.9.19.6

TEREO CONTROL UNIT KIT Model USC-1. Push-button selection, accurately matched ganged controls to \pm 1 dB. Accepts inputs from most tape heads and any stereo or mono pick-up.



HI-FI STEREO AMPLIFIER KIT. Model S-88.
16 w. output, 10 mV. basic sensitivity (2 mV. available, 20/- extra). Ganged controls. Stereo/ Monaural gram., radio and tape recorder inputs. Push-button selection. Two-tone grey metal cabinet. 425.5.6

3 watts per channel, 0.3% distortion at 2.5 w/chnl., 20dB N.F.B. Inputs for Radio (or Tape) and Gram., Stereo or Monaural, ganged controls. Sensitivity 100 mV.

HI-FI SPEAKER SYSTEM KIT. Model SSU-I.
Ducted-port bass reflex cabinet "in the white."
Twin speakers. With legs £11/12/6. £10.5.6

STEREO-HEAD BOOSTER KIT. Model USP-I. Hi-Fi Stereo pre-amplifier for low output Hi-Fi P.U.'s. Input 2 mV to 20 mV. Output adjustable from 20 mV. to 2 v 40–20,000 c/s. Also suitable as low-noise R.C.-coupled high-gain 25.19.6

TRANSCRIPTION RECORD PLAYER, Mod. RP-IU. 4-speed A.C. motor. Ronette Stereo/Mono pick-up. Complete on plinth. £12.10.0

TAPE AMPLIFIER UNIT KITS. Models TA-IM and TA-IS. This Combined Tape Record/Replay Amplifier is available in both monophonic and Stereophonic models. Model. TA-IM can be modified to the stereo version with modification kit TA-IC. TA-IM £16.14.0; TA-IS, £22.4.0; TA-IC £6.

Sin. OSCILLOSCOPE KIT. Model O-12U. Has wide-band amplifiers, essential for TV servicing, F.M. alignment etc. Vertical frequency response 3 c/s to over 5 Mc/s, without extra switching T/B covers 10 c/s to 500 kc/s in 5 ranges £34.15.0

ELECTRONIC SWITCH KIT. Model S-3U. (Oscilloscope Trace Doubler). Enables a single beam oscilloscope to give simultaneous traces of two separate and independent signals. Switching rates approx. 150, 500, 1,500, 5,000 and 15,000 c/s. Sig. freq. response 10-100 kc/s. ± 1 dB. Separate gain controls and sync. output. Sig. input range 0.1-1.8 v. r.m.s. £9.18.6

CAPACITANCE METER KIT. Model CM-1U Direct-reading 4½in. scale. Full-scale ranges 0-100μμF, 0-1,000μμF, 0-0.01μF and 0-0.1μF £14.10.0

POWER SUPPLY UNIT KIT. Model MPG-I Input 100/120 v. 200/250 v., 40-60 c/s. Output 6.3 V., 2.5A A.C.; 200, 250, 270 V., 120 mA. max. D.C. 44.9.0

MULTIMETER KIT. Model MM-IU. Ranges 0-1.5 V. to 1,500 V. A.C. and D.C.; 150μ A to 15A d.c.; 0.2Ω to 20 M Ω . 4½in. 50μ A meter.

DECADE CAPACITOR KIT. Model DC-1 Capacity values 100 μμ το 0.111 μ in 100 μμ ξ5.18.6

VALVE VOLTMETER KIT. Model V-7A. 7 voltage ranges d.c. volts to 1,500 a.c. to 1500 r.m.s. and 4,000 peak to peak. Resistance 0.1 Ω to 1,000 M Ω with internal battery. D.C. input impedance 11 m Ω . dB measurement has centrezero scale. Complete with test prods, lead and arrandardising battery. standardising battery. €13.0.0

R.F. PROBE KIT. Model 309-CU. Extends the frequency range of our V-7A to 100 mc/s. and enables useful voltage indication to be obtained up to 300 Mc/s.

R.F. SIGNAL GENERATOR KIT. Model RF-IU. Provides extended frequency coverage on six bands from 100 kc/s.-100 Mc/s. on fundamentals and up to 200 Mc/s on calibrated harmonics £11,11.0

GRID-DIP METER KIT. Model GD-IU. Functions as oscillator or absorption wave merer. Model GD-IU. With plug-in coils or continuous frequency coverage from 2 Mc/s. to 250 Mc/s. £9.19.6 Two Additional Plug-in Coils Model 34-IU extend coverage down to 350 kc/s. With dial correlation 15/-

TRANSISTORISED VERSION. Model XGD-I. Similar to GD-IU. Fully transistorised with a frequency range of 1.75 to 45 Mc/s, £9.18.6

AUDIO WATTMETER KIT. Model AW-IU.
Up to 25 w. continuous. 50 w. intermittent
£13,18.6

6 W Amplifier (S-33) £11 8 0 Twin Speaker Systems (SSU-I) £20 II 0

Deferred Terms

Available on all orders above £10.

Pedestal Speaker legs £2/14/- optional extra.

23 in. SERVICE 'SCOPE KIT. Model OS-I. Light, compact portable for service engineers. Dim. 5 x 8 x 14½ in. long. Wt. 10½lb. £18,19.6

AUDIO VALVE MILLIVOLTMETER KIT MODEL AV-3U. I mv. to 300 v. A.C. 10 c/s. to 400 kc/s.

AUDIO SIGNAL GENERATOR KIT. Model AG-9U. 10 c/s. to 100 kc/s., switch selected. Distortion less than 0.1%. 10 v. sine wave output metered in volts and dB's.

RESISTANCE CAPACITANCE BRIDGE KIT. Model C-3U. Measures capacity 10pf to 1,000 μ F., resistance 100Ω to 5 $M\Omega$ and power factor. 5-450 v. test voltages. With safety switch,

DUAL-WAVE TRANSISTOR RADIO KIT.
Model UJR-I. This sensitive headphone set is a fine introduction to electronics for any youngster.

4-WAVE TRANSISTORISED PORTABLE KIT. Model RSW-I. 7 Transistors and three diodes. For Short and Medium wave-bands (200–550, 90–200, 18–50, and 11–18 m.). In solid leather case fitted with retractable whip aerial.

TAPE DECKS are now available as " packaged deals "with other equipment.

Details on request.



TRANSISTOR PORTABLE RADIO KIT. Model UXR-I. Pre-aligned I.F. transformers, printed circuit and a 7 x 4in. high-flux speaker. Reai hide case

HI-FI F.M. TUNER. Tuning range 88-108 Mc/s. For your convenience this is available in two units sold separately as follows: Tuner Unit (FMT-4U) with 10.7 Mc/s. I.F. output £3/2/- inc. P.T I.F. Amplifier (FMA-4U). Complete with case and valves £10/10/6. Total £13.12.6

AMATEUR TRANSMITTER KIT.
DX-100U. Covers all amateur bands
160-10 metres. Self contained including bands from uding Power Modulator and V.F.O.

"HAM" TRANSMITTER KIT. Model DX-46 U. From 80-10 m Power input 75 w. C.W., 60 w. peak controlled carrier phone. Output 40 w. to aerial. Provision for V.F.O.

VARIABLE FREQUENCY OSCILLATOR. KIT. Model VF-IU. From 160-10 m. Ideal for our DX-40U and similar transmitters. Price less valves £8/19/6.

BALUN COIL UNIT KIT. Model B-IU. Will match unbalanced co-axial lines to balanced lines of either 75 or 3000 impedance £4.4.6

Prices include free delivery in the U.K.


DEPT. W.W.12 GLOUCESTER, ENGLAND

A member of the Daystrom Group, Manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KIT-SETS

1	Please send me FREE CATALOGUE (Tes/No)
ı	Full details of model(s)
İ	NAME(Block Capitals)
İ	ADDRESS
i	W.W.I2

Microwave equipment

and for the band

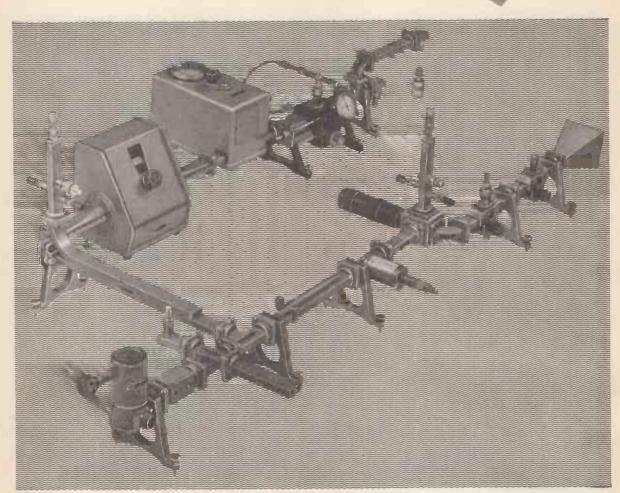

Measuring bench for 8.2-12.4 kMc s

PHILIPS electronic measuring

Sold and serviced by Philips Organizations all over the world Sole Distributors in the U.K.: Research & Control Instruments Ltd., 207 King's Cross Road, London W.C. I Overseas enquiries please, to the manufacturers,

N.V. Philips, EMA-Department, Eindhoven, the Netherlands.

ТҮРЕ	DESCRIPTION	MAX. VSWR.	
PP 4020 X	Straight Waveguide Section	_	Length 10, 20, and 40 cm
PP 4025 X	E-plane Bend	1.07	Radius of curvature 29 mm
PP 4030 X	H-plane Bend	1.07	Radius of curvature 29 mm
PP 4035 X	Twist	1,10	Length 187 mm
PP 4040 X	Shunt Tee		Length 80 mm
PP 4045 X	Series Tee	-	Length 80 mm
PP 4050 X	Hybrid Tee	_	Decoupling > 40dB
PP 4070 X	Waveguide/Coaxial Adapter	1.50	50 Ω N-connector
PP 4080 X	Horn	1.25	Directivity: E-plane 20°, H-plane 25°
PP 4090 X	Multi-hole Directional Coupler	1.05	Directivity: >40dB, coupling factor I0dB or 20dB (± 0.2dB)
PP 4095 X	Cross-guide Directional Coupler	_	Directivity: 20dB, coupling factor 26dB (± 0.5dB)
PP 4110 X	Fixed Attenuator	1.10	Attenuation 6, 10 or 20dB (± 0.2dB), max. peak power 1 kW
PP 4130 X	Variable Flap Attenuator	1.15	Max. attenuation > 20dB
PP 4150 X	Variable Rotary Attenuator	1.15	Max. mean power I W, max. attenuation 50dB, accuracy ± 20/0
PP 4170 X	Low-power Matched Load	1.05	Max. mean power 2 W
PP 4200 X	Klystron Mount		When using klystron 2K25 the output power is > 20 mW
PP 4220 X	Adjustable X-tal Mount	1.10	Sensitivity: I mV D.C. for 0.1 μW, S0Ω N-connector
PP 4225 X	Broadband X-tal Mount	1.50	Sensitivity: 1 mV D.C. for 10 μW, 50Ω BNC-connector
PP 4245 X	Tunable Thermistor Mount	1.10	Freq. range 8.2-II kMc/s, 50 Ω BNC-connector
PP 4260 X	Calibrated Short Circuit	from 20 to >1.02	Accuracy of the displacement 0.02 mm Insertion loss for a VSWR of 20 is > 2dB
PP 4280 X	Sliding Screw Tuner	10m 20 to >1.02	
PP 4290 X	Direct Reading Wavemeter		Freq. range 8.5-9.8 kMc/s, absolute accuracy ± 2 Mc/s, loaded Q 10,000
PP 4300 X	Broadband Wavemeter	01.1	Relative accuracy 3.10-4, loaded Q > 3,000
PP 4360 X		1,10	Freq. range 8.65-8.95 kMc/s, loaded Q > 3,000,
PP 4360 A	Measuring Cavity	_	magnetic field for electron resonance 3,300 gauss
PP 4380 X	Standing Wave Detector	1.05	Accuracy of the probe displacement 0.01 mm.
PP 4380 A	Standing Wave Detector	1.03	50 Ω BNC-connector
PP 4385 X	High Procision Counting Ways		Measurable VSWR between 1.005-2.000, accuracy
PP 4303 A	High Precision Standing Wave		probe displacement 2 μ , probe penetration 0-3 mm
PP 4421 X	Ferrite Isolator	1.15	Freq. range 8.5-9.6 kMc/s, forward att. < 0.8dB,
LC 4471 V	Terrice isolator	1,113	reverse att. > 13dB, max. peak power 50 kW
PP 4422 X	Ferrite Isolator	1,20	Freq. range 8.5-9.6 kMc/s, forward att. < 0.5dB,
11 4477 V	Terrice isolator	1.20	reverse att. > 20dB, max. mean power I W
PP 4500 X	3 cm Noise Generator	>1.20	Noise factor 18.7dB (K50A), attenuation 0-13dB
11 1300 X	J cili 110isc Generator	, ,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,	110.00 100.00

Additional Instruments: D.C. Microvoltmeter, type GM 6020 - Klystron Supply, type GM 4561 - Bolometer Bridge, type GM 4460

Q TYPE	DESCRIPTION	MAX. VSWR.	
PP 4020 Q	Straight Waveguide Section	_	Length 5, 10 or 20 cm
PP 4025 Q	E-plane Bend	1.07	Radius of curvature 35 mm
PP 4030 Q	H-plane Bend	1.07	Radius of curvature 37 mm
PP 4035 Q	Twist	1.07	Length 50 mm
PP 4050 Q	Hybrid Tee	_	Decoupling >35dB
PP 4080 Q	Horn	1.15	Directivity: E-plane 15°, H-plane 16°
PP 4130 Q	Variable Flap Attenuator	1.15	Max. attenuation > 20dB
			max, mean power 200 mW
PP 4150 Q	Variable Rotary Attenuator	1.15	Max. attenuation 50dB, accuracy ± 30/0
PP 4170 Q	Low-power Matched Load	1:05	Max, mean power I W
PP 4200 Q	Klystron Mount		When using klystron 55,335 the output power is 100 mW
PP 4222 O	Adjustable X-tal Mount	1.25	50 Ω BNC-connector
PP 4260 O	Calibrated Short Circuit	50	Accuracy of the displacement 0.02 mm
PP 4270 Q		from 10 to 1,03	Insertion loss for a VSWR of 10 is > 2dB
PP 4300 Q	Broadband Wavemeter	1.20	Relative accuracy 5.10-4 loaded Q > 3000
PP 4382 Q	Standing Wave Detector	1.03	Accuracy of the displacement 0.01 mm
	0		max. probe penetration I mm, 50Ω BNC-connector
PP 4420 Q	Ferrite Isolator	1.15	Freq. range 33-36 kMc/s, forward att. < IdB
			reverse att. 13-26dB, max. mean power 200 mW

Additional Instruments: Klystron Supply, type 4485 - D.C. Microvoltmeter, type GM 6020

instruments: quality tools for industry and research





THREE YEARS AGO we offered the first SERVISCOPE* to Industry with notable success. Last year we introduced a double beam version and again acceptance was immediate. Now we extend the range still further with the new S.42, a high performance version of the original Serviscope with many outstanding features.

- 4" spiral P.D.A. C.R. tube operating at 3.7 Kv.
- Increase gain—maximum sensitivity 10 mV.
- Unique extendible light hood.
- Pulse bright-up for single stroke working.
- H.F. synchronisation compatible with Y amplifier performance.

Accurate calibrated input attenuator, Wide range calibrated time base (down to 5 sec/cm. if necessary). X expansion control to 10 dia. D.C. coupled flyback banking. Versatile triggering circuit unique to 'Serviscopes'. Illuminated graticule. Weight:

18 lbs.

Price: 592


Basically the same rugged, lightweight, versatile instrument as its well-tried predecessors, the S.42 has the ability to meet more exacting demands with its high writing speed and additional high gain facility. Evolved originally for computer development and servicing, the S.42 has special applications wherever pulses have to be measured at low repetition rates, for example, a single shot 1µ sec. pulse can be seen and photographed. In addition, it has general applications throughout the electronics industry.

TELEQUIPMENT

* 'Serviscope' is the registered trade mark of

TELEQUIPMENT LIMITED 313 Chase Road, Southgate, London, N.14. Telephone: Fox Lane 1166

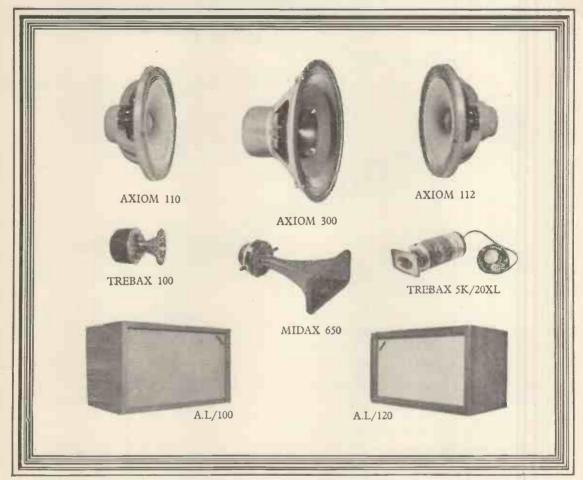From the Greatest Range with the Greatest Name...



... Goodmans High Fidelity Loudspeakers

 Established over 30 years ago, Goodmans Industries are now the largest manufacturers of High Fidelity Loudspeakers in Europe.
 A Tradition of Excellence has been maintained throughout this period, achieving World-wide recognition.

Please send copy of High Fidelity Manu	ual.
Name	••••
Address	••••
,	••••
G43WW	****




GOODMANS INDUSTRIES LIMITED Axiom Works, Wembley, Middlesex

Tel: WEMbley 1200 (8 lines) Grams: Goodaxiom, Wembley, England In every sense the greatest range—in every country the greatest name



for true-depth reproduction

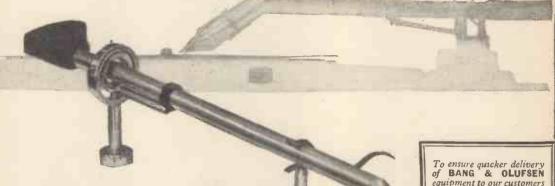

The Bang and Olufsen STEREODYNE Pick-up is a unique 4 pole 4 coil moving iron system. FUNDAMENTALLY correct in principle and geometry for stereo disc recordings and provides equal compliance in all directions with high channel separation through the entire frequency range.

* PRECISION ENGINEERED LIGHT ALLOY ARM

★ LOW FRICTION—LOW MASS

* ADJUSTABLE TRACKING PRESSURE 1-4 GRAMS

★ PLUG-IN CARTRIDGE—EASY CHANGE, DIAMOND STYLUS

* HIGH OUTPUT-LOW IMPEDANCE, HUM BALANCED SYSTEM

Stereodyna arm complete with cartridge

£17.17.0 inc. P.T.

Cartridge complete with stylus

£7. 7.0 inc. P.T.

Replacement Diamond stylus

£2.14.0 inc. P.T.

We maintain that the BANG & OLUFSEN pick-up is the best available. Why not listen and judge for yourself.

ASK YOUR DEALER FOR A DEMONSTRATION or write direct to:

equipment to our customers in the trade or otherwise, MAIN DISTRIBUTORS have been established at:

LONDON & S.E.

Webbs Radio 14 Soho Street London, W.I.

WEST

Bristol and West Recording Services Limited Park Row, Bristol, I

SOUTH

University Cameras 12 Bargate Street Southampton.

MIDLANDS

Leicester Co-operative Soc. High Street Leicester

NORTH

High Fidelity Development Ltd. 8 Deansgate Manchester 3

SCOTLAND

James Kerr & Co. Ltd. 435 Sauchiehall Street Glasgow, C.2.

Aveley Electric Limited

SOUTH OCKENDON, ESSEX

Telephone: South Ockendon 3444

Telex: 24120 Avel Ockendon






wherever

rugged contactless control equipment is vital you'll need




STATIC SWITCHING SYSTEMS

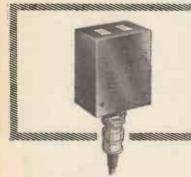

The Proximity Switch will provide a signal to operate a Basic Logic Unit. whenever a mass of ferrous material comes within 5mm of the operating face. Having no moving parts, it is an encapsulated wound commonent suitable for use in conditions of vibration, shock, dust, damp-in fact, in any environment where the epoxy potting compound and the cable gland will not be damaged.



The Contactless Changeover Switch, a form of differential transformer, will provide signals to operate Basic Logic Units, changing over when the armature is rocked by about 1.5 degrees i.e. 1mm movement at one end. Apart from the solid steel armature which pivots on a stainless steel pin in a bronze bush, there are no moving parts; the body of the device being similar to that of the proximity switch.

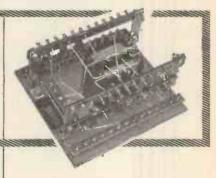

The Basic Logic Unit provides the normal logic functions i.e. OR, AND, AND/NOT, LATCH etc. The standard inputs signal is 1.5 Volts at 68 ohm, although pre-amplifiers can be provided if required. An output of 900mW into 47 ohms is normal for the basic logic unit. sufficient to drive any Sanders transductor from 1 Watt output to 10kW output.

The latching units have a "MEMORY" facility enabling them to remain latched during total power failure.

This Static Switching System provides control equipment without the use of electrical contacts which may corrode, weld or wear out and with the minimum moving parts required to provide the initial information to the system. The only electrical components used in the entire system are encapsulated transductors, wirewound resistors, transformers and silicon rectifiers - components used well within the manufacturers' limits to ensure reliability.

The information fed to the basic logic units can be derived from photo-electric cells, tacho-generators and any device that will provide a few milliamps into a 100 ohm


winding.

This is one of a series of new instruments and components by



W. H. SANDERS (ELECTRONICS) LTD

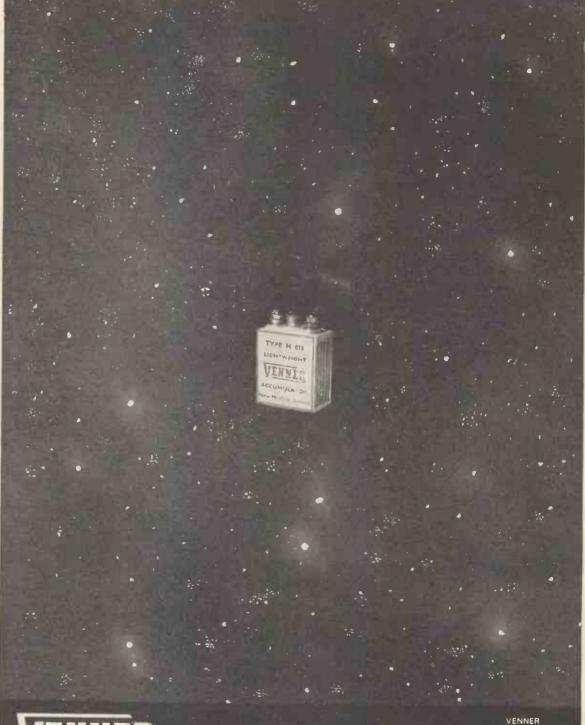GUNNELS WOOD ROAD . STEVENAGE . HERTS Telex 82159 Sanders Stev. Telephone Stevenage 981.




Accumulators



SILVER-ZINC ACCUMULATORS

VENNER ACCUMULATORS LIMITED Kingston By-Pass, New Malden, Surrey MALden 2442 A member of the Venner Group of Companies

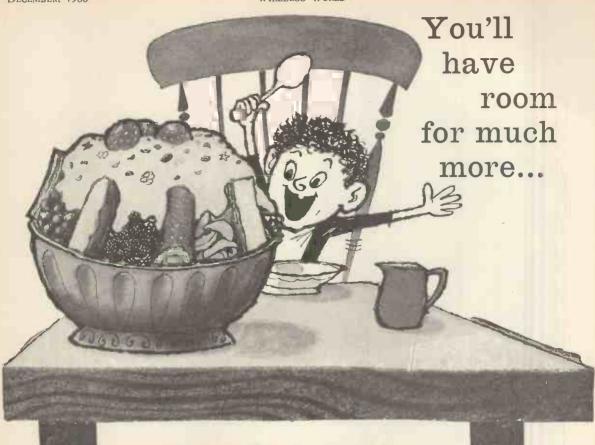The lightest and smallest rechargeable accumulator in the world



... with the A.T.E. Series TAA Telegraph Terminal Equipment

This unit is specially built to be as compact as possible, giving you room for much more equipment without overcrowding. The unit, comprising an electronic distributor and an operating head, is equipped with two tape readers arranged to operate alternately for continuous transmission of messages. The space taken is kept to a minimum because the operating head measures only 6½" in width.

Equipments are available to operate with conventional point to point, synchronous and semi or fully automatic switching systems.

Special features are:

- a. Automatic transmission of:-
 - 1. Station call sign and serial number before any message.
 2. Start of message and end of message preambles when operating in conjunction with automatic switching system.
 3. Error signal and end of message
 - preamble in the event of a mistake in the tape message being dis-covered by an operator. 4. A 100 character test message.
 - A routine message of up to 48
- 5. A routine message of up to 48 characters.
 6. Station call sign and serial number at pre-determined intervals while no traffic is being handled.
- b. Speeds 45.5, 50, 75 bauds selected by means of a switch, together with a

spare position for an optional speed.

spare position for an optional speed.
c. 7, 7½ or 8 unit code.
d. Stopping a transmission and restarting at the point when a transmission was interrupted, or at any point without starting a new preamble. In the case of a tape, this facility may be used to repeat, or omit a particular portion of the message.

Transmitting the test message. e. Transmitting the test message direct from the distributor.

Operating Head


Dimensions 6½" x 22" x 9" (16.5 cm x 56 cm x 23 cm). Weight 31 lbs, (19.1 Kg).

Electronic Distributor

Dimensions 19" x 84" x 3½" (48 cm x 21 cm x 9 cm). Weight 23 lbs. (10.7 Kg).

AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

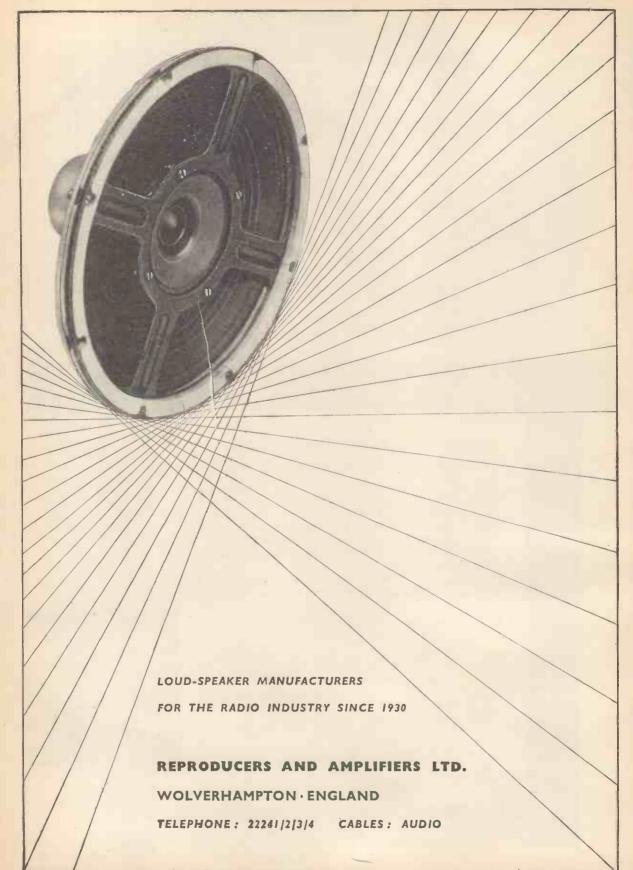STROWGER HOUSE, ARUNDEL STREET, LONDON, W.C.2. Telephone: TEMple Bar 9262, Strowger Works, Liverpool 7.



Hermetic Sealing


STEATITE & PORCELAIN NICKEL METALLISING

Quality Approved (Joint Service R.C.S.C.)

WILL MEET THE MOST EXACTING REQUIREMENTS



Perfect Terminations

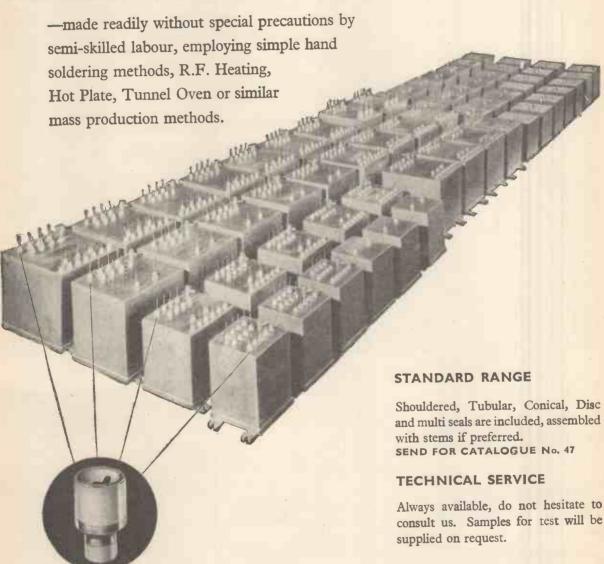

STEATITE & PORCELAIN PRODUCTS LTD.

STOURPORT ON SEVERN, WORCS.

Telephone: Stourport 2271

Telegrams: Steatain, Stourport

Radiotelephones by ATE—a vital service for isolated communities

In situations like this...





TYPE 800

ATE Radiotelephones are used by industrial, mining, agricultural, civil and military enterprises—and by research and survey teams—in 60 countries.

In situations like this, the new A.T.E. Type 800 equipment, which has been extensively tested under arduous tropical conditions, can supply the vital link. Latest in the A.T.E. single-channel, V.H.F., Rural Radiotelephone range, the versatile Type 800 can be linked direct to the nearest telephone exchange to provide duplex speech with full signalling and dialling facilities. The most advanced of its kind, Type 800 has already proved itself in service to be absolutely reliable and efficient.

Extended frequency coverage over V.H.F. and U.H.F. bands

New compact cabinet-type construction with slide-in chassis for easy access and maintenance

Plug-in test meter facilities

High or low power versions to suit propagation conditions

Will work into any type of telephone exchange with improved 'outband' tone signalling facilities.

Modern design conforming to G.P.O. and D.O.T. specifications

If you would like to know more about this new mains-operated equipment, or its battery-operated counterpart, the "Country Set", write for full details to your local representative . . . or send for bulletin REB.4101/1 to . . .



AUTOMATIC TELEPHONE & ELECTRIC CO. LTD

STROWGER HOUSE, 8 ARUNDEL STREET, LONDON, W.C.2. Telephone: TEMple Bar 9262

THEY LOOK SO GOOD The moment you see the styling of a Truvox Tape Recorder,

you know it is the machine for you. Foolproof and simple in operation with professional facilities, a Truvox Recorder will be the centre of your home enjoyment of speech and music.

See them at your dealers.

THEY SOUND SO GOOD

You'll enjoy 'listening' more than ever before. All the technical know-how of a decade of specialisation, to give perfect sound enjoyment, is embodied in the Truvox R6 and R7... the original sound truly recorded and truly re-played through large



THEY ARE SO GOOD That you'll never be satisfied with any



other Recorder . . . once you've seen and heard them, you'll decide for yourself . . .

THEY MUST BE

loudspeakers. Hear them at your dealers.

TRUVOX

R.7

H.P. Facilities available.

SERVICE IN YOUR OWN HOME.

R6


7in. spools. 10 watts output. Records/Replays both directions. Two speakers (tweeter and woofer).

Response 30-17,000 c/s.

Retail Price 75 gns.

7in. spools. 4 watts output. 2 speeds. 8in. × 6in. speaker. Response 30-15,000 c/s.

Retail Price 55 gns.

 







15

that's the stuff!

MS4? Extraordinary sort of name.

Still it's extraordinary sort of stuff-a nonmelting, highly water-repellent silicone grease with excellent dielectric properties and a working temperature range of -50° to +200°C. Extraordinarily good for lubricating, protecting and sealing disconnectable plugs and sockets, cable harnesses, ignition circuits, for maintaining high surface resistivity in wet conditions, for lubricating turret tuners and preventing 'leakage' around the anode caps of CRT's -in fact for so many uses that we cannot possibly list them all here. Why not write in for our special brochure on MS4?

MS4 Silicone Insulating Compound For full information, write or 'phone the nearest branch office of Midland Silicones or any of the following distributors: BRITISH CENTRAL ELECTRICAL CO LTD 6 & 8 Rosebery Avenue, London, E.C.1 Tel: Terminus 3666 Also at Briticent House, Addlewell Lane, Yeovil CASELCO LTD Midland Works, Canal Road, Leeds 12. Tel: 630551
DIRECT TV REPLACEMENTS LTD 138 Lewisham Way, New Cross, London, S.E.14 Tel: Tideway 6666 ELECTRICAL TRADES SUPPLY LTD Loveday St., Birmingham 4. Tel: Aston Cross 5671 T J GRAINGER & CO LTD 9-13 St. James Street, Newcastle-upon-Tyne 1 Tel: Newcastle 24552 HOLIDAY & HEMMERDINGER LTD 71 Ardwick Green North, Manchester 12 Tel: Ardwick 6366

R D TAYLOR & CO LTD 9 Lynedoch Street,

Glasgow C8. Tel: Douglas 1202-3-4

(MS) MIDLAND SILICONES LTD

(Associated with Albright & Wilson Ltd and Dow Corning Corporation)

first in British Silicones

68 KNIGHTSBRIDGE . LONDON . SW1 . TELEPHONE: KNIGHTSBRIDGE 7801 Area Sales Offices: Birmingham, Glasgow, Leeds, London, Manchester. Agents in many countries.



Freedom from breakdown is an outstanding feature of Leevers-Rich magnetic recorders, a feature which has been achieved by sound design, fine workmanship and, not least, by accessible layout.

Accessibility of Tape Drive Mechanism

Tape decks on both portable and console models can be hinged up (even while running) to expose underside of mechanism and all pre-set adjustments to thorough inspection.

Accessibility of Mechanical Units

Capstan drive, spool motors, and head assembly are each built as integral units and are accessible for removal without disturbing adjacent parts of the mechanism or wiring.


Accessibility of Electronic Units

Standard single channel amplifiers hinge open for inspection and maintenance. Multi-channel amplifiers consist of easily removable plug-in units in a modular system which combines flexibility, compactness and accessibility.



Engineers responsible for the largest recording installations know that Leevers-Rich accessibility permits thorough preventative maintenance, reduces "down time," and cuts operating costs. That is why more and more Leevers-Rich recorders are going into service with organisations where reliability is vital.

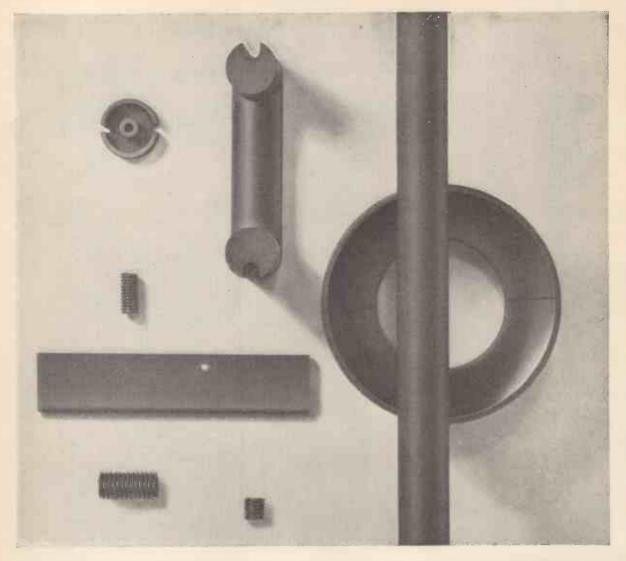LEEVERS-RICH EQUIPMENT LTD. 78, Hampstead Rd., London, N.W.1. Tel. EUSton 1481



For superior and reliable ferrite cores use FERRAMIC by

Plessey

Plessey Ferramic components are already accepted for their reliability and are produced by advanced techniques with rigid quality control. As leading producers of ferrite components Plessey offer wide ranges of pot cores and slugs, aerial rods and TV cores—together with any help you may need on applications. A series of data sheets covering the range of products is freely available on request.

* FERRAMIC is a registered trade mark

Components Group

CHEMICAL AND METALLURGICAL DIVISION

THE PLESSEY COMPANY LIMITED
Wood Burcote Way · Towcester · Northants

Telephone: Towcester 312/6

OVERSEAS SALES ORGANISATION: PLESSEY INTERNATIONAL LIMITED - ILFORD - ESSEX - TELEPHONE: ILFORD 3040

Transparent

covers for above now

available.

Men in the Know

HAVE THE RIGHT CONTACTS

MAJOR TYPE 'BPO 3000'

The best known and most useful relay available. Spring sets allow from one make or break to 12 change-

overs. For minute or heavy switching. Sensitivity down to 20 milliwatts. Adjustable for critical timing, fast or slow operation. Standard or Tropical finish. Special adaptations can be supplied.



Plug-in facilities in addition to all the versatility and well-established, reliable features of the world's best known

relays.

* Positive contact between male and temale gins.

★ Contacts: up to 18 light duty or 12 heavy duty.

* Complete (ransistorized utilits.

A.C. or D.C. operation.


* Transparent or metal cover.

★ Clip retains relay positively in any position.

SOCKETS AND FITTINGS ARE AVAILABLE FROM STOCK for immediate assembly of units.



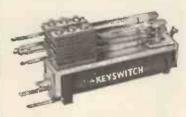PLUG-IN — TRANSISTORIZED UNIT Operation AC or DC Swit hing or Signal Current AC or DC 5 to 500 micro-amps. Transfer switching current 10 amps. or 500 v.



MINOR TYPE '600' (Fitted with double pole changeover for 250 volts, 2 amps.)

Ideal for simple switching operations where lightness, compactness and economy are prime considerations. When fitted with contacts similar to those of the "B.P.O. 3000" type it is faster in operation and release.

This relay incorporates 15 amp. Micro Switch; 5 amp. Mercury Switch and standard 0.3 to 8 amp. contacts.

明明



KEYSWITCH

SALES MANAGER

2 IRONGATE WHARF ROAD, PRAED ST., LONDON, W.2

Telephone: PADdington 2231

Extremely advantageous quotations can be offered for quantity orders.

Contractors to Home and Overseas Governments and H.M. Crown Agents.

RELAYS FOR ALL PURPOSES can be supplied to customers' requirements for:—

AUTOMATION COMPUTERS

BATCH COUNTING and PHOTO-ELECTRICS

TELEPHONY and INTERCOM
SYSTEMS

AUTO-TIMING and AUTOMATIC

MOTOR and MACHINERY CONTROL
CURRENT and VOLTAGE
REGULATION, etc.

OXLEY

DEVELOPMENTS CO. LTD.

ULVERSTON NORTH LANCS 76/: Ulverston 3306

Delay Lines

Plugs & Sockets

Miniature

Concentric Piston Condensers

> Air Dielectric Trimmers

Tempatrimmer Adjustable for Temperature Coefficients

P.T.F.E. Stand-Off and Lead-Through Insulators

Ceramic Stand-Off Insulators

> Multi-Tag Insulators

OXLEY

DEVELOPMENTS (DEAL) LTD. 72-74, DOVER ROAD, WALMER, KENT.

SPECIALISTS IN SUB-MINIATURE

TELECOMMUNICATIONS

TEL. DEAL 1225.

COMPONENTS



These two instrument tubes are being produced by ETEL to fulfil the requirements of a variety of applications where a 5-inch tube is needed. Both the 5BUP31 and 5BVP31A are high quality p.d.a. tubes with flat screens and side plate connections. Their range of operating voltages is wide and is an important feature of their versatility. The screen of the 5BVP31A is aluminized, and the higher operating voltages allowed with this tube suit it for recording faster phenomena. Full data is available upon request to the address below.

Abridged Data

Heater		
Vh = 6.3V	Th = 0.55A	

Capacitances Cx'-x" . . . 1.6pF. Cy'-y" . . . 1.5pF. One X plate to all other electrodes less other X plate—3.0pF. One Y plate to all other electrodes less other Y plate—2.7pF.

Typical Operation

	ODOLOI	ODATOTE
Va1	2.0k V	1.5kV
V a2	500V	1.0k V
(for focus)	approx.	approx.

Va3			2.0kV	4.0kV	
Va4			4.0k♥	8.0kV	
Vg			-28 to -62 V	-43 to -92	V
Sx			29V/cm	57 V /c	m
Sy			17.5 V/cm	35 V/c	m

(The green medium persistence phosphor used by E.T.L. has now been designated P31. It is exactly the same as the E.T.L. phosphor previously called P1.)



Cathode Ray Tubes

ELECTRONIC TUBES
LIMITED

Kingsmead Works
High Wycombe. Bucks
Tel: High Wycombe 2020

MARCONI

six series

DESIGN FOR

RELIA

A new generation of

AIRADIO EQUIPMENT




Transistor Reliability



Component Reliability



Environmental Reliability

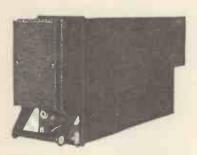

AD 160 V.H.F. communication system. V.H.F. Transmitter type 6400 (short \(\) ATR. 14 lbs.).




V.H.F. communication system. V.H.F. Receiver type 6401 (short \(\) ATR. 8 lbs.).

BILITY



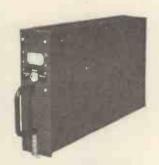AD 260 V.H.F. Navigation system. V.H.F. Receiver type 6401 (short \(\frac{1}{2} \) ART. 8 lbs.).




AD 260 V.H.F. Navigation system. Navigation unit type 6402 (short \(\) ATR. 9 lbs.).



AD 260 V.H.F. Navigation system. Glide Slope Receiver type 6404 (short \(\frac{1}{4} \) ATR. 6 lbs.).



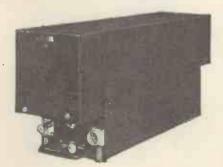AD 260 V.H.F. Navigation system. Marker Receiver type 6403 (dwarf short ½ ATR. 3 lbs.)



AD 360 Automatic Direction Finder ADF Receiver type 6407 (short \(\frac{1}{2} \) ATR. 18\(\frac{1}{2} \) ibs.).



AD 308

Radio Teleprinter Receiver.

Receiver type 4486
(short \(\frac{1}{2} \) ATR. 9 lbs.).

And Now! the Transcription Unit with Autochange

LABORATORY SERIES AUTO TURNTABLE TYPE A designed specially to meet the demand for a Transcription Record Player with provision for automatic use if desired. The heavy turntable incorporates a magnetic shield and sufficient thickness of non-magnetic materials to provide ideal operating conditions for the most sensitive pick-ups. A unit for those who want perfect playing for both stereo and monophonic records.

Garrard
of course



"The 'HI-Fi' fans in Great Britain, but not in America, have hitherto set their faces against record changers; perhaps this will eduse them to look round a little."

Vide Percy Wilson, Gramophone, Sept. 1960

THE GARRARD ENGINEERING AND MANUFACTURING CO LTD

SWINDON WILTSHIRE







armstrong Quality Tuners

T4 FM TUNER A high fidelity VHF tuner of attractive appearance and superb design. Incorporating features normally found only in the most expensive tuners it represents outstanding value at its price. It is completely stable with no trace of drift and A.F.C. provides broad easy tuning. A polished wood cabinet (£2/16/-) is available for those who require a separately mounted tuner.

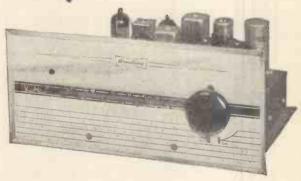Self-powered.
Full VHF band (87-108 Mc/s.).
Automatic frequency control.
Cathode follower output.
Variable output 0-500mV.
Multiplex output for stereo radio adapter.
Separate 75 ohm and 300 ohm aerial inputs.



are designed to match any

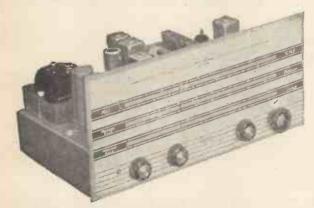

ST3 Mk2 AM/FM TUNER .

This new tuner is the successor to the well-tried and successful ST3. Improvements in design and a considerable reduction in size make the new tuner even more attractive than its predecessor. It includes all the features of the T4 tuner and the A.M. section covers the long and medium wavebands. The ferrite aerial and unique 2nd I.F. stage ensure good continental reception and there is a miniature bright-line indicator for easy tuning.

Self-powered.

Self-powered.
Automatic frequency control.
Cathode follower stage with variable output.
Multiplex output for stereo radio adapter.
Ferrite rod aerial on AM and separate aerial inputs on FM.

amplifier or tape recorder

RF125T AM TUNER . £29 . 14 . 4

A reliable high performance tuner with medium and long bands and three short wavebands. Coverage is: 13-37.5 metres, 30-90 metres, 85-250 metres, 200-550 metres, 600-2,000 metres. A tuned high gain RF stage and two I.F. stages ensure outstanding sensitivity and selectivity. The RF125T incorporates an audio pre-amplifier with separate bass, treble and gain controls for use with existing power amplifiers. It is also available as a complete receiver (RF125R, price £44/14/4) including a high fidelity power amplifier giving 10 watts push-pull output.

Although Armstrong tuners are suitable for use with any amplifier, we recommend, for the enthusiast who wants the best, the Armstrong PCU27 Stereo Pre-Amplifier (£26.10.0d.) together with A10.Mk2 Power Amplifier (£21.10.0d.) Use one A10.Mk2 for mono or two for stereo.

Post this coupon for free catalogue or call at your High Fidelity dealer or our Holloway showroom for demonstration.

Open 9-5 including Saturdays

* The name ARMSTRONG is our registered trade mark

ARMSTRONG WIRELESS & CO. LTD, WARLTERS RD., LONDON, N.7 Telephone: NORth 3213

LONDON'S LEADING STOCKISTS OF -

EQUIPMENT • ACCESSORIES • MATERIALS - GOODS SENT TO ALL PARTS OF THE WORLD

MASTERLINK TAPE UNIT M2A AND COLLARO "STUDIO" DECK

Build your own Hi-Fi Tape Equipment using our tape pre-amp and the new Collaro deck. INC. PRICE 41 gns. Carr. extra. Complete with instructions.

The M2A is complete with external powerpack and is also suitable for use with Wearite and Brenell decks. C.C.I.R. Characteristic. PRICE 27 Gns. Plus P. & P. 41-. Leaflet on

PNEUMATIC LID STAY with pressure adjuster. Heavy duty, 10/- complete, P. & P. 1/6.

SPECIAL OFFERS!

- Rola 7" x 4" Elliptical Speaker 3-5 Ω 13/6. P. & P. 1/6.
- 2. Mains Transformer. Drop through. Primary 0-200-10-20-30-50. Secondary 303-3-300 v. at 70 mA., 6.3 v. 2.4 A. 15/6. P. & P. 2/3.
- 3. Choke IOH 250 mA. Potted "C" Core,
- 4. Choke 20H 50 mA. Potted, 15/-.
- 5. Chake 16H 120 mA. Potted " C " Core,
- 6. Choke 5H 100 mA. Potted, 5/6.
- 7. Choke 5H 300 mA. Potted, 12/6.
- 8. Rectifier 300 v. 300 mA. 13/6.
- 9. R.F. Chokes 4MH Pot cored 7/6.

JASON CONSTRUCTIONAL KITS

"EVEREST" PORTABLE RADIO. Super model. 7 transistors with 3 gang tuning and RF stage, efficient speaker and attractive case. Kit £13/18/9.

"MERCURY." Switched FM/BBC/ITV TV tuner of simple design with AFC for cabinet mounting. Price of complete kit with valves less power pack, £11/14,6. (Power Pack kit £2/14/-, extra.)

AUDIO GENERATOR AG.10. Capacity tuned Wien bridge gives good stability from 10 c.p.s. to 103 ke/s. sine/square wave output. Kit. £15/19/-.

OSCILLOSCOPE QG.10. Push-pull scan on

OSCILLOSCOPE QG.10. Push-pull scan on X and Y plates with an X bandwidth of 10 c.p.s. to 1.5 Mz/s. ± 1dB. Kit £2½/10/s.

ATTENUATOR AA.10. Calibrated in dB giving any reading between 1dB and 110dB. Uses 1% resistors. Kit £7/15/s.

CRYSTAL CALIBRATOR CC.10. Complete with crystal oscillator and audio output, so that signal generators in the range of 100 kc/s.-200 Mc/s. may be accurately checked. Kit £19/19/s.

£19/19/-

VALVE VOLTMETER EM.10. A four valve bridge circuit. May be used as a general purpose meter since there are 23 ranges including D.C. current ranges. Kit 613/13/-W.11 WOBBULATOR KIT. Produces a frequency modulated signal for alignment F.M./A.M. including 465 kc/s. I.F. and T Sound and Picture channels, £14/19/-. and T.V.

45 Œ

riage charged extra

at cost.

LARGE STOCKISTS OF COMPONENTS & EQUIPMENT

by well-known Manufacturers including:-A.B. METAL PRODUCTS • AVO •
BELLING-LEE • BULGIN • COLVERN
• DU3ILIER • ERIE • MORGANITE •
MULLARD • PAINTON • T.C.C.
• WELWYN • WESTINGHOUSE.

STEEL METER CASES

4 x 4 x 4in. Sloping Front		9	- 5
5 x 5 x 8in. S.oping Front		14	11
6 x 6 x 12in. Sloping Front	-61	4	9
4 x 4 x 2½in. Rectangular		6	8
6 x 4 x 3in. Rectangular		8	10
8 x 6 x 3in. Rectangular		H.	0
10 x 6 x 2\frac{1}{2}in. Rectangular		13	3
10 x 7 x 7in. Alum. Panel	£Ι	4	9
12 x 7 x 7in. with Alum. Panel	13	H	5
14 x 7 x 7in. with Alum. Panel	€1	15	9
14 x 9 x 8in. with Alum. Panel	£2	5	8
16 x 9 x 8in. with Alum. Panel	€2	9	6
16 x 11 x 8in. with Alum. Panel		16	8
19 x 11 x 10in, with Alum, Panel	€3	3	10
ALSO FULL RANGE OF CHAS		_	

Chassis and Case List Free on request.

ROTARY WAFER SWITCHES

A.B. Metal and N.S.F. Made to order. Price List free on request.

Immediate dispatch TELE-RADIO (1943) LTD of goods available from stock. Car- 189 EDGWARE ROAD, LONDON, W.2

Phone: PAD 445516

ī

H

B

.

ı

п

ı

Our only address. Few mins, from Marble Arch Open all day Sat.

Superb equipment by



for stereo or monaural

Variable 3 speed motor.

For 334, 45 and 78 r.p.m. Stroboscope fitted with internal light source. Synchronous motor dynamically balanced, resiliently mounted. Mechanical speed change giving 4% variation on all speeds.

£27/16/1 (incl. tax)

2 speed transcription motor

334 r.p.m. and 45 r.p.m. Full 12in, turntable is lathe turned. New nylon graphite bearings. Synchronous motor motor dynamically balanced Neon indicator on/off warning light.


£16/13/1 (incl. tax)



Stereo Amp'ifier and Control Unit Type S66.

Twin channel, delivering 7.5 watts per channel with ultra linear output stage. Inputs for P.U., Tape and Radio, sensitivity being 6mV Separate treble and bass controls.

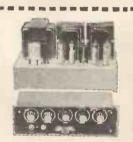Pre-amp £16/10/- (No tax) Amp £24/10/- (No tax)



Stereo Pickup Mark III.

Designed to accept both monaural and stereo heads. Adjustable for heights of various turntables. Pick-up head specification identical with the Type CSI.

Arm only £3/19/11 (incl. tax)


A. R. SUGDEN & Co. (Engineers) Ltd. Market Street, Brighouse, Yorkshire.



Stereo Pickup Type CS1.

Pick-up arm fitted with integral lifting device. The pick-up head employs miniature ceramic units, frequency range 20-16,000 c.p.s. Output 20 mV. with channel separation of 20-25 dbs. Downward pressure 3\frac{1}{2}-4 grams. Diamond stylus. Will accept Mark II monaural heads.

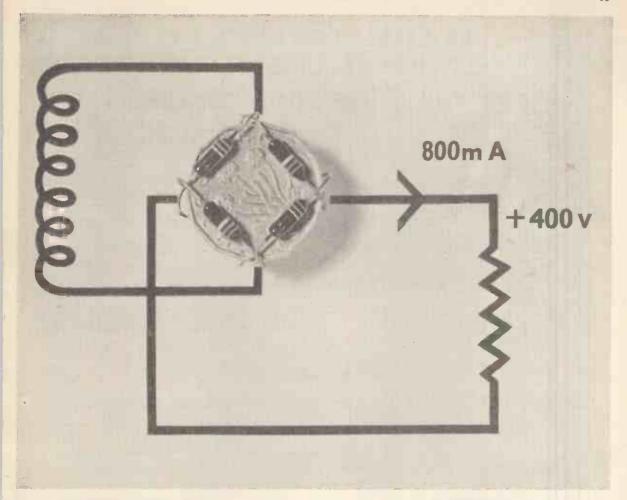Complete £12/19/10 (incl. tax) Arm only £4/19/11 Head only £7/19/11



The big
performance
micro-miniature
SILICON
RECTIFIER
High

SIMET 'M' Series Rectifiers

- High reverse resistance typical value 5,000 MΩ
- High forward conductance
- High temperature operation (up to 150°C)
- All-glass tubular case
- Conforming to CV-7013, 7045 and 7046
- Diameter -12", length -3"

COMPONENTS GROUP Semimetals Division:

THE PLESSEY COMPANY LTD WOOD BURCOTE WAY, TOWCESTER, NORTHANTS Telephone: TOWCESTER 312 Telegrams: PLESSEY, TELEX, TOWCESTER

Overseas Sales Organisation:

PLESSEY INTERNATIONAL LIMITED
ILFORD, ESSEX, ENGLAND
ILEOPHONE: ILFORD 3040
Overseas Telegrams: PLESSINTER, TELEX, ILFORD

Plessey




TRANSISTORIZED F.M. RATIO DISCRIMINATOR & I.F. TRANSFORMERS

FOR THE HOME CONSTRUCTOR . .

I.F. TRANSFORMER, IFT.15

A 10.7 Mc/s double-tuned transformer with tapped secondary and primary windings. Wound on polystyrene former complete with irondust tuning cores and sub-miniature polystyrene foil capacitors. Completely enclosed in an aluminium screening can measuring 7/8in. high by 17/32in. square with two fixing clips. Termination is made to base mounted silver plated pins which are ideal for either printed circuit board or normal metal chassis mounting. Bandwidth of single transformer at -6 dbs is approx. 250 kc/s. Unloaded 'O' of winding 70. Price 10/6

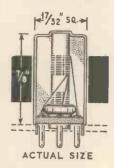

RATIO DISCRIMINATOR TRANSFORMER, RDT.2

A sub-miniature 10.7 Mc/s transformer for use in ratio discriminator type circuits. Secondary winding is of bifilar construction. Dimensions as IFT.15.


Peak Separation approximately 220 kc/s.


Connection diagram supplied with each coil. Price 10/6

GENERAL CATALOGUE covering full range of components send 1/4 in stamps.

PLEASE SEND S.A.E. WITH ALL ENQUIRIES

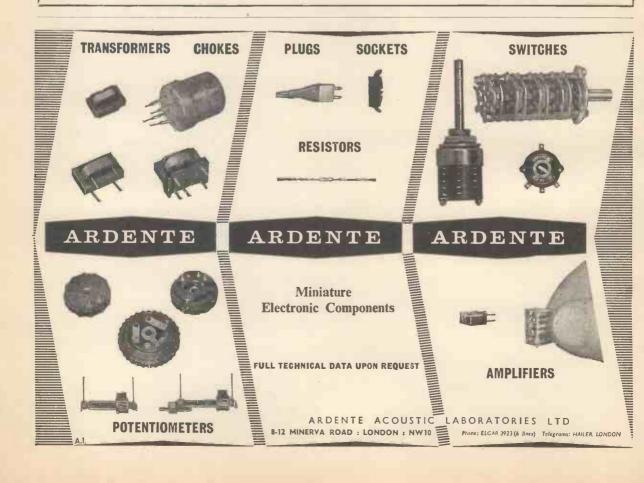DENCO (CLACTON) LTD. (Dept. W.W.), 357/9 Old Road, Clacton-on-Sea, Essex



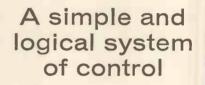

The Quad 22 Control Unit incorporates every practical refinement for the full appreciation and enjoyment of the discriminating listener. For instance

PICK-UP MATCHING

The system of plug-in adaptor units pioneered in the QUAD II Control Unit has been extended in the QUAD 22 to provide for all stereo and monaural pick-ups. Thus any pick-up may be accurately matched independently for stereo and mono, merely by plugging in, during installation, the correct adaptor as shown on the chart provided.

Once this adaptor is fitted, all switching is carried out by the push-buttons on the front panel and there is no need to change connections or adaptor units at the rear of the equipment.

Send a postcard to Dept. W.W. for Illustrated leaflet

ACOUSTICAL MANUFACTURING CO. LTD. HUNTINGDON, HUNTS. HUNTINGDON 361

for the closest approach to the original sound



R. E. COOKE, B.Sc. (Eng) as Technical Editor

224 Pages. 160 Illustrations (of which 110 are original) Fine art paper. Cloth bound. Price 15/6 (16/6 post free)

About 400 technical words and subjects relating directly or indirectly to Audio are explained and commented upon in non-technical terms and occasionally in lighter vein. Many facts and figures about loudspeakers, pickups, sound recording and reproduction, record players, tape recorders, television, transistors, etc., are included, thus providing a handy book of reference.

OTHER BOOKS BY G. A. BRIGGS INCLUDE




Sold by radio dealers and bookshops.

Tel: Idle 1235/6 Grams: "Wharfdel" Idle, Bradford Whattedale WIRELESS WORKS LTD IDLE BRADFORD YORKS



designed for

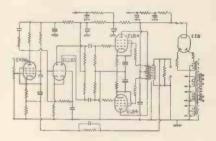


Type AS.7012*, Solent series Audio Output Transformer, has been designed especially for the Mullard 5 Valve 10 Watt High Quality Amplifier, and is capable of the highest quality reproduction. The static frequency response (without feedback) is within 0.5 db. from $20 \sim$ to $25,000 \sim$, and there is appreciable response at 50kCs. and above. Primary tappings for feedback are provided at 43% and 20%, of the windings, and the secondary windings are suitable for 3.75Ω and 15Ω , with identical characteristics on both outputs. A response curve, panel layout and loudspeaker connection chart are included with each transformer. Priced at 49/3, it can be obtained through your local radio dealer, or direct from us, post free.

* This is one of twenty-two Audio Transformers in the Solent and Minford series described in Gardners new-leaflet "S/M," which includes over a hundred standard Mains Transformers and Chokes. We shall be pleased to post you a copy upon request.

RESPONSE CURVE:-



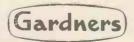

GARDNERS RADIO LTD CHRISTCHURCH, HANTS. Tel.: Christchurch 1734



Model Atelier I. Table radio-gram, with two U Loudspeakers for monophonic or stereophonic reproduction of radio and record.

T22. L.M.S. & V.H.F.

2

3

4

Portable T23. 4 S.W. (inc. Trawler) & M.W. T24. S.M. & L.W.

Loudspeaker Ll, matching Atelier I

Model SK5 Table Radiogram, in sycamore and white with plastic lid

Model TPI Transistorised Battery Portable Radiogram

TYLED in beauty to delight your eyes and ears.

Providing the most critical listener with concerthall mono or stereophonic reproduction of radio and record in the comfort of his own home, in cabinets of undating charm and beauty . . . a range of moderately priced radio receivers and radiograms that will satisfy the taste of the most fastidious, in keeping with modern furnishing trends.


Available from leading Departmental Stores and Radio Dealers Sole Concessionnaires for United Kingdom

WINTER TRADING CO. LTD. 95/99 Ladbroke Grove, London, W.II. Telephone: Park 1341 (10 lines)



58



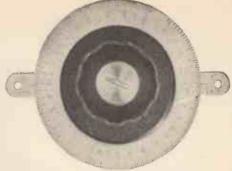

stability for vision circuit testing

For the really effective testing of vision circuits the Video Oscillator Type 022B provides an input signal that is exceptionally accurate and stable.


The accuracy of calibration is, in fact, 1% over the frequency band 10 kc/s to 10 Mc/s, whilst the amplitude remains constant to within $\pm \frac{1}{2}$ dB throughout this frequency range and is independent of variations in mains voltage and range setting. Thus the necessity for resetting the reference level no longer exists, and instead a means of measuring the load impedance by the reading on the output voltmeter is provided

output voltmeter is provided.

The total harmonic content of the output waveform of this high quality oscillator is less than 1%. These standards of performance in a compact, portable item of equipment explain why the Wayne Kerr Video Oscillator Type O22B is so widely used by the G.P.O., B.B.C. and throughout the television industry.

The Wayne Kerr Video Oscillator is fully

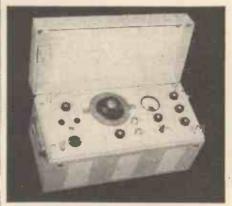The Wayne Kerr Video Oscillator is fully described in Information Service Leaflet DO 22B, copies of which are available on request.



THE WAYNE KERR LABORATORIES LTD., Sales and Service, 44 Coombe Road, New Malden, Surrey. Tel: MALden 2202

R.C.12



WAYNE KERR Video Oscillator O22B





Noise power excluding image frequency contribution 15·25db Operating Current 35mA Overall Length $6\frac{21}{32}$ " Base Diameter 0.64" Discharge Tube Diameter 0.185"

FERRANTI LTD . KINGS CROSS ROAD . DUNDEE

Telephone DUNDEE 87141





There was a designer from Wigan Who said "there's no room for a big 'un, It's got to be small

Or it's no use at all ..."

















Search as you will, you'll find no better line in the end; we've been making miniature transformers for long enough to know when they're good. Can we tell you about them in detail?

FORTIPHONE LTD. TRANSFORMER DIVISION DEPT. 5 124-126 DENMARK HILL LONDON S.E.5


GOOD COMPANIONS!

MINIATURE TRANSISTORIZED SIGNAL GENERATOR TYPE 40

- Up to 20 Mc/s on fundamentals.
- R.F. and Audio Output, Attenuated.
- Accuracy better than 2%.
- Miniature size only $4\frac{1}{2}$ in. x $3\frac{1}{2}$ in.

PRICE NET £5.15.0. Post (C.O.D. or C.W.O.), 2/6.

Battery 2/6 extra

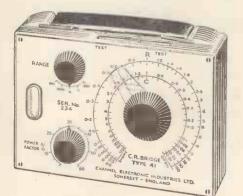



MINIATURE TRANSISTORIZED R.C. BRIDGE TYPE 41

- Capacitance 5 $\mu\mu$ F to 20 μ F. Resistance 5 Ω to 20 M/ Ω .
- Magic Eye Balance Indicator.
- Calibrated Power Factor Check.
 - Miniature Size-Light Weight.

PRICE NET £5.10.0.


Battery 3/3 extra.


Post (C.O.D. or C.W.O.), 2/6. EXPORT ENQUIRIES INVITED.


SEND S.A.E. FOR LEAFLETS, OR ORDER TODAY, FROM

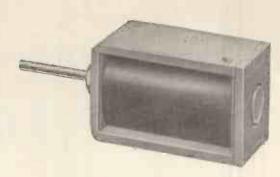
ELECTRONIC INDUSTRIES LTD. DEPT. P., DUNSTAN RD. BURNHAM-ON-SEA, SOM.





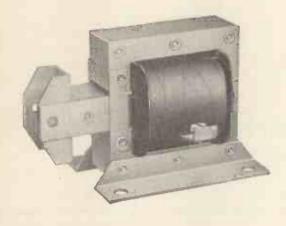

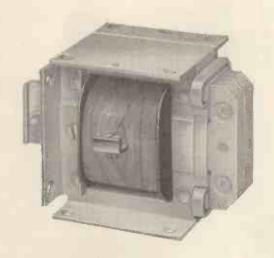

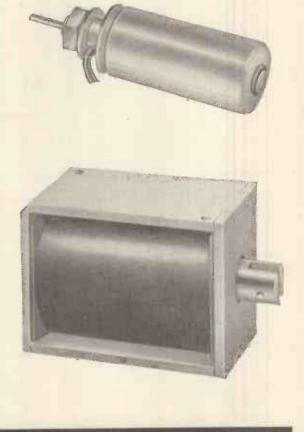

A FULL RANGE OF A.C. & D.C.
SOLENOIDS

PROMPT DELIVERY

Illustrated technical data sent on request:

ELECTRO METHODS LTD., General Products Division, CAXTON WAY, STEVENAGE, HERTS

UNUSUAL SINGLE SPEAKER SYSTEM

An inexpensive column speaker constructed from a concrete pipe and fitted with a good 8in or 10in. unit has attracted much interest and admiration because of its clean open sound.



A CONCRETE COLUMN

Complete kits of wooden fixtures are available including absorbent wadding and diffusing cone.

Price £3 15 0 for 8in. model.

Recommended 8in. unit-8/145, £6 19 11 including purchase tax.

Price £4 18 o for 10in. model.

Recommended 10in. units—W10/FSB, £12 9 10. Golden/FSB, £8 6 7. 10in. Bronze/FSB, £5 5 11. Prices include purchase tax.

Suitable concrete pipes can be purchased from builders' merchants at about 12/6 and 17/6.

Descriptive leaflet on request from:

Wharfedale WIRELESS WORKS LTD IDLE BRADFORD YORKS

Telephone: Idle 1235/6 Telegrams: 'Wharfdel' Idle, Bradford

your press tool costs

HUNTON

UNIVERSAL BOLSTER OUTFIT

In addition to the range of Punches and Dies in. to 3\frac{3}{4}\text{in.} dia. available from stock, some of the tools usually required in the Radio and Electronic Industries have been standardised for use with the Hunton Universal Bolster Outfit. Illustrated here are a few which can be supplied quickly or from stock.

In London and Home Counties, ask for a practical demonstration in your own works.

Write for illustrated brochure W.W.I

HUNTON LTD.

Phoenix Works, II4-II6, Euston Road, London, N.W.i

TELEPHONE: EUSton 1477 (3 lines) Telegrams: Unotonexh, London

MAIN DISTRIBUTORS FOR LANCASHIRE, YORKSHIRE AND CHESHIRE

JAS. H. VICKERY & CO. LTD. 21 Bradshaw Street, Manchester, 4 Telephone: Blackfriars 3221. Telegrams: Vickery, Manchester






... SAY VOLSTAT

VOLSTAT is the one simple word you need to remember when you are up against any mains voltage fluctuation problem.

VOLSTAT stands for a range of Constant Voltage Transformers produced by "Advance"—the leading authority on voltage stabilization.

VOLSTAT is backed by exclusive design, development and manufacturing skills which over many years have so often provided the only solution to mains voltage stabilization problems.

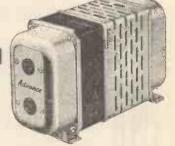Full details in Folder W63 available on request.



ACUTE COMPONENTS LIMITED
MAINS STABILIZATION DIVISION

ROBBUCK ROAD . HAINAULT . ILFORD . ESSEX . TELEPHONE : HAINAULT

IT/GD82

FOR BERYLLIUM COPPER PRESSINGS TO THE CLOSEST TOLERANCES

CONSULT

RANDAUER OF BIRMINGHAM



TOLERANCES NOW + '00025":

By pione ring the use of beryllium copper and preclous metals, Brandauer have achieved many manufacturing successes which can be of great value to you. Today we are among the largest most sought-after fabricators of beryllium copper pressings in Britain—thanks to a hundred years of heat treatment experience, specialised plant, and ten years of research. Being craismen, experts and indeed the outs anding specialise in beryllium copper, we work with extreme precise in in ministure and subministure presswors: in certain circumstances, we regularly maintain an accuracy of plus or minus .00025in.

All components are made to customers' own requirements. It is significant that several million Brandauer un'ts are in daily use in the radio, television and aircraft indus, ries, in radar installations, record players, switch gear, electronic computers and a wide range of other equipment.

EARLY DELIVERIES OF FOUR SLIDE WORK:

This is also belyful. So are our large stocks of material. They enable us to quote early deliveries for most pressings and competitive prices for all. Therefore—for time and tolerance, quality and price, choose Brandauer. Further information and samples gladly sent on request.

BRANDAUER

MODEL FE WAS

Brandauer also specialises in precision pressings manufactured from all ferrous and non-ferrous materials including the cupro-fickel alloys.

C. BRANDAUER & CO. LTD., 401 NEW JOHN STREET WEST, BIRMINGHAM 19
Telephone: ASTON CROSS 3818

Small, neat and easy to fit



Write for details of this and other equipment in the range to:

POWER UNIT

Preset output voltage from 2 to 18 volts. Output current | A. max.

Source impedance less than 0.02 ohms.

High stabilization ratio 400—1.

Small size 5 x 5¼ x 5in.

Ripple I mV.

INSTRUMENTS LTD.

CRAWLEY ROAD, HORSHAM, SUSSEX. Horsham 3232/5

Thinking of Transformers? DEBAND

Considerable research and a unique, patented construction are behind the standard Balun range. For an aperiodic system of matching, without the necessity for tuning devices or resonant circuits.

BALUN LTO HORSHAM

. think of

LIMITED

Insertion loss never greater than 3 db.
Balance ratio always better than 20 db.

ohms.

First with Wide Band Transformers.

Three basic frequency ranges: 25 c/s.—2 Mc/s.
100 kc/s.—100 Mc/s.
3 Mc/s.—300 Mc/s.
Other types up to 1,000 Mc/s.
available.
Choice of six balanced output impedances from 50 to 600 ohms.

CRAWLEY ROAD, HORSHAM, SUSSEX, Horsham 3232/3

OT125

QT1250

'ENGLISH ELECTRIC'

TRIGGER TUBES

QTI25I was developed by the ENGLISHELECTRIC VALVE COMPANY LTD. from the well known 5823 with the object of reducing the tolerance on trigger breakdown voltage. Flying leads have been incorporated for direct wiring-in. The improved characteristics find particular application in electronic telephone exchanges.

A B7G version of the QT1251 is available with the type number QT1250.

Characteristics	QT1250 & QT1251	5823
Peak Cathode Current max. (mA)	100	100
Mean Cathode Current max. (mA)	25	25
Operating Voltage max. (V)	68	85
Trigger Breakdown Voltage max.(V)	80	105
*Transfer Current nom. (µA)	140	135

*at Va=100V

AGENTS THROUGHOUT THE WORLD


ENGLISH ELECTRIC VALVE COMPANY LTD.

CHELMSFORD · ENGLAND


Telephone: CHELMSFORD 3491

Buller's CERAMICS FOR INDUSTRY

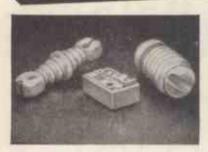High quality material and dimensional precision are attributes of Bullers die-pressed products. Prompt delivery at competitive prices.





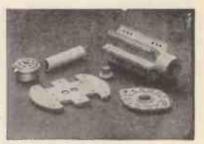

We specialise in the manufacture of -PORCELAIN for general insulation

REFRACTORIES

for high-temperature insulation

FREQUELEX for high-frequency insulation PERMALEX & TEMPLEX

for capacitors



Phone: Stoke-on-Trent 54321 (5 lines) · Telegrams & Cables: Bullers, Stoke-on-Trent

Ironworks: TIPTON, STAFFS London Office: 6 LAURENCE POUNTNEY HILL, E.C.4
Phone: Tipton 1691 Phone: MANSion House 9971





POTENTIOMETERS . POTENZIOM RI . POTENTIOMETER POTENTIOMETRES . P ENCIOMETROS

Choose from hundreds of factory models


Custom made to your specifications

World renowned reliability

LESA COSTRUZIONI ELETTROMECCANICHE S. P. A. - VIA BERGAMO, 21 MILANO (ITALY) LESA OF AMERICA 11 WEST 42ND STREET - NEW YORK, 36 NY. - U.S. A. AUSMIT IN THE HERE THE OM

CARTRAM CLARKE LTD - 121-123 EDGWARE BOAD, MARBLE ARCH, LONDON, W. 2

TRANSFORMERS

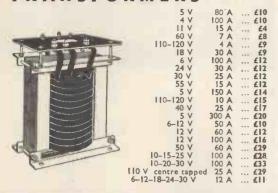

All for 240 V Input. Other Supply Voltages as Required CONTINUOUS RATING. Short Rating Transformers also available

5 V	5,000 A	************	£110	1 10
2.5 V	5,000 A	************	£64	240
4 V	5,000 A		£94	90
2 V	10,000 A			
3.5 V	20,000 A			
2 V	30,000 A		£130	
10 V	700 A		£59	
10 V	2,000 A		£103	
10 V	1,000 A		£66	
10 V	900 A		£62	
10 V	500 A			2 /2
10 V	300 A			
20 V	800 A			
20 V				Company of the last
5 V	1,000 A			
22 V	1,000 A		-	201
28 V	1,000 A		£90	-01

TRANSDUCTORS

SATURABLE REACTORS



Saturable Reactors for controlling AC loads from .5kVA to 300kVA. Available for all standard AC supply voltages, single-phase and 3-phase. Standard DC control volts: 12, 24, 36, 110 and 240 V.

THREE-PHASE TRANSFORMERS

Input 400/440 V.

40 V 50 A 3-phase £40 230 V 50 A 3-phase £78 110 V 100 A 3-phase £90 4 V 5,000 A 3-phase £130

These and other Transformers can be supplied for 3-phase, 6-phase and 12-phase Rectifiers.





VOLTMOBILE

VOLTAGE SELECTOR AUTO-TRANSFORMERS

Range: From 1.6% to 100% of Supply Volts in 64 steps of 1.6%.
ON LOAD SWITCHING.

VOLTMOBILES can be used by themselves or in the primary of another transformer to give very fine changes of output Overvoltage available as extra.

Single Phase Units	240 V	440 V
15 A	£28	£37
30 A	£39	£50
60 A	£69	£81
100 A	£99	£121



D-CMOBILE RECTIFIER SETS

For 240 V AC. The larger outputs are available for 3-phase supply.

	Full load	DC Vol	ts and Amps	s are stated.	
	Prices are wi				
6 V	15 A	£14	36 V	IO A	£26
6 V	50 A	£47	36 V	20 A	
6 V	100 A		36 V	40 A	£42
12 V	I0 A		36 V	60 A	£55
12 V	20 A		110 V	5 A	
12 V	30 A		110 V	10 A	£42
12 V	60 A	£45	110 V	15 A	£53
12 V	105 A	£62	110 V	20 A	
12 V	210 A	£83	110 V	25 A	
12 V	1,000 A	£185	220 V	130 mA	
24 V	12 A		250 V	6 A	
24 V	20 A		250 V		
24 V	30 A	£33	250 V	15 A	
24 V	60 A		250 V	20 A	
24 V	105 A		1.200 V	225 mA	
24 V	200 A	£86	.,	Built in to o	
24 V	750 A	£262		Stabilising Ci	
T-1 A	700 /1	4242			



Built in to order—Ammeters—Voltmeters—Rheostats— Stabilising Circuits—Chokes—Variacs.


CARRIAGE EXTRA on all units
SPECIFIC ENQUIRIES are invited for
Transformers and Rectifiers. We specialize
in HEAVY CURRENT EQUIPMENT.

HARMSWORTH, TOWNLEY & CO.
2 JORDAN STREET, MANCHESTER 15. CENTRAL 5069



SOLDERING INSTRUMENTS EOUIPMENT

PRODUCTS FOR PRODUCTION

 


ALL BRITISH MANUFACTURE

ILLUSTRATED

SOLDERING INSTRU-MENT, LIST No. 70 WITH COMBINED PROTECTIVE UNIT, LIST No. 700 SHOW-ING WIPER/ABRA-SION PAD AND SOLDER REEL.

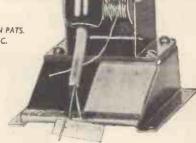BRITISH AND FOREIGN PATS. REG. DESIGNS ETC.



APPLY FULL PARTICULARS

ADCOLA PRODUCTS LTD.


HEAD OFFICE

GAUDEN ROAD, CLAPHAM HIGH ST., LONDON, S.W.4

Telephones: MACaulay 4272 & 3101


Telegrams: "SOLIJOINT," LONDON

INCREASE YOUR SALES AND PROFITS WITH...

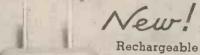

"Blue Battery" for Transistor Radio using 9-Volt Battery.

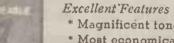This revolutionary miniature "BLUE BATTERY" is designed as a perfect companion for your Transistor Radio. "BLUE BATTERY" is continuously rechargeable for more than 100 times.



- * Magnificent tone * Most economical
- * Reliable power
- * Easy to charge

SPECIFICATION



KIND OF PLUGS TRC-9-2A1 2 flat pins TRC-9-2B1 2 flat pins

非正行主义

PAT. NO 497725 (JAPAN

TRC-9-2824 2 round pins (4mm)
TRC-9-2825 2 round pins (5mm)

MANUFACTURERS & EXPORTERS ...

TOREI INDUSTRIAL CORPORATION

No. 150, KUGAHARA-CHO, OHTA-KU, TOKYO, JAPAN Cable: "TOREINDUST" TOKYO


REDIFFUSION




solderless wiring devices



 Auto/Machine applying AMPin and Miniature Faston terminals.





 

Miniature Factor for quick connect/ disconnect of leads to board. ...to the end

* Miniature Faston

A SPEEDY APPLICATION

A LOWER APPLIED COSTS

A UNIFORM HIGH QUALITY

A HIGH ELECTRICAL AND MECHANICAL STABILITY

WRITE NOW ABOUT THE CREATIVE APPROACH TO BETTER WIRING

AIRCRAFT-MARINE PRODUCTS (GT. BRITAIN) LTD


TRADE MARK

* Trade Mark of AMP Incorporated. U.S.A. Head Office: Dept. 15, AMPLO HOUSE, 87/89 SAFFRON HILL, LONDON E.C.1. Tel: CHAncery 2902 (7 lines) Telex. 23513 Cables: AMPLO LONDON TELEX. SOUTH AFRICA: DISTRIBUTOR: E. S. MOWAT & SONS (PTY) LTD., 51-57, MILNE STREET, P.O. BOX 437, DURBAN, NATAL, SOUTH AFRICA.

AUSTRALIA: MANUFACTURING COMPANY: AIRCRAFT-MARINE PRODUCTS: (AUSTRALIA) PTY. LTD., BOX 78, P.O. AUBURN, N.S.W. AUSTRALIA. DISTRIBUTOR: GREENDALE ENGINEERING AND CABLES PTY. LTD., 43-51 NELSON STREET, ANNANDALE, N.S.W. AUSTRALIA.

ASSOCIATED COMPANIES IN: U.S.A., CANADA, HOLLAND, FRANCE, GERMANY, ITALY, JAPAN, PUERTO RICO AND MEXICO.

AP 137

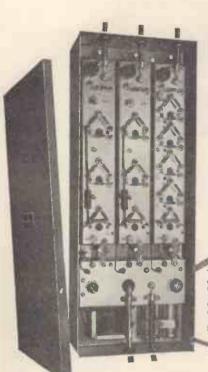

Leads again with the FIRST

TRANSISTORISED AERIAL AMPLIFIER

TELENG again leads in the full use of the latest H.F. Transistors in revolutionary amplifier equipment, operating in Bands 1, 2, & 3, for general use in Communal Aerial and Wired T/V Systems.

TRANSISTOR AMPLIFIER Type U4000

Three amplifiers with power unit in case overall size 13in. x 6½in. x 2in.
Gain 40db any Channel to order in Bands 1 and 3.
Gain 37db all V.H.F. Channels in Band 2.
O/P 130 m/V of each channel with Xmod—

43db, For AC Mains, consumption 1-5 watts


SIZE — PRICE — PERFORMANCE — RELIABILITY —

are all truly astounding and the workmanship and finish are fully in line with the usual Teleng high standards.

Send for fully descriptive list to :-

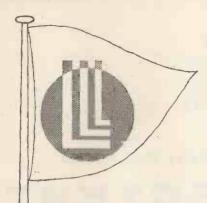TELENG LIMITED, TELENG WORKS, CHURCH ROAD, HAROLD WOOD, ROMFORD, ESSEX Ingrebourne 42976-7-8





UNDER ONE ROOF

THE WORLD'S BEST MANUFACTURERS
IN BOTH GREAT BRITAIN AND OVERSEAS



NEW TOOL FOR HIGH VACUUM SPECIALISTS Introducing a whole new series of ion pumps that will develop absolutely clean vacuum, better than 10-9 mm Hg. They are available In pumping capacities of 100 and 250 litres/second. Larger sizes can be supplied on special order. They offer tremendous advantages in such applications as particle accelerators, space research chambers, fusion processes, mass spectrometers, electron microscopes, vacuum tube processing—whenever uncontaminated ultra-high vacuums are required.

KLYSTRONS, TRAVELLING WAVE TUBES, BACKWARD WAVE OSCILLA-TORS, HIGH VACUUM PUMPS.

In the field of instrumentation, Livingston Laboratories offer a unique service in the form of expert advice in the choosing of test equipment to meet your needs.

The relevant factors are not who makes it or where it is made, but will it do the job? At Retcar Street you can discuss the technical problems of instrumentation and the new techniques developed both in this country and abroad. If it is impossible to call—write or telephone about your particular problem or requirement and our representatives will supply you with full information.

Some of the manufacturers outside Great Britain whom we represent and for whose products we offer full service facilities:


BIRD ELECTRONIC CORP. • BOONTON RADIO CORP. • BRUSH INSTRUMENTS • DYMEC INC. • E. H. RESEARCH LABORATORIES. • ELECTRO SCIENTIFIC INDUSTRIES INC. • EMPIRE DEVICES PROD. CORP. • JOHN FLUKE MANUFACTURING • GERTSCH PROD. INC. • HEWLETT-PACKARD CO. • KAY ELECTRIC CO. • KEITHLEY INSTRUMENTS INC. • ARTHUR KLEMT • MAGNETIC A.B. • F. L. MOSELEY CO. • RADIO FREQUENCY LABORATORIES INC. • RADIOMETER • S.I.D.E.R. • TEKTRONIX INC. • TELECHROME MANUFACTURING CORP. • VARIAN ASSOCIATES (Microwave Tube Division).



LIVINGSTON LABORATORIES LTD.

RETCAR STREET . LONDON N.19

Telephone: Archway 6251

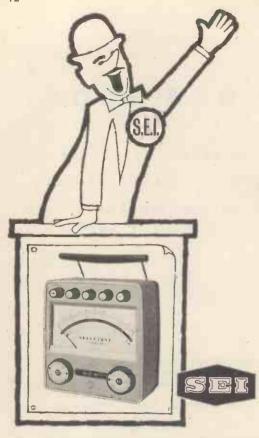

every electrical engineer should have....

THE NEW SALFORD

SELECTEST

MODEL SUPER K

1 mA movement.

39 self-contained ranges for measuring A.C., D.C. voltages and currents and resistance,

MODEL SUPER 50

50 µA movement

Send for leaflet No. SK.50/6002/WW

SALFORD ELECTRICAL INSTRUMENTS LTD.

PEEL WORKS, SILK STREET, SALFORD 3, LANCASHIRE, Tel: Blackfriars 6688

London Sales Office: Magnet House, Kingsway, W.C.2. Tel: Temple Bar 4668

A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND





We can get you
out of an
Audio-Valve problem

Here is a brilliant newcomer to the much celebrated KT series of beam tetrodes—the KT 77. We have been getting people out of valve problems for over 40 years and now we've put all that experience into this valve, which joins our KT 55, 66 and 88 range.

S. E. C.)

		P out† (W)	Distortion†	v supply (V)	Seated height (mm)	Max diameter (mm)
	KT 55	25	1,5	*	128	53
m.	KT 66	50	3	525	120	53
9	KT 77	70	1	600	98	33
	KT 88	100	1.5	500	110	53

† Class AB₁, ultra-linear connection * 190—260 V. AC or DC mains

A comprehensive range of audio valves is available, to give outputs up to at least 50 kW.

For full details, write to:-

THE M-O VALVE CO LTD

BROOK GREEN • HAMMERSMITH • LONDON W6 A subsidiary of The General Electric Co Ltd

25/-

32/6

IUST RELEASED! GARRARD AUTO-TURNTABLE



(with G.C.8 cartridge)
A transcription Record Player with
provision for automatic use, if
desired. Perfect playing from both
Stereo and Mono records.

PYE MOZART



FM TUNER

Incorporating a push-button on-off control and built-in power pack. It gives good reception up to 30 miles (indoor aerial) and 80 miles (outdoor aerial). Features includes (indoor aerial) and 80 miles (outdoor aerial). Features include: Automatic Frequency Control: Twin Limiters. Frequency response: 20-20,000 c.p.s. In expanded metal case or chassis form. Model HFT108M £24. Model HFT108 (Chassis) £22.

MOZART STEREO AMPLI-FIER IOW. Per

Channel Output Model HFS20 (Chassis) £35. expanded metal case £36/15/0. Or in

"O-MAX"

SHIET METAL PUNCHES Patent No. 619178 and Patents

pending Round, Square and Rectangular

NEW SIZES: II/I6in. SQUARE

21/32in. x 15/16in. RECTANGULAR

SOLE LONDON DISTRIBUTORS 0F

ELCOM

MINIATURE MULTI-WAY PLUGS & SOCKETS



"Q-MAX" MODEL G D.O.-2 GRID DIP OSCILLATOR

An ideal instrument for the determination of tuned circuit resonant frequency, tuning transmitters with-out application of power, for the determination of coil mutual and stray inductances and both fixed and stray capacitances. Built-in mains pack. Covers 1.5 to 300 Mc/s. in eight ranges. PRICE 15 GNS. Complete.

LARGE STOCKS ALWAYS AVAILABLE OF

- BELLING-LEE BULGIN
- COSMOCORD
 GILSON
- " LAB " GOODMANS • T.C.C. WELWYN, etc., etc.

Full Range of HI-FI. MONAURAL **STEREO** ON

DEMONSTRATION

25 HIGH HOLBORN, LONDON, W.C.1.

Tel.: HOLborn 6231/2

For HIGH SENSITIVITY! HIGHEST FIDELITY! MAXIMUM RELIABILITY! REASONABLE COST! Also Available

Illustrated

CATALOGUE

of HI-FI and

ELECTRONIC EQUIPMENT

6d. Post Free

MODEL LIO HIGH FIDELITY IO WATT **AMPLIFIER**

WITH SEPARATE PRE-AMPLIFIER

Supplied complete 1 Retail Supplied complete only (i.e. Main)

Size of main amplifier 9in, x 7in. x 5in., Preamp, 11in. x 4½in. x 2½in. Front Plate 12in, x 3½in. Stoved Gold hammered finished chassis. Front Plate Polychromatic Gold. Weight of main amplifier 101b. Pre-amp. 3lb. For 50/60 c.p.s. A.C. mains 200–230–250 v. or to order for export.

The Following Ourstanding Test Figures include Pre-amplifier.

include Pre-amplifier.

Sensitivity (for 10 watts) L.P. 25 m.v. 78 r.p.m. 20 m.v. Radio, 35 m.v. Microphone, 2.5 m.v.

Input Impedance

All inputs 500k, Plus 10pfd. Frequency Response ±2 d.b. 30-25,000 c.p.s. Power Consumption


90 watts. Maximum Power Output In excess of 12 watts. Negative Feedback Total 32 d.b.

DISTORTION (Inc. Pre-amplifier) 0.09% measured at 10 watts. Damping Factor 35 Bass Control +9 d.b. to -9 d.b. at 50 c.p.s. Treble Control +9 d.b. to -9 d.b. at 12,000 c.p.s.

Hum Level - 70 d.b. Filter

-7 d.b. at 9 Kc/s.

-10 d.b. at 5 Kc/s.

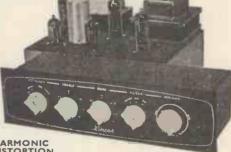

MULLARD VALVES EF86 (1); ECC83(2); EL84 (2); EZ81(1).

OUTPUT MATCHINGS For 3 ohm and 15 ohm L/Speakers from high grade sectionally wound output transformer.

RESERVE POWER SUP-PLY (for Radio Tuner) 300 v. 30 m.a. smoothed and 6.3 v. 1.5 a. at 4-pin socket.

The L45. A Compact High Quality 4-5 watt amplifier.

Size approx. 7-5-5% in. high. Sensitivity is 28 millivolts so that the input socket is 28 millivolts so that the input socket can be used for either microphone or gram, tape, radio tuner, etc. B.V.A. valves used are: ECC83, EL84, EZ80. Controls are: Vol., Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5/19/6. THE LT45 TAPE DECK AMPLIFIER. A complete unit (power pack and oscillator incorporated) ready for connection to A.C. malns. 3 ohm loudspeaker and practically any make of connection to A.C. mains. 3 ohm loud-speaker and practically any make of deck. Negative feedback equalization adjustment by multi-position switch for 3½, 7½ and 15in. per sec. Retail price 12 gns.

DIATONIC 10-14 WATT. High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

CONCHORD 30 WATT. Hi-Fi amplifier with two separately controlled inputs. Retail 16 gns.

L50 50 WATT AMPLIFIER. Size approx. 13 x 9 x 7in. Sensitivity 25 m.v. Outputs for 3 and 15 ohm speakers. Retail price 19 gns.

L3/3 STEREOPHONIC AMPLIFIER. Sensitivity 150 m.v. Output 3 watts on each channel. Retail 7 gns.


TRADE AND EXPORT ENQUIRIES TO:

PRODUCTS

LTD.

ELECTRON WORKS, ARMLEY, LEEDS.

Tel.: Leeds 63-0126 (3 lines)

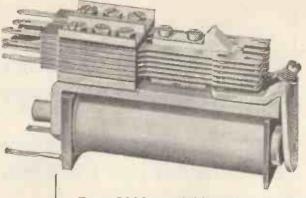


RELAYS

Type 3000, available with a wide range of contact. combinations, coil resistances and slugs.

Tropical finish type approved to RCS 161.

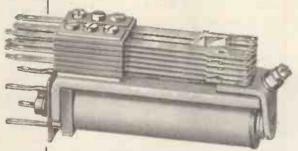Standard finish for telecommunications applications in temperate climates.




Type 600, available with a wide range of contact combinations and coil resistances.

Tropical finish type approved to RCS 161.

Standard finish for telecommunications applications in temperate climates.

Remanent (magnetic latching) versions of type 3000 and type 600 are also available.

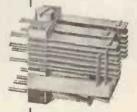TELECOMMUNICATIONS
PLUGS · LEVER KEYS · CABLES
FUSE MOUNTINGS · AMPLIFIERS
CONTROL PANELS · MOULDINGS
COUNTERS · PLUNGER SWITCHES
MAGNETIC AMPLIFIERS · RELAYS
SATURABLE REACTORS · JACKS
TRANSFORMERS · INSTRUMENTS
CORDS · INTERNAL TELEPHONES
TRANSISTOR INVERTERS · BELLS
PROTECTORS · WIRES · BUZZERS




Cubic Inch, combining high speed and sensitivity in a new miniature design with twin contacts of the well-proven form used on the type 3000 relay.

THE PHOENIX TELEPHONE AND ELECTRIC WORKS LIMITED, THE HYDE, LONDON, N.W.9. Telephone COLINDALE 7243

TELEVISION AERIAL COMPONENTS

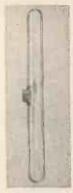DESIGNED FOR CONSTRUCTING
BAND I & BAND III T.V. AERIALS



Tel: HEYWOOD 6868

ELEMENT DIMENSIONS SUPPLIED FOR ALL CHANNELS

Selecting at random from our new multi-page catalogue:

- Band III Folded Dipoles (As illustrated).
- Reflector and director rod holders.
- Masthead Fittings for $\frac{3}{4}$ ", 1", $1\frac{1}{2}$ " and 2" Masts.

TIMES MILL


- Mast Coupling Units for 2" Masts.
- Insulators, Both Rubber and Plastic (As illustrated).
- Alloy Tubing for Elements, Crossboom and Masting.

Send I/- P.O. for the revised, fully Illustrated catalogue to

Pringevision Ltd

96.C

MARLBOROUGH, WILTS. Phone: 657/8

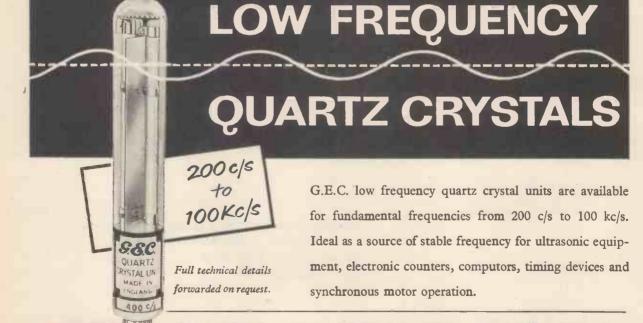

SALFORD ELECTRICAL INSTRUMENTS

London Sales Office: Magnet House, Kingsway, W.C.2. Tel: Temple Bar 4668

A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

· HEYWOOD · LANCASHIRE



... and 200 miles away a telephone rings!

Eight hours ago, an expanse of barren mountainous country made communication impossible. Tonight, 60 telephone channels and teletype span the wilderness.

Transportable MICROSCATTER is a super high frequency radio system for long-range communication. Developed by Canadian Westinghouse, MICROSCATTER beams signals high above the earth sending two-way voice and teletype messages up to 200 miles over land and water ... without costly relay stations.

The compact MICROSCATTER radio system fits in a standard 30 ft. truck trailer. Now, whenever men and equipment move, MICROSCATTER moves right along with them. It is particularly suited to military and government projects in remote locations. Units designed for self-contained field operations are set down by helicopter.

A Westinghouse communications specialist will be pleased to explain fully the MICRO-SCATTER operation and relate it to your problem. Contact your nearest Westinghouse office, or write to Canadian Westinghouse Company Limited, Electronics Division, Hamilton, Canada. YOU CAN BE SURE... IF IT'S WESTINGHOUSE.

MICROSCATTER APPLICATIONS

Fixed Station —120 telephone channels —television and

-television and

Transportable—60 telephone channels—teletype

Wide Band —radar

—data —120 telephone

channels
Tactical and —60 voice channels
Transportable—teletype
—data

FEATURES

- Frequency—4400-5000 mc
- Antennas 10 to 28 ft. diameter
- Power—2 KW
- Range—100 to 200 miles

CANADIAN

Westinghouse Microscatter

60-A-745



MANUFACTURED

Designed and built to rigid services specifications.

TYPE T75.
Frequency Range: 85 to 1,000 megacycles.

TYPE T74.

Frequency Range: 20 to 250 megacycles.

Frequency calibration accuracy: .002% at 25° C. (or .01% between -20° C. to +70° C.).

Crystal-controlled, portable heterodyne-type Frequency Meters used for Field testing and measurement of pulsed, modulated, or C.W.R.F. transmitters, receivers and signal-generators.

Mains Operated Power Unit available as optional extra and designed

Reconditioned and calibration-checked B.C.221 Frequency Meters, range 125 Kc/s to 20 Mc/s, still available.

Provisional specifications on a new wide-range, very high accuracy Frequency Meter and also an instrument covering the range 100 Kc/s to 1,000 Mc/s (higher under favourable conditions) available on request.



INSTRUMENT

Complete Specifications on application to:-

Sole Manufacturers

TELEMECHANICS

(Instrument Division Dept. W.W.8)

TELEMAX WORKS, BROKENFORD LANE, TOTTON, HANTS, ENGLAND. Telephone: Totton, Southampton 3666 Cables: "Teleset," Totton, Southampton Agents: Some overseas territories still available.

If it's Electronic

and you want it Designed and Developed or produced * to your specification



Makers of High Voltage Test

Sets and other Electronic Equip-

ment for H.M. Government.

Compact Stabilised High Voltage Supply. Safe and reliable supply for photo-multiplier cells and cathode ray tubes. Variable output between 0-1250V D.C. at 250 micro amps. Size 6" × 4" × 3".

Consult

(formerly P.A.M. Ltd.)



R.F., E.H.T. Unit. A safe, D.C. high voltage unit specially designed to meet the need for a reliable source of supply for television C.R. tubes. Also satisfactory for flash testing where a D.C. supply is necessary.

Tyer & Co. Ltd. Electronics division combines the technique of several companies, long-established in the Electronic field, with the extensive modern production resources of Tyer & Co. Ltd. Examples of recent work are illustrated.

Whichever stage of the struggle you've reached, we can save you time and trouble—maybe money too—write or 'phone withous delay.



PERRAM WORKS, MERROW SIDING, GUILDFORD, SURREY Telephone Guildford 2211

member


of the

Southern

Areas

Electric

Corporation

 



AMERICANS

select

MARCONI TEST EQUIPMENT

MARCONI FM SIGNAL **GENERATOR**

TF 1066A

Sets the standard of ease and accuracy in bandwidth measurement. More than four hundred of this series of signal generator are in use in the U.S.A., and world sales exceed a thousand.



BRIEF SPECIFICATION

Frequency range: 10 to 470 Mc/s in five bands. Stability: 0.0025%. Stepped as well as continuously-variable incremental tuning. Internal modulation at I and Ske/s. Amplitude Mod: Use with Marconi TF 1102 for A.M. without spurious F.M. For full technical details send for Leaflet G186.

AMERICAN USERS INCLUDE:

A.E.C · AVCO MFG. CO · BELL TELEPHONE · BENDIX RADIO · COLLINS RADIO · COLORADO STATE PATROL CONVAIR · DOUGLAS AIRCRAFT · F.C.C · GENERAL ELECTRIC · GLENN L. MARTIN CO · HUGHES AIRCRAFT LOCKHEED AIRCRAFT CO. . M.I.T. . MOTOROLA PACKARD-BELL · PAGE COMMUNICATIONS · PHILCO RAMO-WOOLRIDGE · R.C.A · SANDIA CORP · SPERRY-PIEDMONT · STAMFORD UNIVERSITY · STROMBERG-CARLSON · TEXAS INSTRUMENTS · U.S. AIR FORCE U.S. ARMY · U.S. NAVY · WESTERN ELECTRIC

MARCONI INSTRUMENTS

MEASUREMENT THE INTERNATIONAL CHOICE FOR ELECTRONIC

AM & FM SIGNAL GENERATORS · AUDIO & VIDEO OSCILLATORS · FREQUENCY METERS · VOLTMETERS · POWER METERS · DISTORTION METERS TRANSMISSION MONITORS · DEVIATION METERS · OSCILLOSCOPES, SPECTRUM & RESPONSE ANALYSERS · Q METERS & BRIDGES

London and the South: English Electric House, Strand, London, W.C.2. Telephone: COVent Garden 1234. Midlands:

Marconi House, 24 The Parade, Leamington Spa. Telephone: 1408

North:

23/25 Station Square, Harrogate. Telephone:.67455.

Export Department: Marconi Instruments Ltd., St. Albans, Herts, England. Telephone; St. Albans 56161.

"SERVICE AFTER SALES"

words so easy to say . . . so easy to promise.

Recommendations are the mainstay of our business, hence the importance we attach to fully effective after-sales policy. We spend quite a deal of money on our Service Department, which is well equipped and staffed with skilled men who specialise in maintaining the high-grade Communications and Hi-Fi apparatus we sell. We know our apparatus

inside and out, and take pride in being one of the few dealers who not only repair but also instrument measure audio and radio performance to a maker's specification.

Our Service Department with its many instruments, benches and gadgets occupies a floor to itself, but does not operate as a separate entity. Instead it has constant liaison with our sales movements, and our Service Manager personally supervises customers'

installations.

WE MAY BE OLD FASHIONED . . .

in still believing THE CUSTOMER IS ALWAYS RIGHT, but to this end we give patient, painstaking attention to customers' troubles.



mised and fulfilled

14 Soho St., Oxford St., London, W.I.

Tel: GERrard 2089/7308. Shop Hours: 9-5.30 (Thurs. 7 p.m.) Saturdays: 9-1 p.m.

·M. R. SUPPLIES, LTD.

For over a quarter of a century have held the highest reputation for the best quality material at keenest possible prices. Prompt despatch—careful packing. Satisfaction assured.

FREQUENCY METERS (Crompton Parkinson). Calibrated 45 to 55 cycles per sec. 6in. dial, panel mounting. Brand new in maker's boxes, £10/15/s (despatch 3/6). STDD SWITCHES (Multhead Precision) 1 bank, single pole, 26 position. the ideal instrument switch. Brand new, 12/8 (despatch 1/-). BATTERY TESTING DUAL VOLTMETER, 3-0-3 volts D.C. and 30-0-30 volts D.C., 3 in. scale length, 12/8 (des. 1/-).

display work and many industrial purposes. Either speed, only 69/6 (despatch 27-).

MIMIATURE COOLING FANS (200/250 v. A.C.) with open type induction motor

3in. by 2½in. by 1½in. and 4in. 4-bladed metal impelter. Ideal for projector tamp
cooling and convector heaters, etc., 28/8 (despatch 2/-).

HIGH DUTY EECTIFIEES (8.T.C.) D.C. output 36 voits 15 amps, full-wave, 57/6
[des. 3/-). Also 240 voits 5 amps, 28/14/6 (des. 4/6).

SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS. 200/250 v. 50 c/s. Fitted with
spindles for hours, minutes and seconds hands. Self-starting, central bole fixing.

Dia. 2½in., depth behind dial only lin. Very latest model. With dust cover, 29/6
(despatch 1/6). Sets of three hands to fit, in good style for 5/7in. dial, 2/6 set, or
8/10in. dial, 3/6 set.

SYNCHRONOUS TIMER MOTORS (Sangamo). 200/250 v. 50 c/s Relf-starting. 2ln. dla. by 1 lin. deep. 1 r.p.m., 1 r.p.h. and 12 r.p.h.. any one 37/5 (des. 1/-). Also high torque model (G.E.C. 6 r.p.m., 57/6 (des. 1/-). These are suitable for display

SYNCHBONOUS TIME SWITCHES. (Sangamo) for accurate pre-set switching opera-tions on 200/250 v. 50 e/s. Providing up to 3 no-off operations per 24 hours at any chosen times, with day-omitting device (use optional). Capacity 20 amps Com-pacity housed 4in, dia., \$1m. deep. With full instructions. £5/8/6 (despatch 2/9), Also Smith's Relyon Twin-circuit model, 20-amp. switching £7/8/- (des. 2/6).

EXTRACTOR FANS. A very popular line. Well-made units at much lower than normal prices. 200/280 v. A.C. induction motor, ellent running, no interference. With mounting frame and back grille, ready for easy installation. With Sin. Impeller (10in. overall dia.), 200 C.F.M., 25/5/-. 10in. impeller (12in. overall). 240 C.F.M., 25/12/8. Also minor model, 6in. overall dia., 75 C.F.M., 24/12/8 (despetch any one 3/-).

COMPLETE SEWING MACHINE MOTOR OUTFITS. No better lob obtainable at any price. 200/250 v. A.C./D.C. Fitted latest radio/T.V. supressors. Comprising motor with fixing bracket, foot control and switch, needle light with switch, belt, etc., and instructions for easy fixing to ANY machine. The complete outfit still £8/15/- (despatch 3/-).

SYNOHERONOUS TIMERS (by well-known British maker—brand new). Good news for those who applied too late for first supply—s limited new delivery now available. 200/250 v. 50 c. Providing any "on "period between 5 mms. and 8 hours, switching "off" at the end of the set period. Made for electric cookers and suitable for many other purposes—tape recorders, mamerison heaters, etc. Capacity 25 amps., fitted neon indicator. Housing film sq. by 34m., £4/12/6 (destatch 2/*).

M. R. SUPPLIES, Ltd., 68 New Oxford Street, London, W.C.1 (Telephone: MUSeum 2958)

SUPREME AMONG SOLDERS

Grey & Marten make solders specifically for the Radio, Television and Electronic industries.

Amalgam 'Resinact' Cored Solder with specially activated resin flux, to specification DTD 599, and B.S.441.

Amalgam P.C. Alloys for diptinning printed circuits (free service for checking analyses of metal in customers' baths).

Amalgam Fusible Allovs made in all forms, for all uses. Fully approvedA.I.D., C.I.A., G.P.O., I.R.C.S.C. and M.O.S.




ESTABLISHED 1833

CITY LEAD WORKS, SOUTHWARK BRIDGE, S.E.I

Telephone: HOP 0414 Telegrams: Amalgam, Sedist, London and at Birmingham, Manchester and Ipswich

CAPACITORS

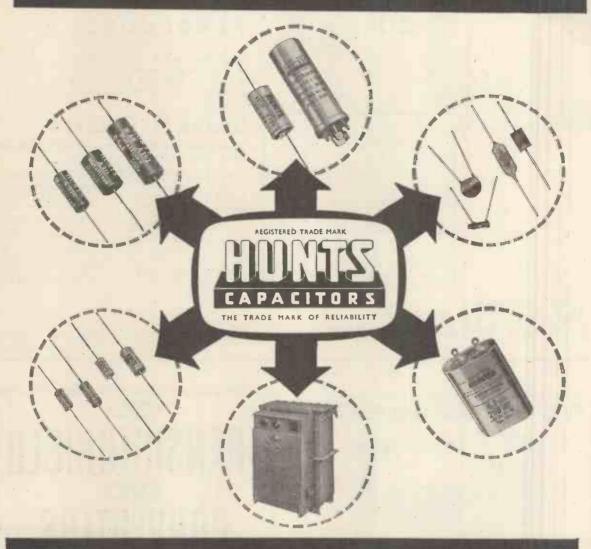

for all applications

TVDES

DRY ELECTROLYTIC · METALLISED PAPER (HUNTS PATENTS)

METALLISED PLASTIC FILM (HUNTS PATENTS)

PLASTIC FILM · FOIL & PAPER · SILVERED MICA

STACKED MICA · CERAMIC · POWER CERAMIC

TRANSMITTING AND SPECIAL R.F. TYPES

APPLICATIONS

RADIO AND TELEVISION EQUIPMENT · ELECTRONIC EQUIPMENT
POWER FACTOR IMPROVEMENT · CAPACITOR MOTORS
FLUORESCENT LIGHTING · PHASE SPLITTING
H.F. AND R.F. HEATING · IGNITION AND INTERFERENCE SUPPRESSION
TELEPHONE INSTALLATIONS

A. H. HUNT (Capacitors) LTD., WANDSWORTH, LONDON, S.W.18. Tel: VANdyke 6454

NEW from S. G. Brown



SUPER

HEADPHONES

"Super K" Headphones are the newest product of S. G. Brown Ltd., and are designed especially for High Fidelity Stereo requirements. They are attractive in appearance, extremely comfortable to wear and incorporate plastic head band and earpieces.

Spans 9 Octaves

These Frequency Response curves were produced under the following conditions:

BEAT FREQUENCY OSCILLATOR Type 1014 producing a signal of 2.5V. (modulated to 32 c/s with a swing of 30 c/s) to SUPER K EARPIECE, close coupled to ARTIFICIAL EAR Type 4109 with 6 c.c. coupler, measured signal being amplified by MICROPHONE AMPLIFIER Type 2603 and recorded on a Type 2304 LEVEL RECORDER Recorded Medium shows Response flat ±1 dB 20 c/s-6,000 c/s; 6 dB reduction to 12,000 c/s. With continued reduction to 20,000 c/s. Nine octaves pianoforte coverage from 24 c/s to 7,800 c/s.

Write for full information to:

LTD. SHAKESPEARE STREET

WATFORD

HERTS

Telephone: Watford 27241

EDDYSTONE COMMUNICATION RECEIVERS



Model 840A illustr. ted

HIRE PURCHASE TERMS

Cash Deposit 12 Monthly 24 Monthly Price £33 £55 No. Payments £2/6/8 Payments £1/5/4 870 £6/12/-£11/-/-£22/-/-£3/18/10 £7/17/8 840 888A £4/4/4

888A £110 £22/-/- £7/17/8 £4/4/4
680X £140 £28/-/- £10/-/8 £5/7/4
Carriage paid per passenger train.
The fabulous Model 880. Probably the world's most powerful production model receiver, 21 valves, complete coverage, 500 Kcs. to 30.5 Mcs. 30 ranges. Price-on application.
These sets are the choice of the discerning professional and amateur users. Descriptive literature gladly forwarded.



The Eddystone **Specialists**

SERVICES LTD

49/51 COUNTY ROAD, LIVERPOOL,

Telephone: AINTREE 1445

ESTAB. 1935



TRANSISTORISED

- High efficiency-over 80°
- One to 400 watts from 12 v. battery.
- 50 or 400 cycles output Small and compact

Existing or planned AC Mains equipment can be operated from low voltage input. In many cases Valradio Converters are small enough for immediate adaption into existing instruments.



Por full details contact: VALRADIO LIMITED ept. WW/C Browells Lane Feltha Tel: Feltham 4242

AIRMEC VOLTMETERS

This Valve Voltmeter is an accurate general purpose instrument suitable for measuring a.c. balanced, unbalanced and differential voltages, positive and negative d.c. voltages and resistances.

VALVE VOLTMETER TYPE 217



- Exceptional Stability obtained by balanced circuitry
- Very low input capacity
- Balanced, unbalanced or differential inputs
- A.C. Voltages from 0-150 volts in 5 ranges
- D.C. Voltages from 0-500 volts in 3 ranges
- Resistance measurement from 100 ohm
 —100 Megohm in 6 ranges
- Frequency Range 20 c/s-200 Mc/s
- Immediate Delivery

This instrument consists of a stable negative feed-back wide-band amplifier terminated in a rectifier circuit and indicating meter. The input is taken either to a high-impedance low-capacity probe or to a 75 ohm socket. A low impedance output is also provided to enable it to be used as an amplifier up to 20 Mc/s.

MILLIVOLTMETER TYPE 264

(Wide band Pre-amplifier)



- 300 UV-100 V in 8 ranges
- High-impedance low-capacity probe input
- Low impedance input—75 ohms
- Frequency range 20 c/s—10 Mc/s
- High Stability
- Accuracy ± 3% up to 3 Mc/s
- Can be used as an amplifier up to 20 Mc/s

Airmec

ELECTRICAL & ELECTRONIC INSTRUMENTATION

AIRMEC LIMITED . HIGH WYCOMBE

BUCKS.

Telephone: HIGH WYCOMBE 2501/7



The three types of WAVEFLEX Flexible Waveguides-

plumbing.

Twistable—flexible in E and H planes, and twistable about the longitudinal

problems of complicated waveguide

Non-twistable-flexible in E and H planes.

Premoulded Twisted-flexible in E and H planes, with a built-in longitudinal twist. Premoulding relieves the end connections of all twisting stresses, and the angle of twist can be much greater than with ordinary twistable

Manufactured under exacting scrutiny and tested to strict Government specifications.

Ideally suited for use in pressurised systems, remain stable when bent or twisted, unaffected by extremes of temperature.

Performance covers a broad band. 'Type approval' has been given by the Royal Radar Establishment and the Admiralty.

Waveflex guides are available in a range of lengths 3" to 36" fitted with standard flanges. Special lengths and flanges can be made to order. An additional range of short guides, under 6", are particularly useful as malalignment units and vibration decouplers.


Write for full technical details to:-

GABRIEL MANUFACTURING CO. LTD.

Newton Road, Torquay, Devon. Telephone: Kingskerswell 3333 A MEMBER OF THE TECALEMIT GROUP OF COMPANIES

WAVEFLEX FIFXIBLE AND TWISTABLE WAVEGUIDES

BROOKES (rystals

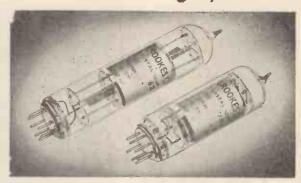

DEPENDABLE mean frequency control • Illustrated above

Left: Type G.2 Crystal Unit. Frequency 62 kc/s. Right:
Type G.1 Crystal
Unit. Frequency
100 kc/s.

ALL Brookes Crystals are made to exacting standards and close tolerances. They are available with a variety of bases and in a wide range of frequencies. There is a Brookes Crystal to suit your purpose-let us have your enquiry now.

BROOKES

Brookes Crystals Ltd

Suppliers to Ministry of Supply, Home Office, B.B.C., etc. LASSELL STREET, GREENWICH, S.E.10

Phone: Greenwich 1828 Grams: Xtals, London, S.E.10 Cables: Xtals, London

Mechanical Relay Latch

This latching device enables the P.O. 3300 type relay to be held in the closed position when the coil is de-energised and until manually released.

FOR

Does not impair the versatility of the ments, nor affect the position.

> WILL TRIP AND HOLD ON A.C. IMPULSE



EITHER TYPE CAN BE FITTED TO YOUR EXISTING 3000 TYPE RELAYS IN A MATTER OF MINUTES.

Please send for illustrated leaflet

RELAYS. UNISELECTORS KEY SWITCHES TO SPECIFICATION.





T.626

104

Arcolectric


SWITCHES & SIGNAL LAMPS

T.225: Miniature Slide Switch D.P. change-over switch

S.L.166: Very small low cost

T.280: Sensitive Snap Action Switch Popular switch for tape recorders T.626: Double pole 3-AMP switch

with tags to fit printed circuit boards

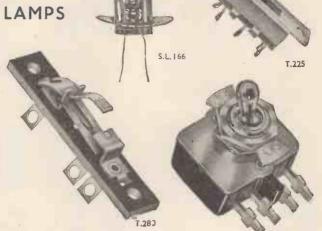

Write for Catalogue No. 132

ARCOLECTRIC

CENTRAL AVENUE, WEST MOLESEY, SURREY. TEL.: MOLESEY 3232

GILSON TRANSFORMERS

Provide a first-class service to manufacturers in prototype design and small or medium, scale production of transformers and chokes for use in electronic valve or transistor operated equipment for

AUTOMATION INSTRUMENTATION COMMUNICATIONS




OUR AUDIO
TRANSFORMERS
are used for RECORDING
and BROADCASTING F.M.
and TELEVISION
PROGRAMMES

Their use in receiving equipment will complete the chain to the satisfaction of the most discriminating listeners.

High Fidelity Enthusiasts please write for Set Makers' List.

R. F. GILSON LTD. 11a ST. GEORGE'S ROAD, WIM 5695

AUTOMATIC CABLE TESTER

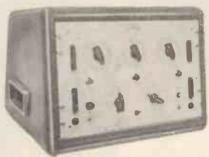


Multicore Cables and Harnesses such as are used extensively in aircraft, marine and similar installations can be easily checked for correctness of wiring and conductor resistance by means of the Automatic Cable Tester. With electrically operated special switches automatic checking of Multicore Cables up to 69 cores may be carried out at a rate much faster than is normally possible by manual means. Coupled to this is the absolute certainty that no conductor is accidentally left out of the test. "SELF TEST" means are included.

KENURE, HOLT ELECTRONICS LTD.
BOYN VALLEY ROAD, MAIDENHEAD
BERKSHIRE

Telephone Maidenhead 5331-2-3



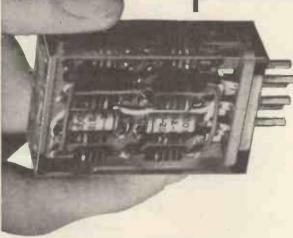



If your problem is the handling of information by means of digital techniques, Venner packaged circuits can help.

They combine the benefits of standardised production of well-tried circuit elements with plug-in flexibility of operation. Instruments built up from these circuits will drive reperforators, present an in-line display of 1" figures, or print at high speeds on paper tape. Development and test-set projects are simplified; control equipment can be quickly modified as need arises.

Now available from stock. Also from our Sales Counter at Venner House, Ebury Street, Victoria, London, S.W.I.

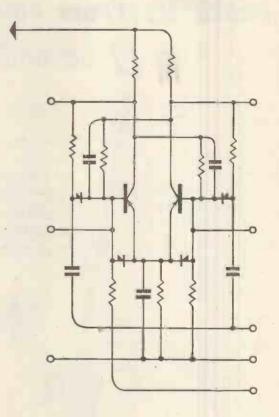For full details of our circuit blocks, send for a copy of leaflet VE 104.




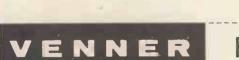

Venner Electronics Limited

Kingston By-Pass, New Malden, Surrey. MALden 2442

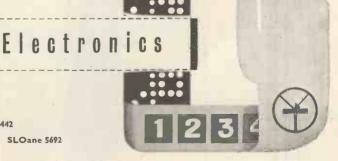London Office: Venner House, Ebury Street, S.W.I. SLOane 5692



The


Superspeed

heats up from cold in 6 seconds

Designed on an entirely new principle, this light-weight, versatile iron is eminently suitable for soldering operations in the radio, television, electronic and telecommunication industries. For test bench and maintenance work it is by far the most efficient and economical soldering iron ever designed.

Length, 10"; weight, 3½ ozs.

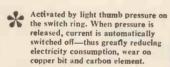For best results
with this iron
use ENTHOVEN
SUPERSPEED
CORED SOLDER
and ALUMINIUM
CORED SOLDER



Can be used on 2.5 to 6.3 volt supply (4 volt transformer normally supplied) or from a car battery.

More powerful than conventional 150-watt irons; equally suitable for light wiring work or heavy soldering on chassis.

Simple to operate; ideal for precision work.

Requires minimum maintenance—at negligible cost; shows lowest operating costs over a period.

LIST PRICES

IRON 39/6

TRANSFORMER 35/6

All prices and trade discounts subject to revision

ENTHOVEN SOLDERS LTD.


(Industrial Equipment Division)

Sales Office & Works:

Upper Ordnance Wharf, Rotherhithe Street, London, S.E.16. Tel.: BERmondsey 2014

Head Office:

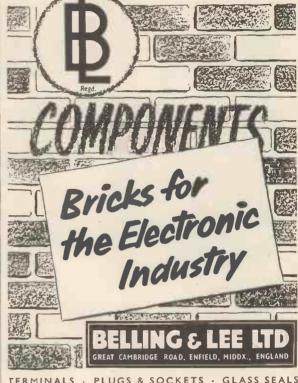Dominion Buildings, South Place, London, E.C.2. Tel.: MONarch 0391



TERMINALS . PLUGS & SOCKETS . GLASS SEALS CIRCUIT PROTECTION DEVICES

INTERFERENCE FILTERS . RECEIVING AERIALS

An essential book for research workers and designers

MICROWAVE DATA TABLES


A. E. Booth, M.I.R.E., Graduate I.E.E.

An accurate and labour-saving aid for computations involving basic microwave quantities which occur continually in design and development work on waveguides and similar transmission lines, such as decibel relationships, guide and free-space wavelengths, voltage standing-wave ratio, and voltage or power reflection coefficients. Contains 26 tables comprising over 23,000 separate computations. The figures in the tables have been computed on a Pegasus electronic digital computer to the limit of practical measuring accuracy.

27s 6d net by post 28s 8d 61 pp

from leading booksellers

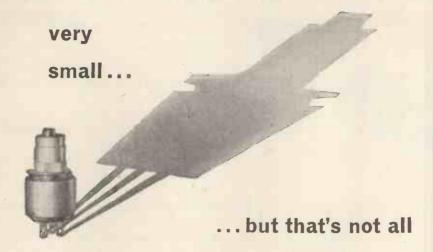Published for WIRELESS WORLD by
Iliffe & Sons Limited
DORSET HOUSE STAMFORD ST. LONDON S.E.I



This is the smallest 'spindle operated' moulded carbon track potentiometer in production. Although it measures only $\frac{1}{2}$ " diameter, it is rated at $\frac{1}{4}$ W and the range of values is from $1k\Omega$ to 2.5 M Ω . These factors will commend the Type L to all those design engineers who strive for greater miniaturisation in electronic equipment. Further constructional details and parameters are contained in Plessey Publication No. 313. Please write for a copy.

type L potentiometer

by Plessey

THE PLESSEY COMPANY LIMITED

CAPACITORS & RESISTORS DIVISION · SWINDON GROUP

Kembrey Street · Swindon · Wiltshire

Tel: Swindon 6211 · Telex: 44-355 · Telegrams: Plessey Telex Swindon


Overseas Sales Organisation

PLESSEY INTERNATIONAL LIMITED · Overseas Telegrams: Plessinter Telex Ilford Head Office; Ilford · Essex · England

Tel: Ilford 3040 · Telex: 23166 Plessey Ilford · Telegrams: Plessey Telex Ilford

WEYRAD P.50 TRANSISTOR COILS AND I.F. TRANSFORMERS

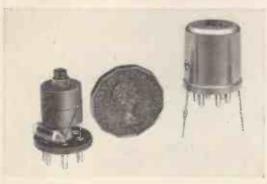FOR 2-WAVE PORTABLE WITH PRINTED CIRCUIT AND ROD AFRIAL



TOR E TORTE I ORTABLE THE	THE THE STATE OF T
	P50/IAC M.W. OSCILLATOR COILS. For I76pF TUNING CONDENSER PRICE 5'4d.
	P50/2CC 1st and 2nd 1.F. TRANSFORMER. 470 Kc/s. OPERATION. "Q" = 150 PRICE $5/7d$. (2 REQUIRED)
	P50/3CC 3rd I.F. TRANSFORMER. 470 Kc/s OPERATION. "Q" = 170
	RA2W L.W. and M.W. ROD AERIAL 6in. long, flying-lead connections. For 208pF TUNING CONDENSER PRICE 12/6d.
	LFTD2 DRIVER TRANSFORMER. Split Secondary Type, semi-shrouded. With 6 connecting tags' PRICE 9/6d.
PCAI PRINTED CIRCUIT PANEL, $2\frac{3}{4} \times 8\frac{1}{4}$ in. ready drilled on rear	with component positions and references printed PRICE 9'6d.
BOOKLET OF DETAILED ASSEMBLY INSTRUCTIONS	AND CIRCUIT DIAGRAMS FOR 6-TRANSISTOR

ALL IN BULK PRODUCTION—TRADE ENQUIRIES INVITED

WEYMOUTH RADIO MFG. CO. LTD., CRESCENT STREET WEYMOUTH, DORSET

MINIATURE ELECTRIC BULBS FROM 1V to 50V

IN SIZES FROM 4.5mm to 18mm DIAMETER

After nearly 30 years of specialising solely in the production of Miniature Electric Lamps, we have accumulated a store of information that is freely available to the Electronics Industry. You are invited to write or phone us for any information you may require about Miniature or Sub Miniature Filament Lamps for use in existing or new projects.

VITALITY BULBS LTD.

Neville Place, Wood Green, London, N.22.

'Phone: BOWes Park 0016

TRANSFORMERS

LARGE OR SMALL QUANTITIES

CHOKES TRADE ENQUIRIES WELCOMED

SPECIALISTS IN

FINE WIRE WINDINGS

MINIATURE TRANSFORMERS, PICK-UP, CLOCK AND INSTRUMENT COILS, ETC. VACUUM IMPREGNATION TO APPROVED STANDARDS

ELECTRO-WINDS


CONTRACTORS TO G.P.O., M.O.S., LE.B., ETC.

123-5-7 PARCHMORE ROAD, THORNTON HEATH. SURREY LIVINGSTONE 2261

EST. 1933

2'0d.

LOUDSPEAKER UNITS

 

Model 157 15" HD UNIT

Diameter over lugs 15½in.; overall depth 7¾in.;
Power handling 35 watts R.M.S.; Voice ooil
diameter 3in.; Flux density 12,000 gauss; Total
flux 310,000 lines; Main resouance 20-25.c.p.s.;
Frequency response 20-3,500 c.p.s.; Loput
impedance 15 ohms; Nett weight 17bs.

This 15in. unit is fitted with a curvilinear cone
foam plastic surround and an extra long voice
coil winding which permits large amplitude
movements without introduction of harmonic
distort on. The very large voice coil diameter
and special construct on result in a very large
power handling capacity and this unit may be
used for any heavy duty requirement such as
cinema or public address or as the bass unit in
a bigh fidelity multi-speaker system. It is
suitable for all types of refex enclosure horn
loading or open baffle mounting.

Price £18.

Model 301 H.F. UNIT

Overall dia. Sin.; Overall depth 12in.; Power handling 15 watts; Instantaneous Peak; Voice coil dia. 2in.; Flux d nsity 17,000 gauss; Frequency response 1,500-18,000 c.p.s.; Input impedance 8-15 ohms.

pedance 8-15 ohms.

A pressure type high frequency loudspeaker.

Randles high note portion of 15 watts of music.

Response is level over rauge 2,000 to 14,000 c.p.s. beyond which there is gradual roll-off giving useful range of 1,500 to 18,000 c.p.s.

The special hardened altuminum diaphragm with unique loading system gives clean distortionless output at all frequencies in its rature which is completely free of resonances or colorations. Will extend range of any existing speaker system and greatly increase transient response and "realism." £3/15/-


and greatly increase "realism." £3/15/-.



Not subject to Purchase Tax (Carriage paid in U.K.).
Illustrated leaflet available

FANE ACOUSTICS LIMITED

BATLEY YORKSHIRE

 



miniature soldering iron


for mains or low voltage operation

FINGERTIP CONTROL

with sharp, controlled heat for transistor and other small assemblies. Location of element under soldering tip produces 30 watt capacity for only 15 watts consumption.

Available for 230/240v.
220, 200, 100 and low voltages 6, 12, 24, 28, 50v.

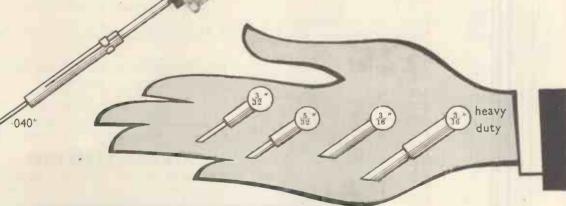List prices range from 25/- to 29/6 (subject)



INTERCHANGEABILITY

The 5 sizes of bits shown can be easily changed by sliding on and off the shaft. Heavily plated, split right through to facilitate changing, special hard wearing alloy.

send for detailed catalogue to

A-N-T-E-X

LIST OF WHOLESALE STOCKISTS SENT UPON REQUEST


LIMITED 7-8 IDOL LANE, LONDON EC3

Telephone: MANsion House 2716.



INTERNATIONAL T.R. SERIES WHICH ARE ALREADY BEING USED IN VAST QUANTITIES IN AMERICA AND OTHER COUNTRIES

I-E-R-C DISSIPATING VALVE SHIELDS

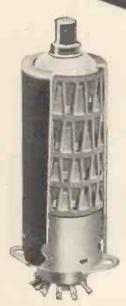

- International T.R. Series Shields reduce bare-bulb temperatures by 15% to 25%.
- International T.R. Series Shields eliminate vibration.
- International T.R. Series Shields fit standard sockets.
- International T.R. Series Shields are available in various sizes.



Full Technical information is available on request.

Joint service numbers have been allocated.



ARRARD

Special Products Division. 23, Westminster Palace Gdns., Artillery Row, London, S.W.1

ENGINEERING AND MANUFACTURING CO. LTD.



Remember-Radiospares components are delivered absolutely "by return"

Send us your enquiries for all types of

OUARTZ CRYSTALS

RADIO FREQUENCY CONTROL FILTER PURPOSES ULTRASONIC PURPOSES

METALLIZED TO SUIT REQUIREMENTS ANY SHAPE AND SIZE CUT TO SPECIFICATION

PIEZO LIMITED

26 St. Albans Rd., Watford, Herts. Tel: Watford 27808



CHERRY ORCHARD RD, EAST CROYDON, SURREY TELEPHONE: CROYDON 3379/6390

TOP RELIABILITY


A narrow-band FM radiotelephone equipment for the 450 - 470 Mc/s band with 50 kc/s channel spacing

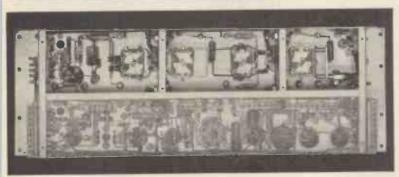Designed and tested to the exacting specifications of an important oil company for unattended operation during extended periods and under adverse climatic conditions









STORNO CQF 63

Full tropicalization

24 teleprinter or telecontrol channels

Receiver sensitivity 0.5µV, noise figure

8 dB

Frequency stability better than ± 5 x 10-6

Attenuation of undesired frequencies better

than 80 dB

Modular construction

For 19" rack mounting

Ideal for

Data transmission
Telemetering
Telecontrol
Teleprinter links
Radio link to isolated telephone
subscribers et cetera.

series built and for quick delivery

A product from STORNO of COPENHAGEN, Ved Amagerbanen 21, Copenhagen, Denmark

Enquiries also to: STORNO-SOUTHERN LIMITED, Frimley Road, Camberley, Surrey

Storno

WE SEND THE BEST OF BRITAIN'S HI-FI EVERYWHER

	PROMPT	DESPATCH	SERVICE
•		D EXPORT E	

243	 PROMPT DESPAT 	CH	SER	VICE
F	 HOME AND EXPOR 	T E	MOLLI	RIES
2				IXIEO
	WELCOME AT ALL		ES	
	• 110 VOLT ITEMS A	VAIL	ABL	E.
ಚ				
-	* RECORDERS	402 I	2 0	\$267
	Vortexion W.V.B.			\$315
E	Brenell Mk. V	64 gi	15.	\$192
0	Brenell 3 Star Stereo	89 gi		\$267
L	Clarion Transistor	25 g		\$75
	Cossor [60] 4 Tr	37 gi	15.	\$111
	Cossor 1602 4 Tr. 3 spd	59 gi	15.	\$127
	Simon Minstrelle	39 gi	ns.	\$117
ó	Ferrograph 4AN	81 gr		\$243
	Ferrograph 4AH	86 gi		\$258
A	Ferrograph 808 Stereo	. 105 g		\$315
5.	Grundig TK60 Stereo	128 gr		\$384 \$276
2	Grundig TK55 Stereo	92 gi		\$156
	Grundig TK20 with Mic Grundig TK24	52 gr		\$186
	Grundig TK30	72 gr		\$216
品	Philips 4 Track	59 gi		\$117
وبالنا	Philips 4 Track Stereo	92 gi		\$276
	Philips 4 Track	34 gi		\$102
NG	Reflectograph 'A ' Tr	95 0		\$285
	Reflectograph 'B' 4 Tr	105 gr		\$315
	Stuzzi Magnette	69 gi	15.	\$207
	Stuzzi Tri-corder	75 gi	18.	\$225
YTH	+ DECKE			
	★ DECKS Wearite 4A	£36 19	0 0	\$105
	Wearite 4B			\$119
KE	Brenell Mk. V			\$84
-11	Brenell Stereo Deck			SIDI
	Brenell Pre-Amp. and Amp.			\$69

crophon non Sou			raphone, Re	slo, Acos,
TAPES	BY	ALL	LEADING	MAKERS

* SPEAKER SYSTEMS				
Quad Electrostatic	£52	0	0	\$149
Wharfedale SFB/3	£39	10	0	\$113
Wharfedale Coaxial 12	£25	0	0	\$156
Wharfedale Golden 10	£8	14	11	\$18
Tannoy 12in. Monitor	£30	15	0	
Tannoy 15in. Monitor	£37	10	0	
WB. 1016	£7	12	3	\$16
Goodmans AL.120	£29	10	0	\$84
Goodmans AL.100	£23	10	0	\$67
Goodmans Triaxiom	£25	0	0	\$72
Goodmans 300	EII	5.	9	\$32
Goodmans 400	£16	17	0	\$46
Kelly Ribbon Mk. II	610	10	0	\$30
B. J. Tweeter complete	£5	5	0	\$11
* MOTORS AND PICK	UP:	S		

* MOTORS AND PICK	-UP	s		
Decca Stereo P.U		0	0	
Lenco GL60 Trans. Unit	£28	19	2	
Lenco GL58/R, Stereo P.U.	£29	3	10	
Garrard 301		7	3	
Garrard 4HF/Stereo P.U		17		
Garrard TA/Mk. II				
Connoisseur Motor Type 'B'				
Connoisseur, 2 sp. Motor		3		
Goldring 700		14		
Ronette DC284	£4	3	5	

	_	-	
* AMPLIFIERS & TUNERS			
Out 32 Consulting		^	
Quad 22-Control Unit £25	. 0	0	
Quad II Amplifier£22	10	0	
Leak Stereo 20 Amp £30	9	0	
Leak Point One Pre-Amp £21	0	0	

į	Rogers Junior Stereo	£28	10	0	\$81
	Rogers Master Stereo Unit	£35		0	\$100
	Quad FM Tuner	£28	17	6	\$60
	Chapman AM/FM	£29	8	0	\$60
		e			2

Enquiries for all items by firms mentioned in this advertisement invited.

BINSON "ECHOREC"

Bistributed exclusively by Modern Electrics
Ltd. (see W.W. Feb. page 92). For superimposing controlled echo on to any audio
signal. Compact, fully portable instrument,
with three working channels, echo interval is
variable, swell and other effects are
obtainable.

ABRIDGED DESCRIPTION

Three inputs and outputs.

Push-button channel selection for 1, 2
or 3 channels.

Push-button channel selection for 1, 2 or 3 channels.
Controls for echo intervals, volume of echo, swell effect, volume level on input channels, etc.
Complete with fitted carrying case, leads, plugs. A.C. mains.

Professional Discounts 140 gns. \$420 Leadet on request.

BINSON "BABY ECHOREC"
Similar to above but for single channel working 80 gns.

ATTENTION! Ecrivez nous en français S.V.P. Schreiben Sie uns bitte auf Deutsch. ATTENTION!
Ecrivez nous en français S.V.P.
Schreiben Sle uns bitte auf Deuts
Escrivanos en español por favor.

MODERN ELECTRICS, (RETAIL)

We carry extensive up-to-date stocks of equipment, components and accessories by Britain's leading makers. Enquiries dealt with by return

164 CHARING CROSS ROAD, LONDON, W.C.2

(3 shops from Tottenham Court Road Station Underground) Tel.: TEM 7587 & COV 1703 Cables: MODCHAREX, LONDON

SOLENOID TYPE



Continuous 3 ozs, at 1" Instantaneous to 2lbs. Larger sizes available.

Also-Transformers to 7kVA 3 phase.

18 FOREST ROAD, KINGSWOOD, BRISTOL

STABILIZE YOUR AC MAINS with the finest equipment, at a fraction of the normal cost:-

FERRANTI 71-KVA MOVING COIL AUTOMATIC VOLTAGE REGULATORS

Any stabilized output voltage in the range 200-250 v, can be selected by plug-board tappings. The selected output voltage is automatically maintained constant within $\pm \frac{1}{2}\%$, at all loads 0 to $30/37\frac{1}{2}$ amps., when the supply voltage is varying over the range +8% to -12%

Frequency compensated 45-55 and 54-66 c/s.

Excellent output wave-form.

\$54

\$22

536

Can also be used as a variable transformer. Unused. Complete with spares and instruction

P. B. CRAWSHAY

94 Pixmore Way, Letchworth, Herts. 'Phone 1851



For Safety's Sake use AVO Prodclips

Safety first every time with these patented springloaded AVO Prodelips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.


Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Post Free 15/- per pair



AVOCET HOUSE . 92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.

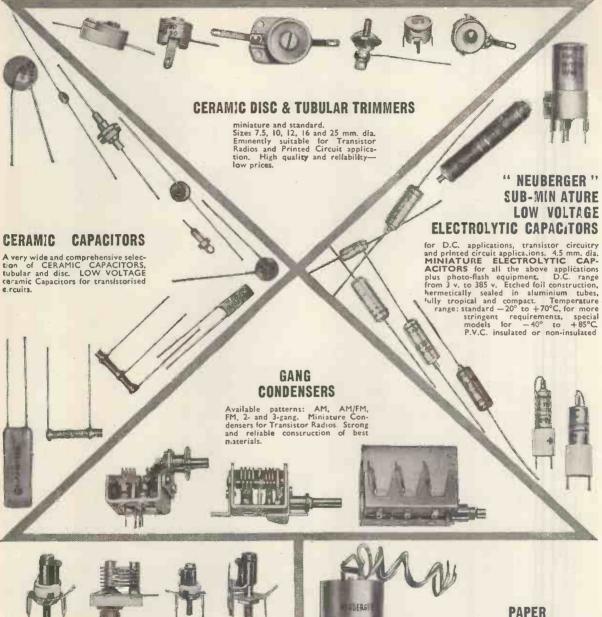VICtoria 3404 (12 lines) A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES



SPECIAL TRIMMERS

Tubular-screw adjustment, mica dielectric. Wide capacitance sweep, e.g. 2/20 pF, 3/30 pF, 3/40 pF, 3/50 pF, AIR TRIMMER 2/20 pF mounted on ceramic base.

CAPACITORS

hermetically sealed in aluminium tubes. CAPACITORS for discharge lighting applications. CAPACITORS for Motor Starting. BOTH TYPES ARE SUITABLE FOR OPERATING IN TEMPERATURES OF UP TO +90°C WITH PEAK OF +100°C.


STEATITE INSULATIONS LTD

HIT AS

31, GEORGE STREET, LOZELLS, BIRMINGHAM, 19

Telephone: NORthern 8357/8

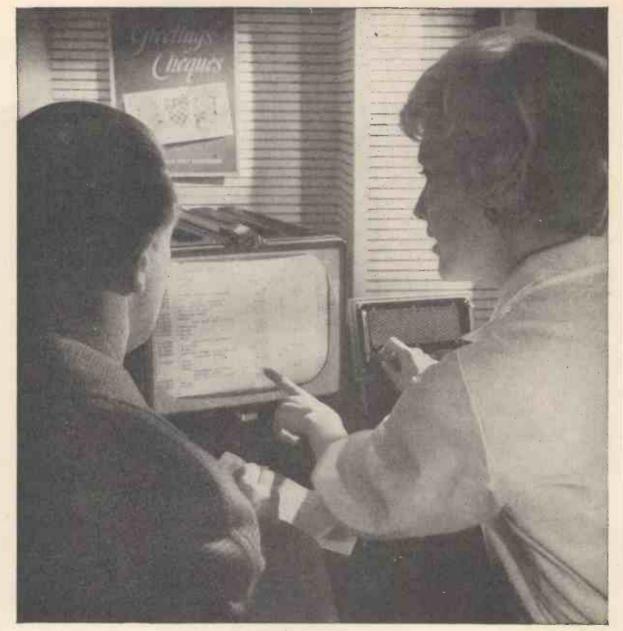Telegraphic Address: "Steatite-Birmingham, 19"



Westminster Bank uses Pye Television



The Pye Industrial TV Division, a member of the Pye Instrument Group, has supplied all the television equipment to the Westminster Bank for the first inter-branch TV network. The new system which makes centralised book-keeping possible has been brought about by the closest co-operation with the GPO who have supplied Post Office lines to carry the signals. The illustration shows a customer checking his banking account.

The Pye Instrument Group consists of: Pye Atomics Division, Pye Industrial Television Division, Faraday Electronic Instruments Ltd., Labgear Ltd., W. G. Pye & Co. Ltd., Pye Telecommunications Ltd., Unicam Instruments Ltd., W. Bryan Savage Ltd., W. Watson & Sons Ltd.

Wireless World

ELECTRONICS, RADIO, TELEVISION

DECEMBER 1960

Managing Editor: 579 Editorial Comment 580 Practical Aerial Measurements HUGH S. POCOCK, M.I.E.E. By F. C. Judd 585 100-kc/s Crystal Marker By F. G. Rayer Editor: 587 Amateurs' National Convention 588 Interkama 1960 F. L. DEVEREUX, B.Sc. 590 World of Wireless 592 Personalities Assistant Editor: 594 News from Industry 595 Ceramic Permanent Magnets By 7. W. Bunn and 7. H. W. BARNARD Harrison By F. R. B. Jones 599 Nodal Analysis—2 605 Camera Remote Control By G. W. H. Larkby 607 Short-wave Conditions 608 Letters to the Editor 613 Technical Notebook 615 Manufacturers' Products 617 Principles of Digital Computers—2 By D. S. Wilde 622 High-power Loudspeaker System By Michael Lorant VOLUME 66 No 12. 623 Valve Noise By " Cathode Ray" 627 Elements of Electronic Circuits-20 By J. M. Peters PRICE: TWO SHILLINGS 629 December Meetings By " Diallist " 630 Random Radiations FIFTIETH YEAR By " Free Grid" 632 Unbiased OF PUBLICATION

Offices: Dorset House, Stamford Street, London, S.E.1

Please address to Editor, Advertisement Manager,
or Publisher, as appropriate

© Hiffe & Sons Ltd. 1960. Permission in writing from the Editor must first be obtained before letterpress or illustrations are reproduced from this journal. Brief abstracts or comments are allowed provided acknowledgment to the journal is given.

PUBLISHED MONTHLY (4th Monday of preceding month) by ILIFFE & SONS, LTD., Dorset House, Stamford Street, London, S.E.1.


Telephone: Waterloo 3333 (65 lines). Telegrams: "Ethaworld, Sedist, London." Annual Subscriptions. Home and Overseas, £1 15s. 0d.

Canada and U.S.A., \$5.00. Second-class mail privileges authorised at New York, N.Y. BRANCH OFFICES: BIRMINGHAM: King

Edward House, New Street, 2. Telephone: Midland 7191. COVENTRY: 8-10, Corporation Street. Telephone: Coventry 25210. GLASGOW:
62, Buchanan Street, C.1. Telephone: Central 1265-6. MANCHESTER: 260, Deansgate, 3. Telephone: Blackfrlars 4412. NEW YORK

OFFICE: U.S.A.: 111, Broadway, 6. Telephone: Digby 9-1197.

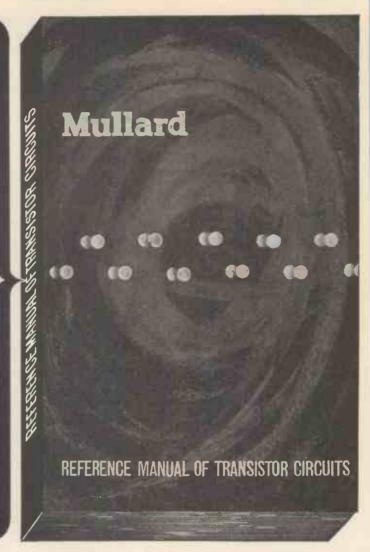over 30 new circuits are in the Mullard REFERENCE MANUAL OF TRANSISTOR CIRCUITS



This new manual of transistor circuitry has been prepared by Mullard engineers, as an up-to-date and readable volume which will be of use and interest to technicians, service engineers, junior designers and electronics students.

It has a page size of $8\frac{1}{2}$ ¹¹ x $5\frac{1}{2}$ ¹¹ and describes more than 60 circuits—over 30 are made generally available for the first time—including both domestic and industrial applications.

308 PAGES · 241 DIAGRAMS · U.K. PRICE 12s. 6d.

PUBLISHED BY MULLARD LTD.

Get your copy of the Mullard "Reference Manual of Transistor Circuits" today from your radio dealer, or order direct from Mullard Ltd. (postage and packing 1s. Od. extra in U.K.).

MULLARD LIMITED . MULLARD HOUSE . TORRINGTON PLACE . LONDON . W.C.1.

Overseas readers should enquire of their local Mullard Agents.

THE MARK IV CAMERA CHAIN

EXPERIENCE COUNTS

Marconi's pioneered the use of the 41 inch Image Orthicon Camera using the tube developed by their associates, the English Electric Valve Company. Marconi's have amassed more 'know-how' on the use of the 4½ inch Image Orthicon than any other manufacturer.

OVER 500 MARCONI IMAGE ORTHICON CAMERA CHAINS

HAVE BEEN SOLD THROUGHOUT THE WORLD

MARCONI

COMPLETE SOUND AND TELEVISION SYSTEMS

BD 863 MARK IV IMAGE ORTHICON CAMERA

EXTREME STABILITY


Novel circuit design and careful choice of components give such a high degree of stability that operational controls have been removed from the camera.

FIRST CLASS PICTURE QUALITY

The 41 inch Image Orthicon tube gives a picture quality substantially better than any other type or size.

LIGHT AND COMPACT

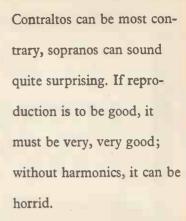By reducing and simplifying the camera electronics its weight has been held below 100 lb. and its size made correspondingly small.



At the heart of sound reproduction lies the pick-up; for the most exacting ear,
Acos have evolved what is undoubtedly one of the finest mono and stereo pick-up arms in the world: the Acos Hi-Light.

HARMONIGS HARMONIGS

ON THE ACOS HI-LIGHT

The new Acos Hi-Light pick-up achieves the most superb sound reproduction of the day. The frequency range is from 20-20,000 c/s ± 3 dB. Tracking weight is less than 1 gramme on mono, 2 grammes on stereo, which virtually eliminates record wear. U.K. Retail Price 18 gns. including mono and stereo heads and P.T.





ARE DOING THINGS IN STYL

"BELLING-LEE" NOTES No. 23 of a Series Fusing, part 7

A convenient way of expressing the degree of protection afforded by a fuse is by stating the "Fusing Factor"; this is the ratio of the minimum value of current which will blow it to the current rating. Thus a 2 amp, fuse having a fusing factor of 2:1 will not operate normally at any current below 4 amp., although it should be appreciated that if it is subjected to currents between 2 and 4 amp, there will be an excessive temperature rise (possibly beyond what is permitted) and, depending on the material of which its element is made, embrittlement may result, followed ultimately by failure as we have seen earlier.


Now fuselinks having different types of construction and performance can have similar fusing factors, and so, useful as this characteristic is, it gives no indication of the mode of operation, which is a function of current and time. The readiest way of expressing this is pictorially, in the form of graph. In its conventional form, this is a curve

current (r.m.s. value) would give the same result as D.C.

A typical set of characteristic curves is shown for four different types of fuses having the same rating and fusing factor. The usefulness of these curves can be considerably extended by plotting them as envelopes containing the spread of results obtained in practice due to random variations between different specimens, as we indicated in part 3 of this series. The upper boundary then provides information on the absolute protection given by that particular type of fuse, while the lower boundary defines the maximum isolated surge that the fuse will withstand.

Curves of this type are indispensable when considering problems of discrimination. In any system which includes two or more circuit protection devices arranged in series, it is obviously undesirable that a fault should operate more than one of them. For instance, in an ordinary domestic electrical installation there are a number of individually fused outlets (sub-circuits) fed through a main circuit fuse, and it would be most inconvenient if a fault arising in one of the sub-circuits blew the

COMPARISON OF FUSE CHARACTERISTICS

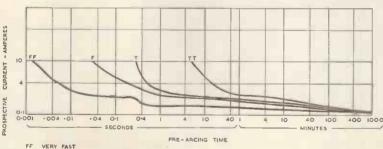

FAST

TIME LAG


TT EXTRA TIME LAG

drawn through a minimum of six points plotted on Cartesian coordinates whose axes are prospective current, and pre-arcing time, shown on logarithmic scales. The current source which is used to obtain the results so plotted is usually D.C., since an alternating supply would give misleading results at very short pre-arcing times because they would depend on the instantaneous value of the current at the time of applying the overload; at fairly long prearcing times, of course an alternating

main fuse thus putting all the other sub-circuits out of action; in some situations it could even be dangerous. The characteristics of the main fuse must therefore be such that it is able to discriminate between main circuit fault and an overload in a sub-circuit and the simplest way of ensuring this is by seeing that its performance curve nowhere intercepts those of the sub-circuit fuses.

Advertisement of BELLING & LEE LTD. Great Cambridge Road, Enfield, Middx

"Belling-Lee"

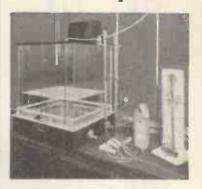

TECHNICAL KNOW-HOW

To any manufacturer of electronic components electro-plating is one of the fundamental techniques for it governs the efficient life of most contact surfaces, as well as overall "Belling-Lee" have appearance. always taken a special pride in the quality of their electro-plated finishes, and the Sulphur Dioxide Corrosion Test, which is carried out by means of the apparatus illustrated, is the latest procedure used in our type testing laboratories for monitoring these essential standards. The process is used for detecting undesirable discontinuities in plated surfaces (not silver). Briefly, it consists in exposing the articles to be tested to a dilute concentration (2%) of sulphur dioxide in moist air (95% relative humidity) at a controlled temperature (25°C.) for a specified period of anything up to 24 hours. The specimens are then allowed to dry without wiping, and examined for any corrosion products of the sub-surface; these will only have been formed if the surface has any holes or cracks in it.

The method is also useful for testing for discontinuities in joints, e.g. crimped joints, in conjunction with continuity resistance measurements made before and after exposure. It is complementary to normal salt spray tests, and somewhat easier to evaluate.

> Most "Belling-Lee" products are covered by patents or registered designs or applications.



Telephone: Enfield 5393 . Telegrams: Radiobel, Enfield



EMI. GOLOUR T.V.



Colour TV makes its first appearance on any European race-course, and 3,000 people in special marquees at Redcar see two days' racing in brilliant, accurate colour...

An operation takes place in Hammersmith Hospital, and a large audience many miles away sees every detail faithfully reproduced in colour...

Just two examples from the ever-growing list of successful uses of E.M.I.'s Colour Camera Channel Type 204. Smaller, easier to use and less expensive than existing equipment, E.M.I.'s Colour Channel uses a novel optical system and three vidicon tubes to provide extremely faithful

rendering of colour, even under difficult lighting conditions. E.M.I.—holders of original patents for the world's first high-definition TV system—has already demonstrated the suitability of this new Channel for many applications in industry, medicine and science.



A demonstration will gladly be arranged for you. Write or telephone:

E.M.I. ELECTRONICS LIMITED

BROADCAST EQUIPMENT DIVISION, HAYES, MIDDLESEX TELEPHONE: SOUTHALL 2468, EXT. 2011

Aspects of design


This is No. 29 in the series of articles dealing with advanced problems in circuit design published by The Ediswan Mazda Applications Laboratory. No. 30 will appear next month. We shall be pleased to answer queries arising from this or other articles. Reprints of the first twenty-four articles, in booklet form, are available on request.

29
TUNING OF
TELEVISION
LINE OUTPUT
TRANSFORMERS

The operation of line deflection output stages of television receivers was dealt with in "Aspects of Design" numbers 8 and 26. It was pointed out in "Aspects of Design" number 26 that an output stage can be operated more efficiently if the ratio of the number of turns on the efficiency diode winding of the transformer to the number of turns on the pentode winding is kept as high as possible. This results in a high value of boosted HT voltage which, although assisting in producing good efficiency, subjects the pentode and efficiency diode to higher peak voltages during the line flyback interval. The Maximum Peak Voltage ratings of diode and pentode often set a limit to which this course can be pursued. By suitable proportioning of transformer leakage inductance and self-capacitance a condition of tuning can be achieved which allows these peak voltages to be considerably reduced. This process is often termed 3rd Harmonic Tuning.

This technique can best be understood by considering the equivalent circuit of a line output stage.

Fig. 1 shows the equivalent circuit of a typical line output stage in which a winding or "overwind" is included to step up the peak voltages during flyback for the purpose of generating the cathode ray tube extra high voltage supply. The various elements of the circuit are shown as referred to the primary of the transformer. L₁ represents the parallel combination of deflector coil load inductance and primary inductance. L₂ represents the leakage inductance between pentode anode connection and EHT rectifier connection

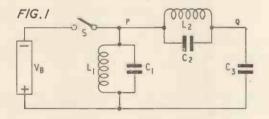

 C_2 and C_3 are the small capacitances associated with this inductance. C_1 which is large provides most of the tuning of the inductance load. The switch represents the combination of pentode and efficiency diode. At the end of the deflection stroke L_1 carries a high current which is rising linearly at a rate slow compared with the natural resonance periods of the circuit. The switch is opened and the circuit commences a free oscillation. At the end of the flyback interval the current in L_1 has reversed and has reached a maximum in the opposite direction. Very shortly after this time there comes a moment when the rate of change of current in L_1 and therefore the voltage across C_1 have the same value as they had during the previous deflection stroke. The switch is now closed once more and this current is constrained to collapse linearly to zero at a rate L_1 $\frac{d_1}{dt} = V_B$.


This linearly decaying current flows into the battery returning energy in doing so.

If there is current in L_2 or charge on C_2 at the moment of closing the switch the circuit L_2 C_2 C_3 will continue to oscillate during the next stroke. In any practical circuit the switch comprising the pentode and efficiency diode has finite resistance which serves to couple oscillations of L_2 C_2 C_3 into the load inductance L_1 where they produce velocity modulation of the trace. In addition the energy of this circuit L_2 C_2 C_3 will be dissipated in its losses and will not be available for recovery by the energy recovery process. The aim of third harmonic tuning is that at the end of the flyback interval there shall be no current in L_2 and no charge on C_2 . This implies that at the end of the flyback interval the current in L_2 is zero and the rate of change of current is also zero. During the free flyback oscillation L_2 can be supposed to carry components of current at the two natural frequencies of the circuit. These frequencies are f_1 , a low frequency mainly governed by L_1 C_1 and f_2 a higher frequency governed mainly by L_2 in parallel with C_2 and C_3 , C_1 appearing as a very low impedance.

Fig. 2(a) shows a plot against time of these two components of current in L_2 during the flyback interval with the circuit constants critically adjusted for the "3rd Harmonic" tuning condition. This occurs when f_2 is slightly less than $3\,f_1$. The total current in L_2 is the sum of these components and this is shown in Fig. 2(b). It is seen that this condition achieves the requirement of current in L_2 and rate of change of current being simultaneously zero at the beginning and end of the flyback interval. The voltage waveform across L_2 is shown by the dotted curve in Fig. 2(b) (voltage of point P with respect to point Q). The effect of this is to depress the voltage peak at P, the pentode anode, and increase the voltage peak at Q, the EHT rectifier point.

These waveforms are shown in Fig. 3. (a) The waveform at Q, of course, is of greater amplitude than that at P by the step up action of the transformer ratio which, for simplicity, has been omitted from the equivalent circuit. (b) $t = t_R > \frac{1}{2 t_1}$

FIG. 2 815 EXAGGERATED GIVING \$2=263 fg

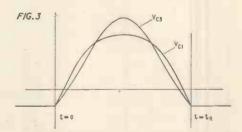

In practice L₂ C₂ and C₃ are governed by the transformer winding configuration and only C₁ is under control by adding capacity across the transformer primary. The procedure in design is to adjust C₁ for the tuning condition by observing cancellation of ringing on say the pentode anode waveform and then measuring flyback time. If, for instance, flyback time is too short then the winding must be redesigned for greater leakage inductance L₂ or greater self capacitance of the EHT overwind to reduce f₂ and the transformer re-tuned for the "3rd Harmonic" condition.

The Ediswan Mazda 30P4 and 30P19 are processed to have good high voltage performance to give the engineer scope for achieving very efficient designs using this procedure.

Associated Electrical Industries Ltd

Radio and Electronic Components Division Technical Service Department 155 Charing Cross Road, London, W.C.2 Tel: GERrard 8660. Grams: Sieswan, Westcent, London

BEAM TETRODE POWER TRIODE NEW HIGH

EDISWAN MAZDA 30PL14

The 30PL14 Triode Beam Tetrode is intended principally for use in frame deflection circuits of television receivers using 110° and 114° cathode ray tubes. The tetrode section has been designed to operate with a low ratio of screen to anode current whilst the available peak anode current and anode dissipation are higher than in the 30PL13. The higher available peak anode current will, in many cases permit economies in output transformer design. The triode section is a general purpose triode with identical characteristics to the 6/30L2, and that of the 30PL13, for use as a deflection drive voltage oscillator, frame sync. pulse separator etc.

Heater Current		I _h	0.3
Heater Voltage		V _h	16
Ticater voitage	(ADIT2)	v <u>n</u>	10

TENTATIVE RATINGS AND DATA

Maximum Design Centre Ratings	
Triode Tetr	ode
Anode Dissipation (watts) pa(max) 1	3
Screen Dissipation (watts) pg2(max) —	2
	2*
	0.5*
Anode Voltage (volts) Va(max) 250 250	0
Screen Voltage (volts) $V_{g2(max)}$ — 25	0
Heater to Cathode	
Voltage (volts rms) V _{h-k(max)rms} 150† 15	0+
Mean Cathode Current (mA) Ik(max) - 7	
Resistance Grid 1 to Cathode	
Self Bias (M Ω)	2
Fixed Bias (M Ω)	1

^{*}Maximum pulse duration 5% of one cycle with a maximum of 1 msec

†Measured with respect to the higher potential heater pin.

TRIODE CHARACTERISTICS

Anode Voltage (volts)	V_{a}		200
Anode Current (mA)	Ia		10
Grid Voltage (volts)	V_{g1}		-7.7
Mutual Conductance (mA/V)	gm		3.4
Amplification Factor	L	**********	18



TETRODE OPERATION IN FRAME TIME BASE


Allowance must be made in circuit design, not only for com-ponent variation, but for valve spread and deterioration during life. Values of total tetrode peak anode current, for an average valve when new and at the assumed end of life point for any valve, are as follows:-


	V _a	V_{g2}	V_{z1}	I a
	(V)	(V)	(V)	(mA)
Average New Valve	55	170	<u>- 1</u>	210
Assumed End of Life Conditi	on 50	170	1	135
Average New Valve	55	185	 1	235
Assumed End of Life Condition	on 50	185	-1	151


Mounting Position: Unrestricted

Base: B9A (Noval)

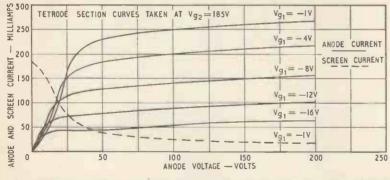
Tentative Characteristic Curves of Ediswan Mazda Transistors Type 30PL14



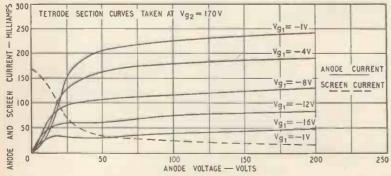

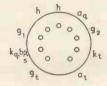

VIEW OF FREE END

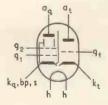

Maximum Dimensions (mm)

78.5
71.5
22.2

Associated Electrical Industries Ltd

Radio and Electronic Components Division Technical Service Department 155 Charing Cross Road, London, W.C.2 Tel: GERrard 8660. Grams: Sieswan, Westcent, London





RADIO · TELEVISION · ELECTRONICS

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics; etc.

FOR ... Your Career ... Your Own Business ... An Absorbing Hobby ...

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis.

You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning! Fill in the coupon below, for full particulars:—

RADIOSTRUCTOR LEADS THE WORLD IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G66), READING, BERKS.

Please send brochure, without obligation, to:-

* Name

Address

* BLOCK CAPITALS PLEASE

(We do not employ representatives)

12/60


People of importance...

they prefer to take the best and think no more about it.

This is why, when semiconductors are to be used, they look first to G.E.C.

Here is the most versatile range of semiconductor devices in the country; sub-miniature signal diodes to Q-band mixers, low-power zener diodes to high-power controlled rectifiers and low-noise audio preamplifier transistors to high-speed switching transistors!

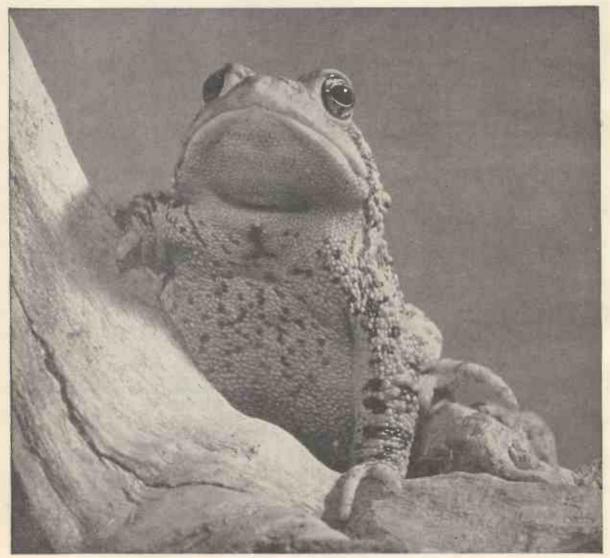All these devices are backed by the G.E.C. standard of reliability ensured by continuous and extensive life-testing of the product.





Write now for details of this remarkable rangel

SEMICONDUCTORS



BRAND recording tape

WORLD'S LARGEST SALES OF MAGNETIC TAPE

Plessey

Power transformers

- * Generous rating
- * Optimum performance
- * Standard, semi-tropical or tropical finish

Audio frequency transformers

- * Interstage and output types
- * Special mountings for printed circuits
- * Low distortion

More information on Plessey Transformers and the Plessey service will gladly be sent to designers and engineers.

transformers for extra reliability

Plessey resources bring many skills and new techniques to support a big production capacity making transformers for industry.

A special service offers early delivery based on a standard range plus facilities for winding transformers exactly tailored to individual specifications.

At every stage of manufacture rigorous quality control and stringent test schedules ensure controlled characteristics and outstanding reliability.

Let Plessey know your requirements at an early stage—their advice can often mean important economies.

Plessey

COMPONENTS GROUP

HAVANT COMPONENTS DIVISION

THE PLESSEY COMPANY LIMITED

New Lane · Havant · Hants Telephone Havant 1701

Overseas Sales Organisation:
PLESSEY INTERNATIONAL LIMITED • ILFORD • ESSEX • ILFORD 3040



-Vortexion quality equipment

The W.V.B. recorder has an additional amplifier and head with provision for "before" and "after" record monitoring while the recording is in progress, and this also has echo facilities.

The W.V.A. recorder has provision for a plug in stereo head and can be supplied with this and stereo playback pre-amplifiers with equalisation each having an output of 1 volt from a cathode follower. This is type W.V.A/S.

A heavy mumetal shielded microphone transformer is built in for 15-30 ohms balanced and screened line, and requires only 7 micro-volts approximately to fully load. This is equivalent to 20ft. from a ribbon microphone and the cable may be extended to 440 yds. without appreciable loss.

The 0.5 megohm input is fully loaded by 18 millivolts and is suitable for crystal P.U.'s, microphone or radio inputs.

The playback amplifier may be used as a micro-

phone or gramophone amplifier separately or whilst recording is being made.

The meter fitted for reading signal level will also read bias voltage to enable a level response to be obtained under all circumstances. A control is provided for bias adjustment to compensate low mains or ageing valves.

The power output is 4 watts heavily damped by negative feedback and an oval internal speaker is built in for monitoring purposes.

THE VORTEXION W.V.B. or W.V.A/S

are eminently suitable for making a high quality recording almost indistinguishable from the original since these models have facilities for monitoring the recording actually put on the tape with only a fraction of a second delay.

By this means, when for any reason the signal is distorted or not as required, the result of the recording on the tape can be heard almost instantly, and adjustments can be made until the results are as required.

Many types of music today have the treble boosted considerably, and may result in greater power being recorded at high frequencies than at middle frequencies, an overload of the tape at high frequencies gives a mushy quality with lots of hiss and background noise.

Adjustment to the bias level while listening to the result is useful in this connection especially where the brand of tape and the bias setting for it are not exactly known.

Again if clean treble recordings at $3\frac{3}{4}$ in. are of prime importance it is now recognised that no other method is quite so effective in achieving this as reducing the bias slightly while listening to the results. The meter reading of the new bias setting for the particular tape used may be noted for future use.

VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, London, S.W.19


Telephones: LIBerty 2814 and 6242-3.

Telegrams: "Vortexion, Wimble, London."

-Vortexion quality equipment

Will deliver 120 watts continuous signal and over 200 watts peak Audio. It is completely stable with any type of load and may be used to drive motors or other devices to over 120 watts at frequencies from 20,000 down to 30 cps in standard form or other frequencies to order. The distortion is less than 0.2% and the noise level —95 dB. A floating series parallel output is provided for 100-120 V. or 200-250 V. and this cool running amplifier occupies $12\frac{1}{4}$ inches of standard rack space by 11 inches deep. Weight 60lb.

120/200 WATT AMPLIFIER

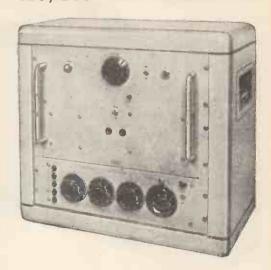

30/50 WATT AMPLIFIER

Gives 30 watts continuous signal and 50 watts peak Audio. With

voice coil feedback distortion is under 0.1% and when arranged for tertiary feedback and 100 volt line it is under 0.15%. The hum and noise is better than -85 dB referred to 30 watt.

It is available in our standard steel case with Baxendale tone controls

and up to 4 mixed inputs, which may be balanced line 30 ohm microphones or equalised P.U.s to choice.

ELECTRONIC MIXER/AMPLIFIER


This high fidelity 10/15 watt Ultra Linear Amplifier has a built-in mixer and Baxendale tone controls. The standard model has 4 inputs, two for balanced 30 ohm microphones, one for pick-up C.C.I.R. compensated and one for tape or radio input. Alternative or additional inputs are available to special order. A feed direct out from the mixer is standard and output impedances of 4-8-16 ohms or 100 volt line are to choice. All inputs and outputs are at the rear and it has been designed for cool continuous operation either on 19 x 7in. rack panel form or in standard ventilated steel case.

Size $18 \times 7\frac{1}{2} \times 9\frac{1}{2}$ in. deep. Price of standard model £49.

The 12-way electronic mixer has facilities for mixing 12 balanced line microphones. Each of the 12 lines has its own potted mumetal shielded microphone transformer and input valve, each control is hermetically sealed. Muting switches are normally fitted on each channel and the unit is fed from its own mumetal shielded mains transformer and metal rectifier.

Also 3-way mixers and Peak Programme Meters. 4-way mixers and 2 x 5-way stereo mixers with outputs for echo chambers, etc. Details on request.

12-WAY ELECTRONIC MIXER

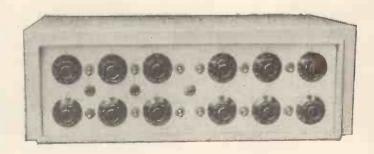

Full details and prices of the above on request

VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, London, S.W.19

Telephones: LIBerty 2814 and 6242-3

Telegrams: "Vortexion, Wimble, London,"



Evidence in Camera



Of interest not only for its story, this picture has provided (quite unintentionally) striking evidence of the reputation enjoyed by LEAK. It is a typical incident of the use of LEAK equipment by professional audio engineers in broadcasting and recording studios throughout the world, who choose LEAK for quality of performance and reliability Does your installation measure up to these standards? If it does not, your LEAK Dealer can help you. The prices of LEAK studio quality equipment are made possible only by world-wide sales.



The new LEAK Varislope Stereo pre-amplifier (Illustrated above) incorporates facilities which make it the most comprehensive pre-amplifier presently available.

We shall be pleased to send you a copy of Thomas Heinitz' review of this "Remarkable new control unit for stereo" reprinted from "Records and Recording."

Whether you are for Monaural or Stereo, LEAK equipment offers you the best of either. These suggestions may help you.

Monaural

Varislope III Pre-Amplifier TL/12 Plus Power Amplifier Southdown Cabinet. Total £55 13 0

Stereo


Point One Stereo Pre-Amplifier Stereo 23 Power Amplifier Southdown Cabinet Total £72 9 0

Ask your Dealer or write to us for brochures

EAK the first name in High Fidelity


H. J. LEAK & CO. LTD., BRUNEL ROAD, WESTWAY FACTORY ESTATE, LONDON, W.3 Telegrams: SINUSOIDAL, EALUX, LONDON Telephone: SHEpherds Bush 1173.

Television Noise Limiting

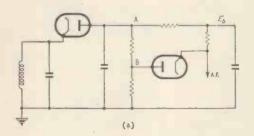

The current November issue of ELEC-TRONIC TECHNOLOGY includes among other interesting articles one in which methods of noise limiting in the sound channel of television receivers are discussed. The author considers various well-known noise-limiting circuits, draws attention to some of their defects, and shows how they may be overcome to provide improved performance.

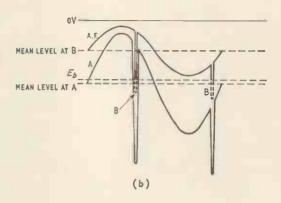Design criteria and practical circuit details are given for a number of noise-limiting circuits and it is shown that a considerable improvement in noise suppression of an indifferent receiver can often be made without resorting to expensive and complicated circuitry.



ARTICLES IN THE DECEMBER ISSUE INCLUDE:

SWITCHING TRANSISTORS

Various methods used for predicting the performance of switching transistors are described in this article and their validity under conditions of large collector current is discussed. Different types of transistor are included and it is shown that, at high levels, evaluation of switching times in terms of the charge control is to be recommended with certain reservations.

TWO-SIGNAL BRIDGES

In this article the author shows that by a simple modifica-tion to the usual bridge-circuit arrangement it is possible for the input and output of the bridge to have a common terminal. This arrangement can also be used to reduce stray admittances and some arrangements enable the bridge to be remotely situated.

ELECTRONIC TECHNOLOGY retains all the familiar features of ELECTRONIC & RADIO ENGINEER including the well-known Abstracts and References section. Regular readership will keep you in constant touch with progress in the entire field.

Electronic technology

POST THIS COUPON TODAY

TO ASSOCIATED ILIFFE PRESS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.I ENGLAND

Please enter my name as a subscriber to: ELECTRONIC TECHNOLOGY for 12 months commencing with the December issue.

I enclose remittance £3.7.0d.

(U.S.A. and CANADA \$9.50) (THREE YEARS \$19.00)

NAME	٠.	٠.	٠.					٠.			 ,.	,												.)				 			
ADDRE:	SS			. 0	las 19			. 1	٠.		 . ,													٠.	. ,				. ,		
						Se y	. 9												٠.,			 									
DATE													, ,			 				 		 				 					

ORDERS CAN ALSO BE PLACED THROUGH ANY NEWSAGENT

F

Crystal Mike by Acos



Model 39/1, this is ideal for tape or general amplifiers, complete with screened lead 39/6, plus 1/- post.

Speaker Bargain



12in. H1-fidelity loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coll. Will bandle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

TV Workshop Aids

E.H.T. SEALER. Apply with soldering iron, Stops corona discharge, etc. 2/6 iron, Stops corona uncomposition, Stops corona uncomposition, POLYTHENE TAPE. 2in × 10 thou, for E.H.T. insulation up to 25 kV. 5/- per 12ft.

SPONGE STRIP, in. xin. For scaling or euchloning, 9d. per foot.

ANTI-STATIC SCREEN CLEANER. For TV tubes and screens. Perspex or glass. Delays accumulation of dust, 3/- per tube. CELLULOSE CEMENT. Specially prepared for radio gluing of metal, glass, ceramic wood, fabrics, 4/8 per tin.

Component Storage Drawers

Stout board con-struction these drawers are ideal for small parts. Bupplied plete with simple plete with simple erection instruc-tions. 1/6 each or 12 drawers each 6×2½×6½ in., 13/6, post 2/-.



Morganite Potentiometers

Single and 2-gang types available, types standard good les spindle, l size length all and

b o x e d .
Single types, 1/- each,
values available: 5 K,
10K, 25 K, 50K, 100 K,
25 0K, 1 meg., 2 meg.
6 mg type, 3/-, each,
5 K ± 5 K, 100 K ± 100 K, 1 meg. ± 1 meg.,
2 meg. + 2 meg.

Hi-Fi Snip Infinite Wall Baffle



THIS MONTH'S

SNIP

CAB OHARGER RECTIFIER. SuitA able for 6 or 12 volts up to 6 amps.
11/- post free.

TRANSISTOR LOUDSPEAKER RADIOS

RESULTS GUARANTEED. Nothing can be nore disappointing than to find that despite care in making up you little radio just will not work. This is unlikely to happen with our set, but if it does, you may send it in for service, we guarantee good results.

for service, we guarantee good results.

Two MODELS

Pocket 4 uses three transistors and one diode and has refinements for receiving weak stations, price 42 c. last nut and bolt, with proper case, tuning coudenser and miniature loudspeaker.

Our sets do not need aerials, also they may be built in stages to car radio output. Post and murance 276.

Pocket 5 uses 4 transistors approx. 3 times output with better tone, price 55/-

PHILIPS TRANSCRIPTION LINIT

Philips AG 2009 Record Player, 4 speed, ideal for the enthu-stast. Pick-up arm wired for stereo fine adjustment on all four speeds. Continuously variable stereo fine adjustment on all four speeds. Continuously variable pick-up weight (2.12 gms.) Supplied with Philips HI-FI crystal type AG3019 for micro-growe and 78 r.p.m.
Prequency response 30-15.000 c/s Pick up lifting and slowering device. Individually balanced heavy turntable. Muting switch. Can be used with any amplifier or radio set. Complete with monaural pick-up \$210/10/0 or \$2\$ Gms. deposit and 20 fortnightly payments of 10/r. Available also with stereo head, diamond or sapphire stylus. Prices on request.

THE TAYLOR METER MODEL 127A

A pocket size meter but with a big scale and a sensitivity of 20,000 Ohms per voil D.C., therefore an ideal unit for television sensiting—robustly made and complete with leads and prods—20 ranges as follows:

D.C. current 50 micro-amps, to 1 amp.
D.C. voitages—0-1,000 voit in seven ranges (23 KV with external probe, optional extra).

Voita A.C.—0.2.500 in six ranges.

Ohms—0-20 meg. Ohm in three ranges (self-controlled) Self-contained 3 in, movement. Price £10 or 10/- deposit and 23 fortnightly payments of 10/-. Non-callers add 5/- carriage and insurance.

COMPONENTS FOR TRANSISTOR SETS

Parts for " Practical Wireless " Pocket Transistor Radios available. Send

Sub-miniature Electrolytics. 1 mfd. 18v., 2.5 mfd. 6v., 4 mfd. 6v., 8 mfd. 6v., 8 mfd. 6v., 25 mfd. 6v., 30 mfd. 3v., 50 mfd. 3v., 50 mfd. 3v., 50 mfd. 3v.,

Transistor Ferrite Rod Aerial with medium and long wave coils with circuit. Price 7/8

Ospillator Coil and set of 3 L.F. transformers for transister set with circuit. Price 23/6

Midget 3in. P.M. Loudspeaker for transistor set. 3 ohm or 80 ohm coil.

Midget 208 pF + 176 pF two-gang Tuning Condenser with trimmers, ‡ spindle drilled and tapped. Price 9/-, plus 1/- post.

Pash-pull Output Transformers, for transistors OC78, etc. Sub-miniature Price 8/6, plus 1/- post.

Push-pull Input Transformer to match the above Output Transformer, 8/16.

0.0005 mld. Single Tuning Condenser. Solid di-electric in. spindle for translator or crystal set. 3/9; ditto with spindle tapped 6 BA, 4/-.

Transistor of crystas set. 3/8; into with spinute tapped o BA. 4:-.
Transistor stated. Set of six for Superhet Includes matched pair, Mullard 23/10/0, ditto unbranded. 45/-; suitable as mixers, 9/6 each. Suitable as I.F. ampliders, 8/6; sutable for R.F. and Regen, circuite, 6/6; matched pairs for Push-pull Output, 16/- per pair. High guln for single ended output, 7/8. Ordinary white spot. 3/9; red spot. 3/8.

Resistors, miniature quarter watt type for transistor sets. All popular valves, 5d, each.

Miniature ceramic condensers 6d. each.



Transistor Set Cabinet

Very modern cream cabinet, size $5! \times 3 \times 1!$ in, with chrome handle tunding knob and scale. Price 7/6, plus 1/6 postage and packing.

Connecting Wire



P.V.C. covered in 100ft. coils—2/9 a coil or four coils different colours, 10/- post free.

Rectifier Bargains



Selenium rectifier type 12, 500 v. j. A. half-wave, easily rebuilt into full wave or multiple type, contains 30 35 mm. discs. Price 8/6, plus 1/6 post. Type 13, 36 volt 9 amp. easily rebuilt into six full wave charger rectifiers suitable for 6 or 12 volt batteries. 3 amps, contains 24 84 mm. discs. Real bargains at 19/6, plus 1/6 post.

Band III Converters

Suitable Wales, Lon-Wales, Lon-don, Midland, North Scot-land, etc.. All the parts, in-cluding 2 EF80 don, North alves. coils, ine tuner, con-



fine tuner, con-trast control, condensers and resistors. (Metal case available as an extra). Price only 19/8, plus 2/6 post and insurance. Date free with parts or available separately, 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sert of letter every day of the week, so if you have hestated because you thought our kits too cheap you need hesitate trast control, no longer.

Miniature Microphone

American made. Dynamic type, real bargain at 2/6, plus 6d. postage.



8 8

Building A Scope?



3in. oscilloscope tube. American made type No. 3FP7, octal base 6.3 v. .6 amp, heater, electroetatic defection, brand new and guaranteed, with circuit diagram of scope. 15/- each, plus 1/6 post and insurance



Wrap our heater wire (blanket wire) around the pipes in your loft, to prevent freeze-ups Complete blanket wire suitable for up to 50ft, of pipe 10/- post free. With instructions.

PRECISION EQUIPMENT, **ELECTRONIC**

post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road,
Eastbourne, marked Department 2. Callers may use any one of the Companies below.

Electronics (Croydon) Ltd., 266 London Road, Croydon.

Phone: CRO 6558. Half day, Wednesday Electronics (Finsbury Park), Ltd., 29 Stroud Green Road, Finsbury Park, N.4. Phone: ARChway 1049 Half day, Thursday

Electronics (Manor Park) Ltd. 520 High Street North, Manor Park, E.12.

Phone: ILFord 1011 Half day, Thursday

Electronics (Ruislip) Ltd., 42-46 Windmill Hill, Ruislip, Middx.

Phone: RUISLIP 5780 Half day, Wednesday




If you are a designer or engineer in computer circuitry, instrumentation or any other field of electronics you will find this McMurdohm Resistor technical catalogue invaluable. Send for your copy.

THE McMURDO INSTRUMENT CO. LTD.

ASHTEAD · SURREY · ENGLAND Telephone: ASHTEAD 3401



Send for full technical information to

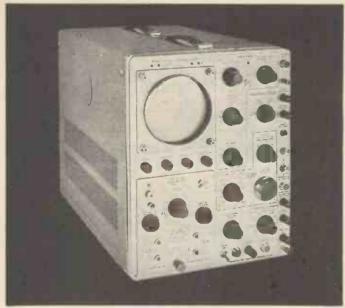

"The 545" has set a new standard in wide band measuring Oscilloscopes.

FOUR MORE FROM THE TEKTRONIX RANGE

Dual Beam Oscilloscope, Type 502

True dual Beam differential display at $200\mu V$ to 20V/cm from D.C. to 100~kc/s. Band width increases as sensitivity is reduced.

Full sensitivity X-Y facility.

Specially suitable for electro - medical and similar work.

"X - Y" Oscilloscope, Type 536

Identical X & Y axes D.C.—10Mc/s, $0.03\mu sec.$ risetime.

Relative phase shift less than 1° to 15Mc/s. Linear sweep with type T time base plug-in unit.

OUR FIRST CONSIDERATION—

the *right* instrument for your application

In the field of oscilloscopes, Livingston Laboratories offer a unique service in the form of expert advice in the choosing of equipment to meet your needs. The relevant factors are not who makes it or where it is made, but will it do the job? Livingston Laboratories are sole representatives in Great Britain of Tektronix. When top performance oscilloscopes are required, the range of Tektronix instruments can satisfy the most rigorous demands.

Extend your oscilloscope facilities with these new Tektronix Plug-in Units



TYPE S—Converts Types 540 and 550 Series to display semi-conductor diode switching characteristics and to measure:—
Effective lifetimes to 2 nanoseconds
Stored charge to 10 picocoulombs
Junction capacitance to 2 picofarads
Base resistance to 0.25 ohm.

TYPE Q.—Plugs into any Tektronix Plug-in Oscilloscope to provide information from strain gauges and many resistive, capacitive and inductive transducers plotted against time.

Dual Beam Oscilloscope, Type 551

True dual Beam D.C.—25Mc/s. Signal Delay 0.2µsec. both channels. Linear sweep 20mµsec. to 5 sec/cm calibrated. Single sweep lock out reset circuitry. 4 Channels, D.C.—22 Mc/s with two 53/54C units. 10Kv E.H.T. enables single shot

Transistor Curve Tracer, Type 575

C.R.T. Display of families of N.P.N. or P.N.P. Characteristic curves. Collector sweep 200 volts at 1A, 20 volts at 10A positive or negative. Base or Emitter Step Generator 4-12 steps at 1µA to 0.2A per step. 5 constant voltage/step divisions. Polarity negative or positive. X and Y axes calibrated ± 3%.



Full details of Tektronix Equipment from sole distributors:

LIVINGSTON LABORATORIES LTD
RETCAR STREET - LONDON - N.19 Telephone: Archway 6251




DERRITRON Electronic GROUP

BEME TELECOMMUNICATIONS LTD . CHAPMAN ULTRASONICS LTD

DORAN INSTRUMENT CO. LTD · L.S.B. COMPONENTS LTD · RESLOSOUND LTD

PRECISION VERNIER POTENTIOMETER

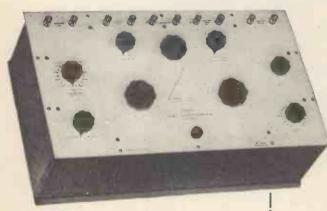

Cat. No.: E.4240

Ranges: 10 microvolts to 1.89999 volts &

I microvolt to 0.189999 volt.

Accuracy: I part in 100.000 of the I volt

setting.
Weight: 38lbs.

Dimensions: $23 \times 13\frac{1}{4} \times 8\frac{1}{2}$ in.

THERMO-COUPLE POTENTIOMETERS

D.C. POTENTIOMETERS UNIVERSAL SHUNTS

STANDARD CELLS GALVANOMETERS

RESISTANCE BOXES CONDUCTIVITY BRIE

RESISTANCE BOXES CONDUCTIVITY BRIDGES WHEATSTONE BRIDGES PH METERS and TITRATORS

pH ELECTRODES, etc., etc.

DORAN INSTRUMENT COMPANY LTD.

FM AM CONSOL RECEIVER

The Commander is a pure marine radio receiver which not only gives high quality drift-free F.M. reception, and excellent reception of the more powerful continental stations on the Medium and Long wavebands, but also incorporates a transistorised Beat Frequency Oscillator for the reception of Consol signals.

Operating from the ships 12v. or 24v. supply, no converters or other bulky units are required, as the Commander is completely self-contained, with a built-in transistorised "Power-pack" for trouble-free reception.

Circuit employs 7 valves and 4 transistors

3 wavebands give following coverage:

L.W. Band: 150kc/s-400kc/s (200-750m)

M.W. Band: 550kc/s-1,560kc/s (545.5m-192.3m)

V.H.F. Band: 87.5mc/s-100kc/s



"COMMANDER"

Transistorised.

Power Supply: 12/24v. D.C. at 2.85A.

Finished in grey dimple stove enamel.

Dimensions: 12in. wide, 5\frac{5}{8}in. high.

RADIO TELEPHONES

D/F EQUIPMENT

SHIPS P.A. SYSTEMS


BEME TELECOMMUNICATIONS LTD.

INSTRUMENTS

SO YOU THINK
COSSOR SPECIALISE
ONLY IN OSCILLOSCOPES

-then study this spot-on Cossor LCR bridge

This Cossor L C R Bridge enables you to measure inductance and capacitance more easily, quickly and accurately than any other bridge of comparable cost. Its unique feature is a special miniature cathode-ray tube that provides obvious discrimination between phase and amplitude out of balance, ensuring unambiguous readings. Just reduce the ellipse on the screen to be sure you're spot-on. Resistance is measured under DC conditions; this means you can also obtain the resistance of an inductance.

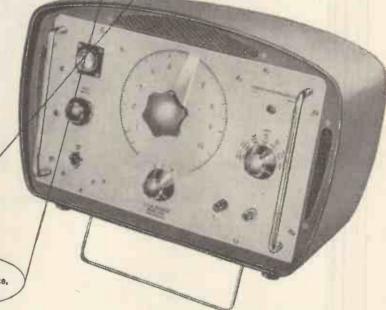

with phase balance.

Please send for full information and specifications



Cossor Instruments Ltd

COSSOR HOUSE, HIGHBURY GROVE, LONDON, N.5 Telephone: CANonbury 1234 (33 lines)

BEST-

AWAY AHEAD OF THE REST-IN HEADS FOR

FOUR-TRACK RECORDERS

Sometimes the British do not speak up enough for themselves—so let us say quite emphatically that it is a complete myth that certain European countries excel in the manufacture of heads.

- * MARRIOTT HEADS have been used for many years by G.P.O., Government Research Establishments, H.M. Armed Forces, B.B.C., Cine Manufacturers, T.V. Recording, in missile and space rocket research, in Automation, in Talking Books, in Telephone answering machines and of course by the majority of Tape Recorder manufacturers in this Country as well as many others overseas. In fact wherever Recording Heads are used.
- ★ MARRIOTT HEADS are backed by 14 years of experience—by unique and specialised machinery and by some of the most highly skilled instrument engineers in the world.
- ★ MARRIOTT 4-TRACK HEADS have a better performance and consistency than most heads at several times the price. They represent the best value in the World for quality at a quantity price.

PRIVATE AND MANUFACTURERS **ENOUIRIES INVITED**

- ★ MARRIOTT 4-TRACK HEADS have accurately controlled gaps of .0001in, giving as high or better top response than any other head available. Engineer lapped and honed surfaces of all metal low friction coefficient material ensure very minimum wear. Complete mumetal screening ensures perfect results.
- ★ MARRIOTT HEADS, STOP PRESS! Latest specials just passed test are for space research and record 12 tracks on in tape with a i micron gap. They have been made by the same skilled instrument makers assembling our current 4-track production.



MAGNETIC RECORDING HEADS

P. A. MARRIOTT CO. LTD., WATER ROAD WEMBLEY, MIDDLESEX. TEL.: WEM 7493

1961 DIARY for the radio man

everything that is needed in the day-to-day work

The 80 pp. reference section of this week-to-an opening diary includes in tabloid form, the kind of technical and general information so often needed by radio men but seldom readily available. It is a veritable mine of information and will be much appreciated by everyone interested in radio and television.

Wireless World **Diary 1961**

Leather 6s 9d (Postage 4d) Overseas 6s 9d Rexine 4s 9d (Postage 4d) Overseas 4s

from booksellers and photographic dealers

Circuit diagrams (including a transistor a.f. oscillator and a transistor mixer circuit)

Coil winding data.

Aerial dimensions and aerial sharing circuits.

Licensing regulations.

World television standards.

Radar frequency bands

Lists of U.K. television and v.h.f. sound broadcasting stations.

Tabulated base connections for over 700 valves.

Published by T. J. & J. Smith, Ltd. in conjunction with

ILIFFE & SONS LIMITED

DORSET HOUSE

STAMFORD STREET

LONDON S.E.I

Hewlett-Packard

Oscillators

for frequencies 0.008 cps to 10 MC



-hp- 650 A Test Oscillator

-hp- 650 A Test Oscillator

One of the most popular -hp- oscillators is Model 650 A, 10 cps to 10 MC, a highly stable instrument for audio, supersonic, video and RF measurements. Output is flat within 1 db full range, voltage range 0.00003 to 3 V. Distortion less than 1 % to 100 KC.

Hewlett-Packard offers you 13 high-quality, very accurate oscillators. Each uses the resistance-capacity circuit pioneered by Hewlett-Packard – the circuit that makes possible high stability, wide range, compact and rugged instruments. These dependable oscillators are simple to operate and require no tiresome resetting or adjustment during operation.

Many world-famous Hewlett-Packard laboratory instruments are now made in the new Hewlett-Packard GmbH plant at Böblingen, near Stuttgart. Here quality engineering and latest manufacturing techniques bring you instruments of exceptional performance at moderate price.

Prices delivered U. K. exclusive of duty where payable. Continuous progress in design may affect the above specifications which are therefore subject to change without notice.

Instrument	Primary Uses	Frequency Range	Output	Price
-hp- 200 AB	Audio tests	20 cps to 40 KC	1 watt / 24.5 V	£ 62
-hp- 200 CD	Subsonic through super- sonic audio and ultra- sonic tests	5 cps to 600 KC	160 mW or 10 V / 600 ohms; 20 V open circuit	£ 69
-hp- 200 J	Interpolation, frequency measurements	6 cps to 6 KC	160 mW / 10 V	£ 123
-hp- 200 SR	Driving ·hp- 739AR Frequency Response Test Set	.5 cps to 600 KC	3 V rms into 50 ohms	₤ 76
-hp- 200 T	Telemetry, carrier current tests	250 cps to 100 KC	160 mW or 10 V / 600 ohms; 20 V open circuit	£ 185
-hp- 201 C	High quality audio tests	20 cps to 20 KC	3 W or 42.5 V / 600 ohms	£ 93
-hp- 202 A	Low frequency measurements	0.008 to 1200 cps	28 mW or 30 V p-p / ·4000 ohms	£ 216
-hp- 202 C	Servo equipment tests, measurements	1 cps to 100 KC	160 mW or 10 V / 600 ohms	£ 119
-hp- 205 AG	High power audio tests, gain measurements	20 cps to 20 KC	5 watts	£ 205
-hp- 206 A	High quality, high ac-	20 cps to 20 KC	+ 15 dbm	£ 308
-hp- 207 A	Audio sweep generation	20 cps to 20 KC	160 mW or 10 V / 600 ohms	£ 134
-hp- 233 A	Carrier oscillator	50 cps to 500 KC	3 W / 600 ohms	£ 205
-hp- 650 A	Wide range video tests	10 cps to 10 MC	15 mW/3 V	€ 201

For information, technical sales and engineering help, or a demonstration please write or call



Hewlett-Packard S.A.

Geneva (Switzerland) Rue du Vieux-Billard 1, Tel. (022) 26 43 36

Exclusive Distributor for United Kingdom:

LIVINGSTON LABORATORIES LTD. RETCAR STREET, LONDON, N. 19

Telephone: ARChway 6251

HSPA - 1 - 412

leads the way

Now made in Great Britain -

DEAC

PERMA-SEAL

SEALED RECHARGEABLE

NICKEL CADMIUM CELLS & BATTERIES



- * No corrosion.
- * No gassing.
- * No maintenance.
- * Unlimited Shelf life.
- * Robust and compact.
- ★ From 20 mAh to 23 Ah.

For Radios, Hearing-aids, Tape Recorders, Shavers, Torches, Electric Toys, Portable Measuring Instruments.

All enquiries to the sole Distributors

G. A. STANLEY PALMER LTD. Maxwell House, Arundel St, London, W.C.2.

Tem. 3721.

Manufactured in Gt. Britain by DEAC (GT: BRITAIN) LTD., Altona Way, Buckingham Ave., Trading Estate, Slough, Bucks. Slough 24539

There's a quarter of a century's experience built into every one

PLUG-IN QUARTZ CRYSTAL CONTROLLED TRANSISTOR **OSCILLATORS 100 Kc/s**

A range of units is now available covering a frequency range from 1 kc. to 15 Mc/s. Typical data for Q.C. 925-100 kc/s. unit. Frequency tolerance is ± .015% over temperature range 13°C-60°C. Stability less than 5 parts in a million change with a 10% change in supply voltage. Output 3 volts on open circuit conditions. 1½ volts across a 20,000 ohm load. Power supply 6 volts D.C. Power consumption 5 milliwatts.

Write for full technical specification.





TIMES MILL · HEYWOOD · LANCASHIRE Tel: HEYWOOD 6868 London Sales Off ce: Magnet House, Kingsway, W.C.2. Tel: Temple Bar 4668 A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

FROM EIMAC:


Breakthrough in tube technology opens up new range of reliability

You are looking at a major advance in tube design. This ceramic envelope is made with beryllium oxide—an amazing insulating material now introduced by Eimac for electron tubes. It offers thermal conductivity ten times greater than any other material in use today. It provides low losses, high breakdown strength and a comparatively low dielectric constant for improved bandwidth in critical applications such as output windows.


With the introduction of beryllium oxide, Eimac breaks through the problem of dissipating ever larger amounts of heat in dielectrics. And opens a new chapter in power-output capabilities of high power microwave and certain negative grid tubes. The result: a whole new spectrum of tube reliability and performance. Beryllium oxide is now being used in several Eimac production tube types generating ten kilowatts and above.

This significant advance in the state of the art of manufacturing electron tubes has been pioneered by an Eimac sponsored research program. Eimac sponsored research has also resulted in the recent introduction of the first practical quartz-to-metal seal. Contact your nearest representative.

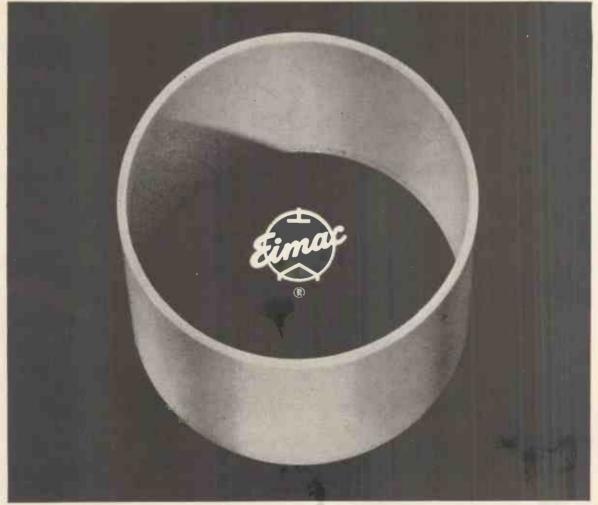Eitel McCullough, Inc., San Carlos, Califorria
European Subsidiary, Eitel-McCullough, S.A., Geneva, Switzerland



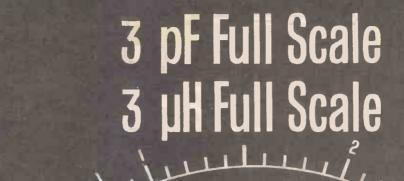United Kingdom Representatives: WALMORE ELECTRONICS LTD. Phoenix House 19/23 Oxford Street, London, W.I Gerrard 0522
Write or phone for immediate technical information, data and quotations



μμΕ/μΗ




DIRECT READING INDUCTANCE AND CAPACITANCE METER MM 906

The Solartron L-C Meter MM 906 is the ideal instrument for quick, accurate component checks and in situ measurements of L and C, including 'strays'. Valve interelectrode capacitances are measured with ease.

Circuit-development and service engineers will appreciate the usefulness of the MM 906 in optimising component and wiring layouts; it provides a continuous monitor of inductance or capacitance, down to very low values, whilst circuit changes are being made.

 - Accurate in situ measurements.
- 0-3 pF and 0-3 μH F.S.D. ranges.
- 'Guard Voltage' to eliminate effects of unwanted capacitances.
- Instant readings on a 4" scale.
- Portable.



Inductance Ranges: 0 – 3, 10, 30, 100 and 300 uH Capacitance Ranges: 0 – 3, 10, 30, 100 and 300 pf Accuracy: ±3% Voltage (120 – 140 kc/s) across unknown

Voltage (120 – 140 kc/s) across unknown L: 0.25 V max. C: 1 V max.

Load Resistance Limits. The accuracy is maintained with the following loads: Inductance: $20~k\Omega$ shunt, 10Ω series Capacitance: $0.1~M\Omega$ shunt 'Guard Voltage' sufficient to drive 200 pF. ($Z_{Out}=250\Omega$).

Mains Input: $110|220 \text{ V} \pm 20 \text{ V}$, 50-60 c/s. Size and weight: $10\frac{1}{2}^n \times 6\frac{3}{2}^n \times 10\frac{1}{2}^n$. 10 lbs.

Write now for full details to: SOLARTRON LABORATORY INSTRUMENTS LIMITED

Cox Lane, Chessington, Surrey.

Tel: LOWer Hook 2150 Cables: SOLARTRON CHESSINGTON Telex: 23842 SOLARTRON T. DIT (TC) A member of the Firth Cleveland Group

transistor scaled down for ultracompact equipments



The OC123 is a ferrite core driver transistor similar to the OC23, but scaled down into a small metal can for those applications where space saving is of cardinal importance—such as in closely packed printed circuit boards—and where the dissipation rating need not be so high as with the OC23.

The total dissipation rating of the comparatively small OC123 is, in fact, 200 mW at an ambient temperature of 45°C. The peak current is 1 amp, and the voltage rating and current gain are also high. Even at a collector current of 1 amp $\tilde{\alpha}'$ is 50 minimum.

The OC123 is particularly suitable for gating current pulses generated by its larger companion type OC23 for driving ferrite cores. In such an application, a 350mA 2 microsecond pulse with a leading edge rise time of 0.4 microsecond can be passed by the transistor when it is fully bottomed.

Abridged details are given below—for full data please write to Mullard House.

Mullard

industrial semiconductors



V_{cb} max. $(I_e = 0)$	50 V
V_{ce} max. $(V_{be} > +0.5V)$	50 V
$V_{ce} max. (I_{c} = 0.5A)$	25 V
i _c (pk) max	. 1.0 A
Ic (av) max. (averaging time 20 ms)	. 0.5 A
ptot at 45°C ambient	200 mW
T _i max	. 90°C
Junction temp. rise above	
ambient in free air	0.22°C/W
Junction temp. rise above case	0.06°C/W
V_{c} (knee) ($I_{c} = 400 \text{ mA}$)	-350mV
$f_1 (V_C = -2V, I_C = 100 \text{ mA}, T_j = 25^{\circ}\text{C}$) 1.5Mc/s

MULLARD LIMITED : Semiconductor Division · Mullard House · Torrington Place · London W.C.1 · Telephone LANgham 6633

LASKY'S SAVE POUNDS! RADIO

ORDER BY POST IF YOU CANNOT CALL

3-SPD. TAPE RECORDER

Complete with Microphone, Tape & Spool

Carr. & Ins., 251-

SPECIAL OFFER OF TAPE

Famous make. P.V.C. base on latest type plastic spools. Brand new, boxed and guaranteed. 1,200ft. on 7in. spool, 20/-



1,	80	Oft.	on	7in.	spoo	1		32/6
1,	20	Oft.	on	5åin.	spoo	1		21/-
8	50	ft.	on	5%in.	spoo	l		16/6
	S	CO1	CH	PL	AST	[C]	ΓAΡ	E
1,	20	Oft.	on	7in.	spoo	1		25/-
	- 1	Vi.S.	8.	LONG	PL	AY 1		
1,	80	Oft.	on	7in.	spoo	1		39/6
1,	20	Oft.	on	5%in	spoo	1		29/6
	85	Oft.	on	5in.	spoo	1		25/6
	22	Oft.				1		7/11
			Pos	t: 1		1 1/6		
		Ord	ers	over	60/-	post	free	3.

ALL MAKES OF TAPE. Long Play, Double Play and American "MYLAR."

HIGH FIDELITY TAPE RECORDER HEADS

Leading make, new and unused. Upper or lower track. RECORDA PLAYBACK high imped-Double



ance. Double wound and will reproduce up to 12,000 c.p.s. at 7½ i.p.s. Azimuth adjustments. Output 5 millivolts at 1 Kc. at 7½ i.p.s. BRASE, low impedance. Lasky's Price Post free. Per pair Please specify upper or lower track.

MICROPHONE BARGAINS

"Diana," High impedance moving coil mike unique magnetised table



history in the state of the sta

Acos CRYSTAL STICK MIKE, type M.C.39/1, complete with cable. Listed at £5/5/-.

Lasky's Price 39/6

MINIATURE moving coil dynamic microphone, incorporating switch and complete with pocket clip.
used for the "Fi-Cord,"
Post 1/6.

ALL TYPES OF CHASSIS

We hold the largest selection of leading makes: ARMSTRONG, DULCI, EMPRESS, etc. A.M. 7 Gns. 7 Gns.

EXPORT ORDERS

Our Export Dept. ships goods to all parts of the world. We also all parts of the world. We also operate the "Personal Export Service" (free of purchase tax) for visitors to Great Britain.

HI-FI EQUIPMENT

(STEREO & MONAURAL)

GREAT REDUCTIONS

For mains 200-250 v., 50-60 c/s. New and fully guaranteed, only slightly soiled. Very limited quantity.



SAVILLE STEREO SEVEN Pre-Amplifier and Control Unit. Uses two EF86 and two ECC81 valves. Separate controls, bass and treble, balance and switched selector for various inputs. List £15. Lasky's Price £9/19/6 Post 3/8.

POWER UNIT. Twin push-pull Amplifiers of 7 watts each. Freq. range 45 c/s to 28,000 c/s ± 1 dB. Distortion at 1,000 c/s and 7 watts <0.2%. Extra power supplies for Tuner. Five valves: four ECL82, one GZ34. List £33. Lasky's Price £13/19/6

Post 7/6.

SPECIAL COMBINED OFFER The Saville Stereo Seven Pre-Amp. and Power Unit, if pur-chased at the same time, \$23 Carr. 10/-.



Constructed to finest laboratory standards, silver-grey hammer finish. 20 watts nominal, 30 watts peak from "C" core distributed load stage. Freq, range: 34 c/s to 30,000 c/s ±1 dB at 20 watts. Distortion at 1,000 c/s and 20 watts <0.1%. Mains transformer will sustain 100% over-load continuously. Power supplies for Tuner: 300 v. 50 mA. 6.3 v. 2.5 amp. 4 valves: 2 EL34 push-pull, ECC81, GZ34. List £27 Lasky's Price Carr. 9/8. \$14/19/6

SPECIAL COMBINED OFFER Two Saville Twenty Amplifiers and one Saville Pre-Amplifier (as illustrated), if purchased at same time.

Lasky's Price £36 time. Carr. 12/6.

Full provision for stereo disc or tape. Controls: volume, treble, bass, balance for stereo and 6-position selector switch (for various inputs). Two ECC81 valves.

Lasky's 8 GNS. List £13/10/-. Post 3/6.



LAST FEW! AVANTIC STEREOPHONIC HI-FIDELITY EQUIPMENT

For 200-250 v A.C. mains. New and fully guaranteed. Stereo Pre-Amplifier Con-

trol Unit, twin channel. List £28/10/-. Lasky's Price £16/19/6. Carr. & Ins. 7/6.

DL7-35. Power Amplifier. 54 peak output. Two of these can be used with SP21/2 Pre-Amp. Control Unit for stereophonic reproduction. List £31/10/-. Lasky's Price Carr. & Ins. 12/6. £16/19/6

SPECIAL COMBINED OFFER

One SP21/2 Stereo Pre-Amp. Control Unit and two DL7-35 Power Amplifiers if bought at the same time, 47 Gns. Carr. 21/-.

SPA11. Stereo Amplifier and Pre-Amplifier, two 10 watts output. List £29/8/-. Lasky's Price 19 Gns. Carr. & Ins. 7/6.

PL6/21. 20 watt Monaural Amplifier and combined Control Unit. List £20/8/-. Lasky's Price 19 Gns. Carr. & Ins. 7/6.

Stereo Pick-up Amplifier Unit, two identical lownoise voltage amplifiers. £6/16/6. Lasky's Price 84/-. Carr. & Ins. 7/6. List

STEP21. Stereo Tape Pre-Amplifier provides full equalisation and gain to operate any Amplifier direct from high or medium impedance Tape Deck.

Lasky's Price 84/-Carr. & Ins. 7/6.

Full details of any of the above post free on request.



GET THIS BARGAIN FOR CHRISTMAS!

A complete Tape Recorder using Collaro Studio 3-speed Deck, 17, 33, 7½ i.p.s. Twin track, with pause control, rev. counter, latest type electronic recording indicator. Superimposing switch, volume and tone controls, 7 x 4 loudspeaker, 4 watts output. Takes 7in. spools. In contemporary design carrying case, $9\frac{1}{2} \times 16 \times 16$ in. Brand new, fully assembled ready for use. Limited number.

TAPE DECK OFFERS



COLLARO STUDIO TAPE TRANS-CRIPTOR. 3 motors, 3 speed, 1½, 3¾, 7½ i.p.s., takes 7in. spools. Push - button controls. Lasky's Price complete with Tape and Spool £12/19/6. Carr. & Ins. 12/8.

COLLARO TAPE TRANSCRIPTOR Mk. IV, fitted digital counter. List £25. Lasky's Price £17/16/6 Carr. & Ins. 12/6. Tape extra.



B.S.R. "MONARDECK" single speed, 3½ i.p.s., uses 5in. spools, Lasky's Price including 850ft. Tape 28/19/6. Carr. free.

TAPE RECORDER AMPLIFIER

TAPE RECOUNTS AND A STUDIO Transcriptor. Uses 3 valves, magic eye, contact cooled metal rectifer. Incorporates mike; gram/radio inputs, ext. i.e. jack, superimposing switch. Complete with gold/black knobs.

12 GIS. Post 3/6. 12 Gns.

PLASTIC TAPE SPOOLS

5in. 5in. 7in. 2/9 2/9 2/9 7in. Metal Spools, 1/9 each. Post extra.

"INSTANT" BULK TAPE ERASER

ERASER
and Head Demagnetiser. Erases a
complete reel of magnetic Tape in few
seconds, 27/6. Post free.

ASKY'S RADIO COURTEOUS SERVICE & TECHNICAL ADVICE RADIO · TELEVISION · HI-FI · ELECTRONICS · RECORDERS

London's Finest Selections of the Latest Hi-Fi Equipment

Visit either of our addresses for Selective Demonstrations.



AMPLIFIERS

QUAD, ROGERS, LEAK, RCA, JASON, LINEAR, PAMPHONIC, DULCI, W.B., ARMSTRONG, etc.

TAPE RECORDERS

Largest stocks in London. BRENELL, CLARION, COSSOR, ELIZABETHAN, ELEKTRON, FIDELITY, FI-CORD, FERGUSON, FERROGRAPH. GRUNDIG, HARTING, KORTING, MINIVOX, PHILIPS, REFLECTOGRAPH, SOUND, SIMON, STEELMAN, STUZZI, TANDBERG. TELEFUNKEN, TRUVOX, TRIX, STELLA, WALTER

4-SPD. AUTO-CHANGERS



B.S.R. type UA8	£6 1	9 6
B.S.R. UA8, stereo	£7 1	9 6
B.S.R. UA12, stereo	£8 1	9 6
B.S.R. type UA14	£7 1	9 6
COLLARO Conquest,	wired	for
stereo, with monaural p.u	. £6 1	9 6
As above, Stereo	£7 1	9 6
Post on all above	5/	

GARRARD

Model 120	83	8	0
Model 121	£9	9	0
Model 209	£9	19	6
Mdl. 210, Stereo 1	113	11	0
Mdl. 210 with monat	ıral	aı	nd
stereo heads			
RC.88	279.68	10	6
RC.88 STEREO			

SINGLE PLAYERS

Auto start and stop. Complete with pick-up and crystal cartridge. GARRARD 4SP £6 19 6 GARRARD TA Mk. II, wired for STEREO, plug-in head £8 9 0 E.M.I. 4-spd., wired for STEREO and fitted Acos stereo T.O. cartridge £6
Post on all above 5/-. £6 19 6

B.S.R. TU9, non-auto Turntable and separate Pick-up.... \$3 19 6
Post free.

COLLARO JUNIOR 4-speed motor and separate pick-up..... £3 15 0 and separate pick-up...

PICK-UP CARTRIDGES

ACOS HGP.59 or HGP.37 turnover crystal cartridge with L.P. and standard styli. List 39/7. Lasky's Price 18/- post free

ACOS 73-1A STEREO. List 52/6. Lasky's Price 29/6 post free.



TRANSCRIPTION TURNTABLES

COLLARO, GARRARD, LENCO, CONNOISSEUR.

STEREO ADAPTOR

CONVERTS ANY RADIOGRAM TO GIVE STEREOPHONIC REPRODUCTION

2-valve Amplifier using EF80X and EL84 metal rectifier (full-wave bridge). Mains voltage 195-250, 50/80 c.p.s. Ganged volume control and ganged tone control CAN ALSO BE USED AS A SINGLE-END AMPLIFIER.

LASKY'S PRICE complete with printed circuit, circuit diagram, full service data and 2 new 59/6 valves. Post & Pkg. 3/6.

SPECIAL OFFER. The above, plus Acos 73-1a Stereo Cartridge and 6in. or 8in. Loudspeaker, 95/-. Post 5/-.



Famous make. For 200-250 v. A.C. Output 4 watts matched to 3 ohms speaker. 7 valves: E.C.25, ECH81, EF89, EABC-0, EL84, E280, EM81, magic eye tuning indicator. Covers medium, long and FM bands. Length 12:n., height 7/lin., front to back 84:n.

LISTED AT 22 GNS. £16/19/6

Carr. and Ins. 12/6. Available on H.P. terms

TRANSCRIPTION MOTORS

GARRARD 4HF, stereo and monaural, complete with two plugstereo and

GARRARD 301 (Strobe) £23 18 4 PHILIPS £10 10 0 Lenco, Connoisseur, etc. also in

Post 1/6.

SEND FOR OUR FABULOUS

HI-FI CATALOGUE

Nothing like it has ever before been offered. Over 100 large pages, 111×81in. in photogravure and colour. It is a COMPARATOR-CATALOGUE to enable you to choose from all the latest and most advanced equipment. Send for a copy today.

Price 3s. 6d. part post 6d.

Fully refunded on making your first hi-fi purchase.

PICK-UPS

COLLARO, GARRARD, CONNOISSEUR, LEAK, BJJ, ORTOFON, GOLDRING, etc.

TRANSISTOR RECORD PLAYER



v. operation. For all L.P. and available services. standard records. All components available separately

AMPLIFIER

300 milliwatts push-pull output, using two OC71 and two OC72 transistors. Fully assembled, 79/6. Knobs, 3/6 extra.

LOUDSPEAKER 30 ohms, 7 × 4in. elliptical, matched to Amplifier, 25/-.

3-8PD. TURNTABLE 6 v., with rubber mat and speed adjustment, complete with t.o. crystal cartridge and two sapphire styli. 79/6.

CARRYING CASE

As illustrated, handsome two-tone finish. 17in. deep, 14in. wide, 52in. high. Well made and finished. 49/6.

Batteries extra

THE 'VANCOUVER' 3-TRANSISTOR POCKET RADIO

Employs 3 transis-tors plus german-ium diode, on printed circuit size 3½×4×¾in. Tun-able over medium and long waves. Built-in Ferrite rod aerial. CAN BE BUILT FOR 39/6



Circuit diagram and step-by-step instructions, 1/6 (free with parcel).

DULCI, QUAD, LEAK, JASON, ROGERS, etc.

SPEAKERS

WHARFEDALE, GOODMANS, LOWTHER, G.E.C., LORENZ, PHILIPS, TANNOY, etc.

CABINETS
W/B, PRELUDE, G-PLAN,
NORDYK, CAPRIOL, etc. G-PLAN,

"LINEAR" AMPLIFIERS
DIATONIC "10-14 watts 12 Gns.
CONCHORD" 30 watt 15 Gns. L45 4-5 watt Amplifier \$5/19/6 LT45 Tape Deck Amplifier 12 Gns. L50 50 watt Amplifier 19 Gns. L10 10-12 watt with pre-amplifier

L3/3 Stereo Amplifier 7 Gns. All other types in stock.

PRINTED CIRCUIT **GRAM AMPLIFIER**

Uses two valves, ECL82 and EZ80 and separate mains transformer to and separate mains transformer to minimise hum. Incorporates Elac 8 × 5in. loudspeaker with output transformer mounted. Con-centric volume and tone controls. Size of printed circuit: 4×3×2½in. Lasky's Price 69/6 complete.

Post 2/6. Less Speaker, 55/-.

P.M. SPEAKERS

ROUND

3½in. 4in. 5in. 6½in. 8in. 10in. 17/6 19/6 14/6 16/- 16/6 25/-

ELIPTICAL
7×4 9×6 10×2½ 10×6 10×2
14/6 22/6 25/- 25/- 25/-Post extra.

'EASY-SIX' 6-TRANSISTOR PORTABLE RADIO CAN BE BUILT FOR

£9/15/- Post 3/-.

500 milliwatts p.p. output. Full medium and long wave coverage. Uses six first-grade Mullard transistors, 5in. loudspeaker, internal ferrite rod aerial with provision for car radio aerial. The printed circuit with component positions clearly shown, plus pre-assembled dial makes construction very simple. Smart blue/cream Vynide covered cabinet 8½×6½×3in. Uses PP7 battery (8/3 extra).

CIRCUIT DIAGRAM and full step-by-step instructions, 1/6 (free with parcel).

LASKYS RADIO

EVERYTHING FOR HOME CONSTRUCTOR & SERVICEMAN

* The largest and most combrehensive stocks of all components, test gear, etc., and the finest value in Great Britain.

LASKY'S MIDGET T.R.F.



CAN BE BUILT FOR £4.19.6 Post & Pkg.

For A.C. mains, 200-250 v. Med. and Long wave. Uses 2 double-purpose valves EBF89 and ECL80 contact-cooled rectifier. 5in. P.M. Speaker. Plastic cabinet, 8½ × 5 × 41in. deep. FULL DATA, instructions, circuit

LASKY'S

diagram, shopping list, 1/6.

CAR RADIO

CAN BE BUILT ABSOLUTELY COMPLETE

FOR £11.19.6 Post 3/6



Will fit any car.

12 volt operation. New Hybrid circuit.

★ Small size.

★ 12 volt ope

★ New Hybric

★ Transistor

New Type

No Vibrator

★ T.C.C. Print ★ New Hybrid circuit.

★ Transistor output.

★ New Type Brimar valves.

★ No Vibrator, 12 volt H.T. & L.T.

★ T.C.C. Printed Circuit and Condensers.

★ Tuned R.F. stage.

★ Medium and long waves.

★ Permeability tuning.

★ 7in. ★ 4in. elliptical speaker.

Instruction Booklet giving full details, illustrations, dimensions, circuit diagram and shopping list 2/6 (returned if you order).

12-CHANNEL

TURRET TUNERS

Large selection, many by famous makers such as Cyldon, Brayhead, Plessey, Cossor, etc., all I.F.s. New and unused. Let us quote you for the model required. Examples: 33-38 mc/s., 37/6, 6-9 mc/s., 59/6, 9-14 mc/s., 59/6, 14-25 mc/s., 59/6.

OPEN ALL DAY SATURDAY

Early Closing

Thurs., I p.m.

(Both addresses)

C.R. TUBE BARGAINS

NEW AND UNUSED



FERRANTI, 12in. types T12/44 or 9in. type T9/8 and 4 v. heater.

LASKY'S PRICE Carr. & Insur. 12/6. 49/6

FERRANTI 17in. type TR17/10, 6.3 v .3 amp. heater. Brand new and unused LASKY'S PRICE Carr. and Insur. 12/6. \$6.19.6

16in. METAL CONE, famous make, type T901/A, 6.3 v., 0.3 amp. heater. £6.9.6 Carr. & Insur. 21/-.

17in. 90 degrees C.R. TUBES

Seconds but in perfect working order and guaranteed.

Carr. and insur. 12/6. 79/6

RE-GUNNED C.R. TUBES CHARANTEED FOR 12 MONTHS

& Ins. ...12/6 ...12/6 ...12/6 ...12/6 12in. round 14in. rect. 15in. & 16 round 17in. rect. 21in. rect.

TAPE

Look at these star features:-

- * Very latest Printed Circuit.
- * T.C.C. condensers.
- Amplifiers can be supplied fully assembled and connected to Deck.
- New Mullard valves; EF86, ECC83, EL84, EM34, magic eye, EZ80 rect.
- ★ Choice of speaker: 7×4, 8×5, 9×4, 63in., 8in. etc.
- * Collaro Studio or B.S.R. Monardeck Tape Deck.
- ★ Complete with Acos 39/1 Mike. Tape and Spool.

PRICES FROM

20 GNS.

25 GNS.

(B.S.R. deck) (Collaro deck) All components available separately.
Full details and shopping list post free on request.

Send for the Finest Components Catalogue

ever produced for the "ham" or service man.

OVER 100 PAGES, SIZE 8½in. × 5½in. COPIOUSLY ILLUSTRATED.

Price 2/- Post 6d.

Our latest 12-page "BARGAIN BULLETIN" free with each copy or available separately by post, price 6d.

SPECIAL OFFER!

Handsome contemporary style cabinet, polished veneer, dark walnut finish, complete with modern detachable legs with brass ferrules. Ideal for housing single or auto record player, tape deck and associated equipment. Overall dimensions. Height, including legs, 27in. Width 20in., Depth 15in. Length of legs, 10in. Motor board size, 15jin. x 14in.
Today's value at least £8.

Lasky's PRICE
Carr. & Ins. 15/-

LASKY'S F.M. TUNER

PRINTED CIRCUIT VERSION OF G.E.C. 912 " F.M. PLUS" TUNER FOR HOME CONSTRUCTION

Uses 5 valves, 2 germanium diodes and brand new T.C.C. condensers. The PRINTED CIRCUIT ensures that the I.F. and R.F.-amplifiers are extremely stable at maximum gain and results are consistent on

Circuit diagram and clear step-by-step instructions supplied. All parts available separately. ALIGNMENT SERVICE available.

20,000 VALVES IN STOCK

Mullard, Brimar, G.E.C., Mazda, Cossor, E.M.I., Philips, Pin-nacle, Telefunken, etc. Send for our latest Valve List.

Tygan and "Someweave." Any size

7 GNS.

CAN BE BUILT FOR (including valves)
Post free.

TRANSISTORS

P.N.P. Junction types. AUDIO, suitable for high gain and low freq. amplifiers, and for output stages up to 250 milliwatts. Double stages up to 250 innitives.
spot—yellow and green.
Each 5/-

R.F. suitable for medium and low freq. oscillators, freq. changers and I.F. amplifiers (1.5 to 8 Mc/s). Double spot—yellow and red Each 7/6

Type T81. Suitable for all audio applications. Each Post 6d.
One dozen 35/- post free.

Special prices quoted for large quantities.

0C44 15/-; 0C45 15/-; 0C70 8/6; 0C71 8/6; 0C78 15/- (Matched Pair 30/-); 0C73 14/-; 0C16 54/-

EDISWAN MAZDA TRANSISTORS. The very latest types. XB/102 10/-; XB/103 10/-; XC/101 12/6; XA/101 15/-; XA/102 17/6.

SPECIAL OFFER. Set of 7 Ediswan Transistors: XA/101, XA/102, 2 XB/102, XB/103, 2 matched XC/101. Price 79/6.

CRYSTAL DIODES. General Purpose GEX00, each 1/-. Per doz. 9/-. All other types in stock.

"GOLDTOP" POWER TRANSISTORS

All types in stock. Example:— V15f10P. Ideas for output stage of car radio, will give approx. 3 watts operating from 12 v. Each 15/- post free. Suitable Output Transformer for above, correct ratio, matched to 3 ohms, 9/6. Post 1/-. Driver Transformer, 9/6. Post 1/-.

RESISTORS. The largest stocks of all types, high stability, wire wound, carbon, vitreous enamel, minia-ture and sub-min. Millions in stock. Why buy unwanted assortments? We will send you the types and values you actually want.

SUB-MIN RESISTORS, ith watt, most values available. Each 3id. Per doz. 2/6.

5 milliamp METER RECTIFIERS. Specia offer of limited number at only Post 9d. 8/6

TRANSFORMERS.

Complete ranges in stock, mains and output, by Partridge, Gilson, Parmeko, Ellison, Elstone, Douglas, etc., etc.



TWO ADDRESSES FOR PERSONAL SHOPPERS

PADdington 3271/2. Few yards from Praed Street

42 TOTTENHAM COURT ROAD, W.1

Nearest Stn.: Goodge Street. MUSeum 2605

Please address Mail Orders and Enquiries to Lasky's Radio, Dept. W. 207 Edgware Road, London, W.2.



SEE OVERLEAF FOR MORE NEWS FROM LASKY'S RADIO

ADJUSTING SCREWS

Portable/Mobile ROD AERIAL V.H.F RADIO TELEPHONE METER TYPE W.S B44 MK2. VOLUME FUSE (10 AMP) OFF STAND BY ON REMOTE AF LOUD HAILER MICROPHONE L.T. 12 VOLTS ALEROPHONE HAND RECEIVERS HEADSEAL TRIPOD BATTERY COMMECTOR TWO BATTERIES

EXPORT ONLY
CRYSTAL CONTROLLED 60-95mc/s.

A modern 14-valve superhet receiver and AM transmitter using current series of B7g valves. Valve line-up: 2-CV136/7D9, 1-CV137/EAC91, 7-CV138/EF91, 4-CV416/6F17. Robust cast aluminium case includes 5in. loudpseaker. Internal vibrator pack (synchronous type) provides operation from 12-volt accumulators or vehicle or boat 12-volt supply, in fixed or mobile use. Available, less crystals and accessories, but with connecting plugs, ex-stock. Accessories and crystals for specified frequencies in the range 60-95 Mc/s can be supplied to order at extra cost.

Each unit is fully tested and in good condition. Price (including packing FOB London), £20 each,

Special quotation for quantities up to 500 sets.

50 MICRO AMP MOVING COIL METERS

Brand New & Boxed-Large Stocks available

Made on Government Contract by Famous British Maker

3lin. Square—800 ohms resistance. 4 Scales operated by lever "Set-zero"—

"0-3"—"0-30"—"0-300." Easily coupled to rotary range switch by cord or lever. Ideally suitable for transistor tester, output meter, volt-milliameter. Adjustable to work as centre-zero 25-0-25 μA.

A RANGE OF METER BOXES

Useful for all kinds of testgear, a quality job in welded steel, finished in grey hammer stoved enamel. Standard panel size $4\frac{1}{2}$ " x $7\frac{1}{4}$ ", available in depths 2", 3", 4" and 6".

UNDRILLED: 2'' 12/6: 3'' 13/-: 4'' 13/6: 6'' 15/-. With panel punched to take one 50μ A meter, add 1/6, or to take two meters 2/6.





Complete with data

ONE 19'6 (plus post) METER 19'6 (din U.K.)

TWO 35'- (plus post | l)- in U.K.)

SPECIAL PRICES FOR 100 LOTS

TEST GEAR COMPONENTS (LONDON) LTD

15 ARCANY ROAD, SOUTH OCKENDON, ESSEX TEL: SOUTH OCKENDON 2610



SELENIUM L.T. RECTIFIERS. Full wave, bridge connected. 12/18 v. 1.5 A. 4/3; 12/18 v. 2.4 A. 6/9; 12/18 v. 4 A. 9/9; 12/18 v. 5 A. 12/6; 12/18 v. 6 A. 13/6; 24/36 v. 1.4 A. 12/6; 24/36 v. 4 A. 22/6; 24/36 v. 15 A. 62/6. Please add postage.

L.T. TRANSFORMERS. For charging or models. All 200/250 v. primaries. 3.5, 9 or 17. 1 A. 9/9; 3.5, 9 or 17 v. 2 A. 14/3; 3.5, 9 or 17 v. 4 A. 16/6; 9 or 17 v. 6 A. 26/-; 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 v. 2 A. 18/6. 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 v. 4 A. 30/-. P/P 1/3.

I Megohm I% WIREWOUND RESISTORS. 10/- per doz.

6 VOLT AC/DC BUZZERS. 3/6 ea. P/P 6d.

CV. 320. Iin. C.R.T. 4 v. heater, 600-1 kv. anode. Boxed, 19/6 ea. P/P 1/6.

MARCONI TF. 340 OUTPUT METERS. Reconditioned, perfect order. £9/19/6 ea. P/r 7/6.

MARCONI TF. 373 UNIVERSAL IMPED-ANCE BRIDGES. Reconditioned to maker's spec. 0-100H., 0-100 mfd., 0-1 megohm, 0-100 Q. each on 5 ranges at 1,000 c/s., £35 ea.

MARCONI TF. 329 "Q" METERS. Range 0 to 500 Q. Frequency 50 kc/s to 50 mc/s. Re-conditioned to maker's spec., £65 ea.

CERAMIC SWITCHES. I pole 6 way, 2/6; 2 pole 3 way, 2/6; 4 pole 3 way, 2/6; 2 pole 12 way, 2B., 5/6; 3 pole 12 way, 3B., 7/6; 8 pole 5 way, 4B., 7/6. P/P extra.

DEAF-AID EARPIECES. ER.100, 250 ohm imp. 4/6; ER.250, 1,000 ohm imp. 7/6. P/P 6d.

MINIATURE JONES PLUGS AND SOCKETS. All new. 2 pin 2/6 pr.; 4 pln 3/6 pr.; 6 pin 4/- pr.; 8 pin 4/6 pr.; 12 pin 5/6 pr.; 18 pin 7/6 pr.; 24 pin 8/6 pr.; 33 pin 10/6 pr.

MINIATURE PYE COAXIAL PLUGS AND SOCKETS. Available male or female cable, per 2/6 pr.

7.5 K.V.A. AUTO TRANSFORMERS. 115/230 volts. Brand new, boxed, ex-U.S.A. £15 ea. Plus carr.

POST OFFICE TELEPHONE HANDSETS. Standard type, 12/6 ea. P/P 1/6.

A.R. 88 WAVECHANGE SWITCHES. 8 banks, 6 positions, complete with all screens. New, boxed, 17/6 ea. P/P 2/6.

AMERICAN HS-30 LIGHTWEIGHT HEAD-SETS. Res. 50 ohms. Extremely high quality. Brand new, 15/- pair. P/P 1/3.

SPRAGUE/MICAMOULD CONDENSERS. Highest quality, I mfd, 500 v. .01 mfd, 1,000 v. 6/- per doz. P/P 9d.

AMERICAN H.T. BATTERIES. Brand new. Tapped 90 v., 67½ v., 45 v., 22½ v., 5/- ea. P/P 1/6.

24 VOLT D.C. PUMPS



Self lubricating, capacity 60 g.p.h. at 30 lb./sq. in. Will operate O.K. on 12 v. 4 BSP inlet/outlet union. Only 15/6 ea. P/P 2/6.

FIELD TELEPHONES TYPE F.

Ideal for all intercom, systems. house, office. building sites, etc. Generator bell ring-ing, 2 line connection. Supplied with batteries and wooden carrying case, fully tested. telephone. 3/6

1,000 WATT MAINS ISOLATION TRANSFORMERS
230 v. primary, 230 v. secondary. Ex-Admiralty heavy-duty type. New boxed, 65 ea. P/P 10/-.

R.1155 COMMUNICATION RECEIVERS Standard Model Standard Model B. Frequency coverage 75 kc/s to 1,500 kc/s and 3 mc/s to 18 mc/s 75 kc/s to 1,500 kc/s and 3 mc/s to 16 mc/s on 5 bands. New improved geared slow-motion drive fitted. All receivers overhauled, aligned and tested. £8/19/6 ea. P/P 7/6. Combined A.C. mains power pack and audio output stage supplied 85/- extra.

BRAND NEW MEDRESCO HEARING

AIDS
Supplied fully tested and complete with earpiece, leads and battery pouch. Incorporates 3 sub-minlature valves and sensitive crystal mic. Only 32/6 each. Batteries 5/- extra.

125 kc/s -to 20 mc/s. As new condition. Supplied complete with valves and crystal but no calibration charts. Only £14/10/- ea. P/P 7/6.

FIELD TELEPHONES TYPE H. Ideal for all intercom. systems. Generator bell ringing, two line connection. Supplied complete with batteries, ready to operate, 62/6 each, P/P 3/6.

SPARES KIT FOR CR.100 RECEIVERS Contains 15 valves: 2-U50, 2-DH63; 2-KT63; 2-X66; 7-KTW61. Condenser and resistor packs. pots, toggle switch, output transformer, etc. brand new, 59/6. P/P 3/6.

R.C.A. LOUDSPEAKERS

High-quality 3 ohm speaker housed in black crackle metal case to match AR-88 or H.R.O. receivers. Supplied brand new and boxed, 45/- ea. P/P 3/6.

COLLARO STUDIO TAPE TRANS-SCRIPTORS

Latest 1960 model. 3 speeds, 17, 31 or 71. Fitted with 3 separate motors, digital counter, press-button switching, provision for fitting extra stereo head. Supplied brand new and guaranteed complete with spare 7in. spool, £12/10/- ea. P/P 3/6.

DON Mk. 5 FIELD TELEPHONES Ideal for all intercom. systems. Buzzer calling, 2 line connection. Housed in metal carrying case. Supplied complete with batteries, fully tested, 39/6 ea. P/P 3/6.

R.C.A. PLATE TRANSFORMERS Primary 200/250 v. 50 cycles. Secondary 2,000/1,500/0/1,500/2,000 v. 500 milliamps. Supplied brand new and boxed, £6/10/- ea. P/P 10/-

PARMEKO TABLE TOP TRANSFOR-MERS. Input 230 v. 50 c/s. Output 620/550/ 375/0/375/550/620 v. 250 mA, 5 v. 3 amp, 5 v. 3 amp, 5 v. 6½ x 5½ in. Brand new, boxed, 45/– ea. P/P 5/–.

12/24 V, D.C. MODEL MOTORS. Reversible. Brand new, 8/6 ea. P/P 1/-,

200/230 V. A.C. MAINS MOTORS. Made for hair dryers. New, 12/6 ea. P/P 1/3.

E.M.I. 50 : I MICROPHONE TRANSFOR-MERS, 4/6 ea. P/P 1/-

GERMANIUM DIODES. General purpose type, 6d. ea. High quality type equivalent to OA81, 2/- ea.

White TRANSISTORS. Red spot, 4/6 ea. White spot, 4/6 ea. Yellow/green, 4/6 ea. Red/yellow, spot, 4/6 ea. Y 7/6 ea. P/P 3d.

SPEAKER BARGAINS

2tin.	Perdio	3 ohm	17/6
2≟in.	Perdio	15 ohm	17/6
3in.	Plessey	5 ohm	15/6
3in.	Rola	3 ohm	17/6
4±in.	Plessey	3 ohm	15/6
5in	Goodmans	3 ohm	15/6
6tin.	Plessey	3 ohm	17/6
8in.	Elac	3 ohm	19/6
IOin.	R.A.	3 ohm	27/6
6 x 4in.	Plessey water	r 3 ohm	12/6
7 x 4in.	Plessey	3 ohm	15/6
8 x 6in.	Rola	3 ohm	17/6
10 x 7in.	Plessey	3 ohm	27/6
12 x 8in.	Plessey	3 ohm	49/6
8 x 21in.		3 ohm	17/6.
-			11,0.
All brand	new. Please	add postage.	

AMPHENAL IS PIN UNITERS. Brand new 3/6 pr., ditto 18 pin, 3/6 pr. P/P 6d.

4 POLE II-WAY METER SWITCHES, 4 bank, 6/6 ea. P/P 9d.

LEACH 12 V. DOUBLE POLE AERIAL CHANGEOVER RELAYS. 7/6 ea. P/P I/-.

SOUND-POWERED TELEPHONE HAND-SETS. Just connect with twin flex 'or complete telephone system. No batterles required, 15/- ea.

INSTRUMENT TRANSFORMERS. 240 v. primary. Secondary 220 v. 85 mA and 6.3 v. 3.5 amps. New, 9/6 ea. P/P 1/3.

CONTACT-COOLED RECTIFIERS. 125 v. 85 mA 3/9; 250 v. 50 mA 5/6; 250 v. 85 mA 9/-; 250 v. 75 mA, full-wave bridge, 12/6. P/P 6d. ea.

HOOVER ROTARY TRANSFORMERS. Input 12 v. D.C.; output 310/360 v. 30 mA. New, boxed, 12/6 ea. P/P 1/3.

PORTABLE PRECISION VOLTMETERS.

Brand new moving iron instruments by famous manufamous Housed manufac polished teak case 8in. mirror scale. 2 ranges, A.C. or D.C. 0 to 160 v. or 0 to 320 v. Accuracy within 2%, £5/19/6 ea. P/P 3/6.



E.M.I. LOW VOLTAGE POWER SUPPLIES, 200/250 vole Input. Output 6 volt 3 amp. D.C. Fully smoothed. Compact chassis contains potted transformer and choke, 2 electrolytics and metal rectifier. Brand new, 35/- each. P/P 3/6.

LOOK!

THOUSANDS OF BARGAINS AVAILABLE WHICH WE ARE UNABLE TO ADVERTISE IT IS WORTH YOUR WHILE TO PAY US A VISIT



BRAND NEW Boxed METERS.

METERS. Standard ing. Scale calibrated 0-100 microamps. 42/6 each. P/P. 1/3.

Also available 31 in. panel mounting 62/6 each.

MAINS PANEL NEON INDICATORS.
Chrome escutcheon, flying lead connections.
Available red, green or clear, 3/6 each. P/P. 6d.

ALUMINIUM CHASSIS. 18 swg. four sided, reinforced corners. All sizes 2½in. deep. 6 x 4in. 3/6; 7½ x 5½in. 4/6; 10 x 7½in. 5/3; 11½ x 7½in. 6/-; 13½ x 9in. 6/9. Post extra.

PARMEKO MAINS TRANSFORMER. Fine heavy duty job. Primary 0/110/230 volts. Sec. 350/0/350 volts 150 ma. 6.3v. 4 amps, 5 volts 4 amps. New, boxed, 32/6. P/P 2/-.

PRECISION WIREWOUND POTENTIO-METERS. Linear track, 3½in. dia. Available, 100 ohm, 500 ohm; lk, 2.5k; 5k; 10k; 25k; 50k and 100k ohms. All 10/6 ea. P/P I/-.

750 WATT AUTO TRANSFORMERS. Fine heavy Admiralty type. Tapped from 110 to 230 volts to give any spot voltage. 69/6 each. P/P. 5/-.

POTTED "C" CORE CHOKES. 16 H. 150 ma.; 20 H. 100 ma.; 16 H. 120 ma.; 20 H. 30 ma. All 10/6 ea. 5 H. 500 ma. 17/6; 10 H. 500 ma. not potted, 25/- ea. Post extra. FERRANTI POTTED FILAMENT TRANS-FORMERS. Primaries tapped 200/250 volts, 1, 6.3v, ct. 5,6 amp; 6.3v, ct. 4.8 amp; 63v, ct. 1 amp; 19/6 ea. 2, 6.3v, ct. 3.3 amp; 6.3v, ct. 1 amp; 19/6 ea. 2,6.3v, ct. 3.3 amp; 6.3v, ct. 1 amp; 15/6 ea.

POST OFFICE JUMPER LEADS. Screened twin lead fitted with two standard Jack plugs, 3/- ea. P/P. 9d.

MUIRHEAD PRECISION STUD SWITCHES. 4 banks, Each bank I pole 24 position. Heavy contacts. Only 17/6 ea.

ROTARY TRANSFORMERS. 12 vol input. Output 250 volts 80ma. 22/6 ea. 6 volt input, 22/6. P/P 2/6. 12 volt DC. Ditto

CHOKE BARGAINS. 4H. 22.5ma, 2/6; 5H. 60ma. 3/6; 5H. 200ma. 5/6; Collins 8H. 100ma. 8/6; Rich & Bundy 50H. 120ma. 12/6. Post extra. HEAVY "C" CORE TRANSFORMERS. 230 volt primary. 725/700/675/0/675/700/725 volt 500ma. 6.3v. 6 amp, 6.3v. 1 amp, 5v. 6 amp. New boxed, 72/6 ea. P/P 5/-.

FERRITE CORED LOOP AERIALS. Operative up to 2 mc/s. New boxed, 22/6 ea. P/P. 2/6. ADMIRALTY SLOW MOTION DRIVES. 180°, scaled 0 to 100. Fast and slow knob with lock and also flick mechanism for setting to fixed frequencies, new 7/6 ea. P/P. I/3.

24 AMP. VARIAC TRANSFORMERS. Primary 230 volts. Adjustable sec. from 185 to 250 volts. 24 amps. £12/10/0 each. P/P. 10/-.

"C" CORE POTTED L.T. TRANSFOR-MERS. Primaries all 230 volts.
1. 6.3v. 3 amp. 6.3v. 3 amp., 6.3v. 1.5 amp. 21/e a. P/P. 2/-.
2. 6.3v. 5 amp., 6.3v. 4 amp., 2 x 6 6.3v. 3 amp, 6.3v. 2 amp., 6.3v. 1.5 amp., 6.3v. 1 amp, 35/e ea. P/P. 2/6.

VALVE VOLTMETERS No. 2. A laboratory instrument at a fraction of cost. Five ranges A.C. and D.C. 1.5 v., 5 v., 15 v., 50 v. and 150 volts. Operation 200/250 volts A.C. Supplied as new, fully tested and complete with internally mounted H.F. probe. £17/10/- each. P/P. 10/-.

MINE DETECTORS NO. 4A.

Complete equipment comprises search head, amplifier, headset, control box, telescopic rods for search head, search head test unit, test measure and haversack.

Operation is from standard 67½/1½v. battery. The unit will detect ferrous or non ferrous metals to a depth of 24 ins. giving maximum signal but can be used at greater depths giving lower output. Ideal for tracing under-ground pipes or cables and any hidden metal objects. Fully waterproof.

Complete equipment supplied brand new in original transit cases complete with operating instructions. Price 39/6 ea. Carriage 10/-

HALLICRAFTER 6 VOLT VIBRATOR
POWER SUPPLIES. Magnificent units POWER SUPPLIES. Magnificent units housed in grey metal case and supplied with all necessary connectors, etc. Made for SX28, S27, S36 receivers etc. Output 300 volts 170 ma., fully smoothed. Supplied new boxed, 29/6 each. P/P 3/6.

AVO SIGNAL GENERATORS. Frequency coverage 95 kc/s. to 40 mc/s. Ideal for all general radio work. Supplied fully tested and checked. £7/19/6 each. Operation is from 2 v. and 60 v. batteries but original Avo mains units can be supplied at 19/6 ea. P/P 3/6.

FIELD TELEPHONES TYPES L.

ldeal for all intercom systems. House, office or building site. Generator bell ringing. Two line connection. Supplied complete with batteries, fully tested. As new, 59/6 ea.

8 RANGE SUB-STANDARD D.C. AMMETERS

AMMETERS
Ranges 1.5, 3, 7.5, 15, 30, 60, 300 and 450
amps. 8in. mirror scale. Housed in polished
teak case. Supplied complete with all shunts
and leather carrying case, £15 each. P/P. 7/6.

PHOTO VOLTAGE AMPLIFIERS

These special units contain a 1 microamp. Tinsley mirror galvonometer and a double selenium photo electric cell. Brand new, £9/19/6 ea., P/P. 7/6.

HIGH FIDELITY RECORDING TAPES

225 ft.	L.P.	***********	6/-		
600 ft.			12/-		
900ft.			17/-		
1200ft.	L.P.		19/6		
1200ft.			19/-		
	L.P.	******			
SPARE PLASTIC SPOOLS, 52in. 2/3; 7in. 3/6.					
New, Boxed, Guaranteed. Post extra.					
	600 ft, 900ft. 1200ft. 1200ft. 1800ft. STIC SPC	600 ft. std. 900ft. L.P. 1200ft. L.P. 1200ft. std. 1800ft. L.P. STIC SPOOLS,	600 ft. std		

COSSOR 339 DOUBLE BEAM OSCILLOSCOPES.



Operation 110 / 200 / 250 volts A.C. Time base frequency sweep 6 cps. to 250,000 cp.s. A mplifier bandwidth 10 c p s . t o 2,000,000 cps. Supplied in perfect working order fully tested, £IS ea., P/P.



HALLICRAFTER S-36A U.H.F. COM-MUNICATION RECEIVERS. This is the later version of the S-27. Frequency coverage 27 to 143 mc/s split on 3 bands, capable of receiving F.M. or A.M. signals. Circuit incorporates calibrated S meter, B.F.O., noise limiter, etc. Operation 110/ 230-v. A.C. Output for phone or speaker. Supplied reconditioned and in superb con-dition. Price £27/10/- each. P/P. £1.

NEW BLOCK PAPER CONDENSERS. NEW BLOCK PAPER CONDENSERS.
Nitrogol, Visconol types. 25mfd. 4kv 3/6;
25mfd. 7.5kv. 40/6; .25mfd. 10kv. 15/-; 1 mfd.
600v. 1/9; 1 mfd. 1kv. 3/6; 1 mfd. 2.5kv. 6/6;
1 mfd. 5kv. 15/-; 2 mfd. 400v. 2/6; 2 mfd. 600v. 4/6;
4 mfd. 400v. 3/6; 4 mfd. 600v. 4/6; 4 mfd. 1.5kv. 15/6; 8 mfd. 400v. 6/6; 4 mfd. 1.5kv. 15/-; 10 mfd. 1.5kv. 17/6;
22 mfd. 570v. 17/6. 32 mfd. 500v. 17/6. Post extra.

CRYSTAL MICROPHONES

Brand new and guaranteed

I. Hand or desk type with screened

ONLY 15/6 each. P/P. 1/-. Type 2. High fidelity stick type, metal cased and fitted with switch.

Supplied with screened lead and screened 2-pin connector. ONLY 37/6 each.

nector. P/P, I/→. Type I



POTTED TRANSFORMERS. 230v. primary. Secondary 350/310/0/310/350v. 220ma. Total of 6.3v. 13 amps.; 5v. 4 amps. 49/6 ea. P/P. 3J-. 110/230 VOLT AUTO TRANSFORMERS. 20 watt, 9/-; 50 w. 12/6; 150 w. 18/6. Post extra. 100 AMP. A.C. MOVING IRON METERS. 6in. scale. Moden type, flush mounting Ideal for switchboards etc., new, boxed, 65/-. P/P 3/6. "C" CORE E.H.T. TRANSFORMER. 230v. primary. Secondary 3,850v. 5.5ma. 4v. 2.5 amp. 4v. 1 amp. New boxed, 52/6 each. P/P. 2/6. JOHNSON VARIABLE INDUCTANCES. Large type 8in. x 2½In. Supplied brand new boxed, 22/6 each. P/P 2/-.

METER BARGAINS

20 microamp D.C. M/C flush rd. 2\frac{1}{2}\text{in.}

25 microamp D.C. M/C proj. rd. 2\frac{1}{2}\text{in.}

25 microamp D.C. M/C proj. rd. 2\frac{1}{2}\text{in.}

100 microamp D.C. M/C flush rd. 2\frac{1}{2}\text{in.}

100 microamp D.C. M/C flush rd. 2\frac{1}{2}\text{in.}

200 microamp D.C. M/C flush rd. 2\frac{1}{2}\text{in.}

1 milliamp. D.C. M/C flush sq. 2\text{in.}

1 milliamp. D.C. M/C flush sq. 2\text{in.}

30/0/30 milliamp. D.C. M/C flush sq. 4\text{in.}

30/0/30 milliamp. D.C. M/C flush 2\frac{1}{2}\text{in.}

rd. 59/6 49/6 42/6 62/6 29/6 29/6 22/6 25/ 69/6 32 6

rd. 120 volts D.C. M/C proj. rd. 2in. 120 volts D.C. M/C flush rd. 3½in. 1300 volt A.C. M/C rectifier flush rd. 2½in. 300 volt A.C. M/I flush rd. 2½in. 500 volt A.C. M/I flush rd. 2½in. 1500 1,500 volts electrostatic. proj. rd. 2½in. Postage extra

25/-25/-

8/6

25/-

Phone: GERRARD 8204/9155 Cables: SMITHEX LESQU 3-34 LISLE STREET, LONDON,

NE RADIO LTD

TOTTENHAM COURT RD., LONDON, W.1 18

MUSeum 5929/0095
ALSO AT: 162 HOLLOWAY ROAD, LONDON, N.7
NORth 6295/6/7
99 CHEAPSIDE, E.C.2. MON 6860
All post orders and correspondence to 162 HOLLOWAY RD., LONDON, N.7

Cheapside: 9 a.m. to 6 p.m. Mon. to Fri., Sat. I p.m. Holloway Road; 9 a.m. to 6 p.m. daily. Thurs. I p.m., Sat. 5.30 p.m.

Open: Tottenham Court Rd., and

If not stated, please add postage on orders under £1. Cash with order or C.O.D. (charges extra),

Our advantageous H.P. and Credit Sale Terms are available on any single item over £5. Your enquiries invited. Please print your name and address !!

CLYNE CATHODE RAY OSCILLOSCOPE

for Home Construction
A recent addition to our comprehensive stocks (37)of quality equipment for the con-structor. This is an exceptionally sound and robust instrument of the most versatile type, that will be a boon to the seriously minded amateur, serviceman or constructor. Specifications: 8-Range Time Base, switched from 20 c/s to 160 switched from 20 c/s to 160 Kc/s. Y-Plate Amplifier has a sensitivity of 50 mV. and frequency response of 20 c/s to 600 Kc/s with a gain of 150. A calibrating voltage of 6.3 v. 50 c/s. is provided. Employs ECR30 2½in. Cathode Ray Tube and 4 valves: 2/ECP80, 1/EP91, 1/6X5. Controls: X-Shift, Y-shift, Focus, Width, Brilliance, ON/OFF. Time Base Frequency (Fine), Time Base Frequency (Coarse). Sync. Selector. Sync. Amplitude, Y-input Selector. X-input Selector. Amplifier Gain. Operates from 200/250 v. A.C. Mains. All required components for the construction of this wonderful instrument, including comprehensive assembly instructions, available at a SPECIAL INCLUSIVE PRICE OF ONLY £12/19/6, plus 5/- c. and p. Attractive engraved ivorine Front panel, optional extra at only 10/6. Just arrived! Portable carrying case at 45/- extra.

NEW LOOK ECONOMY FOUR



THE R.C. 3/4 WATT AMPLIFIER

THE R.C. 3/4 WATT AMPLIFIER
Compare the advantages. Treble bass AND middle controls. For crystal or magnetic pickup. A.C. Mains 200/250 v. Valve line-up: 6/66T, 65G7 metal, 6X5GT. Negative feedback. Built on stove enamelled steel chassis, measuring only 8in. x 4in. x 12in. Four engraved cream knobs are included in the price of the complete kit with all necessary practical and theoretical diagrams at £4/51- only, plus 2/6 p. & p. or Instruction Book fully illustrated for 1/- post free. This amplifier can be supplied assembled. tested and ready for use at £5/51- plus p. & p.

bled, tested and ready for use at £5/5/-, plus p. & p.

Our very popular three-valve rectifier mains T.R.F. receiver is rectifier mains T.R.F. receiver is now available with a new De Luxe cabinet with polished Walnut finish and Cream trimming (as illustrated). Brlef Spec.: Valve line-up 6K7, 617, 6V6 and contact cooled rectifier. Ready drilled chassis, good quality Sin, loudspeaker, Special Denco Coils Covers Medium and Long Wavebands. Overall dimensions: 12in. x 6in. x 5in. high A.C. 200/250 v. Simple construction with guaranteed results. Easy to follow practical and theoretical diagrams supplied. All necessary components, down to the last nucl

(14)

cal diagrams supplied. All necessary components, down to the last nut and bolt, are offered at a SPECIAL INCLUSIVE PRICE OF £5/10/-, plus 5/- p. & p. Instruction book available separately 1/6, post free. Also available with plastic cabinet in IVORY or BROWN if preferred at ONLY £5/5/-, plus p. & p.

CLYNE RADIO **ELECTRONIC** ORGAN

(42)



available in book form at 15/- plus 1/6 p. and p. We shall be happy to forward a complete price list on receipt of a stamp. Please address all organ enquiries for the attention of Mr. L. Roche.

SUPER I-VALVE SHORT-WAVE



p. & p. Send 2/- for point-to-point wiring diagram and price list.

THE NEW LOOK RAMBLER PORTABLE

This wonderful little Medium and Long wave battery superhet incorporates IRS, IT4, ISS, 3V4 miniature valves, Sin. speaker and frame aerial. Housed in smart two-tone Red/Grey cabinet. All required components at the NEW LOW PRICE of £6/19/6, plus 2/6 p. & p.; LOW PRICE of £6/19/6, plus 2/6 p. & p.; or with the latest low consumption "96 range" valves at the NEW LOW PRICE of £7/7/-, plus p. & p. Uses all-dry batteries AD35 (1/6), B126 (9/-). Full descriptive instruction book, itemised price list, diagrams, etc., available separately at 1/6 post free.

(2) MAINS UNIT FOR ABOVE This into battery compartment. A.C. 200/250 v. All required components at ONLY 47/6 plus 1/6 p. & p. or assembled and tested at £3/5/- plus p. & p. (Also suitable for many other portables.)



CRY (19) 5000 BABY ALARM This highly efficient unit is simple to assemble, extremely sensitive and may be installed in a matter of minutes. Completely SAFE employing a double wound mains transformer. Attractively finished in Red and Grey (washable) "Lionide" with cream plastic escutcheon. Size only 7½ in his to supplied in kit form complete with mike at ONLY 72/6 plus 2/6 P. & P. or ONLY 72/6 plus 2/6 P. & P. or assembled and tested 89/6 P. & P. 6. Suitable mike flex available at 3d, a yard. Instruction book and price list separately I/- post free. A.C. 200-250 v.



THE "SUPERIOR FOUR" superior four-valve receiver mains 200/250 v. M. and Long waves. As with our very suc-cessful

my Four my Four " (6) all required components are supplied. Valve line-up: 2-6SG7's, 6X5GT and 6V6GT. Chassis ready drilled. Cabinet size 10½in. x 10in. wide. Maximum depth at base 5in. tapering to 3½in. at top. Sloping front. Very attractively finished in light walnut and peach. Each component brand new and tested prior to packing. Complete instruction booklet with practical and theoretical diagrams is pro-(6) instruction booklet with practical and theoretical diagrams is provided. Booklet available at 1/6 post free. Our price complete \$5,15/\text{.}\$. Please add 2/6 P. & C. If preferred, we can supply Cabinet Assembly only, comprising Cabinet and bracket, wave-change switch; dial pointer, drum, pulleys, drive spingle and known and the statement of t spindle, drive spring and knobs, at 45/-, plus 2/6 P. & C.

VISIT OUR FULLY EQUIPPED HI-FI SHOWROOM AT TOTTENHAM COURT ROAD FOR DEMONSTRATIONS OF THE LATEST

I-FIDELITY EQUIPMENT BY ALL LEADING MANUFACTURERS

We stock equipment of Quality by all leading makers:

i.e., Leak, Quad, Armstrong, Dulci, Ferrograph, Reflectograph, Vortexion, Linear, Wharfedale, Grundig, Goodmans, W.B., Rogers, Garrard, Lenco, B.T.H., Pamphonic, Simon, Brenell, Collaro, Telefunken, Fi-Cord, etc., etc. A full range of high quality cabinets to suit all purposes is on show, i.e., "RECORD HOUSING," "W.B." "A.D.," etc. Enquire about our interesting part-exchange scheme for personal callers. H.P. Available.

" FAMILY FOUR "

Our supersensitive T.R.F. Receiver for home construction. Covers Long and Medium Wavebands, and is housed in very smart plastic table



cabinet in Brown or Black. For A.C. mains 200/250 v. Comprehensive assembly instructions provided, in-cluding practical and theoretical diagrams, cluding practical and theoretical diagrams, which are easy to follow and will enable you to complete this receiver which will be the envy of your friends. ALL NECESSARY COMPONENTS ARE BEING OFFERED FOR LIMITED PERIOD ONLY AT THE REMARKABLE PRICE OF ONLY 79/6, plus 2/6 P. & P. In Pstruction book available separately if you wish to study before purchase at 1/6 post free.

THE CLYNE RADIO "DE LUXE" PRINTED CIRCUIT SUPERHET



A new two-wave band (L and M) Superhet using the latest miniature valves: ECH81, EF85 and ECL80,

(32)

(33)

plus contact cooled Rectifier. Incorpora-tes Ferrite Rod Aerial and Is of unit construction. Ex-nsitivity and selectivity. Outand Is of unit construction. Exceptional sensitivity and selectivity. Outstanding performance and quality T.C.C. condensers throughout. Easily constructed in one evening. Brown or ivory Bakelite or wooden Walnut finish cabinet. A.C. mains 200/250 v. All necessary components at special inclusive price of £7/19/6 plus 3/6 P. & P. Instruction Book with itemised price list available separately at 1/6 post free. Also available in De Luxe Cabinet (as "Economy Four" at 5/- extra).

SUPER PERSONAL POR TABLE. A wonderful little set that you can take anywhere. Ideal for camping. Detachable picnics. etc. picnics, etc. Detachable aerial rod supplied. Covers Medium waveband 200-500 metres. Can be built in approx. I hour. All necessary

approx. I hour. All necessary components available at the following SPECIAL INCLUS-IVE PRICES: I-valve version ONLY 35/- plus 2/- P. & P. Super 2-valve version ONLY 41/- Plus 2/- P. & P. Sender 2-valve version ONLY 5/- point-to-point wiring diagram and parts price list 2/- post free. Extra for use with the above DLR5 balanced armature headphones, 7/6 pair. 7/6 pair.

"PAGEBOY" 2-TRANSISTOR NEW ! POCKET PORTABLE

Completely portable—NO EXTERNAL AERIAL

OR EARTH REQUIRED. This is an amazing

OR EARTH REQUIRED. This is an amazing little receiver with built-in aerial and small enough to be held in the palm of the hand. Medium wave reception at wonderful volume. No fiddley tuning!

—condenser tuned | Supplied with drilled and colour coded components. Easily assembled with rhe assembled with the ald of the easy-to-

follow assembly instructions provided.

Total cost of all (45) necessary components, including transistors, whring wire and even solder ONLY 32/6 plus 1/6 P. & P. Battery 3/- extra. Ardente type deaf-aid earpiece complete with cord and plugs Plans 2/- post free. Callers welcome to hear this set demonstrated at any of our branches. Our reputation is your guarantee.

PRINTED CIRCUIT CAR RADIO

(for Home Construction). We are proud to be able to offer this New type Car Radio employing up-to-the-minute circuitry, special 12 volt valves and transistorised out-put stage. The highest degree of sensitivity is assured by the incorporation of Permeability Tuning and a tuned R.F. Stage. Covers Medium and Long Wavebands. NO VIBRATOR PACK IS REQUIRED. This is a really compact receiver that will fit any car. Comprehensive assembly Instructions are provided with all necessary components, including valves and transistor at a Special New Low inclusive Price of Only £11/19/6 plus 3/6 P. & P. Instruction booklet with itemised price list, full description dimensions, etc., available separately at 3/6 post free.

THE "WAVEMASTER" 7-TRANSISTOR LUXURY PORTABLE

400 MILLIWATTS OUTPUT
To build yourself Medium and Long waves—Push-Pull Superhet A.V.C. Perfect Car Radio reception. Size 10in. x 6\{\}in. x

het A.V.C. Perfect Car Radio reception. Size 10in. x 6\frac{1}{2}in. x 4\frac{1}{2}in. at base tapering to 4in. at top.

Very attractive two-tone grey Vynide covered cabinet with black and gold printed escutcheon plate, cream and gold knobs, handle and cabinet fittings. \(\text{Weight} \)—complete with long-life 7\frac{1}{2} volt battery—4\frac{1}{2}lb. \(\text{Mazda high-grade transistors throughout.} \(\text{High-Flux 7in. x 4in. Elliptical Speaker.} \(\text{Slow motion tuning.} \(\text{Co-axial socket at rear for direct connection to Car Radio Aerial.} \(\text{Improved reception by use of seven-section plated telescopic aerial disappearing into Cabinet when fully extended.} \)



when fully extended.

Construction simplified by Bakellte chassis board with the following components already mounted:
1.F. Transformers (3). Oscillator Coil, Trimmer Bank, Output Transformer, Interstage Transformer, Aerial Brackets and Earth Bar. SPECIAL INCLUSIVE PRICE for all required components, full assembly instructions—nothing more to buy—is £10/19/6 plus 3/6 P. & P. Alignment service available.

Full assembly instructions and Individually priced parts list, all of which are available. separately, 2/6, post free.

ALL PARTS AVAILABLE SEPARATELY

· · · · · · · · · · · · · · · · · · ·			
"PRACTICAL WIRELESS" POCKET SUPERHET	All		nstruction
All required Components for the Pocket Superhet as described	required		Book and
(in November issue of "Practical Wireless" now available at	components	P.	itemised
special inclusive price of £9/15/6 complete, including Printed	at special-		price list
Circuit. All items available separately, send stamp for list.	Inclusive	P.	available
(I) New Look "RAMBLER all dry s'het portable. NEW LOW	price		separately
PRICE		2/6	1/6
(2) "RAMBLER" Mains Unit (suits most portables)		1/6	9d.
(3) "ECONOMY FOUR" T.R.F. Mains Receiver	£5 5 0	2/6	1/6
(4) "ECONOMY FOUR" with New Look Cabinet	€5 10 0	2/6	1/6
(5) "FAMILY FOUR" (our new T.R.F. Receiver)	£3 19 6	2/6	1/6
(5) "FAMILY FOUR" (our new T.R.F. Receiver) (6) "SUPERIOR FOUR" (four valve mains receiver)	£5 15 0	2/6	1/6
(7) Standard JASON F.M. Tuner FMT1	£6 15 0	2/6	2/-
(8) Fringe area JASON F.M. Tuner FMF	£7 15 0	2/6	2/-
(9) JASON "MERCURY 2" Switched F.M. Tuner plus ITA/B.B.C.	c10 10 0	014	244
Sound	£10 10 0	2/6	3/6
(10) OSRAM 912 Printed circuit F.M. Tuner. NEW LOW PRICE	£5 19 6	2/6	2/6
(11) JASON "ARGONAUT" AM/FM Chassis	£15 5 0	2/6	2/-
(12) JASON "ARGONAUT" AM/FM Tuner	£13 19 6	3/6	2/-
(13) F.M. Power Pack (suitable for most tuners)		1/6	1/-
(14) R.C. 3/4 watt Amplifier (with Bass, Middle and Treble controls)	£4 5 0	2/6	i/-
(15) 2-amp Battery Charger	£1 16 6	2/6	3d.
(16) R.C. Transistor/Crystal Receiver ('phones extra)	. £1 1 0	1/3	3d.
(17) R.C. Super Transistor/Crystal Rec. (ditto)	£1 7 6	1/3	3d.
(18) R.E.P. 1-valve Battery Receiver	£2 2 0	2/-	9d.
(19) "CRY-BABY" ALARM (Baby Alarm)	£3 12 6	2/6	<i>y</i> -
(20) MULLARD 510 Amplifier (printed circuit) Ultra Linear Version (21) MULLARD 510 as above plus input selector and spare power	£9 9 0	3/6	1/6
(21) MULLARD 510 as above plus input selector and spare power supplies	€11 10 0	3/6	2/6
(22) "DE-LUXE" Printed Circuit Superhet		3/6	1/6
(23) " DE-LUXE " with New Look Cabinet		3/6	1/6
(24) JASON J.T.V. 2 Tuner	£13 19 6	3/6	2/6
(25) RADIO JACK	. 19 6	1/6	6d.
(26) MULLARD TYPE "C" Tape pre-amp. (27) JASON WII Wobbulator	£12 9 6	3/6	2/6
(27) JASON WII Wobbulator	£14 19 0	3/6	3/6
(28) JASON Valve Voltmeter EM10 (23 ranges) (29) NEW JASON F.M. TUNER FMT2 with built-in power supplies	£18 10 0	3/6	2/6
and cabinet		3/6	2/6
(30) NEW JASON FRINGE F.M. TUNER FMT3, as above	£10 19 6	3/6	2/6
(31) PULLIN Series 90 TEST METER	£5 19 6	2/6	1/6
(32) R.C. Super Personal Portable 1-valve (phone extra) (33) R.C. Super Personal Portable 2-valve (phone extra)	£1 15 0	2/6	2/-
(33) R.C. Super Personal Portable 2-valve (phone extra)	€2 0	2/6	2/-
(34) R.C. TRANSETTE 2-Transistor Personal Portable	£3 9 6	2/-	-2/-
(35) JASON EVEREST 6-Transistor 2-wave Portable		3/6	3/6
		5/-	10/-
(37) CLYNE Cathode Ray Oscilloscope	£2 19 6	1/6	1/6
(39) CAR RADIO, Printed Circuit, 5-valve S'het. NEW LOW		1,0	.,,
PRICE	£11 19 6	3/6	2/6
(40) JASON Audio Generator AGIO	£14 5 0	3/6	2/6
(41) JASON Oscilloscope OG10.	£22 10 0	5/-	3/6
(42) Super SHORT WAVE RADIO, I valve	£1 15 0	2/- 3/6	2/-
(43) "WAVEMASTER" 7-Transistor Luxury Portable(44) "GOLD STAR" De-Luxe I-valve Portable		2/6	1/6
(45) "PAGEROY" 2-Transistor Porket Portable ("phone evera)		1/6	2/-
(45) "PAGEBOY" 2-Transistor Pocket Portable ('phone extra) Instruction Books which contain full description, easy-to-follow practical wiring	diagrams theor	etical di	agrams item-
ised price lists, etc., are free of charge with all parcels but may be purchased sep	arately as shown	above.	
PLEASE NOTE:—A selection of the above items are described me	ore fully in thi	s adver	tisement!!

TURN OVER FOR MORE CLYNE BARGAINS-



THE COMPONENT

18 Tottenham Court Road, London, W.I. SPECIALISTS 162 Holloway Road, London, N.7.

99 Cheapside, London, E.C.2.

MORE CLYNE RADIO BARGAINS



CABY UNIVERSAL

TEST METERS
These pocket-size multi-range test meters are of excellent test meters are of excellent quality and cover all the most use-ful ranges (A.C. Volse, D.C.) useful ranges (A.C. Volts, U.C. volts, resistance and current). Supplied complete with test prods, instruction book and batteries. Model A.10 (2,000 ohms per volt) £4/17/6

Model B.20 (10,000 ohms per volt) £6/10/-.
Plus P. & P. 3/6 on each.
Fully detailed and illustrated

leaflet available on request

RECORD PLAYERS Full range at usual competitive prices. Interesting H.P. facilities E.M.I. 4-SPEED STEREO/MON-

E.M.I. 4-SPEED STEREO/MON-AURAL SINGLE RECORD UNIT. Complete with Stereo Head and Sapphire Styli. Brand New and Fully Guaranteed. ONLY £6/19/6 plus 3/6 P. & P. JUST ARRIVED! LATEST GARRARD MODEL 210. Four-speed manual or auto-matic. 10in. and 12in. records of same speed can be mixed in any order, wired for stereo, attractive white colour scheme. Price 10½ gns. white colour scheme. Price 10½ gns. plus 3/6 P. & P.

LATEST B.S.R. UAI4. Attractive appearance. Wired for stereo. Fully guaranteed. £7/19/6. plus 3/6 P. & P. B.S.R. UA8 STEREO/MON-Wired

B.S.R. UA8 STEREO/MON-AURAL. Few only at £7/19/6, plus 3/6 P. & P. Brand new Guaranteed. COLLARO CONQUEST. 4-speed. Wired for stereo. Brand new. £7/19/6, plus 3/6 P. & P. speed. Wired for stereo. Brand new. £7/19/6, plus 3/6 P. & P No. 38 AFV WALKIE-TALKIE. No. 38 AFV WALKIE-TALKIE. A wonderful offer. This famous trans-receiver unit, with relay operated SEND/RECEIVE switch covering 7.4-9 Mc/s band, range approx. 5 miles. Good condition. ONLY 22/6 plus 2/6 P. & P. per unit (less accessories). Quant export inquiries welcomed. AERIAL TUNING UNIT Quantity

unit tiess accessories). Quantity export inquiries welcomed.

AERIAL TUNING UNIT

ZA.0841. This well made ex-W.D. unit contains a host of useful components including: I mA. 2in. flush round M/C meter, I mA. Westinghouse full-wave meter rectifier, 5-pole 5-way heavy-duty silver plated wavechange switch. 3in. dia. silver plated rotary tuning findicator. 350 pF tuning condenser with insulated coupler and 3½in. calibrated dial (0-180 deg) etc. etc. Contained in strong metal carrying case 9in. x 9in. x 8in. with hinged lid. ONLY 27/6 plus 5/- C. & P.

A CONSTRUCTOR'S MUST

A CONSTRUCTOR'S MUST
The latest "Pifco" Instrument
Bit Soldering Iron
With integral Stand and built-in

Spot-light for illuminating work 200/250 v. ONLY 22/6. P. & P. I/6. SOLDER. New boxed 1 lb reels, 16 S.W.G. 50/50 at 8/6 only, plus I/- P. & P.

VIBRATOR PACKS. VIBRATOR PACKS. Limited quantity of both 6 volt and 12 volt types available. Output 300 volt. 100 m/a. Fully smoothed. Brand new ex-Govt. surplus. Price 35/ea., plus 2/6 P. & P. Please specify input voltage required.

(Mallory). Output 150 v. @ 40 mA. Complete with synchronous vibrator. Brand new. ONLY 12/6, plus 2/- P. & P.

BAKERS I2in. SELHURST 12in. BAKERS SELHURST LOUDSPEAKER. 15 ohms, 15 watt 30-14,000 cps. Brand new, 64/10/-. P. & P. 3/6.
12in. RICHARD ALLAN P.M. LOUDSPEAKER. 3 ohm speech coil. Brand new. Only 32/6 plus 2/6 P. & P.

DEAF AID TYPE EARPIECES.
Ardente Standard magnetic type
complete with lead and plug.
Only 12/6. P. & P. 1/-.

SUPER MAGNETIC RECORDING TAPE SPECIAL!!!

famous American Ferrodynamics "BRAND FIVE"

An enthusiast's "must."

SUB-STANDARD) High grade Acetate Base,
5in. 600ft. 16/-, 5in. 900ft. 18/6, 5\frac{1}{2}in. 1,200ft. 23/6,

7in, 1,200ft. 25/-, 7in, 1,800ft. 35/-. Extra quality Mylar Dupont. 5in. 1,200ft. 37/6. 7in. 1,800ft. 44/--7in. 2,400ft. 60/-. Each on plastic spool. P. free. Trade enquiries invited.

EXTRA SPECIAL OFFER !! A small three-valve PORTABLE RE-CORD PLAYER AMPLIFIER mounted on baffle 12 x 7in., with High Flux 61in. Loudspeaker. Valve line-up ECC83, EL84, Loudspeaker. Valve line-up ECC83, EL84, EZ80. Incorporates separate bass and treble controls. Max. output 3 watts. Will match all types of high impedance pick-up. Ready to use, £5/12/6. P. & P. 3/6. NEW STYLE CABINET finished in two-tone Leatherette. Will accommodate above Amplifier and Baffle without modification, also most types Will accomwithout modification, also most types of Ancillary Equipment. Overall size 18 x 13½ x 8½ in. Fitted with carrying handle, £3/9/6 plus 5/– P. & P.

NOTE. If both items purchased together they will be supplied at a special inclusive price £8/7/6 a special in plus 6/6 P. & P.



★ TAPE RECORDER CONSTRUCTORS ★
FOR THE CONNOISSEUR ★
COLLARO TAPE TRANSCRIPTOR MK. 4. 3-speeds, fitted with digital counter. List price £25. Our Price £17/10/-, P. & P. 5/-.
COLLARO TAPE PRE-AMPLIFIER AND BIAS OSCILLATOR. Complete with power pack for use with the above deck. 4 valve plus EM81 magic eye. II 0-240 v. A.C. Input sensitivity: mlcrophone socket 5 m/v., auxillary socket 500 m/v. Speed equalisation switch gives compensation at all 3 speeds. Full wiring instructions included. List price £21. Limited quantity only at £15/19/6. P. & P. 5/-.
LATEST COLLARO STUDIO TAPE TRANSCRIPTOR. 3 motors, 3 speeds, [4, 34, 74, 1-ys. takes 7in. spools. Push-button controls, £12/19/6 plus 5/- P. & P. Usual H.P. facilities.
LATEST B.S.R." MONARDECK." Single speed Tape Deck. Takes 54/10. spoils—34 i.p.s. At only £8/19/6 plus 5/- P. & P.

Takes B.S.K." MONANDECK." Single speed lape Deck. Takes \$\frac{1}{2}\in, spools—\frac{3}{2}\in, ip.s. At only \$\frac{6}{2}\in/3\in \text{for} \text{ & P.}

TAPE RECORDER AMPLIFIER—MANUFACTURER'S SUR-PLUS: Suitable for use with either of the above Tape Decks, and most other types. For A.C. mains, 4 watts output. 40-12,000 CPS at 7\frac{1}{2}\in\text{l.p.s.} \pm 3 db. Facilities for superimpose. Valves: ECL82, 12AX7, EM84, and contact cooled metal rectifier. Radiogram input, microphone input, volume control and separate treble and bass controls. Chassis measurevolume control and separate treble and bass controls. Chassis measurement 11½ x 3 x 4½in. Supplied complete with attractive grey/blue escutcheon plate finished in black and gold. Circuit diagram and connecting instructions Included. Price £10/10/- only, plus 3/6 P. & P. Limited quantity. If purchased with either of the above decks, both items post

ATTRACTIVE TWO-TONE PORTABLE CARRYING CASE Suitable for above amplifier and Collaro, Studio deck. Limited quantity only at 72/6 plus 3/6 P. & P.

only at 72/6 plus 3/6 P. & P.

MIC 45-1 Acos latest flat pistol-grip crystal microphone. Attractive black and gold finish. OUR PRICE 29/6 plus I/- P. & P.

ACOS MIC 39-1. Crystal stick microphone. List price 5 gns. Our price 39/6 plus I/6 P. & P.

MIC 40. General purpose crystal microphone with desk stand. Our price 25/- only plus I/6 P. & P.

M.C.24. Imported, crystal, attractive streamlined polished metal case; incorporates muting switch. List price 64/-. OUR PRICE 42/- only. I/- P. & P.

ANOTHER HAND MIKE BARGAIN! Lightweight crystal with built-in desk stand at only 19/6. P. & P. 1/-.



LIMITED IMPORT QUOTA ONLY! **OUTSTANDING BUY!**

MODEL U.I MULTI-RANGE TEST-METER. Ideal for amateurs and service engineers. Incorporates 3 inch rectangular meter. Ranges: A.C. and D.C. voltage. 0-10-50-250-500-1,000 v. D.C. current 0-100-500 m/a. 0-1 m/a. (used at 0-10 v. range). Resistance 1-2,000 ohms (centre 24 ohms). 100-200,000 ohms (centre 2.4 k.). Sensitivity 1,000 ohms per volt A.C. and D.C. Size: 5in. x 3in. x 2½in. Weight 22 ozs. only. Fully sugranged. Supplied complete, and ready to very low price of only (Bona fide trade enquiries invited).



18 Tottenham Court Road, London, W.I. 162 Holloway Road, London, N.7. 99 Cheapside, London, E.C.2.

COMPONENT SPECIALISTS

ALSO PREVIOUS

BERNARDS Latest Manual No. 167. "Eleven Tested Transistor Circuits, using Pre-Fabricated Circuit Units." Price 2/6, post free. Covers the use of the new Items listed below. TSL LP45F MINIATURE LOUD-SPEAKER, diameter 1\(\frac{1}{2}\)in., depth \(\frac{1}{2}\)in. High flux 9,500 guass, 150-15,000 cycles, 25/-, plus 1/6 P. & P.

TOROTOR TRANSISTORISED FM FRONT END (80-100 m/cs.). Completed with 2-OC171 VHF Transistors. Ready assembled, 79/6. Transistors. Plus 26/9 P.T.

Suitable set of 10.7 mc/s, sub-minia-ture IF TRANSISTOR Transformers (2 IF-I RDT) 27/6 per set, plus 1/6 P. & P.

SUB-MINIATURE DRIVER and Output Transistor Transformer 12/6 per pair, plus 9d. P. & P.

MINIATURE TRANSISTOR
Twin Gangs 196/87 pF. size approx.
Iln. x lin. x iin. 17/6, plus 9d. P. & P.
Set of Miniature Transistor IF and
OSC Coils (455 kc/s.). (3 IF and I
OSC), 21/-, plus 1/- P. & P.

3 WAVEBAND CONVERTER
TA-12401. With OC170 transistor
in emitter injected autodyne converter circuit. S.W., 5.9-13 Mc/s.;
M.W., 510-1,620 kc/s.; L.W., 150275 kc/s. Wavechange and on-off M.W., 510 275 kc/s. by four pushbuttons. Overall size 3.4 × 2.1 × 1.8in. 67/6. Plus 22/9 P.T.

TRANSISTORS!!!

SURPLUS P.N.P.
RED SPOT (Audio/Experimental

OCI69 VHF PNP JUNCTION
TRANSISTOR. Drift-type, Alpha
cut-off frequency 80 Mc/s. 18/- ea.
Attractive discounts for bulk purchases. The above is a selection only.
Full range in stock by all leading
manufacturers. Let us have your
enquiries (All POST ERFET) manufacturers. Let us ha enquiries. (ALL POST FREE).

FRUSTRATED EXPORT. Not repeatable! L., M. and S.W. SUPER-HET RECEIVER. Manufactured by McCarthy for export. At present for operation on 6 volts, but conversion details supplied free.



Valve line-up: 6K8G, 6K7G, 6Q7C 6F6G, 6X5G and 6 volt 4-pin non-synchronous vibrator. 8in. P.M. synchronous vibrator. 8in. P.M. Speaker, 4 watts output, P.U. socket Ext. L.S. socket, etc. Tone control. Fitted in pollshed wood cabinet, size 21½in. x 10½in. x 10½in. These cabinets are slightly soiled owing to storage, but each is guaranteed unused, in serviceable condition, tested prior to despatch. Price £5/19/6 only plus P. & P. 7/6, plus 27/6 for A.C. Mains Conversion Components if required. OUTSTANDING BUY!

ACOS GP73-2A: Turnover cart-ridge for Stereo and Monaural Standard and L.P. Few only at 29/6, also GP67-3 Mono at 18/-. Both plus 9d. P. & P. LOUDSPEAKERS, EX. CHASSIS.

As new guaranteed perfect, by leading manufacturers. Sin. 9/6; 6½in. 10/6; 8in. 13/6; also 10in. with O/P transformer (5,000 ohms), 17/6.

All 3 ohm speech coil, also Bin. available, in attractive cloth covered cabinet, ideal for extension speaker, 22/6. Each item plus 1/6 P. & P. Complete list of new speakers on request.



AVOMETER MODEL D

£8.19.6 (P. & P. 3/6)

D.C. Volts	A.C. Volts	D.C. Current	A.C. Curr
105 mV.	7.5 V.	15 m/A.	75 m/A.
300 mV.	15 V.	30 m/A.	150 m/A.
1.5 V.	75 V.	·150 m/A.	750 m/A.
3 V.	150 V.	300 m/A.	1.5 Amps.
15 V.	300 V.	1.5 Ampa.	7.5 Amps.
30 V.	600 V.	3 Amps.	15 Amps.
150 V.	750 V.	15 Amps.	
300 ♥.	1.5 KV.	30 Ampa.	Resistance
750 V.		_	0-1000 oh

0-1000 ohms 1.0 kv. 0-16 k o Thoroughly overhauled. Complete with batteric instructions. An extremely robust meter very reasonable price.

MOVING COIL PHONES. MOVING COIL PHONES. Finest quality Canadian with chamois ear-muffs and leather-covered headband. With lead and jack plug. Noise excluding and supremely comfortable. 19/6. Post 1/6. MATCHING TRANSFORMER (for HI impedance), i.e. for HRO, CR100, etc., with standard jack plug, 4/6.

SELENIUM BRIDGE RECTIFIERS. Funnel cooled. A.C. input 45 v. RMS. D.C., output 30 v. 10 amps. BRAND NEW. Boxed. 45/-. Post 3/6.

MARCONI IMPEDANCE BRIDGE.
Type TF373. Measures, L, C & R at
1,000 Cycles. Accuracy 1%. 0-100H;
0-100μF; 0-1MΩ each in 5 ranges. Power
Factor and "Q." First-class condition. Factor and "Q." First-class condition.

HALLICRAFTER VIBRAPACK. Input 6 v. output 300 v. at 170 mA. Designed for SX28 or S27. Size 6½ x 7 x 7in. BRAND NEW, BOXED. A real bargain at 29/6. Carr. 3/6.

ADMIRALTY HT TRANSFORMERS ADMIRALTY HT TRANSFORMERS Pri, 230 v. 50 c/s. Secs. 620-550-375-0-375-550-620 v. (620 and 550 v. 200 m/amps., 375 v. 250 m/amps.), plus two 5 v. 3 amp. rectifier windings. Total rating 278 VA. Upright mtg. Vt. 251b. Made 1953. BRAND NEW. Original boxes. 45/-. Carr. 5/-.

INSTRUMENT TRANSFORMERS. 1830 v. A.C. input. Outputs 0-65-130-195 v. 85 m/amps., 6.3 v. 5 amps., 6.3 v. 0.3 amps. Shrouded Size 3½ x 3½ x 3½in. high. 15/-. Post FREE.

MAINS TRANSFORMERS. Input 110-240 v. Output 345-0-345 v. 125 m/amps., 6.4 v., 4.5 amps., 5 v. 2 amps. 4\frac{3}{4} \times 4\frac{1}{4} \times 5\frac{1}{2}\times in, high. Wt. 12lb. Potted. Tag ends. RCA BRAND NEW. Boxed. 29/6, post 3/6.



TRIPLETT METER MOVEMENT

This article consists of a basic 400 microamp meter movement mounted on a Bakelite panel 53 x 27. The dial is scaled as a 15 range Testmeter. A circuit and parts list of the A circuit original instrument is supplied.

BRAND NEW. Boxed. 35/-, post paid.

QQV06-40 37/6

PVI-35 32/6, 2021 7/6, OC3 6/-, PTI5 12/6, CV51(Y65) 5/-, 6F33 5/-. BRAND NEW in individual cartons. Bulk enquiries invited

RECEIVERS R-1155B

A first-class 10-valve Communications receiver, covering 75 Kc/s, to 18 Mc/s, (16.2-4,000 m.) in 5 bands. The large scale and superior dual ratio slow-motion drive make tuning easy and the R.F. stage and 2 I.F. stages ensure world-wide reception. All the receivers we sell have been thoroughly overhauled, completely realigned and are in first-class working order. ONLY £9/19/6.

working order. ONLY £9/19/6.

A.C. MAINS POWER PACK OUTPUT STAGE. In handsome black crackled steel cabinet to match the R-1155. Fitted with RCA 8in. speaker. Just PLUG IN and switch on! Only the finest quality components are used and we guarantee OUR power packs for 6 months. ONLY £6/10/-. Deduct 10/- when purchasing receiver and power unit together. Send S.A.E. for further details or I/3 for 10-page illustrated booklet giving technical data and circuits etc. (FREE with each receiver). Add 10/6 carriage for receiver, 5/- for power unit.

RCA AR-88 SPEAKERS

A high quality 3 ohm unit fitted into heavy gauge black crackled steel cabinet, size 10½ x 11½ x 6in. Fitted with rubber feet and 6ft. lead. Ideal for extension speaker. CR 100, etc. In original cartons. BRAND NEW. 45/-. Post 3/6.

MINIATURE 373 IF STRIPS. For FM tuner described in "Practical Wireless." Complete with 3 of EF91, 2 of EF92 and 1 of EB91. A fresh release enables us to offer these once again. BRAND NEW. Complete reprint of conversion gain. BRAND NEW. Complete reprint of conversion astructions and circuit supplied free. 35/-. OR less valves, 12/6. Post, either, 2/6.

HRO SENIOR RECEIVERS



Complete with ALL NINE general coverage plug-in coilsets for 50 Kc/s. to 30 Mc/s. Instruction booklet, and circuit, but less external power supply unit. Table models, as new condition, 2I GNS. Packing and carriage 22/- extra. Send S.A.E. for further details.

HRO POWER PACKS: 115/230 v. A.C. mains input.

HRO POWER PACKS. 115/230 v. A.C. mains input. Tested, and in good condition. S9/6. Post 3/6.

LOUD-HAILER EQUIPMENT

IDEAL FOR CROWD CONTROL, FACTORIES, FETES, ETC. CON-SISTS OF 4 SPEAKER UNITS AND CONTROL UNIT. COMPLETE WITE MUROPHONE, HEADPHONES AND SPARES, OFFRATES FROM 12 VOLTS 1.0. (OR 6 VOLTS 1.0. WITH SLIGHTLY REDUCED OUTPUT) CONSUMING ONLY 3 AMPS. OUTPUT POWER S WATTS. ALL TESTED AND WORKING, BUT SLIGHTLY SOLLED. A GENUINE BARGAIN. 24/13/6. PARRIAGE 25/6.

T.C.C. VISCONOL CONDENSERS. 8 mfd. 800 v. D.C. wkg. at 71 deg. C. CP152V. Size 3 x 1\frac{3}{4} x 5in. high. BRAND NEW. Boxed. 8/6 each, post paid. 4 mfd. 600 v. wkg. CP 130T. 4/6 each, post paid.

M1052

GIANT COMPONENT PARCEL

Contains 100 and 1 watt resistors, 50 Hi Stab resistors, wire wound resistors, carbon and W/W pots, 100 capacitors (mica. paper, 8prague, blas, variable, etc.), valveholders, tag strips, metal rectifiers, sleeving, etc. All components are unused. GUARANTEED VALUE, 25/- plus

CHARLES BRITAIN (Radio) II UPPER SAINT MARTIN'S LONDON, W.C.2 TEMple LANE TEMple Bar 0545

Near Leicester Sq. Station. (Opposite Thorn House) Shop Hours: 9-6 p.m. (9-1 p.m. Thursdays). Open all day Saturday.



CRYSTAL CALIBRATOR No. 10 CRYSTAL CALIBRATOR No. 10
A crystal controlled heterodyne wavemeter covering 500 Kc/s. to 10 Mc/s.
(Harmonics up to 30 Mc/s.) Requires 300 V.
15 mA, and 12 V. 0.3 a. D.C., but can be
easily modified for 120 V. and 1.4 V. working. Size 7 x 7½ x 4in. Good condition,
complete with valves, crystal, instruction
manual and circuit. ONLY 59/6. Post 3/6.
This item available complete as above.
BRAND NEW and with spare set of
valves. £4/10/-, post 3/6.

CANADIAN CRYSTAL CALIBRA-TOR. Uses double crystal and multi-vibrator circuit to give "pips" at I Mc/s., 100 Kc/s, and 10 Kc/s. Incorporates Modulator. Handbook supplied. 79/6. Post 2/6.

ELECTROSTATIC METER. D'a. 6½ in. reads 5-18.5 Kv. Manufactured 1953. Contained in wooden case 10 x 10 x 9in. high. £9/19/6. Post paid.

SANGAMO WESTON ANALYSER E772. A useful multi-range meter. Thoroughly overhauled and in perfect working order. For full details see previous adverts. £7/10/-. Carr. 4/6.

MARCON! TF987/I NOISE GENERATORS. Range 100 Kc/s. to 200 Mc/s. Determines noise factor of AM and FM receivers. Fully stabilised H.T. supply A.C. mains operation. Brand new and in original boxes. £15. Carr. 7/6.

HEAVY DUTY SLIDER RESISTORS. 1.25 Ω 20 A., 12/6, post 3/6. $|\Omega|$ 12 A., 8/6. PRECISION RESISTORS. 1 Megohm. 1% I watt wire wound, Ex-U.S.A. BRAND NEW, 10/6 per dozen.

D.C./A.C. CONVERTERS. Input 12 v. D.C. Output 230 v. 50 c/s. A.C. at 135 watts. Fitted with 0-300 v. A.C. 2½in. meter and slider resistor for voltage adjustment. In stout wooden carrying case with lid. Perfect working order. adjustment. In stout wooden carrying case with lid. Perfect working order. £9/19/6. Carr. 10/6. 24 v. Input 230 v. A.C. 50 c/s. 100 watts output. In grey metal case. BRAND NEW. 92/6. Carr. 7/6.

RADIATION METERS. Portable dose-rate meter, containing modern type rectangular 50 micro-amp. meter, CVX.494. electrometer valve, etc. BRAND NEW. In canvas carrying case, £3/19/6. Post 2/6. For details of other equipment, see our previous adverts.

MICROAMMETERS

R.C.A. 0-500 microamps. 2‡in. circular flush panel mounting. Dials are engraved 0-15, 0-600 volts. As used in the American version of the No. 19 set. BRAND NEW. Boxed. 15/-.

American 0-100 microamps, 21in. square flush panel mounting. BRAND NEW. flush panel m Boxed, 42/6.

FERRANTI VOLTMETERS

VOLTMETERS N5.
0-300 volts, 25-100 c/s. Moving iron, 6in. scale. Fi. mtg. Hermetically sealed, grade IN. Made 1955. BRAND NEW. Boxed. 79/6. Post 3/6.



Each Model incorporates the highly success-ful HF/TR3 Amplifier (described opposite), thus ensuring truly "Hi-Fi" record and playback facilities.

~~~~ All prices quoted provide for the COM-PLETE RECORDER including CRYSTAL MICROPHONE and and 1-200ft. Spool of Tape.

There are no "better value for money" Tape Recorders on the market—if you can't call and hear them send S.A.E. for fully descriptive leaflets.

~~~~~



REFORE YOU BUY-YOU SHOU HEAR THESE RECORDERS—THEY ARE COMPARABLE TO THE MUCH HIGHER PRICED MODELS £39.10.0

MODEL CRE/S. Incorporates the new COLLARO "STUDIO"
TWIN "RAOK 3-speed Deck.
H.P. Terms: Deposit £7/18/- and 12 months of £2/17/11.
MODEL CRE/T. Incorporates the very popular 3-speed COLLARO
Mk. IV "TRANSCKIPTOE" Deck, which has both upper and lower tage tracks.

H.P. Terms: Deposit 29/10/- and 12 months of 23/9/8.

MODEL TR3/Mix. VI. Incorporates the New TRUVOX Mix. VI.

TWIN TRACK 2-spect Tape Deck.

H.P. Terms: Deposit 29/18/- and 12 months of 23/12/7.

£47.10.0

£49.10.0

_____ presented from MULLARD DESIGNS TAPE AMPLIFIERS and PREAMPLIFIERS

MODEL HF/G2A-D

A complete self-contained Tape Recorder chassis incorporating Loudspeaker and comprising the Model HF/G2A Amplifier connected to the Garrard Tape Deck. Operates at 3fln.] sec. speed and supplied fully tested and ready for immediate operation, designed for easy fixing into a portable case or cabinet, only four fixing screws being required. \$225.0.0

Complete working unit containing 4in. spool of Long Playing Tape.

H.P. TERMS: Deposit £5 and 12 monthly payments of £1/16/8. Alternatively we offer—Complete Kit of Parts HF/G2A Amplifier with the ASSEMBLED AND TESTED GARRARD TAPE DECK for

£22.0.0 H.P.Deposit: £4/8/- and 12 months of £1/12/3

The Amplifier, Model HF/G2A is available separately for:

£11.0.0

(a) Complete kit of parts £12.15.0 (b) Assembled



MODEL HF/G2P-D

THE IDEAL "LINK "TO ADD FULL TAPE RECORDING FACILITIES TO HIGH QUALITY HOME INSTALLATIONS, RADIOGRAMS, etc. Comprises the HF/42P Tape Pre-amplifier fitted to the Garrard Tape Deck, operates at 3½In./sec. speed, connects into the tape input or pick-up sockets of existing amplifier or Radio Chassis.

COMPLETE WORKING UNIT, containing 4in. spool of Long Play Tape. £23.15.0

Hire Purchase Terms: Deposit, £4/15/- and 12 monthly payments of £1/14/10.

Alternatively we offer—Complete Kit of Parts to build the HF/G2P Pre-amplifier with the TESTED \$20.15.0 Deposit, £4/3/- and 12 months at £1/10/5

The Preamplifler Model HF/G2P is available separately for

£9.10.0 (a) Complete kit of parts £11.5.0 (b) Assembled



Contains the UNIT (described HF/G2A-D Model HF/62A-D UNIT (described opposite). A small robust recorder with outstanding performance. Truly portable, weighs only 22lbs, Twin Track operates on 3\$in./sec. speed.

Price \$29.15.0

H.P. Terms. Deposit £6 and 12 months at £2/3/7.

MULLARD TYPE "C" TAPE-PREAMPLIFIER **ERASE UNIT**

The "H-F" link to add full tape recording facilities to High Fidelity home instillations. Incorporate FERROXCUBE POT CORE PUSH-PULL OSCILLATOR and 3-speed treble equalisation by FERROXCUBE POT CORE INDUCTOR. FOR WEARITE — COLLARO — TRUVOX — BRENELL OF MOTEK TAPE DECKS. Includes separate Power Supply Unit KIT OF PARTS £14.0.0

E £14.0.0 or ASSEMBLED. £17.0.0

H.P. £3/8/- Deposit and 12 months at £1/4/11.

(Excluding Power Unit £11/15/- and £14/10/- respectively).

MODEL HF/TR3 TAPE **AMPLIFIER**

(Muliard Type " A " design)
A very high quality Amplifier incorporat ing 3-speed treble equalisation, using the latest FERROXCUBE POT CORE INDUCTOR. FOR COLLARO-TRUVOX-BRE-NELL WEARITE or MOTEK Tape Decks, has GILISEN Output Transformer. Includes separate Power Supply Unit.



£25.10.0

£29.0.0

£30.15.0

£12.15.0 or ASSEMBLED. £16.10.0 H.P. £3/6/8 Deposit and 12 months at £1/4/2 KIT OF PARTS

FOR THE HOME CONSTRUCTOR SPECIAL "COMBINED ORDER" PRICES

£29,10.0

£26.10.0 £35,0,0

£32.0.0

£40.0.0

£36,10.0

£46.0.0 £43.0.0

£56.0.0

The COLLARO "STUDIO" TAPE DECK and our Mullard Type "C" PRE-AMPLIFIER and Power Unit assembled and tested (6)

assembled and tested
H.P. Terms: Deposit £5/18/- and 12 months at £2/3/3.
As above but Type "C" PRE-AMPLIFIER supplied as complete Kit of Parts
The COLLARO Mk. IV TAPE DECK and the MULLARD Type "C" PRE-AMPLIFIER and Power Unit assembled and tested...

H.P. Deposit £7 and 12 months £2/11/4.
As above but the Type "C" supplied as complete (d)

Rit of Parts
The TRUVOX Mk. VI TAPE DECK and the assembled
Type "C" PRE-AMPLIFIER and Power Unit.....
H.P. Deposit £8 and 12 months £2/18/8.

(f) As above but the Type "C" supplied as complete

Kit of Parts
The BRENELL Mk. V Deck and the assembled Type
"C" PRE-AMPLIFIER and Power Unit
H.P. Deposit £9/4/- and 12 months at £3/7/6.
As above, but the Type "C" supplied as complete Kit of Parts

The WEARITE 4A DECK with Type "C" assembled

and tested

H.P. Deposit £11/4/- and 12 months £4/2/1.

(Carriage and Insurance on above quotes 10/- extra)

THE ABOVE SUPPLIED IN PORTABLE CASE FOR £5/10/0 extra, THUS
FORMING A COMPLETE PORTABLE PRE-AMPLIFIER.

(d) COMPLETE KIT to build the HF/TR3 Amplifier, together with the COLLARO "STUDIO" DECK...
(b) As above but HF/TR3 ASSEMBLED and TESTED ...
H.P. TERMS: Deposit £5/16/0, 12 months of £2/2/6.
(c) COMPLETE KIT to build the HF/TR3 together with the Mk. IV COLLARO "TRANSCRIPTOR" DECK

STERN RADIO LTD.

TEPT. W. 109 FLEET ST.

Telephone: FLEET STREET 5812/3/4

FULLY DESCRIPTIVE LEAFLETS ON ALL OF ABOVE ARE AVAILABLE-BUT PLEASE ENCLOSE S.A.E. AND STATE WHICH LEAFLET IS REQUIRED.

£15,15,0

£21,10.0

£25.0.0

£21,10.0

£25,0.0

£31.0.0

£36.0.0

PARTS
Designed by MULLARD—presented by STERNS strictly to specification
MULLARD "5-10" MAIN AMPLIFIER OF



Alternatively we supply ASSEMBLED AND TESTED

£11.10.0

AROVE INCORPORATING PARTRIDGE OUTPUT TRANSFORMER £1/6/- extr

MULLARD'S 2-VALVE

PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard MAIN AMPLIFIER, but also perfectly suitable for other makes.

Supplied strictly to MULLARD SPECIFICATION and incorporating:

Squalisation for the latest R.I.A.A. characteristics.

Input for Crystal Pick-upe and variable reducatnee magnetic types.

Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier

Sensitive Microphone Channel

Wild range BASS and TREBLE Controls.

Sensitive Microphone Channe Price: COMPLETE KIT ETE KIT \$6.6.0

ASSEMBLED AND TESTED \$8.0.0

COMPLETE MULLARD 5-10 AMPLIFIER

The popular and very successful complete "5-10" incorporating Control Unit providing up to 10 watts high quality reproduction.

Specified components and new MULLARD VALVES are supplied including PARMEKO MAINS TRANSPORMERS and choice of the latest PARMEKO OF PARTICIOGE ULTRA Lincar Output Transformers.

Price: COMPLETE KIT. Parmeko Transformer. \$11.10.0

£13.10.0 Alternatively we supply ASSEMBLED AND TESTED.

Hire Purchase (Assembled Amp. only). Deposit 22/14/-, 12 months at 19/10. ABOVE incorporating PARTRIDGE OUTPUT TRANSFORMER £1/8/- extra.



MULLARD FOUR CHANNEL MIXING UNIT

mpiner vosates selt d. P. TEBMS: Deposit 27/4/- and 12 months of £2/12/- Carriage and insurance 7/6 extra.

Prices quoted are subject to £1/6/- extra for Partridge Trans

PRICE REDUCTIONS

(a) The COMPLETE KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-Stage Pre-Amplifier Control Unit.....

(c) The COMPLETE KIT OF PARTS to build the Dual Channel "3-3" Amplifier and the Dual Channel Pre-Amplifier Control Unit.

(d) The Duai Channel " 3-3 " Amplifor and th

(e) The COMPLET E KIT OF PARTS to build one "5-10" Main Ampilier (Parneko Trans-former) and the Dual Channel Pre-Amplifier Control Unit

(g) COMPLETE KIT OF PARTS to build Two
"5-10" Main Amplifiers (incorporating Parmeko
Output Transformers) and the Dual Channel
Pre-Amplifier Control Unit

(h) Two "5-10" Amplifiers (Parmeko Output Transformers) and the Dual Channel Pre-Amplifier Control Unit both Assembled and

(f) One 45-10". Amplifier (Parmeko Transformer) and the Dual Channel Pre-Amplifier both Assembled and Tested

H.P. TERMS: Deposit £5 and 12 months of £1/16/8.

Relf powered wth Cathode follower output .
Lucorporates Two inputs for CRYSTAL MICRO ...
PHONES, one for CRYSTAL PICK-UPS and a Fourth for Radio or Tape.

KIT OF SS.8.0 ASSEMBLED \$10.0.C

PARTS Depost \$2 and 12 mounts at 15/Model I.L. one microphone input matched for moving coil or ribbon mike \$1,17.0 extra.



COMPLETE STEREO AMPLIFIER Meets the many requests for a low priced but good quality Stereophonic Amplifier. Output power is 4 watts. Inputs for Crystal Pick-ups and Radio Tuner.

KIT OF PARTS....

£10.10.0

£9.18.9

£6. 9.6

£8. 7.6

£10.10.0

£10.10.0

£23.18.4

£18.7.6 £8.10.0

Our kit is complete to the MULLARD specification including supply of specified components, valves and PARMEKO OUTPUT TRANSFORMER. We also include switched inputs for 78 and L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. STEREO " 3-3" MAIN AMPLIFIER

Comprises two MULLARD 3-3 Main Amplifiers on one chassis. Operates with MULLARD STEREO PRE-AMPLIFIER. Output power 6 watts. Inputs for Crystal Pick-up and Radio Turner.

KIT OF PARTS £10.0.0 or ASSEMBLED.

Mk. II "Fidelity" FM TUNING UNIT

An attractively presented Unit incorporating MULLARD PERMEABILITY TUNING HEART and corresponding Mullard vaive line-up. Very suitable to operate with our Mullard Amplifiers.

FOR THE CONSTRUCTOR £10.10.0

or ASSEMBLED.

COMPLETE MULLARD 3-3 A VERY HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-VALVE 3-WATT AMPLIFIER DESIGNED IN THE MULLARD LABORATORIES.

Price for COMPLETE KIT
OF PARTS
(Plus 6/6 carriage and insurance).
Alternatively supplied ASSEMBLED AND
FULLY TESTED (Plus 6/6
E8.19.6

earriage and insurance)... £8.19.6

H.P. TERMS: Deposit 22 and 8 monthly payments of 21.

£14.5.0

SPECIAL CASH ONLY OFFER!

This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER, ALL FOR ONLY \$8.7.6 (plus 7/6 carr. and ins.). The Amplifier consists of a 2-stage design incorporating the 3 modern BVA valves and has separate BASS and TREBLE CONTRUES. The Portable Case with also accommodate almost any make of Autochanger and is attractively finished in Grey Colour Rexing—WE ALBU SUPPLY SEPARATELY:—

3. The 2-stage (plus Rexing—AMPLIFIED)

a) The 2-stage (plus Rectifier) AMPLIFIER (b) The PORTABLE CARRYING CASE £3 17 6 9

(c) 6}in. P.M. SPEAKER....



"Hi-Fi" LOUDSPEAKERS WE HAVE IN STOCK A COMPLETE RANGE BY GOODMANS—WHARFEDALE—W.B., ILLUSTRATED AND PRICED LEAFLETS ON REQUEST

THE "ADD - A - DECK" incorporating the NEW B,S,R.

"MONARDECK" & MATCHED PRE-AMPLIFIER

Thus providing full tape' Recording facilities

Carriage and Insurance 10/ -.

Carriage and insurance 10y-.
Deposit \$23/12!12 mths. \$21/8/2
12 mths. \$21/8/2
2 mths. \$21/8/



H.P. TERMS ARE AVAILABLE ON ALL EQUIPMENT OVER £9.
FULLY DESCRIPTIVE LEAFLETS ARE AVAILABLE FOR ALL
EQUIPMENT, BUT PLEASE SEND S.A.E.

£8.10.0 or ASSEMBLED ..

STEREO DUAL CHANNEL PRE-AMPLIFIER This model incorporates two 2-valve Pie-Amplifiers (described above) combined into a Single Unit enabling it to be used for both STERROPHONIC and MONAURAL operation. It is designed primarily operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 m/y.



Price: COMPLETE \$12.10.0 Alternatively ASSEMBLED &15.0.0 KIT OF PARTS H.P. Terms on assembled unit: £3 Deposit and 12 months of £1/2/-.

!! RECORD PLAYERS!! The LATEST MODELS are in Stock.

Many at REDUCED PRICES!!! Send S.A.E. for ILLUSTRATED LEAFLET

B.S.R. MONARCH UAS 4-spd. Mixer £6.19.6
Autochanger with Crystal Pick-up £7.10.0
The COLLARO OUNQUEST the page 57.10.0
The NEW COLLARO Model RP594, 4 speed Single Record Player, Studio Carticlar RO Model RO Mod

Studio Cartridge
The COLLARO 4-speed Single Record Player, incorporating the Studio
"O" Pick-m

"O" Pick-up
THE NEW B.S.R. Model UA12 is in stock. A 4-"SPEED" MIXER
AUTOCHANGER AUTOCHANGER
UA12 is also available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 records.
GARRARD RC210 4-speed Autochanger fitted with latest Crystal

Pick-up
The latest GARRARD TRANSCRIPTION MOTOR "301" with

The latest GARKARIJ TRANSCRIPTION BOUND 304 With Strobosopically marked turntable.

The new GARRARD Model 4HF High Quality Single Record Player fitted with the latest T.P. A. 12 Pick-up arm and G.C.S. Crystal Cartridge GARRARD Model TA/Mk, Il Single Record Player fitted with high output Crystal Pick-up, detachable head to the property of the William Country of the Cartridge of the Cartridge on all units 28/19/6 and over Cartridge and insurance on each above 5/- extra.

HOME CONSTRUCTORS 1 1

A RANGE OF "EASY TO ASSEMBLE" PREFABRICATED CABINETS
Designed by the W.B. "STENTOBIAN" COMPANY for "HI-Fi" Loudspeaker systems
or to accommodate high quality equipment. The acoustically designed Bass Reflex
Cabinets containing the very successful "Stentorian" speakers give really first-class
reproduction and are well recommended. Models are also available to accommodate
high-quality Amplifiers, Pre-amplifiers. Tuning Units, Record Players, etc. All models
are very easily assembled, in fact only a screwdrive is required.
Pully illustrated leafets are available, including complete specifications of the various
STENTORIAN LOUDSPEAKERS. Please enclose S.A.E.

T W 109 FLEET ST. LONDON, E.C.4 Telephone: FLEET STREET \$812/3/4

PROOPS Walk-around Store

52 Tottenham Court Rd., London, W.1 • Open 9-6, including Sats., Thurs. 9-1 • LANgham 0141

F. & S. PROOPS send

SINCERE XMAS GREETINGS to the hundreds of customers they never meet—and promise them that Proops advertising will stay reliable and Proops guarantees will hold good throughout 1961.

Tenadre and Proops guarantees will load good (modglood 1401)

RECEIVER TYPE 88 (R1475)

Highly stable, specially accurately calibrated, Marconi design, RAF communications receiver covering 2-20 Mc/s in 4 bands with built-in 600 kcs Xtal reference oscillator for checking dial which can be reset by special panel trimmer control. 11 Valves: 3x6K7, 6K8, 6J5, 3x6Q7, 6H6, Y63 tuning indicator and VR150-30 voltage regulator. Two stage IF with 8 tuned circuits, Xtal controlled B.F.O. Four position selectivity with audio filters for narrow bandwidth C.W. Fast and slow AVC, high and low noise suppression. A plug-in unit with additional mixer provides a "listening through" guard channel of either 2-4 or 4-7‡ Mc/s. Receiver 16‡ × 9 × 11in. Power pack 8 × 9 × 11in. Complete with 200-250 volt AC (or 12v. DC) power pack type 360, and operating and alignment instructions. Used, but in very good condition. Guaranteed serviceable. A sound

buy indeed at £13.10.0 carriage paid.

Double pole knife changeover switch on porcelain base. 2 for 5/-G.P.O. 230 volt mains, twin six inch gong, outdoor bells ... 33/6 Siemens high-speed relays. 1,000-0-1,000 ohm coils ... 8/6 Pyrex Aerial Insulators. Four 3in. OR two 8in. ... 7/6 U.S.A./British co-ax adaptors. Four for ... 5/-Neons. Ten 115 volt for 12/6; Six 80 volt for ... 7/6 G.P.O. mechanical counters. 0-9999 ... 7/6 33/6 8/6 7/6 5/-7/6 7/6

This is the attractive lightweight American Radio Altimeter that superseded the British version. A complete 14-valve radar set cover-ing 420-460 Mc/s it is ideal for conversion to radio control of models or 70 cm. work. It or 70 cm. work. It embodies three self-contained sub-units in separate aluminium detachable cases, follows:



A push-pull feed-back oscillator tuneable either side of 445 Mc/s. frequency modulated at 100 c/s by a particularly robust moving coil transducer. Two 955 high frequency acron valves. Case size only $3\frac{1}{2} \times 6\frac{1}{2} \times 2$ in. plus $2 \times 2\frac{1}{2}$ in. dia. for transducer.

RECEIVER

Tuneable to transmitter frequency. Size 3½ × 6½ × 2in. Two 9004 acorn valves.

AUDIO AMPLIFIER

AUDIO AMPLIFIER
Self-contained RC coupled 12SH7, 12SH7 and 12SJ7. Size 3 × 5 × 1 kin. Amplifies the received signal which is passed to detector circuit giving a D.C. voltage proportional to the difference between the transmitted and received (reflected) signal to operate internal relays which pass appropriate correction signals to autopilot and supply external indicator (5 mA meter). indicator (5 mA meter).

MAIN CHASSIS

The main chassis carries the 3 sub-units and has a further three 12SH7 one 12SJ7, two 12H6 and one VR150 regulator, three 1% wire-wound resistors, one 4-pole changeover relay, two SPCO relays, three twinganged pre-set potentiometers, trimmers, fuses, etc.

Power supply is derived from a 27-volt dynamotor (charging rate for 24 v supply) delivering 285 volts at 75 mA

BRAND NEW, a very useful buy indeed at only £2 plus 7/6 carriage.

MEGISTORS 125, 1,000 or 10,000 MEGohms

Glass encapsulated 10% tolerance high value resistors for minute grid current applications. Ideal for extending the range of sensitive meters or using in probes to provide a really high impedance input for VTVW's or 'Scopes. One of each value plus any chosen two, the 5 for 10/- post free by return.

HIGH QUALITY POWER PACK

Admiralty Rectifier Unit Design 95, totally enclosed in heavy gauge attractive light grey case size 11½ in. high × 6in. wide × 14in. deep. Admiralty ratings: transformer 400–0–400 at 50mA, 6.3v at 1 Amp, 5v at 3 Amp for 5U4G. Insulation tested to 3 kV. Two 350 olum 20 henry 80 mA chokes; Two 4 µF at 600v. ceramic terminal square canned paper smoothing capacitors. Double pole mains switch, two 2A fuses and two spares all in screw-in holders on front panel. 3 pin 250v. 50 c/s mains input, and 3 pin output with matching plug on short screened cable providing 650 volt D.C. and 6.3 AC with common earth. An unusually rest attractive, high quality unit, Brand New, still boxed

for only carriage paid

Attractive, lightweight, black crackle box $11 \times 7 \times 13\frac{1}{7}$ in. deep with $4 \times 2\frac{1}{7}$ in and $3\frac{1}{7} \times 3$ in. square windows on front panel for twin 5FP7 tubes. Neat arrangement of appropriate (independent) controls and variable scale illumination. Totally enclosed detachable magnetic focussing coils. All connections to rear sockets. Ideal TV monitoring unit as used by many amateurs. Used, but in very good condition, tubes guaranteed O.K. £1/10/0 carriage paid.



ANTENNA INDICATOR

Remote indication to within 1° on precision instrument type flush fitting black crackle indicator with 3in. dial calibrated in 2° steps plus the four cardinals. Simple D.C. wiring (6-30 volt) from specially wound potentiometer in sealed die cast housing with 4-incl 1-inch

drilled spindle transmits accurate signal of horizontal or vertical bearing. Brand New, Post Free

SCR.522 RECEIVER & TRANSMITTER CHASSIS

Receiver chassis 10/-. former) 15/-. Post Transmitter chassis (with modulation trans Post paid

These relatively small but really heavy duty generators were designed for a continuous output of 200 amps at 29 volts and are very successfully employed as a portable welding plant when driven from at ractor take-off pulley or separate engine as required.

Guaranteed fully serviceable.


carriage Only 10 . 15 paid.



robust aluminium face plate. Lightweight fibre and brass reduction gear to double ball bearing spindle terminating in miniature bevel

gear. Adjustment for varying speed. Jewelled bearings. Gold brushes. Brand New, post paid.

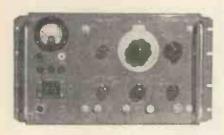PRECISION SIGNAL GENERATOR CT53. A modern laboratory standard instrument still



FEATURES

Vernier tuned, Triple screened, 6-Band coll turret covering 8.9 to 300 Mc/s with 72 ohm output from 100 mV down to 1µV.
 Precision decade ladder and silver slide wire attenuator calibrated in voltage and

Precision decade ladder and silver slide wire attenuator calibrated in voltage and 0-90db.
 Variable carrier level monitored by cathode follower and VTVM.
 CW or modulated 30% by 1,000 c/s Sine or Square wave (variable mark/space ratio).
 External mod. by sine wave from 50c/s to 10 kc/s. or pulses down to ½μ Sec.
 Seven B7G Valves, Potted "C" core transformers, Paper capacitors, Stabilised HT.
 Selected spare oscillator, pre-aged spare monitor, 100μA meter.
 Mains, HT, Bias and Filament supplies fully RF filtered.
 Combined cabinet/rack mounting case, Pressure sealed, Desicator, Panel Mains voltage adjustment, Triple fused, in fact, "the lot"!
 Offered straight from Service use, complete with calibration book, cables, circuit diagram and principal technical information, checked serviceable and fully guaranteed

and fully guaranteed Plus 15/- for careful packing and carriage

1-30A SIGNAL GENERATOR 100-156 Mc/s

Modern, portable, battery operated, 5 valve Signal Generator with alternative crystal or master oscillator, either optionally modulated by 1,000 c/s Hartley oscillator. Large directly calibrated dial with precision slow motion drive. Five step and variable attentuator. Supplied with matching black crackle carrying case for 6 and 135 volt batteries with 10ft. supply cable, and metal cased 1 mA. test meter for checking crystal resonance, etc. Brand new. £2/17/6 plus 7/6 packing and carriage.

1-95-A FIELD STRENGTH METER 100-156 Mc/s

Self-contained, tunable-input, valve-voltmeter with telescopic aerial and battery-fed diode rectifier and pentode amplifier for measuring field strength, presence of modulation, and approximate frequency of transmitter. Compensating circuit for state of 1½ and 45 volt batteries. In attractive black crackle case. Brand new.

£2/5/- plus 5/- packing and carriage.

D.C. GYRO & SERVO MOTOR

Beautifully engineered Minneapolis-Honeywell precision gyro, totally enclosed in sealed light-alloy housing about 8½in. cube. Automatic erection and precession correction. Large diameter Dessyn type transmitting potentiometers provide signals corresponding to the magnitude of the deviation of gimbal arms. Powerful D.C. motor coupled through a differential reduction gear to a 4in. spur driving gear integral with a 3in. dia. spiral groove cable driving drum. Two powerful solenoid clutches and corresponding brakes hold drum rigidly in position or set free for "neutral." Nominally for 26-volt operation, but operates at 12 volts. Size 10 × 6 × 8in. £10 each unit or £17/10/- pair, carriage paid.

£10 GEIGER COUNTER

Circuit embodes U.K.A.E.A. patent. Specially moulded case. Currently being supplied throughout the world. Three ranges—highly sensitive—light—portable—visual and audible response—plus output socket. Ideal for introduction to radiation measurement and nucleonic circuitry. Specially written 40-page instruction manual supplied. Batteries £2/15/3 extra.

KIT OF PARTS £4/17/6

Identical parts. Guaranteed performance Manual and printed circuit plates for battery pack supplied (assembled pack £2/15/3 extra). Fully illustrated assembly instructions. Spares and service permanently available.

hin. thick, moulded inset dielectric block. A highly recommended spares box buy at 7/6 each, post free. CHROMELIALUMEL THERMOCOUPLE LEADS

7, 10 and 21 foot lengths of flat twin lead—90% nickel, 10% chrome and 95% nickel, 5% aluminium. Total resistance 0.875 ohms. For use with millivoltmeter to read 0 to 1,000°C. Sheathed in heat resisting silicon rubber that will stand 200°C. Price, post paid, 7/6, 10/6 and 21/- respectively.

ROTARY RELAY. Superb, fast acting, brand new precision unit made by Price for RCA. Nominally 12 volt, but mighty lively on 6-volt supply. Two heavy duty single pole changeover contacts and one low current for external circuits, plus one break set that extends coil winding to reduce initial energising current to 50 mA. (at 6 v.) for holding. Solid milled armature, laminated steel frame, $2\frac{1}{2} \times 2\frac{1}{2}$ in.

VARIABLE SPEED HYDRAULIC GEARBOX

VARIABLE SPEED HYDRAULIC GEARBOX

This specially made oil-filled caseing houses a hydraulic torque conversion unit originally precision made by Westinghouse from high quality materials for the U.S. Government at an acquisition cost exceeding £150 each. Highly suitable for lathe head drive, workshop variable speed power take-off, etc.

Basically the unit is a back-to-back mounted, oil submerged, variable displacement hydraulic pump (input shaft) feeding a reversible hydraulic motor (output shaft) so that variation of the pump displacement by manual control gives very fine selection of output speed from zero up to 6% below input speed while a changeover valve in the supply lines to the motor provides instantaneous reverse at any speed. Recommended intput speed 500-1,000 r.p.m., maximum power 1½ h.p. Both shafts §in. dia. with Woodruff key.


Tested and fully guaranteed, supplied complete with technical data and performance curves for the remarkable price of £16 only, carriage paid.

NOMOTRON DECADE COUNTER TUBES

STC Type G10/241 latest type cold cathode, gas-filled, single pulse, uni-directional decade counter which illuminates numerals on tube face. Operating range—20 kc/s. Cathode output 40 volts, 3.7 mA. HT supply 310 v. plus. Applications include: tachometers, counting and batching, frequency and time measurement, direct operation of electro-magnetic relays, sequential monitoring of up to 10 different waveforms, etc. Brand New, complete with special base and Instructions.



Neat, modern indicator unit especially suitable for quick conversion to attractive general servicing scope. (Suitable circuit diagram and all component values supplied.) Contains fully mumetal screened 3BP1 tube, intensity and focus controls, 3-position rotary switch 8 pre-set, potentiometers, plus and 2×6SH7, 2×6H6, 6G6, 6X5 and 2X2 valves. Designed for 24 v. D.C. or 400 c/s A.C. input. Size 14 × 8½in. square. Well known and deservedly popular buy. Offered new, less (unwanted) motor driven aerial 50/switching unit, for post paid.

 

New 200-watt D.C. to A.C. rotary inverters in sound-proof cabinet. £9/10/carriage paid.



EVERETT EDGCUMBE SYNCLOCKS

Grade 1 industrial process timer with 3 inch dial covering 3 to 10 minutes in one tenth divisions. Driven by a 16 volt 50 c/s synchronous clock. A metal rectifier provides D.C. to pull in a relay that engages the drive until the time set on the dial elapses. As it reaches zero heavy duty contacts snap shut to close the external circuit (at the same time other contacts break to arrest the clock). Switching off the power trips the relay and the spring loaded dial returns to the time set ready for the next cycle. Whole totally enclosed in a heavy cast wall mounting case, stove enamelled black, size 61 × 7 × 4 inches. Brand new in original packings **55/-** post paid.


VENNER TIME SWITCHES

Type T.S.2, first grade precision time switches as supplied to G.P.O. Comprises absolutely silent self starting 250 volt 50 c/s synchronous clock, mechanism totally enclosed in heavy gauge brass case. Central drive takes detachable dial that revolves to operate sensitive on and off trips for external mains operated circuit. Self contained clock is easily detachable from rear mounting panel (self starting down to 80 v. and keeps running down to

Brand new, in original packings, and with dial and adjustable stops, post paid. 37/6

PROOPS

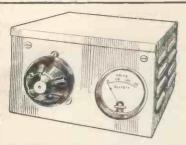BROTHERS LTD., 52 Tottenham Court Road, London, W.I. Head Office and mail order enquiries LANgham 0141 Shop hours 9 a.m. to 6 p.m. Thurs. 9 a.m. to 1 p.m. OPEN ALL DAY SATURDAY



BRAND NEW VARIABLE VOLTAGE TRANSFORMER. 230 volt A,C. input. Fitted in steel hammer finish case complete with 0-300 volt M,C. A,C. Meter, fuse and neon Indicator light. Output constantly variable from 0-270 volt A,C. Type 1. 2.2 amp. Price £8/10/-, carriage 10/-. Type 2. 5 amp. Price £12, carriage 10/-.

BRAND NEW VARIABLE VOLTAGE TRANSFORMER. For 230 volt A.C. input. In cases exactly as above with meter, fuse and indicator light. Output constantly variable from 0-230 volt A.C. Type 15. 15 amp. Price £22/10/-. Carr. 15/-.

W. W. RHEOSTAT. New. 3.5K or 5K. 25 watts. Price 7/6. P. & P. I/6.

NEW WIRE WOUND RHEOSTAT ON CERAMIC. 58 ohm. 50 watt, complete with instrument knob. Price 8/6. P. & P. 1/6.

EX P.O. MAGNETIC COUNTER. 500 ohm type for 24 volt also 3 ohm type for 6 volt D.C. operation. Price 6/6 each, P. & P. I/-.

AUTO TRANSFORMERS. Step up, step down, 110–200–220–240 v, Fully shrouded, New, 300 watt type £2/2/- each, P. & P. 2/6. 500 watt type £3/3/- each, P. & P. 3/9. 1,000 watt type £4/4/- each, P. & P. 6/6.

HEAVÝ DUTY L.T. TRANSFORMER. Very conservatively rated for continuous duty. New. In manufacturer's cases. Input 110-260 volt multi-tapped. 50 cycles, single phase. Output 28-29-30-31 volts at 21 ampere. Price £6/15/-, carriage 10/-.

GALVA-NOMETERS. Solid brass, 3in. dial, in polished wooden case. 70 degree scafe, 35 mA either slde. 100 ohm coil. Price 12/6 each. P. & P. 1/6.

EX R.A.F. AIR DICATOR, containing

taining 3 ball and plate infinitely varia-ble resolving gears, miniature spur bevel and worm gear drives, also toggle, push button and rotary switches, repeater motor, 4 mechanical counters, miniature lamp holders and lamps etc. As new. Illustration below. Price 22/6. P. & P. 3/6.



OTA R SWITCH REGU LATOR, 25 ohms. very conservatively rated at 4 amp., will handle 8 amp. Overall size 7 x 8 x 6in. Price 15/-. 6in. Price P. & P. 2/6.



EVERSHED AND VIGNOLES "WEE MEGGER." 500 volt in brand new leather case. Guaranteed perfect. Price £13/15/-. P. & P. 2/6.

A.R.B. U.S.A. RECEIVERS. 24 volt. Covering 195-9,050 k/c. in 4 bands. As new, suitable for use on boats, etc. Price £6 including car-

HIGH SPEED RELAY. Siemens. Two bobbins 1,000 ohms each. New, 10/6 each. P. &

18-WAY P.V.C. COVERED 14/36 WIRE, screened overall, covered with P.V.C., all colour coded, 3/6 per yd.; £15 reel of 100 yds. Carriage paid.

BRAND NEW FREQUENCY manufactured METERS by Nalder & Thompson Ltd. Calibrated 45 cycles to 55 cycles per second. 6in. dial. Panel mounting type. In original manufacturer's boxes. PRICE £10/15/- ea. Postage 3/6.



20 WAY STRIP containing standard Post Orfice telephone Jack Sockets, overall size 11 x 3½ x ½in. New. Price 15/- each. P. & P. 1/6.

10 WAY STRIP standard Post Office telephone Jack Sockets, spacing allowing Igranic Jack Plugs. New. Price 10/-. P. & P. 1/6.

19-INCH RACK MOUNTING 20-WAY P.O. JACK STRIPS with 40 terminals at rear. Price 25/-. P. & P. 3/6.

19-INCH RACK MOUNTING 20-WAY P.O. LAMP STRIPS. Price 25/-. P. & P. 2/6. LATEST MOST MODERN TYPE OF EX

W.D.MINIATURE HEADPHONES. As illustrated. Brand new, low impedance. Price: 10/6 plus P. & P. 1/6.

MOVING COIL HEAD. Complete

with Tannoy carbon hand microphone, with plug suitable for No. 19 set. Price: 12/6 each, plus P. & P. 2/-.

D.C. AMP-LIFIER, as new, for operation on 12 v. car battery, 10 watts undis-

watts output, with 6L6 valves in push-pull. Mike/ Gram. input, tapped output 7½, 15, 62, 10, 69/17/6 each. Carr. 15/-. CIN D 0 tap-1, 15, 62, 100, 250 or 500 ohms.

PYE LEVER OPERATING MICRO SWITCHES. Single pole change over. Brand new. 4/- each or 42/- dozen, p. paid.

VARIABLE VOL-TAGE TRANS-FORMER. "BERCO." Brand new in manufacturer's boxes. For 110 volt A.C. Input, Constantly variable from 0-135 volts. 2.2 amp. type. £4. P. & P. 3/-. 5 amp. type £6/10/-. P. & P. 3/6.





E L L I O T T SWITCHBOARD M O U N T I N G PEN RECORDER. PEN NE. 1 mA. 2‡in. chart. 1 mA. movement. 2 speed Complete with pen, and charts. Recondicharts. Recondi-tioned as new and guaranteed. Limited quantity. Price £55, carriage 10/-.

ATE TRANS FORMER of very best U.S.A. make, brand new, origi-nal manufacturer's cases. Input tapped at 190/210/230/250 at 190/210/230/250 • Output 2250-0-2250, centre tap-ped 400 mA. Nett weight 76lb., size 13in. x 9in. x 6½in. Price £6/10/- each, plus carr. 10/-



NEW UNCHARGED UNCHARGED UNFILLED

unspillable plastic cases. Comprises 6 x 2 y, separate cells connected by terminal strips. 6 × 5½ × 4½in. over terminals. Price 19/-, plus P. & P. 2/9.



245 AMP. 2 VOLT ACCUMULATOR. Admiralty type in wooden casing. Size 15 x 7½ x 7½in. Weight 60lb, Unfilled, uncharged. New. Price £4. Carriage 10/-.



MINIATURE P.M. MOTOR. 12/24 volt, re-e. lain. rersible. dia. New. Price 10/6 each. P. &

AIRCRAFT CINE CAMERA G45B Mk. III.



Fully modified, fitted with f/3.5 triple anastigmatic lens, takes 25ft. of 16 mm. film, fitted with 24 v. motor. 16 exposures

per sec. Brand no each. P. & P. paid. Brand new, original packing, £4/10/-

SERVICE TRADING COMPANY-

SLIDER RESIST. ANCES. 2 amp. 500 ohms, size 14in. x 6in., plus handle 6in., 27/6. P. & P. 6in., 27/6.





SOLENOID OPE-RATED RELAY.

Type 5CW/3945, 4 pole changeover, 10 A contacts 24 v. operation. Brand new 13/6. P. & P. 1/6.

CARPENTER'S TYPE POLARISED RELAYS. 2× 9,500 turns at 1,685 ohms. Price 22/6 each. P. & P. 1/-

Carpenter's similar to above. but type 5A48. Coils 1 x 3200 turns at 100 ohms and 1 x 2000 turns at 145 ohms, 22/6 each. P. & P. I/- Bases for same 2/6



SIEMENS H.S. RELAY. Ver latest type, sealed. H96E. 1,700 ohms plus 1,700 ohms, single C.O. contacts. Brand new with fixing clip. In maker's cartons, Price 16/6 each, plus 1/- P. & P.

Siemens sealed similar relay to above, but 2.2 ohms plus 2.2 ohms. Minus clips, 12/6 each. Plus 1/- P. & P.

SUPERIOR BRAND NEW RELAY. 7,000 ohms coil. Will pull in at 750 microamp, and out at 450 microamp. Change-over, platinum contacts. Vacuum sealed, will therefore not be affected by oil, moisture or water and never needs adjusting. Weight 2½ oz. Price 18/6. needs adjusting. P. & P. I/-.

MINIATURE MOVING COIL DIFFER-ENTIAL RELAY. Two coils 350 ohms each.



Operating current minimum 140 micro-Current amp., nominal 400 microamp, maximum

8 milliamp. One pole two way, or, centrer stable. Two contact current 100 mA at 50 V. A.C. or Size 1½ x ½ x ½in. Price 22/6 each.

G.E.C. SEALED RELAY. Type M.1090. 180 ohms coil. 6/12 volt. 4 C/O. Brand new. 18/-. P. & P. I/-.

G.E.C. SEALED RELAY.
670 ohms coil, 12/24 volt.
equipment. Unused. 10/-.
P. & P. 1/-.

G.P.O. 600 TYPE RELAY. 400 ohms coil. 24 volt. 2 C/O plus 2 M. New 7/6. P. & P. I/-.

MINIATURE OPEN TYPE RELAY. 700 ohms coil. 24 volt. 2 C/O. Ex new equipment. Unused. 7/6. P. & P. I/-.

ROTARY RELAY. 12 volt. Heavy duty change-over contacts and one low current for external circuit, plus one break set. Price 7/6. P. & P. 1/6.



MINIATURE UNISELECTOR SWITCH. Two banks of ten plus home contacts one bank continuous of normal. 30 ohm coil for 24 volt operation. Brand new, manufacturer's packing. Price 22/6 each. P. & P. 2/6. As illustrated.



MADE GEARED MOTOR BY DRAYTON REGULATOR CO., for 230 volt 50 cycles A.C. TYPE R.Q.R.,

versible. 37 r.p.m., overall size 5in. x 4in. x 5½in. Weight 4in. x 5½in. Weight 4½ lb. Ex brand new equipment. Unused. Price £3/17/6. P. & P. 3/-.

PRECISION

SOLAR OIL-CON-FILLED DENSER. 240 mfd. for 230 V.A.C. or 600 volt D.C.

Overall size 14in. x 9in, x 5½in, plus feet. Weight 46 lb. Brand Guaranteed perfect. Manufacturer's packing. Price £7/10/-, carriage 10/-



DIAL THERMO-METER. Made by Short & Mason, Calibrated 0-160 degrees Fahrenheit. 4½in. Fahrenheit. 4½in. dial. 6in. rim for flush mounting with 6in. long rod pro-truding at the back. Brand new. Manu-facturer's packing. Price 22/6. P. & P. 3/-.

SPECIAL OFFER. LIMITED QUANTITY.

GENERAL PURPOSE
CATHODE RAY OSCILLOSCOPE
The famous model 160-B.C.R. 'Scope..manufactured by R.C.A. of U.S.A. Best general purpose instrument of its kind, complete with 6in. cathode ray tube. Unused, guaranteed perfect. For operation on 110 v. A.C. Price £22/10/-. Carr. 10/-.
Step-down transformer to enable the above to operate on 230 v. Price 19/6.

BRAND NEW SOUND POWER OPERATED EX-ADMIRALTY. HEAD AND BREAST SETS. Two such sets connected up will provide perfect intercom., no batteries required. Will operate up to ½ mile.

Original manufacturer's boxes. Price 17/6 each, plus P. & P. 2/-; or 32/6 per pair. P. & P. 3/-.



MUIRHEAD PRECISION, bank, I pole, position Stud bank. Switch, Brand new. Price 12/6. P. & Price 12/6. P. 1/-.

MIDGET ROTARY TRANS-FORMERS

24in. dia. x 45in. Input 11.5 volt. Output 310/365 volts at 30 mA. Brand new. 12/6 each. P. & P. 1/6.

MINIATURE INSTRUMENT RECTI-FIERS. Bridge Type I milliamp. Guaranteed perfect, 7/6 each.

S.T.C. RECTIFIER. 36 plates by 120 mm. Bridge connected. Maximum A.C. input 60 volt, D.C. output 15 amp. New, perfect. Price 60]-. P. & P. 3/6.

8-day clockwork Time Switch. Contacts 21 amp., 230 volt, 24 hour phase, & hour divisions, allow setting for one make and one break to be made every 24 hours, complete with key. Used but guaranteed perfect. Price 27/6 each. P. & P. 1/6.



	METERS GUARANTEED PERFECT	
	Charging Types 2½ amp. D.C. M.I. 2in. fl. rnd 5 amp. D.C. M.I. 2½in. fl. rnd 7½ amp. D.C. M.I. 3½in. proj. rnd 9 amp. D.C. McVire W.R. 2½in. fl. rnd. 15 amp. D.C. M.C. 2in. rnd. 30 amp. D.C. M.C. 2in. fl. sq	7/6 11/6 12/6 6/6 10/6 12/6 32/6
	Voltmeters 12 v. D.C. M.C. 2½In. proj. rnd. 20 v. D.C. M.C. 2in. fl. sq 25 v. D.C. M.C. 2in. fl. rnd. 30 v. M.I. 3in. proj. rnd. 40 v. M.C. 2in. fl. sq 300 v. A.C. M.C. 2½in. fl. rnd. 300 v. A.C. M.I. 2½in. fl. rnd.	8/6 10/6 7/6 10/6 10/6 27/6 22/- 35/-
	Milliammeters I mA. M.C. 2½ in. fl. rnd	25/- 12/6 12/6
	Microamp 50 microamp, scaled 0-100, M.C. 2½in, fl. rnd. 50 microA. 2½in, square, side fitting scales 500 microamp, M.C. 2in, rnd. F.L. scaled 15/600 volt. NEW Postage on all meters 1/- each.	35/-
ш		

Miniature latest type moving coil 0-5 milliamp meter, 1½in. diameter, flush fitting, complete with fixing clip. Price 17/6. P. & P. 1/-.



CRYSTAL CALIBRATOR No. 10.



crystal controlled 4-valve high-grade instrument in the same category as the famous B.C. 221. Directly calibrated, does not require cross reference or charts — functions

charts — functions as follows: (1) A crystal controlled oscillator which provides fixed frequency signals of 500 KC to beyond 10 Meg. and up to 30 Meg.

(2) A variable oscillator from 250 KC to 500 KC, this enables all intermediate frequencies between 250 Kc/s. and 30 Meg. to be produced and modulated.

Supplied complete with 3 spare valves, all leads and maker's instruction book in carrying haversack. The complete outfit is brand new repeat NEW. Price: £4/19/6. Carr. 3/-

TWELVE PLATE F.W. BRIDGE CONNECTED

RECTIFIER mounted on 200/250 volt A.C. input transformer. Output 36/40 volt D.C. at 1.2 amps. New, perfect. Price 16/6. P. & P. 3/6.



WE ARE EXPERTS AT OVERSEAS PACKING & SHIPPING!

RVICE TRADING

PERSONAL CALLERS ONLY: 9 Little Newport Street, London, W.C.2 TEL: GER 0576 ALL MAIL ORDERS (Early Closing Thursday)

47-49 High Street, Kingston-on-Thames Telephone: KINgston 4585



23 Tottenham Court Rd., London. W.I. Tel: MUSeum 3451/2



3 16

100

8/15/18

THE EASY SIX


6-Transistor Battery Portable MAY BE BUILT FOR £9.15.0 plus 3/- p.p. Ever Ready PP7 Battery Extra 3/3

Ever Ready PP7 Battery Extra 3/3

STAB FRATURES: Str lst grade Mulnd
Transistors & Internal Perrite Rod Aerial &
Provision for Car Radio Aerial &
Provision for Car Radio Aerial &
Provision for Car Radio Aerial &
Provision for Car Radio Aerial &
Provision for Car Radio Aerial &
Provision for Car Radio Aerial &
Position sindicated & Preasembled Dial Assembly
\$ 500 milliwatts Push Pull output & Pull
unclium and long waveband coverage Attractive
two-tone Blue/Cream Vynide covered Cabinet,
dimensions \$\sin \text{x} \text{c} \text{in} \text{x} \text{in}. \text{ Fill} point-topoint instructions supplied. \$\frac{1}{2}\$ Weight 3lb. with
battery.

Assemble it yourself and SAVE £ £ £'s

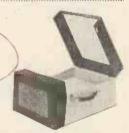If all the above items are purchased at the same time they can be supplied at £13/15/-, plus 10/- P. & P.



STORES TO STORES TO STORES TO STORE ADVANTAGE OF THESE STORES TO STORES STORES TO STORE TO STORE TO STORE TO STORE THE STORES TO STORE THE STORES TO STORE THE STORES TO STORE THE STORES TO STORES TO STORES TO STORES TO STORES THE STORES TO STORES TO STORES TO STORES TO STORES THE STORES TO STORES TO STORES TO STORES TO STORES THE STORES TO STORES THE STORES TO STORES THE

PRICE DRAMATIC REDUCTIONS

AVANTIC DL7/35 Power Amplifier. Specifications: power output 54 watts peak; L.S. impedance 4, 8 or 16 ohms, power inputs 105-250 v. Valve line-up GZ34, 2-EL34, ECC83, EF86. Dimensions 14½ x 9 x 8½in. Original price 30 gns. P. & P. 12/6. OUR PRICE £16/19/6.

AVANTIC SP21. Stereophonic Pre-amp. Control Unit. Brief specifications, 6 inputs for each channel, bass, treble, volume control, on/off stereo/3D/reverse stereo switch, stereo phase switch, low pass filter, Power requirements 6.3 v. at 1.3 A., A.C. 350 v. at 5 mA. D.C. Dimensions 14½ x 9 x 4in. Original price £28/10/-. P. & P. 7/6. OUR PRICE £16/19/6.

> THE Petite **PORTABLE**

MAY BE BUILT FOR \$7.7.0 P. & P.

• High Q frame aerials

High sensitivity on both wavebands.

Batteries extra.

AVANTIC SPAII Stereophonic Amplifier. Technical details: power AVANTIC SPATI Stereophonic Amplifier. Technical details: power output (each channel) 10 watts peak, L.S. impedance, 4, 8 and 16 ohms 6-position input selector, bass, treble, volume on/off controls, stereo reverse switch, phase reverse switch, stereo balance control, P.U. balance control. Dimensions 14½ x 8½ x 4in. Original price 28 Gns. P. & P. 7/6. OUR PRICE 19 Gns.

AVANTIC PL621 20-watt monaural Amplifier, frequency response 10 c/s-30 Kc/s, IdB. L.S. impedance 4, 8 or 16 ohms. Dimensions Idin. x 8½in. x 7½in. Original price 29 Gns. P. & P. 7/6. OUR PRICE

AVANTIC STEP II. Stereophonic Magnetic Pick-up Amplifier Unit. Price £4/4/-.

All this equipment is Brand New and in manufacturer's original sealed cartons. Full descriptive literature available.

WHY NOT TAKE ADVANTAGE

WHY NOT TAKE ADVANTAGE PREMIER BATTERY ELIMINATOR Housed in two containers which are to replace AD 35 and B126 batteries. KIT 37/6 plus 2/- post and packing. Only Suitable for use with DK 96 Series valves.

Two DL7/35 POWER AMPLIFIERS Combined Price SP21/2 STEREO CONTROL UNIT 47 Gns. CANAL NO CANO CANO CANO CANO CANO CANO

H.T. 10'- (Type B126) or equivalent. THE MODEL FMA/1 FERGUSON LT. 16 (Type AD 35) or equivalent. FM TUNER

13 gns plus 3/- p. & p.

13 gBs plus 3r-p. & p.
For use with Radio Recelvers or Hi-Fi equipment. Dompletely selfcontained, self-powered
and housed in a hammered metal
finished steel case. 10 x 72 x 2 in. Frequency coverage 87.5-100 Mc/s. (continuously). Valve lineup. 2—EF80, EOF80, 2 germanium diodes and metal rectifier
for operation on A.C. mahs 200/220 v. 50-60 cycles.

TUNERS FOR THE HOME CONSTRUCTOR BY 'JASON'

JASON JTV2. T.V. SOUND & F.M. complete with Turret Tuner and Case less Valves, £14/19/0, plus 3/6 p. & p. Valves £1/12/0. Instruction Book available separately

Power Supply Kit, suitable for above £2/14/0, plus 2/-

• Medlum and long wave superhet circuit.

Instruction book 1 6.
Size only 8 x 8 x 4 in.

WHY NOT DO IT YOURSELF!

SUPERHET £7 . 7 . 0 Plus 3/may be built for T.R.F. may Plus 3/-p. & p. £5 . 10 . 0

● Weight including batteries 51b. ● 4 valves of the

These two receivers use the latest type circuitry and are fitted into attractive cabinets 12 × 6 ½ × 51/2 in., in either walnut or ivory Bakelite or wood 1/- extra. Individual instruction books 1/each, post free.



THE 'CLARION

Transistorised miniature battery-operated

TAPE RECORDER

* Completely transistorised circuit.

* Constant governed speed of 31 L.P.S.

* Recordings interchangeable with other recorders.

* Remarkable reproduction on both speech and music.

Price complete with Microphone 25 GNS. plus 5/- and tape— 25 GNS. p. & P.

THE 'MID-FI' A NEW DESIGN 4 WATT AMPLIFIER KIT MAY BE 95/-BUILT FOR

Plus 3/- p. & p.

A new circuit for the home constructor requiring a good quality medium-powered Amplifier for reproduction of Records or F.M. Broadcasts, Technical Specifications: separate bass and treble controls. Valve inc-up EF86, EL84 E280, Voltage adjustment for A.C. mains from 200,250 volt, 3 or 15 chms impedance. Negative feedback, Size 7 x 5 x 2in., overall height 5in. Silver-hammered finished Chassis.



THE VICEROY QUALITY CRYSTAL MICROPHONE A good-quality crystal Microphone for the discerning enthusiast, finished in polished steel with Muting Switch and detachable lead. Price 42/-, P.P. 1/6.

FOR THE BEGINNER
A three-transistor, medium wave, receiver, ideally suited for the young anthusiast or the beginner. Incorporating two transistors and one diode and operating on two

tors and one gloss are the period of the period of botteries. Simple to construct, with full instructions supplied. No headphones required. Complete set of components, including plastic case. 27/6 plus 1/6 P. A. P. Batteries extra.



THE MODEL VT41 VALVE FILAMENT TESTER

FILAMENT TESTER
Will instantly check the
filaments of all Radio and
T.V. Valves, Fuses and Dial
Bulbs. Will also give an
accurate circuit continuity
test and also has built-in
7 and 9 valve straighteners.
PRICE 30/-with Battery, post paid.

CABY MODEL B20 MULTI-METER

DCIV 0.0.5 v. 0.2.5 v. (2K.ohms/V)
DCIV 10-50-250-500-1000 v. (4K.ohms/V)
ACIV 10-50-250-1000 v. (4K.ohms/V)
DCIMA 0.100 microamps (500mV)
DCIMA 0.2.5-25-250mA (250mV)
OHMS, 2K.-20 meg.
COMPLETE WITH TEST LEADS—

PRICE £6/10/0 plus 2/. P. & P.

CABY MULTI-METER A-10

DC/V 10-50-250-500 1kΩ (2kΩ/V) AC/V 10-50-250-500-1kΩ (2kΩ/V) Ranges: DC/mA 0.5-25-250 (250mV) OHM 0-10 kΩ-1MΩ.

Complete with test leads £4/17/6

ASTANDORASTAND

309 Edgware Rd., Landon. W.2. Tel: PADington 6963



Visit our large and comprehensive HI-FI showrooms



PRICE including Microphone, Tape and Spare Spool, 19 Gns. Plus 15/-P. & P.

First Again!! "THE PREMIER TR/2"

Once again, Premier is first, with another magnificent offer. Introducing the "TR/2" the latest and cheapest addition to our range of popular Recorders. Star features:

*Latest BSR Tape Deck, with inter-locking device to prevent accidental erasure.

Single speed 3fin. per sec.

wingie speed 3\lin. per sec.

\[\Playing time b\frac{1}{2}\lin. std \tape-1\right\r

★Extension speaker socket. Size: 13½ × 9½ × 6in., weight 17 lb.

TAPE DECKS

LATEST BSR MONARDELK, Single speed 32 Lp.s. Will take 52in. spoots. £8/19/6. P. & P. 5/COLLARO STUDIO TAPE TRANSCRIPTOR.
3 speeds 1; 3; 7; l.p.s. 3 motors. Furbbutton controls. Will take 7in, spools.
£19/19/6. P. & P. 7/1 RANSCRIPTOR.
COLLARO MK, 4 TAPE TRANSCRIPTOR.
Twin track operation, 3 speeds, 8; 7; 15
i.p.s. Will take 7in, spools. £17/19/6.

Twin track operation, 3 speeds, 3\frac{3}{2}, 7\frac{1}{2}, 10\structure, #### RECORDING TAPE

By well-known		brand	new.
boxed and fully 1,800ft, on 7in. o 1,200ft, on 5 in. P. & P. 1/- per	spool		32/6 22/6

AMERICAN C.B.S.

RECORDING TALE	
Brand new, fully guaranteed and	with
Leader Tape:— 600ft, on 5in. Spool	
1,200ft. on 5lin. Spool	25/-
1.200ft. on 7in. Spool	25/-
Plus 1/s per Spool P & P	

SINGLE PLATE.

Collaro Junior 4-speed Player complete with
23 15 0 Collaro Junior 4-spects range.

23 15 0
Garrard 48P 4-speed Player, complete with
Pick-up and automatic stop. 26 19 6
Garrard TA Mk, 2 4-speed Player, wired for
sterco, with plug-in Head. 28 10 0
Philips AG2009 4-speed Player, with diseast
turntable and Microlitt wired for sterco

P. & P. 3/6 on above units.

RECORD CHANGERS

BSR UAS, 4-speed £6 19 6 BSR UAS 4-speed with stereo cartridge BSR UA12, 4-speed wired for stereo and complete with Stereo cartridge £7 19 6 Collaro Conquest, 4-speed Changer Collaro RCAR2

Collaro RC467, latest type 4-speed Changer £7 10 6
Collaro RC467, latest type 4-speed changer £8 10 0
Garrard RC111 3-speed Changer £7 19 6
Garrard RC120 Mk. 2, 4-speed £8 19 6
Garrard RC121/4D, 4-speed ... £9 19 6
tiarrard RC121/4D, 4-speed ... £9 19 6
P. £ P. 5/- on above units.

TRANSCRIPTION UNITS

Garrard 301 Garrard 301 (Strobe turntable) Garrard 4HF (Stereo) Garrard 4HF (GCS)	£23 £19	18	3489
P. & P. 7/6 on above units.			

TAPE RECORDER RADIO JACK



May be built for 29/6 plus 1/6 p. and p. Tape Recorder Plug Extra

Improve the quality of your recordings with the most inexpensive Radio Jack available, suitable for any type of Tape Recorder, only a short external Aerial required for full medium waveband coverage. Phono Plugs-9d., Jack Plugs-3/-.

INSTANT BULK TAPE ERASURE

Erase complete Reels of Tape in a matter of seconds. PRICE 27/6 post paid.



MODEL 379 AM/FM RADIO-GRAM CHASSIS BY FAMOUS MANUFACTURER

PRICE £12.12.0 plus 7/6 p. & p.

The 'Magnaphon

A truly top quality and versatile Tape Recorder at a price well below the original cost. Incorporating the latest Collarc 3-speed Studio Tape Deck.

- Volume and Tone Control for record-
- ★ Volume and separate Bass and Trebie

* Volume and separate Bass and Trebic Controls for replay.

* Facilities for monitoring.

* Output 4 watts.

* Beparate Output Sockets for Amplifier and Extension Speaker.

* Mixing Facilities.

* Housed in attractive red and beige two-tone Cabinet with detachable lid.

* Fully guaranteed and supplied complete with the following accessories:

Price 232.0.0 Good quality Crystal Microphone with Lead and Jack Plug Rited, 61. Reel of Standard Tape and Spare Reel spare Lead fitted with Jack Plug and Wander Plugs for recording from Radio.



STEREO ADAPTOR

Why not convert you Becord Player or Radiogram to stereo with this easy to install Stereo Conversion Unit, complete and ready to install giving an output of 3 watts.

STEREOPHONIC PICK-UP CARTRIDGES

£2.19.6 Plus 2/- P. & P.

AVAILABLE, 35/- post paid. The 'Vogue'

A quality tape recorder, at a popular price including interophone, tape and spare spool.

Price 29 gns. Plus 21/. P. &

- . Collaro 3-speed Tape Deck.
- * Separate Input for Microphone and Gram Recording.
- * Separate Volume Controls for recording.
- ★ Volume On/Off and Tone Control for
- # 3 watts output.
- ★ Housed in smart two-tone Blue/Beige Cabinet with detachable Lid.





THE PREMIER TRANSISTORISED

BABY ALARM



79/6 Plus 3/- P. & P. Battery extra (Ever-Ready PPI 6 volt or equiv.) Battery extra 2/9

(Ever-Ready PPI 6 volt or equiv.)

The answer to the modern Parents' problem for "Beby Sitting", this extremely efficient Unit is completely set any part of the house Extra Microphones may be used in different rooms without impairing the efficiency of the Unit. It is the most economical Unit of its kind and will run on one Battery for approximately two months of continuous day and night use. It is housed in an attractive bakelite Cabinet in either fivory or pastel blue. The price includes one different properties of the continuous day and Microphone Lead at 5d. per yard.

3-WAVEBAND RADIOGRAM CHASSIS

By Famous Manufacturer

£10.19.6 plus 5/- p. & p. A special offer for a limited period only

of this Continental style Radlogram charsis.

Brief details: Long, Medium and Short wavebands covering 1007-1960 metres, 185-555 metres, 16-32 metres. Valve line-up: ECH81, EBF80, ECL82, Mains voltage 200/250 v. A.C. Gramophone Pick-up Input D.mensions 174in long, 5in. blgh 6in. deep

R.S.C. HI-FI TAPE RECORDER KIT

Build a high quality recorder in the £70 class for only

25½ GNS. Carr. 17/6.

Can be assembled in 1 hour.

INCORPORATING THE LATEST COLLARO STUDIO TAPE TRANSCRIPTOR THE LINEAR LT45X HIGH QUALITY TAPE AMPLIFIER. A HIGH FLUX 7 × 4in. LOUDSPEAKER, Reel of Best Quality TAPE, Spare Tape Spool, a Portable Cabinet, size approx, 16 × 13 × 9in., finished in durable and attractive duo-tone Polierome, and connection diagram for wiring amplifier to transcriptor,

FEATURES INCLUDE

★ 3 SPEEDS ★ FREQUENCY RESPONSE 50-11,000 c.p.s. ★ SWITCHED NEGATIVE FREDBACK EQUALIZING FOR EACH SPEED. ★ OUTPUT NEGATIVE FREDBACK EQUALIZING FOR EACH SPEED. * OUTPUT 4 WATTS * MAGIC EYE RECORDING LEVEL INDICATOR * 3 MOTORS. Fast rewind. * TAPE MEASURING AND CALIBRATING DEVICE. * TAKES
FULL 7in. DIAMETER REELS OF TAPE. * NEGLIGIBLE HUM. * EN-TIRELY EFFECTIVE AUTOMATIC ERASURE

Full descriptive leaflet supplied on receipt of S.A.E.

OR DEPOSIT £5/7/6 and 12 monthly payments of 42/-. Cash price if settled in 3 months.

HI-FI 10 WATT AMPLIFIERS

BRAND NEW CARTONED MANUFACTURERS DISCONTINUED CART. 7/6.

A REMARKABLE OPPORTUNITY A REMARKABLE OPPORTUNITY
Push-pull output. Latest high efficiency Mullard valves
Dual separately controlled inputs, for mike and gram.
Separate base and treble controls. High sensitivity. Output
for 3 ohm or 15 ohm loudpseaker. Guaranteed, teated and
in perfect working order. Please state speaker matching
required when ordering.

SUPERHET RADIO FEEDER UNIT

SUPERHET RADIO FEEDER UNIT
Design of a high quality Radio Tuner Unit (specially suitable
for use with any of our Amplifiers). A Triode Heptode
F/changer is used. Pentode I.F. and double Diode Second
Detector, 'elayed A.V.C. is arranged so that A.V.C. distotton is avoided. The W. Ch. 8W. incorporates Gramposition. Controls are Tuning, W. Ch. and Vol. Output
will load most Amplifiers requiring 500 mV. input depending
on Ae location. Only 250 v. 16 mA. H.T. and L.T. of
6.3 v. 1 amp. required from amplifier. Size of unit approx.
9-6-7in. high. Send S.A.E. for illustrated leaflet. Total
building cost is £4/1.5f-. Point-to-Point wiring diagrams
and instructions 2/6.

R.S.C. JUNIOR TAPE RECORDER KIT.
B.S.R. Monardeck Tapedeck, as used by most leading manufacturers of Recorders, our TRI 3 watt amplifier ready wired provides excellent quality at up to rated output, portable cabinet, fin. reel Scotch tape, empty spool, and 6in. x 4in.

Carr. 15/-.

Carr. 15/-.

Recorder With Taper Provided Pr

RE-ENTRANT LOUDSPEAKERS

For factory or outdoor use. Tannoy 7.5 ohms 8 watts 25/9.

Parmeko horn type, highly rarman type, highly efficient. Handles up to 10 watts. 15 ohm 200 ohm and 600 ohm matching 59/6. R.C.A. 20 watt rating, 3 ohm, 15 ohm. and 200 ohm 600 ohm matching 6 gns. ACOS HI-FI CRYSTAL 'MIKES' Mic 30 hand or Desk type 27/9 (Listed) 39-1 Stick typ 39/6 (Listed) Limited number.

Type BM1. An all-dry battery eliminator, Size 54 x 44 x 2in, approx. Completely replaces batteries supply 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s. is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagram 39/9 or ready for use 46/9.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM2. Size $8 \times 5\frac{1}{9} \times 2\frac{1}{9}$ in. Supplies 120 v. 90 v. and 60 v., 40 mA. and 2 v. 0.4 a. to 1 amp., fully smoothed. THEREBY COMPLETELY REPLACING BOTH H.T. BATTERIES AND H.T. 2 v. ACCUMULATORS when connected to A.C. mains supply 200-250 v. 50 c/s. SUITABLE FOR ALL BATTERY RECEIVERS normally using 2 v. accumulator

Complete kit with diagrams and instructions. 49/9 or ready for use 59/6.



VALVES! Full range at really competitive prices.

THE SKY FOUR T.R.F. RECEIVER



design of a 3 ve 200-250 v.

R.S.C. A12 STEREO AMPLIFIER KIT

A complete kit of parts to construct a good quality 3 + 3 watt (total 6 watt) stereo amplifier providing really life-like reproduction, stereo pick-up heads at present available. Ganged volume and tone controls. Preset balance control. Outputs for matched 2 3 ohm speakers. For 200-250 v. A.C. mains. Astonishing value.

R.S.C. STEREO/TEN HIGH QUALITY

nut veneered type. It employs valves 6K7, 8P61, 6P6 eK7, 8P61, 6P61, 6P6

SELENIUM RECTIFIERS

We can quote special prices for quantities of 12 to 10,000

it most types. Special types	made to order.
.T. Types	H.T. Types H.W.
2/6 v. la. h.w 1/9	120 v. 40 m.A 3/9
/12 v. 1 a. h.w 2/9	250 v. 50 mA 3/1
following F.W. (Bridge)	250 v. 60 mA 4/11
3/12 v. 1 a 3/11	250 v. 80 mA 6/11
3/12 v. 2 a 6/11	250 v. 250 mA 12/9
3/12 v. 3 a 9/9	200
1/12 v. 4 a 12/3	Coptact Cooled
3/12 v. 5 a 14/6	250 v. 80 mA 6/11
7/12 v. 6 a 15/6	250 v. 75 mA 10/11
3/12 v. 10 a 25/9	F.W. (Bridge)
3/12 v. 15 a 35/9	
00,0	

-

SPECIAL OFFER, of R.C.A. replacement stylli for Collaro Studio "O" and "P" Ronette and other pick-up heads. Sapphire type stan-dard of L.P. 3/11 each. Diamond type normally 83/5. Only 29/11.

HEAVY DUTY CHARGER KIT

CHARGER KII
6/12 v. variable charge
rate up to 6 amps.
Consisting of Mains
Trans., F.W. (Bridge)
Selenium Rectifier, 0-7
amp. meter, multiposition switch with
knob, fuses, fuseholders, panels, plugs,
and circuit Only 59/8. and circuit. Only 59/6.

ASSEMBLED CHARGERS

6 v. 1 a. 19/9 6 v. 2 a. 29/9 6/12 v. 1 a. 29/9 6/12 v. 2 a. 38/9 Above ready for use with mains and output leads. Cases well ventilated and finished in stoved blue hammer. Carr. & Pkg.

CHARGER TRANSFORMERS

Battery Chargers and Kits for 200-230-250 v. 50 c/s. A/C. Mains BATTERY CHARGER KITS Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses, fuse-holders, grommets, panels

fuse-holders, grommets, panels and circuit. Carr. 2/9 extra. 6 v. or 12 v. 1 amp. 24/9
As above, with ammeter... 32/9 31/6 42/9 6 v. or 12 v. 4 amps. 6 v. or 12 v. 4 amps, with 53/9

19/9 CHARGER AMMETERS As above, but for 3 amp. 0-1.5 amp., 0-25 amp., 0-60 amp. 8/9 Only 59/6. Carr. 3/9

variable charge rate selector

and ammeter

ASSEMBLED CHARGER

6 v. or 12 v. 2 amps. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready for use with mains and output leads.
Double Fused. Only Carr. 3/9. 49/9

ASSEMBLED 6 v. or 12 v. 4 amps.

Fitted Ammeter and variable charge selector. Also selector plug for 6 v. or 12 v. charging Double fused. Well ventilated steel case with blue hammer finish. Ready for use with mains and 69/9output leads. Carr. 5/-. Or Deposit 13/3 and

Or Deposi 5 monthly payments of 13/3.

As above, but for 6 amp. charging 4 GNS. Carr. 5/-. Or Deposit 16/- and 5 monthly payments of 16/-. The 6 amp. model only is slightly store soiled and is being offered at well below usual price

LINEAR L45 MINIATURE 4/5 W. QUALITY AMPLIFIER.

Bultable for use with any record playing unit and most microphones. Negative feedback 12 D.B. Bass and Trabes controls. For A.C. mains input of 200-250 v. 50 c.p.s. Output for 2/3 ohm speaker. Three miniature Mullard valves, Exe only 6x5 x54 in, ligh. Chassis fully isolated from mains. Guaranteed 12 months. Only Deposit 22/- and 5 monthly payments.

55.19.6 On SUPPLY KITS. Sultable for electric trains. Consist of mains trans. 200-250 v. 50 c.p.s.: 12 v. 1 amp. selenium with trans. 200-250 v. 50 c.p.s.: 12 v. 1 amp. selenium direct. (F.W. Bridge); 2 fuseholders, 2 fuses, change direction. Partially drilled steel case and circuit. Very limited number, 33/9.

REPANCO TWINETTE TRANSISTOR PORTABLE RADIO DESIGN. Constructional Envelope and parts list 1/3. Built-in Ferrite Aerial, 7in. x 4in, speaker, Long and dedum waves. Size approx. 7x4x3in. Total cost of all divine waves. Size approx. 7x4x3in. Total cost of all divine waves. Size approx. 7x4x3in. Total cost of all

SPEAKERS

HF1012, 10 watts, 15 ohm (or 3 ohm) speech co l. Where a really good quality speaker at a law price is required, we highly recommend this unit with an amazing performance. £4/10/9. Please state whether 3 ohm or 15 ohm required.

SPEAKERS

LINEAR TAPE PRE-AMPLIFIER Type TF/L Switched regative feedback equalisation. Foolitons for Record indicator. besigned primarily as the link between Collaro Tape Transcriptor and high fidelity amplifier but suitable almost any Tape Deck.

SGIS-

59/9

DESIGN. Constructional Envelope and parts list 1/3 Built-in Ferrite Aerial, 7in. x 4in. speaker, Long and Medium waves. Size approx. 7x4x3in. Total cost of al parts 5 gns.

POWER PACK KITS. Only 18/11. Fully smoothed H.T. output of 230 v. 60 ma. and L.T. supply of 6,3 v. 1.5 amp. Consisting of Double Wound Mains Transformer 230/250 v. 50 c.p.s. A.C. primary. Sele-nium -Rectifier, Smoothing Choke, Double Electro-iytic Condenser. Aluminium Chassis and Circuit.

P.M. SPEAKERS. 2-3 ohms 2¼in. Perdio 21/9. 5in. Goodmans 17/9. 7 × 4in. R.A. Elliytical 19/9. 6¼in. Rola 19/9. 8in. Rola 19/9. 8n. Rola 19/9. 8 × 6in. Eliac. with high flux magnet 25/9. 10in. R.A. 28/9. 10 × 6in. Elliptical goodmans 29/9. 12in. R.A. 29/11. 12in. T.A. 3 or 15 ohms. 10 watts, 12,000 lines, 59/6.

TWEETERS. 4in. Piessey, 3 ohms, 18/9, R.A. 15 ohms 25/9.

R.S.C. A10 ULTRA LINEAR WATT AMPLIFIER

HIGH FIDELITY
PUSH-PULL UNIT
EMPLOYING SIX
VALVES. EF86, EC38, 807,
807, GZ34. Tone
Control Pre-Amp. stages are nicorpor ated. Sensitivity, i ated. Sensitivity is extremely high. Only 12 millivoit minimum input is required for full output. THIS ENSURES THE SUITABLITY OF ANY TYPE OR MICROPHONE OR PICK-UP. Bass and Treble give both "lift" or the process of t



IN provided so that two separate imputs such as "mike" and gram. cto., can be simultaneously applied for mixing purposes. AN OUTPUT SOCKET WITH PLUG IS INCLUDED FOR SUPPLY OF 300 v. 20 mA. and 6.3 v. 1.5 A. FOR A RADIO FEEDER UNIT. Price in kit form with easy-to-follow wiring diagrams. ONLY

Carr. 10/.

11 GINS.

ON ASSEMBLED UNITS. DEPOSIT 31/9 and 9 monthly payments of 31/10/10. TERMS ON ASSEMBLED UNITS. DEPOSIT 31/9 and 9 monthly payments of 31/10/10 view as the subject of the control of the c

FULL RANGE OF LINEAR HIGH FIDELITY AMPLIFIERS ALWAYS IN STOCK.
GL3A MINIATURE 3. WATT GRAM AMPLIFIER
For 200-250 v. 50 c.p.s. A.C. mains. Overall size only 11½ ×2½ ×2½m. Fitted Vol. and Tone
Control with mains switch. Designed for use with any kind of single player or record changing unit. Output for 2-3 ohm speaker. Guaranteed 12 months. Only 59/6.

R.S.C. A7 3-4 WATT QUALITY AMPLIFIER. Spec. exactly as A5 below with exception of output voltage. Complete kit of parts, diagrams and instructions £3/15/-, carr. 3/6.

of output voltage. Complete kit of parts, diagrams and instructions £3/15/-, carr. 3/6.

R.S.C. A5 4-5 WATT HIGH GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads in addition to all other types of pick-ups and practically all makes, Separate Bass and Treble controls are provided. These give full long playing record equalisation. Hum-level is negligible being 71 D.B. down. 15 D.B. of negative feedback is used. H.T. of 300 v. 26 mA, and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit or Tape Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with the blue hammer finish, and point-to-point wiring diagrams and instructions. Exceptional value at only 24/15/- or assembled rady for use 25/- extra, plus 3/6 cargar, or Deposit 22/- and five monthly payments of 22/- for assembled unit.



R.S.C. TRANSFORMERS. Fully Guaranteed. Interleaved & impregnated WE CAN QUOTE FOR SPECIAL OR STANDARD TYPES IN ANY QUANTITY. OU FACTORY HAS SUPPLIED LEADING EQUIPMENT MANUFACTURERS AND GOV

DEPTS. FOR 15 YEARS.	
MAINS TRANSFORMERS. Primaries 200-230-230 v.	50 c/s
FULLY SHROUDED UPRIGHT MOUNTING.	
250-0-250 v. 60 mA., 6.3 v. 2 a., 5 v. 2 a. 21-3-3ins.	17/11
250-0-250 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a	27/9
300-0-300 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a	27/9
350-0-350 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a	27/9
350-0-350 v. 150 mA., 6.3 v. 4 a., 5 v. 3 a	33/9
425-0-425 v, 200 mA., 6.3 v. 4 a., c.t. 5 v. 3 a	49/9
TOP SHROUDED DROP-THROUGH TYPE	
260-0-260 v. 70 mA., 6.3 v. 2 a., 5 v. 2 a.	16/11
250-0-250 v. 100 m.A., 6.3 v. 3.5 a	19/9
250-0-250 v. 100 mA., 6.3 v. 2 a., 6.3 v. 1 a	21/9
350-0-350 v. 80 mA., 6.3 v. 2 a., 5 v. 2 a	18/9
250-0-250 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a	
300-0-300 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a	25/9
300-0-300 v. 130 mA., 6.3 v. 4 a., c.t., 6.3 v. 1 a.,	
suitable for Mullard 510 Amplifier	29/9
350-0-350 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a	25/9
350-0-350 v. 150 mA., 6.3 v. 4 a., 5 v. 3 a	29/9
ELIMINATOR TRANSFORMERS.	
120 v. 40 mA., 5-0-5 v. 1 a.	14/9
90 v. 15 mA., 6-0-6 v. 250 mA,	9/11
FILAMENT TRANSFORMERS	
6.3 v. 1.5 a 5/9 12 v. 1 a	7/9
6.3 v. 2 a	8/11
0-4-6.3 v. 2 a 7/9 6.3 v. 6 a	17/9
12 v. 3 a. or 24 v. 1.5 s	
AUTO (Step Up/Step Down) TRANSFORMERS	
50-80 watts 110-120 v./230-250 v	11/9
150 watts 110-120 v./200-230-250 v.	27/9

OUTPUT TRANSFORMERS Midget Battery Pentode 66:1 for 384, etc. . . 3/9 8mall Pentode 5,000 \(\Omega\$ to

Standard Pentode 5,000 18 x Sin. £7/19/6 or De	no
to 3Ω 5/9	
	9
	9
	9
Push-pull 10-12 watts 6V6 to 3Q or 15Q 16	9
Push-pull 10-12 watts to match 6V6 to 3-5-8 or 15Ω 17.	
Push-pull EL84 to 3 or 15 ohms 10-12 watts 17	
Push-pull Ultra Linear for Mullard 510 27.	19
Push-Pull 15-18 watts, sectionally wound, 6L6,	
KT66, etc., for 3 or 15 ohms	9
Push-pull 20 watt high-quality sectionally wound,	
6L6, KT66, etc., to 3 or 15Ω 47	19
MICROPHONE TRANSFORMERS	
120:1 High quality, clamped 6	19
120:1 High quality Mu metal screened 8	19
SMOOTHING CHOKES	
250 mA., 5 H., 100 Ω 11/9 80 mA., 10 H., 350 Q 5	IR
150 mA., 7-10 H., 250 Ω 11/9 60 mA., 10 H., 400 Ω 4/	
	16
PARMEKO MAINS TRANSFORMERS. Fully shroude	
450-0-450 v. 100 mA. 6.3 v. 1.5 a., 4 v. 3 a., 4 v. 2 a. 19	
500-0-500 v. 120 mA., 6.3 v. 4 a., 5 v. 3a 31	18

R.S.C. (LEEDS) LTD. MANGHESTER, LEEDS & BRADFORD

Open to callers at the following branches:—
5-7 County (Mecca) Arcade, Leeds, I.
54-56 Morley Street (above Alhambra), Bradford.
8-10 Brown Street (Market St.), Manchester, 2.

TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/9 extra on all orders under £2, 2/9 extra under £5 unless carririage stated. Trade supplied. Post orders Mail Order Dept.

29-31 Moorfield Road, Leeds, 12.

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT " BUILT-IN " TONE CONTROL PRE-AMP **STAGES**



R.S.C. PORTABLE GUITAR AMPLIFIERS



JUNIOR 5 WATT. High Quality Output. Separate Bass and Treble "cut" and "boost" controls Sensitivity 16 mv. High Flux Sin. Japeaker. Input sockets for Radio/Tape or Gram Pick-up and Mike Instrument Pick-up. Handsome strongly made cabinet (size approx. 14×14×71m.). Finished in satin walnut and fitted carrying handle.

28/19/6. Carr. 7/6. Or Deposit 21 and nine monthly payments 21.

SENIOR 10 WATTS.

output. Separate Bass and Treble "cut" and 'boost" controls. Twin separately controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two Loudspeakers are incorporated a 12h. P.M. for Bass notes, and 1 7 x 4h. elliptical for Treble. Cabinet is well made and finished satin 14 x 4h. elliptical for Treble. Cabinet is well made and finished satin 14 x 4h. elliptical for Service 15 Gen. Plus 10/- carr H.P. TERMS. DEPOSIT 34/9 and 9 monthly payments 34/9. Both models for 200-250 v. A.C. mains.

COLLARO CONTINENTAL 4 SPEED DE LUXE MIXER AUTO-CHANGERS with TX88 Transcription Cartridge for standard and L.P. records. F. Few only at unrepeatable price of £10/19/6. Carr. 4/6.

COLLARO CONQUEST 4-SPEED AUTO-CHAN-GERS. With studio pick-up with turnover head. Latest model for 200-250 v. A.C. mains, £6/19/6

Latest model for 200-200 v. A. Type
Carr. 4/6.
B.S.R. MONABCH AUTO-CHANGERS. Type
UA8. 4 speed T/O Pick-up with sapphire stylue
£6/119/6. Carr. 4/6.
Any of the above supplied with T/O stereo/monaural head for £1 extra.
COLLARO JUNIOR. 4-speed Single Players with
HI-Fi T/O crystal pick-up head, £3/18/6.

LOUDSPEAKER IN POLISHED WALNUT FINISHED CABINET. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4/19/6. Carr. 5/- TERMS: DEPOSIT 11/- and 9 monthly payments of 11/-. 12in. 20 WATT 15,000 line l/speakers 15 ohms in

bove, Size 18 x



9 ACOS HGP59 Hi-Fi Crystal Cartridges. (Turnover type 9 with sapphire stylus). Standard replacement for Garrard 9 and Collaro. Only 19/9. B.S.R. Ful-Fi 19/9. Garrard 9 GC2 19/9. Acos Stereo/monaural 49/9.

ACOS HIGH FIDELITY PICKUPS. GP54 with HGP59/52 Cartridge. Turnover sapphire styll, cream finish. Limited number at approx. half price. Only 35/9.

R.C.A. TRANSCRIPTION PICK-UPS. Variable Reluctance type for standard and L.P. Records. Normal price approx 214. Limited number brand new perfect at £3/19/8.



PLESSEY DUAL CONCENTRIC 12in. P.M. **SPEAKERS**

SPEAKERS
(15 ohms), consisting of a high quality 12ln. speaker of orthodox designs supporting a small elliptical speaker of crithodox designs as mall elliptical speaker of crithodox designs and elliptical speaker of the critical speaker of the cr

WAYNE, KERR SIGNAL

GENERATORS, TYPE CT53

HEAVY DUTY EX GOVT. SELENIUM RECTIFIERS

With large square siuminium cooling fins. 12 v. 15 amp. F.W. (Bridge). Limited number. 19/9.

VIBRATORS

Oak and Wearite, synchronous 7-pin, 2 v. 7/9. 6 v. 8/3. 12 v. 4-pin non-synchronous 7/9.

EX. GOVT. MAINS TRANSFORMERS

	All 200-250 v. 50 c/s. input.	
	Pr. 0-110-200-230-250 v. 275-0-275 v. 100 mA.,	
	7 a. 5 v. 3 a	22/9
•	250 v. 60 mA. 6.3 v. 2 a	10/11
	6.3 v. 5.2 a., 6.3 v. 1 .5 a., 6.3 v. 0.5 a., 5 v. 3	a., 5 v.
	3 a., 5 v. 2 a., High Insulation, Potted	27/9
	6.3 v. 2 a., 6.3 v. 1 a., 6.3. v. 2 a., 6.3 v. 0.5 a., 5	v. 3 a.,
	6.3 v. 5 a., 5 v. 6 a., Potted	27/9
	340-0-340 v. 90 m.a., 700-0-700 v. 100 m.a.,	Potted
		27/9
	AUTO 500 watts 0-215-220-225-230-235-240 v.	Carr
	7/6	
	50 watts, 0-110/120-230/250 v	8/11

EX. GOVT. SMOOTHING CHOKES

60 mA. 10 b. 400 ohms 3/11 150 mA. 10 h. 100 80 mA, 20 h, 900 ohms 5/11 120 mA, 12 h, 100 ohms 9/9 100 mA, 5 h, 100 ohms 3/11 200 mA, 5-10 h, 100 ohms 100 mA. 10 h. 100 ohms 6/9 250 mA. 5 h. 50 ohms 10/9

GARRARD RECORD PLAYING UNITS

Dry battery operated. Consisting of motor, turnable and pick-up. For standard 45 r.p.m. records. Only

EX. GOVT. CASES

Well ventilated, black crackle finathed, undrilled cover. Size 14×10×8 im. high. IDBAL FOR BATTERY CHARGER OR INSTRUMENT CASE. COVER COULD BE USED FOR AMPLIFIER. ONly 9/9, plus 2/9 post.

8.9 to 300 megacycles. Output 1 micro-volt to 10 millivoits. Five position switched attenuator. Variable multiplier 1 to 10, calibrated 0-20 db. C.W. square wave and sine wave outputs. Vernier tuned, 6 Band Coil Turres. Potted "C" core Transferriers. Stabilized H.T. All voltage supplies including maxim. R.F. filtered. External mod. by sine wave from 50 c.p.s. to 10 kc/s. or pulses down to [Lesc. Complete with all valves and

240

churas.

SUITABLE FOR ALIGNING T.V. and V.H.F. RADIO.

For 200-250 v. A.C. mains. Beautifully made to very high standards. Worth over £100. Very 17 Carr. 15/-limited number available at only 17 Cars. 18.

MICRO-AMMETERS

0-100. Plush mounting METHR RECTIFIERS 0-5 mA.....

VOLTMETERS

0-300 v. A.C., 50 c.p.s. Diameter 25in. approx.
M.I. Only 16/9

MULTI-METERS

CABY A10 Basic meter, sensitivity 155 micro-amps. A.C. and D.C. Ranges. £4/10/-. CABY B20. Sensitivity up to 10,000 ohms per volt. A.C. and -D.O. £6/10/-. TAYLOR MODEL 127A. 20,000 ohms per volt. 20 Megs. 20 Ranges. £10. S.A.E. will bring leadlet on any of above. Megs. 20 Rany of above.

V.H.F./F.M. A.M. 4 WAVEBAND RADIO RECEIVERS

Complete in beautiful veneered Walnut Cabinet. Covers normal Short, Medium and Long wavebands, plus V.H.F. Brand new and covered by usual 12 months' guarantee. 12 months' guarantee. For 200-250 v. 50 c.p.s. A.C. mains 12 Carr. 10/-

RADIOGRAM CABINETS

For callers only. Console type size. Beautiful traditional design. Worth £25 at least. Only 12 gns. Suitable AM/FM 3 waveband chassis £12/19/8. Table model type. Polished wainut finish 39/6. SPECIAL OFFER OF ASOVE CONSOLE CABINET and CHASSIS. 4-SPEED AUTOCHANGER and Sim. SPRAKER. A really exceptional opportunity.

Only

31 1/2 GNS.

RELAYS

Carpenters Type Polarised 2 x 9.500 turns at 1,685 ohms.

Carpenters Type Polarised 2x9.500 turns at 1,685 ohms. 19/6.
Miniature Mowing Coll Differential Type. Single pole 2-way, or center stable. Two colls each 350 ohms. Minimum operating current 140 micro-amps, nominal 400 micro-amps, maximum 8 milliamps. Two-way contact current 100 ma. at 6 v. A.C. or D.C. Size approx. 1½ x | x | fm. 19/6.
Miniature type G.E.G. 670 M1092 sealed, wire ends, 4 g/overs, platinum. 18/9.

FIELD TELEPHONES



Complete including bell. Suitable for office, ware-house, factory or outdoor communication. Operate with small dry battery lasting many months. Supplied complete in wooden carrying case. Only 59/6 Carr. 5/-

VARLEY 2 v. 14 A.H. EX GOVT. **ACCUMULATOR8**

New Boxed. Only 5/9 each, 3 for 15/-, plus 3/6 carr.

Open to callers at following branches:

5-7 County (Mecca) Arcade, Briggate, Leeds, I. 54-56 Morley Street (above Alhambra Theatre), Bradford. 8-10 Brown Street (Market St.), Manchester, 2.

(Leeds) LEEDS, BRADFORD R.S.C. Ltd. and MANCHESTER

Mail Orders to 29/31 Moorfield Road, Leeds, I For Terms see double page advert., pages 142 & 143

A SHORT LIST FROM **OUR VAST STOCK**

COSSOR "TRAVELLER'S FRIEND"
4 TRANSISTOR POCKET RADIO
Complete kit of parts to build this wonderful set. Size 6 x 3½ x 1½ins. Weight
17 ozs. Printed circuit, ferrite aerial,
2in. speaker. Original price 18 gns.

£7-19-6 Complete P. & P. 2/6

"EASY SIX" PORTABLE TRANSISTOR RADIO

Printed circuit, ferrite aerial, 5in. speaker, push-pull output. Long and Medium waves. Complete kit of parts.

P. & P. 1/6 £9-15-0

LABGEAR AUDIO POWER OUTPUT METER

Build this wonderful meter in an evening. Two ranges: 25 mW-1 W and 1 W to 10 W. Accuracy 5%. Complete kit.

£2-19-6 P. & P. 2/-

TAPE DECKS COLLARO STUDIO TAPE TRANSCRIPTOR 3 motors, 3 speeds 17, 32, 74. Push button controls. LIST PRICE 16 GNS.

£12-19-6 P. & P. 3/6

TRANSISTORS

P.N.P. Junction types.

AUDIO, suitable for high gain and low freq.
amplifiers, and for output stages up to
250 milliwatts. Double spot—yellow and

Each R.F. suitable for medium and low freq. oscillators, freq. changers and I.F. amplifiers (1.5 to 8 Mc/s.). Double spot—yellow and red.

7/6 Type T81. Suitable for all audio applications.

Post 6d.
One dozen 35/- post free Special prices quoted for large quantities.

AVANTIC STEREOPHONIC HI-FI AMPLIFIERS-

AT ALMOST HALF LIST PRICE WHILE EXISTING STOCKS LAST. BRAND NEW IN MAKER'S CARTONS—100—250 VOLTS—SMALL DEPOSIT SECURES.

PL6/21 10 WATT MONAURAL AMPLIFIER AND COMBINED PRE-AMPLIFIER CONTROL UNIT 5 Inputs. Size 14 in. wide, 9in. deep, 4in. high. 118 PRICE £29-8-0 CARR. & INS. 7/6.

SPA11 STEREO AMPLIFIER AND PRE-AMPLIFIER

Twin 10 watts output, 3-dimensional Monaural reproduction by combining both channels, 3 inputs for each channel. Size 14in. wlde, 4in. high, 8in. deep.

19 GNS.

CARR. & INS. 7/6

CARR. & INS. 7/6

STEP 11 STEREO PICK-UP PRE-AMPLIFIER

Size 73 × 48 × 2 16 in. LIST PRICE £6-16-6

£4-19-6

CARR. & INS. 7/6

£6-19-6 £7-19-6

£7-19-6

9 GNS.

£3-15-0

RECORD CHANGERS

B.S.R. U.A.8 complete with latest "ful-fi" cartridge

COLLARO CONQUEST 4 Speed auto

GARRARD RC120 4 Speed auto

COLLARO JUNIOR 4 Speed Single Play Complete with Arm and P.U. P. & P. 3/6.

CRYSTAL DIODES

General Purpose GBXOO, each 1/-, per doz. 9/-. All other types in stock. All types of Sub min. Condensors and Resistors. Send S.A.E. for our List of All Components.



DL7-35 POWER AMPLIFIER 54watt peak output. Freq. response 5 c/s-30 Kc/s ± 0dB. Two of these can be used in conjunc-tion with SP21/2

Pre-Amp. Con-trol Unit for stereophonic reproduction. Size 144 in. long, 9in. wide, 84 in. high.

£6-19-6

CARR. & INS. 12/6

SPECIAL OFFER TO ALL OUR CUSTOMERS Two DL7-35 Power Amplifiers and one SP21/2 Stereo Control Unit at a special price of 47 GNS.

Ideal for use in clubs, halls, public performances, etc.



SP21/2

STEREO PRE-AMPLIFIER CONTROL UNIT Twin channel. Designed primarily for use with two DL7 35 Power Amplifiers. Six inputs for each channel. LIST PRICE \$28-10-0

£16-19-6

CARR. & INS. 7/6

WIRECOMP ELECTRON

378 HARROW ROAD LONDON, W.9. TEL.: CUNNINGHAM 9530
Hours of business: 9 a.m. to 6 p.m. Open all day Saturday
Opposite Paddington General Hospital. Buses 18B & 36 pass the door.

RCA AR88 RECEIVERS.

One of the most renowned American Communications Receivers ever manufactured. Widely used by all the Armed Services to maintain World-wide Communications and Monitoring Posts under all conditions. Employs 14 valves, and has 6 switched overlapping wave bands for complete overage. Refinements include Mechanical Band Spread with Logging Scale, Automatic or Manual Volume Control. Automatic or Manual Noise Limiter, BFO with pitch control, RF and AF Gain Controls, Variable HF Tone Control, Variable Selectivity with Crystal Filter, Aerial Trimmer, Choice of Headphones or Speaker. Has internal mains power pack for nominal 115-230 volts A.C. In Black Crackled Case, size 19 in. W. x 11 in. H. x 19 im. D. Thoroughly reconditioned, immaculate in appearance, and in perfect working order. "D" Model covers 500 kc/s-32 Mc/s, price 245. "LF" Model covers 75-550 kc/s. and 1.5-30.5 Mc/s. Price 235 (add carriage 30/- and 50/- deposit on returnable transit case).

ROA Sin. P.M. SPEAKER in heavy black crackled metal case, size 114in. x 104in. x 6in. Designed for use with AR88 Receiver or any set with 3 ohms output. BRAND NEW IN MAKEE'S CARTONS. ONLY. (Post 3/6).

CANADIAN MOVING COLL PHONES. Low resistance, fitted noise excluding chamols ear muffs, and leather covered head-band. Lead terminates to jack plug. BRAND NEW. ONLY 19/6 (Post 1/6).

OSCILLOSCOPE No. 11 by Cossor. A First Grade L.F. Oscilioscope incorporating a Hard Valve Time Base with speeds of 1-5-40 milliseconds but easily converted for a few shiltings to produce 3 c.p.s. to 30 kc/s. Has High Class Amplifier with Fine and Coarse Gain controls, Brightness and Focus controls, X and Y shifts. A.C. mains pack for 118 v. -230 v. nominal, fully fuse protected. Employs 24 in. Tube ACR 10, Front panel 19 in. x 7 in. for rack mounting, depth 12 in., or can be used in Steel Transit Case on bench. Complete with suggested Modification data. BRAND NEW AND UNUSED. ONLY £12/10/- (carriage 15/-).

CARRYING CASES, solid leather. SLIGHTLY USED. Internal dimensions \$\frac{1}{2}\text{in}. \text{ K}. \times \$\frac{1}{2}\text{in}. \text{ V}. \times \$\frac{4}{2}\text{in}. \text{ D}. \text{ Value.} \text{ V} is the first runnent, Camera and accessories, etc. ONLY 25/-(postage 2/-).

BC 342 RECEIVERS. A few only of these famous American sets covering 1.15-18.0 Mojs. In six bands. Internal 115 v. A.O. Mains pack. A super receiver in first-class condition and perfect working order, ONLY £25 (carriage 15/-).

HEO MAINS POWER UNITS. A.C. Input 115/230 volts, Output D.C. (fully smoothed) 230 volts 75 mA., and 6.3 volts 3.5 amps. Complete in black crackled case ONLY 59/6.

12-WAY SCREENED CABLE. In 10ft. lengths, fitted with plugs, originally made for No. 19 Wireless Set. UNUSED. ONLY 15/- per lead.

P.M. SPEAKERS. 3in. 19/6, 61in. 17/6, 8in. 21/-, 12in. 29/6.

SPRAGUE CONDENSERS. Metal cased wire ends. New. .01 mfd. 1,000 v. and .1 mfd. 500 v. 7/6 per dozen. Special quotes for quantities.

HETERODYNE FREQUENCY METERS TYPE LMI4



Frequency range 125-20,000 kc/s. in 2 bands. This is the United States Navy Model of the well-known BC.221 Frequency Meter, but has many additional features which increase its usefulness. Voltage stabilisation of cuits and Crystal control ensure extreme accuracy, and in addition it is fitted with an Internal Modulation switch to allow use as a Signal Generator. Size only Shin. × Shin. Full information on request.

R1155 RECEIVERS.

The famous Bomber Command Receiver known the world over to be supreme in its class. Covers 5 wave ranges: 18.5-7.5 Mc/s 7.5-3.0 Mc/s. 1,500-600 kc/s., 500-200 kc/s., 200-75 kc/s. and is easily and simply adapted for normal mains use, full details being supplied. All sets thoroughly tested and in perfect working order before despatch, and on demonstration to callers. Fitted with latest type Super Slow Motion tuning assembly. Have had some use, but are in excellent condition. ONLY £9/19/6.

A.C. MAINS POWER PACK OUTPUT STAGE in black metal case to match receiver, enabling it to be operated immediately.

A.C. MAINS POWER PACK OUTPUT STAGE in black metal case to match receiver, enabling it to be operated immediately by just plugging in, without any modification. Fitted with Sin. P.M. speaker £6/10/-. DEDUCT 10/- IF PURCHASING RE-, CEIVER AND POWER PACK TOGETHER.
Send S.A.E. for illustrated leafet, or 1/3 for 14-page booklet which gives technical information, circuits, etc., and is supplied free with each receiver. Add carriage 10/6 for Receiver, 5/- for Power Unit.

10,000 O HMS PER VOLT TESTMETER

This latest Caby model is a handy pocket sized tester 51 x 32 x 21in. Reads low D.C. voltages at 10,000 ohms per volt, up to 1,000 v. A.C. and D.C. at 4,000 o.p.v. Resistance to 20 megs. D.C. current to 250 milliamps and also Decibels. Complete with Test Leads, Batteries and Instruction Book. ONLY £6/10/-.



DOUBLE BEAM OSCILLOSCOPE TUBES

Type CV 1596 equivalent to Cossor O9D as used in oscilloscopes by Cossor (339 series). Hartley and Erskine (13 series). Listed at £12/10/-.

Our price £2/19/6 (carriage 5/6) Brand new in makers' crates

W 1191A WAVEMETER

Crystal controlled heterodyne frequency meter covering 100 kops to 20 Mc/s. in 8 switched bands and is wirtually the British BC21. Power requirements 2 v. L.T. and 40-60 voits H.T. Complete with Calibration Book. Orystal, Operating Valves and full set of spares. BRAND NEW IN ORIGINAL TRANSIT CASES. ONLY 259110/6 (carriage 15/-).

METERS

		_				
	F.S.D.	SI	ZE A	ND	TYPE	PRICE
25	microamps	D.C.	2lln.	Proj.	circular	59/6
50	microamps	D.C.	2}in.	Flush	circular	59/6
50	microamps	D.C.	3jin.	Flush	circular	80/-
100	microamps	D.C.	2lin.	Flush	circular	39/6
- 1	milliamp	D.C.	2in.	Flush	square	22/6
1	milliamp	D.C.	2lin.	Flush	circular	30/-
1	milliamp	D.C.	22in.	Flush	circular -	25/-
1	milliamp	D.C.		Flush	circular	50/-
200	milliamp	D.C.	2lin.	Flush	circular	12/6
20	amps	D.C.	2in.	Proj.	circular	7/6
40	атрв.	D.C.	2in.	Proj.	circular	7/6
5	amps	D.C.	2ln.	Flush	square	12/6
300	volts	A.C.	2lin.	Flush	circular	25/-
500	volts	A.C.	2lin.	Flush	circular	25/-
			_			

V.H.F. RECEIVER TYPE R.1392. A superb 15-valve superhet receiver covering 95-150 Mc/s. (2-3 Metres), being fully tunable over that range, with provision for Crystal Control. Has 2 stages of B.F., 3 of I.F. BFO. 4GC, etc. Fitted with Zun. square meter for Oscillator and Audio Signal-checking. Size 19m. × 10m. × 10m. × 10m. Used but in very good order, thoroughly air tested before despatch. Power supply required: 240-250 voits at 80 mA., and 6.3 voits at 4 amps. Complete with valves and circuit diagram. ONLY 79/8 (carriage, etc., 10/6).

HIGH FREQUENCY A.C. VOLTMETER. A first-grade moving iron instrument with 6in, Mirror Scale reading up to 150 volts A.C. at 400 and 1,200-2,400 cycles. In substantial cask case with removable ind, overall size \$4 \text{in} \times \frac{3}{6} \text{in} \times \frac{5}{6} \text{in} \text{and in perfect order.} Brand new and unused. ONLY \$2/710/- \text{Can also be supplied for 50 cycles use, either 0-150 volts or 0-300 volts, same price.

POWEE UNIT TYPE 3. Primary 200/250 volts A.C., 50 oycles. Outputs of 250 volts 100 mA., and 6.3 volts 4 amps. Pitted double smoothing and 2 meters to read E.T. current and voltage. For normal rack mounting (or bench use) having grey front panel. Size Ibin. x 7in. BRAND NEW. ONLY 79/6 (carriage 7/6).

INTERCOM. TELEPHONE SET. Two pairs of Brand New Headphones connected to Breast Microphones, with leads, etc., in fitted carrying cases. Supplied with 4½ volt battery, 10 yards twin flex, and full instructions for connecting to make super intercom. ONLY 27/6. (Post 3/6). Extra flex 3d. per yard.

RECEIVER R107. A few more of these fine receivers. 9 valves, 3 wavebands covering 1.2-17.0 Mc/s. (18-250 metres), incorporating built-in speaker and 2 power packs for use on 100-250 voits A.C. or 12 voits D.C. in mgnificent condition, the finest we have yet had ONLY 215 (carriage £1). A few solled sets at lesser prices to callers only.

12 VOLTS AMERICAN DYNAMOTOR. Delivers 220 volts at 100 mills. Size 5½ × 3½in. diameter. Ideal for running Radio and Electric Shaver, etc., from car batter. ONLY 32/6.

MARCONI SIGNAL GENERATOR TF 144G/7. Coverage 83 kc/s.-2.5 Me/s. and 8 Mc/s.-70 Mc/s. Complete, and in AS NEW CONDITION. ONLY £95.

AMPLIFIER N24



Utilises 4 valves, 1 each 524G, 676G, 6J7G, 6J5G and high quality components such as "C" Core Transformers and Block Paper Smoothing Condensers. A.C. Mains Pack for nominal 110×230 volts. Provision for 600 ohms or High Impedance input. Output to 600 ohm Line. For normal use only requires changing Output Transformer. Output approximately 4 watts. Designed for Standard Rack Mounting, having grey front panel size 19in. X 7in. All connections to rear panel, front having "On/Off" Switch. Gain Control, Indicator Light. Fuses and Valves Inspection Panel. BRAND NEW IN MAKER'S PACKING. ONLY 24/9/6 (carriage 10/6).

Cash with order please, and print name and address clearly PLEASE ADD POSTAGE OR CARRIAGE COSTS ON ALL ITEMS

ELECTRON (LONDON) LTD.

Radio Corner, 138 Gray's Inn Road, London, W.C.1. Phone: TERMINUS 7937

Open until I p.m. Saturdays.

We are 2 mins, from High Holborn (Chancery Lane Station) and 5 mins, by bus from King's Cross,

HARVERSON SURPLUS CO. LTD.

83 HIGH STREET, MERTON, S.W.19. CHERRYWOOD 3985/6/7

Special Offer

Mullard OC. 76 —10/6. Matched Pair— £1.0.0 Don't miss this —P. & P. 6d.

MINIATURE AMPLIFIER

Miniature amplifier, size $3\frac{1}{4} \times 2\frac{1}{2} \times 4\frac{1}{2}$ ins. Ideal for record player, etc. Controls, volume/on-off, bass and treble. Supplied ready built, less valves (UY85, UF89, UL84), and mains transformer, at the give away price of 14/= P.& P. 2/6.

HARVERSON SUPERHET 4 KIT

A medlum and long wave superhet, incorporating two I.F. stages, modern B9 valves (UCHBI, UBF89, UCL83, UPS9), built-in ferrite rod aerial. All you need supplied from theoretical wiring diagram to last nut and bolt (main components ready mounted), including an attractive contemporary styled cream plastic cabinet with gold trimmings. Size II½ x 4½ x 6½in.

PRICE £6.12.6 Post 3/6.

12 Wire wound Colvern Pots—all different values. 10/6 P. & P. 9d.

THE FAMOUS E.M.I. ANGEL TRANSCRIPTION P.U. (Model 17A)

A Pick-up for the connoisseur originally priced at £17.10.0. The last remaining few offered at £4.10.0 Plus P. & P. 5/-.

500-500 Twin gang condensers with geared slow motion drive. 3/6 each. 36/- per doz. P. & P. 6d.

A few only—Transistor record player cases in light grey cloth—complete with motor board. Size—12" x 8" x 6"—18/6 each. P. & P. 1/9.

EXTENSION SPEAKER

An attractive cabinet 8 x 6 x 2in. fitted with 3 ohm 5in. speaker complete with lead, a few only.

19/6 P. & P. 2/6.

This Month's Bargain

Complete and ready for your cabinet, 4 valve superhet chassis, complete with valves, ferrite aerial, dial and knobs. Valve line up—UCHBI; UBF89; UCL83; UY85. L and M wave. Price £4/19/6 P. & P. 3/6.

MIDGET GRAM AMPLIFIER READY-BUILT with Speaker

A $2\frac{1}{4}$ watt gram amplifier, fitted with bass, treble, and vol./on-off controls. Supplied complete with 6 x 4in. 3Ω speaker, valves (UY85, UF89, UL84), knobs, etc., all mounted on an attractive baffle board, size $10\frac{1}{4}$ x $7\frac{1}{2}$ ins.

OUR PRICE 49/- P. & P. 3/-

SPEAKER FRET

Super quality heavily woven fret. 54 inches wide. Usual price 50/- per yard. P. & P. I/-.

OUR PRICE, 19/- per yard

MIDGET I.F. TRANS & COILS

A pair of midget 465 kc/s. I.F. transformers, plus LW and MW coils,

OUR PRICE 10/- per set. P. & P. 1/9.

CYLDON 12 CHANNEL

TURRET TUNERS

New purchase offered at still lower

with PCC84 and PCF80 valves and 8 sets of Coils for 5 Band I channels

and 8, 9, 10 Band III. New and

Value over £7

OUR PRICE, Post paid.

unused.

I.F. 33-38 Mc/s. Complete

32/6

TRANSISTOR BARGAINS OC71 ALL MULLARD FIRST GRADE 810C72 81121-

OC71	*** ***	8/- 12/-
OC72		12/-
OC72	Matched Pair	25/-
OC45	Green Spot	15/-
OC45	Blue Spot	15/-
OC44		15/6
SB305	Semi Conductor	10/6
OA41	Diode	3/6
	Postage on all the above 6d.	/

- RECORD CHANGERS -

	LCOND CHANGERS	
GARRARD	RC 98 Mk, 4H, 4-speed autochange RC 120/D Mk, 2 RC 120 Mk, 4D """ RC 120 Mk, 4H """ RC 121 Mk, 1 """ RC 121 Mk, 4H """ RC 121/40 Mk, 2 """	£16,10.0 £9, 0, 0 £9, 0, 0 £9, 0, 0 £11.0, 6 £11.0, 6
COLLARO	RC 54 4-speed autochanger RC 594 , Conquest ,	£6.19, 6 £7.19, 6 £6.12, 6 £7.19, 6
B.S.R.	Monarch UA8 4 speed autochange TU8 4-speed single player less pick-u	

Carriage and ins. on each of above 5/- extra.

NOTE: Any of the above with Stereo Cartridge and Fittings, 16/- extra.

- TAPE DECKS -

MONAURAL AMPLIFIER

This amplifier as illustrated, made by a leading manufacturer. Mullard valves—ECCB3, EL84 x EL84, EZ80, Bass, Treble and Volume on remote panel. Elegant Knobs. OUR PRICE one month only £4.16.6 plus P. & P. 3/6.

RECTIFIERS FOR BATTERY CHARGERS

12	v	1	amp.	4/3	12 v. 4 amp.	12/6
			amp.	7/-	12 v. 5 amp.	14/6
12	٧.	3	amp.	10/-	P. & P. 6d.	

PICK-UP CARTRIDGE

BARGAINS	
STUDIO P	17/6
ACOS HIGH G	17/6
E.U. POWER POINT	12/6
RONETTE	18/6
G.C.Z.	
P. & P. I/	,.

COSSOR C.R.T. SNIP

108K 10-inch. New and boxed,

15/-, plus 6/- P. & P.

75K 10-inch. New and boxed.

15/-, plus 6/- P. & P.

ION TRAP MAGNETS

To suit the above, 2/9 each. P. & P. 3d.

CONDENSER / RESISTOR PARCEL

50 mixed P.F. Condensers and 50 mixed Resistors. An assortment of useful values. All popular sizes—all new—a must for the serviceman and constructor. ONLY 10/-. P. & P. 1/-.

GUARANTEED VALVES *
NEW and BOXED *
PROMPT DISPATCH *
POST 6d. per Valve extra *

YOU ARE INVITED!

Spend a day browsing around our premises at 83 HIGH ST., MERTON, S.W.19 (one minute South Wimbledon Tube.)

We have a wealth of components, valves, chassis, tape decks, autochangers, amplifiers, F.M. tuners, record players, tape recorders, cabinets, and a whole host of other things we just don't have the space to describe. Please come and look for yourself. We will be pleased to see you, and there's no obligation to buy.

STEREO AMPLIFIER

Complete with 2 Loudspeakers. A compact amplifier combining latest features with good reproduction, and ample volume. Complete with valves (ECL82, ECL82, EZ80), panel, knobs, etc. and 2 matched 3Ω loudspeakers. Few only—Order Now. Plus 4/6 P, & P.

н	ATP4	2/2	EB34	3791	ECL82	0/0.	EY51	0/2	KTZ41	919	PY80	797	U50	P0 / O	UL41	0.10	1CbGT	3210	100	m /	6AQ5	797 -	ana	410	ATTENT	0.00
н	AZ1		EB41		EF41		EY86		N37		PY81		176		UL44								6D6	4/6	6K7M	6/8
ж	AZ31		EBC33		EF42		EZ40									25/-	1Db	11/9			6AT6		6CH6	9/9	6K8G	7/-
я											PY82		U801		UL46	25/-	1D6	11/9			6AU6			7/-	6K6GT	6/6
ш	B36		KBC41		EF50		EZ80		N339		P¥83		UABC			8/6	1HbGT		5U4G		6B8G		6F6M		6K7GT	5/€
я	CBL31		EBF80		EF80		EZ81		QZ4		PZ30		UAF42		UU6		1L4		5V4		6BA6		6F1	13/-	6K8GT	9/5
п			EBF89		EF85		EZ90		P61		PEN4		UBC41		UU8	25/-	1LD5	3/-	5Y3G	7.6	6BE6	7/8	6F13	13/-	6 K 25	18/E
я	CL4		ECC81		EF86		GZ32		PCC84	8/6			UBF80			11/9	IN5	9/9	5Y3GT	7/6	6BG6G	22/-	6F15	13/-	6L1	14/6
п	CL33	18/	ECC82		EF89		KT32	9/3	PCF80	9/-	SP41	2/9	UCC84	10/-	UY21	11/9	1R5	7/-	5Z4G	8/6	6BH6	8/6	6F17	11/9	6L6G	7/1
н	CY31		ECC83		EF91		KT33C						UCC85	10/6	UY41	71-	184	9/9	5Z4M	9/6	6BJ6	8/6	6F33		6L6M	9/-
ш	DAF96		ECC84		EL38		KT36	28/-	PCL82	11/6	BP4/5	9/9	UCF80	15/6	UY85	6/6	185	6/-	6A7	10/6	6BR7	11/9	6H6		6L7G	71
н	DF96		ECC85		EL41	9/8	KT55	10/3	PCL83	13/6	SP4/7	9/9	UCH42	9/9	VP41-	- 8/-	1T4		6A8G	8/6	6BW6		6H6GT		6L18	10/%
и	DH63		ECF80			9/6	KT61	9/6	PL38	16/6	T41	22/-	UCH81	9/9	VP133	14/-	2X2		6AC7	6/-			6J5GT		6L19	14/-
п	DK96		ECF82			15/6	KT63	7/-	PL36	14/6	U22	7/6	UCL82	15/6	X22	16/9	3A4		6AG5		6C4				6N7GT	7/-
ш	DL96		ECH21		EL84	8/6	KT66	16/-	PL81	11/9	U25	13/-	UCL83	11/6	1A3	3/-	3A8GT		6AK5	6/-			6.16	5/6	6P28	25/-
в	EA50		ECH42		EM84	8/9	KT88	21/-	PL82	8/-	U26	11/9	UF41	8/6	LASGT	5/6	3D6		6AL5		6C6		6J7G		6Q7G	7/-
н			ECH81			9/3	KTW61	6/-	PL83 .	11/-	U37	25/-	UF85	8/6	1A7GT	11/9	304		6AM5	11/9	6C31		6J7M		6Q7GT	9/-
в	EAF42	9/6	ECL80	9/8	EM81	9/8	KTW63	7/-	PX25	11/9	U45	14/-	UF89	8/6	1C2	11/-	3Q5GT	- 9/- 1	6AM6		6CD6G				68A7GT	

Confinental 6

COMBINED PORTABLE/CAR

EQUALLY SENSATIVE ON MEDIUM AND LONG WAVE BANDS

SPECIFICATION

- 425mW Push-Pull Output
- 6 "Top grade" Ediswan Transistors
- New Type Printed Circuit with all Components Marked
- Full Medium and Long Wave Tuning
- High "O" Internal Ferrite Aerial
- Car Radio Adaptation and AVC
- Slow Motion Fingertin Tuning
- " Hi-Fi " Quality Speaker
- Size 9½ x 7½ x 3½in. Weight 4½lb.

ALL COMPONENTS AVAILABLE SEPARATELY Wherever you are

" First Class in every way "



ALL THE CONTINENTAL AND LOCAL STATIONS AT YOUR FINGERTIPS

CALL FOR DEMONSTRATION

- * STEP BY STEP FULLY ILLUS-TRATED INSTRUCTIONS
- ALL COMPONENTS GUARANTEED * AFTER SALES SERVICE

Total Cost of all Components £11.10.0 P.P. 3/6

including Cabinet, Battery Transistors, Car Radio, AVC and all necessary items.

- * SIMPLE TO CONSTRUCT
- ★ NO TECHNICAL KNOWLEDGE REQUIRED
- * WORTH DOUBLE WHEN BUILT
- * EXCELLENT RESULTS ANYWHERE

DESCRIPTIVE LEAFLET FREE

RANGER-3

PERSONAL POCKET RADIO

LL TUNING OF MEDIUM WAVEBAND AND AMATEUR TOP BAND (120 metres to 500 metres)

OLUXEMBOURG GUARANTEED

- O NO EXTERNAL AERIAL OR EARTH

(where normally receivable)

*Full Station Separation

*Calibrated Dial

*Fingertip Control

*6 Months' Battery Life

Fitted Volume Control
3 High Gain Transistors ★ Size 4% x 3 x 1¼in.

TOTAL COST with Personal Earphone, Battery Transistors, etc. 79/6 P.P. 1/6.

All parts sold separately and guaranteed

Full Instructions and Prices FREE On Request
Continental as well as local stations—GUARANTEED!

MEDIUM LONG AND

SEVEN TRANSISTOR SUPERHET

* PRE-BUILT UNITS *

SPECIAL OFFER

6 MULLARD

- THE NEW EASY WAY TO BUILD A RADIO—Press Button Short, Medium and Long Wave Coil Pack: OC170 OSC/Mixer stage. Printed Circuit. Pre-aligned and Tested. 67/6 P.P. 1/6. Plus 22/9 P.T.
 Printed Circuit IF Strip, 2-OC169, Pre-aligned and Tested 92/6 P.P. 1/6.
 One Watt 4-Transistor Hi-Fi Amplifier. Printed Circuit, 92/6 P.P. 1/6.
- 92/6 P.P. I/6.
 8 inch Ferrite aerial with coils, 12/6. 176pF-176pF Tuner
 - above, 9/6.

FULLY ILLUSTRATED BOOKLET SHOWING INTERCONNECTION OF ABOVE 2/6

SPECIAL OFFER 6 EDISWAN TRANSISTORS
AND TWO DIODES
I—XAI02
2—XAI01 ONLY

1-XB103 2-XC101 57/6 PER SET and 2 Diodes

TRANSISTORS AND TWO DIODES 1--OC44 -OC45 1---OC71 -OC72

PER SET and OA81





"STEREO

STEREO RECORD PLAYER AMPLIFIER

New high-gain circuit with full tone, balance and volume controls. Can be used with all types of records as well as Can be stereo.

★2 WATTS PEAK PER CHANNEL ★ ECC83; 2-ECL82 VALVES ★ MAINS 110/250V A.C.

Complete with speaker sockets, calibrated dials, etc. BUILT and TESTED P.P. 2/-.

** COLLARO 4-SPEED STEREO
AUTO-CHANGER, ideal for use
with above amplifier £7/10/0, P.P. 3/6.
** 9 x 6in, large magnet Elac speaker,
for use with STEREO 3-D, 37/- pair.
P.P. 1/6.

PRACTICAL TRANSISTOR CIRCUITS

GADGETS

RECEIVERS No 2. AMPLIFIERS TEST UNITS TRANSMITTERS All transistor

contains 40 Easy to Transistor Circuits for the home constructor diagrams and prices.


3'6 POST FREE

TRANSMITTER/RECEIVER Army Type 17 Mk. II

Complete with Valves, High Resistance Head-phones. Handmike and

phones. Handmike and circuit. Frequency range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120 v. L.T. Ideal for Civil Defence and communications. BRAND NEW

45/- P.P. 5/-.

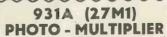

BRAND NEW, ORIGINAL CARTONS 80/- P.P. 1/-. BASE 2/-

OUARTZ **CRYSTALS**

FOR TRANSMITTING RADIO CONTROL, OSCILLATORS, ETC.

Request

Free List on ALL TYPES FOR ALL PURPOSES





TRANSISTORS

From **EACH**

SEND FOR NEW FREE LIST WITH DATA AND USES FULLY GUARANTEED We can Supply a Transsistor for Every Need!

VALVES

TRANSMITTING RADIO AND TV VALVES, TUBES

AND INDUSTRIAL

TYPES.

NEW FREE LIST ON REQUEST.



STANDARD AND MINIATURE COMPONENTS

We stock the largest range of components in the country for the home constructor.



We Have Your Item in Stock

FREE LIST REQUEST. AND DATA

ONLY

62/6

5 HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON W.2

Opposite Edgware Road Tube Station, PADdington 1008/9. OPEN MONDAY to SAT. 9-6 .THURS. I o'clock

TRADE ENQUIRIES INVITED ON ALL ITEMS

QUOTATIONSBYRETURN

KINSONS ESTA

F.S.D. \$ize Type Price 100 Microamp 3 in. MC/FR 80/- 50 Microamp 2 in. MC/FR 770/- 500 Microamp 2 in. MC/FR 37/6 500 Microamp 2 in. MC/FR 37/6 500 Microamp 2 in. MC/FR 37/6 1 Milliamp 2 in. MC/FR 35/- 30 Milliamp 2 in. MC/FR 15/- 100 Milliamp 2 in. MC/FR 15/- 100 Milliamp 2 in. MC/FR 15/- 100 Milliamp 2 in. MC/FR 35/- 50 Mpere 2 in. MC/FR 35/- 5 Ampere 2 in. MC/FR 35/- 5 Ampere 2 in. MC/FR 35/- 50 Volts 2 in. MC/FR 35/- 500 Microamp 2 in. MC/FR 35/- 500 Microamp 2 in. MC/FR 35/- 500 Microamp 2 in. MC/FR 35/- 500 Microamp 2 in. MC/FR 25/- 500 Wolts 2 in. MC/FR 27/6 5 Milliamp 2 in. MC/FR 27/6 5 Milliamp 2 in. MC/FR 27/6 6 Wolts 2 in. MC/FR 27/6 5 Amps 2 in. MC/FR 27/6 6 Amps 2 in. MC/FR 27/6 5	MICIEKS	GUA	KANICI	-
100 Microamp 3½in. MC/FR 80/	F.S.D.	Size	Type	Price
50 Microamp 2½in. MC/FR 70/- 250 Microamp 2½in. MC/FR 37/6 10 Milliamp 2½in. MC/FR 35/- 2 Milliamp 2½in. MC/FR 25/- 30 Milliamp 2½in. MC/FR 15/- 100 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 15/- 3 Ampere 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 10 Ampere 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 35/- 5 Milliamp 2in. MC/FR 35/- 5 Milliamp 2in. MC/FR 25/- 10 Milliamp 2in. MC/FR 25/- 10 Milliamp 2in. MC/FR 27/6 30 Volts 2½in. MC/FR 27/6 40 Volts 2½in. MC/FR 27/6 40 Volts 2½in. MC/FR 27/6 40 Volts 2½in. MC/FR 27/6 5 Amps 2½in. MC/FR 27/6 5 Amps 2½in. MC/FR 27/6 5 Amps 2½in. MC/FR 12/6 5 Amps 2½in. MC/FR 12/6 5 Amps 2½in. MC/FR 12/6 5 Amps 2½in. MC/FR 15/6 5 Amps A.C. 4½in. MI/FR 7PR 65/-				80/-
250 Microamp 2½in. MC/FR 37/6 100 Microamp 2½in. MC/FR 37/6 1 Milliamp 2½in. MC/FR 35/- 2 Milliamp 2½in. MC/FR 25/- 30 Milliamp 2½in. MC/FR 15/- 100 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 35/- 3 Ampere 2½in. MC/FR 35/- 3 Ampere 2½in. MC/FR 35/- 3 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 50 Microamp 1 Milliamp 2in. MC/FR 25/- 5 Milliamp 2in. MC/FR 25/- 5 Milliamp 2in. MC/FR 25/- 5 Milliamp 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 15/6 5 Amps A.C. 4in. MI/F or PR 65/-				
500 Microamp 2½in. MC/FR 37/6 2 Milliamp 2½in. MC/FR 35/- 2 Milliamp 2½in. MC/FR 35/- 30 Milliamp 2½in. MC/FR 15/- 100 Milliamp 2½in. MC/FR 15/- 100 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 35/- 3 Ampere 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 5 Milliamp 2in. MC/FR 25/- 5 Milliamp 2in. MC/FR 27/6 30 Volts 2½in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 15/6 5 Amps A.C. 4in. MI/FR 7 PR 65/-	250 Microamp		MC/PR	
1 Milliamp 2½in. MC/FR 35/- 2 Milliamp 2½in. MC/FR 15/- 30 Milliamp 2½in. MC/FR 15/- 100 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 31 Milliamp 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MI/FR 30/- 5 Amps A.C. 4in. MI/F or PR 65/-	500 Microamp		MC/FR	
2 Milliamp 2½in. MC/FR 25/- 30 Milliamp 2½in. MC/FR 15/- 100 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 15/- 200 Milliamp 2½in. MC/FR 15/- 3 Ampere 2½in. MC/FR 35/- 3 Ampere 2½in. MC/FR 35/- 10 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 31 Milliamp 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 15/6 60-0-50 Amps 2in. MC/FR 15/6 60-0-50 Amps 2in. MC/FR 12/6 5 Amps A.C. 3½in. MI/FR 7/6 50 Amps A.C.	1 Milliamp		MC/FR	
30 Milliamp 2½in. MC/FR 15,- 100 Milliamp 2½in. MC/FR 15,- 200 Milliamp 2½in. MC/FR 15,- 1 Ampere 2½in. MC/FR 35,- 5 Ampere 2½in. MC/FR 35,- 5 Ampere 2½in. MC/FR 35,- 10 Ampere 2½in. MC/FR 35,- 20 Volts 2½in. MC/FR 35,- 30 Volts 2½in. MC/FR 35,- 40 Volts 2½in. MC/FR 35,- 40 Volts 2½in. MC/FR 35,- 500 Microamp 2in. MC/FR 27,6 5 Milliamp 2in. MC/FR 27,6 5 Milliamp 2in. MC/FR 27,6 30 Volts 2in. MC/FR 27,6 30 Volts 2in. MC/FR 27,6 30 Volts 2in. MC/FR 27,6 40 Volts 2in. MC/FR 27,6 30 Volts 2in. MC/FR 27,6 40 Volts 2in. MC/FR 27,6 5 Amps 2in. MC/FR 27,6 5 Amps 2in. MC/FR 12,6 5 Amps AC. 4in. MI/FR 7,6 65,6	2 Milliamp			
100 Milliamp 2½in. MC/FR 15,- 200 Milliamp 2½in. MC/FR 35/- 1 Ampere 2½in. MC/FR 35/- 3 Ampere 2½in. MC/FR 35/- 10 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 27/6 5 Milliamps 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 O-0-50 Amps 2in. MC/FS 27/6				
200 Milliamp 2½in. MC/FR 15/- 3 Ampere 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 10 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 25/- 5 Milliamp 2in. MC/FR 27/6 30 Volts 2½in. MC/FR 27/6 30 Volts 2½in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 30/- 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps A.C. 2½in. MI/FR 7/6 5 Amps A.C. 4in. MI/FR 7 PR 65/-	100 Milliamp		MC/FR	
1 Ampere 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 10 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 20 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps AC. 3¼in. MI/FR 30/- 2½in. MI/FR 7/6 50 Amps A.C. 4in. MI/FR PR 65/-	200 Milliamp		MC/FR	
3 Ampere 2½in. MC/FR 35/- 5 Ampere 2½in. MC/FR 35/- 10 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 5 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 30 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 15/6 5 Amps A.C. ½in. MI/FR 7/6 50 Amps A.C.			MC/FR	35/-
5 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 20 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 27/6 5 O-0-50 Amps 2in. MC/FR 15/6 5 O-0-50 Amps 2in. MC/FR 15/6 5 O-0-50 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 15/6 5 O-0-50 Amps 2in. MC/FR 12/6 5 Amps A.C. 3½in. MI/FR 30/- 25 Amps A.C. 4in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-	3 Ampere		MC/FR	35/-
10 Ampere 2½in. MC/FR 35/- 20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 20 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 3 Amps 2in. MC/FR 27/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 30/-0-30 Amps 2in. MC/FS 27/6 30-0-30 Amps 2in. MC/FS 12/6 50-0-50 Amps 2in. MC/FS 30/-0-30 Amps 2in. MC/FR 12/6 50 Amps 2in. MC/FR 15/6 50-0-50 Amps 2in. MC/FS 30/-0-30 Amps 2in. MC/FS 12/6 50 Amps A.C. 3½in. MI/FR 30/- 25 Amps D.C. 2½in. MI/FR 7/6 50 Amps A.C.			MC/FR	35/-
20 Volts 2½in. MC/FR 35/- 30 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 27/6 10 Milliamps 2in. MC/FR 27/6 20 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 27/6 3 Amps 2in. MC/FR 27/6 3 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 13/6 5 Amps 2in. MC/FR 15/6 5 Amps 2in. MC/FR 13/6 5 Amps A.C. 3½in. MI/FR 30/- 25 Amps A.C. 4in. MI/FR 7/6 5 Amps A.C. 4in. MI/FR PR 65/-		2₹in.	MC/FR	35/-
30 Volts 2½in. MC/FR 35/- 40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 10 Milliamps 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 12/6 3 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 50-0-50 Amps 2in. MC/FS 12/6 500 Milliamps A.C. 3½in. MI/FR 30/- 25 Amps D.C. 2½in. MI/FR 30/- 50 Amps A.C. 4in. MI/F or PR 65/-			MC/FR	35/-
40 Volts 2½in. MC/FR 35/- 500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 10 Milliamps 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 5 Amps 2in. MC/FR 27/6 3 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 50-0-50 Amps 2in. MC/FS 12/6 500 Milliamps A.C. 3½in. MI/FR 30/- 25 Amps D.C. 2½in. MI/FR 7/6 50 Amps A.C. 4in. MI/FR 7/6	30 Volts		MC/FR	35/-
500 Microamp 2in. MC/FR 25/- 1 Milliamp 2in. MC/FR 27/6 5 Milliamp 2in. MC/FR 27/6 10 Milliamps 2in. MC/FR 27/6 20 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FS 27/6 50-0-50 Amps 2in. MC/FR 15/6 500 Milliamps A.C. 3\darksin. MI/FR 30/- 25 Amps D.C. 2\darksin. MI/FR 30/- 25 Amps A.C. 4in. MI/FR 7/6 50/FR 15/6 50 Amps A.C. 4in. MI/FR 7/FR 65/-	40 Volts	2½in.	MC/FR	35/-
5 Milliamp 2in. MC/FR 27/6 10 Milliamps 2in. MC/FR 27/8 20 Volts 2in. MC/FR 27/8 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 O-0-50 Amps 2in. MC/FS 12/6 50-0-50 Amps 2in. MC/FS 12/6 500 Milliamps A.C. 3\darklet{\text{in}} \text{MI/FR} 30/- 25 Amps D.C. 2\darklet{\text{in}} \text{MI/FR} 30/- 50 Amps A.C. 4in. MI/F or PR 65/-	500 Microamp	2in.	MC/FR	25/-
5 Milliamp 2in. MC/FR 27/6 10 Milliamps 2in. MC/FR 27/8 20 Volts 2in. MC/FR 27/8 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 5 O-0-50 Amps 2in. MC/FS 12/6 50-0-50 Amps 2in. MC/FS 12/6 500 Milliamps A.C. 3\darklet{\text{in}} \text{MI/FR} 30/- 25 Amps D.C. 2\darklet{\text{in}} \text{MI/FR} 30/- 50 Amps A.C. 4in. MI/F or PR 65/-	1 Milliamp	2in.	MC/FR	27/6
10 Milliamps 2in. MC/FR 27/6 20 Volts 2in. MC/FR 27/6 30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FS 27/6 3 Amps 2in. MC/FS 27/6 30-0-30 Amps 2in. MC/FS 27/6 50-0-50 Amps 2in. MC/FS 15/6 500 Milliamps A.C. 3\(\frac{1}{2}\)in. MI/FR 30/- 25 Amps D.C. 2\(\frac{1}{2}\)in. MI/F 77/6 50 Amps A.C. 4in. MI/F or PR 65/-	5 Milliamp	2in.	MC/FR	
30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FS 27/6 30-0-30 Amps 2in. MC/FS 27/6 50-0-50 Amps 2in. MC/FS 15/6 500 Milliamps A.C. 3\frac{1}{2}in. MI/FR 30/- 25 Amps D.C. 2\frac{1}{2}in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-	10 Milliamps	2in.	MC/FR	
30 Volts 2in. MC/FR 27/6 40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 12/6 5 Amps 2in. MC/FS 27/6 30-0-30 Amps 2in. MC/FS 27/6 50-0-50 Amps 2in. MC/FS 15/6 500 Milliamps A.C. 3\frac{1}{2}in. MI/FR 30/- 25 Amps D.C. 2\frac{1}{2}in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-		2in.	MC/FR	27/6
40 Volts 2in. MC/FR 27/6 15 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 30-0-30 Amps. 2in. MC/FS 15/6 50-0-50 Amps 2in. MC/FS 15/6 500 Milllamps A.C. 3½in. MI/FR 30/- 25 Amps D.C. 2½in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-	30 Volts	2in.	MC/FR	
15 Amps 2in. MC/FR 12/6 3 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 30-0-30 Amps 2in. MC/FS 15/6 50-0-50 Amps 2in. MC/FR 15/6 500 Milliamps A.C. 3\dark{\frac{1}{2}}\tilde{\text{in}}. MI/FR 30/- 25 Amps D.C. 2\dark{\frac{1}{2}}\tilde{\text{in}}. MI/FR 70/- 50 Amps A.C. 4in. MI/F or PR 65/-	40 Volts	2in.	MC/FR	27/6
3 Amps 2in. MC/FS 27/6 5 Amps 2in. MC/FS 27/6 30-0-30 Amps 2in. MC/FR 15/6 50-0-50 Amps 2in. MC/FR 12/6 500 Milliamps A.C. 3\(\frac{1}{2}\)in. MI/FR 30/- 25 Amps D.C. 2\(\frac{1}{2}\)in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-	15 Amps		MC/FR	12/6
30-0-30 Amps. 2in. MC/FR 15/6 50-0-50 Amps 2in. MC/FS 12/6 500 Milllamps A.C. 3\frac{1}{2}in. MI/FR 30/- 25 Amps D.C. 2\frac{1}{2}in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-	3 Amps	2in.	MC/FS	27/6
30-0-30 Amps. 2in. MC/FR 15/6 50-0-50 Amps 2in. MC/FS 12/6 500 Milllamps A.C. 3\frac{1}{2}in. MI/FR 30/- 25 Amps D.C. 2\frac{1}{2}in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-		2in.		27/6
500 Milliamps A.C. 3½in. MC/FS 12/6 500 Milliamps A.C. 3½in. MI/FR 30/- 25 Amps D.C. 2½in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-		2in.		15/6
500 Milliamps A.C. 3\frac{1}{2}in. MI/FR 30/- 25 Amps D.C. 2\frac{1}{2}in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-	50-0-50 Amps	2in.	MC/FS	12/6
25 Amps D.C. 2½in. MI/FR 7/6 50 Amps A.C. 4in. MI/F or PR 65/-	500 Milliamps A.C	. 3½in.	_ MI/FR	
50 Amps A.C. 4in. MI/F or PR 65/-			MI/FR	7/6
300 Volte A C 91in MI/FR 95/-	50 Amps A.C.			65/-
500 TOIGHTE.O. 2211.	300 Volts A.C.	2½in.	MI/FR	25/-





Complete list of meters available including the available metoding new Taylor pocket-size Multimeter Model 127A. 20,000 ohms per volt. 20 megohms, 20 ranges 20,000 ohms po 20 megohms, 20 A.C. and D.C. post 2/6. £10.

2½in. MIFR 25/METER RECTIFIERS 250, A 1 M.A., 5 M.A., F.W. bridge, 8/6, post 6d.
CROSS POINTER METERS. 2 separate 100 microamp movements, 22/6.
MICROAMMETER. 250 F.S.D. 3\(\frac{1}{2}\)in F.R. Sangamo Mod. S37. Scaled
for valve voltmeter. Circuit available free, 55/-, post 1/6.
UNI-PIVOT GALVANOMETER, by Cambridge Instruments, 50-0-50
microamps, dia. 4 in. Knife pointer, mirror scale. Complete with
leather carrying case. Ideal for laboratory use, 210, carriage 3/-.

PORTABLE VOLTMETER. 0-160 volts A.C./D.C. accuracy within 2%, 8in. mirror scale, knife pointer, in polished case. A precision moving iron instrument at a very low price, £4/19/6, post 3/6.

WHEATSTONE BRIDGE 1 to 10,000 ohms, plug type, \$5, carriage 7/6. AVO TEST BRIDGES. 220/240 volt A.C. Measure capacities from 5 pf. to 50 mfd. and resistances from 5 ohms to 50 megohms. Valve voltmeter range 0.1 to 15 volts and condenser leakage test. Full working instructions supplied with instrument. 29/19/6, post 3/-.

SLOW MOTION VERNIER DRIVE. Scaled 0-180°. Ratio 38:1, diam.

3in. 15/6, post 1/6.


FREQUENCY METERS. 45-55 cycles per second 230 volts, 6in. dia., Flush Round. Brand new in maker's box, £10/10/-, post 3/6.



as two ounces and totally enclosed in protective case. polythene

reverse and stop. 7,000 r.p.m., self lubricating and long life sintered bronze bearing; 15/6, post 9d. Ask for free length of polythene flexible drive.

RELAYS P.O. TYPE 3000

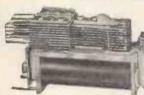

Built to your own specification

Keen Prices

Quick Delivery

Contacts up to 8-Changeover

MINIATURE RELAYS:

Siemens High S	peed Sealed.			S.T.C. and	G.E.C. Se	aled.
$2.2\Omega + 2.2\Omega$	H96A	15/6	2Ω	2 C.O.	4184GA	18/6
$145\Omega + 145\Omega$	H96C	19/6	700Ω	2 C.O.	4184GD	
$500\Omega + 500\Omega$	H96D	22/6	2500Ω	1 makeHI		
$1700\Omega + 1700\Omega$	H96E	25/-	2700Ω	2 C.O.	4184GE	21/6
Siemens High S	peed Open		180Ω	2 m 2 b	M1087	19/6
$100\Omega + 100\Omega$	H85N	15/-	670Ω	4 C.O.	M1092	21/6
$850\Omega + 850\Omega$	H85W	15/-	2500Ω	1 C.O.	M1022	22/6
$1000\Omega + 1000\Omega$	H95A	17/6	5000Ω	2 C.O	M1052	25/-

ERICSSON SEALED. Highly sensitive. 7000Ω 1 C 0 24 v. 25/-. Comprehensive range available from stock.

SWITCHES. 1 hole fixing, 3 amp. 250 volt.

1/6 each, 12/- doz. RACKS—POST OFFICE STANDARD, 6ft. high with U-channel sides drilled for 19in. panels, heavy angle base, 4ft. 10in. in stock.





TELEPHONE SET TYPE "A." Kinging and Speaking both ways on a four-core cable. Carries the voice loudly and clearly over any distance. Two handsets are supplied as illustrated and the set is complete with Pushes, Buzzers, Battery, Plugs and Sockets. We can supply 4-core PVC cable at 10d, per yard or 2-core at 3d, per yard extra. Price 75/- set, post 3/6. TELEPHONE SET "TELE-F." This is the best known portable telephone ever made, it has a built-in generator for ringing the other instrument and requires only twin wire between the sets. The set of two instruments and requires in carrying case, £7/10/-, post 7/6. Twin flat P.V.C. wire 3d, yard. TELEPHONE SET TYPE "K." The most compact telephone set available as the 4½ v. flat battery and buzzer is built-in to the hand instrument. Ringing and speaking both ways on twin wire, instrument is complete with 5ft. flex. Easily hangs on the wall. Set of two instruments, £5/10/-, post 3/6. JACK PLUGS. Cylindrical bakelite screw-on cover, 2 contact 2/6, post 6d.

RESISTORS EX STOCK. IN OUANTITY WIRE WOUND.

RESISTORS EX STOCK, IN QUANTITY WIRE WOUND, HIGH STABILITY CARBON ETC., BEST MAKES AT LOWEST PRICE.



MAGNETIC

COUNTERS Counting to 9999.

2-6 v. D.C., 15 - each, post 1/6, 75-230 v. D.C., 15/- each, post 1/6. HIGH SPEED TYPE No. 100c. 35/-, post 1/6.

VEEDER-ROOT MAGNETIC COUNTER. General purpose type with zero reset. 800 counts per minute up to 999,999. 48 volt D.C. 55/-, post 2/6. SATCHWELL THERMOSTATS adjustable between 70°-190° fahrenheit. Operates 0-440 A.C., 20 anps., 11in. stem. Fitted cover. 25/-, post 2/6. ROOM THERMOSTAT. Adjustable between 45 and 75 deg. Fahr., 250 v. 10 amp. A.C. Ideal for greenhouses, etc., 35/-, post 2/-.

THIS MONTH'S SPECIAL OFFER: 1 H.P. CAPACITOR MOTORS. 230/240 volts, 50 cycles, 1,420 r.p.m. §in. shaft, resilient mounting. Or with iin. shaft on standard foot mounting. Either type \$5.10.0. carriage 10/-.

ROTARY CONVERTERS. Input 12 D.C. Output 230 A.C. 50 cy. 135 watts. In fitted case with variable resistance, 0/300 voltmeter. The ideal job for T.V. and tape recorders where A.C. mains are not available. £10, carr. 15/-. Special connectors, one fitted with 6ft. heavy duty flex and clips for D.C. side, 10/- set, post 1/-. ROTARY CONVERTER, input 12 v. or 24 v. D.C., output 230 v. A.C., 135 watts, £8/10/-, carriage 7/6.
ROTARY CONVERTER. Input 24 v. D.C. Output 220 v. A.C. 250 watts. Pedestal type with D.P. Ironclad switch. BRAND NEW. £17/10/-. Cge. 15/-. BATTERIES. Portable Lead Acid type, 6 volts 125 ampere hours. In metal case 16in. × 8in. × 11in. (Two will make an ideal power supply for our 12 volt Rotary Converters.) Uncharged £6/10/- each, carriage 15/-. 24 volts 85 amperes, £14 each, carriage 15/-.

Rotary Converters.) Uncharged \$6/10/- each, carriage 15/-. 24 volts 85 amperes, £14 each, carriage 15/-. (Westinghouse Type B.C.3) will charge three lead acid cells at 15 amps. Input 200/250 volts, 50 cycles A.C. Charging current is regulated by four-position switch and variable resistance for fine control. Fitted with 0/20 ammeter, rotary on/off switch and rewirable fuses. This first-class instrument at the bargain price of £15/0/0, cgc. 15/-CEARED CAPACITOR MOTORS. 220-240 v. 50 cy., 30 watts, 300 r.p.m. also spindle for 1425 r.p.m. A powerful and useful motor 75/-, post 3/6. TERMINAL BLOCKS. 2-way 4/- doz., or box of 50 for 15/-, 3-way 6/- doz., 50 for 22/6, post 1/6.

T.C.C. CONDENSERS. 0.1 Mfd. 31 kV. 75/- each, 1

T.C.C. CONDENSERS. 0.1 Mfd. 31 kV. 75/- each, 1 Mfd. 10 kV. 45/- each.

SOLENOIDS suitable for remote control, mechanical indicators, etc. 12 v. D.C., 400 M.A., 30Ω, 3½ in. arm, ½ in. movement, 5/- each, post 1/6.

NIFE BATTERIES, Nickel Cadmium 12 volt 18 ampere hours crated and connected alkaline filled Brand New £4 each, carriage 10/-. Also available 2.4 volt 10 ampere hours, 20/- each, post 3/6.

TRANSFORMER. Single Phase 250-115 volts 50 cycles 5 KVA double

TRANSFORMER. Single Phase 200-110 voits 30 cycles 3 KVA double wound, £30, carriage extra.

PUMP Electrically Driven by a 24v. D.C. motor. Works efficiently on 12v. Totally enclosed, self lubricating driven through 4 to 1 reduction gearbox delivering 60 g.p.h./30lb./sq. in. Inlet and outlet unions † BSP 37f6, post 2/6.

OSCILLOSCOPE No. 11 with high-class amplifier, 230 volts £12/10/-, cgc. 15/-

ELAC LOUDSPEAKERS P.M.

5in. Round, 3 ohms, 12/6, post 1/6.

L. WILKINSON (CROYDON) LTD 19 LANSDOWNE RD. CROYDON SURREY

Phone: CRO 0839 Grams: WILCO CROYDON

Get Finest Value from IRONGATE-England's Leading Equipment Wholesalers Bulk Buying means LOWEST PRICES. All Equipment is in TIP-TOP condition



EXPORT ONLY

"88" sets-just released by Ministry of

BATTERY IN POUCH Supply. Produced to exacting specifications by leading manufacturers E. K. Cole & Co. this Transmitter/Receiver weighs only 5½lb. (approx.) and measures $3\frac{1}{2}$ in. \times $5\frac{1}{2}$ in. \times $9\frac{1}{2}$ in. It is a 4 frequency channel set, crystal controlled, 38-40/40-42 Mc/s.,

and operates from a Standard Dry Battery—HT/LT. 94/1.

3 v. (i.e. Ruben Mallory Type I). 14 of the current series 3 v. (i.e. Ruben Mallory Type I). 14 of the current series of B7G valves are employed: 1-3A4, 6-IL4, 4-IT4, 1-IS5.

Only Land each. 2-1A3. Each set is in first class condition.

Special quotations for quantities up to 3000 sets. "22" SETS ALSO—300 available only. New condition £10 each.



UNIQUE OFFER! World Famous TELEPHONES "F" TYPE in Attractive Case

£7-10-0 per pair 9/-

The best portable telephone ever The best portable telephone ever made. Original cost £40! Range up to 5 miles. Ideal for FACTORIES, BUILDING SITES, FARMS, OFFICES, 2 perfect case sets with batteries, 100ft. cable, etc.

D3 STRANDED TELEPHONE CABLE. New Mile Drum 85/-. Carr. 17/6.



OUTPUT (1.3KVA.) Completely Variable 0 to 260 volts, 5 amps. INPUT 230 volts, 50/60~. A SHROUGED FULLY VARIABLE TRANSFORMER FOR BENCH OR PANEL MOUNTING.
SIZE: Approximately 210 inches Cube.
WEIGHT: Approximately 13lb. \$9.0.0
PRICE: RIDICULOUS, ONLY \$9.0.0

Plus 12/6 carr., supplied and boxed new. Also available 10 amps. Transformers £18/5/-and 20 amps. £32/10/-.



VARIABLE TRANSFORMERS


A COMPLETE Ex. Govt. FOR OFFICES, FACTORIES WAREHOUSES & CARS CARR 30'-

TELEPHONE HAND Nº 11

Set by TRUVOX, etc. Comprises : Amplifier, four Loudspeakers. Heavy duty mic., Leads etc. 6 or 12 v. D.C.



HEAVY DUTY 20 AMP. L.T. SUPPLY UNIT

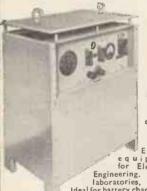

S.T.C.

Normal cost over €100

equipment for Electronic Engineering. research laboratories, schools. Ideal for battery charging etc. Guaranteed for 20 amps.

Output: D.C. Variable up to 20 amps. and 24 v. or trickle charge 125/350/700 ampere hours.

Input: A.C. 100/260 volts 45/65 cycles.

Size: 16 x 24 x 32in. high.

£22-10-0 In attractive Cabinet.

ex Warehouse (Circ, diags, and instru. loaned for 101- deposit.)

750,000 YARDS!! SCREENED WIRE FLEX FOR ONLY 2d. per yd.

For Immediate Delivery—Iar below cost. Specification: Close braided 14/.0048in. Overed 0.24 p.v.c. Tinned Copper. Screened. Assorted colours. Applications: Microphone leads, pick-up heads, etc. ON MAKERS REELS. 220 yd. REELS (min. quantity) 36/8. P. & P. & F. EN REELS £17. Carr. Faid. 6/r.

CONSTANT VOLTAGE **TRANSFORMERS**

FERRANT 7-KVA MOVING COIL

Stabilized output voltage in the range 290-250 v.

Flug-board tapplings. The selected output voltage is
constant with + 1% at all loads 0 to 30/371 amps.

view to the result of the result of the range 29/4 to - 12%

Frequency compensated 45-55 and 54-66c/s.

Excellent output wave-form.

Can be used as a variable transformer.

**Unused, Complete with sparse and instruction book at a fraction of the normal cost.

*** A.C. MAINS STABILIZER. ONLY



AUTO TRANSFORMERS AUTO TRANSFORMERS
3KVA Air Cooled (100% under-rated),
6UARANTEED 230/250 tapped, 12 amps.
6 KVA 105/120 tapped 25.5 amps
Made by well-known manufacturer and bo
in strong metal case. Weight: 2 cwt.
Brand new, is original maker's case.

PRICE £15.0.0 Carr. 25/-

AERIAL IMPROVED TYPE 50 MK.II 36ft HIGH

Kits comprise—six 21in. dia. Tubular Steel Sections of 6ft. bular Bteel Sections of 6ft.

ngth, top-section and base
fickets, Guy and Fittings.

YOU can purchase this
for a fraction of ite cost.

Flease add £1 for (returnable) wooden carrying case.

The MAST is particularly suitable to take serials for Tx, Rx,

F.M. and TV (especially

COMMERCIAL) and has
many other uses. Extra

6ft. sections can be supplied at 17/6 per section.

£8.10.0 only TOT £8.10.0 only Carr. 15/6.

U.S.A. Type 45ft. TELECOM AERIAL MAST. (7 sections, 6ft. 8in. x 2½in., guys, etc.). This entirely complete set in carrying case 12½ Gns. Carr. 17/6. Or 2 sets for £25. Carr. extra. British Manufacture only.

ARMY TYPE 32FT. MASTS similar to above but 10 lin. screw-sections, suitable for permanent lightweight installation. Kit in canvas bag, £5/15/-. Carr. 7/6.

Limited Quantity

Limited Quantity
36ft. TELESCOPE MASTS
Finest quality brass. Non-rusting. Base diameter 2½in. Complete with hand-winding winch for easy, rapid extension; and cablewire bracing stays. One of the best masts ever produced.
Winds down to 9ft.

ronga (M.O.) COMPANY

Dept.(ww13), 2, IRONGATE WHARF ROAD, PRAED STREET, LONDON W.2 PADDINGTON 223112/3

FAMOUS TAPE RECORDER



Famous manufacturer. Huge purchase allows us to offer at this amazing price. Beautifully styled, rexine covered cabinets. Colours: Red, Grey, Black. Storage space for 4 tapes, mike and lead. Incorporating the latest B.S.R. Deck. LOOK AT THESE EXPENSIVE FEATURES. Controls: Record/Playback switch and rewind with interlocking device to prevent accidental crasure. Tone switch and rewind with interlocking device to prevent accidental crasure. Tone and volume controls. Superimpose and electronic eye. Small overall size 14½ × 1½ n. Lightweight, only 21lb. 5½ n. standard tape. Terms: Carr. & Ins. 12/6. Microphone 27/6 extra. Tapes 19/9.

PLESSEY T.V. CHASSIS FOR SPARES

56 resistances. 54 condensers. 13 valve po resistances. 54 condensers. 13 valve holders. 4 transformers. Chokes 250 ma. Metal rectifiers 300 volts @ 250 ma. Fuse panel. Focus magnets. Plugs. Sockets. Carr. 7/6.

REPLACEMENT, REBUILT T.V. TUBES 12 months guarantee

Carr. & Ins. 15/6.

21in. tube £8/10/-, 17in. tube £7/10/-. £2 allowed on old tube. 12, 14, 15in., tubes £5/10/-. £1 allowed on old tube. Terms Terms available over 20 weeks.

CONTEMPORARY EXTENSION 19/9 SPEAKERS

Ideal for extra stereophonic speaker, covered in smart two-tone leatherette.

Beautifully made. Including 8in.

speaker. P. & P. 3/9.

EXTENSION SPEAKERS



8in. P.M. Speakers fitted into polished cabinets. Standard matching to any receiver. (Complete.) Switch and flex included. P. & P. 3/9.

BARGAIN SPEAKER 8in. P.M. Repaired cone defect not affecting reproduction quality.

8in. P.M. SPEAKER As above but with output transformer.

8in. P.M. SPEAKER Perfect quality. Fitted output transformer.

ELLIPTICAL SPEAKERS 8 × 3in. and 7 × 4in. Brand new Also 9 × 4in. @ 19/9. P. & P. on each 2/9.

TELEPHONE SETS

X.W.D. Wireless remote control unit. E.M.K.II (ZAI1954). Including morse tapper, switched, jack plugs, etc. Less phone. Ins. and carr. 3/6.



31 gns. our price

gns.

Beautifully styled rexine covered cabinet in Red/Beige with carrying handle. Size: 14½ x 13 x 9½ in. Storage comp. in lid for tapes and mike. Speed 3½ in. per second. Compact set using latest 5 valve amplifier with 4-stage amplification and separate valve for Bias osc. 2 controls. Contains 7 x 4in. elliptical speaker and incorporating B.S.R. Tape deck. 5½ in. standard tape. 3 months' guarantee. Ins. & Carr. 12/6. Deposit £8 plus Ins. Carr. and 20 payments of 17/-.



Beautifully made Tape Recording Cabinet. Size: 13 × 10½ × 7in. Covered in two-tone coloured rexine cloth. Stylish design. Carrying handle with detachable lid. Easily adapted to Record Player Cabinet. Exceptional value at this very low price. P. & P. 4/6.

17" T.V.'s 17½ gns.

Modern CHASSIS, modified

Complete 17in. TUBE. VALVES — SPEAKER — KNOBS. Tuned ITV/BBC. Ready to use, fully guaranteed, TUBE 12 months, CHASSIS and VALVES 3 months. Cabinet to fit \$1/11/6 if ordered with set. Salvage. Set—tube—cabinet despatched separately. Carr. & Ins. on set £1/5/-; on Cabinet 8/6.

SOLO SOLDERING



110 v., 6 v. or 12 v. (special adaptor for 200/250 v., 10/- extra). Automatic solder feed including 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.

RECORD PLAYER CABINET R.P.9 19/6

Exceptional offer. A lightweight portable Exceptional oner. A lightweight portable player Cabinet in two-tone Rust and Cream. Famous manufacturer. Size: 14½ × 11½ × 6in. Complete with moulded deck board of attractive design. Takes B.S.R. TU9 single player; 2 control Amplifier; 5in. round Speaker. Post, Packing & Ins., 4/8.

"STUDIO TWIN" NOW 29 gns.

Quality Twin Speaker Tape Recorder at this amazing reduced price. 7in. 1,200ft. Standard reels. Latest Studio Standard reels. Latest Studio 3-speed Deck, 17, 32, 72 I.P.S. Includes Twin Tracks, Reverse counter, Pause control and magic eye recording indicator.

Volume and tone control, superimpose switch. Two matched speakers. 3 watts output. Attractive design cabinet in beige. Size 19in. × 13in. × 8in. Ins. & Carr. 12/6.

EXTRAS: Microphone 27/6. Tape 25/-

B.S.R. TAPE "MONARDECK"

Single speed. 3\(\frac{3}{2}\)in. per sec. Uses 5\(\frac{3}{2}\)in. spools. Complete with Record-Playback and erase heads. Simple control for R/P.B. and last rewind with safety switch for record. Size: 13 × 6\(\frac{3}{2}\) × 2\(\frac{3}{2}\)in. Colours: two-tone grey. P. & P. 4/6. Deposit 60/plus P. & P. and 20 weeks at 8/-...

TAPE RECORDER AMPLIFIER

Compact, well designed 5 valve amplifier. Output 3.5 watts. Valve line up—ECC83, double triode first audio amplifiers, ECL82 triode pentode further audio amplifier and output valve, 6BW6 bias and erase oscillator, EM84 record level indicator. EZ80 H.T. rectifier. Input for mike, radio and gram. Controls: record playback volume and on/off playback tone. Dia. 8½ x 3 x 4½in. ins. and carr. 4/6. Terms. EXTRAS: Knobs 2/6 per set. Beautiful Perspex dial plate, Complete with sockets for mike, radio and superimposed switch 3/6.

AMPLIFIERS. All portable, 12 months guarantee

MK. D5.

Simple circuit employing ECL80 trlode pentode output valve giving 3 watts output. A.C. only. Mains isolated. Single control for volume and on/off switch with knob. P. & P. 3/6.

Latest design incorporating negative feedback, giving 4 watts undistorted output. Valves: ECL82, triode pentode and contact cooled metal rectifier. Tone and volume control panel on flying leads with compact amplifier chassis suitable to mount under modern autochangers to give easy mounting in small cabinet. A.C. only. Mains isolated. Output for 2-3 ohms.

MK. D3A. As above de luxe model, with separate tone controls for treble

and bass

PORTABLE AMPLIFIER (Salvage) 69/7 3 valves. 4-5 watts output. Size $7 \times 5 \times 4$ in. An ideal amplifier for stereo record players, Tape Recorders, Microphone, Baby Alarm, etc. Volume and tone controls. 200-250 v. A.C./D.C. P. & P. 4/6.

NEW LOOK AMPLIFIER

Aldeal stereo attachment. Brown/Ivory cabinet, carrying handle. Contains high flux 8in. speaker. A.C. mains. 3 valves—10F3, 10P14, U404. Max. output 4.5 watts. 14 × 11 × 6½in. Completely converted. Ideal stereo, Mike, Guitar, Records. 2 units give world of amusement and special stereo effects. 12 months' guarantee. P. & P. 5/6. Deposit 30/-plus P. & P., 10 weeks at 8/-.

RECORD PLAYER CABINET R.P.2 FOR ONLY 59'6

Made by famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size: 16 × 14½ × 8½ in. deep. Carr. & Ins. 4/6 Will take B.S.R. Monarch Autochanger, 26/19/6; 7in. × 4in. Elliptical Speaker 15/9; Our Mk. D2A Portable Amplifier 79/6.



(LONDON) 621/3 Romford Rd., Manor LTD. Park, E.12 1LF 6001/3

Send for a FREE CATALOGUE

SURPLUS STOCKS BY FAMOUS MANUFACTURERS ARE OUR SPECIALITY

C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having Heater/Cathode shore circuit and for C.R. Tubes with falling emission. Full instructions supplied. Type A. Low Leakage windings. Optional Boost 25%, and 50%. Tapped mains primaries:

10 H 120 m.A., 12/6, 10H 150 m.A., 14/r
MAINS TRANSFORMERS 200/250 v. A.C.
STANDARD 250-0-250, 80 m.A. 6.3 v. 3.5 s.
tapped 4 v. 4 s. Rectifier 6.3 v. 1 s., tapped 5 v.
or 4 v. 2 s. Ditto 350-0-350
MINIATURE 250 v. 20 m.A., 6.3 v. 2 s.
MINIATURE 250 v. 20 m.A., 6.3 v. 2 s.
SMALL, 200-0-200, 60 m.A. 6.3 v. 2 s.
STANDARD, 250-0-250, 65 m.A., 6.3 v. 3.5 s.
HEATER TRANS, 6.3 v. 14 s., 7/6; 3 mup. uts.
6, 8, 9, 10, 12, 16, 18 24 and 40 v. at 2 A.

SECONDARD TRANSFORMERS SECONDARD SECO

CRYSTAL MIKE INSERT by Acos 6/6

ACOS CRYSTAL STICK MIKE 39-1. Bargain 35/-.

MIKE TRANSF. 50:1, 3/9 ea.; 100:1 Potted 10/6. LOUDSPEAKERS PM. 3 DHM. 5in. Rola, 17/6. 6in. x 4ln. Rola, 18;- 7in. x 4ln. Rola, 18;- 8in. Piesey, 19/6. 6jin. Rola, 27/6. 6jin. Rola, 27/6. 6jin. Rola, 21/-. 10in. R.A. 30/-14/-FI TWEETERS, 4in. 25/-. 12in. Piesey, 30/-12in. Baker 15 wt. 3 ohm. and 16 ohm. models, 90/-12in. Baker coam suspension 15 w. 15 ohm. £8. 13in. 16 ohm Piesey 10 wt., 45/-. E.M.I. 14 × 8in. 45/-.

I.F. TRANSFORMERS 7/6 pair
465 ko/s, slug tuning miniature can 2½ × 1×1in. High
Q and good bandwith. By Pye Radio, Data speet supplied.


Wearite M800 I.F. Miniature 465 ko/s., 12/6 pair. Weymouth I.F. Standard size 465 ko/s., 12/6 pair.

Weymouth I.F. Standard size 465 ko/s., 1,2/6 pair.
Weymouth I.F. Standard size 465 ko/s., 1,2/6 pair.
CRYSTAL DIODE G.E.C., 2/-. GEX 34, 4/-. 40 Circuits 3/-.
H.R. HEADPEONES. 4,000 ohms. brand new, 15/- pair.
SWITCH CLEANER FIRID, squirt spout. 4/3 tin.
TWIN GANG CONDENSERS. 565 pf. Miniature, 1in.
TWIN GANG CONDENSERS. 565 pf. Miniature, 1in.
Sylvater of the standard standard single by the standard stan

THE HI-GAIN BAND 3 PRE-AMP

Cascode circuit using Varve ECC84. 17db gain. Kit 29/6 less power; or 49/6 with power pack. Plans only 6d.
Also Band I version same prices.
(PCC84 Valve if preferred)

RADIOGRAM CHASSIS 1960

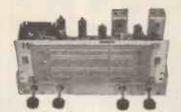

THREE WAVEBANDS

S. W. 16 m. —50 m.

M. W. 200 m. —500 m.

LATEST MULLARD

M. W. 800 m. —2,00 m.

LEMS1, Eksp. hatcsi,

Lemonth Guarantee. A.C. 200/250 v., 4-way switch.

Short-Medlum-Long-Gram.

A.C.C. and Negative

Feedback, 4.2 watts. Chasels 13½m. x 5½m. x 2½m.

Chase Dial Siz: 10 x 4½m. horizontal or vertical. Two Pilot

Lamps. Four Knobs. Wallut of tvory. Aligned and

calibrated. Chassis isolated from mains.

BRAND NEW £9.10.0 Carr. 4/6

MATCHED SPEAKERS 8in. 17/6; 10in. 25/-; 12in. 30/-.

MONARCH RECORD PLAYER



BUILD IT YOURSELF using BSR MONACH AUTOCHANGER READY BUILT 3W. AMPLIFIER HANDSOME PORTABLE CASE HIGH FLUX 6" LOUDSPEAKER

FULL INSTRUCTIONS supplied

Total Price £12.10.0

RECORD PLAYER BARGAINS



Manarch

4 Speed Autochangers, BSR, U.A.8 £6 15
Stereo U.A.8 £7 10
Collaro Conquest £7 19
Garrard Model 210 £10 10
4 speed Single Players, EMI £6 19
Garrard TA Mk. II. £8 8
Garrard 4 HF Transcription £17 19
Garrard Stereo Heads £2 extra. 6

AUTOCHANGER ACCESSORIES

Suitable player cabinets (uncut boards)
Amplifier player cabinets with cut boards
2-valve amplifier and 6jin. speaker for above ...
3-valve amplifier and 6jin. speaker for above ...
Wired and tested ready for usc.

CYLDON TURRET TELETUNER

14 33/38 megs, complete with frame-grid valves. With colls for channels 1 to 5 & 8 to 11. Brand new. price 45/-operating data & circuit supplied.

VOLUME CONTROLS

Midget size: Long spindle. Guaranteed Long spindle. Guarantell 1 year. All values.

5 K. ohms up to 2 Meg. No switch.

D.P. Sw. 4/6 3/-Linear or Log Tracks.

80 Ohm Coaxial

Semi an spaced, Jm. dia. Ideal Band III
Losses cut 50%
Post 1d. per yard extra.
FRINGE QUALITY AIRSPACED ... 1/- yd.
LEAD SOCKETS.. 2/OUTLET BOXES .. 4/8

Linear or Log Tracks. ARSPACED . 11- yd.
COAXIAL PLUGS . 1/- LEAD SOCKETS . 2/PANEL SOCKETS . 1/- OUTLET BOXES . 4/6
BALANCED TWIN FEEDER per yd. 64, 800 or 300.
TWIN SCREENED BALANCED FEEDER 1/6 yd., 80 ob m.

ALUMINIUM CHASSIS. 18 s.w.g. Plain, undrilled, with 1 sides, riveted corners and lattice fixing holes, with 21m. sides 7 x lin. 4/6; 9 x 7m. 5/9; 11 x 7m., 6/9; 13 x 9m., 8/6; 14 x 11m. 10/6; 15 x 14 in., 12/6 and 18 x 16 x 3m., 18/6; 14 x 11m.

BLACK CRACKLE PAINT. Air drying, 3/- tin. P.V.C. CONN. WIRE, coloured, single or stranded 2d. yd.
NEOU MAINS TESTEL SCREWDRIVERS, 5/CORED SOLDER RADIOGRADE, 4d. yd. 4b. 2/6.
PAXOLIN 1/16in. × 8in. × 10in. 1/6. ION TRAPS 5/stranded 2d. vd.

AMERICAN MAGNETIC RECORDING TAPE FERRODYNAMICS "BRAND FIVE"

5in.	600 1	eet		16/-	MYLAR DUPONT		
δin.	900	lect		. 18/6	Super High Fidelity		
δţin	. 120	0 feet		. 23/6	Double Play		
7in.	1200	fcet		25/-	5in. 1200 feet 37/6		
7in.	1800	feet		35/-	7in. 2400 feet 60/-		
	lilustrated leaflet S.A.E.						

RECTIFIERS, RM1, 5/-; RM2, 6/-; RM3, 8/-; RM4, 16/-; RM5, 20/-; FCS1, 27/6; 14A86, 17/6; 14A10, 21/-, MIMATURE CONTACT COOLED RECTIFIERS. 250 v. 50 mA. 7/6; 60 mA. 8/6; 58 mA. 9/6; 200 mA. 21/-; 300 mA. 27/6; Full Wave 250 v. 120 mA., 15/-, COILS, Wearite "P" tyre 3/- each. Osmor Midget "Q" type add, dust core from 4/- each. All ranges. TELETRON, L. and M. T.R.F. with reaction, 3/6. FERRITE ROD AERIALS, M.W., 8/9; M. & L., 12/6. J.R.F. COILS, A/HF, 7/- pair. H.F. CHOKES, 2/6.

JASON F.M. TUNER COIL SET, £91-. H.F. coil aerial coil. Oscillator coil two J.F. transformers, 10.7 Mc/s., Detector transformer and heater chokes. Grequit and component book using four 6AM6 2/6. Complete kit FMT1 with Jason Calibrated disl and 4 vaives. £8/5/-. With new Jason Calibrate. FMT2, £2 extra.

CONDENSERS. New Stock. .001 mfd. 7kV. T.C.C. 5/6-20 kV.,9/6. .1 mfd. 7kV. 9/6. 100pf to 500 pf. Micas, 6d Tubular 500 v. .0001 to .05 mfd., 9d.; 01, 1/-; 0.25, 1/6; 0.5. 1/9: 0.1/350 v., 9d.; 0.1/1.000 v., 1/9: 0.1 mfd. 2,000 v., 3/6; 0.001 mfd. 2,000 v., 1/6 CERAMIC CONDENSERS. 109, 5 pf. to 500 pf., 1/-: SLIVER MICA COMDENSERS. 109, 5 pf. to 500 pf., 1/-:

Shives mich conductions. So that mich conduction of the property of the proper

NEW ELECTROLYTICS. FAMOUS MAKES

TOBOLAR		TOBULAR		OMR LIFES		,	
	1/350 v.	2/-	50/350 v.	5/6	8/500 v.		3/-
	2/350 v.	2/3	100/25 v.	3/-	16/500 v.		4/-
	4/450 v.	2/3	250/25 v.	3/-	32/350 ▼.		4/-
	8/450 v.	2/3	500/12 v.	3/-	100/270 v	7.	5/6
	8/500 ▼.	2/9	8+8/450 v.	3/6	2,500/3 v		4/-
	16/450 v.	3/-	8+8/500 V.	5/-	5,000/6 v		5/-
	16/500 v.	4/-	8+16/450 v.	3/9	8+16/50	0 v.	7/-
	32/450 v.	3/9	8+16/500 v.	5/6	32 + 32/4	50 v.	8/-
	25/25 v.	1/9	16+16/450 v	. 4/3	50 + 50/3	50 v.	7/-
	50/25 V.	21-	16+16/500	6/-	64 + 120/3		
	50/50 v.	2/-	32+32/350 1	.4/6	100 + 200	/275v.]	2/6
			IDGE SELENI				
			9; 2 a., 11/3				
			SFORMERS.				
			or 12 v., 1 a.,				
			A WID WET				

NEW a	and box	red \	/A	LVE	S 90) day gua	rantee
1R5	7/6	6L6G 6N7M	10/6	EA50 EABC8			9/6
1T4		6Q7G			61-	HABC80	12/6
2X2 .	. 3/6	68A7M		EBC33	.: 8/6	HVR2A	
384 3V4 .	7/6	68J7M 68N7		EBC41 EBF80	10/-		. 9/-
5U4 .	7/6	6V6G		ECC84	9/6	PCC84 .	
5¥3 .	. 7/6	6X4	7/6				. 9/6
5Z4 . 6AM6		6X5 12A6	6/6		10/6		11/6
6BE6		12AT7		ECL82	10/6	PL82 .	10/6
6 BH 6	9/6	12AU7		EF39	5/6		. 7/6
6BW6 6D6		12AX7 12BA6		EF41 EF50	9/6		9/6
6FG6		12BE6		EF80			3/6
6H6G	r 3/6	12K7.	6/6	EF86			. 9/0
6J5 .		12Q7		EF92 EL32		WW.TD.A.D.	9/6
6J6 .		351.6 35Z4.		EL41			· 9/6
6K6G'		80	9/6	EL84	8/6	UY41 .	. 8/-
6K7G				EZ40			- 8/-
6K8G	7/6	954	1/6	EZSU	7/0	1092	. 116
6K8G	7/6	954	1/6	EZ80		U52	711 12 Z


A MERRY CHRISTMAS TO ALL READERS OF "WIRELESS WORLD"

POSTAL SERVICE 1/-, OVER £2 FREE. C.O.D. 1/6. (EXPORT C.W.O. POST EXTRA.) Wed. I p.m.

48-HOUR MAIL ORDER 337 WHITEHORSE RD. WEST CROYDON

THO 1665 Buses 133 or 68

BEULAH **ELECTRONICS**

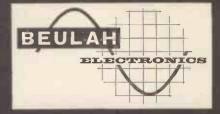

offer a highly competitive Range of

EQUIPMENT!



power supply.

£44

£34 15s.

MODEL 0-12U/F Laboratory 5"

OSCILLOSCOPE

complete with 48-page Handbook

Here's an instrument to

Some of the other top-grade BEULAH ELECTRONICS instruments available.
FACTORY ASSEMBLED, WIRED AND

TESTED.
Capacitance Decade Box

DC-IU/F Model DC-IU (in Kit Form)	£9	0 18	6
Resistance/capacitance Bridge C-3U/F MODEL C-3U (in Kit Form) Audio Valve Millivoltmeter	£13		6
AV-3U/F MODEL AV-3U (in Kit Form)	£19 £13	18	0
MODEL AW-IU (in Kit Form) Electronic Switch S-3U/F	£13	18	0 6
MODEL S-3U (in Kit Form)	€9	18	6

Deferred terms available on most items. Please ask for details.

See the range at our London Showroom, 138 Lewisham Way, New Cross, S.E.14.

See an exciting NEW TY DEVELOPMENT on our STAND No. 8

Industrial Photographic & TV Exhibition Royal Albert Hall, 21st-25th November

MODEL V-7A/F

VALVE VOLTMETER

Internationally famous.



Performance and professional appearance equal to many higher priced instruments.

equal to many higher priced instruments. Gold-plated printed-circuit. High Input impedance (11 megohms). The V-7A measures A.C. volts (0-1.5, 5, 15, 50, 150, 500, 1,500) R.M.S. and A.C. volts (0-4, 14, 40, 140, 400, 1,400 and 4,000) pk.-to-pk. D.C. volts (0-1.5, 5, 15, 50, 150, 500, 1,500). Ohms (with 10 ohms centre) XI, X10, X100, X1,000, X10K, X100K, and X1 megohm.

complete with 32-page Handbook.

MODEL V-7A (in kit form)

Beulah Electronics Research has produced this revolutionary instrument for you ...



blus carriage.

MODEL 0-12U (in Kit Form)

Save You

Time & Money!

The most efficient lowest priced time base component shorting turn tester.

Line Output Transformers, Deflector Coils, Biocking Oscillator Transformers.

Shorting Turns Open Circuit. £7, 10. 0. (Nett Trade)

Subject to quantity discount to

a new, compact, dynamic

TRANSISTOR TESTER POWER SUPPLY

- Makes possible dynamic transistor testing in situ.
- Tests CURRENT GAIN (AC) ALPHA GAIN.
- Tests CURRENT GAIN (under D.C. conditions) BETA GAIN.
- Measures leakage Currents be-tween Collector/Base and Collector/Emitter, at any between 0-25 v. voltage



Tests transistors in circuit. Has its own seir-contained power supply providing smoothed D.C. 0-25 v. Size 5½ x 3 x 2½in. Price £10. Order or send for full details TODAY.

PLEASE SEND CASH WITH ORDER NOW OR ASK FOR ILLUSTRATED LEAFLETS TODAY stating instruments in which you are interested.

SOLE DISTRIBUTORS for



DIRECT TV REPLACEMENTS LTD.

(The Largest Stockists of specialised TV Replacements in Great Britain)

Note new business hours; Monday to Friday 9 a.m. to 12.30 1.30 p.m. to 6 p.m. Closed Saturday.

TIDeway 6666 Dept. WW/II/60 138 Lewisham Way, New Cross, London, S.E.14 Day and Night Service: TIDeway 6663

PRECISION WIDE RANGE SIGNAL GENERATOR

MODEL SWO-300 150 Kc/s-300 Mc/s

The Model SWO-300 is an outstanding instrument specially designed to cover the wide frequency range from 150 kc/s-300 Mc/s, which covers all the requirements of equipment in general

SPECIFICATION:-

- FREQUENCY RANGE: 150 kc/s-150 Mc/s on fundamentals (6 bands). 150 Mc/s-300 Mc/s on harmonics.

 CALIBRATION ACCURACY: within ±1 per cent.

 MODULATION: Internal and external.


- ATTENUATION: To -40 db.
- OUTPUT: Facilities for high and low
- POWER SUPPLY: Internal 230 v. A.C.

ONLY £14.19.6 P. & P. 5/6

FULLY GUARANTEED



Size: 7" x 10" x 5

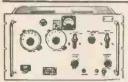

V.H.F. COMMUNICATION RECEIVER 1392 **15 VALVE SUPERHET**

Frequency Range 95-150 Mc/s. (2 to 3 metres)

Gives reception of Police, Aircraft and Amateur transmissions Gives reception of Police, Aircraft and Amateur transmissions. Valve line up: 1st and 2nd R.F. Amp. VR.136 (EF.54), 1st Local Oscillator; VR.65 (SP.61), 2 Oscillator Multipliers; VR.136 (EF.54); 3 1.F. Amp.; VR.53 (EF.39); A.G.C. 6Q7; Output 615; Muting VR.92 (EA.50); Noise Limiter VR.92 (EA.50); B.F.O. 617; Mixer VR.136 (EF.54); De Mod. 6Q7. Slow motion tuning, normally crystal controlled, or tunable over 95-150 Mc/s. Power supply required: 240-250 volts at 80 mA., 6.3 volts at 4 amps. Size 19in. x 10in. x 10in. Standard Rack Mounting. Rack Mounting.

ONLY £6.5.0

CARRIAGE 15/-



R.F. UNITS

Undoubtedly the useful Govt. surplus units ever released. The R.F. units will extend the frequency range of your receiver to enable you to receive, amateur, and VHF stations.

22/6

R.F.24 R.F.25 R.F.27

20-30 Mc/s. Switched tuning 40-50 Mc/s. Switched tuning 65-85 Mc/s.

8/6 29/6 Variable tuning

Circuits supplied. P. & P. 3/6 on each.

NEW! TRANSISTOR RADIOS With



Miniature Speaker Gives reception over the entire broadcast band. Each kit is supplied with all latest miniature parts including two transistors ferrite rod speaker coloured plastic case * step by step illustrated instructions. 4 x 3 x \$\frac{1}{2}\$ in. structions ONLY 27/6 P. & P. 1/6. Battery 1/- ex.

CLIPER MINIATURE EARPHONE FOR TRANSISTOR CIRCUITS



Here is a really sensitive dynamic earphone of exceptionally fine quality. This lightweight miniature earpiece is convenient and comfortable to wear. The practically invisible core is connected to the earphone. Provides clear reproduction of music as well as speech. Fully Guaranteed and complete with transparent ear insert, 3 feet cord, subminiature plug and socket. Model CR.5 Crystal Earpiece, high imp., 12/6. Post I/-.
Model MR.4 Magnetic Earpiece, low imp. 10/6. Post I/-.

imp. 10/6. Post 1/-

COMMUNICATION AR-88D

Undoubtedly the finest communication receiver ever produced for service and laboratory use. Now Relda's exclusive purchase enables you to obtain this Rolls-Royce of communication receivers at the lowest price ever offered

SPECIFICATION:

Range: 540 kc/s to 32 Mc/s in 6 bands. Power Supply: 110/260 v. A.C. Power Output: 2.5 W into 2.5 or 600 ohm line or H.l. Headphones. Sensitivity: From 15 to 2.5 uv per 500 mW.


mW. Image Ratio: From 1,000,000 at 60 kc/s to 200 at 28 Mc/s. Circult: Two R.F. stages (65G7); Oscillator (6J5); Frequency Changer (65A7); Three I.F. stages (65J7); A.V.C./Detector (6H6): Noise Limiter (6H6): Audio Amplifier (6SJ7); Power Output (6K6); B.F.O. (6J5); Voltage Regulator (VR-150); Reccifier (5Y3); I.F. – 455 kc/s. Size: 19½ x 11 x 19½in.

PRICE **FULLY GUARANTEED** ONLY

£39.10.0

Carriage 50/-.

Model AR-88 L.F. 73-550 kc/s and 1.48-30.5 Mc/s. ONLY £37/10/-. Carriage

 



MODEL 74

This basic scope repre-sents one of the finest buys we have ever made! Contains Brilliance, Focus, Gain and 2-speed time base controls. Separate X plate terminals. Signal generator modulated at 2 freqs. over 150-255 Mc/s. Complete with 12 valves, rnal A.C. power pack and technical description.

VCR 139A tube, internal A.C. power complete circuit and technical details.

ONLY 97'6 Carr. 12/6



VARIABLE

■ Input Voltage 230 v. continuously variable output from 0-260 v. ■ GOOD REGULATION. Output voltage is substantially independent of load. ■ SMOOTH CONTROL. Can be set closely to any output voltage within its range. ■ HIGH EFFICIENCY. Very low losses under all load conditions. ■ LONG LIFE. The same as that of any standard fixed-ratio power transformer when operated at rated loads. ■ SMALL SIZE. Smaller than any other type of control of equal power rating. ■ LINEAR OUTPUT VOLTAGE. Continuously adjustable from zero to 30% above line voltage by a 320-degree rotation of the knob. The dial is calibrated to read directly in output voltage at rated line voltge. ● DIRECT-READING DIALS. All models are supplied with reversible direct-reading dials. Large white figures, easy to read at a distance. ■ MODERATE TEMPERATURE RISE. Less than 50 degrees C. for continuous use. ■ ADVANCED MECHANICAL DESIGN. Rugged construction—no delicate parts—protected with a strong, iron cover.

ALL FULLY GUARANTEED. DELIVERY EX-STOCK.

MODEL B.10

Current rating 10 amps.

£18.5.0

MODEL B.20

Current rating 20 amps.

£32.10.0

Kadio

Callers: 87 TOTTENHAM COURT ROAD, LONDON, W.1

Mail Orders: (DEPT. W.) 32a COPTIC ST., LONDON, W.C.I. MUS. 9606

Shop at RELDA for EVERYTHING IN ELECTRONICS

BARGAIN OF for the Constructor!

Manufacturers' brand new, current production offer. Latest 5-valve circuit based on Muliard's famous design. Magic eye level indicator, Volume and tone controls. T.G.C. printed circuit already wired. Only power pack and controls to assemble and wire. Valves EP66, EOC38, EL84, EM84 & EZ30. A sensitive quality recorder at Special Unit Prices.

Wired printed circuit, power pack components, controls and knobs, etc. P. & P. 216.

Bargain reduction for complete kit. Carr. 5/Attractive two-tone Cablact and 9m. x 5in. speaker to house above at special discount price. P. & P. 4/1 did details. Post free Collaro Studio Tape Deck can be supplied with modified circuit as alternative for approx, (extra) £5 15 0 £2 5 0 £8 19 6 £16 10 0

£5 10 0

RECORD PLAYER BARGAINS Latest 4-speed models

NEW RELEASE by E.M.I.—4 speed Single Player Unit fitted with latest stereo and monaural xtal cartridge and dual sapphire styli. Auto stop and start. A fidelity unit and bargain buy at only £6/19/6, carr. & ins. 3/6.

SINGLE PLAYERS, B.S.R. (TU9) 90/-; COLLARO JUNIOR studio P.U. £4/10/-AUTOCHANGERS, B.S.R. (UA8), £6/19/6; UAS STEREO £7/19/6. B.S.R. (UA14) latest model, £7/19/6. COLLARO CONTINENTAL £3/10/6. NEW VALVES GHAPAVIED

BARGAINS PLAYER UNITS

SINGLE PLAYERS
Model 48F £61,7/6. Carr. 3/6.
Model TA Mk. 2, £7/19/6. Carr. 3/6.
Model 4HF, £18. Carr. 3/6.
AUTOCHANGERS. Model BC 210. With-plug-in GCS Head 10 and Carr. 4/6.
Transcription Auto Changer Model 'A' just realessed £18/19/6. Carr. 5/-.

AUTO CHANGER RECORD PLAYER KIT

A.C. Supply
Attractive 2-tone
cabinet—famous
B.S.R. Monarch 4speed, full mixer,
10-record gram
unit. Ful-fl 10-record gram unit. Ful-fl xtai pick-up with dual styli for 8td. L.P. recordings. 2-valve amplifier with quality neg. feedback circuit, volume and tone controls. Fully isolated from me

trois. Fully isolated from mains by double-wound transformer, NOT the line chassis type as often offered in cheap commercial models.

A recommended buy while stocks last! Ready wired 2-valve Amplifier; complete with 6in. high flux speaker.

£3/19/8, P. & P. 2/6
Two-tone Cabinet 18in. x 13in. x 8in.

Two-tone Cabinet 18in. x 18in. x 8in. 23/13/- P. R P. 3/6
B.S.R. Monarch U.A.S (160 v. model). 25/13/6, P. R P. 4/6
Complete 3 unit kit at special Autumn Bargain price. 212/12/6, Carr. 7/6

ple assembly, a screwdr TRANSISTORS BVA—1st Grade New Reduced Prices

MAZDA	MULLARD	G.E.C.
XA101 14/6	OC70 9/6	GET114 9/6
XA102 16/6	OC71 12/6	GET1512/
XA103 15/-	OCT72 15/-	Newmarket
XA104 18/-	OC44 23/8	"Goldtop"
XB102 10/-	OC45 21/-	V15/10P
XC101 10/6		15/

anium Diodes OA70 2/9; OA81 3/6; GEX 34 4/-

DUKED	- u	OTTAKE THE
JT4 6/-	EABC808/6	EZ81 7/6
1R5, 1857/6	ECC84 9/6	MU14 9/-
384,3V4 7/6	ECF80 9/6	PCC84 9/6
6Z4 9/-	ECL82 10/6	PCF80 9/6
6K7 5/-	ECL80 10/6	PCL83 12/6
6K8 7/6	EF80 8/-	PL81 12/6
607 7/8	EF86 12/6	PL82 9/6
6V6 8/6	EF91 5/-	PL83 10/6
DAF96 9/-	EL41 9/6	PY80 7/6
DF96 9/-	EL84 8/6	PY81 9/6
DK96 9/-	EY51 9/6	PY82 7/6
DL96 9/-	EY86 10/-	U25 12/6

SPECIAL PRICE PER SET 1R5, 1T4, 185 or 384 or 3V4, 25/-DK96, DF96, DAF96, DL96, 35/-6K8, 6K7, 6Q7, 6V6, 5Z4 or 6K5, 32/8.

JASON FM TUNER UNITS

(87-105 Mcs)

Designer-approved kits of parts for these quality and highly popular tuners available as follows:—

STANDARD MODEL (FMT)—as previously extensively advertised, COM-PLETE KIT, 5 gns., p. & p. 2/6. Set of 4 spec. valves, 20/-.

spot. varves, 2U'-.
LATEST MODEL (FMT2)—attractively presented shelf mounting unit in enclosed Metal Cabinet with Built-in Power Supply. COMPLETE KIT, 27, p. & p. 3/6. Set of 5 spec. valves, 37/6.

MODEL JTV2. 8elf-powered Switch Tuned B1-B2-B3 AM/FM Unit. 5 preset stations, AFC and AGC circuits. Complete Kit incl. ready-built and valved Turret Tuner, £12/19/6. p. & p. 3/6. 4 apec. valves, 32/6 extra.

MERCURY 2 similar to JTV2 less power pack. Complete Kit inc. ready-built curret unit 10 gns, p. & p. 2/6. 4 spec. valves 25'-.

NEW JASON COMPREHENSIVE F.M. HANDBOOK, 2/6 post free. 48hr. Alignment Service, 7/6, p. & p. 3/6.

MAINS TRANS. AND QUALITY OUTPUT TRANS. Mfd. in our own workshops to top grade spec. Fully interleaved and impregnated. Enquiries welcomed for small production runs, prototypes or individual jobs

Recommended Buy

RECORDING TAPE BARGAINS

EMI 1st grade. Brand new sealed boxes.					
Standard Long Play					
3in., 175ft 7/- 250ft., 9/-					
5in., 600ft 19/- 850ft 25/-					
5§in., 850ft					
7fn., 1,200ft					
SPARE REELS: Emitape, new, boxed 3in. 3/-, 5in. 3/8, 51m. 4/-, 7in. 4/6.					
SPECIAL PURCHASE. Famous manufacturers, 1st grade tape, in Sealed white					
boxes.					
Standard Long Play					
5in., 600ft					
5 tin., 850ft					
7in., 1,200ft					

Plastic Tape Reels, special offer. Manufacturers' surplus. 3in. 2/9, 5in. 3/-, 5in. 3/3, 7in. 3/6.

2 WAVEBAND CAR RADIO KIT 12v. operation Med. & Long Waves



Complete Kit Bargain Price £12.19.6 P&P \$/6.

Famous manufacturer's 6 x 1 design based on Mullard and G.E.C. developments. Printed circuit, 6BVA 1st grade transistors, XA102 XA101 (2), OA70, XB103, XC101 (2) or equivalents. Quality components only supplied to ensure best results at attractive price. Set of 6 BVA Transistors and Diode. P. & P. 6d. . . 70/-

Printed Circuit, I.F.'s (3), Osc. coil, Driver Trans. and Ferrite rod aerial. P. & P. 1/6 51/6 7in. x 4in. Quality 35 ohm matching Speaker. P. & P. 1/6.......

Handbook and Circuit details, post free

KNOBS. Modern Continental types, walnut and ivory.
14im. dia. with GOLD RING 1/- ea. Ditto with GOLD CENTRE 1/3 ea.
1im. dia. with GOLD KING 9d. ea. Ditto with GOLD CENTRE 10d. ea.
LARGE STOCKS—SEND YOUR ENQUIRIES.

ORT HTR ISOLATION TRANSFORMERS

New improved types, low capacity, small size and tag terminated, A.C. 200/250 v. Secondaries Nil, +25%, +50% BOOST for 2 v., 4 v., 6.3 v., 10.5 v., 12 v. or 13 v. tubes. 12/8 each. P. & P. 1/6.

COAX 80 ohm CABLE Now only 6d. a yard.

High grade low loss Cellular Air Spaced Polythene—in. diam.— Famous mfr.

BARGAIN PRICES - SPECIAL LENGTHS.

9/- P. & P. 1/6 17/6 P. & P. 2/-25/- P. & P. 3/-Coax Plugs, 1/-; Coax Sockets, 1/-; Couplers, 1/3; Cable End Sockets, 1/6 Outlet Boxes, 4/6.

RE-GUNNED TV TUBES NEW REDUCED PRICES

and now 12 months'

All tubes rebuilt with new heater, cathode and gun assembly reconditioned virtually as new.

12in. £5, 14in. £5/10/-, 17in. £6, etc.

10/- part exchange allowance on old tube

Carr. and ins. 10/-. Compre-hensive stocks—quick delivery.

CONDENSERS—Silver Mica, All pref. values, 2 pf. to 1,000 pf., 6d. each. Ditto ceramics 9d. each. Tubulars 450 v. T.G.C. etc., 001 mfd.-01 and 1/350v., 9d. each. 0.2-1/500v., 1'- each. 25 Hunts 1/6. 5 T.C.C. 1/9. 001 6kv. 5/6. 001 20 kv. 9/8. RESISTORS—FULL RANGE 10 ohms—10 megohms 20%, ½ w. and ½ w. 3d., ½ w. 5d. (Milget type modern rating), 1 w. 6d., 2 w. 9d., 10% HI-Stab, ½ w., 5d., ½ w., 7d., 5% ½ w., 9d., 1% HI-STAB, ½ w., 1/6 (10-100 ohms 2)-1.

omms 2;-).

PRE-SET W/W POTS. T/V type, 25 ohms—
50 K ohms 3;-, 50K—2 Meg. (Carbon 3;-).

SPEAKER FRET—Expanded Bronze anodised metal 8 × 8in, 2/3; 12 × 8in, 3;-,
12 × 12in, 4/6; 12 × 16in, 6/;-; 24 × 12in.

9/-; 36 × 12in, 13/6, etc., etc.

TYGAN FRET (Contemporary pat.), 12 x 12in. 2/-; 12 x 18in., 3/-; 12 x 24in. 4/-; etc 13m. 2; 12 × 24m. 4; 12 × 24m. 4; 12 × 24m. 4; 12 × 24m. 2 hm., 2 hm., 2 hm., 2 hm., Elac, 17/6; 3 hm. Goodmans 18/6; 5 m. Rola, 17/6; 6 in. Elac, 18/6; 7 × im. Goodmans Elliptical, 18/6; 5 in. Rola, 20/-; 10 in. R. and A., 25/-; 10 in. W.B. HF1012, 95/-; 12 in. Plessey 15 ohms with 6/4in. Tweeter and Cross Over Filter, 97/6.

Electrolytics All Types New Stock TUBULAR CAN TYPES

25/25 v. 50/12 v. 1/9 8+8/450 v. 4/6 50/50 v. 100/25v. 2/- 32+32/275 v. 4/6 8/450 v. 4/350 v. 2/3 50+50/350 v. 6/-3 16+18/450 v. 5/6 60+250/275 v. 12/6 32+32/450 v. 6/6 100+200/275 v. 12/6

Comprehensive range in stock.

VOLUME CONTROLS—5K—2 Megohms ALL LONG SPINDLES, MIDGET TYPE 1tin. diam. Guar. 1 yr. LOG or LIN Ratios less 8w., 3/-. D.P. 8w., 4/6. Twin gang stereo controls less 8w.. 6/6. D.P. 8w

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve Line-up: ECC85, ECH81, EF89, EABC80, EL84, EM81, EZ80.

Three Waveband and Switched Gram positions. Med. 200-500 m., Long 1,000-2,000 m., VHF/FM 88-95 Mc/s. Philips Cont. nental Tuning insert with permeability tuning on FM and combined AM/FM IF transformers, 460 Ke/s. and 10.7 Me/s. but core tuning all colls. Latest circultry including AVC and Neg. Feedback. Three watt output Sensitivity and reproduction of a very high standard. Chassis size 13 × 3 in. Height 7 in. Edge Illuminated glass dial 11 x 3 in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250 v. operation, Magic-eye tuning. Cont nental Tuning

Maglo-eye tuning.

Aligned and tested ready for use. £13. 10. 0 Carr. & Ins. 5/-.

Complete with 4 Knobs—wainut or ivory to choice. Indoor FM aerial 3/6 extra. Three ohm P.M. speaker only required. Recommended quality speakers. 10in. Rola (Heavy Duty) 10in. Rola (Heavy Duty) . . 8in. Goodmans special cone

8in. Goodmans special cone

Post & Pkg. 1/6.

As previously announced fresh supplies are now being received, but we regret some slight delay may be experienced in fulfilling orders for this popular item.

ONLY A FEW ITEMS ARE LISTED FROM OUR COMPREHENSIVE STOCK. WRITE NOW FOR FULL BARGAIN LISTS, 3d.

Terms: C.W.O. or C.O.D., post and packing up to 11b. 7d.;

11b. 1/1; 31b. 1/6; 51b. 2/-; 101b. 2/9.



RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK RD., THORNTON HEATH, SURREY Established 1946.

Tel.: THO 2188. Hours: 9 a.m.-6 p.m. 1 p.m. Wednesday.

SAMSON'S SURPLUS STORES LTD.

LONDON'S GREATEST DEALERS IN RADIO AND ELECTRONIC EQUIPMENT



All ratings tropical and in perfect condition.

No. 1. Pri. 230 v. Sec. tapped 11, 11.5, 12, 12.6 v. 100 amps. £9/15/-. Carr. 10/-.

No. 2. Pri. 230 v. Sec. tapped 28, 29, 30, 31 v. 21 amps., £4/19/6. Carr. 7/6.

No. 3. Pri. 240 v. Sec. 6-12 v. 10 amps. 45/-. Carr. 4/-

No. 4. Pri. 100-240 v. Sec. two separate windings. Tapped 15, 16, 17 v. 4 amps. 37/6. Carr. 4/-.

Pri. 200-240 v. Sec. 6.3 v. IS amps., 25/-. P.P. 3/6.

No. 6. Pri. 220-240 v. Sec. four separate windings 3 x 5 v. C.T. 4 amps., 4 v. 4 amps. Potted type, 32/6. P.P. 3/6.

No. 7. Pri 220-240 v. Sec. three separate windings. 6.3 v. 4 amps. C.T., 6.3 v. 4 amps. C.T., 6.3 v. 4 amps. C.T., 6.3 v. 4 amps., 29/6. P.P. 3/6.

No. 8. Pri. 230 v. Sec. 6.3 v. 5 amps., 6.3 v. I amp. and tapped H.T. winding, 65 v., 130 v., 195 v., 85 mA., 15/-. P.P. 2/6.

No. 9. Pri. 220-240 v. Sec. tapped 9 v. 15 v. 4 amps., 22/6. P.P. 3/6.

No. 10. Pri. 220-240 v. Se 24 v. 2 amps., 22/6. P.P. 3/6. Sec. tapped, 12, 20,

No. 11. Pri. 200-240 v. Sec. tapped 48, 56, 60 v. 1 amp., 27/6. P.P. 3/6.

No. 12. Pri. 200-240 v. Sec. tapped 3, 5, 12, 20, 30 v. 2 amps., 25/-. P.P. 3/6.

No. 13. Pri. 230 v. Sec. 10 v. C.T. 10 amps. and 4 v. 7 amps., 32/6. P.P. 36/.

No. 14. Pri. 200-240 v. Sec. tapped 30, 32, 34, 36 v. 5 amps., 57/6. Carr. 4/-.

No. 15. Pri. 200-240 v. Sec. tapped 10, 17, 18 v. 10 amps., 57/6. Carr. 4/-.

No. 16. Prl. 230 v. 50 v. 2 a., 6.3 v. 5 a., 6.3 v. 2 a., 6.3 v. 1 a., 6.3 v. 0.6 a., 5 v. 3 a., 5 v. 5.6 a. Potted type, 39/6. Carr. 5/-.

No. 17. Pri. 240 v. Sec. tapped 6 v.-12 v., 20 amps., 69/6. Carr. 4/-.

No. 18. Pri. 240 v. Sec. tapped 12 v.-18 v., 10 amps. 52/6.

ADMIRALTY THREE-PHASE TRANS-FORMERS. Pri. 400-440 v. 50 cycles. Sec. 50 v. 6 amps. Completely tropicalised. Size 7½ x 14 x 5in., weight approx. 60lb. Brand new in maker's cases. Price 85/-. Carr. 7/6.

SPECIAL OFFER OF H.T. TRANSFORM-ERS. Oil filled potted. By London Sperry. Pri. tapped 100-250 v. Sec. 450-0-450 v. 106 mA 5 v. 3 A., 6.3 v. 2 A., 6.3 v. 1.5 A. Brand new 35/-, p.p. 5/-.

SPECIAL OFFER! AMERICAN POTTED OIL FILLED LF CHOKES. 8 H. 800 mA. 200Ω 7,000 v. Rms test 45/-, carr. 7/6. 18 H. 200 mA. 175Ω, 41,000 v. RMS test 45/- carr. 7/6.- 8 H. 300 mA. 90Ω, 7,000 v. RMS test 15/-, carr. 4/-. 10 H. 250 mA. 135Ω, 2,000 v. RMS test 12/6, p.p. 3/6.

SPECIAL OFFER: PARMEKO L.T. TRANSFORMERS. Pri. 230 v. Sec. 24 v. 2 amps. Tropically rated, completely enclosed in metal cases with fitted fuses and neon indicator. Brand new in maker's cartons.— Fraction of cost. 25/-. P.P. 3/6.

MINIATURE L.T. TRANSFORMERS. Pri. 230 v. Sec. 30 v. 0.75 A. 1½ x 1½ x 1½ ins. 7/6, p.p. 1/6,

E.D.C. LTD. ROTARY CONVERTOR. D.C. input, 230 v. A.C. putput 230 v. 8.7 amps. Complete with starter switch and fuse box. Reconditioned as new £45. Ex-warehouse. CROMPTON PARKINSON. D.C. -input, 240 v. A.C. output 230 v. 6.5 amps. Complete with 6 inch 0-300 volt meter. Starter switch and fuse box, £40. Ex-warehouse.



Manufactured by Crompton Parkinson MI 50 cycles, supplied new and guaranteed, 32/6. p.p. 3/6.

BRAND NEW A.M. A.C. VOLTMETERS M.I. 2½in. flush C-300 volts, 50 cycles, 32/6, p.p. 2/6. Rectifier Type 2,000 ohms per volt. 2½in. flush 0-2 volts, A.C. 50-10,000 cycles., in. flush 30/-, p.p. 2/6.

M.C. $2\frac{1}{2}$ in flush, 0-20 microamps, scaled minus 15—plus I decibels, 57/6. Rectifier unit suitable for audio, 3/6.

RECTANGULAR 500 MICROAMMETERS. in. Panel mounting. Scaled 0-250, 59/6, p.p. 2/6.

WESTINGHOUSE HEAVY DUTY L.T. SUPPLY UNITS

SUPPLY UNITS TYPE 115. A.C input TYPE IIS. 200-250 volts. D.c. 26 amps. into a 24 volt (nominal) battery. Rating continuous. Max. ambient temp. 35 deg. C. Completely smoothed and stabilised. Built in metal case approx. size 17 x 21 x 19 inches. With fitted fuses. On/ Off switch. Reconditioned as new. £32/10/- ex. warehouse. Original

makers price over £100.



400 v. wkg. 30 mfd. BRITISH TYPES. BRITISH TYPES. 30 mfd., 400 v. wkg., 26 mfd., 500 v. wkg. 20 mfd., 500 v. wkg., 15/each. 8 mfd., 1,500 v. wkg., 12/6. 10 mfd., 450 v. wkg., 8/6. 8 mfd., 500 v. wkg., sub chassis mounting, 8/6. 8 mfd., 250 v. wkg., 5/6. 4 mfd., 1,000 v. wkg., 5/-4 mfd., 800 v. wkg., 4/6. 2 mfd., 1,000 v. wkg., 3/9. 0-5 mfd., 2,000 v. wkg. 4/6.

AMERICAN TYPES. 45 mfd., 200 v. wkg., 10/6. 16 mfd., 400 v. wkg., 8/6. 10 mfd., 1,500 v. wkg., 15/6. 10 mfd., 600 v. wkg., 10/6. 8 mfd., 1,500 v. wkg. 6 mfd., 330 v. wkg. A.C., 7/6. Please add 2/- postage on all capacitors.

HEAVY DUTY AMERICAN OHMITE HEAVY DUTY AMERICAN PRHEOSTATS. 6in. dia. 160Ω 1.95 A./0.S6, 35/-. P.P. 3/6. 3in. dia. 15Ω 2.24 A., 12/6. P.P. 2/-. 2½in. dia. 15Ω 1.83 A., 30Ω 1.9/0.67 A., 8/6. P.P. 1/6. 1½in. dia. 25Ω 0.75 A., 5/6. 350Ω 25 watt, 5/6, P.P. 1/6. Twin gang 25Ω each section 0.75A., 7/6. P.P. 1/6.

SANGAMO SYNCHRONOUS MOTORS

A.C. 200-250 v. 13in. dia., 7/6, p.p. 1/6.
S.T.C. F.W. RECTIFIERS. Brand new
Max. A.C. input 75 volts. Output 18 amps. Max. A.C. input 75 volts. Output 18 amps. 67/10/-. Carr. 5/-. Max. A.C. input 80 v. Output 3 amps., £3/2/6, carr. 4/-.

SPECIAL OFFER LATEST A.M. RELEASE Isolation Transformers. Pri. tapped 100, 200, 220, 240 v. Sec. 225 v. I.I. Amps. Tropically rated. Guaranteed £3/5/-. Carr. 7/6.



G.P.O. 3000 Type 22,000 Ω 2M, 15/*. 10,000 Ω 1CO 1HD,B, 15/*. 6,000 Ω 4M 2B, 12/6. 6,000 Ω 2M 2B, 12/6. 6,500 Ω 1CO 1B, 12/6. 5,000 Ω 1HDB, 10/6. 500 Ω GCO, 15/*. 500 Ω 2CO 1B, 10/6. 500 Ω 1CO 2B, 10/6. 2,000 Ω 1B, 7/6. 2,000 Ω 1M, 7/6. 2,000 Ω 5CO, 15/*. 250 Ω 4M 4B, 10/6. 200 Ω 3CO, 10/6. 120 Ω 3M 1HDM, 10/6. 100 Ω 3M, 8/6. 50 Ω 2 HDM, 8/6.

AMERICAN SEALED RELAYS. 7,500Ω ICO IM, 12/6. 9,000Ω ICO, 10/6. P.P. 1/6. WINSTON SEMI-DECADE OSCILLA-TOR. Fre. 10 C.S. 70, 100 kc/s. in four ranges. Amplitude stability plus or minus 1% at any frequency. A.C. 100-250 v., £48/10/-.

DECADE CAPACITOR BOX. Range .001 to 1.11 mfd. Zero capacitance 50 pF voltage 750 v. D.C., £11/11/-.

DECADE RESISTOR BOX. 100 ohms-11 100 ohms, zero res., 0.006 ohms, £13/13/-. Further information on the above instruments will be sent on application.

HEAVY DUTY AUTO TRANSFORMERS. Tropically rated at 5 kVA. Tapped 250, 240, 230, 220, 120, 115, 110, 105 volts. Completely enclosed in metal case. Size 23 x 14 x 11ins. Weight approx. 2 cwt. Brand new, £15. Ex-

We have London's largest selection of Auto Transformers from 60 watts to 15 kVA. Available from stock. Let us know your requirements.

AMERICAN HEAVY DUTY AUTO TRANSFORMERS. 7½ kVA, 115-230 v. "C" core winding. Completely enclosed £12/10/-, ex-warehouse.

A.M. D.C. SUPPLY UNITS. A.C. input 200-240 v. D.C. output 160-200 v. 0.25 amp., £2/7/6, carr. 7/6.


A.C. ELECTRIC CHECK METERS. 200-250 v. 20 amp., 22/6. 10 amp., 19/6, carr. 3/6. Reconditioned and guaranteed.

A.M.L.T. SMOOTHING CHOKES. Resistance 1 ohm. Ideal for smoothing 12-24 v. D.C. 5 amps. Tropically rated. Brand new, 17/6, p.p. 4/-



DOUBLE READING, MOVING COIL. 0-3 v. and 0-30 v. D.C. Centre zero. Offered at a fraction of maker's price, 12/6, p.p. 2/-. HOOVER HEAVY DUTY BLOWERS. A,C. 220-240 v. Inlet 6in, dia. Outlet 73 x 64in. Motor spec. I/6th h.p. Cap. start, 950 r.p.m., £8/15/-, carr. 15/-,

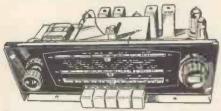BRAND NEW AM/FM (V.H.F.) CHASSIS AT £13.6.8. (P. & P. 10/-)



Tapped input 220-225 v. and 226-250 v. A.C. ONLY.
Chassis size 15 × 6 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 5 \(\frac{1}{2}\) × 4 in. in gold and black.
Pick-up. Extension Speaker, Ae., E., and Djole sockets. Five "piano" push buttons—
OFF, L.W., M.W., F.M. and Gram. Alligned and tested.
With all valves & O.P. Transformer, Tone-control fitted.
Covers 1,000-1,900 M., 200-500 M.; 88-99 Mc/s.
Valves EZ90 rect., ECH81, EF89, EABC80, EL84, ECC85. Speaker and Cabinet to fit chassis, 57/8.

Valves E230 Feets, ECHOS, BEOS, EARDON, EART, ECONOMIC STREAMS, 5716.

10 × 6in, ELLIFPIOAL SPEAKER, 20/- to purchasers of this chassis.

TERMS:— (Chassis) 25/6/8 down fine, carr.—and 6 Monthly Payments of 30/-, or with Cabinet and Speaker 25/9/2 down and 7 monthly Payments of 32/-.

Some tarnished but fully working unused chassis at £10 (10/- carr.).



3-VALVE AMPLIFIER (INCL. RECT.)

Capable of giving 4 watts. Mains and output transformer. Valves EOC83, EL84, EZ80, 3 Controls, volume, base and treble. On/Off switch. Pully guaranteed. Chassis size 6½ × 3 × 2½m.; with 7 × 4in. elliptical speaker or 6½in. round (Goodmans); state which.

ONLY 67/-. (3/- P. & P.).

STUPENDOUS OFFER! 13-CHANNEL TUNER

I.F. 34-38 Mc/s. complete with valves PCF80 and PCC84. Removed from chassis but in working order. Also 16-19 Mc/s.

15/- (2/6 P. & P.) Knobs 2/6 extra. Some tuners less valves 7/6. 50 SILVERED MICA AND CERAMIC CONDENSERS, 10/-. 50 RESISTORS, 5/-.

NEW WAXED TUBULARS, 350 v. or above, 3 of each. .001, .002, .005, .01, .02, .05, .1 mF. Total 21 for 4/6, post paid.




NEW ITA AND BBC TUNER

By well-known manufacturer for superhet TVs with 35-38 Me/s. LF. For all a-east covers all 13 channels. Switch gives BBO and two ITA selections. Built GLEC, sets BT6-45, 45-45 5146, 5147, 5543, 5642 and 6641 without alteration. Easily adapted as aerial convertor, and instructions can be provided free. WITH VALVES ICF80 and FCO94, 2216 (F. & F. 3f-.). Some without valves at only 12/6 (F. & F. 3f-.).


GRAMOPHONE AMPLIFIER

 with 5in. SPEAKEE. On Fabriccovered Baffe 121 × 8in. Mains
and Output Transformers. E240
and E141 Valves. Tone and
Volume Controls. On/Off switch
Plenty of Volume. Pully Guarant-ed.
for Stereo. ONLY 57i-, post 3j-.





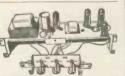Brand new 200-240 A.C. mains. treble and vol. controls flying panel. With valves EZSO, ECCS3 and 2-ELS4 giving full 8 w Chassis 12 x 31 x 31in. trans. for 2-3 ohm speaker.



A Quality Tape Recorder. Valves EZ80, ECC83, ECL82, DM70 Record Level Indicator. Acos Crystal Mike. 850ft. Emitape. Extra spool. 3½m./sec. B.8. R. Monardeck (1) Vol. (2) On/Off Tone. (3) Ext. L.8. (4) Monitor. (5) Radio Input. (6) Mike input. Fast forward and reverse controls. Cabinet size 14 x 11½ x 7in. Today's Best Value at 22 gns. (10/- P. & P.). Low Interest Terms: £6 down and 6 monthly payments of £3. Write for descriptive leaflet. Cheaper model at £20 carr. pd.



LISTEN WITHOUT INTERFERENCE

Fully built V.H.F./F.M. Set. Mullard permeability tuner. FOUR Mullard valves, 88-98 Mc/s. Metal (Blue and grey) cabinet 12 x 71 x 6in. ONLY £8/8/- (4/carr.). Cheap room dipole 10/-, 300 ohm twin feeder. 6d. yd. With 12 months' guarantee.

Delivery by return. C.O.D. 2/- extra. Terms: Cash with order or one-third down and balance plus 7/8 (up to £7/10/-) in equal four monthly payments. Balance over £7/10/- add 1/- in £1 and pay in not more than 0 monthly payments. See special terms for AM.-F.M. chasels. All new goods unless stated. Send 6d, for 16-page catalogue. SATISFACTION GUARANTEED. Posted orders to Camberley.

GLADSTONE RADIO 58A HIGH ST., CAMBERLEY, SURREY. Tel. 22791
3 Church Road, Bristol 5. Tel 51207 (Camberley closed Sat.)
247, New Road, Copnor, Portsmouth, Hants.
(Portsmouth and Bristol closed Wednesday afternoon)

Just out! the NEW

STANELCO

An ideal general purpose iron

100 WATT SOLDERING IRON

costs only 2 G

including post and packing. Trade quantity discounts on request.

Perfectly balanced

- Flat copper bit shaped for any application
- New stainless steel side plates eliminate corrosion
- Strong robust element with large surface ensures good heat transfer and long life
- Improved shock resisting moulded

10

A really professional, high wattage iron at an economical price.

Suitable for operation at 12 v., 50 v., 100/


Please state voltage required when ordering. Send for leaflet or order direct from:

Standard Telephones and Cables Limited Industrial Supplies Division

Stanelco Process Heating, Footscray, Sidcup, Footscray 3333


All elements flash tested at 1000 volts to earth to ensure RELIABILITY. QUALITY AND SAFFTY

High Torque!

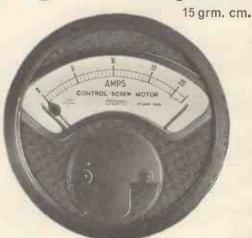

6" Contact-Making Indicator

 This exceptionally high torque instrument can be supplied for D.C. and A.C. rectifier operation, with high and low contacts (100mA, 50 volts D.C. or non-inductive A.C.).



Full details from: - Electrical Measurement Division Elliott Brothers (London) Ltd Century Works, Lewisham, London SE13. Tel: TIDeway 1271 EMD6 S.T.C. SELENIUM METAL RECTIFIERS. F/B, FOR BATTERY CHARGERS, ETC. 6 or 12 v. 1 amp. 5/-; 24 v. 1 amp. 10/-; amp. 15/-;

24 v. 2 amp. 24 v. 3 amp. v. 2 amp. 7/6; v. 2\frac{1}{2} amp. 12/6; v. 4 amp. 30/amp. 24 v. 6 amp. 32/6; 24 v. 10 amp. 70/-; v. 6 amp. 20/-; v. 10 amp. 35/-;

NEW AND UNUSED ACCUMULATORS



12 v. 25 A.H. (as illus.) 45/-. Carr. 7/6. (Ideal for use with our Amplifier in centre column).

2 v. 100 A.H. 75 (ex-Govt.) with carrying handle. Size $6\frac{1}{2} \times 6\frac{1}{4} \times 3\frac{1}{2}$ in., 15/- each. Carr. 3/6.

2 v. 16 A.H., as above. $7\frac{1}{2} \times 4 \times 2$ in., 5/- each. P. & P. 2/-.

6 for 24/-. P. & P. 10/-. 2 v. 14 A.H., as above (less handle). 7 x 2\frac{1}{4} x 2\frac{1}{2} in.,
5/- each. P. & P. 2/-.

TRANSFORMERS

POTTED C CORE

Pri. 230 v. 50 c/s. Sec.: 450-0-450 v. 220 mA. 5 v. 3 amps., 6.3 v. 5 amps., 6.3 v. 3 amps. £2/10/-. Carr. 5/-.

Pri.: 230 v. 50 c/s. E.S. Sec.: 500-0-500 v. 500 mA. 6.3 v. 500 mA., 6.3 v. 5 amps., 5 v. 6 amps. £3/10/-. Carr. 5/-.

Pri.: 230 v. 50 c/s.

Pri.: 230 v. 50 c/s. Sec.: 6.8 v. 5 amps., 6.3 v. 1 amps., 6.3 v. 3 amps., 6.3 v. 15 amps., 6.3 v. 2 amps., 6.3 v. 3 amps., 6.3 v. 4 amps. £1/12/6. Carr. 5/MAINS ISOLATING TRANSFORMER (Gresham). Pri. 230/250 v. Secs. 240-0-240 v. 1.5 amps., 5 v. 12.5 amps. Potted. Size 7in. x 7½in. x 10½in. Weight 50 lb. Ideal for obtaining TWO ISOLATED 240 v. lines at 360 watts each. Perfect condition. 80/-. Carr. 10/-.

Perfect condition. 80/-. Carr. 10/-.

L.T. TRANSFORMERS for Battery Chargers etc. All Pri.: 200/250 v. Tapped 50 cycles. Type 048B. Sec. 24, 30, 36 v. 6 amps. 4 x 4 x 4in. £2/9/6. Carr. 3/6. Type 056A. Sec. 18, 24, 30, 36 v. 8 amps. 4 x 4 x 5in. £3/19/6. Carr. 3/6. Type 053A. Sec. 12, 24, 30 v. 10 amps. 4 x 5 x 5in. £4/4/-. Carr. 3/6.

AUTO TRANSFORMERS. 0-110, 205, 225, 245 v. Fully shrouded. Terminal block

connectors,

Connectors, Type 063A. 500 w., 4 x 5 x 5in. £3/7/6. Carr. 3/6. Type 064A. 750 w. 4 x 6 x 5in. £3/17/6. Carr. 3/6. Type 065A. 1000 w. 4 x 7 x 5in. £4/17/6. Carr. 5/-. 3 kV/A. AUTO TRANSFORMER. 250/110 v. 50 cycles (fully tapped primary and secondary). Capable of 25% over actual rating. Brand new and unused, £12/10/-. Carr. 20/-. Also 6 kV/A. as above. £18. Carr. 20/-.

20 kV/A. AUTO-TRANSFORMER. 230/115 v. 50-60 cycles, by Jefferies Transformer Co. U.S.A. Perfect condition, £20. Carr. 20/-.

CONSTANT VOLTAGE TRANSFORMER 190-260 v. primary, sec. 115 v. at 1½ kV/A. (tisted at 2 kV/A). Brand new and unused. £25 or £45 per pair. Carr. 10/- each.

per pair. Carr. 10/- each. E.H.T. TRANSFORMER. 400 mA. Primary 230 v. 50 8.000-0-8.000 at E.H.T. TRANSFORMER. 8,000-0-8,000 at 400 mA. Primary 230 v. 50 cycles. Oil filled. New and in original crates. £25. Carr. 10/-E.H.T. TRANSFORMER. 1,800-0-1,800 at 1 kV/A. 230 v 50 cycles primary. Fully tropicalised. New and boxed. £6/10/-. Carr. 10/-E.H.T. TRANSFORMER. 1,100-0-1,100 at 250 mA. plus 4 v. L.T. Pri. 200/250 v. at 50 cycles. £5. Carr. 10/-.

CONDENSER, oil filled. 240 mfd. 230 v. A.C. or 600 v. D.C. Made in U.S.A. Size 21in. x 5⅓in. x 9in. Brand new In original cases. £7/10/-. Carr. 5/-.

ROTARY CONVERTER. 24 v. D.C. input. 230 v. A.C. output at 250 watts. Complete with starting switch. New and unused. £15. Carr. 7/6.

Carr. 7/6.

ROTARY CONVERTER. 24 v. D.C. to 230 v. A.C. 50 cycles, 150 watts. Brand new and unused. £8/10/-. Carr. 7/6. Ditto, 100 watts £6/9/6. Carr. 7/6.

ROTARY CONVERTER. Ex-Govt. D.C. input, 230 v. A.C. output 50 cycles at 135 watts. Complete in carrying case with lid. Voltage control, sliding resistance, mains switch and 0-300 v. A.C. flush meter. In good condition. £10. Carr. 10/-.

Motor only, without case, etc. Brand new and unused. £8/10/-. Carr. 5/-.

GEE BROS. (RADIO) LTD.

15 LITTLE NEWPORT STREET, LONDON, W.C.2. GER. 6794/1453

ADJOINING LEICESTER SQ. TUBE STATION-Open 9-6 Weekdays. 9-1 Sat.

BAKERS 'SELHURST' SPEAKERS



SPECIAL NEW ARRIVAL! " 15în. VISCOUNT

AUDITORIUM " 15 ohms at 400 c.p.s., 35 warrs Flux density 18,000.

OUR PRICE £15.

"12in. P.M.," 15 ohms, 15 watts, 30-14,000 c.p.s. Our price £4/10/-.
"AUDITORIUM" 12in., 15 ohms, 12 watts. 35-16,000 c.p.s. Flux density 14,500. OUR PRICE £7/10/-.
"SUPER HI-FI 25" 12in., 15 ohms, 25 watts. 25-20,000 c.p.s. Flux density 17,600. OUR PRICE £9/9/-Full descriptive specification is available.

12 VOLT D.C. AMPLIFIER (Parmeko, Ardente) As new, 15 watt output with 2-EL35's in push-pull. Mike and gram, inputs, tapped output transformer, £9/19/6. Carr. 10/6. (Suitable microphone for above 30/- extra.)

EXPONENTIAL HORNS by famous manufacturer of P.A. systems, 15 watt, 25 15 watt, 25 in.long,20in. square flare 15 ohms speech coil. Tannoy) ood dition £7/10/-. Carr. 10/-. NEW P.M. HEAVY

DUTY SPEAKERS
Complete with O.P.
trans., in all steel
blue-grey double grilled cabinet. 6in. 30/-.
8in. 32/6. Carr. 3/6 each.

10in. SPEAKER in wooden cabinet, size approx. 14 x 16 x 8in. with padded interior and volume control, 50/-. Carr. 3/6.



LOUD HAILERS (Ex-Govt.) Heavy duty 20 watts all metal 15 Diaohms. meter 15in., length 15in. (approx.) £6/10/-Carr. 10/-. Brand new, 10/-.

HEAVY DUTY ALL STEEL TRIPOD STANDS (as illus. Sept. issue). Adjustable every 6in. to approx. 9ft. 6in. when fully extended. (Folds up to only 4ft. 6in. for storage.) Suitable for outdoor speakers, public address systems, flood-lighting, etc. OUR PRICE \$3/10/-. Carr. 5/-. (Ideal stand for the above loud hailer.)

TRUVOX/TANNOY LOUD-HAILERS With 180 ohm line transformer and condenser. Impedance denser. Impedance
7½ ohms, handling
capacity 8 watts.
Complete in slopefront wooden case.
Brand new 25/--

Carr. 4/6. G.P.O. RACKS 19in. Heavy duty all steel Standard drilling. 5ft. 6in. angle uprights. £3/10/-. Carr. 15/-. 6ft. channel uprights. £5. Carr. 15/-. 7ft. channel uprights. £6. Carr. 15/-. AR88-D RECEIVER.
Frequency 540 kc/s-32 Mc/s £50 carr. 20/-,
also model L.F. available 75/550 kc/s, 1-5/30
Mc/s £45, carr. 20/-, both mint condition
and overhauled for the Ministry to the
highest specifications. Limited quantity only.

OUALITY TEST **EOUIPMENT**

RECORD MEGGERS. 500 v. insulation tester, 0-20 megohms. In leather case. Perfect order. £10. EVERSHED AND VIGNOLES MEGGER

EVERSHED AND VIGNOLES MEGGER CIRCUIT TESTER (low reading ohm meter). 2 ranges 0-3, 0-30 ohms. The perfect meter for continuity and polarity testing, complete with test leads and ready to use. Brand new. Only £4/17/6. P. & P. 3/-.
BRIDGE MEGGERS. Evershed and Vignoles. Series 2 in perfect condition. 250 v. £22. Carr. paid. Leather case available at 20/- extra. MARCONI SIGNAL GENERATOR. TYPE TESTIZ-EIL CONSTITUTION.

paid. Leather case available at 20/- extra.

MARCONI SIGNAL GENERATOR. TYPE
TF517-F/I. Covering 10-18 Mc/s. 33-58 Mc/s.
150-300 Mc/s. In very good condition. Complete with full technical data and instructions.
Unrepeatable at only £12/10/-. Carr. 20/BRAND NEW CRYSTAL CALIBRATOR
No. 10. (Battery powered 1.4 v. valves.) Complete with full working instructions, circuit diagram, carrying haversack, connecting lead and spare valves. Frequency range: 1.5 to 10 Mc/s. (nominal) but can actually be used up to 30 Mc/s. Weight 51b. Size 7 x 7½ x 4in. A miniature B.C.221 in every respect. A must for every laboratory, etc. ONLY £4/19/6.
P. & P. 2/6.

MULLARD BRIDGE. Type GM. 4140/I. Mains operated from 100-250 v. A.C. Will test resistances from 0.1 ohm to 10 megohms and condensers from 10pf. to 10mfd. Good condition and complete with instruction booklet. £6/19/6. P. & P. 2/6.

TAYLOR VALVE TESTER Model 47A. Input 200-250 v. A.C. Will test all types of finglish and American valves with filaments from 1.1 v. to 117 v. Perfect condition. Complete with full instruction manual, £12/10/-. Carr.paid. Also MODEL 45A available at £10/10/-. Carr.paid. Also MODEL 45A available at £10/10/-. Carr.paid.

10-LINE TELEPHONE SWITCH-BUANDS. For the complete control of 10 extensions (Tele. "F" etc.). Complete with jacks, leads and operator's hand set. Good condition. £9/19/6. Carr. 10/6

TELEPHONE SETS (TELE "F")
Housed In Bakelite cases, complete with bullt-in ringing generators and batteries. Ideal between two or more positions up to practically any distance. Tested before despatched. ONLY 70/-. P. & P. 3/6. 2 sent for £6/10/-. Carr. paid. TELEPHONE CABLE. Twin one-mile drums (Don 8), £5. Carr. 20/-. Single one-mile drums (Don 3), 50/-. Carr. 7/6.

COLLARO "STUDIO" TAPE TRANS-CRIPTORS. Brand new In original cartons. TELEPHONE SETS (TELE "F"

COLLARO "STUDIO" TAPE TRANS-CRIPTORS. Brand new lin original cartons 3 speeds. 12, 32, 74 i.p.s. 3 motors, digital counter. etc. Complete with 7in. spool instructions and fixings. A.C. 200/250 v. operation. SPECIAL PRICE £12/10/- only. RECORDING TAPES. Super quality P.V.C. 1,800ft. L.P. 7in. spools, 30/-; 1,200ft. Std. 7in. 19/-; Empty 7in. spools 3/9 each. Send S.A.E. for current Tape Bargain List.

A.C.-D.C. RECTIFIER POWER SUPPLY UNITS

UNITS
110/230 v. A.C. 50 cycles input, 100/110 v. D.C. output max. 2½ amp. Brand new and unused. £4/10/-; Carr. 7/6.
230 v. A.C. 50 cycles input, 200/220 v. D.C. output at 3/4 amps. approx. Good condition. £10. Carr. 10/-.
200/250 v. pri., 110 v. sec. at 4 amps. max. Brand new and unused. £8/10/-. Carr. 10/-.
Type 67. 200/230 v. A.C. 50 cycles input, 240-0-240 v. D.C. output at 1½ amps. (Yalve rectification.) With overload controls. Brand new In maker's original crates. £10. Carr. 10/-.

AIRBORNE TRANSMITTER RECEIVER TYPE 1986. A mobile 10-channel crystal con-trolled V.H.F. Tx/Rx. covering 124.5/156 Mc/s. I.F. band width 23 kc/s. Complete (less external I.F. band width 23 kc/s. Complete (less external attachments) in metal case, with all valves and 24 v. rotary power unit. Used but in first-class condition. ONLY £8/10/-. Carr. paid Also, complete with control box and all necessary connecting leads, £12, carr. paid.

HEAVY DUTY REGULATING RESISTOR. 0.25 ohm, 200 amps. Carr. 10/-. Wheel control



TRANSISTORISED POWER SUPPLIES

7	INPUT VOLTAGE YPE A	OUTPUT VOLTAGE	OUTPUT FREQUENCY	OUTPUT POWER
	12VDC or 24VDC	200-250V	50c/s squarewave	75 V A to 750 V A
For use where a squarewave output waveform is acceptable				

TYPE B

	or 28VDC	115V	400c/s sinewave	to 750VA
- 1		a strictly sinusoi content less tha	dal output wavefor in 5%.	rm is essential;

24VDC 200-250V 50c/s sinewaye 75VA

TYPE C

1	24VDC	240V	2,000c/s	10W or 40W
	For battery oper	rated fluorescen	t lighting; no star	ters or ballasts



12VDC or 24VDC	As required	DC	Up to 600W
For H.T. DC s	upplies.		

TYPE E(1)

12VDC	275V	DC	30W
For receiver p	ower supply; pri	ce £15 . 0 . 0d.	

TYPE F (2)

12VDC	310V	DC	80W
For transmitter power supply; price £17.10.0d.			


Type's E(1) and E(2) have been specially designed to replace the rotary generators or vibrator packs used in mobile VHF transmitter-receivers. They are compact, cheap, require no maintenance and effectively reduce battery drain. Other voltages are available, as required.

Full particulars from

ELLIOTT BROTHERS (LONDON) LTD

TELECOMMUNICATIONS DIVISION

 Elstree Way, Borehamwood, Hertfordshire. Telephone: Elstree 2040



EXPORT ONLY



A 10 valve High-Grade Super Heterodyne Receiver with facilities for Receiving R/T (A.M. or F.M.) and

Hermetically sealed. Built on miniature valves and in-corporating its own vibrator power supply unit driven by a 6 v. battery (2 point connector included).

The set provides for Reception from rod, open-wire or dipole aerial, with loudspeaker or phone output. Overall measurements:—Length 12in., width depth 9in. Weight 23 lbs.


FULLY GUARANTEED AND TESTED

All enquiries:

P. C. RADIO LTD.

170, GOLDHAWK ROAD, W.12 Telephone: SHEpherds Bush 4946

EXPORT ONLY
PROMPT deliveries Mobile V.H.F. Radio Telephones. Frequency ranges on five bands (1) 36-44 Mc/s, (2) 65-78 Mc/s, (3) 78-100 Mc/s, (4) 118-132 Mc/s, (5) 156-174 Mc/s. R.F. output 10 watts. A.M. Single Channel, crystal controlleu. To operate from 6 v., 12 v. or Mains supply sources. Reconditioned with same as new guarantee. Prices from £55 per complete station FOB U.K. Port, as illustrated.

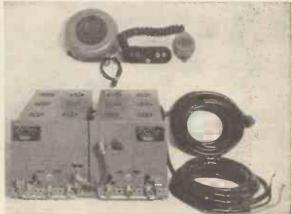

GENERALLY AVAILABLE

H.F. Radio Transmitters 300 watts Modulated R.F. Output.
H.F. Radio Telephones 1½-12 Mc/s, 25 watts R.F. Output.
Military Wireless Sets of very many types including Handy-Talkies.
Spares of all types for military equipment.
Field Telephones of all types, Switchboards and line components of British

Post Office types. Carrier Telephony Systems-Terminals and Repeaters-Components of

all types.
V.F. Telegraphy Systems—Terminals and Repeaters—Components of all types.
Aircraft Radio Compasses, Distance Measuring Equipment and also 10-Channel V.H.F. Radio Telephones.

R. GILFILLAN & CO. LTD. NATIONAL PROVINCIAL BANK CHAMBERS 29 SOUTH STREET, WORTHING, SUSSEX Tel.: Worthing 8719 & 30181 6

6

6 ò



ATP4 AZI AZ3I

B36 CV73

DAF96

DF96 DH101

DK96

DL82 DL96

DM70 DN4I EA50 EABC80

EAF42 EB34

EBC33

EBF80

EBF89

ECC81 ECC82 ECC83 ECC84 ECC85

ECF82 ECH42

ECH81

ECL82 ECL83

EF22 EF36

EF37A EF39

FF40

EF41

FF47

EE55

FF85 EF86

FF89

EF91

EL32 EL33

FI 34

EL41

EL42

EL84

EM34 EM80

EM81

EY81 EY86 EZ40 EZ41 EZ80

EZ8I EZ90

E638

E1148

H30

H63

FW4/500 GZ32

EF50SYL

EB4 EB91 3/6/KT33C

10/- KT61

10/- KT66 4/- KT74

5/- KT76 8/- KT101

8/- KTW61 10/- KTW63 8/- KTZ41 9/- MH41

10/6 MHL4 8/- MSP4/5 7/6 MSP4/7 12/6 MSP4/1

1/6 MX40 9/- OZ4

9/6 P61 2/- PCC84

8/6 PCC85 4/- PCF80 6/9 PCF82 8/9 PCL82

9/9 PCL83 9/6 PL36

7/6 PL8I 8/- PL82

8/- PL83 10/- PL84

9/6 PL820 12/- PX25

10/6 PY80

9/6 PY81

O/ PYRT

9/6 PY83

10/6 PEN4VA 19/3 PEN25

8/6 PEN45

15/- PEN220A 5/9 PENA4 13/6 PMI2M

13/6 PM12/ 9/6 QP2/ 11/- SP4/ 4/- SP6/ 17/- SP4/5 6/- SP4/7 10/- TP25 7/- U10 7/- U14

12/6 ML4

4/- U16 17/3 U22 7/- U25 4/6 U26

14/- U37 15/- U45 9/- U50

10/6 U76

9/- U81 4/- U82

9/6 U101

10/6 U329 9/6 U403 13/3 U404 10/- UABC80 7/6 UAF42

7/6 UAF42 7/6 UB41 7/- UBF80 7/6 UCC84 26/6 UCC85 2/- UCH42 10/- UCH81

11/6 UCL82

5/- UCL83 8/6 UF41

8/6 UF80

8/6 UF85 5/- UF89 5/- UL41

8/9 M54B

FOR VALVES. TUBES AND COMPONENTS-BY RETURN POST SERVICE

	UYIN	12/616K8G	6/6.78	7/
	UY4I	7/6 6K6GT	7/-180	8/
	UY85	7/- 6K7GT	5/9 142BT	3/
	VP13C	3/6 6K8GT		
	VP23	6/6 6K25	19/11 210DDT	4/
	VR22	6L6G	8/- 210VPT	3/
	(PM2A)	3/- 6L6M	9/6 85A2	10/-
8/-	-IVP4I	8/6 6L7	7/6 807	61
19/3	VR105/30	8/-16L18	11/6 954	2/
7/-	VRII6	41-16L19	23/3	-,
	VR150/30	7/6 6N7GT	7/61	_
	VU120A	3/6 6P28	26/6	

7/6 9/-8/-7/6

4/6

7/6

8/6 6/-7/6 6/9 7/-7/-

10/6

8/6

13/6 8/-9/-9/6

8/

3/6 12/-

12/-

7/6 8/-8/-

8/-9/-9/-

616

6/6

10/-

10/6

10/-

10/-

10/6

10/6

12/6

12/6

9/9

7/-8/-9/-11/6

8/6

6/-

6/6 VU39 (MU

10/= 12/14 6/6 VUIII 7/6 W21/7

3/6 W76 7/9 W77

7/6 W101 7/6 W729

8/6 IL4

8/6 ILD5 12/7 IN5

18/7 IR5 12/6 IS4

7/6 IS5 8/6 IT4

7/ 345

12/6 4D1

8/- 5R4GY 5/- 5U4G 3/- 5V4G

3/- 5V4G 3/- 5Y3G 10/6 5Y3GT 10/6 5Z4G 10/- 5Z4M 9/6 6A7 8/6 6A8G

10/- 6AG5

12/6 6AK5 8/- 6AL5

13/6 6AM5

10/- 6AM6

26/6 6AQ5 15/- 6AT6 8/- 6AU6 7/- 6B8G

8/- 6BA6 8/- 6BE6 8/- 6BH6

16/7 6BJ6

23/3 6BR7 16/7 6BW6 11/4 6BW7

9/- 6C4 9/6 6C5GT 9/- 6C6 8/6 6D6

9/- 6CH6 10/11 6F6G

9/6 6F6M 9/6 6F33

11/6 6H6GT

9/6 6H6

13/6 6J5G

10/6/6/5M

9/- 6J6 9/- 6J7G 9/- 6K7G 9/- 6K7M

8/6 3A8GT 10/- 3D6 6/- 3Q4 26/6 3Q5GT 7/- 3S4 4/- 3V4

7/6 W61 6/- W61 (M) 12/6 X22 C1 5/6 X41M 3/6 X101M 8/6 Y63

8/6/Y63 7/6/6/Y68 11/6/Z21 (4 pin) 5/-6/Y6GT 8/9/Z309 26/6/6/X4 11/6/Z359 9/6/6/X5G 12/-1A7GT 12/6/6/X5GT 13/6/1C2 11/6/6/30L2 15/-1CSGT 12/6/786 11/-1H5GT 9/-787 14/11/4 4/788

8/9 6Q7G 8/9 6Q7GT 2/6 6SA7GT 10/- 6SG7

6/6 6SH7 8/6 6SJ7

10/- 6SK7 10/6 6SL7GT

6/- 65N7GT 8/- 65Q7 24/7 6U4GT 12/6 6U5G

8/- 6U7G 7/6 6V6G

9/- 7B7 4/- 7B8

3/6 7C5 10/6 7C6 7/6 7D6 10/6 7H7

6/6 7Q7 5/6 7S7

12/6 7Y4

6/- 8D2 5/- 9D2 7/6 10D2

9/6 10F1 7/6 12A6 8/- 12AH8 3/- 12AT6 9/6 12AT7

6/- 12AU6

8/- 12AX7 7/6 12BA6

9/- 12BA6 10/- 12BE6 10/- 12C8GT 10/- 12H6 9/- 12J5GT 4/- 12J7GT

5/6 12K7GT

5/- 12K/G1 5/- 12K8GT 4/- 12Q7GT 4/- 125G7 4/- 125H7 7/6 125J7 8/6 12SK7

8/6 125K7. 10/6 125L7GT 4/- 125N7GT 7/6 1457 7/6 15D2 9/- 25A6G 9/- 25L6GT 12/6 25Z4G

9/6 25Z5 7/- 25Z6

4/6 30C1

5/-|30FL1 5/-|30P4

8/6 30P12 7/- 30P16 7/6 30PL1 7/6 35L6GT

3/6 3574GT

5/- 42 6/6 35Z5GT

6/6 50L6GT

2/6 2575



METAL RECTIFIERS

Alpha Range of Guaranteed Bridge Rectifiers suitable for Battery Chargers 6 and 12 volt output:

2	amp.		7/-
4	amp.	,	12/6
3	amp.	0 * * * * * * * * * * * * * * * * * * *	10/-
5	amp.		14/6

MILKOPHUNES

Acos Mic 39/1, crystal stick microphones for use as a hand, desk or floor stand unit, listed at 3 gns, our price 39/6. Table stand 7/6 extra, floor stand

our price 39/6. Table stand 7/6 extra. floor stand adaptor 12/6 extra.

Acos Mic 40, as supplied with modern tape recorders, with a folding rest and 8ft. lead, listed at £1/15/-, our price 19/6.

G.B.S. Microphone, pencil stick type, fitted with muting switch, 42/-.

T.S.L. Crystal "stick." microphone, model MX3, for general purpose use, complete with table stand 45/-.

stand, 45/-.
T.S.L. Moving Coil Microphone, for high or low

impedance, brown and cream plastic case with a fold-in table rest, 6ft. cable and a standard 3-way connecting continental plug, £4/4/-

LOUDSPEAKER UNITS PERMANENT MAGNET All Brand New

0

lin. Square Rola C25	26/1
2in. Square Celestion	18/6
lin. Square Celestion	18/6
lin. Square Elac	19/6
in. Round Plessey with O.P.T	16/6
in. Round Celestion	17/6
Bin, Round Richard Allen	18/6
Oin. Round Philips type, with Tweeter	27/6
Oin. Round Elac	25/-
2in. Round Plessey	29/6
2in, Round Plessey, 15 ohms speech coil	52/6
in. x 4in. Plessey	19/6
in. x 4in. Plessey	19/6
Bin. x 5in. Celestion and Richard Allen	25/6
Oin. x 6in. Celestion and Plessey	25/6

SPECI	AL MAINS DROPPER RESIST	rors
	As used in	Price
SMDI	As used in Philips 209U	6/3
SMD2	Bush DAC81, DAC90 and DAC12	11/3
SMD3	Bush DAC81, DAC90 and DAC12 Philips 200U, 205U, and Stella ST101	5/3
SMD4	Philips 290U and Stella 5T100	5/3
SMD5	Bush DAC90A, DAC10 and DAC11,	3
	Ekco U76, U109	5/3
SMD6	Ultra Twin 50	5/3
SMD7	Ultra Twin 50	5/3
SMD8	Ferguson 983 and 988 Ekco T205, T164 and T174	9/-
SMD9	Ekco T205, T164 and T174	2/6
5MD10	Ferguson 983T, Philco BT1412 and	
	BT1551	9/-
SMDII	KB FPI5I	5/3
SMD12	Post-war Double Decca	5/3
SMD13	Marconi TI8DA	7/6
SMD14	Philips 12IU, 210U	6/-
5MD15	Philips 1410 and Stella ST1050	5/3
SMD16 SMD17	Ferguson 989 Ekco MBP 183	4/9
SMD18	Invicta 118T-119T-120T PAM958	9/-
5MD19	Ultra 814, VT814	4/9
SMD20	Pye V4 and C. V7 and T and 126T	6/-
5MD21	Invicta 112	7/6
SMD22	Ekco U122 and U159	6/6
SMD23	Champion Model 825	5/3
SMD24	Ferguson 998	9/
SMD25	Ferguson 998	9/-
SMD26	Pye VTI7CDL, VTI7, VTI7CD,	
	VT21C, VT21CD, PAM752, 753	9/-
SMD27	Pye Piper	
SMD28	Regentone Double 2 Portable	6/-
SMD29	Regentone Double 2 Portable	6/-
SMD30	KB Rhapsody, MP151/1	7/6
SMD31	Pye CW17 Series	6/9
SMD32	Pye C17175/213, CVV175/213	6/9
SMD33 SMD34	Pye CW17F	6/9
SMD34	Cosses 927 929 939A 939F 939	0/7
31.1033	939A, 939F, 942, 942B, 944, 946,	
	947 RI7A	6/9

947, RI7A.....

AUTUMATIC RECORD CHANGER UNITS

B.S.R. Monarch UA8, 4-speed unit with a BSR monaural ful-fi cartridge,

B.S.R. Monarch UA8, 4-speed unit a BSR stereo ful-fi cartridge, €6/19/6.

£6/19/6.
B.S.R. Monarch UA14, 4-speed unit in two-tone grey, £8/19/6.
Collaro Conquest, 4-speed fully mixing changer, complete with studio cartridge, £6/19/6.
Collaro RC4\$7, 4-speed record changer, fitted with transcription cartridge TX88, £6/19/6.
Garrard RC120, Mark II, 4 speed unit with manual control, to enable records to be played singly, fitted with GC2 Cartridge, £8/19/6.

SINGLE RECORD PLAYER UNITS

Garrard, Model TA, Mark II, 4-speed single player, dic-cast aluminium pick-up with a GC2 cartridge, automatic stop, 9½In. diameter turntable, £8/10/-.
Collaro Junior, 4-speed turntable and

Collaro Junior, 4-speed turntable and pick-up, complete with a crystal cartridge and sapphire styli, finished cream with a maroon turntable mat and speed control, £3/15/-, or turntable and motor only at £2/12/6, pick-up only £1/7/8.

AMPLIFIERS

Deccamatic, fitted with valve ECL82, contact cooled rectifier, tone and volume on/off, chassis size 8½in. x 3ln., complete with Celestion speaker 8in. x 6in., £4/5/-.

TELEPHONE ADAPTOR Geloso type 9010, 45/-.

TRANSFORMERS FOR BATTERY CHARGERS

Standard primary connections. 200/ 250 v 250 v. Type MT3 secondary tapper. 0-12-15-20-24-30 v., 2 amps., 21/9 ea. Type MT5 secondary tapper. 0-5-11-17 v., 4 amps., 21/- ea. Type MT5A secondary tapper. 0-5-11-17 v., 1½ amps., 15/- ea.

SOLDERING IRONS - SOLON Instrument type. 220/240 v., 25 watts. Model 625 24/-. Standard type. 220/240 v., 65 watts. Model 964 29/-. Spare elements, bits and bit holders

CARTRIDGES - STYLI ETC. Acos Stereo Cartridge. 73-1. Dual purpose for mono and stereo use. 32/6 ea. Garrard GC2/PA, white moulding, increased frequency response to ted frequency, 15/6 ea. "Ful Fi" Cartridge. GC2. 15/6 ea BSR, TC8M, Styli for B5R Collaro, Garrard, Acos,

RECORDING TAPES


Plastic Reel 7in. 1,200ft. Tape. Top quality. 23/- ea.




103 LEEDS TERRACE, WINTOUN STREET

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. For full terms of business see inside cover of our catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday. Saturday 10 a.m. to 1 p.m.

etc., from 6/- each.

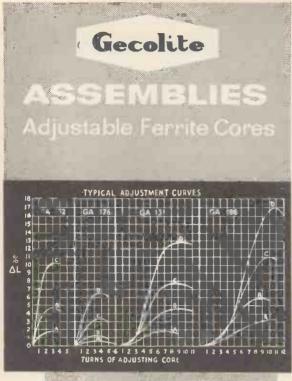

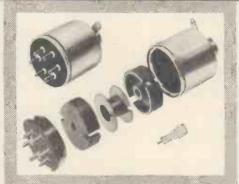



In Grade P. Gecolite, nominal initial Permeability 1200/1800 Write for Data Sheet 592



Full details of assemblies with non-adjustable cores, ask for Data Sheet 591.

ELECTRICAL INSTRUMENTS

TIMES MILL . HEYWOOD . LANCASHIRE Tel: HEYWOOD 6868 London Sales Office: Magnet House, Kingsway, W.C.2. Tel: Temple Bar 4668 A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

BETTER ^ BENSON'S BETTER BARGAINS

MORSE KEY with buzzer, on board, wired for 4½ v. battery, 8/6 (p.p. 1/6). Keys, morse, small, brass, 8 A., 3/-; covered with plug, 4/6; large 7/6. TELE "F" intercom. sets, good condition, pair 65/-, post free Gt. B. METERS (100/4) with two centre-zero movements, 600 and 400 uA, 8/6. TRANSFORMERS. Open, upright, input 200/250 v. Outputs:—250-0-250 v., 150 mA., 5 v. 3 A. and 6.3 v. 5 A., 25/-. Input 110/230 v. Outputs:—6 v., 2 A. twice, shrouded, 10/6. Potted, "C" core: Input 230 v. Outputs:—6.3 v., 0.3 A. (1A. actual), twice, 8/6; Outputs: 510-0-510 v. 275 mA., 375-0-375 v. 83 mA., 5 v. 3 A., 6.3 v. 7 times (17 A.), 45/-. CONDENSERS, block, paper, 8 mid. 250 Vv. 4/-; 600 Vw. 6/-; 4 mid. 2 kWV. 7/6; 600 Vv. 3/6. SWITCH fuse splitter, DP 15 A. 15/-. MONITOR 56, triggered oscilloscope, comprising Indicator 548 and Power Unit 675, 230 v. A.C. input, with cables and circuit. Cathode probe unit extra, 17/6. 28/10/- (Rail 15/-). HEAD-PHONES, CLR, 7/6. OR100 Noise Limiter assembles with valve, 3/6. NEW M.G. METERS, 3jin. round flush, 50µA, 70/-; 200 µA centre zero, 50/-; 1 mA., centre zero, 45/-; 1 mA., 55/-; 2½in. 1 mA., 22/6; 100 mA., 8/6; 2in. 300 mA., each 8/6; 2½in. MI. 20 v. A.C., MI., 6in., in case, 45/- VIBRATORS Mallory G634C 12 v. 4-pin, 7/6; 6 v. 5-pin reversible, 7/6. R1155B, good condition, tested, with handbook, £8 (Rail 10/-). DRIVES: slow-motion Admiralty 200:1 ratio, scaled 0-100 8/6. R1155 S.M. "N" type, new, 10/6. VIBRAPAK, 6 v. D.C. to 250 v. 60 mA., smoothed case, 22/6 (p.p. 3/6). DYNAMOTORS (post 3/6). 12 v. to 230 v. 60 mA., 11/6, 6 v. to 250 v. 60 mA., 11/6, 6 fl. C v. 10 H., 250 mA., 12/6; 51H, 400 mA., 5/6; Potted 10H, 100 mA., 7/6; "C" "10 H., 250 mA., 12/6; 51H, 400 mA., 16/6; 6 v. to 250 v. 60 mA., 11/8, 6 fl. hughly split sp

LIST AND ENQUIRIES S.A.E. please. Terms, C.W.O. Postage extra. Immediate despatch. Callers and post: W. A. BENSON (W.W.), 136 Rathbone Road, Liverpool, 15. SEF 6853. Callers: SUPERADIO (Whitechapel), Ltd., 116 Whitechapel, Liverpool, 1. ROY 1130. LIST AND ENQUIRIES S.A.E. please. Terms, C.W.O. Postage extra.





TESTING OF MULTI-CORE CABLES

Example of testing speed 25 pt cable tested:—
625 insulation tests, 25 leakage to screen, 25 continuity tests—
all in 25 seconds.
Insulation faults are shown and faulty circuits indicated by lamps.
Cross connected circuit leakage to screen are discovered also involved circuits indicated. circuits indicated.

Continuity tests are carried out with low voltage, insulation tests 500 v. A.C.I.T. stops automatically after discovering any fault or when the test is finished.

the test is minsted.

Brass type Plessy Mk. IV sockets and flags are used, also an aluminium version Mk. IV is available if required.

A.C.I.T. is built for 25, 50 or to order for more circuits.

Fully descriptive leaflet on request.

P.C.A. RADIO BEAVOR NEAL, HAMMERSMITH, LONDON, W.6. Riverside 8006

RADIO CLEARANCE LTD.-

TRADE **ENOUIRIES** INVITED

27 TOTTENHAM COURT RD., LONDON, W.I. The oldest Component Specialists in the Trade

Telephone: **MUSEUM 9188** EST. 30 YRS.

The Management would like to wish all our customers throughout the world a Very Happy Christmas and Good Health and Prosperity in 1961.

Give a present that will really be appreciated

THE MIRACLE SUPER SIX PLUS 2 TRANSISTOR KIT—THE GREATEST OF THEM ALL

ANY PART SOLD SEPARATELY

Makes up to a portable transistor superhet embodying all the latest design developments including a self-oscillating mixer, two double-tuned IF stages, audio amplifier and a matched push-pull output stage. Also two germanium diodes are incorporated, additional to the six Mazda transistors, one as detector and the other to assist the AGC as a variable damping element.

12 Good Reasons why the Miracle has no equal

- * Printed Board engraved with component locations
- * Special provision for use as a CAR RADIO
- * Double-tuned IF Transformers
- ★ 6 First Grade Mazda transistors plus 2 Mazda hi-efficiency diodes
- ★ Hi-flux 5in. (12000 lines) 25-ohm loudspeaker
- * Full coverage Medium and Long wavebands

- * 3½in. tuning dial with 5 : I slow motion
- Long life dry battery. 150/200 hours
- * Internal high-Q Ferrite Aerial
- * Push-Pull matched output stage 400-milli-watts
- \bigstar 3½in. x 7½in. x 10in. attractive two-tone case - total weight approx. 4 lb.
- * Comprehensive Manual supplied -so easy to build

Our inclusive price for all components, cabinet and battery complete in every detail:

plus 3/6, Regd. p.p.

or any associated component parts supplied separately at the published prices.

INSTRUCTION MANUAL AND CIRCUIT BOOK containing itemised list of all component prices, 3/6 post free. See and hear a complete working model in the shop.

ACCLAIMED BY OVER 10,000 PEOPLE THE FINEST TRANSISTOR KIT OBTAINABLE

MOULDED TROPICAL PAPER CONDENSERS

Small, non-inductive, insulated, high-grade Capacitors. 150 v. Wkg., 15 Mtd. 5% 10d. 22 Mtd. 10% 9d. 2 Mtd. 10% 1/10. 250 v. Wkg., 068 Mtd. 9d. 1 Mtd. 1/1. 22 Mtd. 2% 1/4. 1 Mtd. 10%, 1/7. 500 v. Wkg., 680 pF., 1,000 pF., 1,500 pF., 2,200 pF., 7d. cach. 3,300 pF., 9d. 5,000 pF., 1,500 pF., 2,200 pF., 7d. cach. 3,300 pF., 1/2. 092 Mtd. 30 Mtd. 10d. each. .047 Mtd. 2%, .05 Mtd. 1/d. cach. .1 Mtd. 11d. .25 Mtd. 1/7. 5 Mtd. 1/3. 750 v. Wkg., 470 pF., 10%, 820 pF., 1,500 pF., 2,000 pF. 8d. each. 5,000 pF., 6,800 pF., 9d. dach. .022 Mtd. 1,0d. 1,000 v. Wkg., 1,500 pF., 9d. 6,800 pF., 10d. .01 Mtd., 1,500 v. 1/-. .12 Mtd., 15 Mtd. 1/1 each.

VALVE HOLDERS

4 pin UX, 7d. 7 pin Brit. Pax. 3d. 7 pin Brit. Porc 4d. Int. Octal Pax. 3d. Internat. Octal McMurdo 6d. Mazda Octal Pax. 3d. Loctals Amp. 6d. B7G Pax. 6d. B7G P.T.F.E. 8d. B7G Cr. with saddle and valve retaining spring 1/-. B8A Pax. 4d. B8A Amp. 6d. B8A Cr. 8d. B9A Pax. 6d. B8A Cr. 7d. B9A Pax. 6d. B9A Cr. 8d. B9A Cr

VARIABLE GANG CONDENSERS

Twin Gang .0005 MFD. 23in. x 2in. x 13in. Spindle 16 in.

4/-.

4/-.

4/-.

1/-.

4/-.

1/-.

4/-.

4/-.

4/-.

4/-.

DISC CERAMIC CONDENSERS 500 v. Wkg.

8.2 pF., 470 pF., 500 pF., .001 Mfd., .002 Mfd., .0025 Mfd., .003 Mfd., .005 Mfd. 6d. each. .01 Mfd. 9d.

TRANSISTOR COMPONENTS

SUB MINIATURE ELECTROLYTIC CONDENSERS SUB MINIATURE ELECTRODATIC CONDUCTION. Most with sleeves, all at 2/3 cach.

1. mld. 50 v., 25 mld. 15 v., 5 mld. 50 v., 1 mld., 10 v. 25 v., 2 mld., 6 v. 15 v. 70 v., 4 mld., 12 v. 6 mld.

25 v., 6 mld. 3 v. 6 v., 8 mld. 3 v. 6 v. 15 v. 30 v., 10 mld.

6 v. 25 v., 14 mld. 3 v. 6 v. 80 v., 20 mld. 15 v., 25 mld.

12 v., 30 mld. 3 v. 6 v. 12 v., 50 mld. 6 v.

SUB MINIATURE TRANSISTOR COILS Set of 3 I.F. Transformers 470 Kc/s plus Oscillator

coli,
As specified for Mazda Circuits 23/6 complete.
As specified for Mullard Circuits 23/6 complete.
WTC oscillator Colis for Jackson or Plessey Gang 4/6
each. WTC 470 kc/s. I.F. Transformers 4/- each, 7/6 pair.

SUB MINIATURE CARBON POTS 5K., 50K., 220K., 330K., 1M, 2/-. 5 M with switch. 4/6. 5 K., 1/6, 500K preset 1/-. 1M Transistor Pots 2/-, 5K Transistor Pots 1/6.

FULLY MOULDED TRACK POTS (Dlameter lin. SHORT SPINDLES) 2/6 each. 100 \(\Omega_2 \text{50} \text{10} \) 400 \(\Omega_1 \text{50} \text{10} \) 600 \(\Omega_1 \text{10} \text{

SUB MINIATURE METALLISED PAPER CON-DENSERS in. x in. 100 v. working. .005 MFD., .0022 MFD., .002 MFD., .001 MFD., 8d. each. .02 MFD., .04 MFD. Price 9d. each.

MIN. POLYSTYRENE CONDENSERS 10 pF., 50 pF., 59 pF., 75 pF., 82 pF., 100 pF., 125 v. wkg., 6d. each. 300 pF., 350 pF., 390 pF., 470 pF., 560 pF., 1,000 pF., 1,200 pF., 4,000 pF., 9d. each.

TV PRESET CONTROLS

Knurled knob and 6Ba fixing holes. Diam. lin. 100 D 5K., 10K., 25K., 50K., 100K., 200K, 250K., 500K., 1.5M., 2M., 1/3 cach. 25K. wirewound, 1/6.

Size 1½ ip. dia. 2in. spindles. Price 2/11 each.
1 pole 10 way. 1 pole 12 way. 2 pole 2 way. 2 pole 3 way.
2 pole 4 way. 2 pole 5 way. 2 pole 6 way. 3 pole 3 way.
3 pole 4 way. 4 pole 3 way.

Moulded Tracks. Diam. 14in., 24 in., spindles, 5K., 10K., 25K. Linear, only. 56K., 106K., 256K., 506K., 1M. 2M, Log or Linear, less switch, 2/6 each. With switch 4/6.

TRANSFORMERS

Audio Output Types. 50000 3/9. to 3Ω 3/6. $30,000\Omega$ 4/6. to 3Ω 3/8. $30,000\Omega$ 4/6. to 3Ω 3/8. Universal CRT Boosters with tapped primares 2 v. 6.3 v. 13 v. 25% boost all taps. 10/6. Flument transformers, centre tapped, 6.3 v. output, 1.5 amps., 5/9; 3 amps. 9/6. Charging Transformers. Tapped all voltages 2 amps., 14/3, 4 amp. 16/6.

MODERN TV COMPONENTS'
Ferox Line 0/F Transformers, 16 kV. U25 10/6. (90° Types 12/6). Frame 0/F transformers to match 4/6. Scanning Coils to match 10/6. 90° types 12/6. Fanel containing 6 preset pote 5/-. Smoothing Chokes: 2 Hy. 220 mA. 3/11. 19. Hy. 220 mA. 2/16. 13. Hy. 220 mA. 2/6. G.E.C. Metal Rectifier 250 v. 250 mA. 10/-. 34 Meg. I.F.T. 1/6 ea. 38 Meg. I.F.T. (1lnk) 2/- ea. Masks 14in., 17in. and 21in. 2/6, 3/6, 4/6 (plus 2/6 p.p.).

MISCELLANEOUS
Crocodile clips 4d. Coax. Plugs and Sockets 2/2 per pair.
Condenser clips lin., lin., lin. and lin. 6d. ca. Parmeko
Smoothing Choke 8/9 Hy. 100 mA. 6/6, 500 pF. 15 Ky.
moulded Condensers 2/6, WX28 Westector 6d. Transistor
Twin gang condensers 387 +166 pF., ex equip., 4/6. Vibrator Hash Chokes 1/Ext. Loudspeaker panel with

We have an extensive range of Waxed Paper Condensers (average price 5d. each). Metallised Paper Condensers (average price 11d. each) and Wirewound resistors 5/6/7-watt types (average price 1/- each).

All Electrolytic Condensers as advertised in May issue still available.

STAMPED AND ADDRESSED ENVELOPE with any enquiry please

PLEASE ALLOW FULL POSTAGE AND PACKING CHARGES

TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. ON ORDERS OVER 10/-

BENTLEY ACOUSTIC CORPORATION LIMITED The Valve Specialists

38 CHALCOT ROAD, LONDON, N.W.1

Nearest Underground: Chalk Farm Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED.
TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.

0.22 17/6 68.86 7/6 08070 8/- 120/07 5/- 85.2 15/- DM70 7/5 EFP 22/3 02/2 0/- 12/3 26/6 UV2N 18/7 18/8 18/9 6 10/08 15/- 18/8 18/9 6 10/08 15/- 18/8 18/9 6 10/08 15/- 18/9 18/9 18/9 18/9 18/9 18/9 18/9 18/9		TELEPHO	ME AND	ELEGRAM	OKDEKS F	OK CHOL	Old DEFL	LIKI SEITT	IOE MOOL!		, 0.00	
0 22 17/9 6 888 6 6/- 6 6 10 24 71 12/9 128 128 7 8/6 1008 1 15/8 6 128 7 8/6 1008 1 15/8 6 128 7 8/6 1 158	0.49 17/8	6BA6 716	69070T 9/-	1207GT 5/-	85 A 2 15/	DM70 7/6	EF9 .23/3	GZ30 9/-		U50 6/6		Transistors
1.2 1.2								GZ3210/-				and Diodes
ABC 1.0							EF36 4/-	GZ33 19/11			UY41 7/6	GD3 4 5 6
1. 1. 1. 1. 1. 1. 1. 1.			8V8G 7/-				EF37A 8/-	GZ34 14/-				
105. 9 68RY 15 68GV 6 6 19AQ5 10 6 80V 6 6 19AQ5 10 6 19AQ5 10 8 6 19AQ5 10 8 6 19AQ5 10 8 6 19AQ5 10	3A70T 10/							HABC80	PL83 9/-			
106 176 6BW 8 66 6/3015 196 197 798 EB84 2/6 EP41 9/- HL2 7/6 PL820 18/7 U281 19/11 VP43 23/3 OA73 4/- 185 GT 10/6 6BW 6/7 6/- TB8 .21/3 1981 10/- 156 GS293/3 6031 12/6 EB91 4/- EF50(A)-77- 185 GSG 6/- TB7 8/6 2DD1 15/3 AGPEN7/6 EBC33 5/- EF50(B)- TB7 8/6 EP41 10/- TB7 8/- EF50(A)-77- 1NS GT 10/6 6BW 8 6/- TB7 8/6 2DD1 15/3 AGPEN7/6 EBC33 5/- EF50(B)- TB7 8/- EF50(A)-77- 1NS GT 10/6 6BW 8 6/- TB7 8/- EF50(B)- T								13/6		U25114/-		
186								HL2 7/6	PL820 18/7	U281 19/11		OA73 4/-
1114 3/6 6BX	300 8/-								PM24M 21/3	U282 22/7	VP23 6/6	
111.06								HVR2A 6/-	PX410/6	U301 23/3	VP41 6/-	OA81 4/-
11.05									PY31 16/7	U329 34/-	VB105 8/-	OA86 6/-
11 12 13 14 15 15 16 16 16 16 16 16											VB150 7/6	OA91 5/-
National National			700 01						PY80 7/6	U404 8/6	VT501 5/-	
Section Color Co									PY81 8/6		VT61A 5/-	OA210 25/-
184 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 16/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 16/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 9/- 185 12/8 187 12/8 185 12/8 12/8 185 12/									PY82 7/-		VU39 8/-	OA211 40/-
Secondary Seco					BLA3 7/8		EF86 . 10/6		PY83 8/6	UABC80 9/-	W76 5/6	OC16 ·54/-
18						ERF89 9/8			PZ30 19/11	UAF42 9/6	W77 4/6	OC1954/-
101	JISO 0/-									UB41 12/-	W81M 6/-	OC26 44/-
10									QP25 14/6		X3126/6	OC2825/-
3A4 8 - 6F33 10/6 1005 28/6 2525 9/6 VY1 .18/7 EC54 8 - EK32 8 6 KTW68 9/6					CV63 10/6				QB150/15	UBC81 11/4	X4115/-	OC35 48/-
3A4											X6112/6	OC44 26/-
28.6 1.0 6 66.8 6.8 6.8 10.9 1.1 6 278U 19/11 D1 3/- 28.7 11.9 64637 3/- 101.D1 3/- 28.7 11.9 64637 3/- 101.D1 3/- 28.7 11.9 64637 3/- 101.D1 3/- 29.8 1.7 1.7 10.5 1.0 6 1.2 1.3 1.7 3 29.4 7/8 6.7 6.7 1.8 1.7 1.3 1.7 3 29.4 7/8 6.7 6.7 1.8 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.7 1.3 1.3 1.3 1.3 1.3 1.3 1.3 1.3 1.3 1.3					CV31 18/7				R13 9/-	UBF89 9/6	X63 9/-	OC45 23/-
\$\frac{3}{2}\$\frac{1}{2}\$\frac										UBL21 23/3	X6512/6	OC65 22/6
301 . 3/6 . 6/6 .						RCC281 15/-		1.63 6/-	B19 19/11			OC6625/-
3QG T 9/6 6176 6 676 6 676 6 15/11 3095 6 9/7 0 6 12/10 6 15/1 5							EL38 26/6	MU14 8/-				OC70 14/-
30 30 30 30 30 30 30 30									BP41 3/6	UCF80 18/7	X7821/3	OC7114/-
\$84. 7/- 6K6OT \$/- 10P14 19/3 \$011. 8/- DAP96 8/6 KCX5 8/6 E181 12/6 N108 19/11 8U2526/6 UCR42 9/6 XD(1.5) 6/6 OC73 .29/- \$184. 7/- 6K7G 5/- 12.46 5/- 30P12 7/6 DD41 13/11 ECX40 23/3 E184 7/6 N308 29/7 T41 .23/3 UCR81 9/6 XPG1 18/- \$184. 6/- 30P12 7/6 N308 29/7 T41 .23/3 UCR81 9/6 XPG1 18/- \$184. 6/- 30P12 7/6 N308 29/7 T41 .23/3 UCR81 9/6 WCR5 18/6 DC75 .15/- \$184. 6/- 30P12 7/6 E185 18/11 EXX40 19/6 DF66 15/- ECX8 6/- E185 13/11 N339 15/- TDD4 12/6 UCL82 11/6 XPY12 9/6 OC75 .15/- \$184. 6/- 518. 519/11 12.40 11/3 35.45 21/3 DP91 .3/6 ECX82 6/- E185 13/11 N339 15/- TDD4 12/6 UCL82 11/6 WCL83 19/3 WF34 17/6 OC77 .21/- \$184. 6/- 518. 519/11 12.40 11/3 518. 518/- DP96 8/6 ECX82 6/- E185 13/11 N339 15/- TDD4 12/6 UCL83 19/3 WF34 17/6 OC77 .21/- \$184. 6/- 518. 519/11 12.40 11/3 518. 518/- DP96 8/6 ECX82 6/- E185 13/11 N339 15/- TDD4 12/6 UCL83 19/3 WF34 17/6 OC77 .21/- \$184. 518. 518. 518. 518/- DP96 8/6 ECX82 6/- E185 13/11 N339 15/- TDD4 12/6 UCL83 19/3 WF34 17/6 OC77 .21/- \$184. 518. 518. 518. 518. 518. 518. 518. 518								N78 19/11				007217/-
SY4 7/6 6K72 5/- 12.46 5/- 30P12 7/6 DIA1 13/11 ECOAS 2/3 ELSA 7/6 N308 20/7 T41 23/3 UCR81 9/6 KPG1 18/- OC75 15/-		SERCIT OI						N108 19/11				OC73 20/-
\$\frac{\text{Stag}}{\text{0}} \text{0}								N308 20/7	T41 23/3	UCH81 9/6	XFG1 18/-	OC7515/-
5 5 5 6 6 6 6 7 6									TDD4 12/6	UCL82 11/6		OC7615/-
FY4G 10/- 611 25/8 12.465 13/11 25.16GT 9/8 DP98 8/8 ECCS3 7/6 E195 10/8 13/11 TP5515/- UF41 9/- XH(1.0) 6/8 OC78 17/- 673GT 8/6 6146 3 - 12.481 12.6 35.874 7/8 DP97 9/- ECCS3 49/- EM34 9/6 PCCS4 8/- EM34 9/6 PCCS4 8/- EM34 9/6 PCCS4 8/- EM34 9/6 PCCS5 9/8 UF18 13/3 UF24 12.6 UF58 17/- OC78 DT7/- 6A96 9/- 6119 23/3 12.406 23/3 3525GT 9/- DH77 7/- ECFS9 10/6 EM81 9/- PCCS8 11/- UF58 1/- 266 17/- OC78 DT7/- 6A97 4/- 6LD015/11 12.407 6/6 4310/- DH40 21/3 EFFS9 10/6 EM84 10/6 PCFS0 10/6 PCFS0 10/6 EM91 9/- PCCS8 11/6 UF58 17/11 Z774/6 OC200 54/- 6A03 8/- 6P25 12/6 12.877 7/6 S0C00-06G BP2 9/- ECHS3 6/6 EV78 19/- PCFS 10/6 UF2 8/- UF38 17/- UF38 18/- UF38								PABC80	TP22 15/-	UCL83 19/3	XFY34 17/6	OC7721/-
6Y3GT 6/6 61AG 8/- 12AH8 12/6 35W4 7/6 DF97 9/- ECC38 8/- PC62 1.76 1.786F 13/3 UF42 12/6 763 .7/6 OC78D 17/- 52.3 .12/6 61.77 6 0.18 13/- 2.24T6 7/6 3.52 10/6 0.08 18/- ECC38 8/6 EM91 2.37 10/6 0.08 18/- 6.08 9/- 0.08 18/- 0.08 18/- 0.08 18/- 0.08 18/- 0.08 18/- 0.08 18/- 0.08 18/- 0.02 5.6 0.07 5.6 0.02 5.6 0.02 5.6 0.02 5.6 0.02 5.6 0.02 0.02 5.6 0.02				351.6GT 9/6					TP25 15/-	UF41 . 9/-	XH(1.5) 6/6	OC78 .17/-
23. 1.2/8 6179T 7/6 12AT6 7/6 3523 10/8 DH78 3/6 ECX8 8/6 EM71 23/3 PCC85 9/6 U12/14 8/6 UF86 10/6 Z637/6 OC81 8/6 EX74 9/6 0.5								PCC84 8/-	TY86F 13/3	UF42 12/6	¥63 7/6	OC78D 17/-
SZ4G 9 SL18 13 12AT7 6 SZZ4GT 8								PCC85 9/6	U12/14 8/6	UF80 10/6	Z63 7/6	OC81 18/-
6A07 9/- 6L10 23/3 12AUG 23/3 3525GT 9/- DH77 7/- ECF80 10/6 EM81 9/- PCC89 11/6 U18/20 8/8 UF88 17/11 Z77 .4/6 OC200 54/- 6A07 4/- 6LD0215/11 12AU7 6/6 4310/- DK90 16/2 ECF82 10/6 BM94 10/6 PCF80 8/- U19 38/- UF98 9/- 6A08 8/6 6N7 8/- 12AV6 12/8 50C3 .10/- DK91 6/6 ECF21 23/3 EN31 87/- PCF82 10/6 U22 .8/- U141 9/- SPECIAL 6AUS 3/- 6P25 12/6 12AX7 7/6 50CDGG 6AUS 3/- 6P25 12/6 12AX7 7/6 50CDGG 6AUS 3/- 6P25 26/6 12BA6 8/- 6AUS 4/- 6P28 28/6 12BA6 8/- 6AUS 4/- 6P28 28/6 12BA6 8/- 6AUS 5/- 6P25 10/- 12BF7 21/3 53KU 19/11 DL58 15/- 6AUS 5/- 68XG 7/6 6E7G 10/- 12BF7 21/3 53KU 19/11 DL58 15/- 6AUS 10/- 68XG 7/6 6E7G 8/- CF77 6/6 CF77 8/- CF77 6/6 CF77 8/- CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 CF77 6/6 12KS 17/11 786/6 DL94 7/6 ECL83 19/3 FC4 15/- PENS 19/6 UN9 17/6 UN9 18/6				35Z4GT 6/-	DH78 5/-			PCC88 18/-				
6AC7 4/- 6LD20 15/11 2AU7 6/6 43 10/- DK40 21/3 ECF82 10/6 RM84 10/6 PCF80 8/- U19 36/- UF99 9/- 6AC6 5/6 6N7 . 8/- 12AV6 12/8 50C5 .10/- DK91 6/6 ECF21 23/3 ECF82 10/6 RM84 10/6 PCF80 8/- U19 36/- UF99 9/- 6AC6 8/- U19 36/- U14 9/- SPECIAL OCF71 25/3 ECF82 12/6 ECF21 23/3 ECF82 12/6 ECF31 23/- PCF82 10/6 U24 29/10 U144 28/6 OFFER! XA101 23/- CAL5 4/- 6P28 26/6 12BA6 8/- 050L6GT 9/6 DK92 9/- ECH35 6/6 EY81 9/- PCF86 15/- U24 29/10 U144 28/6 OFFER! XA101 23/- CAL5 4/- 6P28 26/6 12BA6 8/- 050L6GT 9/6 DL66 17/6 ECH81 9/- PCL83 10/6 U24 10/- U144 28/6 S PCC84 XA103 16/- CAC6 7/- 68AC6 10/- 12BH7 21/3 53KU 19/11 DL68 15/- ECH81 9/- PCL83 10/6 U24 10/- U144 8/6 S PCC84 XA103 16/- CAC6 7/- 68AC6 78/6 18/- CAC6 7/- 68AC6 78/6 18/2 68L7GT 9/6 72 4/6 DL92 7/- CAC6 10/- ECH81 9/- PEX25 4/6 U33 .29/6 UM80 15/3 EF80 XB102 10/- 6AU6 10/- 6SC7 .7/6 12K5 17/11 78 .6/6 DL94 7/6 ECL83 10/6 ECR3 10/- PEX25 4/6 U33 .29/6 UM80 15/3 EF80 XB102 14/- 6AU6 14/8 68NTGT 5/6 12KGT 14/- S .15/- DL81 10/6 ECL83 19/3 FC4 .15/- PEN35 19/3 U45 .9/- UU9 .7/6 post free. XC101 18/-								PCC89 11/6	U18/20 8/6	UF86 17/11	Z77 4/6	OC200 54/-
6AUS 5/6 6N7 5/- 12AV6 12/8 50C3 -10/- DK91 6/6 ECH21 23/3 EN31 87/- PCP82 10/6 U22 .8/- U141 9/- SPECIAL OCT 125/- 6AUS 4/- 6P25 26/6 12NA6 8/- 3/6 DE96 8/6 BE96 8/		6LD20 15/11							U19 36/-			OC203 58/-
6AK5 8/- 6P25 12/6 12/4X7 7/6 50CD65 DK92 9/- ECH35 6/6 EY51 9/- PCP66 15/- U24 29/10 U144 26/6 OFFER! XA101 23/- 6AL5 4/- 6P28 28/6 12BA6 8/- 36/6 DK96 8/6 ECH42 9/- EY35 18/7 PCL93 10/- U25 17/11 U146 14/6 3 PCL93 XA102 23/- 6AN6 4/6 8Q7G 6/6 12BE6 9/- 50L6GT 9/6 DL96 17/6 ECH81 9/- EY58 18/7 PCL93 10/6 U26 .10/- U144 8/6 8 PCC64 XA103 15/- 6AC6 7/6 6BA7G 8/6 127/6T 9/6 72 .4/6 DL92 7/- 13/11 EZ41 7/- PEN25 4/6 U33 .25/6 UM80 15/3 2 EF90 6AU6 10/- 6SC7 .7/6 12K5 17/11 78 .6/6 DL94 7/6 ECL83 10/6 ECR3 17/- PEN45 19/6 U35 .28/6 UR10 9/- All mine 6AU6 10/- 6SC7 .7/6 12K5 17/11 78 .6/6 DL94 7/6 ECL83 10/6 ECR3 17/- PEN45 19/6 U35 .28/6 UR10 9/- All mine 6AU6 12/8 6BL7GT 6/6 12K7GT 5/6 80 .9/- DL94 8/6 ECL83 10/6 ECR3 17/- PEN45 19/6 U35 .28/6 UR10 9/- All mine 7AU6 14/6 6SW7GT 5/6 12K7GT 5/6 80 .9/- DL94 8/6 ECL83 10/6 ECL83 10/3 FC4 .15/- PEN45 19/3 U45 .9/- UU9 .7/6 post free. XC101 18/-								PCF82 10/6	T22 8/-	UL41 9/-		
6A15 4/- 6P98 26/6 12BA6 8/- 36/6 DE96 8/6 8CH29 9/- EY85 16/7 PCL83 10/- U25 17/11 U146 14/6 3 PCL83 XA102 26/- 6A16 4/6 8Q76 6/6 12BE6 9/- 50L5GT 9/6 DL65 17/6 ECH81 9/- PCL83 10/- U26 17/11 U146 14/6 3 PCL83 XA102 26/- 6A16 16/6 EYR 10/- 12BH7 21/3 53KU 19/11 DL68 15/- 6A16 10/- 6876 10/- 12BH7 21/3 53KU 19/11 DL68 15/- 6A16 10/- 6880 16/3 26/6 U86 16/3 2 EF80 18/- 6A16 10/- 6880 16/3 2 EF80 18/- 6A17 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 16/3 2 EF80 18/- 6A18 10/- 6880 18/- 6A18 10			194 Y 7 7/8					PCF86 15/-		UL44 26/6	OFFER!	XA101 23/-
6AN6 4/6 807G 6/8 12BE6 9/- 50L6GT 9/6 DL68 17/6 ECH81 9/- EY86 9/- PCL83 10/8 U26 .10/- UL84 8/8 3 PCC84 XA103 15/- 6AU5 7/6 6BTG 10/- 18BH7 21/3 53KU 19/11 DL83 15/- 6AT6 7/- 68AT6T8/6 1277GT 9/8 724/8 DL92 7/- 6AU6 10/- 68S7 .7/6 12K5 17/11 786/6 DL94 7/6 ECH83 18/- 6AU6 10/- 68S7 .7/6 12K5 17/11 786/6 DL94 7/6 ECH83 18/- 6AU6 10/- 68S7 .7/6 12K5 17/11 786/6 DL94 7/6 ECH83 18/- 6AU6 18/8 68L7GT 6/8 18/- 6AU7 18/8 68L7GT 6/8 18/- 6AU7 18/8 68L7GT 6/8 12K5GT 14/- 6BU7 18/- 6BU7 18/- 6BU7 18/- 6BU7 18/- 6AU7 18/- 6BU7 18/- 6BU7 18/- 6AU7 18/- 6												
*** The first state of the first								PCL83 10/6	U2610/-	UL84 8/6		XA103 15/-
6AT6 7/- 68ATGT 8/6 12/7GT 9/6 72 4/8 DL92 7/- 13/11 EZ41 7/- PEN35 4/6 U33 26/6 UM80 15/3 2 EF80 XB102 10/- 6AU6 10/- 68C7 7/6 12K5 T/11 78 6/6 DL94 7/6 ECL89 9/- EZ80 7/- PEN45 19/6 U35 26/6 UR10 9/- All nine 6AV6 12/8 68L7GT 6/6 12K7GT 5/6 00 9/- DL96 8/6 ECL82 10/6 EZ61 7/- PEN46 7/6 U37 26/6 UU8 26/6 Valves £3 XB104 10/- 6B8G 4/6 68N7GT 5/6 12K8GT14/- 83 15/- DL810 10/6 ECL83 19/3 FC4 15/- PL33 18/3 U45 9/- UU9 7/6 post free. XC101 18/-					DL68 15/-			PCL84 12/6				XA104 18/-
6AUS 10/- 6SC7 7/6 12KS 17/11 78 6/6 DL94 7/6 ECL89 9/- EZ/80 7/- PEN45 19/8 U35 26/6 URLO 9/- All mine XB103 14/- 6AVS 12/8 68L7G7 6/6 12K7 G7 5/6 80 9/- DL96 8/6 ECL89 10/6 ECL81 7/- PEN46 7/6 U37 26/6 UUR 26/6 UUR 26/6 URLO 9/- All mine XB103 14/- 6AVS 12/8 68L7G7 6/6 12K7 G7 5/6 80 9/- DL96 8/6 ECL82 10/6 ECL81 1/- PEN46 7/6 U37 26/6 UUR 26/6 Valves 23 XB104 10/- 6BSO 4/6 68N7OT 5/6 12K8OT14/- 83 15/- DL810 10/6 ECL83 19/3 FC4 15/- PL33 19/3 U45 9/- UU9 7/6 post free. XC101 18/-								PEN25 4/6				
6AV6 12/8 68L7GT 6/6 12K7GT 5/6 80 9/- D196 8/6 ECL82 10/6 EZ81 7/- PEN46 7/6 U37 26/6 UU8 26/6 valves £3 XB104 10/- 6B8G 4/6 68N7GT 5/6 12K8GT14/- 83 15/- DL810 10/6 ECL83 19/3 FC4 15/- PL33 19/3 U45 9/- UU9 7/6 post free. XC101 18/-								PEN45 19/6				
6B80 4/6 68N70T 5/6 12K60T14/- 8215/- Dixio 10/6 ECL83 19/3 FC415/- PL3319/3 U45 9/- UU9 7/6 post free. XC101 18/-		BRITOT BIS						PEN46 7/6				
				8315/-				PL33 19/3	U45 9/-	UU9 7/6	post free.	XC101 18/-
	p volunturing								3 A11	N A . 4.11-		4

Terms of business:—Cash with order or C.O.D. only, Post/Packing charges 6d. per item. Orders over £3. post free. C.O.D. 2/6 extrs. Any parcel insured against demarge in transit for 6d. extrs. We are open for personal shoppers. Mon-Fri. 8.30-5.30. Sate. 8.30-1 p.m.

Latest catalogue of over 1,000 different valves, also metal rectifiers, volume controls, electrolytic condensers, transistors, germanium diodes, valve bolders, and Hivac miniature valves, with full terms of business, price 6d.

All valves boxed, fully guaranteed, and new manufacturers' stock or government stores surplus. First-grade goods only, no secones or rejects. Please enquire for any type not listed. S.A.E. please.

EXTENSIVE STOCK MORE BARGAINS FROM OUR POTENTIOMETERS

10 27 40 40 11 21 21 31 31 31 31	ohm, small Colvern w/w 0 ohm, Burco w/w 0 ohm, Burco w/w 0 ohm, Golvern w/w 10 ohm, 4 watt w/w 10 ohm, 4 watt w/w 10 ohm, small Colvern w/w 10 miniature pre-set 10 w/w, for CR. 100 10 K Colvern large precision w/w 10 miniature pre-set 11 American w/w, with switch 12 Burco w/w, instrument 12 + 50 ohm Colvern tandem 13 transistor pre-set 14 K Colvern w/w	1/6 3/6 2/6 1/6 1/6 1/3 2/6 4/6 1/3 2/6 3/- 6d. 1/3	Each	IOK + IOK American, ganged type J IOK + IOK Morganite, ganged, carbon 20K T.V. pre-set 20K Colvern w/w ½ meg. log. with s.p. switch 50K Colvern m/w 75K Colvern precision, new and boxed 200K Instrument, new and boxed 500K miniature pre-set 500K carbon I meg. Iin. with d.p. switch 2M miniature slides 2M miniature Deaf Aid	2/6 2/- 1/6 2/- 1/9 4/6 6/6 1/9 1/6 2/6 6d. 1/3	Each
			SWITCH	HES		
2 p 2 p 2 p 2 p 2 p 2 p 2 p 2 p 2 p 2 p	faxley) . 2w. Type A . 2w. Type B . 4w. . 3w. with on/off switch . 3w. . 3w. P. c/o., intercom. eramic) bank 2p. 3w. bank 2p. 2w.	2/6 1/6 2/9 1/6 1/9 1/9 1/6 2/6	19 10 01 11 12	(Key) Ex. equipment 2 way, new (Micro) Press to make or press to break Sensitive press to make Press to make with reset Press to make roller type B. & L. miniature protective: 0.2A and 0.4A with cut-out on overload	9d. 1/9 2/6 2/6 2/6 2/6 1/6	11
Sr G Br	attery charger Croc. clips larostat mains droppers 250-110V. nall inspection lamps with on/off switch, lead and plug for dashboard PO Jack plugs ulgin Jack plugs eter 500 microamp., 2in. round F. Transformers, 10Mc/s, new	1/- 2/6 2/6 1/9 1/6 12/6 6d.	**	Hand Mic., Canadian No. 3 Morse Keys, Canadian Ringing Generators Mic. Transformers American Jack Sockets 5A. Mains Plugs and Sockets Wheatstone Bridges Ferrite Rod Aerials, medlum wave	3/6 1/- 3/6 1/- 1/- 1/- 27/6 2/-	Each

POSTAGE AND PACKING on all the above-6d, except for Wheatstone Bridges 3/6 each.

limited super

38 MONMOUTH ST., UPPER ST. MARTIN'S LANE, LONDON, W.C.2

DOUBLE BEAM 'SCOPE'



For D.C. & A.C. **APPLICATIONS**

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with inxury instruments. This "SCOPE" will appeal particularly to Service Engineers and Amsteurs. A high gain, extremely stable differential Y-Amplifier (30 mV.C.M.). Provides ample sensitivity with A.C. or D.C. Inputs. Especially suitable for measurement of transistor operating conditions where maintenance of D.C. levels to of paramount importance. Push-Pull X amplifier; Plyback suppression; Internal Tune base Seao Waveform available for external use; pulse/output available for checking T.V. Line 0/P Transformers, etc.; Provision for external X-1/P and BET. Brightness Modulation. A.C. mains 200/250 v 219/1/9 plus P. & P. 7/6 or 50/- deposit, plus P. & P. 7/6 and 12 monthly payments of 33/4.

FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE

ALIGNMENT ANALYSER TYPE MC12

A.C. MAINS, 200/250 volts. Provides:—
"WOBBULATOR" (SWEPT FREQUENCY)
OPERATION, for FM/ITV sligment linear
frequency sweep up to 12 Mc/s. Prom
400 Kc/s—80 Mc/s. CAPACITANCE
MEASUREMENT. Two ranges provided
0-80 pf. and 0-120 pf. SPECIAL FACILITY enables true resonant frequency of any
tuned circuit I.F. transformer, etc., to be
rapidly determined. Cash price 26/12/9/6 and
5/- P. & P. H.P. terms 25/- depost and 5/P. & P. and 6 monthly payments of 21/6.



CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series) LF. 16-19 or 33-38. Also can be modified as an aerial converter (instructions supplied).

omplete with knobs.

32/6 Plus 3/6 P. & P.

HEATER TRANSFORMER

To suit the above, 200-250 v. 6/- Plus 1/6 P. & P.

B.S.R. MONARCH UA8 with FUL-FI HEAD



4-apeed plays 10 records 12in. 10in., or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in and 12in. records of the same speed. Has manual play postsion; colour brown. Dimensions: 12in. x 10in. Space required above baseboard 44in., below baseboard 24in. Fitted with Pul-Fiturnover crystal head. \$8,19i8. Plus 5i-P. & P.

STEREO HEAD 27/19/6 Plus 5/- P. & P.

E.H.T. TRANSFORMER LINE

With built-in line and width control. 14 KV. Scan coll. 90° deflection, on ferrite yokes. Frame O.P. transformer 500 pf. 18 KV. smoothing condenser. Can be used for 14m., 17m. or 21m. tubes.

Complete with circuit diagram.

29'6

4'- P. & P.

As above, but for 625 lines

£2.10 Plus 4/- P. & P.

FOCUS MAGNET suitable for the above (state tube), 10/-, 2/6 P. & P.

MAINS TRANSFORMERS

All with tapped primaries 200-250 volts.

0-180, 180, 200 v., 60 ma., 5.3 v. 2 amps., 10/6, 280-0-280, 80 ma., 6.3 v., 2 amp., 6.3 v., 1 amp., 10/6. 350-0-350, 70 ma., 6.3 v. 1 amp., 6.3 v. 2 amp., 10/6. 250-0-250, 70 ma., 6.3 v., 2 amp., 10/6. Postage and packing on the above 3/*.

SURFACE BARRIER TRANSISTORS

type SB 305, 15 Mc/s. 7/6 each.

100% AUDIO TRANSISTORS

5/- each.

BATTERY RECORD PLAYER AND AMPLIFIER

Incorporating 45 r.p.m. "Starr" motor, "Acos" crystal pick-up, 3 transistor push-pull amplifier complete with transistors. Output 500 milliwatts, 49/6 plus 8/6 P. & P.

SIGNAL GENERATOR



£6/19/6

Covering 100 Kc/s. -100 Mc/s. on fundamentals and 100 Mc/s. to 200 Mc/s. on harmonics. Metal case 10in. x 6½in. x 5½in., grey hammer finish. Incorporating three minature vaives and Metal Rectifier. A.C. Mains 200/250 v. Internai Modulation of 400 c.p.s. to a depth of 30%. Modulated or unmodulated E.F., output continuously variable 100 millivoits C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 22%.

25/- deposit and 6 monthly payments of (6. Post & Packing 5/- extra.

SIGNAL GENERATOR

OT STATE ULTITATION

COVERAGE 120 Ka/s.—23/0 Ka/s., 300 Kc/s.—

900 Ka/s.—20 Mo/s., 275 Mc/s.—56

Mc/s., 28 Mo/s.—28 Mc/s., 16 Mc/s.—56

Mc/s., 24 Mo/s., 84 Mo/s. Mc at lour.

6 jin. x 4 jin. 6 lize of scale 6 jin. x 3 jin. 2

valves and rectifier A.C. malma 20-220 v.

Internal snodulation of 400 c.p.s. to a depth of 30 per cent. modulated or unmodulated R.P.

Output continuously variable, 100 millivoits

C.W. and mod. awitch variable A.P. output and moving coil output meter. Grey hammer finish case and white panel.

Accuracy plus or minus 2%.

\$4/19/6



SIGNAL & PATTERN GENERATOR

£6/19/6

or 25/- deposit. P. & P. 5/- and 6 monthly payments of 21/6.
Coverage 7/6 Mc/s. -210 Mc/s. in five bands, all on fundamentals slow motion tuning audic output. 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ±1% A.C. mains 200-250 v.



CYLDON TURRET TELETUNER

I F 34/38 Mcs. Brand new complete with biscuit for channels 2, 4, 8 & 9

less valves 10/- plus 2/6 P. & P. (Valves required P.C.C., 84 & P.C.F. 80.) Pair of knobs to suit above, 3/6.

3-TRANSISTOR POCKET RADIO

INCORPORATING MINIATURE SPEAKER

Plus GERMANIUM DIODE and PRINTED CIRCUIT

Size $3\frac{1}{4} \times 4 \times \frac{7}{8}$ in.
Incorporating Ferrite Rod Aerial. Two Surface Barrier Transistors and one Audio. Tunable over medium and long waves.

To build 39/6 Plus 1/6 P. & P. yourself SY'S SOLD SEPARATELY. Circuit diagram 1/6, free with kit.



guaranteed 100%



8 WATT PUSH- AMPLIFIER
COMPLETE WITH CRYSTAL MIKE AND
Sin. LOUDSPAKER
A.C. mains 200/200 v. Size 104 in. x 64 in. x
24 in. Incorporating 6 valves. H.F. pen,
2 triodes, 2 output pens., and rectifier.
For use with all makes and types of pick-up and mike. Negative feed-back. Two inputs,
mike and gram. and controls for same.
Separate controls for Bass and Treble lift.
Kesponse flat from 40 cycles to 15 Kc/s.
+2 db.; 4 db. down to 20 Kc/s. Output
8 warts at 5% total distortion. Noise level
40 db down, all bum. Output transformer
tapped for 3 and 15 ohm speech colls. For
use with Std. or L.P. records, muesial
instruments such as Gultars. etc.

£4.19.6 Plus P. & P 7/6.

Or £1 deposit, plus P. & P. 7/6 and 4 monthly payments of 23/-

PORTABLE AMPLIFIER

On printed circuit for A.C. Mains 200/250 v. Size 4in. × 3in. with tone and volume control. Valves: ECL82 and EZ80, 39/6. P. & P. 2/6.

RADIO AND T.V. COMPONENTS (ACTON) LTD. 23A, ACTON HIGH STREET, LONDON, W.3

GOODS NOT DESPATCHED OUTSIDE U.K. ALL ENQUIRIES S.A.E. TERMS OF BUSINESS C.W.O.



36 WINCANTON RD., HAROLD HILL, ROMFORD

MINIATURE ROTARY TRANSFORMER: H.T. 11 watts. 11 volts input, 310 volts 30 m.a. Output: will give approx. 120 volts at 30 m.a. from a 6v. input. 4in. long x 2in. dia. Weight 1½1b. Current consumption under load approx. 2 amps. 17/6 each.

ROTARY TRANSFORMERS TYPE HT.31.



Input: II.5 volt.
Output: 250 volt
at 120 mA. Type
HT.32 Input: 11.5 volt. Output: 490 volt at 65 mA. HT.31. Ex-Units HT.31. Ex-Units but tested, 35/- ea. HT.32. New, in cartons, 20/- ea.

HYSTERESIS MOTORS. By Smith's Aircraft Instruments. Type: HM2/I/D. Drag Cup. 2 volt 400 cycles. 40/- each. New. Type HM/I/4/I. 115 volt 400 cycles. 50/- each. New. Type: HM/I2/I0. 115 volt 400 cycles. 50/- each. New. 8 FOOT WHIP AERIALS. Supplied in 2 sections. No. I and 2. ZA/26800 and 26286. Each section collapsible down to Ift., with retaining wire through each section. Ideal also for Radio Control, fishing rod or pennant mast. 7/6 complete. New.

AMERICAN SEALED RELAYS. Brand new and in maker's original packings. Type A. SIGMA Type 5RJ-761 SPTD. 5,000 ohms. Solder lug connections. Size: $2\frac{1}{4} \times 1\frac{1}{2}$ in. 22/6 each. Type B. HUGHES Pt. No. ME-5002. DPDT. 10,000 ohms. Solder lug connections. Size: $2 \times 1\frac{1}{4} \times 1\frac{1}{2}$ in. 21/-. Type C. R.C.A. MHX-110, 250 ohms. 4 pole DT. $1\frac{1}{4} \times 1$ in. dia. 26.5 v. D.C. 10/6. R.C.A. MHX-84. 300 ohms. 4 pole DT. $1\frac{1}{4} \times 1$ in. dia. 26.5 v. D.C. 10/6 each. COMAR C-519. 400 ohms. 26.5 v. D.C. SPDT. 3 amps. Size: $2 \times 1\frac{1}{2} \times 1\frac{1}{2}$ in. Solder lug connections. 15/6 each.

SENSITIVE RELAY: Miniature type, 250 ohms, D.P.D.T. 12 v. D.C. 2 oz. Overall size I x I½ x Iin. Has adjustable armature tension spring. Will operate on less than I m/a. Suitable for all model radio control. Brand New. 15/6 each.

MINIATURE





CAMERA MOTORS: Fractional horse power. 24 volts. Beautifully con-structed throughout and MOTORS : fully governed. Ratio 2½ to 1. Size 3 x 1½ x 1½ in. Brand new and in new original sealed carrons, ONLY 12/6


8/6 pair

or 5/- each

PLESSEY E.H.T. CONCENTRIC CONNECTORS



OPERATORS or INSPECTION LAMPS

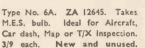

AMPLIFIER FIELD TELEPHONE No. 1. Single stage amplifier designed to extend the working range of Telephone Type "F" & "L." Complete with working instructions, spare valve and canvas carrying case. New. 27/6 each.

DRAYTON COMPACT CAPACITOR START AND RUN MOTOR. Type RQG. Beautifully constructed to stringent Ministry spec. Fully reversible, and made to operate on

ruly reversible, and made to operate on 200/250 v. A.C. 50 cycles, 1.75in.oz. torque at 2,250 r.p.m. Condenser req.: 5 mfd. 350 v. D.C. Size: 2½in. dia., 2½in. wth., ½in. x ½in. spindle. Only 35/-:

TERMS: C.W.O. or 7 days approved accounts. All our goods are guaranteed new or in working order. Money refunded in full if not absolutely satisfied. Orders despatched same day. No postal or packing charges.

(C.O.D 1/9 extra. Carriage extra Ireland and countries outside U.K.)

Tandbeig series 6

Stereo Tape Deck

The Tandberg Series 6 is a "no compromise" instrument capable of delivering consistently fine "professional" quality when used with comparable amplifier and speaker systems.

FEATURES INCLUDE :-

- Free-Standing or Build-in Teak Cabinet
- Flawless Technical Specification
- High and low level mixer inputs & cathode follower outbuts
- Two Recording and Two Playback Amplifiers
- "On and Off the tope" monitoring
- Sound-on-Sound Simultaneous record and playback

RETAIL PRICE 110 gns.

From Specialist Tape Recorder and Hi-Fi Dealers



Tandbera GB

ELSTONE ELECTRONICS LTD . EDWARD STREET . TEMPLAR STREET . LEEDS 2 . Tel: Leeds 3-5111 (7 lines)

Brand new, indi-	°X4 9/-	Z316/-	6F12 4/4	12AX7 71-	629A30-
vidually checked	PY82 8/-	!A5GT 5/-	6HA7 4/3	12C6 7/C	:43
	QP21 6/-	IC5GT 7/6	6H6M 2/-	12H6 2,-	96115/-
VILLULU and guaranteed	QP25 5/3 QQVO 6-40 45/-	ID8GT 6/-	6H6GT 1/1.	12K8GT)/-	666A10/-
AC/DD 2/6 EAC91 4/6 H63 3/6	QS75/20 6/9	IL4 3/9	6J5 3/6 6J7 7/6	12J5GT 3/t	930 8/-
AC/P 4/6 EB34 1/6 HL23 6/-	QS95/10 6/9	ILDS 3/6	6J5G 3/3	125G7 6/6	954 2/-
ACJPI 2/6 EB91 4/3 KBC32 5/- AC5PENDD 4/- EBC33 6/- KF35 5/-	QS108/45 6/9	IR5 6/9	616 4/3	12SH7 4/9	956 2/-
AC5PENDD 4/- EBC33 6/- KF35 5/- AC6/PEN 5/- EBC91 4/6 K12 4/-	QS150/15 6/9 R10 12/6	1S5 6/-	6K6GT 6/6 6K7G 2/3	12517 6/-	957 2/-
AC/SP3 4/6 EC52 3/- KT31 8/-	REL2125/-	1T4 4/- 2A3 8/-	6K7G 2/3 6K7GT 5/3	12SK7 5/-	1619 5/-
AL60 6/- ECC32 4/- KT32 8/-	RK34 2/6	2A5 8/-	6K8G 6/6	12SR7 6/-	1626 416
AR8 5/- ECC816/6 KT33C 7/- ARDD5 2/- ECC826/9 KT44	RL37 3/6	2A6 7/-	6L5G 6/-	15D2 6/-	1629 4/6
ARDD5 2/- ECC82 6/9 KT44 7/- ARP3 3/- ECC83 7/- KT63 6/-	SP2 4/- SP4B 7/6	2C34 2/6 2D4A 4/-	6L6 9/-	15E 8/-	4120 4/-
ARP4 3/6 ECC84 7/9 KT6611/-	SP13C 4/6	2X2 4/-	6L6G 6/6	15R 7/6	7193 1/9
ARP12 2/9 ECC91 4/- KT241 9/-	SP41 2/6	3A4 6/-	6N7G 6/6	35T 30/~	8010AR22/6
ARP21 5/6 ECL80 9/6 KTW62 7/6 ARP24 3/6 EF22 7/3 KTW63 6/6	SP61 2/-	3B24 3/-	6N7GT 7/-	3574 5/-	R013A10-
ARP34 3/6 EF22 7/3 KTW63 6/6 ARP34 4/6 EF32 5/- L30 4/-	SP210 4/- STV280/40 12/-	3E29 (829B) 60/-	6Q7G 6/3 6R7G 7/6	35Z4GT 7/-	9001 6/~
ARTH2 7/- EF36 3/6 LP2 3/6	SU2150A 4/9	305GT 9/-	6R7GT 8/-	53A 3/-	9001 5/-
ATP4 2/9 EF37A 8/- MH4 3/6	T41 7/-	3V4 7/3	6SA7 6/-	58 6/-	9004 4/-
ATP7 5/6 EF39 4/6 ML4 4/- AUI 5/- EF50 2/6 ML6 6/-	TP25 15/-	4A1 4/6 4DI 2/6	6SC7G 5/6 6SC7GT 6/-	59 6/~ 71A 4/6	9006 4/-
AU4 5/- EF52 5/- MPT42 5/3	U17 5/-	5U4G 5/-	6SC7GT 6/- 6SG7 5/-	71A 4/6	Cathode Ray
AW3 4/- EF54 3/6 MS/PEN 6/-	UI8 6/6	5Y3GT 6/9	6SH7 5/-	78 7,-	Tubes:
BL63 6/- EF55 6/- N34 8/- BT45 40/- EF70 4/- NRI5A 3/-	U27 8/-	5Z3 8/6	6SJ7 6/9	80 6/3	3BP125/-
BT45 40/- EF70 4/- NR15A 3/- BT9B 40/- EF80 6/9 NT37	U52 5/- UL84 8/6	5Z4G 8/- 6A6 5/-	6SF5 8/~	82 8/- 83V 12/-	5BP135/- 5CP142/6
D41 3/3 EF85 6/10 (4033A)10/-	UL85 7/-	6AB7 5/-	6SK7 5/6	84 8/-	5FP745/~
D42 4/- EF86 9/- OD3 5/-	UU9 5/6	6AC7 4/3	6SL7GT 6/9	8412/6	VCRX258 (with
D77 4/3 EF89 8/9 P2 4/- DA3012/6 EF9! 4/10 P61 2/6	V2D33B 8/-	6AG5 4/6	6SN7GT 4/6	85A112/~	scanning coil)
DA3012/6 EF91 4/10 P61 2/6 DAF86 8/- EF92 5/- PCC84 8/-	V226 5/- V248A 4/-	6AG7 8/- 6AJ7 4/3	6SQ7 6/6 6SR7 6/6	89 6/- 210LF 3/~	45/-
DET5 15/- EF95 7/6 PCC85 8,-	VMP4G 6/-	6AK6 7/6	6SS7 5/-	210VPT 7 pin 2/6	Photo Tubes:
DET19 2/6 EL32 3/9 PCF80 8/- DET20 2/6 EL35 9/- PFN25 4/6	VP23 3/6	6AK7 8/-	6V6G 5/6	217C17/6	GS1612/6
DET20 2/6 EL35 9/- PEN25 4/6 DF70 9/- EL41 8/3 PEN46 5/6	VR78 4/- VR99 8/-	6AM5 5/-	6V6GT 6/-	446A14/- 705A17/6	Special Valves:
DF72 7/6 EL42 9/- PEN65 6/6	VR105/30 7/6	6AT6 7/-	6X5GT 6/6	715B97/6	2J31 45/-
DF96 8/- EL84 8/3 PEN220A 3/-	VR150/30 7/3	6B8 5/6	6Z4 8/-	717A 8/6	3A/148145/-
DH76 4/9 EL8510/- PENDD/ DK96 8/- EL91 7/6 13609/6	VSI10 4/-	6B8G2/6	723A/B 45/-	801 6/-	31/170/E £35
DK96 8/- EL91 7/6 1360 9/6 DL72 7/6 ESU208 8/- PG7/5 15/-	VT25 8/- VUIII 3/3	6C4 4/- 6C5 6/-	7Q7 7/- 8D2 2/6	80322/6 80530/-	3J192/E £37/10 723AB52/6
DL71 8/- EY51 8/3 PL81 11/-	VUI20 3/-	6C6G 4/6	9D2 3/-	907 AMER 7'-	726A27/6
DL96 8/- EY91 3/6 PL82 8/-	VU133A 3/-	6C8G 5/-	10Y 8/6	807BR 5/-	ACT2540/~
E1232 5/6 EZ40 7/- PL83 9/- E1323 25/- EZ80 7/6 PM4DX 3/-	W21 4 pin 7/- W31 7/-	6E5 5/- 6F5G 5/6	12A6 5/-	8088/-	CV69160/-
E1524 6/6 FW4/500 6/6 PM24A4/-	Y63 5/-	6F6 7/-	12AH7 7/- 12AT7 6/6	813 67 /6 81580/-	KR345/- VX711015/-
EA50 1/6 H30 5/- PT25H 7/6	Y66 8/-	6F8G 6/6	12AU7 6/9	81630/~	WL417A15/-
AND MANY OTHERS	IN STOCK includin	Cathode Ray Tube	es and Special Valve	AS.	

All U.K. orders below 10/- P. & P. 1/-; over 10/- 1/6; orders over £3 P. & P. free. C.O.D. 2/- extra. Overseas Postage extra a* cost.

BRAND NEW ORIGINAL SPARE PARTS FOR AR88 RECEIVERS. Please write your requirements.

MOVING COIL ROUND HAND MICRO-PHONE No. 13. 2½in. diam. with press switch. 12/6. P. & P. 1/-.

DOUBLE BEAM OSCILLO-Fully tested and working, SCOPE 339A.

£15. Carriage 10/-.

HRO MAINS power pack, input 115/250 v. A.C. Output 250 v. 75 mA. and 6.3 v. 3.5 amps. £3, inc. carr.

VARIOMETERS for W/S No. 19. Fully tested and working 12/6. P. & P. 2/6.

TRANSMITTER CABINET with door at back, 77in, high x 29in, wide, Rack fitting type. £17/10/-. Carr. £1.

FERRANTI TRANSFORMER. Oil cooled. 20/19.5 KVA, 3 phase 50 cycles. Pri. 360-380-400-420-440 volts. Sec. 2700-2900-3100-3300-3500 volts. 2.1 amps. Voltage regulation by simple switch. Pri. and sec. Weight 1,150 lb. Price £125. Carr. at cost.

FILAMENT TRANSFORMERS. Primary 0-190-210-230-250 v., 50 c/s. Sec. 1. 2.5 v. CT at 10 amps. 2. 2.5 v. CT at 10 amps. 3. 10.5 v. CT at 11 amps., 4,000 v. insulation. Price £2/19/--. P. & P. 5/-. Primary 0-190-210-230-250 v. 50 c/s. Sec. 1. 10 v. CT at 4.5 amps. 2. 10 v. CT at 4.5 amps. 4,000 v. insulation, £1/16/--. P. & P. 5/-. Primary 230 v. 50/60 c/s. 67 v/amps. Sec. 1. 6.3 v. 1-6 amps. 2. 6.3 v. CT 3 amps., 3. 6.3 v. CT 3 amps., 4. 6.3 v. CT 3 amps., £1/12/--. P. & P. 5/-.

LOW RESISTANCE HEADPHONES. Brand new, balanced armature, DLR, 7/6. P. & P. 1/-.

TELEPHONE HANDSET, Standard G.P.O. type, new, 12/-. P. & P. 1/6.

B.C. 659 TRANSMITTER/RECEIVER, frequency range 27-38.9 mc/s. crystal controlled two preset channels, together with power unit for 6, 12 or 24 v. D.C. good condition, £5/10/-. Carr. 15/-.

NEW PRODUCT OF TAYLOR

Model 127A Pocket size meter. Sensi-tivity 20,000 o.p.v. D.C. 1,000 o.p.v. A.C.

20 ranges. D.C. current 50μA to I amp. D.C. volcs 0,3 v.-1,000 v. (25 kV. by probe).

A.C. volts 10 v.-

3 resistance ranges from 0-20 meg-ohms (self con-tained). Metre

ohms (self contained). Metre 40/1A 3‡in. arc. Accuracy D.C. 3% A.C.4% ohms 5%. Dimensions 5‡ x 3‡ x 1‡in. Weight 14 oz. Price £10 complete with instruction manual. test prods and clips. Leather case £1/12/- extra.

....

OUTPUT TRANSFORMER, in screening can giving 9 different ratios 10:1 up to 120:1 for battery receivers or any high resistance pentodes used as output valves, 6/6. P. & P. 1/6. DRIVER TRANSFORMERS. Primary 500 ohms imp. Sec. to match two 805 in push-pull £1/7/6. P. & P. 5/-.

TRANSFORMERS. Relay supply Primary 230 v. Sec. 0-27/29/31 v. at 0.5 amps., 15/-. 230 v. Se P. & P. 5/-.

P. C. RADIO LTD. 170. GOLDHAWK RD.,

W.12 SHEpherds Bush 4946

ROTARY TRANSFORMERS. 171 watt, 12 v. input. 1,600 v. 110 mA. output, 30/-. P. & P. 7/6.

P. 8. P. 7/6.

COMPLETE SET OF STRONG AERIAL RODS (American). Screw-in type MP45, 50 51, 52, 53, total length 15ft. 10in. top diameter 0.615in., bottom diameter 0.185in., together with matched aerial base. MP37 with ceramic insulator, ideal for car or roof insulation. £2/10/-. Post free.

E2/10/-. Post free. SCR 522 RECEIVERS (BC624), 100–156 Mc/s., including all valves, 25/-. P. & P. 5/-. H.T. CHOKES made by Bendix Radio (U.S.A.) 3 henrys .600A D.C. 25 ohns D.C resistance 18 volts R.M.S. 60 cycle test £1/12/6.

P. & P. 6/-. Ditto 10 henrys 250 Amps. D.C. 90 ohms D.C. resistance 1500 R.M.S. 60 cycle test 16/6. P. & P.

THROAT MICROPHONES T30 U.S.A. 3/6.

THROAT MICROPHONES T30 U.S.A. 3/6. P. & P. 1/6.
VIBRATOR UNIT. 12 v./160 w. 35 mAmps. Exceedingly well filtered and smoothed, excellent for car radios. New, including one 6X5G valve and vibrator. 17/6. P. & P. 5/-.
CARBON INSET MICROPHONE. G.P.O. type 2/6. P. & P. 1/-.
INSULATION TEST METER. Testing voltage adjustable up to 6,000 v. D.C. Mains supply 180/250 v. In wooden case £25. Carr. 10/-.

TCS RECEIVERS made by Collins of U.S.A., In fully guaranteed working condition. 1.5-12 Mc/s. line-up: 1257 (1), 125Q7 (1), 12A6 (2), 125K7 (3), power requirements 12 vol. LT., 225 volts H.T. £11/10/-, carriage 12/6.

SPECIAL BUILT POWER PACK for the above. 230 volt A.C. mains, including 6X5gt valve. £3/10/-. Carriage 5/-.

TRANS-RECEIVER No. 2Z. 2 megocycles to 8 Mc/s Built almost exactly as Number 19. Set much more economical in battery consumption. Complete in fully working condition with power pack for 12 volts, head-gear and microphone, assembly key. £9/19/6. Carriage 15/-TCS RECEIVERS made by Collins of U.S.A.,

PERSONAL CALLERS WELCOME

T.C.C. "OATHODRAY" VISCONAL TYPES. 1 mfd., 2 kV. wkg., 7/6 each. 0.25µF., 4 kV. wkg., 6/* each. 0.05µF., 5 kV. wkg., 7/6 each. 0.1µF., 5 kV. wkg. 6/6 each. 0.05µF., 5 kV. wkg., 6/6 each. 0.1µF., 6 kV. wkg., 7/6 each. 0.5µF., 2 kV. wkg., 6/* each. 0.05µF., 2 kV. wkg., 6/* each. 0.0025µF., 6 kV. wkg., 6/* each. 0.0025µF., 6 kV. wkg., 6/* each. 0.0025µF., 6 kV. wkg., 6/* each. 0.0025µF., 6 kV. wkg., 6/* each. 0.0025µF., 5 each. 0.0025µF., 5 each. 0.0025µF., 2 kV. wkg., 4/* each. 0.0025µF., 2 kV. wkg., 4/* each. 0.0025µF., 2 kV. wkg., 4/* each. 0.003µF., 2 kV. wkg., 4/* e

BLOCK PAPER TYPES. 10 mfd., 1,500 v. wkg. 15/-each, post 3/6. 8 mfd. 1,200 v. wkg. 11/6 each. 8 mfd. 500 v. wkg. 5/-each. 6 mfd. 500 v. wkg. 5/6 each. 4 mfd. 500 and 750 v. wkg. 4/6 each. 4 mfd. 500




POWER UNITS

100-250 v. A.C. input, 24 v. D.C. at 3 amps. or 12 v. twice at 3 amps each winding. Continuous tropical rating switched and fused, etc. In metal case that fits 19in. rack, size 19 × 7 × 7in. Brand new £3/15/-. Carr. 7/6 (with circuit).

SMOOTHING UNIT

for the above power supply.

 2 chokes and 0-1 mA meter (grade 1), metal case, same as the p.u. £2. Carr. 7/6.



(part of R20 6 Rec.), 115-600 kc/s, on three bands, large dial with a Muirhead slow motion drive. Valves EP39. ARTH2, the set can be used with R107. R208 and many other types of receivers. 32/6 each, Carr. 7/6,



GRAHAM GEARED MOTORS

115 v. A.C., 1/6th H.P., variable speed box 0-166. Size of unit 141 x 91 x 8in. £8/10/- Carr. 10/-.

INDICATOR UNIT Type I-152 c (U.S.A.) 3in. tube 3DP1, 1 rectifier 2×2 and $3\times 6\Delta G5$, with controls, etc. In a neat metal box $11\times 6\times 6$ in.. 50/- each. Post 2/6

RCTAX CONVERTORS Type 8A, 24 v. D.C. input, 115 v. A.C. at 1.8 amps. 400 c.p.s. 3-phase. Just the job for the laboratory or experimenting. £6/10/- each. Carr. 7/8 ea.

U.S.A. R-B/APN-4 RECEIVERS, designed for RDF. Valves 1-68N7, 4-68K7 1-VR105, 1-5U4G, 1-68L7, 3-6B4G, 2-879/2, 1-68J7. all GT type. Complete unit with transformers, condensers, etc. As new, first-class condition. Price 65/- each. Packing and carriage 7/6.

MODULATOR UNITS. MD 7/ARC5. 2×1625, 12J5, VR150, Modulation transformer, 5 Relays, etc. 32/6 each. Post 3/6.

MOVING IRON METERS. 0-100 amps. 6in. scale, at £2; 90-180 v., 4in. scale at

AMERICAN LT. TRANSFORMERS. Potted type, finished in black crackle and very conservatively rated. (1) 230 v., input 2×6.3 volts CT, at 3 amps. and 6.3 volts at 3 amps. output, 18/3 each. (2) 230 volt input, 2×6.3 volts at 3 amps. and 6.3 volts CT, at 3 amps. output, 17/8 each. (3) 230 volts input, 2× 6.3 volts at 2 amps. and 2 volts at 1 amp, 12/6 each. (4) 230 volts input. 3× 6.3 volts at 3 amps CT, 1, 6.3 volts 3 amp. 2CF deach. (All these transformers are new and boxed, please include postage 3/6 each.)

1, 6.3 voits 3 amp. 22/6 each. (All these transformers are new and boxed, please include postage 3/6 each.)

GATHODRAY TUBES. CV 1526 (3EG1) 3 inch fil. 4 voits. Anode 1,300 voits, Base same as 139A, U12. 35/r each. Carriage 2/6. CV 1526 (139a). Ideal tube for the small scope, 35/r each. Packing and carriage 2/6. Brand new. Ideal tube for the small scope, 35/r each. Packing and carriage 2/6. Brand new 12 change-over plat. contacts, 8 relays 300 ohms, 2 change-over silver contacts (all relays are small type), 9 x 6 V/6 small GT., 3 x 6 X/6 GT., and 2 6 SNT. Seven small D.C. motors 27 v. 6 selyn motors, 10 small micro switches. Plus gears condensers, ball bearings and pots, etc. This unrepeatable bargain. £10 each.

DOUBLE PARALLAX AN-II-70-9. Smillar to the above but larger, etc., weight 140lb. Brand new, £12/10/r each. Carr. £1.

DEEK TELEPHONES (standard type No. 1) complete with the handset and cord ready to connect to line, £2/15/r each. Post 3/6, or £5 a pair.

DORMEYER GEARED MOTORS. 115 voits A.C. Output 95.8 R.F.M. As new. Price 45/1- each. Transformer to operate this motor 12/6 each. Post 3/6.

MOTOR ASSEMBLY. Servo unit, C-1 11 A G1020. 26 voits D.C. Auto pilot. New means. Price 23/10/- each. Carriage 7/6. C-1 Auto pilot high gyro unit. Price 23/10/- each. Carriage 5/8.

VARIABLE RESISTORS, 3 ohms 10 amps., 18/6 each. Post 3/-.

25FT. AERIAL MASTS. Heavy galvanised steel tubes, four sections, tapered 21 to 1 inch. No guy ropes needed. £12/10/- each. Weight 2 cwt.

TRANSFORMERS (drop thre' type), 110 and 230 volts pri., 275-0-275 at 125 mls., 6.35 v., at 0.9 amps., 6.4 v. at 4 amps. Size 4×4×4½in., 22/6 each. Post 3/-. 6.35 v., at 0.9 amps., 6.4 v. at 4 amps. Size 4×4×4§m., 22/6 each. Post 3/-.
ROTARY CONVERTORS. 24 volts D.C., input 11 amps., 230 volts A.C., output at
80/100 watts D.C., regulated, voltameter 0.300, starter and controls, also fuses on
the front of the panel. Finished in grey, size 24×15×10m. £17/10/- each.
TRANSMITTERS. Type CWS 52244. Model YG.1. Lis v. A.C., 25 watts. Carrier
246 Mc/s. Beacon transmitter, £18/10/- each. (For export only.)

CANADIAN MIKES C3, with lead and plug, 7/6. Post 1/6.

INDICATOR UNIT, with two 5FP7 tubes, etc. 22. Post 3/6.

LIST AVAILABLE SEND 6d. IN STAMPS

PLEASE INCLUDE POSTAGE ON GOODS TERMS C.W.O. All goods offered are ex-W.D. S.A.E. for enquiries.

MILLS

3-B TRULOCK ROAD, TOTTENHAM, N.17

Phone: Tottenham 9213 & 9330

TRANSISTORISED POWER AMPLIFIERS

PORTABLE, MOBILE, MAINS

FOR ALL RADIO, AMPLIFIER & SOUND INSTALLATIONS

ENQUIRIES :-







FULLY R.C.S.C. TYPE APPROVED, 10Ω to $100K\Omega$, our RWV4-K and RWV4-L style resistors conform to Inter-Services Spec. RCS III.

Other styles available. R.C.S.C. type approval pending.

RCSC	cGS	Rating	in watts	Range	
Style	Style	RCSC	Commer- cial		
RWV4-J RWV4-K RWV4-L	VPFI VPF4 VPF10 VPF14	1.5 3 4.5 6	2 4 10 14	$\begin{array}{c} 0.5\Omega \text{ to } 5\text{K}\Omega \\ 0.5\Omega \text{ to } 15\text{K}\Omega \\ 1\Omega \text{ to } 68\text{K}\Omega \\ 1\Omega \text{ to } 100\text{K}\Omega \\ \end{array}$	

THE C.G.S. RESISTANCE CO., LTD. MARSH LANE, GOSPORT STREET, LYMINGTON, HANTS. Tel. Lymington 2811

London Office: 30 Clarendon Rd., Harrow, Middx, Tel, Harrow 4147

BARGAINS

Stock-taking Clearance. All new and unused. Prices post paid. Collaro Tape Motors, clockwise or anti-clockwise rotation. 18/-. 40-40 mFd. 150 volts, size lin. dia. by 2in. long. 1/-.

Contact Cooled Rectifiers, 250 v., 50 mA., 6/-.

R.F. Transistors, White Spot, 4/-.

American Ferrodynamic Recording Tape, 7in. spools, 1,200 feet, boxed, 22/6.

.1mFd., 350 volt, metal tubulars, Sprague or Dubilier, 3/6 doz. Our standard range of instruments are available ex stock. Send for details to:

GRAYSHAW INSTRUMENTS

126 Sandgate High Street, Folkestone, Kent. Tel.: Folkestone 78618.

~HI-FI MAIL ORDER SPECIALISTS~

SPEAKERS AMPLIFIERS TUNERS MOTORS PICK-UPS FREE Carriage, Packing & Insurance (U.K.)
WORLD WIDE EXPORTERS

OVERSEAS ORDERS SENT FREE OF PURCHASE TAX AND SHIPPED PROMPTLY AT MINIMUM COST

Typical Export Examples:
LEAK Stereo 20 amp. with
Varislope Stereo PreAmplifier NEW YORK SYDNEY MELBOURNE £62 14 0 \$176.20 £64 19 6 Two WHARFEDALE W3

£91 17 6 \$258.50 GARRARD 301 motor with £20 5 0 \$56.80

DECCA fiss Stereo P.U. with

£21 1 0 £17 6 0 \$48.60 £17 10

£93 5 0

All the above prices include Carriage, Packing and Insurance !!
C. C. GOODWIN (SALES) LTD.

(Dept.W.13) 7, THE BROADWAY, WOOD GREEN, LONDON, N.22 Gallers Welcomed Tel. BOWes Park 0077/8.

Sect ponics (Fleet ST.)

DEPT. B

152/3 FLEET ST., LONDON, E.C.4

Telephone: FLE 2833

Business hours: Weekdays 9-6. Saturdays 9-1

STOCKISTS FOR THE FOLLOWING

AMPLIFIERS, STEREO AND MONAURAL, BY: VERDIK ARMSTRONG LEAK W.B. DULCI etc.

V.H.F. TUNERS BY:

ARMSTRONG IFAK QUAD

T.S.L. DULCI ROGERS, etc.

HI-FI SPEAKERS BY: GOODMAN PLESSEY WHARFEDALE LORENZ

WR GEC etc.





Following the success of our recent Cossor transistor receiver, we are now introducing

MIGHTY SIX TRANSISTOR PORTABLE NEW RECEIVER.

Build this six transistor superhet battery. Circuit description 6 Mullard transistors, OC44, 2-OC45, I-OC8ID, 2 matched OC8I, I-XI diode, printed circuit, Internal ferrite aerial, 5in. loudspeaker. Assembled dial assembly, medium and long wave coverage, 500 M/W output, attractive blue/cream assembly, medium and long wave coverage, 500 M/W output, attractive blue/cream two tone cabines, size 8½in. x 6½in. x 3in. Weight approx. 3 lb. Detailed point to point and theoretical diagram, including all components for easy construction. Only £9/15/-, plus 3/- post and pkg. E/ready PP7 battery 3/3. Instructions and circuit 1/6 post free. As a complete receiver £14/19/6 plus battery 3/3 Pers and pkg. 4/4 3/3. Post and pkg. 4/-^***********

THE NEW JASON range for CONSTRUCTORS

JTV2 Tuner completely assembled ready for use £25/7/0.

FMTI FM Tuner. In kit form for cabinet mounting. One of the most popular tuners. Up to 60 miles normal range. Less valves £5/19/-. Power pack kit £2/14/9.

FMT2. In kit form with free standing case with power pack. Less valves £8/15/-.

FMT3. Variable tuner 88-108 mc/s. Variable AFC control dual limiters, approx. 80 mile range, less valves £9/19/-.

JTV2 Tuner self powered switched tuner for FM and TV sound. Both BBC and ITA as required, less valves £14/19/-.

MERCURY II switched FM/TV sound tuner in kit form for building into cabinet, less valves, £10/14/-. Power pack kit, £2/14/9.

EVEREST 6 s/het transistor portable, p/pull output, high quality speaker, matched transistors, neatly designed case, aerial input for use in car, complete kit £13/19/9.

EVEREST 7 transistor s/het portable, p/pull output, high quality speaker, extra RF stage, neatly designed cabinet, aerial input for use in car, all components complete £15/18/9. 2/6 post and pkg. on all the above, S.A.E. for details.

Definitely the last of the remaining stocks of the

AVANTIC BEAM-ECHO HI-FI EQUIPMENT

SP2I STEREO PRE-AMP CONTROL UNIT

A twin channel pre-amp control unit, has 6 A twin channel pre-amp control unit, has 6 inputs for each channel INPUT SENSI-TIVITY for 250 M/V or 1.5V output TUNER 100 and 250 M/V. Tape 100 M/V flats 250 M/V. PICK-UP 5 and 50 M/V. Frequency response: 40 c/s. to 15 Kc/s. TAPE OUTPUT 50 M/V. continuously variable bass and treble controls, continuously variable bass and treble controls. loudness control and stereo balance control. Power required 6.3 V. at 1.3 amp. A.C. 350 v. at 5 M/A D.C. Will match any hi-fi amplifler. Manufacturer's price £28/10/—. OUR PRICE now £16/19/6. Carr. and packing 7/6.

AVANTIC PL6-21

High quality monaural power amplifier and Programmer of the monaural power amplifier and pre-amp compactly housed and sultable for shelf mounting or cabinet. Two EL84, three EF86, one ECC83, one EZ81. 30 watts peak; speaker impedance, 4, 8 or 16 ohms. Sensitivity: 4M/V on pickup, 3M/V on tape, 100M/V on tuner. Intermod. distortion 1% at 10W equivalent Sinewave output. Maker's price £28/10/aker's price £28/10/-Post and packing 7/6 Sinewave output. MOUR PRICE 19 gns.

AVANTIC SPAII Stereo Amplifier

A twin channel amplifier and pre-amp., push-pull output, 10W peak each channel, rumble filter speaker impedance 4, 8 and 16 ohms. Tape output: 100M/V. Continuously variable creble and bass, stereo balance control. Input sensitivity: for 7W, 100M/V radio; 100M/V tape; 650M/V pickup. Manufacturer's price 28 gns. OUR PRICE 19 gns. Post and packing 7/6.

STEP II stereo pick up pre-amp. unit £4/14/6. P. & P. 2/6.

STEP 21 stereo tape pre-amp., £4/14/6. P. & P.

A few only, Avantic Hi-Fi speaker cabinets, slight blemish. Dimenslons: height 40½in., width 20½in., depth 14½in., baffle cut to house 1-15in., 2-5in. and 1-7 x 4 speaker, can be used with alternative speakers and porthole at base of cabinet. Nicely finnished and well made. OUR PRICE £9/19/6. Carr. & pkg. 20/-.

THE VERDIK "QUALITY TEN"

10 watt push-pull ultra linear hl-fi amplifier with hi gain pre-amp. Mic., radio, gram and tape inputs, bass and treble controls. Beautifully finished. Control panel in gold lettering on grey green. Fully guaranteed. Original price 23 gns. Our price £14/19/6. P. & P. 7/6.

PORTABLE BATTERY ELIMINATOR MADE BY COSSOR

Housed in two containers which are to replace AD35 and B126 Batteries. 37/6, plus 2/- P. & P. only suitable for use with Dk96 Series valves.

TAPE DECK OFFERS

B.S.R. MONARDECK, uses 5½ tape spools, twin track. Single speed, 3½ 1.P.S. at £8/19/6.

B.S.R. MONARDECK, uses 5½ tape spools, twin track. Single speed, 3½ 1.P.S. at £8/19/6. Post & Pkg. 5/-. Suitable tape amplifier for B.S.R. deck. Completely assembled, 3 watt o/put, valve line up ECC83, ECL82, EL84, metal rectifier, magic eye level indicator, frequency response 60 c/s.—9000 c/s. inputs for radio, gram, mic., superimpose, ideal for monitoring impedance to a control cluster. for monitoring impedance, tone control, volume control. Dimensions Ilin. x 4in. deep x 64in. high. OUR PRICE £9/15/0. P. & P. 3/6.

FOR TAPE RECORDER CONSTRUCTORS

The new Collaro studio tape deck, using 3 motors, 3 speeds at 1½, 3½ and 7½ 1.P.S., will take 7in. spools, push button controls, £12/19/6, 5/- post and pkg. Well designed tape recorder amplifler (not a kit) for the studio deck, incorporating Mic/Gram/Radio inputs, ext. loudspeaker, superimposing .switch, with marching knobs, separately mounted mains transformer. Frequency response 60-10K/c 3DB at 17.5 1.P.S., magic eye level indicator. Using ECG83, ECL82 and EM85 and metal rectifier. Assembly instructions. The 2 units, £25/10/- complete. Crating and insurance, 17/6. Suitable Accs mic. 40 for above, 25/-. A repeat of our previous popular offer. The Collaro Mk. IV tape transcriptor tape deck, £17/10/-, Crating and carr. 11/6. £17/10/-, Crating and carr. 11/6.

The new ARMSTRONG TAPE PRE-AMPLI-FIER PABO-3, high quality unit, can be used with any Hi-Fi equipment, will operate most tape decks, equalisation for tape speeds 32, 74, 151.P.S., can play prerecorded tapes. Valve line up, FF86, ECC82, EM81 and OA81 diode, freq. response, 30-17000 C.P.S., at 15 1.P.S. 40-13000 C.P.S. at 7\frac{1}{2}\text{ 1.P.S. Mic/radio/gram inputs. 20 watts maximum ower required, attractive control panel. Com-lete 16 gns. 3/6 post & pkg. Power pack plete |6 gns

Limited number of this stereo offer



Compact stereo amplifier, 3 watts each channel, using 2-ECL82, using 2-ECL82, I-EZ80, separate balance and tone controls, volume and on/offswitch, channel reverse


for crystal p/up, separate power pack, including 2-6½ P.M. speakers in cabinets, finished imitation Rexine. Complete and ready for use, £8/19/6. Rexine, C P. & P. 10/-

FOR STEREO ENTHUSIASTS

The new Eagle Stereo balancer audio watt meter will balance your stereo speaker system, compensating for variation of acous-tics and unmatched speakers. Ideal for tics and unmatched speakers. Ideal for monitoring audio outputs, suitable as a recording level indicator for your tape recorder, an improved advantage over "magic eyes." The AUDIO WATT METER assists in aligning AM & FM receiver, meter is calibrated for 0.30 watts for both 3 and 15 impedances. Cabinetin grey. 7 Gns. P. & P. 2/6.

DEPENDABLE RADIO

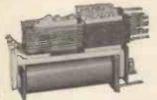12a TOTTENHAM STREET, LONDON, Opp. Heals in Tottenham Court Road.) (2 minutes Goodge Street Street. Phone LANgham 7391/2 Hours of Business 9-6 (Mon. to Fri.) Terms: Cash with order or C.O.D. Callers welcome.



POST OFFICE RELAYS **TYPE 3.000**

BUILT UP TO YOUR REQUIREMENTS

Large Stocks always available

COMPONENT PARTS ALL PLATED

Yokes, 4/- each.
Armatures, 1/3 each.
Adjustable, 1/3 each.
Spindles, 1/9 each.

Top plates, 3d. each, Bottom Plates, 3d. each

Screws. Armature Screws

Fixing Screws (with insulators), 2d. each. Buffer Blocks, each.

		40140500101		
	1100 4	COLITAGE	0011	MALLIEC
BUILD	UPS	CONTACTS	COIL	VALUES

	Silver	Platinum			2	ingle	Iwin
1. C/O	1/3	4/-	Upt	0 100	Ohms	3/-	5/-
2. C/O	2/6	9/-	F1 F1		11	4/-	6/-
3. C/O	3/6	12/-	11 81	, 1,000	19	5/-	7/-
4. C/O	4/6	16/-	12 8		11	6/6	8/6
6. C/O	6/6	24/-		10,000	11	9/-	_
8. C/O,	8/6	32/-	19 1	20,000	11	14/-	_
Other build u		order; all	11 1	40,000	>>	16/-	_
types of relay	s buil	t to your	11 1	, 80,000	21	*0 0	rder
specification.		i .		*Slugged	coils	extra	

SIEMENS HIGH SPEED C/O RELAYS

250+250 ohms Twin Coils 7/6 1,000+1,000 oh 1,700+1,700 ohms Twin Coils 17/6 1/6 Post and Packing on all relays 1.000 + 1.000 ohms Twin Coils 10/6

G.E.C. MINIATURE SEALED RELAYS

No.	Ohms	Build Ups	Voltage	Price
Z530005	2	2 C/O	1.3 v.	12 6
Z530008	670	2 C/O	24 v.	19 6
Z530010	40	2 C/O 2K	7 v.	17 6
Z530014	2	1 C/O	1.3 v.	10 6
Z530015	40	1 C/O	6 v.	12 6
Z530016	180	1 C/O	12 v.	19 6
Z530018	2,500	1 C/O	48 v.	£1 2 6
Z530019	2	2 C/O 2K	1,3 v.	14 6
Z530020	2	4 C/O	1.3 v.	16 6
Z530021	2	2M	1,3 v.	10 6
Z530022	2 2 2	IM IB	1.3 v.	12 6
Z530023	2	2B 2M	1.3 v.	12 6
Z530024	40	2M	6 v.	12 6
Z530025	40	IM IB	6 v.	12 6
Z530026	40	2B 2M	6 v.	15 0
Z530027	180	2M	12 v.	17 6
Z530028	180	IM (B	12 v.	17 6
Z530030	670	2M	24 v.	17 6
Z530031	670	IM IB	24 v.	17 6
Z530034	2,500	IM IB	48 v.	£1 2 6
Z530480	670	2B 2M	24 v.	19 6
Z530430	5,000	2 C/O	48 v.	£1 9 6
Z530429	2,500	2 C/O	48 v.	£1 2 6
				2.0

S.T.C. MINIATURE SEALED RELAY

4184GD	700	2C
4190HC	170	2C
1/6 Post &	Packing on	all relays.

SEND FOR LISTS



ROTARY **TRANSFORMERS**

Delivery ex stock. Quotations on

Input 11.5 v. Output 250

Input 11.5 QUEDUE

AS SUPPLIED TO GOVERNMENT DEPARTMENTS AND LEADING MANUFACTURERS. NEW AND BOXED

ROTARY TRANSFORMERS

Made by DELCO

TYPE 1, 27/6. P. & P. 3/6. TYPE 2, 37/6. P. & P. 3/6. TYPE 1, Dual voltage 12 or Type 1. Dual voltage 12 or Type 2, 120 or A, output; 500 v., 26 mA. output.

Type 2. 12 v., input 275 v. 110 mA. output; 500 v., 50 mA. output.

Both types dual output. Made in U.S.A. OTHER BARGAINS IN ELECTRONIC

LECTRONIC EQUIPMENT AVAILABLE Send for list

HIGHEST QUALITY-NEW LOW PRICES Car & GUARANTEED

MOST MULLARD,		6 Months REVACUUMED	12 Months REGUNNED	12 Months NEW TYPES
EMITRON, EMI-	9/10in.	£2- 0-0	£3-10-0	Mw 31/74
PROCESSED IN	12in.	£2-10-0	£4-10-0	£5-0-0 Mw 36/24
OUR OWN FAC-	14in.	£3- 0-0	£5- 0-0	£6-15-0
New Mullard, Mazda & U.S. A. guns used. NEW 108K39/- Equiv. 3/16)	15/1/in.	£3-10-0	£5-15-0	Mw 43/64 £7-15-0
Equiv. 3/16) 39/-	JZIIn.	£4-10-0	£6-15-0	21-13-0

4-SPEED RECORD PLAYERS 13 CHANNEL TV'S

Latest Turntable, together with light-weight Staar Galaxy dual sapphire crystain turnover pick-up head. Amazing value (Pick-up only 199-). \$3/10/-. Carr. 3'-. B.S.R. Monarch (WAS) \$6.15 COLLARO CONQUEST \$6.19 O. B.S.R. Latest UA14 \$7.19

STEREO OUTFITS Consisting of two 3 valve (10F3, 10P14, UU9) 3-watt mains amplifers each complete with 8in. loudspeaker in neat bakelite cases with independent controls, together with UAS Stereo changer and screened leads. Unrepeatable £11/10/-!

AMPLIFIERS ONLY 49/- EACH. **UAS STEREO CHANGERS**

B.S.R. Monarch Autochangers fitted with quality Stereo Cartridge. Truly amazing value at £6/19/-

TABLE MODELS, FAMOUS MAKES.
Absolutely complete
These sets are unequalled in value due to
huge purchase direct from source. They
are untested and are not guaranteed to
be in working order. QARR. ETC. 15/-.

12" — £3.19 14" — £6.19 17" — £9.19

ALSO 12" 5 CH. TV's 55/-

TRANSISTORS: RED 4/6 48/- doz. WHITE SPOT 6/6, 69/- doz.

PM SPEAKERS Top Makes 6in. 8/- 5in. 11/- 10in. 13/-

I.T.V. CONVERTERS

with power pack. Very compact External /Internal fitting. Band change 39/-switch. Manuf. cartons. Listed £7

VALVES

BY RETURN OF POST GUARANTEED 3 MONTHS 10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozens). Post: 1 valve, 6d.; 2-11, 1/-. FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

NEW LO	OW PRICE	S tee on	goods if return	ed unused wit	bin 14 days.
OZ4 5/-!	6K8G 5/9	20P1 11/6	EB34 1/6	EN31 16/-	T41 7/6
1A7GT 11/9	6K8GT 11/-	20P3 12/6	EB41 7/-	EY51 9/-	U14 8/-
1C5GT 10/6	6K25 7/6	20P4 17/-	EB91 3/9	SMALL 9/-	U18 8/6
1H5GT 9/9	6L1 12/6	20P5 16/-	EBC33 5/-		U22 6/9
1L4 3/9	6L6 9/6	25A6G 8/-		EZ40 6/9	U24 7/8
1N5GT 9/9	6L6G 6/9	25L6G 6/9	EBC81 7/9	EZ41 7/6	U25 13/6
1R5 6/8	6L7 9/-	25L6GT 9/-			U26 10/-
184 8/9	6L18 9/-	25Z4G 8/-		EZ81 7/3	U31 8/3
185 5/9	6L19 11/6	278U 16/-	EBL21 14/-	GT1C 7/-	U33 11/-
174 4/9	6LD29 8/6	30F5 7/-	EBL31 16/-		U35 8/9
2D21 4/6	6P25 9/-	30FL1 9/6	EC52 3/9	GZ34 12/6	U37 26/6
3A4 5/6	6P28 9/-	30P4 12/6		HABC80 9/6	U50 6/-
	6Q7G 6/9				U52 5/8
3Q1 7/3 394 6/6	6Q7GT 9/3	30PLI 10/6	ECC34 9/-		U191 9/6
3V4 6/6	6SA7 5/9	35L6GT 9/-	ECC35 6/9		U281 8/6
	6SG7 4/9				U282 15/-
5R4G 11/-					U301 14/-
5U4G 5/6		50CD6G16/-	ECC82 6/6 ECC83 7/6		
5V4G 9/9 5V3G 6/-	68J7 6/- 68K7 5/3	50L6GT 9/3	ECC84 8/9		U309 12/6 U329 12/6
5Y3GT 6/6	68L7GT 8/8	61SPT 11/-	ECC85 8/3	KT66 12/6	U329 12/6 U339 11/-
	6SN7GT 4/9				
			ECF80 10/3		U403 9/6
5Z4GT 11/- 6A8G 9/6	68Q7 6/3 6887 6/6		ECF82 9/9 ECH21 14/-	KTW61 5/6	
		185BT 16/-		KTW63 4/9	
6AC7 4/3 6AG5 4/3	6U4GT 10/6	807A 5/-			UAF42 9/-
	6V6G 5/6 6V6GT 6/6	807E 3/9	ECH42 8/9	MU14 8/-	
6AG7 8/6		955 3/9	ECH81 8/3		UBC41 8/3
6AK5 6/9	6X4 5 -	956 2/9	ECL80 8/3		UBC81 10/-
6AL5 3/9 6AM6 3/9	6X5G - 5/6	2050 3/6	ECL82 10/- ECL83 14/6		UBF80 8/9
	6X5GT 6/6	9001 4/-		P61 2/3	UBF89 8/6
6AQ5 6/-	7B6 9/8 7B7 7/3	9003 4/-	EF22 12/-	PABC8011/-	UBL21 14/6
6AT6 7/-		ATP4 2/9 AZ31 9/-		PCC84 7/9	UCH21 14/6
6AU6 S/6			EF39 4/3 EF40 13/8	PCC85 9/3	UCH42 8/6
6B8G 3/6		B36 8/6		PCC89 13/9	UCH81 9/-
6BA6 8/-		B65 4/9	EF41 8/9	PCF80 7/8	UCL82 11/3
6BE6 6/-	787 9/6	CBL31 23/3	EF42 7/8	PCF82 9/-	
6GB6G 12/6	7¥4 7/8	CY31 9/9		PCL82 9/3	
6BW6 8/-	10C1 11/-	D63 1/6		PCL83 11/6	UF42 7/9
6BW7 6/9	10C2 13/6	DA90 2/6	EF54 3/3	PCL34 9/9	
604 3/6	10F1 6/9		EF80 5/9	PEN25 4/6	UF85 9/-
6C6 4/3	10F9 10/3			PEN45 7/3	UF86 14/6
6C9 11/6	10P13 9/8				UF89 7/3 UL41 7/6
6CD6G 18/6	10P14 9/6	DF33 9/9			UL41 7/6
6CH6 8/3	12AH8 9/9	DF91 5i-	EF91 3/9	PL36 11/-	UL44 12/6
6D6 4/9	12AT6 7/9	DF96 8/3	EF92 4/9		UL46 9/9
6F1 6/9	12AT7 5/8	DH77 7/-		PL81 9/9	UL84 8/-
6F6G 6/3	12AU7 6/8	DK32 11/9		PL82 7/9	
6F13 6/9	12AX7 7/8	DK91 6/9		PL83 8/-	
6F14 11/6	12J5GT 3/6	DK92 8/6	EL37 11/6	PL84 11/-	
6F15 11/6	12K7GT 6/- 12K8GT12/-	DK96 8/3		PY31 8/3	UYIN 11/-
6H6 2/-	12K8GT12/-	DL33 8/9	EL41 8/6	PY32 11/-	UY41 6/6
6J5G 2/9	1207GT 6/-	DL35 10/6	EL42 9/6	PY80 7/-	UY85 7/-
6J5GT 3/6	128K7 5/6	DL91 8/9	EL84 7/9	PY81 7/-	VR150/305/6
6J6 4/-	12SN7GT 8/6	DL92 6/6	EL91 4/9	PY82 7/-	X65 11/-
6J7G 5/-	1487 14/9	DL94 7/6			X66 11/-
6J7GT 7/9	19BG6G15/-	DL96 8/3		PZ30 11/-	
6K6GT 6/6	20D1 9/6	EA50 9d.	EM81 9/3		
8127G 0/3	20172 8/8	EARCON 7/8	EMS4 0/0	CD41 0:0	Y63 6/3
6K7GT 4/9	201.1 9/8	EAF42 8/6	EM85 10/6	SP61 2/8	266 7/6
	-1-	-1-			

List of 1000 Special Offers 6d. Callers always welcome


350-352 FRATTON ROAD, PORTSMOUTH POST: 2 lbs. 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6. No C.O.D

SOUTH SUPPLIES

(ELECTRICAL LTD.)
95, OLD KENT ROAD, LONDON, S.E.I.
90, HIGH STREET, EDGWARE, MIDDX.
124, JUNCTION ROAD, LONDON, N.I9
72 BOROUGH HIGH STREET, S.E.I.

SECTRIC SMITH'S CLOCKS

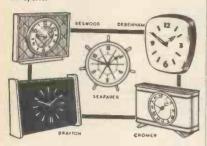all at 25% OFF maker's prices. With full manufacturer's guarantee, 200-250 v.



	List	Our
BESWOOD	105/-	78/6
DRAYTON	95/ - 92/6	71/- 69/6
DEBENHAM	73/- ND	54/6
Plus Postage and Packing	29/6	21/6

AMPLIFIER & SPEAKER in Cabinet

Ex-Rental. Tested and in good working order. Ideal Guitar Amplifier. Complete with valves.

37/6 Plus 3/- post and packing.



R.C.A. AUTO CHANGERS

4 speed, Ronette head. Brand new. A snip for the specialist.

£7.19.6



12-CHANNEL TURRET TUNER

BRAND NEW. Fitted with coils. I to 5 and 8 to 9. 34/38 Mc/s. Complete with P.C.F. 80 and P.C.C. 84 Valves

Manufacturer's price £7,7/-33/- Carriage paid.

LIMITED QUANTITY BRAND NEW BLACK & DECKER

£4-18-6 CARRIAGE



ELECTRIC CLOCK, AUTO COOKER TIMER & TIME SWITCH

BRAND NEW. Modernise and add pounds to the value of your electric cooker. Ideal for automatic cooking, or any heat current control. Complete with handsome electric clock. 200/250 v. 30 Amp. Full fitting instructions. Plus 2/6 P. & P.



OUR £3.17.6

"AS-NU" REGUNNED T.V. TUBES

Supplied from stock, and despatched by British Railways same day COMPLETE NEW GUNS fitted in every tube and fully guaranteed for TWÉLVE MONTHS.

		М		1			A	1.
		. [*]	ulla	ra			Mazo	1a
12in.		€4	10	0		£4	10	0
14in.		£4	15	0		£5	10	0
15in.						£6	0	0
l6in.		£6	10	0			_	
17in.		£5	10	0		£5	17	6
21in.		£8	10	0		£8	10	0
	Plus	10/-	ca	rr.	and	ins.		

Other types available. Please contact:

J. P. WRIGHT

la Shotton Street. Doncaster

Sole Distribution Agent

Phone: DON 2636 or 66252.

Sonic V Portable-TAPE RECORDER



- Manufactured with finest British materials. All frequencies within the range of 40-12,000 c/s.
- Can be used as a straight amplifier having two speakers to which 5.3 watts are de-livered (max. rating 9.5 watts).
- 3-speed recording on four track tape.
- Erase head can be switched off to enable superimposing of recordings, etc.

Price of twin track, complete with crystal microphone, tape, spare spool, telephone adaptor, and lead with jack plugs for recording radio or records.

FOUR TRACK MODEL 50 GNS.

GENERAL SONIC RADIOS

92. Caledonian Road, N.1-Ter. 0322

"RECO" TRANSISTOR KITS

RECO "TRANSONA-3 (3 transistors)

M/L waves, rod aerial. Tuning condenser. Home, and Light Radio Luxembourg too.
Complete kit with
easy-build plans and "Sonotone" minia-ture earpiece. 55/-. With "Min. speaker," 49/6. Post etc. 2/6.



NEW! "RECO" PUSH-PULL SIX.



KIT. (6 transistors and 2 diodes). M/L waves. Sensitivity of a super-het (2 RF stages). Tonal quality of a TRF. Per-formance as Tran-

tty of a TRF. Performance as Transigen-3 but full loud-speaker with full-tone output. Without doubt the finest value in transistor kits today. Competitively priced at £6/19/6, post etc. 2/6. (Case 6½ x 4½ x 1½in. approx.)

"RECO" TRANSIGEN-3 (3 transistors).

M/L waves and T.B.

High-gain ferrite rod



aerial. XA104 (Edis-wan) RF stage. On test (50 miles Lon-don) tuned in Home,

don) tuned in Home, Light, Third, AFN, Radio Luxembourg and many others at good headphone strength. A really fine transistor kit complete with easy-build diagrams, and "Sonotone" min. earpiece 69/6. With super B.A. reproducer (which may be mounted under red speaker grille) 65/- (Case as P.P.6.).

"RECO" PUSH-PULL FOUR (4 tran-

sistors M/L waves with 2 S/W coils free upon request. 3in. HIGH-GRADE speakeraffording fine tonal quality. Ferrite rod erathording line tonal quality. Ferrite rod aerial. Bias sensitivity volume control. Complete kit with easy-build diagrams £4/19/6. Post etc., 2/6. (Case as P.P.5.).



"RECO" PUSH-PULL FIVE (5 transistors). M/L waves and T.B. Indoors or outdoors this brilliant radio brings Home and Continental stations to your finger tips. 3in. Golden-Tone Speaker, 6in. Ferrite Rod Aerial, EDISWAN XCI0I's (350 mw). Push-pull output stage. Gleaming pale blue styrene case with speaker grille in red. Complete kit with easy-build diagrams 25/19/6. Post etc. 2/6. Dorset customer writes:—" Makes fine car radio."

"RECO" SUPER TRANSIGEN-4 (4 transistors) as Transigen-3 but with 3in. speaker. Complete kit £4/19/6. Post etc. 2/6. (XAI04, XBI13, XCI01, XCI01).

"RECO" AMAZON-3 (3 Transistors). Medium waves with 2 S/W coils upon request. Tonal quality above average. Sensitive reflex circuit. Complete kit with super B.A. reproducer and attractive plastic case 55/-, post

All transistors used in our kits are EDI-SWAN FIRST GRADE.

Overseas customers please add 3/6 extra for

Circuits only and parts price list 2/6 for 6.

AFTER SALES SERVICE


RADIO EXCHANGE COMPANY

27 HARPUR STREET, BEDFORD.

Phone 2367. (Opposite Co-op).

Closed Sat. I p.m.

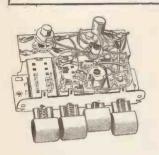TRANSISTORISED MINIATURE R.F., I.F., AUDIO AND F.M. UNITS





THE SMALLEST YET Sub-Miniature M/Coil Loud-speaker, LP45F. O/all dia. 13 x 9,500 gauss ferrite lin. deep. magnet, precision engineered gap.

Max. loading 0.3 watts; min., 1

mW. 25/- (inc. purchase tax).



using the very latest transistors

Using the very latest transistors to provide new standards of sensitivity and low noise level, these units open up exciting new vistas in sub-miniature equipment design. All components are to precision standards and are mounted on printed circuits. All Units are pre-aligned, factory checked and guaranteed.

Obtainable from all stockists of good equipment.

3 WAVEBAND CONVERTER TA-12401

With OC170 transistor in emitter injected autodyne converter circuit. S.W. 5.9-13 Mc/s; M.W., 510-1,620 kc/s; L.W., 150-275 kc/s. Wavechange and on-off by four push-buttons. Overall size 3.4 x 2.1 x 1.8in. 67/6 plus 22/9 burchase tax.

Set of aerial coils 9/-; 8 x 3in. ferrite

I.F. **AMPLIFIER** kc/s 2 x OC169 transistors are used as very high gain common emitter amplifiers. High cutoff frequency makes neutralisation unneceson frequency makes neutralisation unnecessary; high gain provides for greatly increased degree of A.G.C. High "Q" double-tuned I.F. transformers give 5 kc/s square wave response. A signal separated from 460 kc/s by 9 kc/s will be 57 dB down. Size 3.5 x 1.5 x 1in. 92/6.

Inquiries invited from trade and manufacturing houses for quantity deliveries.

1 WATT A.F. AMPLFIER GS-12005 2 x OC71's direct coupled cascade drive to 2 precision matched OC74's in Class B push-pull provide up to 1 W. undistorted output from 5 mV. in at 1.5 K-ohm. Frequency response, 60-16,000 c/s ± 3 dB. Overall size 3 x 2.2 x 1.2in. 92/6.

Power requirements for this and other 2 units-6 volt battery.

TSL

TECHNICAL SUPPLIERS LIMITED

HUDSON HOUSE, 63 Goldhawk Road, London, W.12. phone: SHE 2581/4794


◆ ALSO AVAILABLE

Transistorised FM Front Ends: 10.7

Mc/s I.F. transformers, OC169 transistors; Constructors' Manual No. 167. 2/6. Leaflets on request.

AT LAST, FOR ONLY £1!

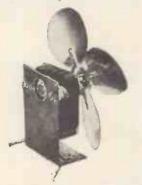A really efficient Fan for use in Electronic Equipment



This is what the Electronics world has been waiting for! At extremely low cost air-stirring and extraction can be easily achieved. Also in production we have Low-Speed Motors from 8 r.p.m. to 40 r.p.m. Price and further details on application to:

KENURE, HOLT & CO. LTD. BOYN VALLEY RD., MAIDENHEAD, BERKSHIRE

Telephone: Maidenhead 5331-2

WE ALSO HAVE SUB-CONTRACT FACILITIES FOR ELECTRONIC WIRING AND ARE FULLY A.I.D. APPROVED

SOUTHERN TECHNICAL SUPPLIES

TRANSFORMERS FOR ALL MULLARD AMPLIFIERS

TRANSFORMERS FOR ALL MULLARD AMPLIFIERS
OUTPUT TRANSFORMERS (Secondaries for 3.75 and 15 ohms)
T.44. 5-10 amp. ultra linear, 8.000 ohm. 43% tappings 30/-. F/F. 2/-.
T.168. 5-10 amp. and Osram 912, 6.600 ohm. 20% tappings, 30/-. F/F. 2/-.
T.100. 6-10 amp. LoW loading, 6.000 ohm. 28/-. F/F. P/F. 2/-.
T.142. 7 watt stereo amp., 9.000 ohm. 28/-. F/F. 2/F. F/F. 2/-.
T.142. 7 watt stereo amp., 9.000 ohm. 20% tappings, 26/-. P/F. 2/-.
T.140. 3 watt amp. type A tape amp., 3 watt stereo, 5,000 ohm. 12/-. F/F. 1/6.
MAINS TRANSFORMERS (Primaries 240-220-200; 0-10 v. 50 ofs).
T.55. 5-10 amp. 300-0-300 v. 120 mA., 6.3 v. 2.5 a., 6.3 v. 2.5 a.,
6.3 v. 1 s., 32/-. F/F. 2/6.
T.56. 5-10 amp. 300-0-300 v. 100 mA. 6.3 v. 2.5 a., 6T. 6.3 v. 1 a., 27/-.
T.143. 7 watt stereo 250-0-250 v., 150 mA., 6.3 v. 4 a. cT., 6.3 v. 1 a., 33/-. F/F.
2/9.

T.143. 7 watt series 250-0-250 v., 60 mA., 6.3 v. 1 a., cT., 6.3 v. 1 a., 22/-, F/F. 2/-, T.141. 3 watt steree 250-0-250 v., 80 mA., 6.3 v. 2 a. cT., 6.3 v. 1 a., 25/-, F/F. 2/-, T.A. Trans, and Rectifier, 270 v. D.C. 100 mA., 6.3 v. cT., 3 a., 32/-, F/F. 2/-, All transformers fully guaranteed, all shrouded fully except T140 and TB. Write for our fully illustrated catalogue, with all data.

SPECIAL OFFERS T44 and T55, 59/-; T143 and two T142's, 82/-, F/F. 3/6 on both. Willsard's latest Publication detailing the complete range. "CIRCUITS FOR AUDIO AMPLIFIERS." 8/6, F/F. 1/-

AMPLIFIERS," 8/6. P/P. 1/-.
SOUTHERN TECHNICAL SUPPLIES, 83, Station Road, Portslade, Sussex

ELECTRICAL & WIRELESS SUPPLY CO.

60, CHURCH ROAD, MOSELEY, BIRMINGHAM I3
Cables: ELEWICO, BIRMINGHAM
Suppliers of American Wireless Communication Equipment for Aircraft such as BENDIX VOR-ILS. Type MN-85 VHF 280 crystal-controlled channels radio system incorporating both navigation and communication facilities operating in the frequency range of 108, 0 to 135, 9 mc/s.

RCA Type 710A Signal Generator. Frequency range 370 to 560 mc/s. Direct calibration. Accuracy ½6. Output voltage luv to 90 mV. Output impedance 50 ohms.

TCS Remote Control Units Type 23270A.

Naval Aircraft Transmitter-Receiver Type AN/ARC-2. 2000-9050 Kc/s; R.F. output 30 watts. Input 26 v. D.C.

AMERICAN AIRCRAFT CAMERAS FAIRCHILD Types K24, K22, K20, K19B, K17B, K8A-B and GUN CAMERAS the most recent type AN/N-9 and G.S.A.P.

AMERICAN FLIGHT INSTRUMENTS such as Air speed, Climb, Fuel, Temperature, Pressure, Horizon, Turn & Slip Indicators, FUEL FLOW AMPLIFIERS, CONTROL DIRECTIONAL GYROS, etc., etc.

AMERICAN AIRCRAFT RELAYS by Leach, Cutler-Hammer, also DELCO FUEL PUMP MOTORS, etc., etc.

UNITED KINGDOM ATOMIC ENERGY AUTHORITY

Vacancies at
A.E.R.E. HARWELL

for

ELECTRONIC MECHANICS

(training would be given to men with a good skilled electrical background who have some knowledge of and aptitude for electronics and wish to further their experience in this work).

ELECTRICIANS AND ELECTRICAL FITTERS

(Several of these vacancies are for men with experience in installation or maintenance of heavy industrial or Power-station electrical plant or control systems).

ELECTRO/MECHANICAL INSTRUMENT MECHANICS

(to operate and maintain a wide range of recording instruments in Reactors and other installations).

Several of these vacancies are with the new establishment being set up at Harwell for the National Institute for Research in Nuclear Science and for another new establishment being built nearby at Culham to take over the thermo-nuclear programme of work at present being carried out at Harwell.

Interesting and varied work where there are excellent opportunities for advancement. Assistance is given towards further education.

The Authority has sick leave and superannuation schemes and is at present operating a local assisted transport scheme.

HOUSING

Married men living outside the Harwell transport area will be housed or given assistance with house purchase.

Please send for explanatory booklet and application forms to:—Industrial Recruitment Office, A.E.R.E. Harwell, Didcot, Berkshire.

UNITED COMPONENTS LIMITED

Design and Manufacturing Organisation for

R.G.D. - REGENTONE - ARGOSY

Invite applications from Electronics Engineers for Senior and Junior positions in expanding design teams in new and well-equipped laboratories. All the vacancies provide interesting work and wide scope to men with enthusiasm and who primarily desire to engage in development. Salary scales are imaginative and the organisation is young with a record of progressive expansion.

TELEVISION

Engineers with H.N.C. or equivalent and some experience in TV Receiver Design.

RADIO

Engineers required with H.N.C. and experience of Transistor Receiver Design.

DRAWING OFFICE

Mechanical Design Draughtsmen required with experience of Radio and TV or electro-mechanical assemblies.

STYLING

Cabinet Draughtsmen required for interesting work on radio and television stylings—knowledge of plastic mouldings and cabinet design an advantage but not essential.

The company offers good working conditions with up-to-date facilities; superannuation scheme; canteen facilities; and many social activities. Applications should be in writing, and will be treated in strictest confidence.

Write to: CHIEF ENGINEER
UNITED COMPONENTS LIMITED, EASTERN AVENUE
WEST, ROMFORD ESSEX

Tel: ROMFORD 45991

TECHNICALLY TRAINED by



IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

Opportunities In Radio Engineering and allied professions await the I.C.S. trained man. I C S Courses open a new world to the keen student

RADIO AND TELEVISION ENGINEERING; RADIO AND TV SERVICING; ELECTRONICS, COMPUTERS & DATA PROCESSING, etc.

I C S Courses give very real help to the man setting up his own business or facing a technical career in the radio industry. Examination Courses for:—British Institution of Radio Engineers, City & Guilds TELECOMMUNICATION TECHNICIANS, C. & G. Radio & TV Servicing (R.T.E.B.) and C. & G. Radio Amateurs.

LEARN-AS-YOU-BUILD PRACTICAL RADIO COURSE
Bulld your own 4-valve TRF and 5-valve superhet radio receiver
Signal Generator and High-quality Multimeter.

FILL IN AND POST THIS ICS COUPON TODAY It brings the FREE ICS Prospectus containing full particulars of ICS courses in Radio, Television and Electronics.

INTERNATIONAL CORRESPONDENCE

SCHOOLS

OF KNOWLEDGE for the KEEN STUDENT

International Correspondence (Dept. 222P), Intertext House, Parkgate Road, London, S.W.II
NAME
ADDRESS

...... 12.60

MARCONI

IF YOU ARE AN EXPERIENCED ELECTRONIC TECHNICIAN

whether you have gained your experience in the Forces or in industry, we may be able to offer you an interesting and well-paid position as a Service Engineer. The work is varied and is concerned with a very wide range of telecommunications and industrial measuring instruments. The Posts are pensionable and offer stability of employment and good prospects of advancement in a progressive and expanding Company.

Please apply to:

Marconi Instruments Ltd.,
Longacres, Hatfield Road, St. Albans,
Herts.

Telephone: St. Albans 56161

ENGLISH ELECTRIC VALVE CO. LTD.

Chelmsford, Essex

SALES ENGINEER

An interesting and progressive career in the commercial field of an expanding industry is offered to an engineer with a sound knowledge of valves as used in radar and telecommunications, and who also possesses sales engineering experience in electronic valves or equipment.

The successful applicant will be required to promote the sales of the Company's products which cover a wide range of specialised valves, by correspondence and direct customer contact.

Preferred age group-30 to 40.

Qualifications: Degree in physics or Electrical Engineering; alternatively Higher National Certificate in Electrical Engineering with endorsements.

Salary will be dependent on experience but we expect applicants to be earning a four figure salary in their present employment.

Replies to:-

Group Personnel Services, English Electric House, Strand, London, W.C.2.

quoting reference WW 1597K

YOU can further your career with

CREI ADVANCED ELECTRONICS EDUCATION

G.R.E.I. home study courses in Electronics are the culmination of 33 years of working closely with leading private companies and Government agencies in the United States. The result is a modern advanced programme of education comparable in technological content to that offered by technical colleges.

C.R.E.I. (London) as the European Division of The Capitol Radio Engineering Institute of Washington, D.C., are now able to offer these courses to you, with the same individual tuition methods which have made our courses outstanding in the United States.

The demand for C.R.E.I.-trained men is shown by the fact that more than fifty corporations and Government agencies in the U.S.A. have agreements with C.R.E.I. for enrolment of employees under company sponsorship.

Specialised Courses are available in:-

Mathematics for Electronic Engineers,

Automation.

Radar and Servo.

C.R.E.I. have recently compiled a complete course in Nuclear Engineering Technology.

(C.R.E.I. courses have been officially approved in the United Kingdom for the purpose of part refund of fees to members of all three Services.)

If you have had at least two years practical experience in electronics or the equivalent please write for full particulars and detailed programmes to: Dept. W.12

C.R.E.I. (LONDON), 132/5, SLOANE STREET, LONDON, S.W.I

Telephone: SLOane 8277/9

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on"... but only for the fully trained man. Let I.C.S. tuition develop your talents and help you to success.

but only for the fully trained mand help you to success.

STUDY IS EASY with I.C.S. guidance. The courses are thorough.

Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. MODERATE FEES INCLUDE ALL BOOKS.

ADVERTISING
Gen. Advertising, Retail &
Dept. Store, Copywriting
ART
Oli & Water Colour
Commercial Illustrating

Commercial Illustrating
BUILDING
Architecture, Clerk of Wks.
Building Construction
Bricklashing, Quantity Surv.
CIVIL ENGINEERING
Highway Eng., Struct. Eng.
Concrete Engineering

COMMERCE
Bookkeeping, Accountancy,
Office Training, Costing,
Secretaryship, Storekeeping
Shorthand & Typewriting
DRAUGHTSMANSHIP
Architectural, Mechanical,
Maths. & Machine Drawing
Drawing Office Practice
Structural Drawing

Drawing Office Practice Structural Drawing ELECTRONICS Industrial Electronics Computers & Maintenance

FARMING
Arable & Livestock
Farm Machinery Maint,
Pig & Poultry Keeping
Market Gardening
FIRE ENGINEERING
L.F.E. Examinations
Fire Service Promotion

Fire Service Promotion
GENERAL EDUCATION
Good Eng., Foreign Langs.
G.C.E. subjects at ordinary
or advanced level

Take the right course now.

HORTICULTURE

Ill & Complete Gardening
Ing Flower & Veg. Growing

MANAGEMENT
Business Management
Hotel Management
Office Management
Industrial Management
Personnel Management
Work Study, Foremanship

MECHANICAL & MOTOR SELLING
ENGINEERING
Engineering Maths, Weld's
Diesel Engines and Locos.
Laspection, Wishop Prot.
Refrigeration, Motor Mech.
Running and Maintenanos
(many other subjects)
And many other subjects.

INTENSIVE COACHING for all principal examinations, including C.J.S., A.C.C.A., I.C.W.A., B.I.M., A.M.I.Mech.E., Brit.I.R.E., I.Q.S., City & Guids of London Institute, R.H.S., etc.

PHOTOGRAPHY

POLICE

Practical Photography P.D.A. Examination

Police Entrance Exam.

RADIO, T.V. & ELECTL. Radio Servicing & Engrg. T.V. Servicing & Engrg. Radio Constro. (with kits)

Start today the I.C.S way!

Intertext	House,	(Dept. 22 Parkgate	2R) Rd., Lon	don, S.W.11
Send FR	EE boo	k on		
Name .				
Address				
				12.60

INTERNATIONAL CORRESPONDENCE SCHOOLS

NEW!

DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS YOU LEARN while you BUILD...

Simple . . . Practical . . Fascinating . . .

ANNOUNGING—after years of successful operation in other countries—the latest system in home training in electronics introduced by a new British training organisation. AT LAST—a simple way of learning—by practical means—the "how and why" of electronics with the minimum of theory and no mathematics! FOU LEARN WHILST BUILDING actual equipment with the components and parts which we send you—and you really have fun whilst learning! And afterwards—you have a first-rate piece of home equipment plus the knowledge of how it works and how it can be serviced.

you have a first-rate piece of home equipment plus the knowledge of how it works and how it can be serviced. THIS NEW SYSTEM brings you an exciting new opportunity at a very moderate cost—and there are RO MATHEMATICS! Post the reply coupon TODAY for FREE Brochure, to Britain's Leading Radio Training Organisation.

BUILD YOUR OWN:-

• RADIO EQUIPMENT

700A

HI-FI INSTALLATION

• TEST EQUIPMENT

AND LEARN AS YOU DO IT No Mathematics

46 Market Place, Reading, Berks.

Please send Brochure without obligation to

LOTS OF

Name Address (812)

BLOCK CAPS PLEASE 11-59

INSTRUCTIVE

EXPERIMENTS AT HOME!

RADIOSTRUCTOR
BRITAIN'S LEADING ELECTRONIC TRAINING ORGANISATION



ELECTRONIC ENGINEERS

We are seeking an engineer to assist in the systems design of Radar Simulators through to Production.

A sound background of engineering practice in the electronics industry covering design and production of sub units and units and their integration into composite systems is required. Responsibilities will include the layout of cabinets and control panels, intercabling and installation.

H.N.C. or equivalent qualification and a knowledge of D.C. Analogue Computer techniques would be an advantage.

Please apply quoting reference 356 to

A. E. Bull, Personnel Officer,

THE SOLARTRON ELECTRONIC GROUP LIMITED,

Farnborough, Hants.



DESIGNER DRAUGHTSMAN

A Draughtsman with at least O.N.C. in electrical or mechanical engineering and some experience of professional recording equipment is required by the Development Laboratories of E.M.I. Ltd. at Hayes, Middlesex, for general work on units of sound recording equipment systems.

He should have sufficient ability to produce complete drawings for small batch production and also have an interest in styling and prototype layout. This position involves a variety of interests and will appeal to those wishing to widen their experience.

Please apply giving full details, and quoting reference GR/B/5, to:

Personnel Manager
E.M.I LTD.,

Blyth Road, Hayes, Middlesex.



At Solartron we believe that people are important and consideration for the individual is the number one priority.

If you feel that you have become just a cog in an impersonal machine and if you have experience in either of the following jobs, we shall be pleased to hear from you.

We can promise you plenty of hard work but a great deal of satisfaction from working in our team. Our amenities and conditions match our philosophy.

We have vacancies for:

ELECTRONIC TEST ENGINEERS

for the Test Department.

Ref: 488/WW

ELECTRONIC SERVICE ENGINEERS

for the Service Department at our Cox Lane, Chessington location.

Ref: 489/WW

Please apply to:

B. B. Lynch, Personnel Officer,
SOLARTRON LABORATORY
INSTRUMENTS LTD.,

Queens Road, Thames Ditton, Surrey

MICROWAVE ENGINEERS AND PHYSICISTS For

KEY POSITIONS IN THE U.S.A.

Several desirable positions are available with a leading Electronics Research and Development Laboratory for competent Inventive microwave engineers and physicists, preterably with at least 5 years experience and a higher degree, to direct and contribute to advanced Research and Development work on existing long-range programs in:

- Solid-State Millimeter and Optical Masers
- Parametric Amplifiers
- Ferrite and Semiconductor Devices
- Microwave Radiometers

Although specific experience in one or more of these areas is desirable, those with an applicable microwave or applied physics background will also be considered.

MINIMUM SALARY \$10,000 (£3,500)
RELOCATION EXPENSES WILL BE PAID

The Laboratory, containing the most up-to-date facilities and equipment is located near New York City, on Long Island.

Further particulars can be obtained by sending a detailed record of professional experience. We will arrange a personal interview at your convenience in England.

WRITE: JOHN N. DYER, Technical Director

AIRBORNE

INSTRUMENTS LABORATORY

A DIVISION OF CUTLET-HAMMER, INC.

COMAC ROAD . DEER PARK . NEW YORK

CANADA

Canada's largest Electronics specialists have vacancies for radio and electronics technicians for duties in remote areas of Canada. Salary \$7,500 per annum. Qualifications three years or more experience in installation or maintenance of communications type equipment with special emphasis on radio relay carrier radar and data transmission systems. Academic qualifications to City and Guilds or Higher National Certificate desirable but applicants with extensive practical experience considered. Suitably qualified applicants should send a résumé of their qualifications and attach a recent passport size photograph.

Interviews will be arranged in London during January 1961 for selected applicants.

Cost of transportation to Canada for personnel accepted will be borne by the Company.

Apply to Box Number 2356 c/o "Wireless World."

ASSOCIATED ELECTRICAL INDUSTRIES LIMITED TELECOMMUNICATIONS DIVISION

Several established positions are available in S.E. London within the Transmission Department carrying attractive salaries and conditions for applicants of a suitable calibre. This Department is expanding and requires qualified engineers for its new Laboratories on a wide range of new projects.

CIRCUIT DESIGNERS

for Transmission Systems, including V.H.F. Radio, Transistor Circuits, Networks and Components.

MECHANICAL DESIGNERS

for new equipment constructions and compact miniature assemblies.

EQUIPMENT ENGINEERS

for contract specifications and preparation of manufacturing information.

TECHNICAL WRITERS

for preparation of operational instructions and handbooks.

There will be opportunities for wide scope and career progress for men with initiative. Applications are invited for both Senior and Junior grades, and interviews may be arranged confidentially and individually by telephone with Mr. K. Bullen, Ext. 736, WOO 2020 Written applications should be addressed to the Staff Officer, Ref. 736/39/WW, Associated Electrical Industries Limited, London, S.E.18.

UNICAM INSTRUMENTS LIMITED

This Company specialises in the production of high quality optical instruments for use in spectrum analysis and has an international reputation as a leader in this field. At all stages of manufacture the best standards of workmanship are needed.

We have vacancies for men with electronic experience for testing. Radar and Radio Technicians with fault-finding experience would be suitable.

If you have the kind of background which you think would fit you for this interesting work in a pleasant University City, please let us have full details of your qualifications and experience.

Write to: The Works Manager, Unicam Instruments Ltd., Arbury Works, Cambridge, quoting reference E.S.47



UNITED KINGDOM ATOMIC ENERGY AUTHORITY

DOUNREAY EXPERIMENTAL REACTOR ESTABLISHMENT

Instrument Mechanics (Physical and Electronic) and Instrument Electricians

There are vacancies in the Instrument Department for men with experience in the maintenance of instruments for the measurement of pressure, flow and temperature, electronic instruments, radar and television and for electricians with experience in the maintenance of temperature recorders and electromagnetic relays.

Applications are invited from men with experience of instruments in industry or with appropriate experience in H.M. forces.

The rate of pay is £13,7.0d. for a 44 hour five day week and there is a superannuation scheme. Housing will be made available to married men and there is accommodation for single men and married men awaiting housing.

Facilities are available for further education and promotion prospects are good.

Application forms and further information can be obtained from Recruitment Officer, Dounreay E.R.E., Thurso, Caithness, Scotland.

PLESSEY NUCLEONICS

are extending their electronics labora-tories at Northampton.

The Company is engaged in the deve-The Company is engaged in the development of an interesting variety of nuclear electronic equipment, employing mainly transistor circuits. Positions are available for senior and junior circuit engineers, also for an instrument engineer with experience in light current electrical systems and sérvo control.

Write in confidence for further details

Personnel Manager, Plessey Nucleonics Limited. Weedon Road, Northampton.

BRITAIN'S CAR RADIO SPECIALISTS INVITE APPLICATIONS FOR THESE POSTS

ASSISTANT FOREMAN

Experience of car radio application and maintenance desirable but not absolutely essential. This progressive appointment is in the Service Department.

EXPERIENCED SERVICE ENGINEERS

These appointments hold out very definite prospects of advancement for the right individuals.

Applications giving full details of career to date should be addressed to: THE STAFF MANAGER, S. SMITH & SONS (ENGLAND) LTD., CRICKLEWOOD, LONDON, N.W.2. quoting ref. SM245



COMPUTER MAINTENANCE ENGINEER

BP has a vacancy for a Computer Maintenance Engineer at its Head Office in the City of London. Age 25-30. Applicants should have H.N.C. or equivalent technical qualifications. Experience of Electronic Equipment Maintenance and the servicing of Computers is necessary. Salary according to age, qualifications and experience. Non-contributory Pension Fund. Assisted House Purchase Scheme. Removal expenses and settling-in allowance payable in certain cases. Luncheon Club. Write quoting H.5158A, to Box 6441, c/o Hanway House, Clark's Place, E.C.2.

FREE TO AMBITIOUS ENGINEERS - THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee "NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING

TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/22), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng., Electrical Eng., Civil Engineering, Radio Engineering, Automobile Eng., Aeronautical Eng., Production Eng., Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.Prod.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.A.E.S.
B.Sc.
A.M.Brit.I.R.E.
City & Guilds
Gen. Gert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate

Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.B.T.(incorporating B.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ash for details.

B.I.E.T. SCHOOL OF ELECTRONICS OPPOPTUNITIES

7 7

POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"

(Write if you prefer not to cut page)

NAME.....

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

PEMBRIDGE COLLEGE OF ELECTRONICS

offers training in RADIO
TELEVISION
AND ELECTRONICS

ATTENDING COURSE

Full-time One Year Course in Radio and Television. College course in basic principles for prospective servicing engineers.

Next course commences 3rd January, 1961.

This course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the new Servicing Certificate examinations.

HOME-STUDY COURSES

- A. Radio and Television Servicing.
 - (1) Introductory course.
- (2) Basic course covering R.T.E.B. Intermediate Radio and Television Servicing Certificate examination.
- B. Courses in Radio, Telecommunications and Mathematics up to City and Guilds Telecommunication Technicians' Final Certificate.
- C. Constructional kits.

For details, write to:

The Principal, P11

THE PEMBRIDGE COLLEGE
OF ELECTRONICS

34a Hereford Road, London, W.2

LINITED KINGDOM ATOMIC ENERGY AUTHORITY PRODUCTION GROUP

INSTRUMENT MECHANICS

Windscale and Calder Works, and Chapelcross Works require experienced men with knowledge of electronic equipment and/or industrial instrumentation for fault diagnosis, repair and calibration of a wide range of instruments used in nuclear reactors, radiation laboratories and chemical plant. This interesting work involves the maintenance of instruments using pulse techniques, wide band low noise amplifiers, pulse amplitude analysers, counting circuits, television and industrial instruments used for the measurement of pressure, temperature and flow.

Men with Services, Industrial or Commercial background of radar, radio, television, industrial or aircraft instruments are invited to write for further information. Training Courses in Specialised Techniques are provided for successful applicants having suitable Instrumentation background.

Married men living beyond daily travelling distance will be eligible for housing. A lodging allowance is payable whilst waiting for housing. Working conditions and promotion prospects are good.

Applications to:

Works Labour Manager, Windscale and Calder Works, Sellafield, Seascale, Cumberland

Works Labour Manager, Chapeleross Works, Annan, Dumfriesshire, Scotland.

ENGLISH ELECTRIC VALVE CO., LTD. **CHELMSFORD**

SEMICONDUCTOR RECTIFIERS

A well qualified engineer or physicist is required by the Company for a senior position in the Semiconductor Department.

The position involves technical responsibility in development and production of germanium and silicon power rectifiers.

Experience in research and development of semiconductor devices is essential and applicants should also possess a good degree in physics or electrical engineering.

Preferred age range-30 to 40.

Applicants should reply to-

GROUP PERSONNEL SERVICES, ENGLISH ELECTRIC HOUSE, STRAND, LONDON, W.C.2.

quoting reference WW 1506J.



ELECTRONIC APPARATUS DIVISION TEST ENGINEERS AND TESTERS

required for Ground Radar, Servo Control, and Computer Systems. H.N.C. and O.N.C. or equivalent qualifications an advantage. Excellent opportunities are available in this field for suitable applicants.

If you have sufficient technical qualifications and experience, then apply to:-

The Employment Supervisor, A.E.I. (Manchester), Ltd., Trafford Park, Manchester 17

VENNER

SENIOR ELECTRONIC **DEVELOPMENT ENGINEERS**

Are you looking for the opportunity to become a member of a team working on transistorized equipment with participation in original research development work? If so, we invite your applica-tion to fill the above positions.

These positions are permanent and the Company offers salaries in line with the requirements. There is an attractive Pension Scheme in operation which applicants may join after having served a probationary period, the scheme providing life assurance over also. Excellent working conditions. There are numerous welfare amenities. 8° aff canchen and good social facilities. The Company is situated on the Kingston By-Pass and therefore is well served by train and bus services, including Green Line services.

Applications in writing, please, marked "Confidential" giving details of experience and salary required, to:—

The Personnel Manager VENNER ELECTRONICS LIMITED. Kingston By-Pass, New Malden, Surrey.

VACANCIES IN GOVERNMENT SERVICE

A number of vacancies, offering good career prospects, exist for:— BADIO OPERATORS
CYPHER OPERATORS
TELEPRINTER OPERATORS
TELEPRINTER OPERATORS
TELEPRINTER OPERATORS Write, giving details of education, qualifications and experience to:—

Personnel Officer, G.C.H.Q. (3/R.C.O.), Foreign Office 53, Clarence Street, Cheltenham, Glos,

IMPERIAL COLLEGE

TECHNICAL ASSISTANT required for chart plotting and other duties in radar research on storms at a base near Ascot. Experience in plotting or radar servicing an advantage.

Apply Imperial College, Silwood Farm, Cheapside, Nr. Ascot, Berks.

TEST ENGINEERS

Required for varied and interesting work (partly experimental) on high quality television and communications equipment.

Good experience in the use of measuring instruments is essential. Starting salary in the range of £750—£950 p.a. according to qualifications and experience, with excellent prospects of advancement.

The Company operates a Pe-Scheme and Sports/Social Club.

Write, in confidence to:

The Manager, Central Engineering Department, BRITISH RELAY WIRELESS LIMITED, 1-7 Croft Street, Deptford, London, S.E.8,



FNGINFFRS

with H.N.C. or young Graduates, and junior engineers above O.N.C. level, are required to work under a Chartered Engineer, on the Development of electronic equipment. The projects are d.c. amplifiers and stabilised power units for industrial and electromedical applications. Encouragement will be given for initiative in design. Emphasis will be given to Technical ability rather than qualifications.

Apply the Personnel Officer,

ASSOCIATED ELECTRICAL INDUSTRIES LIMITED

Brantwood Road, Tottenham, N.17

VACANCIES FOR RESEARCH AND DEVELOPMENT CRAFTSMEN IN GOVERNMENT SERVICE AT CHELTENHAM

- Experience in one or more of the following:—
 (1) Maintenance of radio communication receivers.
 (2) Sub-assembly lay out, wiring and testing of radio type chassis.
 (3) Cabling, wiring and adjustment of telephone type
- equipment.
 (4) Pault finding in and maintenance of electronic
- (s) Faut mining in and maintenance of electronic apparatus.
 (5) Minintenance of teleprinter or cypher machines and associated telegraph equipment.

 Basio Pay \$29/9/8 per week plus merit pay, assessed at interview and based on ability and experience as

at interview and based on activity and Capen week.

ORDINABY RATE 10/- to 50/- per week.

SPECIAL BATE 50/- to 100/- per week.

Opportunities for permanent and pensionable posts Five-day week; good working conditions; single secommodation available.

Apply in writing to:—

Forsonnel Officer,

Forsonnel Officer,

S3, Clarence Street,

Cheltenham, Glos.

ELLIOTT

Opportunities . . .

IN CONTROL ENGINEERING

The following personnel are required to join our teams of Engineers engaged on the design and development of advanced projects:

- 1. ELECTRONIC CONTROL ENGINEERS. Degree standard with a minimum of 5 years' design experience, especially of transistor and/or magnetic amplifiers.
- 2. ELECTRONIC CONTROL ENGINEERS. Degree standard with at least 2 years' experience in the design of transistor and/or magnetic amplifiers.
- 3. AERODYNAMICIST. Degree standard with at least 3 years' experience.
- 4. MATHEMATICIAN. Degree standard, with a genuine interest in aerodynamics and control systems.
- 5. SERVO ENGINEER. Degree standard together with 2 years' experience.
- 6. FLIGHT CONTROL SYSTEMS ENGINEER. Degree standard and having practical experience in Aircraft Control,
- 7. AIR DATA SYSTEMS ENGINEER.

In addition to a challenging and stimulating occupation, successful applicants will be located in a growing engineering area offering reasonable housing and travelling facilities, together with easy access to London and the coast.

Applications, which will be dealt with in strict confidence, stating full particulars of age, qualifications and experience, should be sent to the Personnel Manager.

ELLIOTT BROTHERS (LONDON) LIMITED.

Airport Works, Rochester, Kent.

REBUILT TV TUBES

FULLY GUARANTEED 12 MONTHS Complete New Gun fitted in every Tube

NU-GUN TELETUBES LIMITED

3 The Mews, Duckett Ra., Harringay, London, N.4. Telephone: MO Untview 2903

A. K. & L. G. SMITH LIMITED

Wholesalers and Distributors of Electrical and Electronic Appliances, Household, Etc.

38, Nunhead Lane, Peckham, London, 8.E.15

WALTRAK pocket audio oscillator, transistorised, 1,000 c.p.s., supplied complete with battery, probe, etc. Excellent technical reviews, ideal for circuit checking. etc. \$6/10/- subject.

WAL GAIN transistorised pre-amplifiers, many applications supplied complete with battery, phono plugs, screened lead, etc. Mono £5, Stereo £7/10/-subject.
Full technical literature.

WELLINGTON ACOUSTIC LABORATORIES LTD. Farnham, Surrey Farnham 6461

DRAUGHTSMEN

We have a requirement for a large number of Designers and Draughtsmen at all levels experienced in:

ELECTRONIC AND COMPUTER EQUIPMENT; AIRFRAME STRUCTURES;

HYDRAULIC SYSTEMS; RADIO OR SCIENTIFIC INSTRUMENTATION; STRUCTURAL, MECHANICAL AND ELECTRO-MECHANICAL DEVICES.

HOUSING ASSISTANCE MAY BE POSSIBLE.

Applications to be sent to: Technical Personnel Officer, c/o Dept. G.P.S. English Electric House, Strand, London, W.C.2. quoting reference W.W. 1399U.

ENGLISH ELECTRIC AVIATION LTD.

Guided Weapons Division London—Luton—Stevenage

ELECTRONIC DEVELOPMENT ENGINEER

required

to lead a small team engaged in the development of commercial communication equipment. Applicants should have a degree or equivalent qualification and some years experience as Project Engineers. Preferred age range: 30/35 years.

NON CONTRIBUTORY PENSION SCHEME AND LIFE INSURANCE.
5 DAY WEEK.

EVENING INTERVIEWS ARRANGED.

Write giving details of education, qualifications and past experiences to:-

PERSONNEL MANAGER MULTITONE ELECTRIC CO. LTD., 12/20 UNDERWOOD STREET, N.I.



Associated Electrical Industries Limited

Are you aware of the challenging new opportunities available to **ELECTRONICS ENGINEERS**

in SCIENTIFIC INSTRUMENTATION

A.E.I. Instrumentation Division are expanding their activities in MASS SPECTROMETRY

RADIO-FREQUENCY SPECTROSCOPY **ELECTRON MICROSCOPY** and allied techniques

and Electronics Engineers are required for a variety of new positions in their development, design and engineering teams. Previous experience of the equipments is not essential.

If you think you would be interested in a job in this new field of activity, please write for an appointment, giving brief details of your career and let us show you what we do. Please reply, quoting reference L.16 to:

Personnel Manager,
Associated Electrical Industries (Manchester) Ltd., Trafford Park, Manchester, 17.

TECHNICAL REPRESENTATIVE

Required for Northern Counties area by manufacturer of electrical and electronic Applicants should possess components. a degree in electrical engineering or have experience to an equivalent standard. Preference will be given to those under 35 years of age and resident in the North-The job is specialised and offers considerable potential.

A Company car is provided and a Pension Scheme is in operation.

Applications, giving details of age, qualifications and experience, quoting Ref. P6 to: Morganite Resistors Limited, Bede Trading Estate, Jarrow.

Senior and Junior Electronics Engineers required by internationally known organisation. Candidates must be single, medically fit, prepared to spend periods of up to two years abroad and to be able to accept respon-sibility for the success of projects.

Qualifications: Senior posts—H.N.C., B.Sc., or equiva-lent, plus industrial experience. Junior posts—O.N.C., or experience as first-class skilled radio mechanics. A knowledge of modern survey techniques is an advantage.

Please reply to Box Number 2348, c/o "Wireless World"

BRADFORD INSTITUTE OF TECHNOLOGY Department of Electrical Engineering

Applications are invited for the following posts in this rapidly expanding department which offers exceptional opportunities for teaching, consulting and research work:—
SENIOR LECTURER IN ELECTRICAL ENGINEERING—Salary scale £1,550 to £1,750.

LECTURER IN ELECTRICAL ENGINEERING—Salary scale £1,370 to £1,550.

Candidates should be suitably qualified to teach to final degree standard in electrical power and machines or electronics and telecommunications. Industrial and research experience will be a recommendation.

The successful candidates will be encouraged to develop.

The successful candidates will be encouraged to develop industrial contacts and undertake research for which adequate facilities will be available.

Previous industrial and research experience at a suitable level

will be taken into account in fixing the commencing salary.
Further particulars and forms of application may be obtained from the Registrar, Bradford Institute of Technology, Bradford,

HENRY PATTEN Clerk to the Governors

FOR THE FIRST TIME IN THIS COUNTRY

THE WORLD'S FAIRY TALES DRAMATIZED ON TAPE

Told by MELANIE SCOTT

Complete Set of 4 Reels containing 16 different stories

Price: 29/6 per 5" Reel of Four Stories

Postage: 1/6 per tape

From: H. B. TRADING CO. 60-66 Wardour Street, W.1

PHILIPS FLECTRICAL INDUSTRIES

(NEW ZEALAND) LTD.

DEVELOPMENT ENGINEERS

Two radio and television Development Engineers are required for laboratory posts in the Company's Electronics Centre, Nae Nae, Lower Hutt, near Wellington, New Zealand.

They should be between 25 and 35 years of age, have a degree in electrical engineering or similar qualifications and some years experience of the design and development for production of domestic radio and television receivers.

Lower Hutt is one of the chief manufacturing centres in New Zealand and is about 14 miles from Wellington, the seat of Government.

Applications, in the first instance, should be sent to Miss M. Niven, Central Personnel Department. Philips Electrical Industries Ltd., 171 Shaftesbury Avenue, London, W.C.2. quoring reference NZ/WW:

TAPE RECORDER SOUND HEADS

R/P & Erase. Monaural.

R/P & Erase. 2 Track Stereo. R/P & Erase. 30

HOME & EXPORT

Full specifications, technical data, with samples available to the Trade on request:-

BRADMATIC PRODUCTIONS LTD

124. ALBERT ROAD BIRMINGHAM, 21 ENGLAND

DESIGN DRAUGHTSMAN

Man having experience of mechanical assemblies associated with radio receivers and electronic equipment. Ability to work on own initiative. Excellent prospects. Non-contributory Pension Scheme.

Applications in writing to:

The Technical Director, Stratton & Co. Ltd., Eddystone Works, Alvechurch Road, West Heath, Birmingham, 31.

YONS RADIO LTD

MAINS POWER UNITS. Input 200/250 v. A.C. mains. Output:—H.T. 325 v. at 160 mA. smoothed D.C., L.T. 6.3 v. A.C. at 4 A. twice. Bize: 10 lin. high x. 15m. deep x/ln. Special features include double filter unit ensuring negligible hum, Mansbridge smoothing condensers throughout, separate switches and fuses for mains and H.T. with pliot light indicator for each Everything of top quality, 5U4 rectifier included, condition as new and unused. Truly remarkable value. PRICE ONLY 50/6, carriage 7/6.

MAINS TRANSFORMERS (Manufacturer's surplus). Pri. 200/250 v. 40/60 cps. Sec. 350/0/350 v. at 150 mA.

MAINS TRANSFORMERS (Manufacturer's surplus). Prl. 200/250 v. 40/00 cps. Sec. 350/0/350 v. at 150 mA. G. v. at 4 A. twice and 6 v. at 3 A. Pully impregnated, top grade, inverted mounting, approx. 6 x 8 x 8 in. As new. PRICE ONLY 19/6, post 3/6. SMOOTHING CHOKES. Approx. 10 H. at 150 mA., D.C. resistance 200 ohms. Wt. 6 lb., impregnated. size 4x4 x 3 ½ lm., inverted mig. Highest class make. PRICE ONLY 10/7/6, post 2/9/2000 pc. 10/10/2000 p

MODULATION INDIGATORS (Ex-Gov.). These are battery operated Test Sets designed to measure depth of modulation of signals between 2.4 to 6.25 Mc/s. House in next metal cases 1½ x7½ x6¼in. Fitted with 2½in. dia. 0/500 micro-ammeter, 1 mA. meter rectifier, triode valve, etc. These units should also serve as an excellent basis for a first-class valve voltmeter. PRICE ONLY 35/-, post 3/6.

3 GOLDHAWK ROAD. SHEPHERDS BUSH. LONDON, W.12 Telephone: SHEpherds Bush 1729

RADIO TECHNICIANS IN CI'/IL AVIATION

Men aged 19 or over for interesting work providing and maintaining aeronautical telecommunications and electronic navigational aids at aerodromes and radio stations in the U.K. Fundamental knowledge of radio or radar with some practical experience essential; training provided on special types of equipment. Salary according to age and station, approx. £670 at age 25 rising to £795. Prospects approx. 6670 at age 25 rising to £795. Prospects of permanent pensionable posts. Good opportunities for those who obtain O.N.C. in Elec. Eng. or certain C. and G. Certificates for promotion to posts with maximum salarles of £950, £1,085, £1,335. Apply to the Ministry of Aviation (Est.5(a)/RT), Berkeley Square House, London, W.I., or to any Employment Exchange (quoting Order No. Westminster 3552).

ODDIE FASTENERS



THE FASTENER WITH ENDLESS APPLICATIONS - SIMPLE - POSITIVE SELF-LOCKING. MADE IN A VARIETY OF TYPES AND SIZES. SPECIAL FASTENERS TO SUIT CUSTOMERS' REQUIREMENTS. WIDELY USED IN THE RADIO INDUSTRY.

Illustrated brochure and other information will gladly be sent on request

DEPT. "W.W."

Oddie: Bradbury & Cull Ltd., Southampton

Tel. 55883 Cables: Fasteners, Southampton



Moston

MANCHESTER

have vacancies for

TEST ENGINEERS

for work on

- (1) TRANSISTOR CIRCUITRY
- (2) GYROSCOPES
- (3) ACCELEROMETERS

Candidates should possess at least O.N.C. (Electrical or Mechanical) and preferably experience in these or related fields.

Brief details of age, education and experience should be sent to T. J. Lunt, Staff Manager, Ferranti Limited, Hollinwood, Lancs.

Please quote reference AEBM.

FAIREY AVIATION LIMITED

HAYES,

MIDDLESEX

VIBRATION TEST DEPT.

VIBRATION ENGINEER

required for senior post to work on practical investigations of vibration and fatigue in helicopters. Candidates should be graduates or hold HNC with Endorsements and have several years' experience in this field.

TECHNICAL **ASSISTANT**

required for the maintenance and development of strain gauge equipment used in vibration testing of helicopters. Candidates must hold C. & G. Telecommunications Part IV or HNC or have considerable practical experience and "know how."

Applications for these interesting and rewarding positions should be sent to the:

Personnel manager at Hayes, Middx.

Z. & I. AERO SERVICES LTD.

Head Office: 14 South Wharf Road, London, W.2

Tel.: AMBassador 0151/2

Cables: ZAERO, LONDON

A.R.B. Approved Stockists

RETAIL BRANCH (personal callers only): 85 TOTTENHAM COURT ROAD, W.2 Tel.: LANgham 8403 Please send all enquiries, correspondence and Mail Orders to Head Office

AUDIO FREQUENCY EQUIPMENT

B.S.R. TYPE LO-50 Beat Frequency Oscillators. Free B.S.K. TIPE MO-30 Sea requency Oscillators. For quency Range 0-16,000 of cutput 5 watt; calibrat.on accuracy 1%. Distortion better than 1%. Two-dist differential tuning. Malns operation. Output Im-pedance 600 n. Output Volrage 20V. open circuit. Fully overhauled and guaranted P. & P. 151-250 0 0

FURZEHILL R-C OSCILLATORS; four ranges 40 to 10,000 c/s; output 0.5 watts; output voitage 25V for 600Ω; impedance 10,000 and 5,000Ω. Mains operation £25. P.P. 13/-

FURZEHILL No. 1 BEAT FREQUENCY OSCILLATOR, 0-10,000 c/s.; Output 2 watts into 10 or 600 Q. Mains operation. Fully overhauled and guarantee. P.P. 15/-£22 10 0

HEWLETT PACKARD MODEL 205AG.

REUSELINE TRUEASED MUDEL 200AM, Resistance Timed Oscillator with a frequency range of 20 c/s. to 20 kc/s. in three bands. Output 5 watte into 50, 200, 600 and 5,000 onms with distortion not exceeding 1%. Output Meter; Input Meter. Calibrated Attenuator. PERCE, tilly overhaused and guaranteed £55 0 0 Packing and carriage £1 0

MARCONI TF-885A VIDEO OSCILLATOR

GENERAL RADIO TYPE 700A WIDE RANGE BEA'L PREQUENCY OSCILLATOR. Bangs 50 cts. to 5 mcrs. in two ranges; incremental requency control. Output impedance 3,500 g. Fully overhauled and guaranteed. £70 0 0

Post and Packing

MARCONI TF-142E DISTORTION FACTOR METER

Fundamental Frequency Range 100-8,000 c/s; Distortion Factor Range 5% and 50%. First reading at .05%. Impedance 600 Ω. Power Supplies 200-250V. Mams. Fully overhauled and guaranteed£65 0 0

DAWE INSTRUMENT TYPE 700A DISTORTION FAC-DAWE INSTRUMENT TIPE JOHN DISTORTION FALCOR METER, Frequency range 100 to 8,000 cfs on fundamentals; Distortion range 1 to 50% with an accuracy or 10%. Input unpedance 600 ft. Sensitivity 1 militwatt. Mans operation. Fully overhaused and guaranteed. P.F. 20/

R.C.A. TYPE 69C NOISE AND DISTORTION METER.

CT-49 ABSORPTION AUDIO FREQUENCY METER

Variable Capacitor tuned L-C Resonant Circuit. Detector and Valve Voltmeter Stago. Microammeter resonance indicator. Range 450 c/s. to 22.0 ke/s. m four directly calibrated bands. Power required: dry batteries 1.5 V. and 22.5 V.

PRICE fully overhauled and guaranteed £22 0 0 Packing and carriage

MARCONI TF-340 OUTPUT POWER METER

Meter calibration: 0-50 mW. and 0-17 dB. Impedance settings: 25-30-40-50-60-80-100-125-150-200 obms. Impedance multiplier: 0.1-1.0-10-100. Meter multiplier: 0.1-1.0-10-100. Total power range: 5 mW. to 5 W. F.S.D PRICE£25 0 0 Packing and carriage

VARIABLE AUTO-TRANSFORMERS

115V input, 0-135V output at 7.5 amps. £6 0 0

HETERODYNE WAVEMETERS

TS-173 Heterodyne Crystal Controlled Frequency Meters, As-176 Heterodyne Urystal Controlled Frequency meter ampter 90 to 450 Mays. Individual Calibration Books with numerous rystas check points. Accuracy 605-50 monimal and 0.1% interpolation. Power required: the batteries 6V and 136V. PRICE fully overhanded accuration of the control of the cont

T3-175 Heterodyne Crystal Controlled Frequency Meters, range 80 to 1,000 Mc/s., otherwise as above. PRICE aully overhauled and guaranteed ____ £210 0 0

MARCONI TYPE TF-785 PRECISION HETERODYNE WAVEMETEIL. Bange 3 to 15 Mc/s, on fundamentais, extendible to at least 30 Mc/s, by using harmonics. Acturacy better than .005% Crysta Reference Oscillator giving check points every 20 and 200 ko/s. Direct calibration with linear interpolation. Power supplies 220 V. mains. PRICE, fully overhauted and guaranteed

ALSO BC-221 and LM-14 FREQUENCY METERS. Prices and details on application

PEN RECORDERS

EVERSHED PORTABLE RECORDING VOLT-

.50V D.C. Sin. chart, clockwork chart dry		-spe	ed,
im. and 6in. per minute	£30	0	0
o0mV. D.C., ditto	£30	0	0
150m V. D.C., ditto	£30	0	0

EVERSHED SWITCHBOARD PATTERN RECORDING MILLIAMMETERS

Single Pen imå or ömå Range, titted with "operation" pen to mark the beginning and end or an event, in misgnitude of which is recorded by other pen. Operation pen is energised from an internal transformer by shorting the external ieads. Fully rebuilt and guaranteed

ImA. Range	£58	TO C
5mA Range	£55	0 0
Twin Pen 5mA. D.C. Electric chart drive		
Chart speed in. per minute. 6in. chart		
overhauled and guaranteed	£65	0 0
Ditto 1mA. D.C	£72	0 0

ELLIOTT SINGLE PEN SWITCHBOARD PATTERN RECORDING MILLIAMMETERS

single	Pen 5	mA. I	speed Sin. per minute.	230♥	A.C.,
nauleo	i and	Juars		£45	
Ditto	lmA.	D.C.		£48 1	0 0

MARCONI TF-888 PORTABLE RECEIVER TESTER

MARCONI CIRCUIT MAGNIFICATION METERS

Type TF-329C/1; Frequency Bange 50 kc/s. to 50 mc/s. in four ranges, accuracy ±2%. Magnification range 10 to 500; Tuning Capacitor 500μμF. Vermer capacitor ±2μμF. Fully overhauled and guaranteed. P.P. 20ι. €85 0 0

Type 886A. Frequency Range 15 to 170 mc/s. in four ranges $\pm 2\%$. Magnification Range 60 to 1,200 in three ranges. Tuning Capacitor 12 to $56\mu\mu\text{F}$ with Vernler Tuning Dial. Fully overhauled and guaranteed. P.P. 201. £130 0 0 "MEASUREMENTS CORPORATION" TYPE 84 "STANDARD" SIGNAL GENERATOR



Bange: 300-1.000 Mc/s. Direct Calibration.

Accuracy: 0.5%. Output Level: 0.14.V-100 mV. continuously variable internal Modulation:-

Smewave-30 % Max. at 400, 1,000 and 2,500 c/s. Pulse—I to oursec, width delay variable from 0 to 50,000, p.r.r. 60 to 100,000 d/a.

Output Impedance-50 ohms.

Percentage Modulation Meter.

PRICE, m as new condition, tested before despatch and ruly guaranteed £220 0 0 Packing and carriage

HEWLETT PACKARD TYPE MI-. 6733 SIGNAL CENERATORS (Model LAE)

Frequency range: 520 to 1,300 Mc/s m 1 band.
Accu. acy: ±1%
Output impedance: 50 D.
Output Voltage: µV. to 1 volt.
Fuls. Modulation: 60 to 2,500 p.p.s., 2 to 30µsec. wide:
3 to 300µsec. delay, 8quare shape with .5µsec. rise and

all time. Catbrated Attenuator within ±1dB. PRICE fully overhanded and guaranteed, with frequency and attenuator catbration darks and correction charts. P.P. 62

OSCILLOSCOPES

COSSOR DOUBLE BEAM Type 339 ___ £30 0 0 DUMON'S SINGLE SEAM Type 168, 5th. Tube, Time base up to 30 gc/L., 115 V. operation £25 0 0 DUMONT SINGLE BEAM Type 241, as above £25 0 0

DUMONT SINGLE BEAM Type 208, 5in. tube Time Base up to 50 kg/s. £30 0 0

Packing and carriage £1 0 0

IP-149A/APA-II PULSE ANALYSER

B.T.H. "X" BAND PERFORMANCE TESTING RESONATOR (ECHO BOX)

Directly calibrated frequency dua, graduated from 9,170 to 9,470 Mc/s. Graduated Attenuator; Microammeter Reson-Microammeter Reson-anc Indicator; com-plete with R.F Cable and Waveguide Adaptor. PRICE .. £82 0 0 P. and carr. 15 0



V.H.F. RECEIVER UNITS BC-624 (part of SCR-522 Transmitter-Receiver)



the transfer of the controlled channel, 100-156 Mo/s. (3.0-1.98 metres). Vaives 9003 E.F. stage; 9003 Mixer; Three L.F. stages 128G7; Det/AVC/Audio 1226; Second Audio 1235GT; Oscillator 2AH7GT, Has Generator 9002; Harmonic Har

monic Amplifier 9003; Audio Squelch—other section of 12AH-7GT. High and Low Impedance output. PRICE, complete with valves, with description and circuit diagram, but without squelch relay 25/-, p.p. 5/-. PRICE, chassis only, less valves 7/6, p.p. 3/6. ALSO LIMITED QUANTITY ONLY:

TRANSMITTER UNITS BC-625 (part of SCR-522 Radio Set)

Valves: Speech Amplifier 6887; Push-Pull Modulator (two 12A6); Oscillator 6G6G; 1st Harmonic Ampl. 12A6; 2nd Harmonic Ampl. 832; Power Ampl. 832. Output

PRICE, complete with valves, description and circuit diagram' ... p.p. 5/- 22/6
Price, chassis only, less valves ... p.p. 3/6. 7/6
Descriptions and circuits available at 8d. each.



RATCHET MOTORS, 12 v.

,	1 Amp.	(Impulse	Motors	s) 5. 75
1	ohms		3	/6 each
	Packing	and postage		1/6.

VENNER 8-day olockwork time switches. 24-hour dial with one make and one break. 1 amp. 280%.contacts. 8econd-hand, good condition, complete with winding key....p.p. 2/- 27/6

1B, 5,000 Ω

ROLLER-SMITH MOVING COIL CURRENT RELAY nominal setting 1.54 D.C. with adjustments of ±20% Coil Resistance approx. 90. One changeover contact 200 mA. capacity. Switchboard mounting 35/-, p.p. 4/-

P.O. BUZZERS

WESTINGHOUSE RECTIFIER POWER SUPPLY UNIT Input 115/230V; fully smoothed and fused. Output adjustable from 80 to 140V. D.C. at 400mA continuously, Dimensions: 174m. wide × 104m. deep x 34m. high p.p. 716. £2

3-RANGE MICRO-MILLIAMMETER



Basic movements 50μA D.C. M.C. Ranges of 50μA. 250μA and 1mA switched by a trigger switch in the back, geared with slidling scale having separate graduations for each range. Instrument is fitted with leads for soldering to test prods or crocodile clips (not supplied) 50/-

WESTINGHOUSE SELENIUM RECTIFIER POWER UNITS
Input 116/230V., fully smoothed and fused. Output adjustable from 80 to 140V. D.C. by means of fine and coarse tap switches in the secondary winding. Maximum current 400mA. continuous. Dimensions: 174 im. x 10 jin. deep x 3 jin. bigh. p.p. 7/6. 49/-

NEW FOREIGN MADE POCKET MULTIMETERS



Basio Movement 300µA. Sensitivity 1,000 µ/V. A.C. and D.C. Ranges: 10-00-250-500-1,000V. D.C. and A.C. 1-100-500mA. D.C. 25½/200K ohms. Accuracy: 3% FSD and D.C., 5% FSD on A.C. 10% on. Resistance scale. Dimensions: 5½in. × 3½in. × 2½in. Complete with test leads with prods and 1.5V cell, fully guaranteed 80/-

TERS

25-0-25µA D.C. MC 2jin. Rd. Fr. | 45/50µA D.C. MC 2jin. Rd. Fl. Panel Mtd. | 45/50µA D.C. MC 4jin. Rd. Fl. Panel Mtd. | 45/200µA D.C. MC 4jin. Rd. Fl. Mtd. | 81/200µA D.C. MC 2jin. Rd. Fl. Mtd. | 32/200µA D.C. MC 2jin. Rd. Fl. Mtd. | 35/200µA D.C. MC 2jin. Rd. Fl. Mtd. | 35/200µA D.C. MC 2jin. Rd. Fl. Mtd. | 35/200µA D.C. MC 2jin. Rd. Fl. Mtd. | 17/6
600-0-500µA D.C. MC 3jin. Rd. Fl. Mtd. | calibrated
000-0-500µA D.C. MC 3jin. Rd. Fl. Mtd. | calibrated
Western Electric | 22/Weston | 2jin. Rd. Fl. Mtd. | mounted in a
2jin. square steel box with test lead | 20/5 mA D.C. MC 2jin. Rd. Fl. Mtd. | 17/6
5 mA D.C. MC 2jin. Rd. Fl. Mtd. | 15/200 mA D.C. MC 2jin. Rd. Fl. Mtd. | 15/200 mA D.C. MC 2jin. Rd. Fl. Mtd. | 15/24 mps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 Amps. D.C. MC 2jin. Rd. Fl. Mtd. | 15/5-0-5 A **METERS**

REVERSIBLE 12 V. D.C. MINIATURE MOTORS

Power approx. 5 watts at 7,000 R.P.M. Dimensions 1 in. long × 1 in. dia. Shaft .077 in. dia. × 4 in. long. Centre of reversing switch integral with the motor. Self-iubricating sintered bronze bearings. PRICE, brand new, 15/6 post free.

21-point JONES PLUGS and SOCKETS (Standard Size), per pair. 7/6, p.p. 9d.

093/R160 174 9/- 616 9/- 616 9/- 616 9/- 616 9/- 616 9/- 616 9/- 616 9/- 617 5/- 617 6		
1	OD3/VR150 5T4 9/- 6L6 9/- 1A3 . 3/- 5V4G 9/- 6L6G 7/- 1A4 5/- 5V3G 9/- 6L7 . 5/- 1A14 5/- 5V3G 6/- 6L7 4/6 1L4 . 3/6 5Z3 . 7/- 6N7 . 6/- 1Q22 100/- 5Z4M 9/- 6N76 5/- 1R4 . 7/- 6A6 . 5/- 6Q7G 6/- 1R5 . 6/- 6A7 8/- 6R7 . 6/- 185 . 6/- 6AB4 5/- 68A7 6/- 1T4 . 5/- 6AB7 4/- 68A7GTY	128K7 4/- 703A 30/- 808 . 12/6 931A 60/- 4043 15/- 5702 15/- 60/- 4043 15/- 5702 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60/- 40/- 15/- 60
Sarage 2 Sarage 2	1V2 . 4/- 6AG5 3/6 68C7 7/- 2C26A 3/- 6AG7 6/- 68G7 6/- 2C26A 3/6 6AK6 5/- 68H7 4/- 2C34 4/6 6AL5 4/- 68J7 5/- 2C34 2/6 6AK6 5/- 68H7 5/- 2C34 40/- 6AG6 7/- 2C42 25/- 6AQ6 7/- 2C43 40/- 6AR6 5/6 6887 3/- 2C46 30/- 6AR6 5/6 6887 3/- 2C50 30/- 6AR6 5/6 6887 3/- 2C50 30/- 6AB6 7/- 2C50 30/- 6AB6 5/- 6K3 5/- 2C50 30/- 6AB6 5/- 6K3 5/- 2C50 30/- 6AB6 5/- 6K3 5/- 2C50 30/- 6AB6 5/- 2C2 2K2 4/- 6BB4 4/- 2K2 4/- 6BB4 4/- 3A5 5/- 6B7 6/- 6Z4 6/- 3A5 5/- 6B8 6/- 7A4 4/- 3B22 20/- 6B86 3/6 7AG7 5/-	Type dia. V _b V _{al} V _{a2} V _g Screen Defi. Focus Price 3ACP2 3in. 6.3 545V 2.000V 60V Gr. E8 E8 20/- 2AR1 2in. 6.3 250V 1.000V 60V Gr. E8 E8 25/- 5FF7 5in. 6.3 250V 7.000V 45 Gr/Y EM EM 12/6 5SF97* 5in. 6.3 3250V 7.000V 45 Gr/Y E8 E8 12/6 5SF97* 5in. 6.3 330 7.700V 45 Gr/Y E8 E8 140/- 7BF7 1in. 6.3 330 7.700V 45 Gr/Y E8 EM 45/- 7BF7 1in. 6.3 770 8.800V 70 Gr/Y EM EM 60/- 10UP21 10in. 6.3 770 18.000V 70 Y/R EM EM 60/- 12SF97* 12in. 6.3 500 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Y/R EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 70 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 770 18.000V 250 Gr/Y EM EM EM 60/- 12SF97* 12in. 6.3 1300V 270 Gr/Y EM
We have hundreds of other types in stock. Please send s.a.e. for current price list. Please add 2/6 in £ for packing and postage.	3B26 20/- 6BN6 7/- 7E5 5/- 3B29 30/- 6C4 2/6 7F7 6/- 3C45 30/- 6C4 2/6 7F7 6/- 3C45 30/- 6C4 4/- 7N7 5/- 3D5 4/- 6C56 7/- 7N7 6/- 3D21 30/- 6C4 10/- 11E2 20/- 3Q4 7/- 6F6 5/- 12A6 3/- 3S4 5/- 6F6 6/6 12AH7GT 3TF7 7/6 6660 2/8 4B32 40/- 6H6 1/8 12AH7GT 4B28 15/- 645 3/- 12AU7 6/- 4B28 15/- 645 3/- 12AU7 6/- 4E27 60/- 615G 3/- 12AU7 7/- 4E27 60/- 615G 3/- 12AU7 7/- 5B21 20/- 6K7 3/- 12DGT 3/- 5B/502A 6K7G 4/- 12DGT 3/- 5B/502A 9/- 12SH7 3/-	Packing and carriage 2/- in £ subject to a minimum of 2/6.

WE URGENTLY REQUIRE AND PAY HIGHEST PRICES FOR MODERN TEST EQUIPMENT (e.g., Signal Generators, Oscillators, Microwave Test Sets, etc.), COMMUNICATIONS RECEIVERS (especially U.H.F. and E.H.F. Ranges), AIRCRAFT RADIO COMMUNICATION AND RADIO NAVIGATION EQUIPMENT, SPECIAL VALVES, MAGNETRONS, KLYSTRONS, ETC.

EX A.M. RECEIVERS TYPE R-1359, HALLICRAFTER \$27C RECEIVER\$ (Range 130-210 Mc/s) AND UNMODIFIED BC-348 RECEIVER\$ REQUIRED IMMEDIATELY.

Z. & I. AERO SERVICES LTD.

RETAIL BRANCH: 85 TOTTENHAM COURT ROAD, W.2. Tel: LANgham 8403 Head Offices 14 SOUTH WHARF ROAD, LONDON, W.2. Tel: AMBassador 0151/2

Please send all correspondence and Mail Order to the Head Office

LUNDON CENTRAL RADIO STORES

TIME SWITCHES, VENNER. 8-day clockwork, 250 v. 1 A. Thoroughly reconditioned and guaranteed, 32/6 including post and packing.

10-WAY PRESS BUTTON INTER-COM TELE-PHONES, in Bakelite Case with junction box. Thoroughly overhauled. Guaranteed. £6/15/s—
DESK PHONES. Complete with Hand Set and Dial 0-9 in Bakelite Case. £3/12/6.

PROJECTION LAMPS, Pre-focus 100 v. 300 w. in new condition. 8/6. PROJECTION LAMPS, Pre-locus 100 v. 300 w. in new condition, 8(6, P.25 V.H.F. RECEIVERS in metal case. Weight 37 bs. Size approx. 21; x 9 x 6;in., 57/6. AVO UNIVERSAL TEST METERS. Reconditioned, as new. In periet working order. Model 22, £9/8/s. C.R. VISION UNITS complete with VCR97, Size approx. 21; x 9 x 6;in, in metal case, 37/6. HIGH-SPED ELECTRO-MAGNETIC COUNTERS. Ex-Govt. 0-9,999, 25/50 v.D.C. Size 4x1x1in. Single coil 2,300 g or single coil 200 g, 18/6. VENNER TIME SWITCHES. For switching on/off lighting and power. Reconditioned as new. In Ironclad cases, 10 amp., 75/-; 15 amp., 85/-; 20 amp., 25/5/-.

ironcial cases, 10 amp., 75/-; 15 amp., 85/-; 20 amp., 55/5/-.

ELEPHONE DIALS. 0-9. Suitable for inter-office and factor; installation. 17/8.

3-0-HM P.M. SPEAKERS. In good working order, 10in. 27/6; 8in. 9/6; 6in. 9/6; 5in. 11/6.

3-10. SYNCHRONOUS VIBRATORS. 2 v. 7 pin. 3/8.

ELECTRICITY SLOT METERS. (1/- in slot.) for A.C. mains. Fixed tartif to your requirements. Suitable for hotels, 6to. 10 A., 54/-; 15 A., 94/-; 20 A., 104/-.

Other amperages available. Reconditioned as new. 10 A., 42/8; 15 A., 52/6; 20 A., 57/6. Other amperages available. METERS. Reconditioned as new. 10 A., 42/8; 15 A., 52/6; 20 A., 57/6. Other amperages available. HIGH RESISTANCE EARPIECES. Double with 3tt. length of cord. 10/6 pair.

BALANCED ARMATURE HEADPHONES, with throat mikes, 9/6.

mikes, 9/6. ASSORTED RESISTANCES. Accuracy ±5%. 5/6

per 100.
TECHOMETERS. 0-3,500, 25/-, new and boxed.
THROAT MICROPHONES. 3/- each.
SOUND-POWERED HAND SETS. 17/8.

All prices include carriage

23 LISLE ST. (GER. 2969) LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday

RESISTANCE WIRES

EUREKA-CONSTANTAN

Most Gauges Available

NICKEL-CHROME

MANGANIN

COPPER WIRE

ENAMELLED. TINNED. LITZ. COTTON AND SILK COVERED SMALL ORDERS PROMPTLY DESPATCHED

B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets, EBONITE and BAKELITE PANELS.

TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS SEND STAMP FOR LIST TRADE SUPPLIED

POST RADIO SUPPLIES 33 Bourne Gardens, London, E.4

Phone: CLIssold 4688

- BARGAIN OFFER -

surplus

White Spot R.F. Transistors

at 4/6 each. POST FREE Our Component Lists for 3d. Stamp Money Back Guarantee on all Items

NEO MAIL ORDER SUPPLIES 2A MAXWELL RD., PORTSMOUTH POST PAID—GUT PRICE TOOLS
WHIT. OPEN END SPANNERS, drop forged and plated, set 6, \(\frac{1}{2} \) in. to \(\frac{1}{2} \) in., 13/6. POCKET
NEON TESTER, with retractable screwdriver, 5/-. 5in. SIDE CUTTERS, 5/6. 5in. PLATED
ROUND NOSE TAPERED PLIERS, 5/6.
7in. FLAT NOSE BOX JOINT TAPERED
PLIERS, 8/6. 7in. COMBINATION PLIERS, 6/-. TUB. HACKSAWS (Eclipse Type), 11/6.
H.S. TWIST DRILLS. Set 7, \(\frac{1}{2} \) in. to \(\frac{1}{2} \) in.
4/-. Full size in wallet, 6/-. Set of 13--9/6.
OUR FAMOUS TRANSFORMERS. Input
200/250. Output tapped 3 to 30 v. 2 a. or
tapped 5, 11, 17 v. \(\frac{1}{2} \) a Each 24/6. P.P.
F.W. METAL RECTIFIERS. 12/6 volt, 1 a.,
7/6; 3 a., 13/-; 4 a., 17/6; 6 a., 27/6; 24 v
2 a., 23/6.

TOGGLE SWITCHES DPDT 3/6. SP 1/9.
MICRO SWITCHES. Make and Break, 5/6.
MAINS TRANSFORMER AND RECTIFIER
giving 12 v. 1 a. D.C. Output. 19/6. P.P.
And with Output 30 v. 2 a., 33/6. P.P.
NICKEL NIFE BATTERIES. 1.2 volt 2.5
amp. Size 3x2\(\frac{1}{2} \times \) in. Practically everlasting, 6/- or 3 for 16/-. 4 for 21/-.

EX.W.D. MORSE KEY8. 3/6, 6/- and 8/6.
1,000 NEW S.T.G. FREQ. CRYSTALS. 10,555
k/c to 19,872 k/c 5/6 each. Lists available.
PAXOLIN TUBING. 1\(\frac{1}{2} \) in. O.D. \(\frac{1}{2} \) in. thick,
6ft lengths. 17/6 P.P. Ideal for aerial masts.
Stronger than steel. PAXOLIN PANELS
12×6\(\frac{1}{2} \) in. 3/6 P.P.
12 v. MINIATURE RELAYS. 1\(\frac{1}{2} \times \) 1/2 a.

WW. RHEOSTATS. 1 a, 2/6,
AMERICAN P.V.C. TAPE. Finest quality.
800ft. recis. 19/-.

12 v. MINIATURE RELAYS. 1\(\frac{1}{2} \times \) 1/2 a.

ON DOS STROWGER RELAYS. Open to ofers.
12 v. D.C. RELAYS. 2 make 6/-, 2 for 11/6.
Lists sent on request. All post paid.

THE POST PAID-CUT PRICE TOOLS WHIT. OPEN END SPANNERS, drop forged

THE

RADIO & ELECTRICAL MART P.O. BOX 9 G.P.O., TUNBRIDGE WELLS,

HARRINGAY SUPPLIES 345 HORNSEY ROAD, N.19



"F" TYPE

Complete in fitted case, portable, range up to 5 miles, suitable for factories, building sites, offices, etc., 2 complete sets-£6/10/-. Carr. 5/-.

RE-ENTRANT LOUD HAILERS Dia. 15in. Heavy Duty All Metal, new and unused, £8/10/-. Carr. 10/-.

SMALL MODEL MAKERS
MOTORS 24v. AC/DC.
Reduction geared, new. Size 1 in. x 1in. x 2 in. long, 12/6 each,



p/p 1/6. Other types of small 12 or 24 v. motors in stock.



TRANSFORMERS TRANSFORMERS 210/250 v in, 275-0-275 v, 50 mA 6.3 CT. 3 A. out, 17,6. 210/259 in, 300-0-300 v. 125mA 6.3 CT2.4 6.3 CT2. 4. out, 22/6. 220/240 v. in, 4 v. 6.34 A. Postage 3/- in the 21 on all.

Di., 4 v. 6.34 A. Pottage 3/- in the 21 on all.

Pots 10K, 10k Wire, 2.5K 2 m. 25K Lin and Log., 05/.25M 3/- each, post 6d. Tygan Fret 2/- ag. 12K Lin and Log., 05/.25M 3/- each, post 6d. Tygan Fret 2/- ag. 200/250 v. in, 110 v. 100 watt out 17/6, post 2/- 200/250 v. in, 110 v. 3.04 amps. out £4/10/-, post 5/- 200/250 v. in, 110 v. 3.04 amps. ag. 25/- 200/250 v. in, 110 v. 3.04 amps. 25/- 200/250 v. in, 100/120 DC out at 2.5 amp., £8/00.

**DISTRIBUTION BOARDS* 12*- x6* fitted with 200/300v. AC voil meter, two 15 amp luses, two 3 pin output sockets. 1

volt meter, two 15 amp fuses, two 3 pin output sockets, 1 mains input socket 18/6, post 3/6.

The VZ ELECTRICAL

METERS, we can supply and repair within 7-14 days; to B.S.89: Moving coil, moving iron, electrostatic, thermocouple, also multirange meters, meggers, pyrometers, etc.

AUDIO EQUIPMENT, we supply and repair: Tape recorders, amplifiers, tuners, etc.

Write or phone:

311 EDGWARE ROAD, LONDON, W.2

Phone: PADdington 4515.

MORSE CODE TRAINING Get your Radio Operator's Licence the easy way!

CANDLER has taught MORSE CODE by correspondence for

50 years.
On Land, Sea and in the Air and in every Continent, you will find first-class Radio Operators who have learnt their profession or excelled as Amateurs the CANDLER WAY. Write for the Candler "Book of Facts" without obligation and see for yourself how fascinating the Candler Method of teaching the Morse Code can prove.
as you learn You may if you wish pay

CANDLER SYSTEM (55W) 52b ABINGDON RD., LONDON, W.8 Candler System Co., Denver, Colorada, U.S.A.

USERS FIND THAT A.A. BENDERS HELP THEM TO COMPETE . . . SO WILL YOU



This UNIQUE BENDER

Quickly and Accurately Forms

Angles, Channels, Sections, Boxes, Lids, Trays, Chassis Brackets, Clamps, Clips, Shrouds, etc.

The RO-20 and RXX-26 are becoming "essential equipment" for Electronics, Radio, T.V. and General Research work. Many now prefer the RZ-26.

The RO-20 is similar in general design and finish to the RX-20 shown above, but is lighter and less expensive.

Obtainable only direct or through leading tool merchants.



Wireless World Classified Advertisements

. Rate 9/- for 2 lines or less and 4/6 for every additional one or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 cfo "Wireless World," Wireless World," to Discount details available on application. Press Day January 1801 issue, Tuesday, November 29th, 1990. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components and valves which may be offered for sale through our displayed or classified columns carry no manufacturers' guarantee: Many of these items will have been designed for special purposes making them unsuitable for civilian use, or many have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such items purchased.

NEW RECEIVERS & AMPLIFIERS

NEW RECEIVERS & AMPLIFIERS

THE world-famous "Globe King" kit; new and improved version; complete with all parts, chassis, coils and valve, together with "Easy-Build" charts and instructions; a highly efficient one valve short wave radio with band spread tuning; hundreds of testimonials. 79/6 Postage paid.

H.P. RADIO SERVICES, Ltd., 49-51, County Rd. Liverpool, 4. Estab. 1935. [0203 RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND

ECEIVERS A.R.88, excellent; from £35—LT. Solloman, Ltd., Beaufort St., Manchester, 3, Tel. Bia, 4571.

HRO Rx's, etc., AR88, CR100, BR1400, LG209, S640, etc., etc., in stock.—R. T. & London, E.11. Ley. 4986.

FOR sale, Marconi CR 100, adapted for 250V AC or 12V DC operation, complete and in good working order; £16/10.—H. R. Wilson, 18, Tower St., West Hartlepool. [9351]

NEW TEST EQUIPMENT

HEATHKITS can now be seen in London and processed on easy terms; free brochure.

HEATHKITS can now be seen in London and purchased on easy terms; free brochure— Direct TV Replacements, Ltd. Dept. W.W. 28/12, 138, Lewisham Way, S.E.14. Tideway 6666. 19240

HETERODYNE frequency meter, BC-221, 125Kc/s-20Mc/s. TS-174, 20Mc/s-250Mc/s. TS-175A, 85Mc/s-1,000Mc/s. Receiver-Indicators, APN-9A. Receivers, S-36A, 27Mc/s-145Mc/s. S-27CA, 125Mc/s-220Mc/s. APN-47R-4, 35Mc/s-4,000Mc/s. AB-88S, Eddystone 358X, 40Kc/s-32Mc/s; £16/10, etc.—R. V. Wright, 4a, Nepal Ave., Atherton, Manchester.

TEST EQUIPMENT—SURPLUS AND SECONDHAND

HARMONIC generator, frequency sub-stand-ard, 6 ranges, 100kc/s-50mcs. SANGAMO Weston frequency meter, 200 micro. amp., model 557, round flush mounting, mirrored 6in scale, SANGAMO Weston sub-standard milliampmeter. mirrored 6im Scale.

SANGAMO Weston sub-standard milliampmeter.
model S82.

EVERETT edgcumbe recording milliampmeter.
0-2 milliamp. type MSR.—Box 2334, [9339

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Service, Ashville Old Hall, Ashville Rd. London, E.11. Ley. 4986.

T630 terminal repeater, £12; Taylor 46A valve tester, £6; Taylor 45B valve tester, £6; Taylor 45B valve tester, £6; Taylor athern generator, £5; all carriage extra.—Founsiow Heath Electrical, Ltd., 375, Staines Rd., Hounslow, Midtx. [9338

TEST EQUIPMENT WANTED

WANTED, Mullard tr other modern valve generator; details.—Gilbert, £2, Leybourne Ave., Bournemouth.

NEW COMPONENTS

PLUGS and sockets.

MORE than 1,000,000 in stock, covering over 50 different ranges, British and American; stock list on application to—SASCO., Nutfield, Surrey. Tel. Redhill 5050.

LINE output transformers and scan coils for most makes, exact replacements from 457-new or 257- used, send s.a.e. for imm. quote. telephone orders sent same day c.o.d.—T.C.S., Ltd., 28, Brockley Cross, S.E.4. Tideway 5594, and at 112, Camberwell Rd., S.E.5. Rodney 7917.

7917.

COMPONENTS—SURPLUS AND
SECONDHAND


SEND for catalogue No. 14—500 illustrated items; 2/6 post free.—Arthur Sallis Radio Control, Ltd., 93 (c) North Rd., Brighton.

NEW GRAMOPHONE AND SOUND EQUIPMENT

GLASGOW.—Recorders bought, sold ex-changed, cameras, etc., exchanged for recorders or vice versa.—Victor Morris, 543. Argyle St., Glasgow, C.2.

look . . and hear the difference!

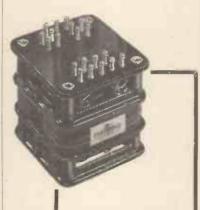A Partridge Transformer makes a world of difference to any equipment—you'll have noticed how many of the better designs specify Partridge. Make sure you're not missing anything. See your dealer today or post the coupon today for full details of the latest types.



Illustrated is a "C" Core Transformer recently developed for electronic equipment. Transformers of similar construction are available for High Fidelity reproduction.



To: Partridge Transformers Ltd., Roebuck Road, Chessington, Surrey.
I would like the latest Partridge Catalogue information.

ADDRESS.....

NEW GRAMOPHONE AND SOUND

THE cheapest in Britain.

COLLARO studio tape deck, £12.
TAPE amplifier, £10/10.
B.S.R. tape deck, £8/5.
COLLARO Junior four-speed turntable and pick-up, £3 conquest autochanger, £6/5.
B.S.R. UAB autochanger, £6/10.
ACOS microphone 40, 24/-. Satisfaction guaranteed.

anteed.
TRABE supplied.
S. BENJAMIN. 2, Prince Charles Avenue, BurySt. Edmunds, Suffolk.
Vortexion. Bre-

St. Edmunds, Suffolk. [9355]
TAPE recorders; Ferrograph, Vortexion, Brenell, Tlelefunken, Reflectograph, & Fl. Cord.
TAPE Decks: Wearlte, Brenell, Truvox, Bradmatic. Amplifiers & Tuners: Quad. Leak.
R.C.A., Dynatron, Duici & Chapman, Microphones: Resio. Lustraphone, Gramplan & Telerunken. All tapes & accessories. Specialists in Audio & Sound Recording.
HIRE purchase facilities available.
LAMBDA RECORD COMPANY, Ltd., 95, Liverpool Road, Liverpool. 23, Great Crosby 4012.

Gine-Vox disc recording mechanisms for L.P. or standard operation from 30gns.-156gns.; also complete tape-disc or direct channels from 50gns.-112gns.

DEMONSTRATIONS can be arranged in London.—For full details write to K.T.S., Ltd.. Coplow, Park Rd., Braunton, N. Devon. Callers by appointment only. Gillow.—For the better class tape recorders for industry, research, music and private use; Ferrograph, Brenell, etc.; complete recording service; music for industry, tape/disc.—31, Peel St., Eccles, Manchester. Eccles 1624, Studio Director Thurlow Smith, A.R.M.C.M. [0122] Director Thurlow Smith, A.R.M.C.M. [0122]

LEE ELECTRONICS. The Tape Recorder and High-Fidelity Specialists. 400. Edgware Rd., Paddington, W.2. have purchased the entire Audiomaster range of tape and high fidelity equipment, and these units are offered as follows:—Monaural Power Amplifier complete with pre-amplifier, chassis mounting, provision for direct tape connection and all types of pick-ups. 25watts output—one of the finest amplifiers of its kind available; listed £59/10—offered at £29/10, new and boxed; carriage 8/6. AUDIOMASTER Monaural tape adaptor—self-powered, separate record and playback amplifiers for 5 head monitoring; listed at £26—offered at £16, p. and p. 5/6. AUDIOMASTER Stereo Recording Amplifiers-self-powered, suitable for use with Telefunken, Marriott Miniffux, etc. stereo heads; listed at £33/15—offered at £19/10, p. and p. 3/6. FULL descriptive leaflets available on all above items.

items.
TRADE and export enquiries invited.
SEND for free lists of other bargain offers.

[9360]

CRAMOPHONE AND SOUND EQUIPMENT—
SURPLUS AND SECONDHAND
FERROGRAPH 4A/N, 6 months; £70; accessories avail., London inspection.—Box 2463,

RECORDING tape; save up to 30%; send for list; also 50 second-hand recorders in stock.

—E. O. Kingsley & Co., 132, Tottenham Court Rd., London, W.I. Eus. 6500. [0253]

GRAMPIAN neg. feedb'k cutter head (std. dand L.P.) type BI/B, £25; M.S. led disk recorder deck, 78 r.p.m. (without cutter head). £15.—Carter, 50, Bagham Rd., Bristol, 4.

SURPLUS equipment: Collaro transcription motor No. 2010; Goldring P.500 diamond stylus Collaro arm; Leak pre-amp, I valve; projection T.V., picture 4ft-4ft; excellent condition; reasonable ofter.—R. S. Langford, Beoley, Nr. Redditch, Worcs.

PRE-RECORDED tapes, all makes, 7½ and 3½ i.p.s., send for free lists or visit Teletape (Dept. TR5), 33, Edgware Rd.; W.2. Pad. 1942.

TAPE RECORDING, ETC.

ASK your dealer for American Ferrodynamics
"Brand Five" recording tapes; the best
tape value! [0258] RENDEZVOUS RECORDS offer comprehensive 78/LP tape to disc recording facilities:

—Leafiet from 19, Blackfriars St., Manchester, 3.

Chester, 3.

RAND new recording tape, 7in reels 1,800ft Long Play 31,-, 5\%in 1,200ft L/P 22,6, 5in 900ft L/P 17/6; other grades, 7in×1,200ft 16/6. 5\% x850ft 13/3, 5in×600ft 12,-; Super quality, 7in 19/3, 5\%in 15/3, 5in 13/9; P. & P. 1/- per reel.

EMPTY plastic reels, 7in 2/10, 5\%in 18/9; P. & P. 1/- per reel.

EMPTY plastic reels, 7in 2/10, 5\%in 2/8, 4in 2/8- ach; P. & P. paid.

GUARANTEED satisfaction.—A. Marshall & Son. Ltd., 18, Cricklewood B'way, London, N.W.2. Gladstone 0161/2.

Tape to disc recording microgroove LP, from 27/6, 45 rpm EP 20/-, 78 rpm 11/-; 48-hour return service; finest quality; s.a.c. for comprehensive leafiet to—A. D. Marsh ("Deroy" Sound Service), 52. Hest Bank Lane, Hest Bank, Lancaster. Tel. HB. 2444.

EXCLUSIVE OFFERS

*	Philips Electronic 5 digit Counters	£22	10
*	Erskine D.B. Oscilloscopes	£35	0
*	Murphy Pulse Amplitude Analyser	£275	0
*	E.M.I. Waveform Monitors	£185	0
*	Edwards Speedivac Pumps, 230 v. AC	£18	10
*	Mulrhead Ipots	£12	10
*	5it. P.O. Racks	£3	10
*	Dowty High Speed Registers	£6	0
de	Avo Geiger Counters	£12	10
*	American Teletype Tables	£4	0
*	50 watt Rack Mounting Power Amplifiers		
~	200/250 ♥. A.C.	£1	15
*	Precision Mains Filters	1	0/-
*	15 kVA Constant Current Transformers	£85	0
*	Trylon Lattice Ladder Towers, 50ft. high	£60	0
*	85ft. 25in. dia. Steel Tubular Masts	£50	0
*	R.201 Triple Diversity Receivers	£125	0
*	Ferranti 7 kVA Automatic Voltage		
	Regulators	£35	0
*		£35	0
*	Westinghouse 30 kV, 100 mA, Cabinet Rectifiers variable from 2 kV	£75	0
rk:		£8	0
*	DFG-20 Direction Finders	£22	10
*		£30	0
*	RCA 5-element Yagi Arrays, 420 Mc/s	£3	0
*	75ft. Plywood Masts, 9in. dia.	£35	0
4	RCA 25-watt Projector Speakers	£14	0
*		£185	0
*		2100	U
Tal.		£25	0
*	Standard Business Machines, Video type		
	Tape Recorders, 3in. tape	£250	0
*		£3	0
*		£ 6	0
*	E.H.T. Power Supply, 7,500 v. 3.5 amps.,	COFO	0
	in cubicle	£250	0
*	E.H.T. Power Supply, 1,600 v. 5 amps., in cubicle	£130	0
*	Sola 2 kW Constant Voltage Trans-	-200	3
-	formers	£16	0
*	300 Amp Ironelad T.P. Switch Fuses	£10	0
*	Airport Runway Floodlights 1 KW	£10	0

AERIEL EQUIPMENT. Whips, Beams and Microwave. Poles and Masts up to 150ft., 70 different types in stock.

RECEIVERS from 15 Kc/s to 650 Mc/s, 60 kinds

TRANSMITTERS, 50 types, Mobile and fixed, up to

CABINETS and RACKS. American and British, open and closed, 30 patterns from 12in.to 9ft.

POWER SUPPLIES. Over 100 varieties giving up to 30,000 volts from standard and off standard inputs. TRANSFORMERS. 300 patterns in stock of all sizes to 20 kVA for power and 5 kW for Radio, Audio and Modulation up to 2 kW also, lists available.

TELEGRAPH and TELEPHONE APPARATUS of all kinds include Printers and Perforators for Morse, 5, 6, 7 unit code also Transmitters and Converters and Carrier and Channeling equipment. Filters, Repeaters and Power supplies for all the above in British and American versions,

40-page List of over 1,000 items in stock available
—keep one by you,

RELAYS and CHOKES. 12 tons of American post-war just arrived—a pleasure to use and look at—usk for special list—others in stock include Miniature, Polarised Post Office, aircraft, Control and Starting Relays, Chokes, open and potted, vary from one inch mumetal to 100-amp. power types—list available.

NUCLEAR GEAR—includes Scalers, Counters, Registers, Ratemeters, Dosimeters, Probes, Monitors, etc. Special list on request.

TEST EQUIPMENT. 200 different items of British and American test gear and hundreds of types of Meters available.

We have a large quantity of " bits and pieces " we cannot list-please send us your requirements as we can probably help-all enquiries answered.

P. HARRIS

ORGANFORD -DORSET

WESTROURNE 85051

TAPE RECORDING, ETC.

TAPE RECORDING, ETC.

TAPE/DISC/TAPE transfer editing; Lopying; if quality and durability matter (especially with L.P. from your precious tapes), Consult Britain's oldest transfer service; new tape recorders supplied with a 2-year free service guarantee; latest American tape (25 to 25 per cent saving), 1.800ft., 35/-, now available.—Sound News Productions, 10, Clifford St., London, W.1. Reg. 2745.

VALVES valves at keen prices; send 1/- for all samples and list.—J. & A., Boxmakers, 75a, Godwin St., Bradford 1

A., Boxmakers, 75a, Godwin St., Bradford 1.

RECLAIMED valves, tested and perfect, huge stocks modern and obsolete, all one price, 5/- plus 6d postage each; delivery by return—tewis, 46, Woodford Ave., Gants Hill, Ilford. Essex. [9357]

Lewis, 46, Woodford Ave., Gants Hill, Indica, Essex.

SPARES, valves tubes, 1930-1960, guaranteed perfect, set-tested, ex-working equipment. Lots from £1. FOTs, Osc. Tr. Def. colls, etc., cheep. Tubes guaranteed 6 months, fitted free. Picture shown to callers. 9in, 30/-; 12in. 40/- 14in. 60/-; 17in, 70/-. Valves, 5,000 types stocked, EF50, SP61, 1/-; EF91. EB91, 646, 2/-; EF80, UF42, 6F1, 2011, 3/-; 10F1. 6V6, B36, KT61, 4/-; PCC84, PCF80, PL81, PL82, PY81, ECL80, PCL83, 6K25, 5/-; KT35c, 10F14, 10C1, UCH42, 6/-; EL38, KT36, U22, U35, U281, 76; PL38, PZ30, U24, 20F1, U25. 185BT 10/-; U801, 20F4, 27SU, U37, 12/6, Pre-war 4-, 5- and 7-pin, 5/- each. Postage 6d. "Constructor's Parcel," 3ib. assorted res cond., etc., from modern Tvs., 7/6; postage 2/6. Send s.a.e for list or with enquiries.—St. John's Radio. 156, St. John's Hill S.W 11. Bat. 9838. [9301]

VALVES WANTED

VALVES WANTED

DEW valves wanted any quantity, best cash prior by return.—Stan Willetts, 43, Spon Lane, West Bromwich, Staffs. Tel. Wes. 2392.

ALL types of valves, British or American, transmitting and receiving; keenest cash prices paid. What have you to offer?—Write or call Lowe Bros., 9a, Diana Place, Euston Rd. N.W.L. Tel Euston 1636-7. [9124]

WE purchase new valves old or modern types for eash; full details please, includ-ing price required, in your first letter.—Wal-tons Wireless Stores, 15, Church St., Wolver-hampton, Staffs,

CABINETS
ABSOLUTE bargain; Vitavox Kupschorn
cabinet; £16.—Enf. 2839. [9353]

WANTED. high quality low impedance mike, S.T.C. ball mike preferred, good price paid.—133. Station Rd., Cropston, Leleesterized

PROMPT cash offer for your surplus brand new valves, speakers, components, test instruments, etc.—R.H.S., 155. Swan Arcade, [0190

WANTED, all types of communications receivers and test equipment.—Details to R. T. & I. Service, Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [0163

URGENTLY wanted, manuals or instruction books, data, etc., on American or British Army, Navy or Air Force radio and electrical equipment.—Harris, 93, Wardour St., W.1. Army, Nav equipment. Gerrard

Army, Navy or Air Force radio and electrical equipment.—Harris, 93, Wardour St., W.I. Gerrard 2504.

Warnette, ex-Govt., surplus field telephone, metal cable drums and portable reclers, state diameter, type and price.—Civil Engineering Department (P.K.), University College, London, Gower St., W.C.I.

WANTED, good quality communication RYS tape recorders, test equipment, domestic radios, record players, amplifiers, valves, components, etc., estab. 18 years.—Call, send or phone Ger. 4638, Miller's Radio, 35a, Newport Court, Leleaster Square, W.C.2.

PROMPT cash for the purchase of surplus stocks of televisions, tape recorders, radios, amplifiers and domestic electrical appliances of every description, substantial funds available.—Spears 14, Watling St., Shudehill, Manchester. Blackfriars 9432 (5 lines). Bankers; Midland Bank, Ltd. [0216]

BOULTON'S OF BRADFORD.

LOUDSPEAKER, pressure unit, and microphone repairs, D.C.B. cone assemblies and field colin cartons, service and satisfaction guaranteed.—D. C. Boulton, 134, Thornton Rd., Bradford. 1, Tel. 22838.

MAINS transformers wound to any specifica-MOTOR rewinds and complete overhauls: first-class workmanship; fully guaranteed. F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel.

[0113 WE undertake the manufacture of transformers singly or in quantities to any specification; all work guaranteed for 12

months.
LADBROKE Transformer Co., Ltd., 820a,
Harrow Rd., London, N.W.10. Tel. Ladbroke Barrow Rd., London, 19222 0914, ARNSFORMERS.—Suppliers to B.B.C. I.T.A., and leading radio manufacturers, single or long runs, prompt delivery, home and export, rewinds to all makes.

FÖRREST TRANSFORMERS, Ltd., Shirley, 2433. 501141, Warwickshire. Telephone Shirley 2433. 15.000+ TO 25-UNITS

PLUS EXTREME NATURALNESS CRYSTAL CLEAR DETAIL ABSOLUTE SMOOTHNESS


MINUS UNDAMPED RESONANCES WHISKERS OR BOOM ADDED COLORATION

There's no mystery about all this! It's just what you will get from the new Duode 12E Sound Unit, which again proves Duode to be THE BEST GOOD SOUND INVESTMENT.

> INSIST on hearing a DUODE Details from :

DUODE LTD. 24, Dingwall Rd., Croydon, Surrey

More than meets the eve

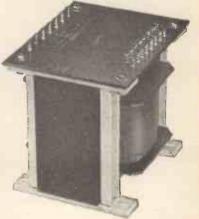

It looks good but there is more in it than meets the eye-enough to make the dis-cerning purchaser feel that he must have Savage Massicore regardless.

Generous design—no compromises on quality—conscientious workmanship—that is what you get when you buy a Massicore Transformer.



SAVAGE TRANSFORMERS LIMITED

NURSTEED ROAD, DEVIZES, WILTS.
Telephone: Devizes 932

EWIS have the CABINET for

EXTENSIVE RANGE OF CABINETS FROM £4-7-6



This beautifully designed Contemporary Cabinet can be supplied in Oak, Walnut or Mahogany veneer and has a waxed semi-matt finish. This cabinet can be fitted with any of the latest Hi-Fi units.



This elegant cabinet is available in veneered figured walnut and polished to a high gloss in a medium shade. Gold embellishments are an attractive feature of the design. 9in. black legs are normally fitted. A three sliding door system reveals cample storage room and space for equipment.

TWO NEW LEWIS CATALOGUI



The Cabinet Catalogue The Equipment Comparator Catalogue

(Designed to assist your choice of cabinet and equipment).
Please send me details of your two new catalogues

BLOCK CAPITALS PLEASE

LEWIS radio

100 CHASE SIDE, SOUTHGATE, N.14 Telephone: Palmers Green 3733

REPAIRS AND SERVICE

REPAIRS AND SERVICE

TRANSFORMERS to any specification.
Singles, rewinds, small or large batches;
quick and efficient service, competitive prices,
estimates by return of post from:
MESSRS, Newman & Son, 1. Grove Crescent,
South Woodford, E.18.

PEAKER repairs, comes fitted, fields and
clock coils wound, guaranteed satisfaction,
prompt service...L. S. Repair Services, Pluckley,
Ashford, Kent.

ELECTRICAL connectors.

MORE than 1,000,000 in stock, covering over 50 different ranges, British and American; stock list on application to—SASCO., Nutfield, Rednill, Surrey. Tel. Rednill 5050. [9224 805 s. neons; 850s, lamps, meters, condenses, sers, relays; s.a.e. lists.—Automaster, Haymarket, Birkenhead [9300

Haymarket, Birkenhead [9300

METALWORK, all types calinets, chassis, racks, etc., to your own specification, capacity available for small milling and capstan work up to lin bar milling and cap-philiportry METAL WORKS, Ltd., Chapman St., Loughborough. [0208

St., Loughborough.

CABLE, full or random coils, 10% to 20% under list prives; conduit, 5% to 10% under list; request new catalogue.—British Distributing, 591, Green Lanes, London, N.8. [9258]

HAVE you heard "CQ Serenade"? The radio amateur's own song! VE2QS crohestra and vocal on 2-sided 45rpm disc, 10/3.—G2HDU, 292, Hatherley Rd., Cheltenham.

DHOTOELECTRIC switches, transistorised, 60 or 12 volts, ideal parking light controller, burglar alarm, garage door opener, light saver; kit, £2/12/6; assembled, £2/17/6; mains model, kit, £4/12/6; assembled, £2/17/6; mains model, kit, £2/12/6; assembled, £2/17/6; mains model, kit, £4/12/6; assembled, £2/17/6; mains model, kit, £4/12/6; assembled, £2/17/6; mains model, kit, £2/12/6; assembled, £2/17/6; mains model, kit, £4/12/6; assembled, £2/17/6; mains model, kit, £4/12/6; assembled, £2/17/6; mains model, £4/12/6; assembled, £2/17/6; mains model, £4/12/6; mains model, £4/12/6; assembled, £2/17/6; mains model, £4/12/6; assembled, £4/17/6; mains model, £4/12/6; mains model, £4/12/6; assembled, £4/17/6; mains model, £4/12/6; assembled, £4/17/6; mains model, £4/17/6; assembled, £4/17/6; assembled, £4/17/6; mains model, £4/17/6; assembled, £4/17/6; mains model, £4/17/6; assembled, £4/17/6;

HIGHLY competitive quotations given for all your prototype and production requirements.—Newlyn Electronics, the Fracgan, Newlyn, Penzance. Tel. Penzance 2462. [9324 SERVICES WANTED MYONE interested in doing up a pre-war s.a.e. to J. Stanley Clarke, Forest Lodge, Sharpthorne, Sx. [0112

LOUIS NEWMARK, Ltd.

LEADING company in the design of auto pilots for helicopters are expanding their facilities at their development laboratories at Croydon and have the following vacancies to be filled

and have the following vacancies to be filled immediately ENGINEERS and Assistant Engineers with degree or E.N.O. and experience in the field of light electrical engineering, electronics, electromechanical devices or semi conductors, to work on the development, installation and flight testing of automatic pilots. Salary commensurate with experience. Pension scheme. Apply in writing, giving full particulars to: Personnel Officer, Louis, Newmark, Ltd., Prefect Works, Purley Way, Croydon, Surrey. [0333]

A SISTANTON & Co., Ltd.
MANUFACTURERS of high quality components for the Electronics Industry, are expanding their activities and wish to appoint an Assistant Chief Engineer; applicants should be graduates in Physics or Electrical Engineering and should have experience in the design and development of Electronic Components for Industrial applications; this is a staff appointment with superannuation scheme.—Applications to the Personnel Officer, Kingsthorpe, Northampton.

[9285]

TEST and prototype engineers.

WANTED by a Company of Industrial Electronic Engineers for work on building and testing a variety of novel industrial control units, knowledge of electronics, keenness, enthusiasm, and initiative of most importance.—Please send full details of experience, etc., and salary required to: Technical Director, Elcontrol Ltd., Wilbury Way, Hitchin, Herts [9352]


CENTRAL London firm requires competent organiser of postal and equipment sales. Age immaterial, refs. wanted, Part-time application considered.—Box 2462. (20133]

INSTRUCTOR wanted, one acquainted with Marconi marine equipment.—Write full particulars, including salary expected, Principal, Wireless College, Colwyn Bay. (2259)

Armstrong

HIGH QUALITY RADIOGRAM CHASSIS


STEREO 12 Mk. 2 42 GNS

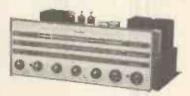

The most complete chassis ever produced, combining AM and FM Tuners, a Stereo Control Unit and two High Fidelity Amplifiers in one compact unit. Eight watts push-pull output from each amplifier provide a total of 16 watts for both mono and stereo. Other features include automatic frequency control on VHP; ferrite aerial, two IF stages and miniature tuning indicator for medium and long waves; inputs for tape recording, playback, pick-ups and stereo radio (should this come about); separate wide range bass and treble controls and balance control; booster units available for low output pick-ups; alternative matching for any loudspeakers.

STEREO 55

32 GNS

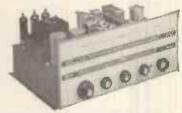

A junior version of the Stereo 12 Mk. 2 providing ten watts output, five watts from each amplifier and covering the VHF and medium wavebands. Ideal for a complete hi-fi system where the higher power output of the Stereo 12 Mk. 2 is not required. Like the Stereo 12 Mk. 2 it can be used for mono only and a second loudspeaker added at a later date.

JUBILEE Mk. 2

29 GNS

A hi-fi mono chassis giving eight watts push-pull output and covering VHF, medium and long bands. Tape recording and playback inputs.

AF 208

22 GNS

An AM/FM chassis providing 5 watts output and covering the full VHF and medium wave-bands. Tape recording and playback inputs.

							description		
or	call	at	our	Ho	llor	vay	showroo	m for	ful
den	nonstr	atio	72.	Ope	11 9	-5	including	Satura	lays.

NAME

ADDRESS

..... WDC

ARMSTRONG WIRELESS & CO. LTD. Warlters Road, London, N.7

Telephone: NORth 3213 -

COVENTRY RADIO LTD.

189/191 Dunstable Road, LUTON Audio & Component Specialists Est. 1925

If you are unable to visit us at Luton, send for a copy of our

HI-FI CATALOGUE

of 300 items 70 pages. Price 1/- plus 6d. postage.

JASON KITS Everest Portable Radio

£13/19/9-6 Transistor. £15/18/9-7 Transistor. Tuner FMT1 £5 5 0 Tuner FMT3 £9 19 Tuner Mercury 2 £10 14 Stereo Amplifier JSA2 £13 19 0 £12 19 0 Tuner JTV2K.... Tuner Argonaut AM/FM Tuner... £10 10 0 Tuner Argonaut Radio Receiver £11 11 0

LUTON'S HI-FI CENTRE

Telephone Luton 7388/9

M TANNOY N

The leading name in sound affairs

WEST NORWOOD SE27 Tel: Gipsy Hill 1131 (7 lines)



YOU are invited to apply for a copy of our illustrated brochure and price list which gives full details of our wide range of

OUARTZ CRYSTAL UNITS

which are renowned for their

Accuracy & Reliability

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. Works, Wellington Crescent, New Malden, Surrey.

Telephones: MALden 0334 & 2988

SITUATIONS VACANT ONDON COUNTY COUNCIL.

NORWOOD TECHNICAL COLLEGE, Knights NORWOOD TECHNICAL COLLEGE, Knights Hill, S.E.7?
REQUIRED Lecturer in Telecommunications and Electronics Department. The department conducts full-time courses in telecommunication and electronics, radio operating and radar; part-time courses additionally include radio, television and electronic servicing; television technology and other specialist subjects. THE lecturer would be required to conduct classes in one or more of the branches of study referred to, would be responsible for the continued development of suitable laboratory work, and would be given certain administrative duties.

study referred to, would be responsible to accontinued development of suitable laboratory work, and would be given certain administrative duties.

HIGH academic qualifications and/or good specialist knowledge or experience appropriate to the work of the department are looked for.

SALARY £1,408-£1,601. Commencing salary depending on experience.—Application forms from Principal (self-addressed envelope). Please quote (FESa/WW/2901/12). [9356]

THE MANCHESTER COLLEGE OF SCIENCE AND TECHNOLOGY.
A SENIOR technician, and a technician required to work with an important chemical research team, to devise, develop and operate electronic equipment vital to this research. RECOGNISED qualifications in electronics desirable but not essential provided good theoretical knowledge with industrial experience or HMF training offered.

SALARY scales: senior technician £700-£765 per annum; technician £450-£685 per emnum. SALARY additions payable for approved qualifications. 40-hour week. Superannuation scheme.

scheme.
APPLICATIONS with full details to—The Bursar, The Manchester College of Science and Technology, Sackville Street, Manchester, 1 CLOSING date: 3rd December, 1980.

CLOSING date: 3rd December, 1980. [9354]

ELECTRONICS, Engineers and Technicians.—
Opportunities in a growing manufacturing organisation in the Channel Islands.
TEKTRONIX, Inc.. in Guernsey, has an increasing need for both technical and non-technicial people; electronics engineers and technicial people; electronics engineers and technicians for test and calibration of laboratory type oscilloscopes as well as production engineering, material evaluation, repair, draughting and capacitor or transformer manufacture; non-electronics people for material control, silk screening, printing, metal finishing, machining and general office work.
WRITE to: Personnel Manager, Tektronix, Inc., Victoria Ave.. St. Sampsons, Guernsey, Channel Islands. Or Tel. Guernsey Central 3767-8.

A SSISTANT experimental officer for R.N. Engineering College, Manadon, Plymouth; unestablished post for duty as demonstrator in electrical engineering department to supervise laboratory work in electronics field. APPLICANTS should have relevant theoretical qualifications of at least H.N.C. level and practical experience to enable them to develop and instrument laboratory experiments. Starting pay £770 at age 26 or over by annual increments to £945 p.a.
APPLICATION forms obtainable from Commanding Officer. R.N. Engineering College, Manadon. Plymouth, should be returned by 30th December, 1960.

ELECTRONIC testers required by Tannoy Products, Ltd., sound equipment designers and engineers; good all-round knowledge and previous experience essential.—Apply, Tannoy Products, Ltd., Norwood Rd., S. 27. [9352] Froducts, Ltd., Norwood Rd., S.E.W. 1950a.

ELECTRONIC test engineer, required for testing oscilloscopes, etc., some experience of magnetic tape an advantage, salary commensurate with experience—Apply Sontranic. Ltd., 105. High St., Edgware, Middlesex. 19361.

RADIO mechanics.—Permanent and pensionable vacancies exist for young men experienced in the assembly, installation and
testing of HF and VHF telecommunications
equipment, preferably in connection with aviation ground services.
STAFF will be based at the Engineering Division of the Company, address below, but their
main duties will take place overseas for varying
periods installing telecommunications equipment. Whilst overseas a generous daily
allowance is pald.
EX-SERVICES personnel of fully skilled cate
gories are particularly welcome to apply.
APPLICATIONS to the Personnel Officer, International Aeradio, Ltd., Hayes Rd., Southall,
Middlesex.

IOSES

TASSAU. Bahamas.—Required as soon as

NASSAU, Bahamas.—Required as soon as possible radio, television and tape recorder technician for an important concern in the Bahamas; please apply with full details of experience and qualifications to.—Box 2033.

International Aeradio. Ltd., has periodic vacancles overseas for Radio Technicians, City ani Guilds Intermediate Telecoms. an advantage but not essential if applicant has considerable experience installation/maintenance H.F./V.H.F. low/medium power comms; Equipment; applications ex-service personnel of fully skilled categories welcomed; posts are permanent and pensionable; normally accommodation is provided with tax free emoluments equated to local conditions; additional marriage and child allowances; free air passages and insurance; kit allowance; generous U.K. leave; apply in writing.—Personnel Manager, 40, Park St., W.1 19313

radio masts and aerial equipment

As supplied to:

Government Dents.

Overseas Administrations.

Major Oil Companies.

Leading Manufacturers of Communications Equipment.

with TECHNICAL SERVICES for

Standard Tubular Steel Masts V.H.F. Installations Rhombics Dipoles Folded Dipoles Vertical Radiators 'T' Aerials, Single & Multiwire Transmission Line Equipment Terminating Resistance Units Lead-in Insulator Panels

Radial Earth Systems System Planning and Installation

12/6

15/--

9/6

60/-

20/-

22/-

15/6

24/-

5/-

5/-12/6

South Midlands Construction Limited ROMSEY RD., CADNAM, SOUTHAMPTON

AMERICAN COMPONENTS - VALVES TEST EQUIPMENT PHONE-WHITEHALL 4856 DALE ELECTRONICS

109 Jermyn Street, London S.W.1

MULLARD REFERENCE MANUAL of TRANSISTOR CIRCUITS

Postage I/-Using Transistors, by Sjobbema. Postage I/-
Tube and Semiconductor Selection Radio Handbook, by Editors and Engineers, 15th Ed. Postage 1/-
Surplus Radio Conversion Manuals, Vols. 1, 2 and 3. Postage 1/- Each Cubical Quad Antennae, by Orr. Postage I/- A to Z in Audio, new book by Briggs. to Z in Postage I/- e Amateur Building Radio

Station, by Berens. Postage I/- ...
R.S.G.B. Radio Amateur Call Book, Postage 6d.

The Oscilloscope Book, by Bradley.

Postage 6d.
Radio Tuners, F.M., A.M., and
Stereo, by Hartley. Postage 6d.
TV. Engineers Pocket Book, by
Hawker. Postage 9d.

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT STREET LONDON, W.C.2 (adjoining Lisle Street)

SOUTHERN RADIO'S SPECIAL BARGAINS TRANSMITTER - RECEIVER

TYPE 38 MK 11

WALKIE-TALKIE



Complete in Metal Carrying Case. 9in, x 6¼in, x 4in. Weight 6lb. Frequency 7.3 to 9 Mc/s. Five valves, £1/2/6. Post paid.

These TX-Rs are in NEW CONDITION, but owing

These TX-Rs are in NEW CONDITION, but owing to demand they are not tested by us and carry no guarantee, but should prove SERVICEABLE.

ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW. Headphones 15/6; Throat Microphones 4/6; Junction Boxes 2/6; Aerials, No. 1 2/6; No. 2 5/-; Webbing 4/-; Haversacks 5/-; Valves—A.R.P. 12 4/6; A.T.P.4 3/6; Set of FIVE VALVES 19/- the set. SPECIAL OFFER No. 2: "38," as above, complete with set of external attachments, 42/6, post paid.

SPECIAL OFFER No. 3:
Transmitter-Receiver "38" Mk. II. Brand new with complete set of external attachments including Webbing, Haversacks and Valves, 57/6 post paid. Fully guaranteed.

CONDENSERS. 100 assorted Mica; Tubular. etc., 15/-. NEW.

etc., 15/-, NEW.
CONTACTOR TIME SWITCHES.
pulses per sec., in case, II/6.
REMOTE CONTACTOR. For use

For use with

above, 7/6.

LUFBRA HOLE CUTTERS. Adjustable 2in.

to 34in. For Metal, Plastics, etc., 7/-.

MAGNETS. Strong Bar type, 2x 4in., 1/6 each.

MORSE TAPPERS. Midget type 2/9; 5tandard,
3/6; Heavy type on base, 5/6. ALL BRAND NEW.

MORSE PRACTICE SET. TAPPER with

BUZZER on base. Complete with battery, 12/6.

BRAND NEW.

PACKARD-BELL AMPLIFIERS. Complete. BRAND NEW, with valves, relay, etc., etc., 17/6

QUARTZ CRYSTALS. Types F.T.241 and QUARTZ CRYSTALS. Types F.T.241 and F.T.243. 2-pin 4in. spacing, Frequencies between 5,675 kc/s. and 8,650 kc/s. (F.T.243), 20 Mc/s. and 38.8 Mc/s. (F.T. 241, 54th Harmonic), 4/— each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/—. Holders for both types, 1/— each. Customers ordering 12 crystals can be supplied with lists of frequencies available for the control of the supplied with 15th 2000 frequencies available for the control of the supplied with 15th 2000 frequencies available for the control of the control of the control of the supplied with 15th 2000 frequencies available for the control of th

supplied with lists of frequencies available for their choice.

CRYSTAL CASES. 2-pin, 241/243, 10/6 per doz. RECORDING BLANKS. Brand new. "Emdisc." Ready for cutting. 13in. 6/- each or 15 complete in metal case, £4.

RESISTANCES. 100 assorted useful values. New wire end 12/6. NEW.

SPECIAL OFFER. 12 ASSORTED METERS. Slightly damaged. Mainly broken cases (perfect movements). Including 3 BRAND NEW Aircraft Instruments. 12 for 45/-.

STAR IDENTIFIERS. Type I A-N Covers both Hemispheres, 5/6.

both Hemispheres, 5/6.
TEST METERS D.C.
Ohms 0-6mA 0-1.5v and 3v. In case 3½in x 3½in x 2½in.
X2½in. Voltage range can easily be extended by

x 23in. Voltage range can easily be extended addition of resistances to suit individual requirements. BRAND NEW, 12/6.
ATTACHMENTS for "18" Transreceivers. ALL BRAND NEW. Headphones 15/6; Hand Microphone 12/6; Aerials 5/-; Set of 6 Valves

TRANSPARENT MAP CASES. Plastic 14in. x 103in. Ideal for Maps, Display, etc., 5/6. Post or carr. extra. Full list Radio Books, etc., 3d.

SOUTHERN RADIO SUPPLY. LTD.

11, LITTLE NEWPORT STREET, LONDON, W.C.2. GERrard 6653

SITUATIONS VACANT

ELECTRONICS engineers: Men or women with at least O.N.C. or equivalent experience to do final tests and inspection on a wide range of high accuracy instruments. These are permanent staff positions with pension fund and club room facilities.—Electronic Instruments, Ltd., Richmond 6434.

Instruments, Ltd., Richmond 6434, [0124]

ENGINEERS with some five years practical experience of radio frequency design work required for interesting new project in laboratory situated in South West outskirts of London. Some experience of cables an advantage, Pension scheme.—Write giving full particulars of experience and salary required to Box 1458.

RADIO and Radar technicians required to Box 1458.

RADIO and Radar technicians required for operation and maintenance of the radars, ground control and airborne radio equipment (including telemetry) associated with the operation of pliotiess aircraft.—Apply, stating experience, to: Short Brothers & Harland, Ltd.. The Aerodrome, Llanbedr, Merioneth

A.R.M.E. "A" licensed radio engineers, also radio and electrical mechanics urgently required for interesting work on light aircraft; knowledge of aircraft radio and electronics desirable but not essential.—Write, giving details of experience, to Radio Superintendent, Pressed Steel Co., Ltd., Aviation Division, Oxford Afrort, Kidlington, Oxford.

SERVICE Engineers.—Hilger & Watts have vacancies for Service Engineers for installation and testing of optical and electronic instruments; driving licence essential: applicants must be prepared to travel: 5-day week, canteen, superannuation.—Please write, quoting Ref. G.20, to the Personnel Officer, Hilger & Watts, Ltd., 98, St. Pancras Way, London, N.W.I. [9334]

Watts, Ltd., 98, St. Pancras way, Bolical N.W.1.

TEST engineers.—Applications are invited from test engineers with previous industrial experience of testing radio communications, receivers and transmitters; successful applicants will be offered positions on the company's permanent staff; starting salaries commensurate with qualifications and experience.—Apply in writing, giving full details, to Personnel Officer, Redifon, Ltd., Broomhill Rd., Sw.18.

INSTRUMENT manufacturer wishes to engage an electronic engineer to assist in the elegin of novel instruments; this is interesting estimated and demands a broad electronic experience to at least H.N.C. level; this expanding field will give excellent prospects and merit a good salary—Write in confidence to Managing Director/TM 32. De Grave, Short & Co., Ltd., Cray Valley Works, St. Mary Cray, Orpington, Kent. [9346]

CIRCUIT Designers and Circuit Laboratory Engineers required for design and testing of automatic telephone exchange systems and ther similar projects. Candidates should have had previous experience of this work and prerably have at least an O.N.C. or an intermediate grouped C. & G. certificate. Knowledge of Crossbar Switching or totalisators would be an advantage. Good salary paid to selected applicants. Pension scheme after qualifying period. WRITE giving full details of qualifications and experience to the Personnel Manager, Ericsson Telephones, Limited, Seeston, Nottingham, quoting Ref. DA/1.

Experience of the Telephones. Limited, Eeeston, Nottingham, quoting Ref. DA/1.

OVERSEAS. Electronic technicians are required by an oil exploration company with headquarters in the U.K. Men should be single on joining. Work will include the maintaining and operating of field equipment often under conditions of desert, jungle and swamp. The equivalent of an H.N.C., with practical experience in electronics, is essential. Tours overseas are of up to two years, followed by home leave.—Write with full particulars, covering any time spent in the Forces, to Box 2228.

CHIEF Technician (Electronics) required for work in university laboratory, having experience in the design and construction of electronic apparatus for research purposes; experience with pulse Circuits and/or V.H.F. and H.N.C. or equivalent would be an advantage; salary according to qualifications and experience in scale £825×25—£925 p.a., plus £45 London Weighting; superannuation scheme. APPLICATIONS as soon as possible to Dr. J. Lamb. Electrical Engineering Department, Imperial College, South Kensington, S.W.7.

[334]


FLECTRONICS.—Senior Technician required

Imperial College, South Kensinston, S.W.7

ELECTRONICS.—Senior Technician required for interesting and varied construction and service of a wide range of research equipment. Salary according to exprience of renge £630 to £740 p.a., plus £45 p.a. preence for renge £630 p.a.; cuperannuation scheme.—Apply in writing, stating age, present salary and previous experience, to Professor Ubbelonde, F.R.S. Department of Chemical Engineering and Chemical Technology. Imperial College of Science and Technology. London, S.W.7. [933]

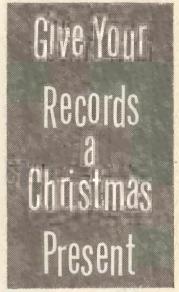ELECTRONIC Engineers.—Ekco Electronics and Technology of the control of the cont





It is vitally important that the stylus pressure should be correct when playing modern records. The Garrard Stylus Pressure Gauge has been designed to provide an inexpensive and simple method of measuring this pressure. The gauge is elegantly styled and has an easily readable scale visible through a clear plastic window. It is accurate through the entire scale, 0-12 grammes. Supplied complete with 5 gramme checking weight.

GARRARD STYLUS PRESSURE 19/6 INC. GAUGE MODEL SPG3



THE GARRARD ENGINEERING & MANUFACTURING CO. LTD. NEWCASTLE STREET, SWINDON, WILTS. TEL. SWINDON 5381 (5 Lines). TELEX 44-271

SOLDERING EQUIPMENT

(REGD TRADE MARK)

PRECISION INSTRUMENTS

Comprehensive range Robust and Reliable-Light weight - Rapid heating - Bit size 3/32 in. to 3/8 in. "PERMABIT" o Copper bits - All voltage ranges 6/7 v. to 230/250 v. - Prices from

ALSO

- CABLE PLASTIC STRIPPERS.
- MINIATURE SOLDER POTS.
- HEAT GUARDS.
- LONG LIFE BITS.

--- ADAMIN---

The The new range of micro-soldering instruments. Weights from 1 -oz. Bit dia. from \(\frac{1}{2}\)-oz. Bit dia. 1/32in. Have you had details?

Brochure \$5 on request from the sole proprietors and manufacturers with 28 years' experience in this years field.

LIGHT SOLDERING DEVELOPMENTS LTD. 28 Sydenham Road, Croydon, Surrey Grams: Litesold Croydon Phone: CROydon 8589

METERS

All makes of Single and instruments Multi-range instruments repaired and recalibrated.

Prompt Service All work guaranteed Priority for urgent



NEW RANGE OF METERS 2 1 TO 5" SCALED TO REQUIREMENTS. DELIVERY 10-14 DAYS

E.I.R. INSTRUMENTS LIMITED 329 Kilburn Lane, London, W.9 Tel: LAD 4168

HAS YOUR T.V. TUBE LOST ITS SPARKLE? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE

Pat. pending. Any Tube size. Reg. designs.

PRICE 35/-

Package and Postage 2/6. (Postal Orders) C.W.O. (Posta C.O.D

- No Soldering.
 No Wiring.
 Just Plug In.



SITUATIONS VACANT

PRODUCTION assistant, O.N.C. (Elect.); duties will cover general production problems with a bias to test and inspection; interesting and progressive post for energetic and capable man.—Write: Daly (Condensers), Ltd., West Lodge Works, The Green, Ealing, W.5. Eal. 3127.

man.—Write: Daly (Condensers), Ltd., West Lodge Works, The Green, Ealling, W.5. Eal. 3127.

MEN with knowledge of basic principles of M. Radio and Radar required in the Meteorological Office, after short initial training, those appointed will maintain and operate radio and radar equipment, including facsimile apparatus, there are vacancies in various localities in the United Kingdom and opportunities to serve overseas; starting salary for Radio (Meteorological) Technicians is £670 (national) at 25 or over, rising annually to £795 subject to deduction for each year below the age of 25, these rates are subject to a small deduction at certain provincial stations and to a small increase in London; good promotion prospects and allowances for overtime, night duty, etc., applicants must be British subjects.—Applications to Meteorological Office (M.O.10 R/M/T). Victory House, London, W.C.2, or any employment exchange quoting Kings Cross 3208. [9348]

MINISTRY OF AVIATION require electrical engineers as assistant signals officers. Duties include planning, evaluation, installation and supervision of operation and maintenance of civil aviation telecommunications and navigational aids at airports and telecommunication centres. Quals: 1st or 2nd Class Hons. degree in Physics or Engineering, A.M.I.E.E. or A.F.R.A.E.S. or equivalent, or of high professional attainment without these quals. considered. Salary Scale: £690 (at age 23) to £1,300. Slightly lower for women and for posts outside London. Promotion prospects.—Purther details and forms from Ministry of Labour, Technical and Scientific Register (K), 26, King St., London, S.W.I. quoting D.161/0A.

NATIONAL Physical Laboratory, Ted6(335). NationAll Physical Laboratory, Ted6(361). Physics of Applications of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of Application of A

26, King St., London, S.W.1. quoting D.161/0A.

[0315]

National Physical Laboratory, Teddington, Middx, require Senior Scientific Officers/S.O.s in Acoustics Section of Applied Physics Divn.; (a) to investigate methods of note measurement, supervision of measurements in field and control of subjective listening experiments, experience in statistics, applied psychology, or electronics useful; (b) to improve standards of instrumentation of sound measurement at audio-frequencies, classical physicist with interest in required conditions of instrumentation of sound measurement at audio-frequencies, classical physicist with interest in second class home selectronics of the property of interest of instrumentation of sound measurement at audio-frequencies, classical physicist with interest in second class home selectronics with interest in conditions of instrumentation of instrumentation of sound measurement at audio-frequencies, classical physicist with interest in the second class home selectronics with the property of instrumentation of instrumen

Ex B.B.C. engineer (49), wide experience available U.K. or overseas.—Box 2094. [9321]

TECHNICAL TRAINING

RADIO and television servicing.

HOME-STUDY courses with special schemes of practical work are available from the Pembridge College (1) Introductory course for beginners. (2) More advanced course covering new R.T.E.B. Intermediate Certificate. (3) Advanced course covering R.T.E.B. Final Certificate (in preparation). DETAILS from: The Pembridge College of Electronics, 34A, Hereford Rd., London, W.2.

TRAINING in radio and television servicing.

NEXT full-time one-year course commences on January 3rd. Recognised by R.T.E.B. for new radio and television servicing certificate examinations.—Details from: The Pembridge College of Electronics, 34A, Hereford Rd., London, W.Z.

L EARN Radio and Electronics the New Prac-tical Wayl Very latest system of experi-menting with and building radio apparatus— "as you learn "—Free brochure from Dept. W.W.10. Radiostructor, 40, Russell Street, Reading, Berks.

CITY & GUILDS (electrical, etc.) on "No Pass—No Fee" terms, over 95% successes.—For details of modern courses in all branches of electrical engineering, applied electronics, automation, etc., send for our 148-page Handbook—free and post free.—B.I.E.T. (Dept. 588A), 29. Wright's Lane, London, W.S. [0017

STUDY radio, television and electronics with the world's largest home study organization; Britling. E.; City & Guilds; R.T.E.B., etc.; also practical courses with equipment; no books to buy.—Write for free pospectus, stating subject to I.C.I. Intertext House, Parkgate Rd., (Dept. 412), London, S.W.11.

No Wiring.

Just Plug In.

It's Automatic.

It's Guaranteed!

Do it Yourself, 10 Seconds' Work. Sinclair Electronics introduce the first series-wired plug-in booster unit for all makes of TV sets.

Waen ordering state make of set, model No. and type of tube

If returned in seven days money refunded.

SINCLAIR ELECTRONICS (1)

33 Berwick Street, Oxford Street, London, W1.

(10559

TUITION

TUITION

FULL-TIME courses for P.M.G. Certificates. Call.I., Telecommunications and Radar Randineance Certificates.—Information from College of Technology, Hull.

[0559

TUITION

TUITION

TV and Radio—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc., on "No Pass —No Fee" terms, over 95% successes.—For freducible of exams, and home training courses (including practical apparatus) in all branches of radio, TV and electronics, write for 148-page Handbook—free—B.I.E.T. (Dept. 397A), 29. Wright's Lane, London, W.8.

USING TRANSISTORS

Phillips' Technical Library. by D. J. W. Sjobbema

Postage 8d.

TOR CIRCUITS. By Mullard. 12/6. Postage I/-.

THYRATRONS. By C. M. Swenne. 15/-. Postage 6d.

ASIC SYNCHROS AND SERVO-MECHANISMS. 2 vols. 16/- each. Post-BASIC age 1/3.

SERVOMECHANISMS. By P. L. Taylor. 42/-. Postage 1/3.

TELE-COMMUNICATIONS PRINCI-PLES (IN M.K.S. UNITS). By R. N. Renton. 45/-. Postage 2/-.

TRANSISTOR PROJECTS. A Gernsback

Lib Pub. 23/-. Postage I/-.
THE RADIO AMATEUR'S HAND-BOOK 1960. By A. R. R. L. 32/6. Postage

ELECTRONIC MUSICAL INSTRU-MENTS. By R. H. Dorf. 60/-, Postage I/-. RADIO VALVE DATA. 6th Ed. Compiled by "W.W." 5/-. Postage 9d.

Complete Catalogue 1/-.

MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books

19-21 PRAED STREET, LONDON, W.2.

Phone: PADdington 4185 Open 6 days 9-6 p.m.

New HI-FI items at WEBB'S

The WORDEN pick-up arm, a new approach to a "knotty" problem £12 12

The SME arm, the ultimate in precision, model "3009"..... £25 0 0
The "All Balance" pick-up arm, precision at a reasonable price £13 4 3

WEBB'S RADIO

14 Soho Street, Oxford Street, London, W.I. Tel: GERrard 2089/7308 Shop Hours 9-5.30 (Thurs. 7 p.m.) Sats. 9-1 p.m.





1910-Jubilee Year-1960 COMPONENT DISTRIBUTORS

Guaranteed components-

made specially for us:-1% tol SILVER MICA CAPACITORS 84 standard values always in stock, 5-1000pF 9d. 2200-3000pF 1/3 1200-2000pF 3300-5000pF P.V.C. COV'D ELECTROLYTIC CAPACITORS Blas 1/8 to 2/8. Smoothing 1/7; to 3/3 Dual 4/3 to 6/-. Full List No. 16. 1jin. dia. CAN TYPES 350/500V. from 4/-

11 in. dia. POTENTIOMETERS 2in. shaft 10K, 25K, 50K, 100K (linear), 250K, 500K 1M, 2M (log.) 3/-. With switch 4/6.

MINIATURE MAINS TRANSFORMER Pri. 0-200-220-240 v. Sec. 250 v. 40 mA., 6.3 v. 1.5 amp Stack size 21 x 11 x 11 in., 14/6.

CELLULOSE WADDING for resonance damping, 40 ply 36in. wide, 5 yd. roll 18/-, post 3/-. Sole distributors for this area.

IMPORTED HIGH STABILITY RESISTORS Miniature half-watt 5% "Preferred value" range (144 values—12 to 10ΜΩ). Very popular line 6d. ea. WIMA "TROPYDUR" PAPER CAPACITORS

Flat oval shape. Small size. Glazed surface. tol. 250V 20% 6d. 20% 6d. 20% 8d. 20% 8d. 20% 9d. 20% 9d. 20% 10d. tol. 250V 500V 10% 1/1 1/2 10% 1/3 1/4 mfd 250v 6d. 6d. 8d. 9d. 9d. 10d. .15 .015 25 10% 1/3 1/4 .033 .83 10% 1/4 1/6 .047 .47 10% 1/6 1/9

2/1 "SURPLUS" HIGH STABILITY RESISTORS
Best makes. Largest selection available. 145 stands
values plus many others.

5% ½W. 7½d. ½W. 9d. 1W. 10½d. 2% ½W. 10d. ½W. 1/- 1W. 1/3 1W. 1/3 1W. 1/4 1W.

AND, OF COURSE, OUR OWN PRODUCTS Precision-made ALUMINUM **BLANK CHASSIS**

Commercial quality, half-hard 16 s.w.g. Same day service. ANY SIZE to nearest 1/16in. 2, 3 or 4 sided.

Max. length 17in., depth 4in.

Specials death with promptly. 4in., 4in. or 4in. flanges (inside or outside). 6d. each extra.

Riveted or soldered corners 6d. each extra.

Price Guide (normal chassis only):—

Total area of material including waste:
48 sq. in. 4i30 sq. in. 5i208 sq. in. 9i308 sq. in. 5i208 sq. in. 9i308 sq. in. 12i240 sq. in. 10i368 sq. in. 14ipost 1/3
post 1/3
post 1/3
post 1/3
Quantity and trade discounts, Finishes arranged for quantities of 25 or over.

Any size up to 3ft. at 4/6 sq. ft.

Postage (sq. in. 1.90 stage (sq. in. 1.432 1/9; 576 2i-,

THE WELL-KNOWN

COOPER-SMITH HI-FI AMPLIFIERS

Each the best in its class-

yet you can build it yourself! KIT BUILT STEREO Control Unit ... £12 12 0 £15 0 0
STEREO Main Amplifier ... £13 13 0 £16 0 0
MK, II Control Unit ... £7 17 6 £10 17 6
B.P.I. Main Amp. 10/12 W. £12 5 0 £14 5 0
20 W. Power Amplifier ... £21 15 0 £24 0 0
"PRODIGY"6/9W.Integrated £12 10 0 £15 15 0 "BANTAM"3/4W.Integrated £7 10 0
Building instructions 2/6 each.
(Bantam 1/6, 20 w. 5/-). 0 £8

Please add postage for all orders under £2

H. L. SMITH & CO. LTD

287/289 EDGWARE ROAD, LONDON, W.2 Telephone Paddington 5891/7595

TUITION

FIND TV set troubles in minutes from that great book. The Principles of TV Receiver Servicing. 10/6, all book houses and radio who esalers.—If not in stock from Secretary, I.P.R.E., 20 Fairfield Rd., London, N.8, 10089 FREE from the I.P.R.E. Syllabus of famous Vadio and TV courses; membership conditions booklet, I/-; sample copy The Prac. Radio Engineer. 2/- post free.—Secretary, 20, Fairfield Ed., London, N.8. [0088] WIRELESS.—See the World as a radio officer in the Merchant Navy; short training period, low fees scholarships, etc., available boarding and day students; stamp for prospectus.—Wireless College. Colwyn Ray. [0018] ADIO and TV servicing, all aspects from Pablic and Pablic

"HOW and Why" of Radio and Electronics made easy by a new, no-maths, Practical way, Postal instructions based on hosts of experiments and equipment buildings carried out as home. New Courses bring enjoyment as well as home. New Courses bring enjoyment as well brochure from Den Waylanns subject.—Free brochure from Den Waylanns subject.—Free Bussell Street, Reading, Berks, Radiostructor Russell Street, Reading, Berks, Radiostructor & Guilds, G.C.E., etc., bring high pay and security: "No Pass-No Fee" terms; over 95% successes—For details of exams. and courses in all branches of engineering, building, electronics, etc., write for 148-page Handbook—free.—B.L.E.T. (Dept. 387B), 29, Wright's Lane, London, W.8.

PATENTS
THE proprietor of British Patent No. 750436, entitled "Radio Navigation System," offers same for licence or otherwise to ensure practical working in Great Britain.—Inquiries to Singer, Stern & Carlberg, 140, So. Dearborn St., Chicago 3, Ill., U.S.A. [0261]

t., Chicago 3, Ill., U.S.A.

BOOKS, INSTRUCTIONS, ETC.

WIRELESS WORLDS," 1949-59, total 111
copies, mint condition: 50/- Uplands
[9528] 7879.
"VIRELESS WORLD" 1945-1960 almost complete; offers.—Martin, 109, Park Teddington, Middx, Teddington, Middx, Teddington, Middx, Teddington, Middx, Teddington, Technician Dooks; Telecomm Principles A and B, 946, p.f.—Riddiford, 384 Tilehurst Rd., Reading, Berks, 1945.

HOW to use ex-Gov. lenses and prisms. Nos 1 & 2, 2/6 ea.; lists free for s.a.e.—H. W English, 469, Rayleigh Rd. Hutton, Brentwood English, 469, Rayleigh Rd... Hutton, Brentwood.

SELL by post—receive cash by post! Learn
mai crder trading, unlimited trade expansion; Mailmethods Manual shows how; details,
s.a.e.—Mailmethods (M.15) Co., 170, Old
Christchurch Rd., Bournemouth. [9330]

DIGITAL COMPUTATORS

Resulting from continued expansion in the computer field, a number of vacancies have arisen for

Graduate Electronic Engineers and for Technicians of O.N.C. standard.

The additional staff are needed for technical supervision and mainten-ance of Digital Computer Installations.

Vacancies exist in London and Birmingham, Manchester and Hull.

Training will be provided for this interesting work and there are opportunities for rapid promotion to positions of responsibility. Salaries are generous and in proportion to ability.

Please write to Personnel Manager THE NATIONAL CASH REGISTER CO. LTD., 206-216 Marylebone Road, London, N.W.1.

Grampian SOUND EQUIPMENT

GRAMPIAN REPRODUCERS LIMITED Hanworth Trading Estate, Feltham, Middx.
Telephone FELtham 2657 EQUIPMENT, ENCLOSURES AND CABINETS BY

STAMFORD
Specialising in Enciosures for OOODMAN SPEAKERS.
Built to the specifications in Goodmans Manual, 1960.
SPEAKERS SUPPLIED. Prices shown under EQUIP-

Shelf Mount-S.53, Shelf Mounting Enolosure 26 in. Mulde, 14 in. high, 12 in. deep. For the 10 in. Axiom No. 110 and No. 112 speakers. Price Sci 12 in. Speakers. Price Sci 12 in. Speakers. 26 in. Speakers. speakers. Price £8/19/6 or 36/-deposit and 9 payments 17/3 nithly.





S.52. The New Exponential Forn Enclosure for the Triaxiette as demonstrated at the recent Radio Show. 29in. high, 23in. wide. Panels. Top size 22in.x Panels. 10p size
32in. wide, useful as a TV
table or bookshelf. Price Price £14/18/6 or 59/9 deposit and 9 payments 28/6 mthly.

S.51. Corner Enciosure in three sizes. (a) For Axiette. Price £10/18/8 or 43/8 deposit and 9 payments 20/11 monthly.

(b) For Axiom 110 and 112. Price £13/13/- or 54/8 deposit and 9 payments £26/1 monthly. (c) For Axiom 300 or the 3 Way system including ARU No. 172. Price £17/15/3 or 71/- deposit & 9 payments 34/- monthly. 9.51. Corner Enclosure

				14.1			
EQUIPMENT SPEAKERS	Ca	sh P	rice d.		posi		urchase 8 Mths.
Goodmans Axiette			ï		6	5	6/4
This seath a		10	Ö	0 .	14	ő	12/10
	15		ő	1 .	0	0	4/10
" Axiom 110	9	0	Ň	1		0	8/2
" Axiom 112	1 3	10	9	1 :	14	0 2	
" Axiom 300			à	2	5	2	10/10
" Midax 650		10	0	1.			9/1
Wharfedale 8/145				1	8	0	6/8
Golden F.S.B.			7	-1	13		8/-
WHITLEY WB HF101	6 7	12	4	1	10	6	7/6
MOTORS							
Garrard 210			5	2	10		12/3
, 4 HF (Mone)					14		17/9
, TK Mk. II	- 8	10	0	1			8/2
310 Strobe	23	18	4	4	15	8	23/-
AMPLIFIERS							
Leak 20 & Control	51	9	0	10	- 5	10	49/5
Leak TL/12 plus ditto			ŏ	6			30/3
Rogers Junior ditto			ŏ	5	12	ō	26/11
2 Quad II & Quad 22		ŏ	ŏ	14	0	ŏ	67/2
TUNERS			-		_		0 87 80
Leak Troughline II	22	15	0	a	15	0	32/6
Quad FM			6	5	15	6	27/8
	60	71	0	9	10	0	6110
CHASSIS	200	0	^	0	-	10	29/3
Armstrong Jubilee	44	9	0	6			42/4
" Stereo 12	44	2	U	8	16	5	4214



5.8/E
47in. wide, 111 record storage on left, Deck size
34in. X16in. with 4in. clearance, also supplied with full length
deck, with record storage omitted. Price £22 or 88/deposit and 9 payments 42/1 monthly.

Write for lists for Equipment. Cabinets and Enclosures. We Specialise in supplying any equipment currently available. Demonstrations at our Weymouth Terrace Showroom. Our Products are supplied in oak walnut and mahogany veneers finished in shade required. Delivery 12/6 England and Wales. 25/- Scotland.

Visit our Hi-Fidelity Showrooms at:
84/86/98 Weymouth Terrace, off Hackney Road, LONDON,
E.2.
Showroom hours: Monday-Saturday, 9,30 to 5,30,
Late night Wednesday, 7 p.m.
Directions: No. 6 bus from Liverpool Street Station to
the Odeon, Hackney Road, walk back two turnings.
A. L. STAMFORD LTD., (DEPT. F4.)

NEW

Guarantee

MICRO-FINE

ALUMINISED

NEW SILVER

SCREEN

NEW

TAKES **SERIES** HEADACHES OUT OF ALL SERVICING PROBLEMS!



Pin-Point

TV troubles in 10 minutes

Find the exact sound or picture trouble in ANY TV set from 700 possibilities! Latest edition now has 332 pages of solid TV

servicing information; 300 diagrams, check chartsl 31/6. Postage 1/-.

SPECIAL OFFER

Circle Book No. 1 on coupon, send only 16/3 after 7 days, and 16/3 in 30 days, making a total of 32/6 including postage.

Pin-Point **Transistor** troubles in 12 minutes





Simple Check Chart System Saves Time

These amazing practical handbooks with an ENTIRELY NEW METHOD

show you how to find the trouble in ANY TV, or transistor circuit FAST! Index tells you where to look; famous Check-Charts help you to pin-point the exact trouble in minutes! These on the job books quickly a minutes! on the job books quickly pay for themselves in profitable new business and valuable time saved!

TRY ANY FOUR BOOKS ON NO RISK FREE TRIAL OFFER

No. 3. Application of Radio and T.V.	
Principles, 299 pages.	26/-
No. 4. Radio, Television and F.M.	
Receivers. 403 pages	26/-
No. 5. Radio & T.V. Circuits. 334 pages	26/-
No. 6. Latest Instruments for servicing	
Radio-T.V. 367 pages	26/-
No. 7. Practical Television Servicing	
and Trouble Shooting Manual. 406 pages	34/-
No. 8. Televison Servicing Cyclopedia.	
868 pages	47/
No. 9. Transistor Circuits. 410 pages	39/1
No. 10. Coyne Technical Dictionary	16/-
No. 11. Television and Radio Handbook	22/

SEND NO MONEY USE TIME PAYMENT PLAN AT NO EXTRA COST IF YOU WISH

Just mail coupon for free trial. After 7 days send only low price or return books and pay nothing! If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum four books). To buy one book send one half in 7 days, one half in 30 days.

MAIL COUPON NOW FOR FAST RETURN SERVICE

SIM-TECH BOOK COMPANY,

Mail Order Division, DEPT. W.3, Gaters Mill, West-End, Southampton, Hants. Rush the books circled below for 7-day FREE TRIAL

	per											
1	2	3	4	5	6	7	8	-9	10	11		
Na	me										 	

Address City..... County.....

Fick here if enclosing full price, we pay postage. Same 7 day money-back guarantee.

Postage £2 or less 1/-, £3 or more 1/6d.

OVERSEAS ORDERS, PLEASE PAY FULL AMOUNT MONEY BACK GUARANTEE IF NOT SATISFIED

EXACT PLUG-IN REPLACEMENTS ALL makes and all types

from stock 12" - - £4-15-0

- £5- 5-0

£5-15-0 15"-17" COD or CWO. Carriage and Ins. 7/6.

10/- GLADLY REFUNDED ON 14", 15", 17" SIZES YOU RETURN YOUR OLD TUBE.

All materials and components used in the manufacture of these Tubes are completely new except the glass savelope which prior to manufacture was carefully inspected to meet the standard of the original new

FACTORY REPROCESSED AND

LAWSON TUBES

156 PICKERSLEIGHS ROAD MALVERN, WORCS, MAL, 3798

COMPLETELY AS

12 months' new tube

NEW GETTERS

RE-GRAPHITED

FITTED NEW MULLARD MAZDA EMISCOPE ETC.,

ELECTRON

DAMAGED METER?

Have it repaired by Glasers Reduce overheads by having your damaged Electrical Measuring Instruments repaired by L. Glaser & Co. Ltd.



We specialise in the repair of all types and makes of Voltmeters Ammeters, Microammeters, Multrange Test Mitters, Electrical Thermometers, Recording Instruments, etc.

Government beartments, we are the leading Electrical instrument Repairers in the Industry. For prompt estimate and speedy delivery send defective instrument Repairers were be industry. For prompt estimate and speedy delivery send defective instrument by registered post, or write to Dept. W.W.

L. GLASER & CO. LTD.

98-100, Aldersgate Street, London, E.C.L. Tel.: Monarch 6822



The finest method for cleaning records

Already over 200,000 enthusiastic users

"Dust Bua" AUTOMATIC GRAMOPHONE RECORD CLEANER PATENT No. 817,599

Price reduced to 17/6 (plus 5/10 purchase tax)

from your local dealer or

CECIL E. WATTS LTD.

Consultant and Engineer (Sound Recording and Reproduction) Darby House, SUNBURY-on-THAMES, MIDDX

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE ROD, BAR, SHEET, TUBE, STRIP, WIRE 3,000 STANDARD STOCK SIZES

No Quantity too small. List on Application. H. ROLLET & Co., Ltd.

5 Chesham Place, S.W.1. BELgravia 4300 ALSO AT LIVERPOOL, BIRMINGHAM. MANCHESTER, LEEDS

NEAR KINGS CROSS SS CROSS LONDON, HAVE VACANCIES FOR **EXPERIENCED**

ELECTRONIC ENGINEERS They must have specialised knowledge in

amplifying equipment. Good salary and working conditions. Write in strict confidence to:

Box No. 1372 c/o "Wireless World"

"BARGAINS WITH PERSONAL SERVICE"

BARGAINS WITH PERSONAL SERVICE

**JOMMUNICATION RECEIVERS \$2.06.

**JOMMUNICATION RECEIVERS \$2.06.

**JOS. 30 May 10 May NIZER CHASSIS (American), contains 28 ceramic cetai valge boiders, blower motor, relay, wave change switches, pots, and host of condensers, resistors, knobs, etc., 15/-, post 2/6. DYNAMO EXPLODERS, for detonating explosive charges, in hide leather case, 45/-, post 2/6. DYNAMO EXPLODERS, to detonating explosive charges, in hide leather case, Many other lems, headphones, microphones, test meters, telephone sets, etc. TERMS: C.W.O. Monthly accounts approved business bouses, etc. 8.4.E. enquiries. Carriage quoted applies only Mainland. A. J. THOMPSON, "ELLING LODGE," Codicote, Hitchin, Herts, Phone Codicote 242.

Instrumentation at its best ...





SIFAM ELECTRICAL INSTRUMENT CO. LTD. WOODLAND ROAD, TORQUAY Tel. 63822/3/4

REBUILT T/V TUBES

12"-14" £4 15 0 15"-17" £5 5 0 21" £7 15 0

ALL TUBES GUARANTEED FOR 12 MTHS. 15/- ALLOWED ON YOUR OLD BULB. CARRIAGE AND INSURANCE EXTRA.

VACUUM ELECTRONIC LTD. 35 SACKVILLE ST., LONDON, W.I.

Phone REG. 6404

SERVO & ELECTRONIC SALES LTD.

SERVO & ELECTRONIC SALES LTD

SUNVIG HOT WIRE VAG SWITCH RELAYS, P203-8
230 v. load 7 kw 45f-es. (3f) other types available.

METER 24in. PROJ. P.1. 0-40 amps. 50 cps. moving
iron 12/6 (2f). HRO POWER UNITS 12 v. D.C. 1/F
35f-new and boxed (3/6). SPRAGUE MOTOR SUPPRESSION CONDENSERS 0.004 mid. 1,000 v. D.C. 1/F
35f-new and boxed (3/6). SPRAGUE MOTOR SUPPRESSION CONDENSERS 0.004 mid. 1,000 v. D.C.

LINING CONDENSERS 0.004 mid. 1,000 v. D.C.

MATORS TYPE 49 220 v. A.C. 1/F 20 to 1/0 Mig.

LAY to 10 mV (with 100µA carrier meter) in 5 ranges
with int. mod. exc. con. £10 (10+). 24V DESYNN
Blank Dial indicators 25f- (1/6) STC MIN. RELAYS
1886ED and 41846D 17/6 (1/6). 25 kw SIMMERSTATS 15f- (1/6). ETH TRANSFORMERS 230 v.

A.C. to 20 v. 2.2 mA. 27/6 (1/6). 2.5 kw SIMMERSTATS 15f- (1/6). EHT TRANSFORMERS 230 v.

A.C. to 9.5 kv. 3 mA. herm. sid. 55f-, (3/6). EHT

CAPACITORS Viscond 0.02µF 11 kv. 12/6. (2/6). MILLIAMMETERS 0-200 mA. 24im. fluah 10/r (2/r).

PRESSURS 6AUGES 3im. dias, flush 10/bls. 250/bs.,
1,250/bs., or 2.000bs. fed 25f-, (3/r). E.E. SEALED

REFRIGERATOR UNITS. 110 v. 50 eps. with cooling
coils, ice box, and thermostat, charged, brand new £20
(carr. extra). 240/110 v. TRANSFORMERS to sile

15/7 (carr. extra). ARCO ELECTRIC PAREL LABINS

17/8 (250 v. 50 cps. or 12 v. D.C. supply. Sensitivity

2-6/14 vin exc. cond. £30 (3/r). CRTS Type 50/Ps.

18 SWG Arax 60/40 alloy 57/r per Type 50/Ps.

18 SWG Arax 60/40 alloy 57/r per Type 10/Ps. etc.

MOTORS, 115 v. 400 cps. and 20 v. 400 cps. control phase type 11M47A brand new. SIZE 11 SERVO


MOTORS, 115 v. 400 cps. and cov. 400 cps. control phase type 11M47A brand new. Cogether with our correction of components for electrical computation and controls.

Post orders to: 1, Hopton Parade, Streatham High Road, Jondon. SW 16.

Post orders to: 1, Hopton Parade, Streatham High Road, London, S.W.16,

Callers to: 43 High Street, Orpington, Kent. Tels.: Orpington 31066 and Streatham 6165.

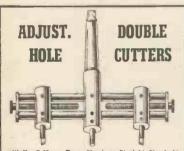TERMS: Nett C.W.O. or monthly approved accounts.



with No. 3 Morse Taper Shank or Straight Shank ‡", Capacities: from 11" to 9" diameter. Send for illustrated Price List.

LUDFRY LTD

5 Hanway Place, London, W.1. Tel. MUS 7472





Our present range includes: Fidelia Major AMI/FM tuner unit with pre-amp. tone controls, etc., R.F. stage on all wavebands, variable selectivity, etc. Price 227/4/s, or with the Major ampillier, 229/14/s.
Fidelia Imperial, VHF tuner. Price 21/5/s-, or with pre-amp. and tone controls, 219.
Fidelia Preciton, switched VHF tuner. Price 214/g/s, or with pre-amp. and tone controls 219.
Fidelia Major amplifier, 218.



Full details willingly on request (6d. for postage is appreciated.)

ELECTRO TIC -DEVELOPMENTS

2 AMHURST ROAD TELSCOMBE CLIFFS Nr. Brighton, SUSSEX.

Tel.: Peacehaven 3156

Since 1931 all types, single and 3-phs, 6w to 12 KVA, over 1,000,000 during the war, UL Output Transformers.

SOUND SALES LTD.

Works & Laboratories: West Street, Farnham, Surrey Farnham 6461

LOUDSPEAKER **ENCLOSURES**

AND AMPLIFIER CONSOLE CABINETS

A. DAVIES & CO. (Cabinet Makers) 3 PARKHILL PLACE (off Parkhill Road) Few minutes walk Belsize Park Underground

MALVYN ENGINEERING WORKS

Engineers to the Radio and Electronic Industries

Manufacturers of: Chassis, Small Pressings, Machined Components, Wiring and Mechanical Assemblies, to specification.


Single and Production Quantities. 7 CURRIE STREET, HERTFORD, HERTS.

- Telephone: Hertford 2264 -

CLEAN AND SILENT

UP 100 WATTS

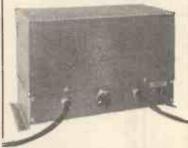WITH THE FELGATE ELECTRONIC INVERTER MK II



FROM 210/250 VOLTS D.C. NO MOVING PARTS FREQUENCY CONTROL

Manufactured by

McCARTHY RADIO AND ELECTRONICS LIMITED

STUDLAND HALL, STUDLAND STREET. LONDON, W.6.

INSTRUMENT REPAIRS

DON'T WAIT. TAKE ADVANTAGE OF OUR QUICK SERVICE, COMPETI-TIVE PRICES AND GUARANTEED REPAIRS

We specialise in the repair and conversion of the following :-

MULTI-RANGE METERS.
AMP-VOLT-WATTMETERS.
ELECTRONIC AND ALL ALLIED
MEASURING EQUIPMENT.
SPC. LABORATORY EQUIPMENT.

LEDON INSTRUMENTS LTD. 96, Deptford High St., London, S.E.8. TIDEWAY 2689



RECORDING TAPE BARGAINS !

SPECIAL OFFER BRAND NEW

BOXED & EXCELLENT QUALITY

DICKINSONS of Pall Mail Ltd. (Dept. W.W.)

11 Royal Opera Arcade, Pall Mall, S.W.1
(Behind Her Majesty's Theatre in the
Haymarket)

EXCLUSIVE

OUR OWN MAKE OF PLAYER CASES AND CABINETS IN WAL-NUT AND MAHOGANY. MADE SPECIALLY TO HOUSE ANY TRANSCRIPTION PLAYER, MO-TOR AND PICK-UP. FROM £5.

WRITE FOR DETAILS

ALSO-WE BUY AND SELL GOOD HI-FI EQUIPMENT

H. C. HARRIDGE

8 Moor St., Cambridge Circus, W.1 Open Daily Except Thursday.

TELEPRINTERS PERFORATORS REPERFORATORS TAPE READERS

Terminals and V.F. Pen Recorders, Pen Recorders, Terminals and V.F. Telegraph multi-channel units; Testing Equipment, Test Frames, Telephone Carriers and Repeaters; Signalling Rectiflers and Relays, Transformers, Transmit and Receive Filters; Repeating and Retardation Coils; Racks, Relay Bases, Uniselectors, Remote Control Transmitters, British, American and German Faulisness. Equipment.

BATEY & CO., GAIETY WORKS, Akeman Street, Tring, Herts. Tel.: TRING 2183 and 2310

INDEX TO ADVERTISERS

PAGE	PAGE	Palmer, G. A., Stanley, Ltd. 120 Partridge Transformers, Ltd. 120 P.C. Radio 158, 160 P.C. Radio 165 Pembridge College of Electronics 177 Philips Electrical, Ltd. 180 Philips, N.V. 30, 31 Phoenix Telephone Co., Ltd. 75 Piezo, Ltd. 92 Plessey Co., Ltd. 44, 53, 89, 108, 176 Post Radio Supplies 164 Premier Radio, Ltd. 140, 141 Proops Bros., Ltd. 136, 137 Pye, Ltd. 10, 96
A.A. Tools 184 Acoustleal Mfg. Co., Ltd. 55 Adcola Products, Ltd. 68 Advance Components, Ltd. 20, 63 Airborne Instruments Laboratory 175 Aircraft Marine Products, Ltd. 69 Airmon Ltd. 69	Gabriel Manufacturing Co., Ltd 84	Paimer, G. A., Stanley, Ltd
Acoustical Mig. Co., Ltd	Gardners Radio, Ltd	P.C.A. Radio 158, 160
Advance Components, Ltd 20, 63	50, 92, 189	Pembridge College of Electronics
Airborne Instruments Laboratory 175	Gee Bros., Radio, Ltd 157	Philips Electrical, Ltd 180
Aircraft Marine Products, Ltd 69	General Electric Co., Ltd. 73, 106 General Sonic Radios 169 Gliladian, R., & Ço., Ltd. 258 Glison, R. F., Ltd. 86 Glastone Radio 156 Glaser, L., & Co., Ltd. 192 Goodmans Industries, Ltd. 33 Goodwin, C. C. (Sales), Ltd. 166 Govt., Comm. H.Q. 178, 179 Gramphone Co., Ltd., The 28 Gramplan Reproducers, Ltd. 191 Grey & Marten, Ltd. 80 Grayshaw Instruments 166	Phoenix Telephone Co., Ltd 75
Airmec, Ltd	Gilfillan, R., & Co., Ltd	Piezo, Ltd 92
Anders Electronics, Ltd 16	Gilson, R. F., Ltd 86	Post Radio Supplies 44, 55, 89, 108, 176
	Gladstone Radio .,	Premier Radio, Ltd 140, 141
Appointments Vacant 170, 171, 172, 173, 174, 175, 176, 177, 178, 179, 180, 181, 191	Glaser, L., & Co., Ltd 192	Proops Bros., Ltd
Archiectric Switches, Ltu	Goodwin C C (Sales) Ltd	2 30, 200.
Ardente Acoustic Laboratories, Ltd	Govt., Comm. H.Q 178, 179	
Ariel Pressings, Ltd 85	Gramophone Co., Ltd., The 28	m-di- 0 mi-4-1-1 25-4
Armstrong Wireless & Television Co., Ltd	Grampian Reproducers, Ltd, 191	Radio & T.V Components (Acton), Ltd. 163
Associated Electrical Industries, Ltd.	Gravehaw Instruments	Radio Clearance, Ltd 161
Ltd. 51, 187 Associated Electrical Industries, Ltd. cover ii, 4, 103, 104, 176, 178, 179, 180 Audix B. B., Ltd 166	Grayona and unions	Radio & Electrical Mart Radio & T.V. Components (Acton), Ltd. 163 Radio Clearance, Ltd. 161 Radio Component Specialists 151 Radio Exchange Co., The 169 Radio Exchange Co., The 169 Radio Resistor, Ltd. 2 Radiospares, Ltd. 92 Radiospares, Ltd. 92 Radiospares, Ltd. 105, 174 Radio Supply Co. (Leeds), Ltd. 142, 143, 144 Rank Cintel, Ltd. 155 Reproducers & Amplifiers 38 Rollet, H., & Co., Ltd. 192
Automatic Telephone & Flectric Co. Ltd. 37 40		Radio Resistor, Ltd 2
Automatic Telephone & Electric Co., Ltd. 37, 40 Aveley Electric, Ltd. 34 Avo, Ltd. 1, 94	Harmsworth Townley & Co	Radiostructor 105, 174
Avo, Ltd 1, 94	Harridge H C 193	Radio Supply Co. (Leeds), Ltd. 142, 143, 144
		Rank Cintel, Ltd
Batey, W., & Co. 193 Belling & Lee, Ltd. 88, 101 Benson, W. A. 160 Bentley Acoustic Corporation, Ltd. 162 Berry's Radio 74 Box 1372 192 B.P. Computers 176 Bradford Institute of Technology 180 Bradmatic Productions 180	Harris Electronics (London), Ltd 145	Reproducers & Amplifiers 38
Belling & Lee, Ltd 88, 101	Harris, P	Rollet, H., & Co., Ltd 192
Bentley Acoustic Corporation, Ltd 162	Hatfield Instruments Ltd 64	Salford Electrical Instruments, Ltd.
Berry's Radio 74	H.B. Trading	72, 76, 120, 160
Box 1372 192	Harris Electronics (London), Ltd. 145 Harris P. 186 Harverson Surplus, Ltd. 146 Hatfield Instruments, Ltd. 64 H.B. Trading 180 Henry's (Radio), Ltd. 147 Hewlett-Packard, S.A. 119 H.P. Radio Services, Ltd. 82 Hunt, A. H. (Capacitors), Ltd. 81 Hunton, Ltd. 62	Samson Surplus Stores, Ltd 155 Sanders W H (Electronics) Ltd
B.P. Computers	Hewlett-Packard, S.A 119	Savage Transformers, Ltd
Bradmatic Productions	Hunt A W (Conscitors) Itd	Service Trading Co 138, 139
Brandaeur, C., & Co., Ltd 64	Hunton, Ltd. (Capacitors), Etc. 62	Sifam Electrical Instrument Co., Ltd 192
Brenell Engineering, Ltd 8		Sim-Tech Book Co 192
Brandaeur, C. & Co., Ltd	Tiefe Books	Smith. A. E. & L. G., Ltd
British Institute of Engineering Tech-	Iliffe Books	Smith. G. W. (Radio), Ltd 128, 129
nology 177	International Correspondence Schools 172, 174	Smith. S. & Sons, Ltd 176
British Relay Wireless, Ltd 178	Irongate (M.O.) Co 149	Solartron Electronic Group, Ltd 122, 174
British Communications Corporation, Ltd. British Institute of Engineering Technology British Relay Wireless, Ltd. Brookes Crystals, Ltd. Brown, S. G., Ltd. Bulgin, A. F. & Co., Ltd. Edit. 651 Bullers, Ltd. 66		South Midland Construction, Ltd 188
Bulgin, A. F. & Co., Ltd Edit, 631	Forum Walt & Co Itid	South Supplies (Electrical), Ltd 169
Bullers, Ltd 66	Kenure Holt Flectronics Ltd	Southern Technical Supplies 170
	Kenure, Holt & Co., Ltd	Stanford, A L
Canadian Westinghouse Co., Ltd		Standard Telephones de Caples, and.
Candles System Co. 194		7, 9, 11, 13, 15, 156
Candler System Co	Tachela Dalla This	Steatite Insulations, Ltd
Candler System Co	Lasky's Radio, Ltd ,. 124, 125, 126	7, 9, 11, 13, 15, 156 Steatite Insulations, Ltd
Canadian Westinghouse Co., Ltd. 77 Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132	Lasky's Radlo, Ltd 124, 125, 126 Lawson, Tubes	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 39 Stern Radio. Ltd 134, 135 Storno
Candler System Co	Lasky's Radio, Ltd	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 59 Stern Radio. Ltd 134, 135 Storno
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188	Lasky's Radio, Ltd 124, 125, 126 Lawson, Tubes 192 Leak, H. J., & Co., Ltd,	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porrelain Products, Ltd. 55 Stera Radio. Ltd 134, 135 Storno
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 130, 131, 132 Cosno Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94	Lasky's Radio, Ltd	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 39 Stern Radio. Ltd 134, 135 Storno
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173	Lasky's Radio, Ltd. 124, 125, 126 Lawson, Tubes 192 Leak, H. J., & Co., Ltd. 111 Ledon Instruments, Ltd. 193 Leevers-Rich Equipment, Ltd. 43 Lesa 66 Lewis Radio Co. 187 Light Soldering Developments, Ltd. 190	Rollet, H., & Co., Ltd
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173	Lasky's Radio, Ltd. 124, 125, 126 Lawson, Tubes 192 Leak, H. J., & Co., Ltd. 191 Ledon Instruments, Ltd. 193 Leevers-Rich Equipment, Ltd. 43 Lesa 66 Lewis Radio Co. 187 Light Soldering Developments, Ltd. 190 Linear Products, Ltd. 74	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 39 Steat Radio. Ltd. 39 Stratton & Co. Ltd. Cover iii, 180 Sugden. A R. & Co. (Engineers), Ltd. 54 Super Radiotech. Ltd. 162 Swindon Condenser Co., Ltd. 26 Tannoy Products. Ltd. 188 Technical Suppliers. Ltd. 170 Technical Trading Co. 168
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72	Lasky's Radio, Ltd	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 55 Steat Radio. Ltd
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 130, 131, 132 Cosnor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 195	Lasky's Radio, Ltd	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 39 Steat Radio. Ltd. 134, 135 Storno 256 Stratton & Co. Ltd. Cover iii, 180 Sugden A R. & Co. (Engineers), Ltd. 54 Super Radiotech, Ltd. 162 Swindon Condenser Co., Ltd. 26 Tannoy Products, Ltd. 189 Technical Suppliers, Ltd. 170 Technical Trading Co. 168 Telemechanics, Ltd. 78 Telegal Ltd. 70 Telegal Ltd. 70 Telegal Ltd. 32
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 193 Davis, Jack (Relays), Ltd. 84	Lasky's Radio, Ltd. 124, 125, 126 Lawson, Tubes 192 Leak, H. J., & Co., Ltd. 111 Ledon Instruments, Ltd. 193 Leevers-Rich Equipment, Ltd. 43 Lesa 66 Lewis Radio Co. 187 Light Soldering Developments, Ltd. 79 Linear Products, Ltd. 74 Livingston Laboratories, Ltd. 77 Londex, Ltd. 70 London Central Radio Stores 184 Ludfry, Ltd. 193	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davles, A., & Co. 195 Davles, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Dence (Clacton) Ltd. 29 Dence (Clacton) Ltd. 54	Lasky's Radio, Ltd. 124, 125, 126 Lawson, Tubes 192 Leak, H. J. & Co., Ltd. 111 Ledon Instruments, Ltd. 193 Leevers-Rich Equipment, Ltd. 43 Lesa 66 Lewis Radio Co. 187 Light Soldering Developments, Ltd. 190 Linear Products, Ltd. 74 Livingston Laboratories, Ltd. 71, 115 Londex, Ltd. 70 London Central Radio Stores 184 Ludfry, Ltd. 193 Lugons Radio, Ltd. 181 Lyons Radio, Ltd. 181	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 95 Steat Radio. Ltd. 134, 135 Storno
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.1. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 193 Davis, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 54	Lasky's Radio, Ltd	Steatite Insulations, Ltd. 7, 9, 11, 13, 15, 156 Steatite & Porcelain Products, Ltd. 35 Steat Radio. Ltd
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 130, 131, 132 Cosnocord, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 792 Davies, A., & Co. 193 Davis, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davles, A., & Co. 193 Davis, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Divert TV Penlegements	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 195 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Candler System Co. 184 C.G.S. Resistance Co., Ltd. 166 Channel Electronic Industries, Ltd. 60 Clyne Radio, Ltd. 130, 131, 132 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 193 Davis, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pali Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davies, A., & Co. 195 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davies, A., & Co. 195 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 193 Davis, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Dude Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Ettel-McCulloch, Inc. 121	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 193 Davis, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Developments 193	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 160
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davles, A., & Co. 195 Davles, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denoc (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Developments 193 Electro-Acoustic Developments 195 Electro-Acoustic Industries, Ltd. 188	Leevers-Rich Equipment, Ltd.	Technical Trading Co.
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davles, A., & Co. 195 Davles, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denoc (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Developments 193 Electro-Acoustic Developments 195 Electro-Acoustic Industries, Ltd. 188	Leevers-Rich Equipment, Ltd.	Technical Trading Co.
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davles, A., & Co. 195 Davles, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denoc (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electro-Acoustic Industries, Ltd. 185 Electro-Acoustic Industries, Ltd. 185 Electro-Acoustic Industries, Ltd. 185 Electro-Acoustic Industries, Ltd. 185 Electro-Methods, Ltd. 61 Electro-Perceiven Equipment, Ltd. 113	Leevers-Rich Equipment, Ltd.	Technical Trading Co.
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davles, A., & Co. 195 Davles, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denoc (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electro-Acoustic Industries, Ltd. 185 Electro-Acoustic Industries, Ltd. 185 Electro-Acoustic Industries, Ltd. 185 Electro-Acoustic Industries, Ltd. 185 Electro-Methods, Ltd. 61 Electro-Perceiven Equipment, Ltd. 113	Leevers-Rich Equipment, Ltd.	Technical Trading Co.
Clyne Hadio, Ltd. 150, 151, 152 Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davles, A., & Co. 195 Davles, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denoc (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electro-Acoustic Industries, Ltd. 18 Electro-Acoustic Industries, Ltd. 18 Electro-Methods, Ltd. 61 Electronic Trechiology 112 Electroic Trechiology 112 Electroic Tubes, Ltd. 47 Electronic Thees, Ltd. 47 Electronic Thees, Ltd. 47 Electronic Thees, Ltd. 47 Electronic Trechiology 112 Electronic Trechiology 112 Electronic Trebes, Ltd. 47	Leevers-Rich Equipment, Ltd.	Technical Trading Co.
Clyne Hadio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 195 Davis, Jack (Relays), Ltd. 84 Darstrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pali Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Developments 193 Electro-Acoustic Industries, Ltd. 18 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Tubes, Ltd. 47 Electronic Sievet Street), Ltd. 167 Electronic Winds, Ltd. 167	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Clyne Hadio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davles, A., & Co. 195 Davles, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Developments 193 Electro-McCulloch, Ltd. 61 Electro-Methods, Ltd. 61 Electronic Precision Equipment, Ltd. 113 "Electronic Tenchology" 112 Electronic Tubes, Ltd. 47 Electronic Tibes, Ltd. 167 Electronic Tib	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Clyne Hadio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics. Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 193 Davis, Jack (Relays), Ltd. 84 Darstrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Developments 193 Electronic Precision Equipment, Ltd. 18 Electronic Technology 112 Electronic Tubes, Ltd. 47 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Servety Ltd. 167 Electro-Winds, Ltd. 90 Elliott Bros. (London), Ltd. 12, 156, 158, 179 Elstone Radio 164 E.M.I. Electronics, Ltd. 162 E.M.I. Electronics, Ltd. 164 E.M.I. Electronics, Ltd. 167 Elstro-Electro-Winds, Ltd. 167 Elstro-Electro-Electro-Winds, Ltd. 167 Elstro-Electro-Electro-Winds, Ltd. 167 Elstro-Electro-Winds, Ltd. 167 Elstro-Electro-Electro-Winds, Ltd. 167 Elstro-Electro-Electro-Winds, Ltd. 167 Elstro-Electro-Electro-Electro-Electro-Winds, Ltd. 167 Elstro-Electro-El	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Clyne Hadio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davies, A., & Co. 193 Davies, A., & Co. 193 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Denendable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Industries, Ltd. 18 Electro-Acoustic Industries, Ltd. 18 Electronic Tenenlogy 112 Electronic Tenenlogy 112 Electronic Tubes, Ltd. 47 Electronic Tubes, Ltd. 47 Electronic Tubes, Ltd. 47 Electronic Tubes, Ltd. 47 Electronic Tibes, Ltd. 190 Elistone Radio 164 E.M.I. Electronics, Ltd. 190 Elstone Radio 164 E.M.I. Electronics, Ltd. 102, 174 English Electric Valve Co., Ltd. 65	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Clyne Radio. Ltd. 100 Cossoor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics. Ltd. 72 Davles, A., & Co. 193 Davles, A., & Co. 195 Davles, Jack (Relays). Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pali Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Developments 193 Electro-Acoustic Industries, Ltd. 18 Electron-Methods, Ltd. 61 Electronic Trechnology 112 Electronic Trechnology 112 Electronic Trechnology 112 Electronic Trechnology 112 Electronic Trechnology 112 Electronic Thes, Ltd. 90 Eliliott Bros. (London), Ltd. 12, 156, 158, 179 Elstone Radio 164 E.M.I. Electronic S. Ltd. 162 Electronic Std. 164 E.M.I. Electronic Ltd. 165 Elentish Electric Co., Ltd. 172, 178, 179 English Electric Co., Ltd. 172, 178, 178 English Electric Co., Ltd. 172, 178, 178	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Clyne Hadio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 193 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electro-Acoustic Industries, Ltd. 18 Electro-Acoustic Industries, Ltd. 18 Electro-Methods, Ltd. 61 Electronic Trechnology 112 Electronic Trechsion Equipment, Ltd. 133 "Electronic Technology" 112 Electronic Trechsion Equipment, Ltd. 167 Electronic Trechsion Ltd. 90 Elictronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 164 Elliott Bros. (London), Ltd. 12, 156, 158, 179 Elstone Radio 164 E.M.I. Electronics, Ltd. 167 English Electric Co., Ltd. 172, 178, 179 Enthoven Solders, Ltd. 172, 178, 178 Enthoven Solders, Ltd. 26, 88 Enthoven Solders, Ltd. 26, 88 Enthoven Solders, Ltd. 172, 178, 178 Enthoven Solders, Ltd. 26, 88	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Clyne Radio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 188 Daly (Condensers), Ltd. 72 Davies, A., & Co. 195 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pali Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electro-Acoustic Industries, Ltd. 18 Electro-Acoustic Industries, Ltd. 18 Electronic Precision Equipment, Ltd. 18 Electronic Technology 112 Electronic Tubes, Ltd. 47 Electronic Tubes, Ltd. 90 Elilott Bros (London), Ltd. 156, 158, 179 Elstone Radio 164 E.M.I. Electronics, Ltd. 167 Electro-Winds, Ltd. 90 Elliott Bros (London), Ltd. 12, 156, 158, 179 Elstone Radio 164 E.M.I. Electric Co. Ltd. 172, 178, 179 Enthoven Soiders, Ltd. 27 Enthoven Soiders, Ltd. 26, 88 Erie Resistor, Ltd. 27	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davies, A., & Co. 195 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electron-Acoustic Developments 193 Electron-Acoustic Developments 193 Electron-Acoustic Development, Ltd. 168 Electron-Methods, Ltd. 61 Electronic Tenchology 112 Electronic Tenchology 112 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Cosmocord, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davies, A., & Co. 195 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electrical and Wireless Supply 170 Electron-Acoustic Developments 193 Electron-Acoustic Developments 193 Electron-Acoustic Development, Ltd. 168 Electron-Methods, Ltd. 61 Electronic Tenchology 112 Electronic Tenchology 112 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tenchology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Trading Co. 163 Technical Co. 164 Technical Co. 164 Technical Co. 164 Technical Corpon 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 154 Truvox. Ltd. 41 Tyer & Co., Ltd. 77 U.S. A.E.A. 171, 176, 178 U.S. A.E.A. 171, 176, 178 United Components 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 172 Universal Book Co. 164 Vacuum Electronics, Ltd. 23 Valradio, Ltd. 23 Valradio, Ltd. 36 Venner Accumulator Co. Ltd. 36 Venner Lectronics Co. Ltd. 37 Venner, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 90 Vortexion, Ltd. 109, 110 V.Z. Electrical Service 184
Clyne Hadio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davies, A., & Co. 193 Davies, A., & Co. 193 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electroa-Acoustic Industries, Ltd. 18 Electro-Acoustic Industries, Ltd. 61 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Tubes, Ltd. 47 Electronic Technology 112 Electronic Technology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street S	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Telemechanics. Ltd. 70 Telemechanics. Ltd. 70 Telemechanics. Ltd. 70 Teles and 1943). Ltd. 52 Tele-Radio (1943). Ltd. 52 Tele-Radio (1943). Ltd. 52 Tele-Radio (1943). Ltd. 127 Thompson. A. 192 Torei Industrial Corpn. 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 164 Truvox. Ltd. 76 U.E.A.E.A. 171, 176, 178 U.E.A.E.A. 171, 176, 178 U.E.A.E.A. 171, 176, 178 U.E.A.E.A. 177, 176, 178 U.E.A.E.A. 177, 178 Unices Bilss & Co., Ltd. 92 Unicam Instruments, Ltd. 176 United Comoonents 172 Universal Book Co. 188 Vacuum Electronics, Ltd. 192 Vacweil Engineering Co., Ltd. 82 Valradio, Ltd. 82 Venner Accumulator Co., Ltd. 87 Venner, Ltd. 178 Venner, Ltd. 178 Venner, Ltd. 178 Venner, Ltd. 199 Walmore Electronics Co., Ltd. 90 Walmore Electronics Ltd. 199 Wayne Kerr Laboratories, Ltd. 194 Wayne Kerr Laboratories, Ltd. 178 Weymouth Radio Mig. Co., Ltd. The 90 Wehlington Acoustic Laboratories, Ltd. 179 Weymouth Radio Mig. Co., Cld. 75 While S. S., Dental Mig. Co., Cld. 75 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wilkinson, Ltd. 76 Wirecomp Electronics 144 Wilkinson, Ltd. 77 Wirecomp Electronics 144 Wilkinson, Ltd. 76 Wirecomp Electronics 144
Clyne Hadio, Ltd. 100 Cossor Instruments, Ltd. 117 Coventry Radio 188 Crawshay, P. B. 94 C.R.E.I. (London) 173 Dale Electronics, Ltd. 72 Davies, A., & Co. 193 Davies, A., & Co. 193 Davies, Jack (Relays), Ltd. 84 Daystrom, Ltd. 29 Denco (Clacton), Ltd. 54 Dependable Radio Supplies, Ltd. 168 Derritron Electronics Group 116 Dickinsons of Pall Mall, Ltd. 193 Direct T.V. Replacements 152 Duke & Co. 150 Duode Natural Reproducers 186 E.I.R. Instruments, Ltd. 190 Eitel-McCulloch, Inc. 121 Electroa-Acoustic Industries, Ltd. 18 Electro-Acoustic Industries, Ltd. 61 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Technology 112 Electronic Tubes, Ltd. 47 Electronic Technology 112 Electronic Technology 112 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Tubes, Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street) Ltd. 167 Electronic Siplest Street S	Leevers-Rich Equipment, Ltd.	Technical Trading Co. 163 Telemechanics. Ltd. 70 Telemechanics. Ltd. 70 Telemechanics. Ltd. 70 Teles and 1943). Ltd. 52 Tele-Radio (1943). Ltd. 52 Tele-Radio (1943). Ltd. 52 Tele-Radio (1943). Ltd. 127 Thompson. A. 192 Torei Industrial Corpn. 68 Trix Electrical Co., Ltd. Edit 629 T.R.S. Radio 164 Truvox. Ltd. 76 U.E.A.E.A. 171, 176, 178 U.E.A.E.A. 171, 176, 178 U.E.A.E.A. 171, 176, 178 U.E.A.E.A. 177, 176, 178 U.E.A.E.A. 177, 178 Universal Bliss & Co., Ltd. 92 Unicam Instruments, Ltd. 176 Unived Comoonents 172 Universal Book Co. 188 Vacuum Electronics, Ltd. 192 Vacweil Engineering Co., Ltd. 82 Valradio, Ltd. 82 Venner Accumulator Co., Ltd. 87 Venner, Ltd. 178 Venner, Ltd. 178 Venner, Ltd. 178 United Comotonents 179 Universal Seok Co., Ltd. 178 Ushility Bulbs, Ltd. 90 Vortexion, Ltd. 198 Walmore Electronics Ltd. 199 Wayne Kerr Laboratories, Ltd. 194 Webber, R. A., Ltd. 93 Webber, R. A., Ltd. 94 Webber, R. A., Ltd. 95 Weynouth Radio Mig. Co., Ltd. The 90 Wehlington Acoustic Laboratories, Ltd. 178 Weymouth Radio Mig. Co., Ltd. The 90 Wharfedale Wireless Works, Ltd. 56, 62 Whilkinson, L. (Croydon), Ltd. 188 Wirecomp Electronics 144



The EDDYSTONE'880'

HIGH Present-day radio communications services call for a receiver with a most exacting performance, particularly as regards frequency stability and setting, allied to ease of control.

The Eddystone ''880'' High Stability Communications Receiver has been designed expressly for use in professional communications systems and the specification reaches the high modern standards required. Many refinements are incorporated, and the versatility is such as to make the receiver eminently suitable for such applications.

The special principles employed result in an exceptionally high degree of frequency stability. Throughout the tuning range of the receiver, which is from 500 kc/s to 30.5 Mc/s, the long-term drift does not exceed 50 cycles. Particular care has been taken to reduce spurious responses to an absolute minimum and the figures for such characteristics as cross-modulation, blocking, inter-**RECEIVER** modulation and image ratio are extremely good. The electrical performance is well maintained in every way and conforms to accepted professional standards.

High "front-end" selectivity is provided by two fully tuned r.f. stages and all tuning is accomplished with a single knob. The tuning rate is linear and the large, clear scale shows only the range in use. The frequency to which the receiver is tuned can be read off easily to within one kilocycle. Radiation at any frequency has been reduced to a remarkably low figure. In practical operation, the "880" possesses marked superiority in rendering signals at maximum intelligibility.

Comprehensive information and the full specification is available on request to Professional and Commercial Organisations.



STRATTON & CO. LTD. BIRMINGHAM 31

140 151

154

1560

Multicore Solders all their users present and future happy Christmas and a prosperous New Year.






SAVBIT **FOR** INDUSTRY

The best present for factory operatives is to know that adequate supplies of 71b. and 1 lb. reels of Ersin Multicore Solder are available for 1961.



HOME CONSTRUCTORS' PACK

The amateur radio enthusiast will always welcome a reel of Ersin Multicore Solder. 19 ft. of 18 s.w.g. 60/40 alloy. 2/6d. per reel (subject). Or if you feel generous give a 5/- carton.

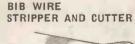

This 3-in-1 tool will be in constant use. It strips insu-

lation .without nicking the wire, cuts wire cleanly and splits plastic extruded twin flex. 3/6d. each (subject).



BIB TAPE ACCESSORY KIT

The perfect present for every tape recorder owner. The kit contains a Bib tape splicer with 6 spare cutters, reel of splicing tape, 24 tape identification labels and quick reference chart of playing times for standard tape lengths at different speeds with typical playing times of standard orchestral works. 28/6d. each (subject).



MULTICORE SOLDERS LIMITED · MULTICORE WORKS · HEMEL HEMPSTEAD · HERTS (BOXMOOR 3636)