

SERVICING AUTO RADIO

RADIO NEWS

AND

SHORT WAVE RADIO

JULY

**CLOSET-DOOR
RADIO
WORKSHOP**



25¢

U. S. AND
CANADA

HENRY
MOORE
PICKER

PREVIEW DOUBLE FEATURE

BOOTHS 40-41, RADIO PARTS SHOW, CHICAGO

THE *New*
MODEL 773
WESTON
TUBE CHECKER
... Companion to Model 772
Equally Outstanding!



Features:

1. Big, easy-reading, sensitive meter.
2. Noise test . . . each electrode.
3. New, exclusive WESTON rapid-reference tube charts.
4. Perfected emission type tester . . . tests tubes under standardized load resistance . . . individually tests all electrodes. Cathode leakage test.
5. Neon short check, each electrode, while tubes are hot.
6. Tests metal, glass, spray shield, "MG" tubes . . . has spare socket.
7. Exclusive WESTON circuit . . . wired for rotating filaments . . . obsolescence forestalled!
8. Handsome, polished, light-weight, solid-wood cases . . . finest construction . . . luggage handles.
9. Size, styling same as Model 772.
10. Furnished in individual carrying case, in combination case for use with 772, or in counter type case.
11. Striking design and finish, modern knobs and 3-color panel, electrode switches grouped for convenience.
12. Outstanding in operating simplicity and dependability. Another LEADER!

Model 773 in solid, polished-wood carrying case. Also sold in counter case shown below . . . as well as in combination case for use with Model 772, 20,000 ohms-per-volt Analyzer. A perfect combination.



A New

CONCEPTION IN COUNTER TUBE SELLERS!

Entirely different! Commands instant attention in this striking, polished solid-wood case. Conveys to customers the impression of true, scientific accuracy. Instrument also fits the single and combination carrying cases. Quickly interchangeable. *Note the new Weston rotator-type tube chart. You 'spot' your tube instantly. Charts easily replaceable.*

See Model 773 at the show, or get your preview by-mail today! Just return the coupon.

Weston Electrical Instrument Corporation,
615 Frelinghuysen Avenue, Newark, N. J.
Send data on Model 773.

Name _____
Address _____
City _____ State _____

WESTON Instruments can be purchased under the WESTON deferred INVESTMENT PLAN!

How a "Tip" got Tom a Good Job

THERE'S D J C IN BERLIN... THE TENTH FOREIGN STATION TONIGHT. RADIO'S CERTAINLY FUN.

HELLO, TOM. HOW'S EVERYTHING?

NOT SO GOOD BILL, BUT I'M STILL PLAYING WITH RADIO. HAD D J C LAST NIGHT. IS RADIO STILL YOUR HOBBY TOO?

NO, TOM, I'VE BEEN TOO BUSY MAKING GOOD MONEY OUT OF RADIO LATELY TO PLAY WITH IT.

YOU'RE SURE LUCKY, BILL. I NOTICED YOUR NEW CLOTHES AND SNAPPY CAR. I THOUGHT YOU HAD INHERITED A MILLION.

YOU HAVE THE SAME CHANCE TOM. ABOUT A YEAR AGO I SHOWED YOU A BOOK FROM NATIONAL RADIO INSTITUTE TELLING ABOUT THE OPPORTUNITIES AND FUTURE IN RADIO, AND HOW OTHERS HAD SUCCEEDED THROUGH THEIR HOME TRAINING. WELL I ENROLLED.

I'M DOING SWELL IN RADIO. MARY AND I ARE TO BE MARRIED NEXT MONTH. RADIO IS MORE THAN A PASTIME. IT'S A BIG BUSINESS AND GROWING FAST. TAKE MY TIP AND GET INTO RADIO NOW, TOM!

IF BILL SUCCEEDED, I CAN TOO!

THEN I CAN MAKE REAL MONEY SERVICING RADIO SETS.

OR INSTALL AND SERVICE LOUD SPEAKER SYSTEMS

OR MAKE GOOD MONEY IN ANYONE OF THE MANY OTHER NEW AND GROWING BRANCHES OF RADIO. I'M GOING TO SEND FOR THAT FREE BOOK RIGHT NOW!

YOU CERTAINLY KNOW RADIO. MINE NEVER SOUNDED BETTER

N.R.I TRAINING CERTAINLY PAYS. I JUST STARTED A FEW MONTHS AGO AND I'M ALREADY MAKING GOOD MONEY IN MY SPARE TIME.

THANKS!

OH, TOM, IT'S WONDERFUL HOW FAST YOU'VE GONE AHEAD IN RADIO. WE NEVER COULD HAVE GOTTEN MARRIED ON WHAT YOU WERE GETTING BEFORE.

OUR WORRIES ARE OVER. I'M MAKING GOOD MONEY NOW, AND THERE'S A FUTURE AHEAD FOR US IN RADIO.



HERE'S PROOF THAT N.R.I. MEN MAKE GOOD MONEY

\$3,500 a Year in Own Business
 "After completing the N. R. I. Course I became Radio Editor of the Buffalo Courier. Later I started a Radio service business of my own, and have averaged over \$3,500 a year."—T. J. TE-LAAK, 657 Broadway, Buffalo, N. Y.

\$10 to \$25 a Week in Spare Time
 "I am making from \$10 to \$25 a week in spare time while still holding my regular job as a machinist. I owe my success to N. R. I."—WM. F. RUPP, 130 W. 6th Street, Conshohocken, Pa.

GET MY FREE LESSON on Radio Servicing Tips



I'll prove that my Training is practical, money-making information, that it is easy to understand—that it is just what you need to master Radio. My lesson text, "Radio Receiver Troubles—Their Cause and Remedy," covers a long list of Radio receiver troubles in A. C., D. C., battery, universal, auto. T. R. F., superheterodyne, all-wave and other types of sets. And a cross reference system gives you the probable cause and a quick way to locate and remedy these set troubles. A special section is devoted to receiver check-up, alignment, balancing, neutralizing and testing. Get the lesson Free. No obligation. Just mail coupon.

... I will train you to start a spare time or full time Radio service business Without Capital

Many Radio Experts Make \$30, \$50, \$75 a Week

J. E. Smith, President National Radio Institute

Do you want to make more money? The world-wide use of Radio sets has made many opportunities for you to have a spare time or full time Radio service business of your own. Three out of every four homes in the United States have Radio sets which regularly require repairs, servicing, new tubes, etc. Many sets are old and will soon be replaced by new models. I will train you to sell, install, service all types of Radio sets—to start your own Radio service business and build it up. Mail coupon for my 64-page book. It's FREE.

Get Ready Now for a Business of Your Own and for Jobs Like These

Broadcasting stations employ engineers, operators, station managers and pay to \$5,000 a year. Spare time Radio set servicing pays as much as \$20 to \$50 a year—full time Radio servicing jobs as much as \$30, \$50, \$75 a week. Many Radio Experts own and operate their own full time or part time Radio sales and service businesses. Radio manufacturers and jobbers employ testers, inspectors, foremen, engineers, servicemen, paying up to \$6,000 a year. Radio operators on ships get good pay and see the world besides. Automobile, police, aviation, commercial Radio, and loud speaker systems offer good opportunities now and for the future. Television promises many good jobs soon. Men I have trained at home are holding jobs in all these branches of Radio. Read their statements in my 64-page book. Mail the coupon

Many Make \$5, \$10, \$15 a Week Extra in Spare Time While Learning

Practically every neighborhood needs a good spare time serviceman. The day you enroll I start sending you Extra Money Job Sheets. They show you how to do Radio repair jobs that you can cash in on quickly. Throughout your training, I send you plans and ideas that have made good spare time money for hundreds of fellows. I give you special Radio equipment for conducting experiments and building circuits which illustrate important Radio principles. My Training gives you practical experience while learning.

Find Out What Radio Offers You—Mail Coupon Now

Mail the coupon now for my Lesson on Radio Servicing Tips and my book, "Rich Rewards in Radio." Both are free to anyone over 16 years old. My book describes Radio's spare time and full time opportunities, and those coming in television; tells about my Money Back Agreement; shows you actual letters from men I have trained, telling what they are doing and earning. Find out what Radio offers YOU! MAIL THE COUPON in an envelope, or paste it on a Penny postcard—NOW!

J. E. SMITH, President NATIONAL RADIO INSTITUTE Dept. 7GR, Washington, D. C.

MAIL THIS. Get a lesson and 64 page book FREE

Without your book (Please write plainly.)

ACB

STATE TAXI

CITY

ADDRESS

NAME

Dear Mr. Smith: I want to take advantage of your offer. Please send me your "Free Lesson and your book" "Rich Rewards in Radio."

J. E. SMITH, President National Radio Institute, Department 7GR, Washington, D. C.



Edited by LAURENCE MARSHAM COCKADAY

S. GORDON TAYLOR
Managing Editor

WILLIAM C. DORF
Associate Editor

JOHN M. BORST
Technical Editor

JOHN H. POTTS
Assoc. Tech. Editor

HARRY VIERLING
Art Editor

Vol. XIX July, 1937

No. 1

Reading Guide to this Issue—

AMATEURS—2, 3, 4, 8, 9, 10, 11, 13, 14, 16, 20, 21, 25, 26, 28
BROADCAST FANS—1, 2, 3, 4, 25, 26, 28
DEALERS—1, 2, 3, 4, 5, 6, 7, 11, 12, 25, 26, 28
DESIGNERS—2, 4, 8, 10, 14, 25, 26, 28
DX FANS—2, 4, 13, 15, 22, 23, 25, 26, 28
ENGINEERS—2, 3, 4, 8, 9, 10, 11, 25, 26, 28
EXPERIMENTERS—2, 3, 4, 8, 9, 10, 11, 14, 20, 21, 22, 25, 26, 28
MANUFACTURERS—2, 3, 4, 5, 12, 25, 26
OPERATORS—2, 3, 4, 9, 10, 25, 26, 27, 28
SERVICEMEN—2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 20, 21, 25, 26, 28
SET BUILDERS—2, 3, 4, 5, 10, 14, 20, 21, 22, 25, 26, 28
SHORT-WAVE FANS—2, 3, 4, 13, 14, 17, 18, 19, 25, 26, 28
STUDENTS—1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 14, 20, 21, 22, 24, 25, 26, 27, 28
TECHNICIANS—1, 2, 3, 4, 5, 6, 8, 9, 10, 11, 12, 20, 21, 25, 26, 28

Our Apologies

WE wish to apologize to the many new subscribers who asked to have their subscriptions start with the May or June issues of RADIO NEWS. The unusual volume of recent new subscriptions has completely exhausted our supply of these issues and made it necessary to start many subscriptions with the current July number instead of the previous issues ordered.

1	Serviceman's Diary.....	Anonymous	4
2	Radio News Index (January-June 1937 Inclusive).....		5
3	"Empire State" Television Advances.....	The Television Reporter	7
4	What's New in Radio.....		9
5	Profits in Inter-Office Call Systems.....	William C. Dorf	10
6	The Service Bench.....	Zeh Bouck	12
7	The "Scope" in Auto-Radio Servicing.....	Edward M. Scribner	13
8	Building and Using a V. T. Voltmeter.....	R. M. Ellis	14
9	Television Operators Wanted.....	Thomas E. Gooteé	15
10	Resistance-Coupled Amplifiers Designed (Part 2).....	J. van Lienden	16
11	Low-Cost Pre-Amplifier.....	M. N. Beitman	18
12	P. A. Units for the Summer Market.....	H. W. Paro	19
13	The "Ham" Shack (Erecting Antennas).....		20
14	Home-Built 5-Meter Converter.....	Nathaniel Bishop (W1EYM)	22
15	Antennas for DX.....	Wilbert T. Golson	23
16	Testing a "Ham" Transmitter.....	Everett M. Walker	24
17	Short-Wave Station List.....		25
18	The DX Corner for Short Waves.....	Laurence M. Cockaday	28
19	World Short-Wave Time-Table.....	S.W. DX Editor	30
20	A "Closet-Door" Work Bench.....	Walter L. Linde	33
21	The Radio Workshop.....	The Associate Editor	34
22	The Radio Beginner (Part 12).....	John M. Borst	36
23	The DX Corner for the Broadcast Band.....	S. Gordon Taylor	37
24	Students' Radio Physics Course.....	Alfred A. Ghirardi	40
25	The Technical Review.....	The Technical Editor	42
26	Free Booklet Service.....		43
27	Q R D ?.....	By GY	44
28	Revised Don Lee Circuit.....		51

Published Monthly by Teck Publications, Inc., Washington and South Avenues, Dunellen, N. J.

Lee Ellmaker
President and Treas.
B. Holcepl
Secretary

H. D. Crippen W. P. Jeffery
Advertising Management
Virgil Malcher
205 W. Wacker Dr., Chicago
Western Representative

EDITORIAL AND EXECUTIVE OFFICES
461 EIGHTH AVENUE, NEW YORK CITY, N. Y.


Entered as second class matter at the Post Office at Dunellen, N. J., under the act of March 3, 1879. Copyright, 1937, by Teck Publications, Inc., in U. S. and Canada. All rights reserved. Registration of title of this publication as a trade mark applied for in United States Patent Office. Printed in the United States of America. The contents of this magazine must not be reproduced without permission. We cannot be responsible for lost manuscripts, although every care is taken for their safety.

25c a copy. Subscriptions, \$2.50 a year, \$4.00 for two years; in Canada and Foreign Countries \$3.00 a year, \$5.00 for two years. Subscribers are notified that change of address must reach us five weeks in advance of the next date of issue.


Here's Why The
"Philharmonic"
 Sets New Standards!

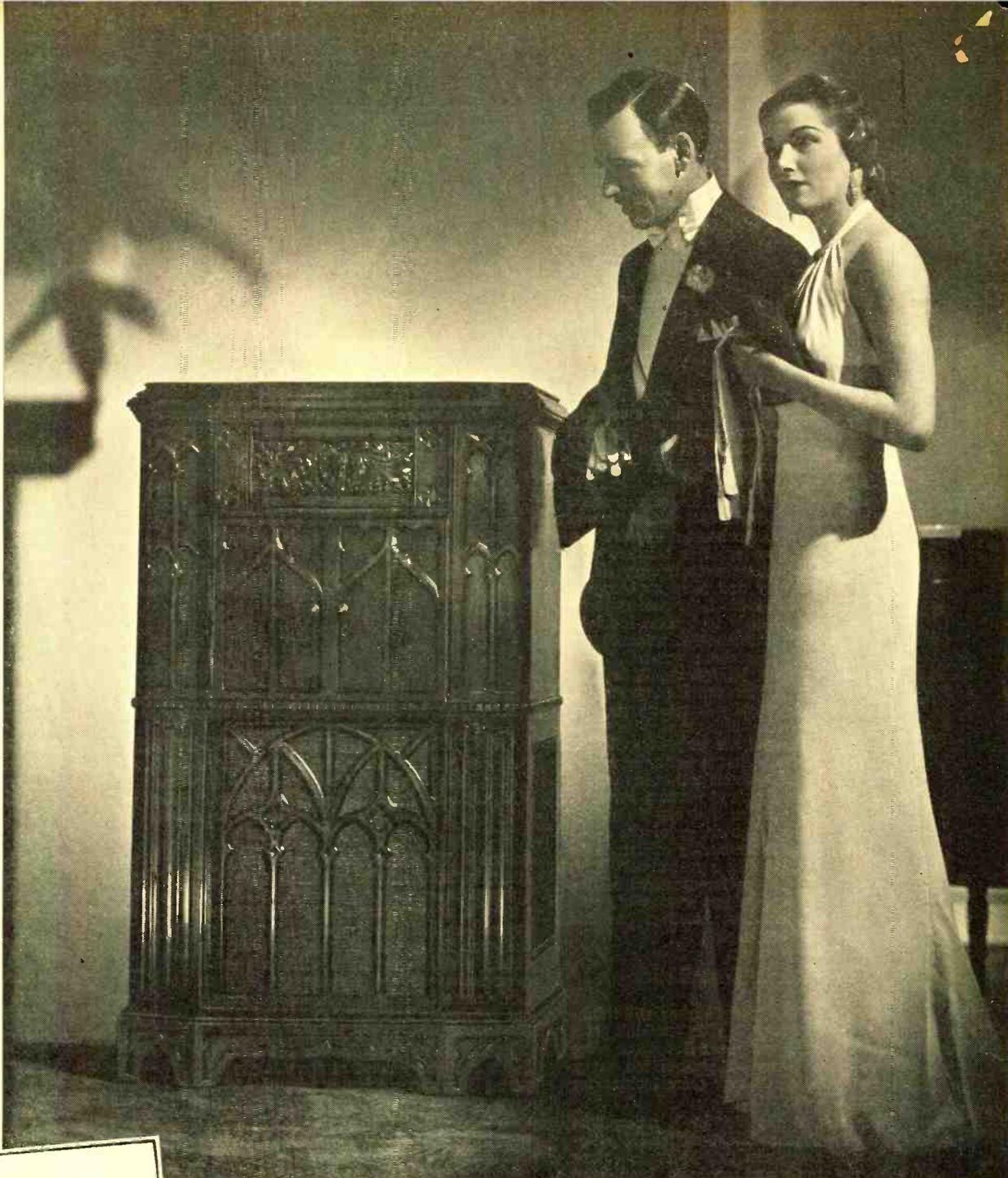1. Covers a *Greater Wave Length Range*. (3.75 to 2000 Meters),
2. Has *Finer Tone and Higher Overall Fidelity*. (From 30 to 16,000 Cycles,
3. Has a *Smoother and More Highly Perfected Continuously Variable High Fidelity Range*,
4. Has *Sharper and More Complete Attenuation* at 10,000 Cycles,
5. Has a *Higher Degree of Selectivity*, which is Continuously Variable from 2 to 16 Kc.,
6. Has *More Perfect Automatic Gain Control Systems* on both R. F. and I. F. Amplifiers,
7. Has *More Usable Sensitivity*,
8. Will Give *Smoother and More Noise-Free Reception of All Programs*, Especially in Difficult Receiving Locations,
9. Has a *More Highly Developed and Distortionless Program Volume Range Expansion System*,
10. Will Give *More Perfect Reproduction from Phonograph Recordings*, Especially the Latest High Fidelity Records,
11. Will Eliminate *Phonograph Needle Scratch at Low Volumes*, Without Affecting Reproduction of *Low, Mid, or High Frequencies* in Any Way at Normal or High Volumes,
12. Is *Custom Built with Greater Precision*—And from Higher Quality Parts,
13. Has *More Advanced Engineering Features* Incorporated in Its Design,

MORE, WE BELIEVE, THAN ANY OTHER RADIO RECEIVER THE WORLD HAS EVER KNOWN!




Custom-Built **BY HAND**

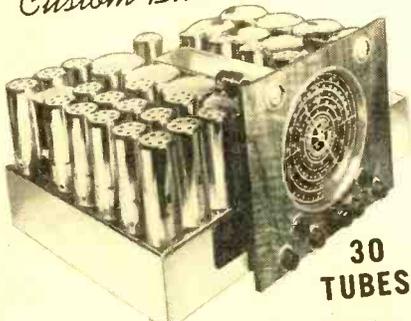

30 TUBES

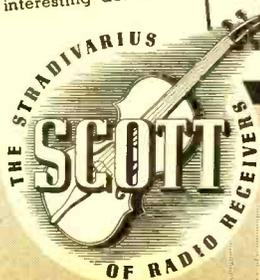See and hear the New 30-TUBE Scott Philharmonic Receiver at our Salons in New York, Chicago, Los Angeles . . . or send the coupon for **FREE** booklet giving interesting details, and laboratory curves. Thrilling 30-day **FREE** trial in your home!



Performance **YOU NEVER THOUGHT POSSIBLE!**

Since 1924 Scott Receivers have been known the world over for their incomparable performance. Sheer merit alone has won for them the preference and praise of noted masters of music, DX enthusiasts, radio engineers and distinguished persons throughout the U. S. and 148 Foreign countries. Now, continuing this tradition, Scott engineers have created an entirely NEW Receiver . . . a superb 30-TUBE musical instrument, so highly perfected, so far advanced in design, performance and beauty that it is not even remotely approached, we believe, by any other receiver in the world. A study of the technical details above will show that the "Philharmonic" is not an ordinary radio. Custom built by hand, it incorporates 8 New Scott Developments (patents applied for). *Greater Wave Length Range* (3.75 to 2000 meters!) gives complete coverage of practically everything on the air . . . it will receive television sound broadcasts. *Greater Tonal Range* (30 to 16,000 cycles) gives for the first time, we believe, perfect reproduction of the entire tonal range of the human ear. *Fifteen Beautiful Cabinets* to suit the most discriminating taste. Get all the surprising details! Send the coupon NOW!

E. H. SCOTT RADIO LABORATORIES, INC.
 4440 RAVENSWOOD AVENUE, DEPT. 5M7, CHICAGO, ILLINOIS
 Please mail me details about the new Scott Philharmonic Receiver. No obligation.
 (Sold direct from Scott Studios ONLY. No dealers).

NAME

ADDRESS

Pages From A Serviceman's DIARY

FRIDAY—How would you like to establish yourself abroad, in a country where there are plenty of expensive sets, many dealers, and yet not a single man who knows anything about radio repairing—where a leading dealer offers excellent shop facilities and his service trade absolutely free and will cooperate with you in building up a larger business—where you can knock out two or three hundred dollars a month or more working only six or seven hours a day and have no competition? The climate is ideal, the scenery beautiful and it is unlikely to become involved in war. If you're interested, write to the Editor and tell him about yourself. If he thinks you will fit in, full details will be forwarded. Remember, this is not a salaried job—it's an opportunity to start your own business with very little capital in ideal territory. There will not only be radios to service, but also sound movies, broadcast transmitters, P.A. systems and nearly everything else which employs vacuum tubes. If you are an American and can fix radios and possess some knowledge of the other fields as well as a smattering of French or Spanish, this looks like a real opportunity. You will need only a few hundred dollars reserve funds to tide you over while getting started, plus some modern portable test equipment and tools.


A Quick Installation

Drove off to the yacht harbor, still thinking of the foreign job. Who wouldn't get a kick out of such a chance? But it's no place for a married man; there are too many unattached damsels over there looking for attention.

Was met at the pier by a sailor, who helped me load an RCA model 123 auto-radio and accessories into a dinghy, along with my tools and analyzer (you need everything for boat installations). He rowed out to a small cabin cruiser anchored in the harbor. The owner wants only a temporary installation for a month's cruise, after which the set is to be removed and installed in his car. Salt air is not so good for any radio, so we thought this a good idea to recommend, particularly since he could not afford two sets but would not object to having two installations, which would bring us about the same net profit.

The set was mounted on a panel previously prepared for the job, with a cut-out for the speaker. There is very little available space in small boats for radio so this had to fit into the door leading from the cabin to the prow. For the aerial, always a headache on such boats, the new "towel rack" auto-radio type was selected. It can be installed quickly without marring the woodwork by means of its rubber suction mounting supports and can be removed easily when not needed.

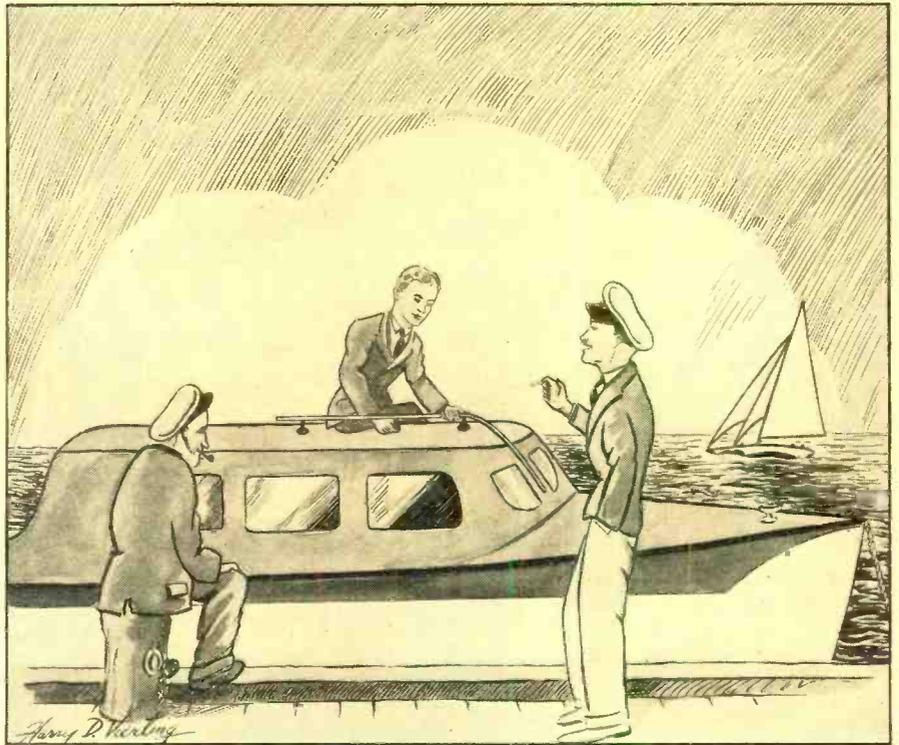Cleaned up this job in a reasonably short time and stopped at the club restaurant for a bite, even though it was a little early for lunch. Then went on to a noon-time date with a Radiola 48, owned by a charming young woman with an old but wealthy



SERVICEMAN: HERE'S A "TWO-IN-ONE" JOB THAT'S PROFITABLE
A thrifty boat-owner, sold on the idea of having an auto radio installed on his boat, then at the end of the cruise (or season) having it transferred to his car. Money saved for the owner—and two installation jobs for the serviceman, with perhaps two more next season.

husband. They have other sets but this one is a tuned r.f. job which is unusually quiet when operating properly. I found it needed a new volume control on a previous call, so brought it along to replace on the spot. It is not practical to pull the chassis on this set due to its mechanical construction so the replacement is most easily made by simply swinging the chassis out into your lap while seated on a low stool or a turned-over kitchen chair.

Pulled up in front of this old Colonial house and was greeted at the door by the young lady, apparently not fully clad. "You came a little earlier than I expected," she said, "but I'm very glad to see you are so prompt."

Seeing America First

I stopped at the kitchen and picked up a small folding step-ladder then went with her to the front room and started to work on the set. She flopped down on a couch and made herself comfortable. I told her about the yacht job I had just done and also about the letter from abroad. She seemed much interested about Europe and asked many questions about places which I had visited years before. "I hope I am

not exposing my ignorance," she laughed, negligently swinging a silk-clad leg over the arm of the sofa, "but don't you think you should see America first?"

Scenery Improves

The scenery here, I began to realize, deserved far more attention than it had been given. I attempted to solder the shield-wire to the new volume control but unfortunately pushed the hot iron against my thumb. A yellowish-white spot formed which will soon blossom out into a nice blister. Funny how absent-minded a fellow will get at times!

As a rule, I believe it is better never to do any set repair work in the customer's home. But, like all rules, there are exceptions.

6W5G

NEW YORK, N. Y.—A new rectifier tube, the 6W5G, has been announced by Raytheon. It is a high-vacuum full-wave rectifier of the indirectly heated type with the cathode insulated from the filament. It can be used to replace the 6X5 and 6X5G in automobile receivers when a higher rating is desired. The maximum a.c. voltage per plate is 350 volts r.m.s.; the maximum output current is 100 ma. d.c. and the maximum voltage between heater and cathode is 500 volts. The filament requires 6.3 volts at 0.9 amps. The octal base has 6 pins, which connect as follows: 1, no connection; 2, heater; 3, plate; 5, plate; 7, heater; 8, cathode.

New Station for Rome

NEW YORK, N. Y.—The Italian Broadcasting Company has placed an order for a 100 kw. short-wave transmitter with the Electrical Apparatus Company of Milan, an affiliate and licensee of the I. T. & T. This station is to be installed in Rome and go into service in 1938.

THESSE records from an anonymous serviceman's diary should be of decided interest to veteran servicemen, as well as to those whose experience in the service field is more limited. Written by a man who "knows his stuff," and shot with an occasional outcropping of humor, these items provide many hints not found in text books. More of these pages will appear from time to time.

RADIO NEWS INDEX

VOLUME XVIII, NUMBER 7 January, 1937 Page

Television For The British Public.....	391
Radio In the Spanish War.....	394
Sound Systems Speed News Distribution.....	395
What Do You Want to Know About Microphones.....	395
Five-Meter Rotary "Beam".....	396
Pocket Size Two-Way Radio.....	397
Crystal Control for 5-10-20 Meters (Part 1).....	398
The "Ham" Shack (Carrier Shift Indicator).....	400
The 807 Tube For Amateurs.....	401
Superregenerative U.H.F. Receivers.....	402
Servicemen's Prize Contest Awards.....	405
The Matter of Service Charges.....	406
Call Systems as a Side Line (Carrier Call).....	407
New Unidirectional Mike (RCA 77A Dynamic).....	407
Exposing Cut-Rate Service "Gyps" (Part 2).....	408
New Circuit for Volume Expansion (RCA 6L7).....	409
Phase Inversion for Push-Pull Circuits.....	410
The Radio Beginner (T.R.F. and Superhets) Part 8.....	411
Station List (U.S. by Call Letters).....	414
Radio News Index (July-December 1936, Inclusive).....	423
The Radio Workshop.....	424
Students' Radio Physics Course (Filters).....	428

VOLUME XVIII, NUMBER 8 February, 1937

The Next Ten Years of Television.....	457
Avoiding Cut-Rate Service Gyps (Part 3).....	460
Tuning Indicator for Hams.....	461
Self-Contained Portable P.A. System (M. Silver 6L6 Amplifier).....	463
Kelley Oscilloscope, Using the Type 913 Tube.....	464
4-Tube Volume Expander (Allied-Knight).....	465
The DX "Clipper" Regenerative Receiver.....	466
"Silent" Radio (Dictograph 6-Tube Super).....	467
The Ham Shack (Amateur's Modulation Problems).....	468
New Transmitter at W2JCY.....	468
Testing a 1-to-10-Meter Receiver (National One-Ten).....	469
The New RK-39 U.F.H. Tube.....	469
Crystal Control for 5-10-20 Meters (Part 2).....	470
Amateur Radio Coast Guard Station.....	471
Superregenerative U.H.F. Receivers (Part 2).....	472
Reducing S.W. Interference.....	473
New Advances in Superhet Design (Hammarlund Super-Pro).....	474
New Zealand-The DX-ers Paradise.....	475
R.N. Listening Post Organization (Regulations and Reports).....	478
Students' Radio Physics Course (Low-Pass Filters).....	488

VOLUME XVIII, NUMBER 9 March, 1937

Italy's Progress in Television.....	519
Correct Time By Radio.....	520
Building the "Quartet" 5-10 Meter Super.....	522
The "Ham" Shack (Reducing Interference on Phone Bands).....	524
The CQ'er II, ICW Unit.....	526
Superregenerative UHF Receivers (Part 3).....	527
Crystal Control for 5-10-20 Meters (Part 3).....	528
Build Your Own Work Bench.....	529
Kelley Oscilloscope with Linear Sweep.....	530
Suggested Trends in P.A. Design.....	533
6-Volt Battery Operates 10-watt Amplifier.....	534
Measurement Standards and Reference Levels.....	535
Broadcast Chain Networks.....	538
Testing the Latest "Pro" Super (Hammarlund-Pro Super).....	539
The Radio Beginner (Tuned R.F. Set) Part 9.....	540
Time Saving Log for DX'ers (Rotolog).....	541
Students' Radio Physics Course (Filters for Power Units).....	550
The Radio Workshop.....	566

VOLUME XVIII, NUMBER 10 April, 1937

The Navy Amateur Net.....	583
Choosing a Radio School.....	586
New Market for Inventions.....	587
The R.N. "Capatron" Signal Generator.....	588
Bridge Analyzer Solves Service Problems.....	591
The Radio Workshop.....	592
Modernistic Network Studios.....	596
Antenna Coupler Kills Noise (Scott All-Wave Set).....	596
Station List (North America Exclusive of the U. S.).....	597
"Sure-Fire" 2-Tube, 5-Meter, M.O.P.A.....	598
The 806 Tube.....	599
The "Ham" Shack (Push to Talk).....	600
Direct Reading Modulation Meter (Triplet Model 1295).....	601
The "Quartet" 5-10 Meter Super (Part 2).....	602
New Receiver is "H.A.C." Nightly (Hallicrafters Super Skyrider).....	604
The Radio Beginner Considers A.V.C. (Part 10).....	605
Students' Radio Physics Course (High-Pass Filters).....	614

VOLUME XVIII, NUMBER 11 May, 1937

Do You Want to Become a "Ham?".....	647
Building a Don Lee Television Receiver.....	649
Television Ready but "Under Wraps" (Philco Demonstration).....	652
New Farnsworth Television Station.....	654
Oscillographs as Money Makers.....	657
Calibrating the R.N. "Capatron" Oscillator.....	658
Growing Dollars in the P.A. Field.....	659
Kelley Direct Coupled Amplifier.....	660
Thoughts on 10-meter Receivers.....	661
The Amateur's Part in Flood Relief.....	662
The "Ham" Shack (10-meter Antennas).....	664
How to Build a 10-Meter Converter.....	666
Station List for Central and South Americas (Broadcast Band).....	670
The Radio Workshop.....	671
Coil Data for Crystal U.H.F. Transmitter.....	689

VOLUME XVIII, NUMBER 12 June, 1937


World Distance Map (Centered Washington, D. C.).....	709
Short Waves in the Classroom.....	711
Time Conversion Chart.....	719
More About Time Signals.....	720
Wavelength-Frequency Conversion Chart.....	721
Testing a Three-Band Superhet (Lafayette B81).....	722
U. S. and World-Wide Mileage Chart.....	723
Short-Wave Station List of the World.....	724
Low-Priced Super (Knight 8-Tube Set).....	727
Where to Write for Short-Wave Veri's.....	728
The "Quartet" 5-10-Meter Super (Part 3).....	730
Remember May Ninth (5-Meter DX).....	731
The "Ham" Shack (Learning the Code).....	732
C-Bias Supply for Amateurs.....	733
5-Meter Receiver-Transmitter.....	734
An Evening With New 500-22,000 Kc. Super (R.C.A. Model ACR 155).....	736
The Radio Beginner (Part 11 Oscillator and Mixers).....	737
Design Chart for Resistance-Coupled Amplifiers (Pentodes).....	739
Building a 60-Watt Amplifier with Negative Feedback.....	740
Students' Radio Physics Course (Band Pass F. Circuits).....	744
New Zealand Broadcast Listeners.....	767

YES...

**MALLORY-YAXLEY
has done more...
but MALLORY-YAXLEY
does not charge more!**



**MALLORY
CONDENSERS
cost
no more!**

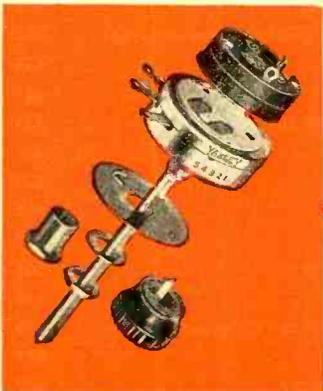

**YAXLEY
VOLUME
CONTROLS
cost
no more!**



**MALLORY
VIBRATORS
cost
no more!**

**MALLORY-YAXLEY
Precision Radio REPLACEMENT
PARTS COST NO MORE
THAN ORDINARY PRODUCTS**

Every once in a while there's an idea that because Mallory-Yaxley products have a reputation for higher quality that they must be higher in price. A service man feels that he ought to use them but he thinks that maybe he can't afford to use them.

Mallory-Yaxley are *big*, he reasons, they'd have to be big to put out a help like the Mallory-Yaxley Radio Service Encyclopedia. They'd have to be big to have given the industry its first real honest-to-goodness Vibrator, Volume Control, and Condenser Service and Replacement Manuals. And the very size of Mallory-Yaxley—the wide scope and the great help of Mallory-Yaxley activities gives him a bad case of "price fright".

He thinks the products of the little fellow may be cheaper . . . and of course he finds plenty of people who'll encourage this belief.

Then some day he checks prices and makes comparisons. He finds that Mallory-Yaxley products *do not* "cost too much"—he finds that Mallory-Yaxley Precision Radio Replacement Parts *do not cost any more than ordinary replacement parts*. He finds they create the kind of customer satisfaction that helps his reputation and his bank account. He puts his radio servicing on easier and a more profitable basis.

It may be that *you* believe that because Mallory-Yaxley have done more for the service man that they expect to *charge more from* the service man. We say that isn't true and don't want you to take our word for it—or any man's word for it. You can compare prices and see for yourself! And—the more Mallory-Yaxley installations you make, the more you'll realize that the complete satisfaction assured by these precision replacement parts makes them *actually cost less in the long run*.



**THE RIGHT "DOPE" On
Over 12,000 Different Radios**

. . . Completely analyzed under *one cover* . . . in the **MALLORY-YAXLEY RADIO SERVICE ENCYCLOPEDIA**. The book that gives the correct answers to all questions—always! Ask the Mallory-Yaxley distributor about *your copy now!*

Use
P. R. MALLORY & CO., Inc.
MALLORY
REPLACEMENT
CONDENSERS... VIBRATORS

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
CABLE ADDRESS—PELMALLO

Use
YAXLEY
REPLACEMENT
VOLUME CONTROLS

Radio News

July, 1937

"Empire State" TELEVISION *Shows Marked Advance*

Latest experimental transmissions from the NBC television transmitter using the new standard 441-line picture bring video images to a point of clarity in marked contrast to earlier efforts. Field tests continue.

By the Television Reporter

LIKE its chief rivals in the race for American television supremacy, the Radio Corporation of America has adopted the 441-line picture standard recommended by the Radio Manufacturers' Association. In this move, RCA was paralleled by Philco and Farnsworth. These new systems were described in May, 1937, RADIO NEWS. This arbitrary agreement on standards between rival contenders for national leadership in sight transmissions is conceded to be one of the greatest strides made toward the establishment of the new industry.

RCA, joined in its television ventures by its energetic subsidiary—the National Broadcasting Company—is always quick on the trigger in its developmental activities but ever conservative in announcing its new findings. And this has been especially true in television.

More Optimism

As far as public statements were concerned, this company always maintained a timidity in relating its experiments with visual transmissions. But, now, with the definition boost to 441 lines—a much higher element image than England's—we find a more optimistic tone in the television statements of the company's chieftains.

This was particularly noted in the Annual Re-

port for the year ending December 31, 1936, by General James G. Harbord, chairman of the board, and David Sarnoff, president. Instead of the anticipated prediction of an indefinite period of development, the report, while not offering an exact prediction of television's commercial arrival, contains the phrase: "The need for additional experimentation indicates that this work will continue for some months to come." To this writer—and to many industry leaders—the use of the word "months" rather than years by the television-conservative RCA heads does truly indicate that sight broadcasting will soon turn that much exploited corner after traveling in a straight line for years.


SHE WILL VISIT YOU AT HOME

Betty Goodwin, NBC's television announcer, as she appears on the screen of the RCA television receiver. When commercial broadcasts are started, you may expect to see and hear her as a regular visitor in your living room.



Finer Images

NBC experimental transmissions from the video station atop the Empire State Building in New York were boosted from 343 to 441 lines last January. The earlier standard was put into effect in June, 1936. In just little more than a half-year, the definition grew by 100 lines! A finer image was achieved. The photographs accompanying this article contain reproductions of actual images received over the air on the new standard. Here, indeed, is progress! Even the non-technical observer is readily impressed by such evidence.

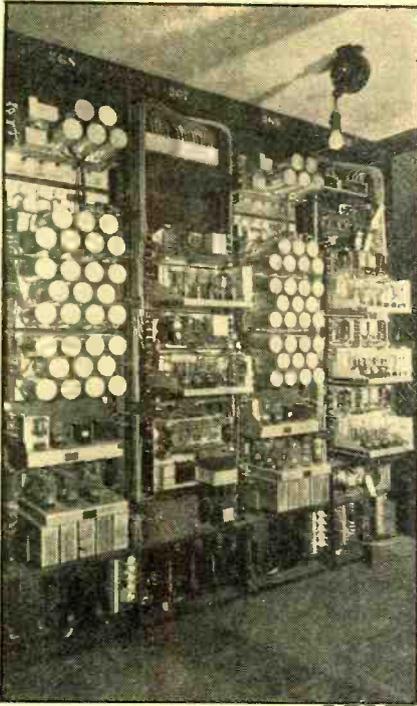

BEHIND THE SCENES

This apparatus, the synchronizing signal generator, is the heart of the experimental television system.


The Empire State transmitter is fed by a coaxial transmission line with programs originating in the NBC television studio in Radio City—about three-quarters of a mile away. The picture wave-frequency is 49.5 megacycles while the sound channel is 52.75 megacycles; provision of 2.5 megacycles is made on each side of carrier. The 441-line system is employed at 30 frames per second. Messrs. Sarnoff and Harbord declared that, in the field tests now in progress, images of motion pictures as well as live performers are being successfully received in about 100 homes of RCA engineers in the metropolitan New York area and in the outlying suburbs.

Larger Service Area

"The distance over which these television programs have been received," they stated, "has exceeded our immediate expectations. In one favorable location programs have been consistently received as far as 45 miles from the

"FELIX" IS NOW A GUINEA PIG!

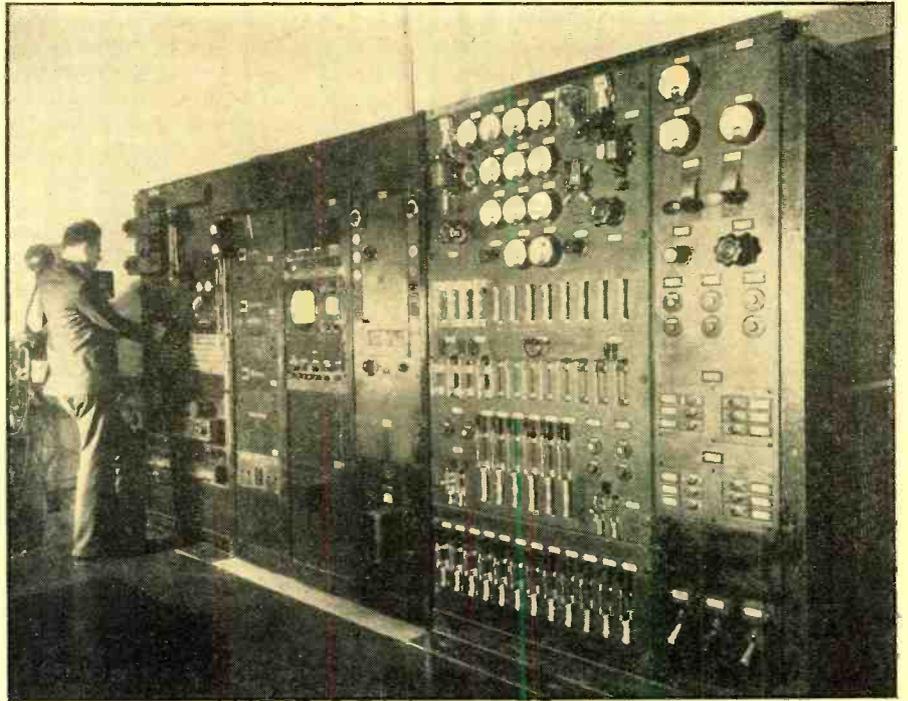This photograph of the grinning cat was received over the new 441-line system. No longer a "ghost" but clear and distinct in every detail.



TELEVISION OPERATORS WILL HAVE PLENTY TO DO

One glance at this Empire State transmitter control board would indicate that future television operators have plenty to learn to thoroughly understand their job. Thus television has become an added subject in radio schools.

television transmitter."

In answer to the writer's query on the power used for television transmissions, NBC referred to a paper by R. R. Beal, RCA Research Supervisor, which stated that "the filament power is sufficient to produce an electron emission of 18 amperes per tube which permits a video carrier power of 8 kw. With a tank circuit loading to pass the 1.5 mc. sidebands." The paper, though, was based on the old 343-line standard and while the author set forth some facts on the boost in definition, no exact mention was made of the new power rating. Likewise, there is still some reluctance to give out data on the probable cost of receivers, the number of tubes to be used in home models, etc. The parent company and the subsidiary hold that it

TELEVISION'S CONTROL ROOM

It takes three trained engineers, pictured below, to keep the system working satisfactorily. In the foreground: One monitors the sound. Center: The program director. At rear: A third engineer monitors the video system.



is premature to make such statements as the definite day for public participation and commercial programs has not been named.


It is understood that the 100 test receivers around the New York area retain the tuning range of 42 to 84 megacycles. As in the case of other leading systems, the receiver gets sight and sound simultaneously. Single-knob tuning is employed and separating is easily achieved by the spacing of the transmitted carriers. A complex array antenna to produce a horizontally polarized field is employed.

Collecting U.H.F. Data

That the tests have been highly instructive was emphasized in the Sarnoff-Harbord report. "Much has been learned about the behavior of ultra-short waves and how to handle them," they stated. "More is known about interferences, most of which are man-made and susceptible of elimina- (Turn to page 60)

A "GHOST" OF YEARS AGO

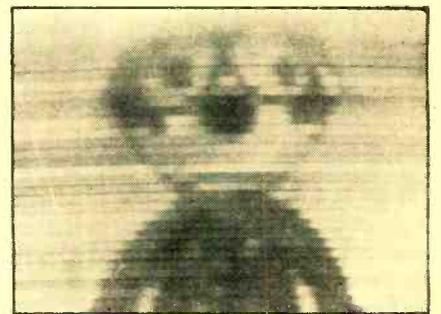This is Felix as photographed a few years ago with the early 60-line transmissions. Compare this picture with the one on the left of this page.



WHAT'S NEW in RADIO

By The Associate Editor

Twin Gadgets for Radio Trouble Shooting

Two new pocket-size trouble shooting cards were recently announced by Alfred A. Ghirardi, author of "Modern Radio Servicing" and other well known radio books. These eyeleted, conveniently indexed cards list all common radio troubles in home and automobile radio receivers. They not only give the probable remedy for each trouble, but also indicate exactly what test to make to definitely "spot" it. The card covering home radio sets is a new, revised, and enlarged edition of Ghirardi's Pocket Trouble Shooter.

Panel Control Kits for All Cars

Because car owners have become "interior-conscious" during the past few years, General Electric has designed a series of instrument panel-board radio control units for the new 1937 "G-E" auto radios to harmonize with the interiors of 1937, '36 and '35 models of all leading makes of cars from Plymouth to Packard.

For cars over three years old, there's an attractive underpanel-mounting control which goes well with any instrument panel. Each individual kit contains an escutcheon plate, essential hardware and control knobs which all harmonize with the instrument panel-board for which it was designed.

New 15-Tube Set Delivers 15-Watts and Uses 15 Inch Speaker

The Emerson model X146 High-Fidelity superheterodyne is equipped with a number of new developments that will recommend it to both the short-wave and broad-



WILL WE HAVE STEREOSCOPIC TELEVISION?

Manfred von Ardenne, German television expert, shows the apparatus with which he can produce stereoscopic moving pictures. If it can be done with movies, we might expect to see three-dimensional television scenes in the future.

cast listener. It employs 15 tubes comprising two 6K7's, one 6A8, seven 6C5's, two 6F6's, two 80's and one 6G5 tuning eye. Covers a tuning range from 16 to 555 meters, has full range volume expansion, and features the "Gemloid" time-tuning indirectly lighted dial with band-spread pointer and mechanical band-spread tuning. The band indicator identifies tuning band in use.

Replacement Condensers For Refrigerator Servicing

A still greater variety and a larger choice of replacement condensers for electric refrigerator servicing is announced by the Aerovox Corporation. Many exact duplicate replacement units have been added to the line and are listed in their new catalog. The catalog lists the various brands and types of electric motors used for refrigerator and other motor-driven appliances, together with their capacitor specifications.

De-luxe Receiver

Setting a new standard for artistry in radio receiver cabinet design, the Scott Radio Laboratories recently announced the "Georgian" model, the latest addition to their line of custom-built de-luxe receivers. This striking console, of distinctive period design, measuring 55 inches high by 52 inches wide by 22 inches deep, houses the Scott 30-tube Philharmonic chassis. It is

equipped with 3 speakers, a standard 15 inch type and two reproducers to cover the high frequencies. This model features a new type record changer that plays both sides of the record, also the new Scott "no-needle-scratch feature" which practically eliminates annoying needle scratch, without cutting off the high frequencies.




Midget Condensers

The Allen D. Cardwell Mfg. Company is producing a new line of standard double section "Trim-Air" midget condensers. The condensers use Isolantite insulation and they are constructed with sturdy over-size double bearings. A 1/4 inch shaft extends at the rear for additional ganging.

New Auto Guide Saves Time and Miles

The Hull "Streamline," airplane type auto compass, of interest to any one owning an automobile, has special possibilities for the radio amateur. This instrument is of the liquid type, the dial rotating on a sapphire pivot. It tells your direction of travel every instant—changing with the slightest bend in the road. For the "Ham" it should be a worthwhile and convenient asset in direction finding and in use with mobile transmitting equipment. For general use it is an excellent guide for tourists

(Turn to page 52)

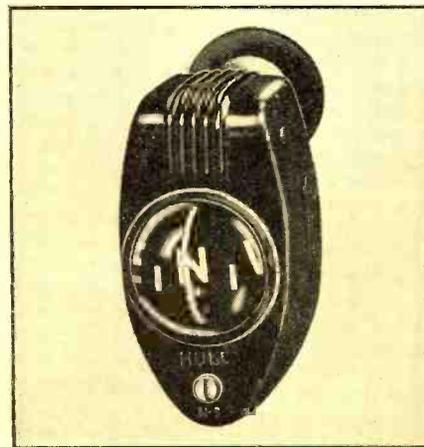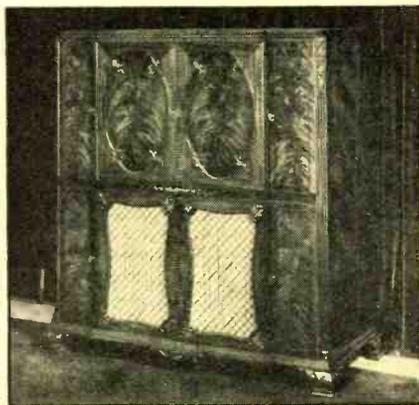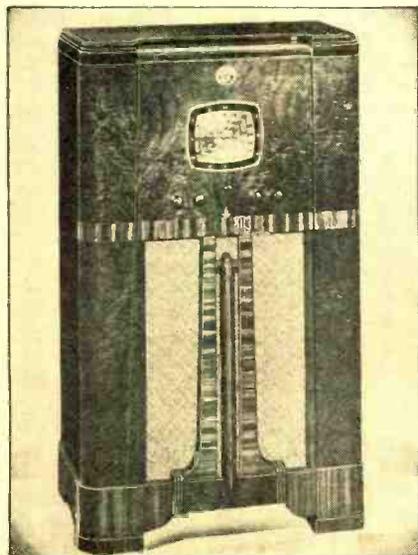



1a

Good Profits in "INTER Communication by

To borrow an appropriate slang cation systems "have gone over with were only two or three companies kind, but radio manufacturers were field and now there are over a score tiple call systems designed

By William

SERVICEMEN and dealers who have taken on inter-communication systems as a sideline, report that public response has exceeded their best expectations. No special sales ability is required to sell these new instruments, they literally speak for themselves and often; the first demonstration means a sale. Installing any one of the instruments described in this article is simplicity itself. It requires no technical ability or special tools.

The market for call-systems is practically unlimited. Their applications range from all types of installations in offices, hotels, department stores, restaurants, and amusement places. Private homes, both large and small, find excellent use for them. The business executive and the professional man are finding in this new device a means whereby they save time and money and promote efficiency in their organization. Special inter-phone systems are now available for auto trailers. Simultaneous two-way talk is possible between the trailer and the car, the driver can talk and listen without taking his eyes from the road or his hands from the wheel.


The systems are divided into two general types, those that use connecting wires between stations and others that transmit the speech over the electric light lines. They are available in two-way and multiple systems, employing as high as eighteen stations.

Instant Two-Way Communication

THE "Philcophone" made by the Philco Radio and Television Corp. provides instant, two-way communication between a master control unit and from one to four remote units (see Nos. 1a and 1b). From the master control you can carry on a strictly private two-way conversation with any one of the remote units or talk with all four at the same time. The instrument features low initial cost, low current consumption and simple installation, which requires merely a wiring connection from the various stations to the master control. The master unit measures $10\frac{1}{2}$ by $8\frac{3}{4}$ inches by $5\frac{5}{8}$ inches, sufficiently small to stand on the ordinary desk without taking up valuable space. The remote stations measure $6\frac{7}{8}$ by $6\frac{7}{8}$ by $3\frac{3}{4}$ inches. The cabinets housing both units are finished in walnut and designed to harmonize with home or office surroundings. The system operates from either alternating or direct current. The master unit utilizes the following type tubes: two 6K5G's, one 25A6G, and one 25Z6G.


"Electro Call"

THE model 202 "Electro Call" inter-communication system (see No. 9) is a product of the United Scientific Laboratories, Inc. It is a multiple selective-system, consisting of a master station and as many as six outlying or branch stations, permitting instant two-way amplifying conversation with various individual departments. The single unit without switching facilities, model 200 (see No. 2) can be employed for two-station communication. Switching devices located on the back of the instrument conveniently control the voice and signal amplification. Both units operate from either alter-

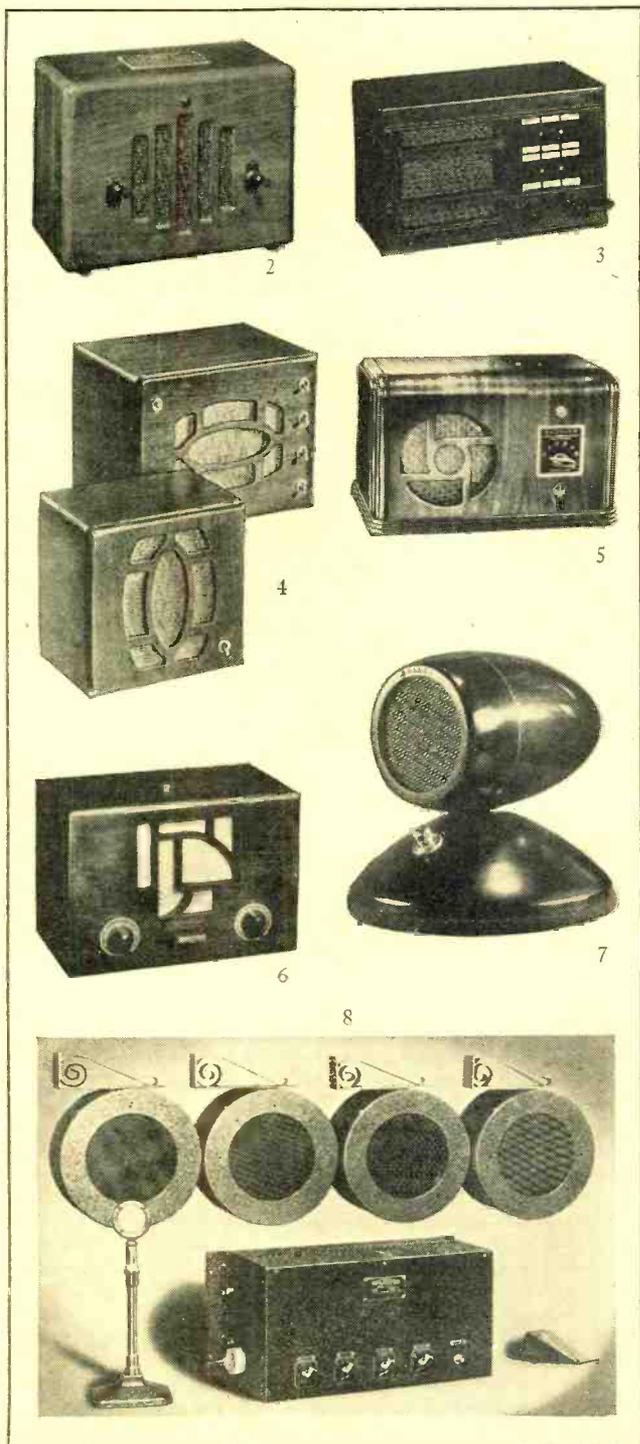

Call Systems for OFFICE"

Wire and Radio

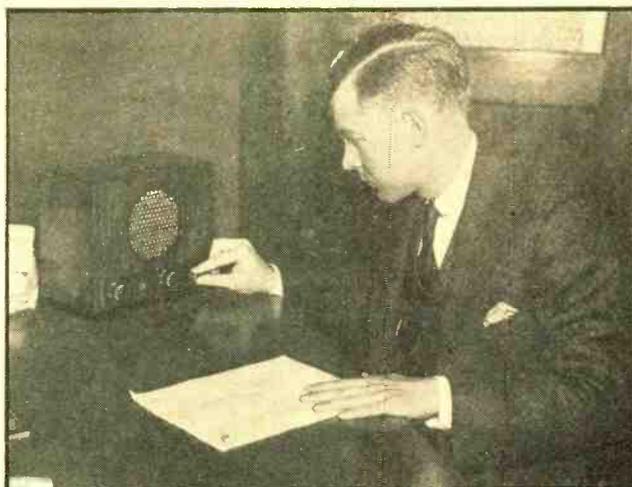

expression, the new inter-communication a bang." Not so long ago there specializing in equipment of this quick to see the possibilities in this of companies offering single and mul- to meet all requirements

C. Dorf

nating or direct current. They use connecting wires between stations.

Simple to Install and Operate

THIS multiple system permits communication between a master station and up to twelve outlying stations (see No. 3). It is made by the Remler Company, Ltd. and, as the manufacturer points out, the owner can start with the master unit and one or more branch stations and at a later time, install additional stations up to the maximum of twelve, thus providing for expansion for this communication service when needed. Metal type tubes are used in the master unit, comprising one 6N7, one 6F6, and one 5Z4 rectifier. A connecting line (single conductor and shield) hooks up the master unit to each secondary station. The system is designed to provide an audio power output of 2½ watts. Both master and secondary units are mounted in moulded bakelite cabinets, 5 by 6¾ by 10 inches.

Announces Complete Line

THE Allied Radio Corp., introduces a complete line of inter-communication systems of the latest design to meet practically every need in this field. They include simple two-way outfits, master station call systems, and super-selective systems, as well as large factory calling equipment. The selective master station system (see No. 4) is designed for centralized control of inter-communication between the master unit and up to four sub-stations. The system comprises one master station unit with tubes, two sub-stations with 50-foot connecting cables and polarized connecting plugs. The tubes employed in the master unit consist of one 6C6, one 25L6 and one 25Z5.


Push-Button Gives Instant Automatic Direct-Communication

UP to five outlying stations may be used with the new Radolek master call-system (see No. 5). When the desired outlying station is selected on the selector control of the master station, you merely push the button to talk and release to listen. Outlying stations calling to the master station must press a button until identified, after that both sides of the conversation are controlled at the master station. The instrument is designed to be operated by means of connecting wires between stations. This company is in a position to furnish dealers and servicemen with a free illustrative booklet describing this and other communication systems.

"Belfone"

THE "Belfone" inter-communication device made by the Bell Sound Systems, Inc., measures only 5¼ by 7 by 9 inches and is no larger than a midget radio. Its installation is as simple as a system of buzzers. An ordinary twisted cable is used for inter-connecting the call units.

The master unit (see No. 6) employs a special permanent magnet dynamic-type speaker which serves both as the re-producer and microphone. The (Continued on page 54)

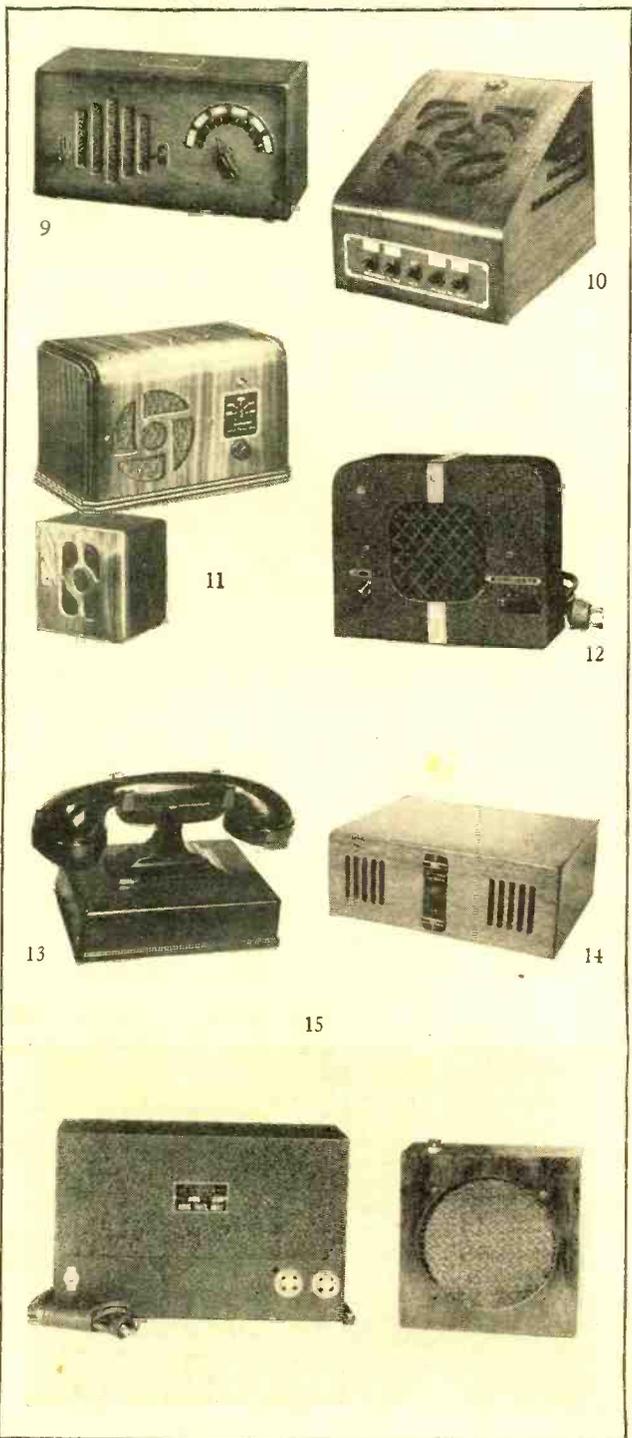

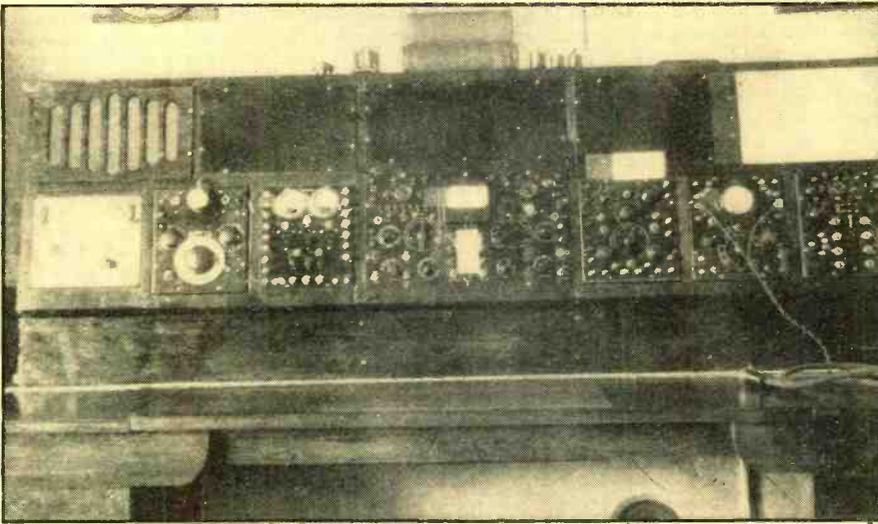


FIGURE 2
Complete service equipment and 100% home design and manufacture.

THE SERVICE BENCH

Free Inspection Again . . . Service Shops . . . Standard Frequency Transmissions
. . . Service Notes . . . Wattage Tests . . . Selling Sound . . . Service Sales Promotion . . .
SERVICING: Stewart-Warner . . . Dewald

Conducted by Zeh Bouck, Service Editor ANOTHER SOLUTION TO THE FREE INSPECTION PROBLEM

IN this department for May we pointed out that a "free inspection" policy was often good business and perfectly justifiable if absorbed by the advertising budget. The profit in free inspections, of course, bears a direct ratio to the number of service jobs resulting from such inspections.

IN an effort to raise the serviceman's battling average in this respect close to the one hundred percent mark, National Union has introduced a system that effects a compromise between free inspection and a charge for examination. Actually free inspection is provided *only when it results in a service job!*

The client is charged one dollar for inspection, and handed the "service rebate certificate" shown in Figure 1. This is filled out with the customer's name, date and an estimate of what the job will cost. This certificate can be redeemed for one dollar against the cost of the service job any time within sixty days, thus nullifying the charge for inspection. Of course, if the customer consents to having his re-



ceiver serviced then and there, no charge is made for inspection and no rebate certificate is issued.

The service rebate certificate can also be used in general sales promotion by mailing to a selected list of customers. This will remind many of them that it is time to have their receivers checked (particularly if the certificate is accompanied with a good sales letter or circular), and most of them will call upon the serviceman within the sixty-day, one-dollar-off period.

As a matter of sound business, at the expiration of sixty days, the number of certificates redeemed should be counted and the value of free service rendered should

be added to the advertising budget over some future period and thus automatically absorbed as future job costs are computed.

THIS MONTH'S SERVICE SHOP

N. Davy, Philco dealer of Birch River, Manitoba, Canada, sends us the accompanying photograph, Figure 2, of his Service Bench. As he puts it, this is really a test bench, the heavy mechanical work being done on a workbench. The particular feature about this layout is the fact that every bit of equipment in it is of home design and construction. The bench is 30 inches high—a comfortable sitting height—17 inches wide and seven feet long. Plenty of elbow room in all directions with four blank panels for future additions in the way of equipment. Recessed in the bench at the left is a phono turntable and pick-up. The center section of the bench is also removable, and discloses a set of clamps which permit the operation of a receiver in an inverted position at bench level. A large baffle board, upon which are mounted a large and a small speaker, can be partially discerned under the bench. The test equipment includes a capacity bridge for measuring small capacities, an all-wave oscillator that can be modulated from any external source, a complete tube tester for emission and amplification tests, a condenser tester, and of course full provision for all voltage, current and resistance measurements.

THE DAY'S WORK

Arnold West, of Scotia, N. Y., points out the fact that while the American broadcasting stations provide a wholly satisfactory check for the all-wave oscillator on the lower broadcast frequencies, the international short-wave stations cannot be similarly depended upon. Changes in sched-

ules, shift of frequency and the unreliability of foreign frequency statements make a calibration check on the short waves pretty much of a haphazard proposition if such stations are depended upon. Some servicemen resort to the laborious method of calibrating by means of harmonics. Mr. West makes the logical suggestion that the servicemen avail themselves of:

The Bureau of Standards Standard Frequency Transmissions

"WWV, the station of the National Bureau of Standards, transmitting from Washington, D. C., sends a standard frequency test on three frequencies, three times a week. The test days are Tuesday, Wednesday and Friday. The frequency of transmission from 12 noon to 1 p.m. is 15,000 kilocycles. From 1:15 to 2:15 the frequency is 10,000 kilocycles, and from 2:30 to 3:30 the frequency used is 5000 kilocycles.

"The Wednesday transmissions are by tone-modulated c.w., the modulation being at 1000 cycles. The tone is continuous for one hour, without announcement of any kind except at the beginning of the period, when the announcement is made in voice (on Wednesday only). The signal cannot be missed even if the announcement is not heard.

"On Tuesdays and Fridays, the transmission is exactly the same, excepting that pure c.w. is employed, and the station announces in code. (However, once again, no difficulty should be experienced in locating WWV, its presence being indicated by the long—one hour—period with constant carrier.) And if the serviceman knows his code at all, he will have no difficulty in copying WWV. The transmission is very slow—about ten words per minute—and the transmission is introduced by the following preamble: 'CQ CQ CQ de WWV WWV WWV National Bureau of Standards, standard frequency 15,000 kilocycles, accurate to better than a part in five million de WWV WWV WWV.' Of course the other frequencies are substituted in their respective transmissions. The accuracy of the tone modulation on Wednesdays is also better than one part in five million, which is better than two one hundred thousandths of one percent (.00002%)—which is fairly good!"


The Right Place for Service Notes

L. C. Warren, of the United Radio Service, Sioux Falls, South Dakota, sends through a good tip—"I have plenty of service notes which I am going to send along to the *Service Bench* as soon as I can copy them out of my Rider's Manuals. We write down the symptoms and the remedy right alongside the diagram and other dope. This saves a lot of time in duplication of tests when a like model comes in a few months later—impressive to the customer also."

Wattage Tests

Commenting upon the article appearing in this department for April, 1937, which described the use of a watt-hour meter as a radio test instrument, George Olsen, of Olsen's Radio Service, Carrington, N. D., writes: "We have used something of a similar nature on our bench for some years. We have one panel on which are mounted a Jewell 0-150 a.c. voltmeter and a Jewell 0-2 a.c. ammeter. The figuring of set wattages is simple—just volts times amperes. Of course a regular wattmeter would be somewhat quicker, but we prefer our layout which gives us a voltmeter, indicating the line voltage at all times. Have found this arrangement of

(Turn to page 38)

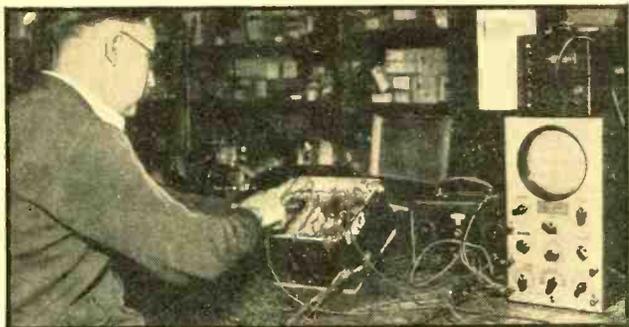

CHECKING SET WITH AN OSCILLOSCOPE
FIGURE 3

The layout for oscilloscopic servicing of home and auto radios.

Taking The "Guess" Out Of Auto-Radio SERVICING

(using an oscilloscope)

By Edward M. Scribner

THIS time of year is marked by the annual overhauling of auto radios preparatory to a summer of motoring reception. Many servicemen take full advantage of this seasonal opportunity through special literature and advertising calling attention to the desirability of a complete auto-radio check-over. The cathode-ray oscilloscope is an especially useful tool in auto radio servicing.

THE oscilloscope can, naturally, be employed for alignment, distortion checks, etc., in auto sets as well as in home-type receivers. But it is in vibrator action analysis that the oscilloscope performs a distinctive function, and only by its use can the serviceman effect adjustments equal in efficiency to those attained at the factory.

The possible variety of vibrator troubles is numerous; some of them so subtle in nature that they can be shown up only through oscilloscope investigation. Vibrators are often erratic in operation. Occasionally they blow out altogether—along with a few fuses. A light jar in removing the set from the car, or tapping, may return the vibrator to apparently normal operation. The points make and break so quickly that it is impossible to make an effective visual inspection, and the inertia of or-

inary meters often makes voltage readings unreliable. Points may burn over a very small area no larger than the head of a pin. They may operate normally during partial disintegration—so far as ordinary tests are concerned—only to cause grief later on. Some vibrators will not start at the agreed low potential rating of four volts, but will operate satisfactorily at from six to eight volts. Some points will burn out as the potential approaches 8 volts. Such conditions are due to vibrator maladjustments, the exact nature of which can be determined only on the oscilloscope.

Reveals Troubles

However, the vibrator is not alone guilty in the matter of power supply troubles in auto radio receivers. The buffer condensers across the secondary of the transformer often cause trouble, particularly when permanently or intermittently open. (A shorted buffer condenser is, of course, readily located.) Replacement of a buffer capacitor with a condenser of the wrong value will result in reduced life and incorrect operation that is best demonstrated on the oscilloscope.

The cathode-ray oscilloscope will de-

tect not only vibrator and contact trouble (with both synchronous and non-synchronous vibrators) and abnormal conditions in the buffer circuit, but will also disclose the presence of "hash" in the r.f. system.

Experimental Tests

To familiarize oneself with the oscilloscopic portrayal of vibrator circuit conditions, the serviceman should produce known troubles in an otherwise perfect vibrating system and note the effects on the oscilloscopic screen. These should be sketched or photographed for future reference. (Photos, or oscillographs, are easily made with an exposure of 1/5 to 1/2 second at f-4.5 on fast, color-sensitive film or plates. Figure 1 is such a photo. A slightly more contrasty image will be secured by dimming the room light, Figure 2 being an example of this technique. The oscilloscopic image can even be discerned in Figure 3, which shows the layout and the author at work on an auto radio. (This was made with a time exposure, followed with a flash-bulb shot of the ensemble.)

As the images vary with different conditions in different receivers, it is hardly practical (Continued on page 57)

FIGURE 4

This oscillogram shows a synchronous vibrator with the rectifying contacts out of adjustment with resulting voltage (vertical deflection) fluctuations.

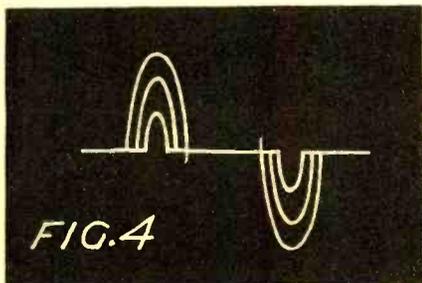


FIGURE 1

Oscillograph of a perfect vibrator on an Arvin 17A auto radio.

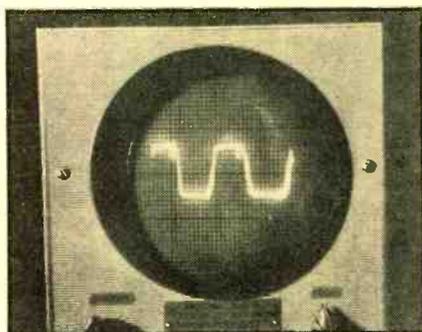


FIGURE 2

The same oscillograph as that shown in Figure 1, but made more contrasty by reducing the room light.




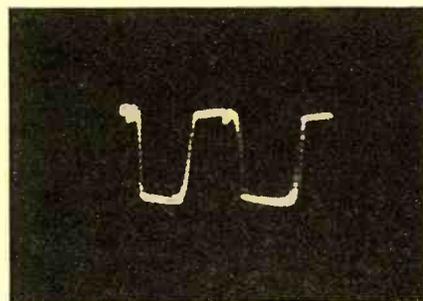


FIG. 5

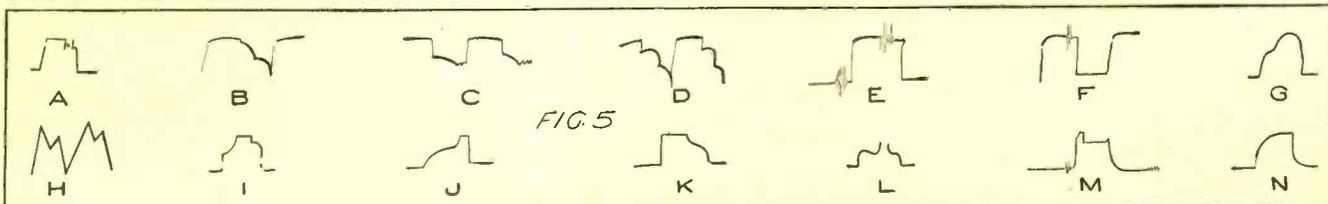

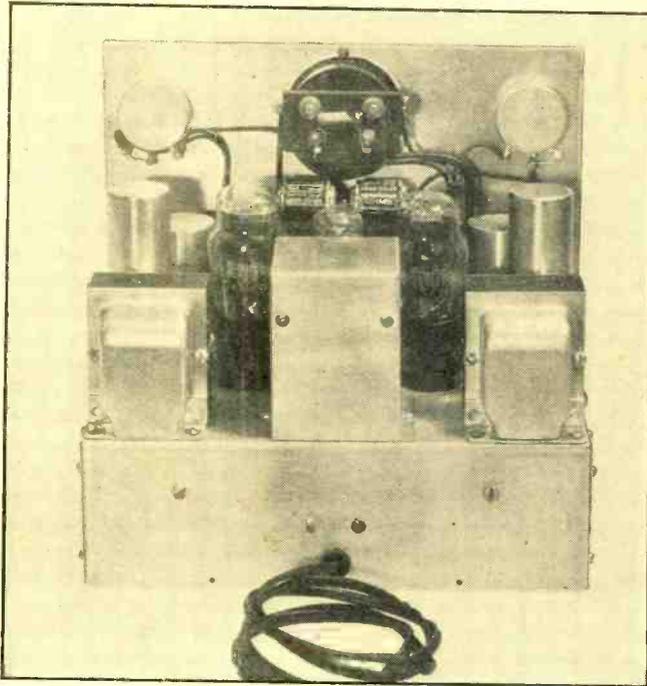

THE AUTHOR'S MODEL—

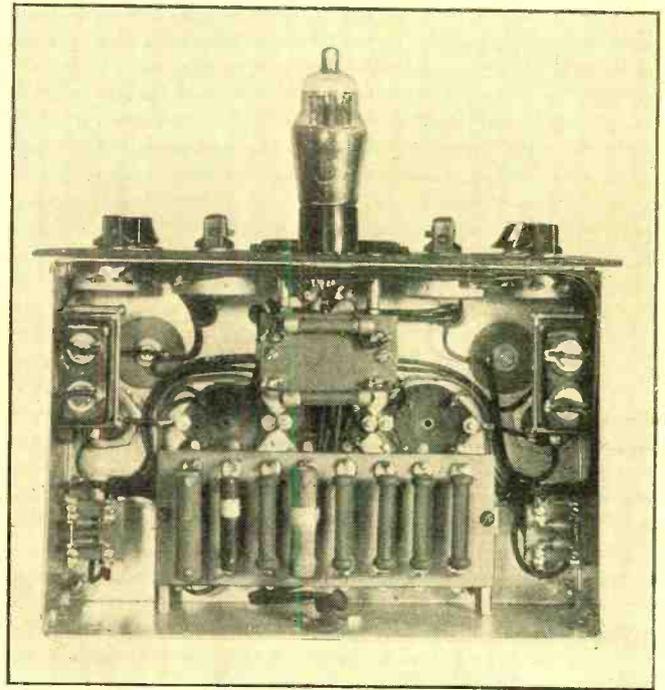

RUGGED AND COMPACT

How to Build and Use a V. T. VOLTMETER

By R. M. Ellis
(Part One)

THE vacuum-tube voltmeter to be described will provide the laboratory technician or advanced serviceman with a versatile instrument for the direct reading of many voltages which are not indicated, or at best only approximated with an ordinary meter. This voltmeter will accurately measure direct or alternating peak voltages up to 500 volts, with an a.c. frequency range from 20 cycles to 20 megacycles. With the original laboratory model, the actual measured error at 15 megacycles was only 2%. This device will save hours of time in locating trouble in receivers which apparently check satisfactorily but still do not perform properly. Mysterious cases of distortion, lack of sensitivity, and broad tuning unfold their secrets with ease.

Solves Mystery

As an example we cite the instance of a certain radio receiver which was a "hoodoo" for several competent servicemen. Although checking perfect in every way, this set distorted badly on local stations during periods of high modulation. A test with the v.t. voltmeter indicated that there was a fairly strong audio component on the grids of the r.f. and i.f. tubes. Since the by-pass condensers in the a.v.c. line were known to be perfect, the cause could only be that insufficient a.v.c. filtering had been incorporated in the original design. When the a.v.c. filtering was increased

by using larger condensers and higher value resistors, the distortion was entirely eliminated.


Here are a few of the measurements

that can be made with ease and accuracy:

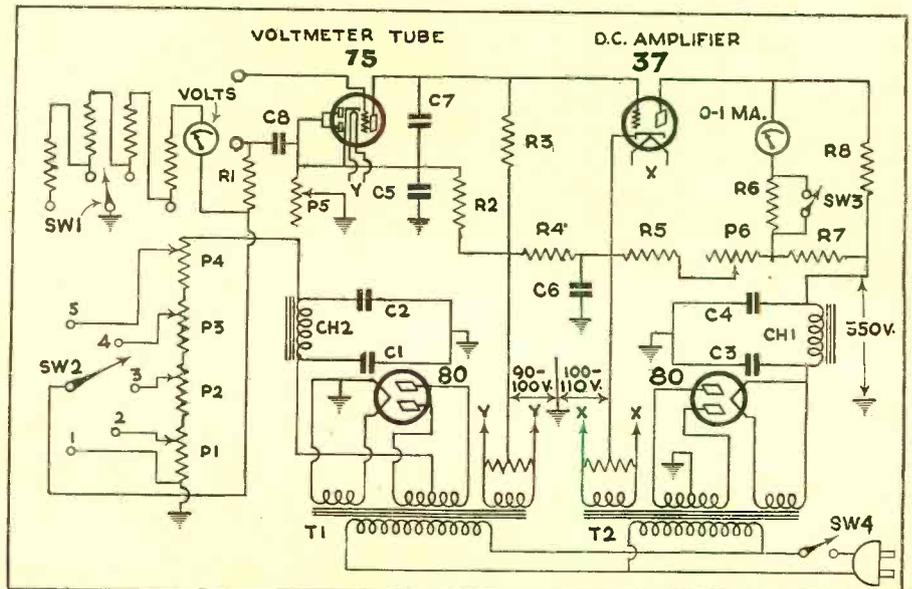1. Peak voltages—r.f., i.f. and a.f.
2. Diode detector peak voltage.
3. Automatic volume control voltage.
4. Audio, r.f. and i.f. gain.
5. Detector efficiency.
6. Amplifier power output.
7. Phase inverter output.
8. Superheterodyne oscillator voltage.

THE SCHEMATIC CIRCUIT

Two power supplies are used, one for the "slide-back" or balancing voltage; the other for the tube-operating voltages.



- 9. Transformer and choke impedance.
- 10. Capacities.
- 11. Peak voltage requirements for vibrator buffer condensers.

The fact that this vacuum-tube voltmeter reads peak voltages is an advantage, since the maximum input to a vacuum tube is governed by the maximum permissible grid excursion, rather than the r.m.s. value. If desired, the r.m.s. value of any sine wave may be determined by multiplying the peak voltage reading by .707.

D.C. Amplifier

The vacuum-tube voltmeter shown here is somewhat unusual in design. Fundamentally, this is a combination slide-back tube voltmeter, plus a d.c. amplifier to give added sensitivity. The reference meter reading slide-back (bias) voltage is permanently connected in the circuit so that when balance is obtained the value of the unknown voltage may be read directly on this meter, eliminating confusing and time-wasting calculations.

The plate circuit of the d.c. amplifier operates into a bridge to permit the plate current to be balanced back to zero or any convenient reading, and also to prevent meter overload.

The merit of any voltmeter is mainly dependent on two factors, accuracy of calibration, and internal resistance (ohms per volt). Assuming that the reference meter is correct, the accuracy of this voltmeter is practically perfect up to high frequencies, except for potentials of less than 2 volts where an error of approximately 5% may be encountered owing to the difficulty of obtaining exact balance in this extremely low range.


High Impedance

The internal resistance of the meter (ohms per volt) startlingly shows the special merit of the voltmeter. Since the type 75 tube is operated at practically "cut-off," and since no connection is made across the voltmeter input except through the voltage sources, the impedance is practically infinite to a d.c. source. The a.c. impedance is inversely proportional to the frequency and is dependent on the inter-electrode capacity of the type 75 tube. At very high frequencies, there is also some effect from the inductance and capacity of the tube leads.

Two power supplies are employed, one to furnish variable bias to the type 75 tube, the other to provide operating voltages for the 75 and 37 tubes. The drain on these power supplies is substantially only the power required to maintain the voltage across the bleeders; therefore, the smallest size midget power transformers will be adequate. It is possible to employ only a single power transformer, but this practice is not recommended because voltage regulation effects will cause considerable interaction between the controls which will affect the accuracy and ease of operation of the instrument.

Power Supply

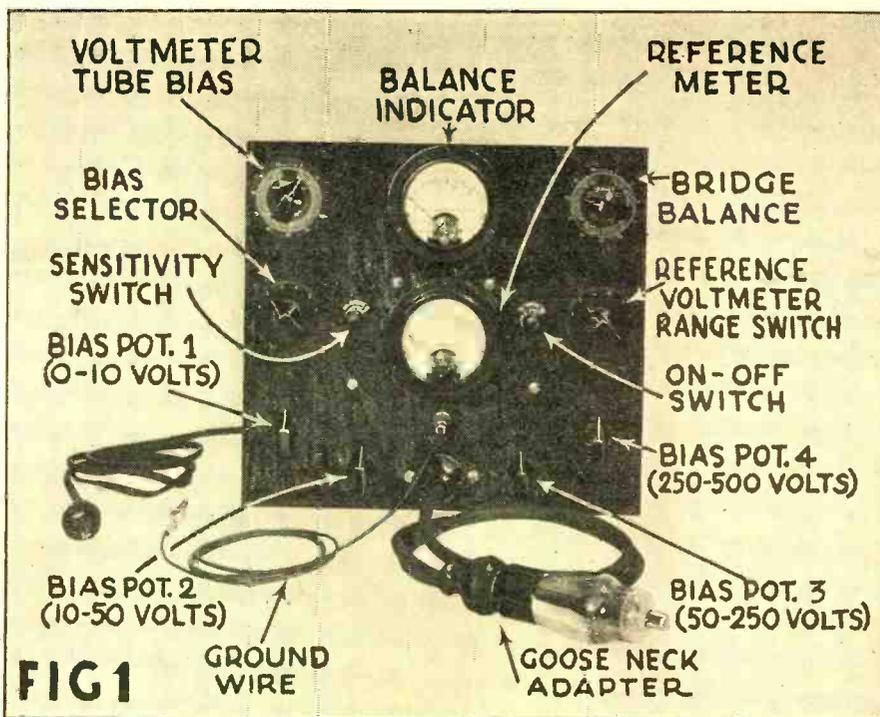The bias power supply should furnish about 500 volts negative bias. The plate power supply should deliver about 350



THE FRONT-PANEL VIEW


The type 75 tube may be plugged into the panel socket direct—or may be plugged into the extension cable as shown and its grid cap touched directly to circuit to be measured.

volts. If it is in excess of this, a small resistor may be inserted between the rectifier tube filament and the filter choke to drop the voltage to this value.

The heaters of the 75 and 37 tubes must be operated from separate fila-

ment windings because of the wide difference between the cathode voltages of the two tubes, as is the case in any direct-coupled amplifier.

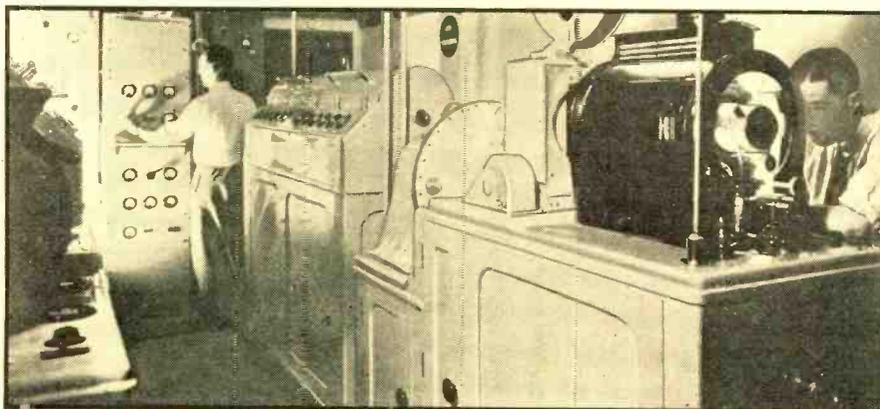The sensitivity switch (SW3) functions by inserting a 30,000-ohm current-limiting resistor in series with the 0-1 milliammeter used as the balance indicator. This protects the meter during the setting-up process, since otherwise the current might (Turn to page 58)



Television Operators Wanted

NOW is the time to prepare if you want to make television your life work. The author offers some suggestions which should help you.

By Thomas E. Gooteé

ALTHOUGH television has not been commercialized in this country as yet, it has developed into a highly specialized branch of the radio industry. There will be many future opportunities for trained television operators, technicians, and engineers who, by their own foresight,

have studied and trained along this specialized line. The television operator of tomorrow must be a trained, skilled worker with knowledge far exceeding that necessary for radio or electricity alone. This is not a technical discussion of television, but a practical analysis of what future television engineers and operators will be expected to know.

A thorough understanding of television is not complete unless the definite relation between the human eye and television is fully realized. Television, in part, is actually duplicating imperfectly the process of the eye. For this reason a study of (Turn to page 59)

Designing Resistance-Coupled AMPLIFIERS

(Amplifiers with Triodes)

By J. van Lienden

(Part Two)

RESISTANCE-COUPLED amplifiers employing triodes have a frequency characteristic which is determined by the capacitance values across the plate and grid resistances and the coupling condenser as well as the cathode by-pass condenser.

Referring to Figure 1, which shows a typical resistance-coupled stage, the condenser C is in series with R_g . The reactance X_c varies with frequency, being the largest at low frequencies with the result that the lower frequencies will be attenuated unless the condenser has a reactance which is small compared with R_g , even at the lowest frequency to be transmitted.

High Frequencies

The plate-cathode capacitance of the tube is across R_L and the effective grid-filament capacitance is across R_g . These two capacitances by-pass the higher frequencies, the amount of attenuation depending on the size of the resistors and the tube capacitances. For a fixed tube capacitance, the lower the resistance values, the better the high-frequency response. The effective grid-cathode capacity of a tube is not equal to the static capacity, measured when the tube is disconnected from the plate supply. The grid-plate capacity is reflected back and adds capacity across the grid leak. The total effective capacity becomes

$$C_{eff} = C_{gc} + C_{gp}(1 + A)$$

Where A is the gain in the tube, C_{gc} is the grid-cathode capacity and C_{gp} is the grid-plate capacity. It will be seen that this effective capacity may become large when high- μ tubes are used. Therefore, in resistance-coupled amplifiers containing several high- μ triodes, the high frequencies will be attenuated too much. Low- μ triodes will have to be used for a flat characteristic or otherwise the pentode will solve the problem.

Effect of Self-Bias

The bias resistor and by-pass condenser also influence the frequency characteristic. The combination of the two will have a voltage drop across them which is re-applied to the grid in reverse phase. Therefore, when the impedance of the combination rises, the reversed feedback increases and the output becomes less. The lower the reactance of the by-pass condenser, the better the low-frequency response.

The accompanying chart, which was prepared by RCA engineers, specifies the values of condensers and resistors which will result in a frequency charac-

teristic as in Figure 2. At the low-frequency end, the output at $f_1 = 100$ cycles is .8 of the output at 420 cycles, while the high-frequency cut-off point, f_2 , is generally very high unless several stages of high- μ tubes are used. If a different value of f_1 is desired, the capacity values of C and C_c given in the table should be multiplied by $100/f_1$. When n similar stages are used in cascade, the voltage output at f_1 will be n (.8) times the output at 420 cycles.

The Hum Problem

The values of the cathode by-pass condenser C_c are given for a d.c. filament supply. When a.c. is used to heat the filament, it may be found necessary to increase C_c to minimize hum distortion. The proper size then depends on the gain, the nature of the associated circuits and the value of f_1 . It may also be desirable to have a potential difference of 10 volts d.c. between heater and cathode.




When the amplifier contains more than two resistance-coupled stages, decoupling filters will be required. For two stages or less, these will not be necessary.

The employment of self-bias has the advantage that the circuit compensates automatically for variations in plate voltage or slight differences in tube characteristics. For this reason self-bias is more convenient than fixed bias.

A variation of 10 percent in the values of resistors or condensers will have only little effect on performance.

Phase Inverters

The data on double triodes refer to the use of the tube as an amplifier-phase inverter according to the diagram of Figure 3. The first section of the tube serves as an ordinary resistance-coupled amplifier while the second section is the phase inverter. The input to this section must be regulated by the tap P so that its output is equal to the output of the first section. The correct ratio of the two resistors making up R_g can

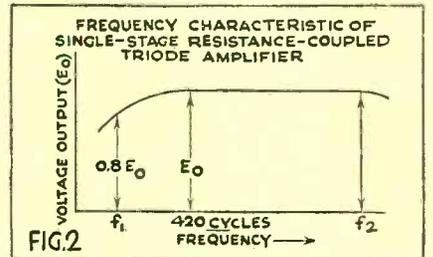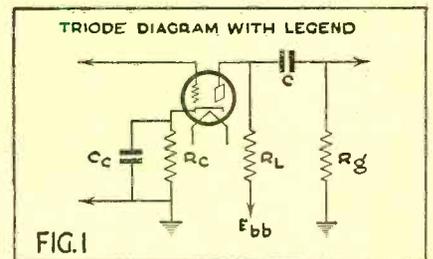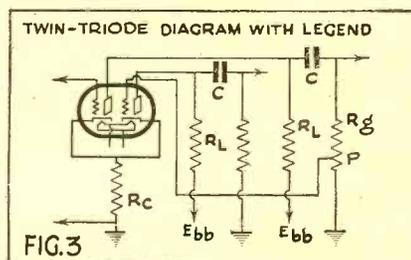

be found from the table. For instance, if the gain of a single section is 20, P should be located so that the resistance from P to ground is $1/20$ of R_g or $1/19$ of the resistance between P and condenser C . For phase-inverter service it is better not to by-pass the bias resistor R_c ; this helps to balance the two sections.

The 5T4

NEW YORK, N. Y.—The 5T4 is a new metal rectifier tube, similar in characteristics to the 5Z3. The maximum ratings with a condenser input filter are: maximum a.c. voltage per plate, 450 volts r.m.s.; maximum peak inverse voltage, 1250 volts; maximum output, 250 ma.

With a choke-input filter, the choke inductance being at least 10 henries, the maximum ratings are: maximum a.c. voltage per plate, 550 volts r.m.s.; maximum peak inverse voltage, 1550 volts.

Octal Base Tubes

New York, N. Y.—The new tubes, types 25A7G, 6Y7G, and 1G5G are announced by Raytheon. These are octal base tubes with glass envelopes. The 25A7G is a rectifier and a pentode for use in a.c.-d.c. receivers. The maximum output of the pentode section is 0.77 watt with 9 percent total harmonics when plate and screen supply is 100 volts. The maximum ratings of the rectifier are 125 volts r.m.s. and 75 ma. The 6Y7G is a twin triode, similar in characteristics to type 79. The 1G5G is a 2 volt power pentode, delivering a maximum of 300 milliwatts output with a 90 volt plate supply. The filament current is 120 ma.


Treated Papers, Fabrics and Tapes

Westinghouse has issued a catalog section listing treated papers, fabrics and tapes for use as insulating material. The publication includes the characteristics, applications and list prices for the various insulating materials. For treated papers are listed express, rope, kraft, fish and fullerboard. Under fabrics are cotton drill, heavy duck, asbestos cloth, combination fishpaper and fabric. Copies are available from Westinghouse district offices, or from Department 5-N at the main office in East Pittsburgh, Pa.

Low-Cost PRE-AMPLIFIER of Wide Utility

(for P. A. and "Ham" Work)

By M. N. Beitman

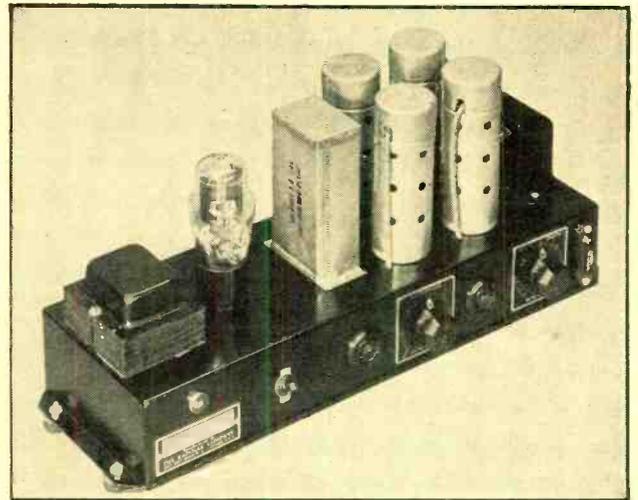

THE 3-CHANNEL PRE-AMPLIFIER

The 2 "Mic" sockets provide for 2 separate, low-level inputs such as crystal microphones; the twin tip jack is for high-level phono or radio input. The right-hand knob is a dual volume control and fader for the high-level and one low-level channels while the left-hand knob controls the volume of the other low-level input.

MANY P. A. amplifiers now in use have insufficient gain to give their rated power output from modern high-quality crystal and velocity microphones, though such amplifiers may give full output when carbon microphones are employed.

TO obtain satisfactory performance from P.A. amplifiers with modern, low-level microphones, a pre-amplifier must be used. The Radolek instrument shown in the illustration has features of considerable value in this application. This modern pre-amplifier is compact, light and completely a.c. operated. It has excellent performance characteristics over the audio range from 50 to 9000 cycles, and adequate gain with negligible hum. Individual input circuits for two microphones and a phonograph pickup provide for mixing or blending the input sources to any desired degree. Speeches or announcements may be superimposed on a background of music picked up from a phonograph record or any other source, just as is done in modern broadcasting studios.

3-Channel Circuit

The complete schematic circuit is shown in Figure 1. The two low-level microphone inputs connect to separate high-gain triode input stages each employing a type 75 high-mu tube. The diode sections are grounded since they are not used. The output of each 75 is individually coupled to a type 6D6, triode-connected. The phono-microphone volume control in the upper channel section is rather unique. A center-tapped 1-megohm control is employed, one half of which controls the "phono" input while the other half regulates the volume of the microphone channel. The extra arm is provided to short out the phono input when the microphone alone is employed. Mixing is accomplished by joining together the output sections of the 6D6 tubes.

Impedance Matching

The output transformer secondary is tapped to match either a 200 or 500 ohm line and a separate high impedance output is also taken from the primary side of the transformer. Thus the pre-amplifier may be either direct-connected or line-coupled to practically any type of amplifier on the market. All input and output connections are made with

polarized plugs and sockets which simplify installation and eliminate possibility of error. The pilot light is a minor but very useful refinement which contributes to its professional appearance as well as providing visual assurance of proper line power connection.

The pre-amplifier described above by Mr. Beitman was submitted to the RADIO NEWS laboratories for test. After it was found to perform satisfactorily for P. A. work, it was decided to investigate its adaptability to "ham" transmitter applications.


Tested at W2JCR

The instrument was accordingly taken to amateur station W2JCR and hooked up ahead of the speech amplifier of a transmitter, operating on 5 meters. This speech amplifier was designed for use with carbon microphones of average gain or better and did not provide sufficient amplification for low-level crystal mikes. With the pre-amplifier, however, the output was stepped up so that full modulation could be obtained, using a crystal mike, with plenty of reserve gain. There was no noticeable increase in hum

nor was any trouble from r.f. pickup encountered.

Several stunts were tried with complete success. The crystal mike was connected to one input circuit while 20-meter "ham" signals were picked up on a communications receiver and fed into the other pre-amplifier channel. Mixing could be accomplished to any desired degree. In the same way, a phonograph pick-up connected into one channel was employed in making modulation tests of short duration, with comments by voice indicating the level, etc., for the benefit of the other station operating in the tests. Also, an audio oscillator and key were tried in one of the pre-amplifier channels. This was employed for CQ'ing, breaking in with voice in the other channel from time to time.

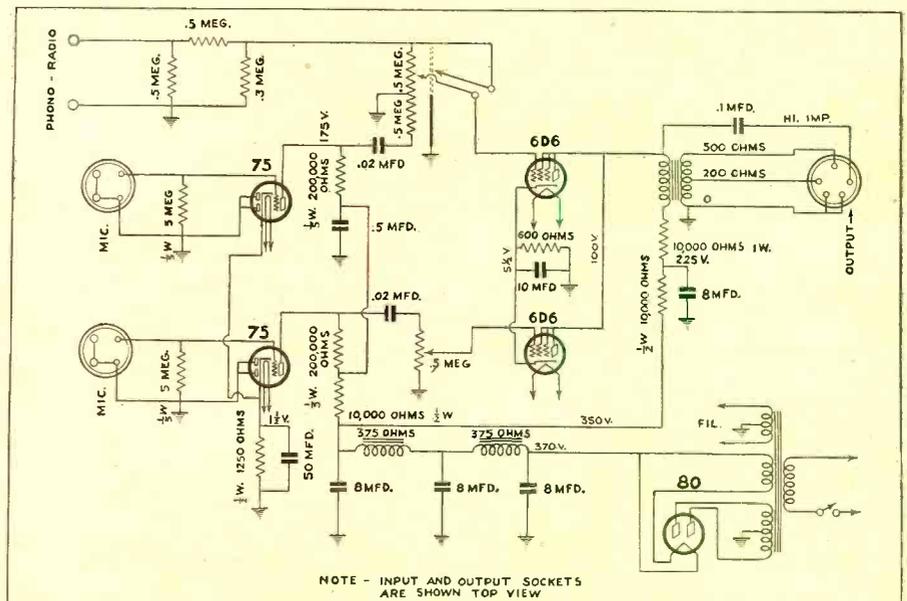Properly used, many unique and striking effects can be secured in P. A. application, in addition to the manifest value of greater amplification.





The "HAM" Shack

Conducted by
Everett M. Walker
 Editor for Amateur Activities

W9VXZ

Amateur station of the National Institute of Technology Radio Club at Minneapolis, Minn.

mast has supported this antenna for three years and shows no signs of strain.

A similar roof support may be constructed of wood. An ordinary piece of 2 by 2 inch stock is used. A mast step similar to the support of a mainmast of a small sailboat forms the base support. A piece of 2 by 6 inch stock one foot long will serve this purpose. A square hole is chiseled out so the 2 by 2 inch mast fits snugly. When such a mast is mounted on the roof peak the step should be made to straddle the peak. If the mast itself is more than 5 feet high, two sets of guy wires will be needed. It is more convenient to use four sets of guy wires on such a mast, although three will provide sufficient strength. As a matter of fact only two guys are necessary at the top of the mast, the pull of the antenna serving as the front guy.

The Problem of Antenna MASTS

PROPERLY supporting a transmitting antenna is a problem that frequently confronts the amateur. Now all of us are not fortunate in having tall trees available. Yet, a good antenna is important to the successful operation of a station, and it cannot be had without an adequate support.

USUALLY the Amateur's house may be used for one support for his antenna, but it is the far end that presents the problem. Here it often is necessary to erect some kind of mast. The writer recently made a survey of types of supports most commonly used. Out of a large number of stations questioned, it was found a majority are fortunate in having trees or good-natured neighbors who have consented to the use of their houses for the far end support of the sky-wire.

Worth While Ideas

But those who use masts have devised many construction ideas that are worth passing on. They range from flagpoles to elaborate lattice construction affairs. Some are inexpensive to build and others costly. By-and-large, the majority use wooden masts of some kind. Those who use steel usually have them put up by construction companies, although there are many home-made pipe masts in use. A few will be discussed here.

The average height of the amateur masts we have investigated is about fifty

feet, although this varies somewhat, depending on the frequency most used. Operators using 20 meters consistently use poles about 30 feet high. On the 40-meter band the average height is between 40 and 50 feet, and on 80 meters it runs closer to 60 feet, although there are many fine signals being radiated on this band from antennas about 40 feet high. One-hundred-foot masts are rare.

Building a support for the house end of the transmitting antenna does not present a big problem. Usually only a small pole is required and consequently few guy wires are needed. The house mast, itself, should be high enough to match the height of the mast or tree support used. This is because it is desirable to have a half-wave antenna horizontal, although a slight tilt will not materially influence the radiation pattern. Most single-family dwellings are between 30 and 35 feet high. Therefore, the average rooftop mast is about 10 feet.

Antenna Poles Available

There are a number of small antenna poles available that may be used for supporting transmitting aerials. One in particular is a telescope affair made of metal tubing that may be varied in height from 4 to 12 feet. It is equipped with guy wires and a mounting bracket that may be fastened to the roof. While small in diameter, it has sufficient strength and guy wires to support a fairly heavy, half-wave antenna. One station is using this type of roof support for a half wavelength 75 meter antenna fed by a twisted-pair line, which, if course, is quite heavy. The

Using Chimneys




Many amateurs use a chimney to support a small pole. This is all right if the chimney is strong. It is not advisable to use this idea if it is an old one, as cement has a way of weakening with age, and the leverage of a pole pulled by an aerial might cause some damage.

A device used by one amateur for such a "stick" is made of a 16-foot, 2 by 3 inch timber. Brackets of wood are mounted 4 feet apart and are equipped with eyebolts separated a distance equal to the width of the chimney. A heavy cable is attached to these and run around the chimney. A turnbuckle in each facilitates drawing the pole tight up to the chimney. No guy wires were used on the one the writer saw and it was effectively supporting a 75-meter antenna. Its owner said it had been up four years.

So much for rooftop antenna supports. An excellent design for a medium-height antenna pole recently was brought to the attention of the writer. It is 48 feet high and is constructed of timbers available in practically all lumber yards. It is strong and at the same time does not require much space for guying. Also, it is not difficult to erect.

Mast Construction

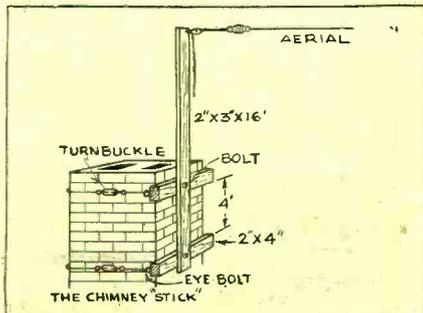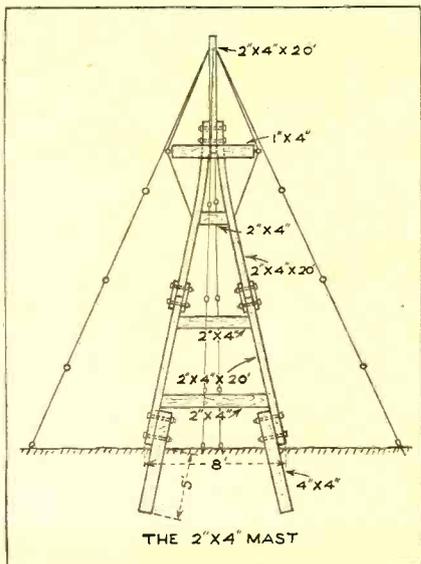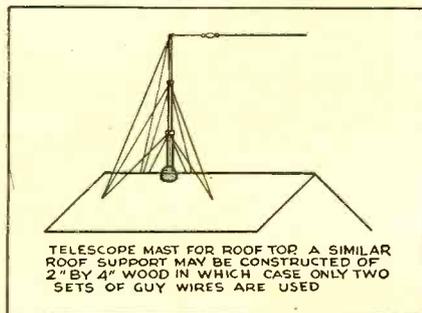The base section of this mast consists of a 30-foot section of 4 by 4 inch timber. Atop of this is mounted two 18-foot lengths of 1 by 4 inch stick. The top section is bolted together at the top and spread out so that it fits over the top of



A Department for the amateur operator to help him keep up-to-date

the 4 by 4 inch section, overlapping it 2 feet, thus forming a narrow "V." At 3-foot intervals in this crotch pieces of 2 by 4 inch cut to fit snugly, are nailed securely. This forms a light but strong top section.

A sling similar to those used for flagpoles is used at the base. This consists of a 7-foot piece of 4 by 4 inch stock and two 11-foot sections of 3 by 4 inch stock clamped securely on each side of the 4 by 4 inch section. The base section is painted with asphalt paint and it is set 5 feet deep in the ground. While, in the particular mast described here, concrete was not used to fix it in the ground, it is suggested as good practice.

Proper Guying



Guying of such a mast is important. Two sets of guy wires are used: one being entirely fixed to the mast and the other attached to buried anchors. The guys fixed to the mast are brought down over cross arms stretching out 4 feet in each direction at the middle of the mast. These are made of 8-foot lengths of 1 by 4 inch stock clamped on each side of the 4 by 4 inch section at the midpoint.

These, like the top section, are bolted together at the ends. The guys are attached to eye-bolts 3 feet down from the top and brought down over the ends of these "yard-arms" and attached to eye-bolts about 8 feet off the ground. Turnbuckles are inserted in each near the bottom of the guywire, facilitating tightening. This method of guying makes the whole unit rigid.

The second set of guy wires are attached to the top of the 4 by 4 inch section and brought down to the ground anchors. The anchors used were 3-foot eye-bolts with old rail plates attached to provide greater ground pull. Each of these anchors was set in concrete, and mounted 5 feet from the base of the mast. No. 10 heavy galvanized wire was used for all the guy wires. It is not advisable to use stranded wire for mast guying, as once this starts rusting, it loses its strength.


A 58-ft. Mast

Another mast encountered was somewhat similar to this but uses 2 by 4 inch timbers exclusively. It is 58 feet high. Five pieces of 20-foot 2 by 4 inch stock are required. Two pairs of these 2 by 4's are mounted end-to-end with a clamp made of 5-foot lengths of 1 by 4 inch stock. The 2 by 4's are mounted end-to-end and 1 by 4's are bolted on each side, thus making two continuous 40-foot sections. The fifth 2 by 4 inch piece is inserted between the top end of these two sections with an overlap 3 feet long. Here again it is securely bolted. Then the two 40-foot sections are spread out to

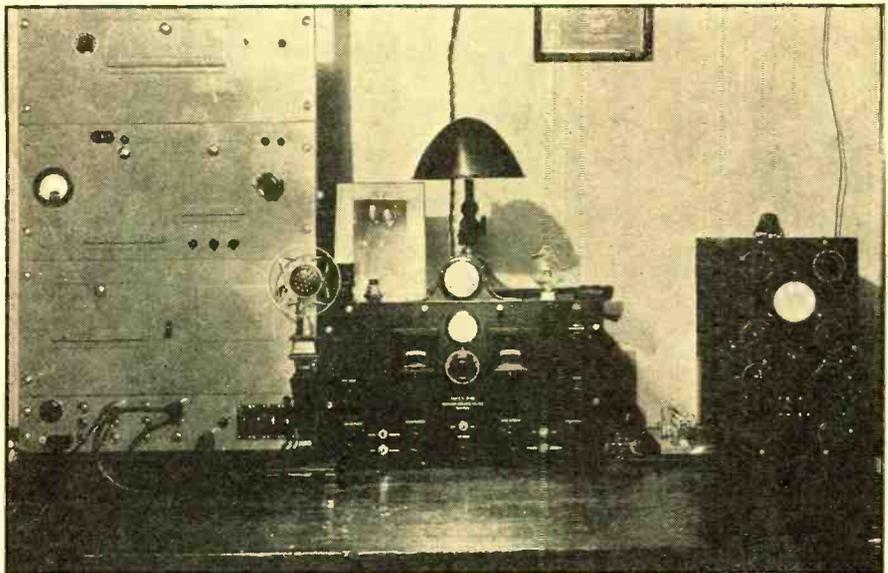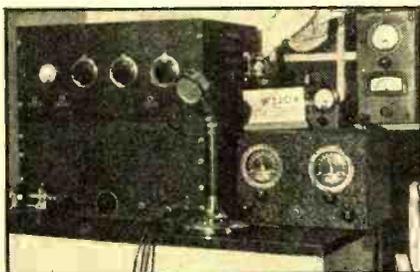

LOOKING IN AT W2BFB

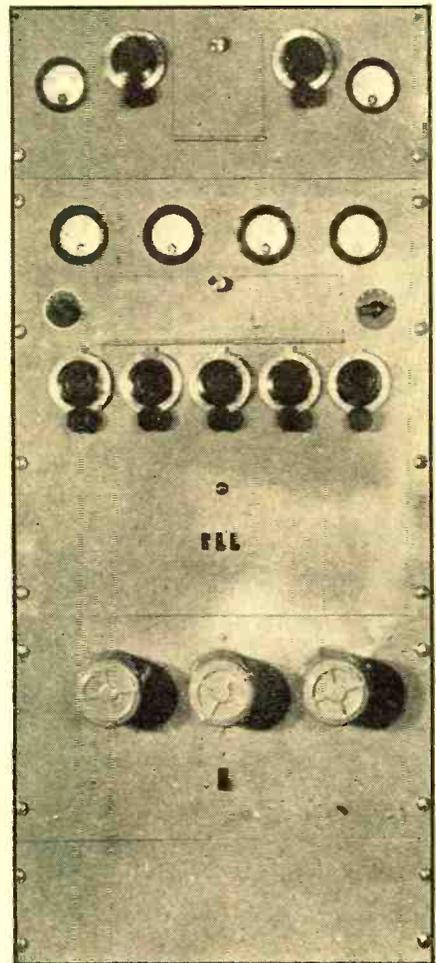Above: The operating table of W2BFB, Bronxville, N. Y., showing, center: The receiver; at right: The oscilloscope; at left: The speech amplifier. In the right-hand photograph is seen the power, rectifier and final amplifier stages. The latter two racks are finished in a dull green enamel, giving the station a unique appearance.



about 8 feet at the base, and cross-section pieces are mounted between the two sides in a manner similar to the top section of the mast previously described.

In view of the fact the top section is only 2 inches across, it is necessary to use the yard-arm method of guying this section to give sufficient strength. Two sets of guy wires were used, although an additional set would provide added security. The base is fastened with bolts to two 4 by 4's, each sunk 5 feet in the ground.

Bolted Sections

Another mast used at a second district station consists of three sections of 4 by 5 inch timber, each 28 feet long. The base of this mast is bolted to a section of a discarded telephone pole. A novel method of guying is used for this mast. The guying requirement is to have the space to permit running the wires at 45 degrees in relation to the ground. Only one guy wire goes all the way to the top—the back one. The two others attach just above the midpoint of the mast, and each is anchored at a point 120 degrees apart. The antenna wire provides additional support in the front and the whole affair is quite rigid.

Amateurs who have a garage in the yard that is conveniently located frequently erect a mast atop of it. Several such arrangements were suggested. One uses a 30-foot section of 4 by 4 inch timber mounted on a step at the middle of the garage. Four guy wires are used. They are attached to the corners of the garage. In this case the peak of the garage is 18 feet high, thus the antenna support is 48 feet above ground.


5-METER STATION

This is a set-up at W2JQX of New Rochelle, N. Y. At left is a 65-watt, 5-meter, crystal-control rig. At right: The 6-tube acorn superhet. In the upper right corner is a rig-checker and monitor. Ken Stevens, owner of the station, has recently moved to Pelham and has installed a 400-watt final on 5 and 10 meters.

Higher masts may be erected atop garages, providing ample space is available for guy wires. Several amateurs are using arrangements somewhat similar to the 2 by 4 inch mast that spreads out at the base previously described. However, there is one problem in erecting a garage-top mast—that is, the mast has to be lifted vertically into place. Therefore, it is advisable to keep down the weight of this type of support.

A number of other mast designs were suggested by amateurs questioned, but these types represent the average amateur's antenna mast. For instance, several said they were using tower types of construction. Masts of this type may be somewhat

(Turn to page 41)

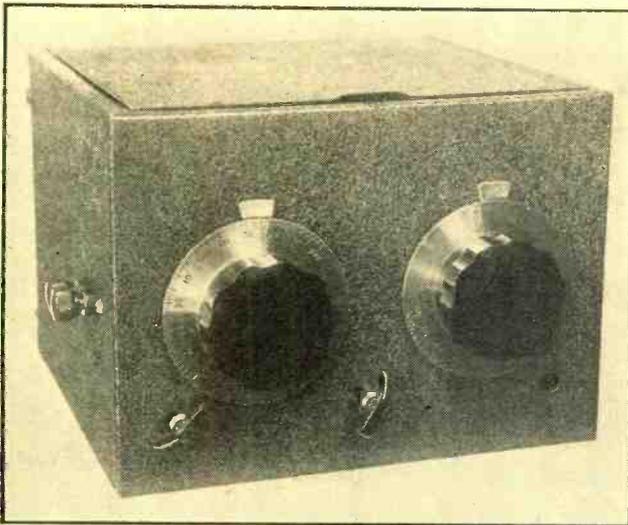

NEAT AND COMPACT


Two-dial tuning is employed, the left-hand dial tunes the r.f. stage; the right-hand dial, the ganged mixer and oscillator. The lower left-hand pointer tunes the antenna.

TO Major Armstrong the amateur fraternity owes a debt of gratitude for simple, inexpensive and extremely effective receivers employing the super-regenerative principle, which have allowed a great many amateurs with limited finances to explore the relatively unknown ultra-high frequencies. The exploration is now practically completed, however, so far as ranges up to 60 megacycles are concerned, and amateurs are studying various ways and means of getting the most out of their 56-60 megacycle band.

IF we are to profit by experience, we should make up our minds at the start not to waste the natural resources of the new and fruitful territory from 56-60 megacycles. The 5-meter band represents a band over four times as wide as the present standard broadcast band. A speech channel of excellent intelligibility should require no more than seven kilocycles—and this 56-60 m.c. band provides 571 such channels. With modulated oscillators and super-regenerative receivers this figure may be divided roughly by 100. The answer is obvious. If we want to realize the full

BELOW DECK

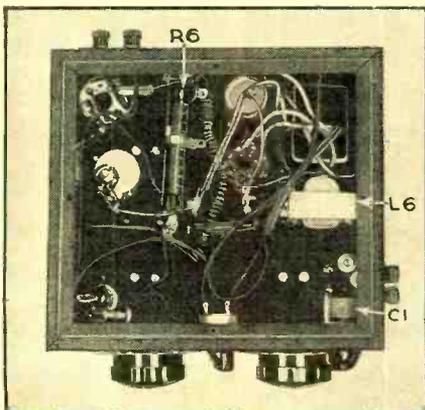Here the cabinet bottom has been removed to show the location of parts and wiring below the shelf.



"Acorn" Tubes Used 5-METER

The author presents constructional some pertinent observations on

By Nathaniel

benefits of the 5-meter band, stable transmitters and selective receivers are in order.

Already the amateur fraternity is better equipped. Crystal control and M.O.P.A. rigs are coming on the air daily, displacing out-moded oscillators. The cost of a good M.O.P.A. is only slightly higher than a straight oscillator, and watt for watt and dollar for dollar, it is capable of a better job. Remember, a stable 10-watt carrier will put through a better signal on a selective receiver than a 1,000-watt "wobulated" carrier. In order to understand a "wobulated" signal, an operator is forced to penalize his receiver and broaden it out, thereby increasing noise, QRM and all the evils of radio reception. Many excellent articles have appeared of late on stabilized transmitters and the amateur will have no trouble in choosing an arrangement which best suits his requirements.

Tuned I.F. Amplifier

Improving 5-meter reception is really a tougher job than stabilizing transmitters. The first step from the super-regenerative circuit has been the widely popular resistance-coupled i.f. superhets. These receivers do an excellent job and are in general quieter and more selective than the super-regenerative set but they are definitely what we might term a temporary expedient because their selectivity is limited, their "image rejection" is nil and their i.f. is so close to the audio spectrum that a.f. noise in the first detector often rides through.


The next logical step is a tuned i.f. superheterodyne. All the disadvantages of the resistance-coupled i.f. superheterodyne can be removed by the use of this type.

Converter Application

Now a superheterodyne should be broken into its two major sections when considering the design of such a set; namely, the r.f. and converter section, and the i.f. and audio section. Many amateurs have available, however, a regular communication type receiver, a broadcast receiver, or can obtain a second hand one which will fill the bill as the second section. Work by the author to date has therefore been confined to building the first or r.f. and converter section and studying its application to various standard receivers used as the i.f. and a.f. sections.

Important Requirements

The result of this work is the four-tube (including rectifier) converter which will be described, and which was designed with the following requirements in mind:
Power Supply—110-120 volts, 60 cycles.
Frequency Coverage—61-54 megacycles (for maximum electrical band spread and ease of tuning).
Useful Sensitivity—Maximum signal to "hiss" ratio with available tubes.
Input Circuit—Adjustable coupling for maximum signal input at all frequencies.
Output Circuit—Primarily designed to couple through twisted pair to low impedance input circuits on communication receivers which are pre-

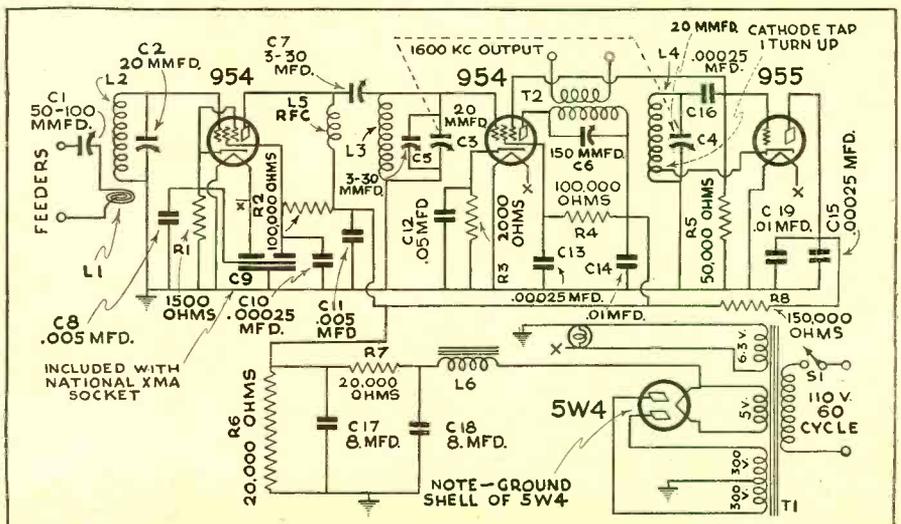

in Home-Built

Converter

details on his 5-meter converter and receiver requirements for this band.

Bishop (W1EYM)

tuned to 1,600 kilocycles.

Controls—Antenna coupling, r.f. tuning, detector and oscillator (ganged), on-off switch with indicator lamp.

Stability—Best possible.

Uses "Acorn" Tubes

From the start, with the above conditions in mind, it was decided to use acorn tubes throughout. There is no reason to believe that standard tubes cannot be built into an acceptable converter, but if one is interested in maximum results, the acorn tube is a foregone conclusion.

The circuit used in this converter is conventional, but at the same time every precaution was taken to assure maximum r.f. and conversion gain. Starting from the feeders, the antenna coupling coil is a "pie" wound affair which is made of solid hook-up wire with fabric insulation. This type of primary seems to give the maximum ratio of inductive to capacitive coupling to the grid coil. This fact helps in the reduction of noise voltages picked up by the feeders. The condenser C1 is provided to allow variable coupling without moving the pickup coil; and it is set at maximum capacity except where the antenna stage will not peak. The r.f. input circuit is not ganged to the oscillator and detector for the reason that with the antenna coupling which will give the best signal transfer, it is impossible to make the antenna circuit track, without using a special condenser in the r.f. circuit.

Effective by-passing of the r.f. stage is simplified by the use of the National type XMA socket for the 954. Each terminal except the plate and control grid is equipped in effect with a small, built-in mica capacitor direct to r.f. ground. C9 on the schematic indicates these capacitors. C8 and C10 are necessary additions for complete stability probably due to the use of the 2.5 milhenry choke in the plate circuit.

Coupling Methods

The type of coupling used from the r.f. plate to the first detector grid was chosen for the sake of simplicity of construction and the results obtained indicate that it works effectively.

The oscillator is coupled to the first detector by connecting the suppressor grid of the 954 directly to the control grid of the oscillator. In effect this amounts to suppressor grid modulating so widely used in phone transmitters.

Suppressor grid bias is obtained from the drop across the oscillator grid leak.


The trimmer is used on the detector input circuit. This works out to best advantage as it simplifies the alignment procedure and simplifies the design as the detector is peaked on the low frequency side of the oscillator.

A good size condenser to start out with for the three main tuning capacitors is 25 micro-microfarads. Plates may be removed for the desired band spread after the unit is completed.

The output transformer consists of a conventional 465 kc. i.f. transformer. One tuned circuit is removed and a ten-turn pickup coil is wound in its place about 1/2 inch from the remaining section. Turns are then removed from the remaining coil until it will tune to 1,600 kc.

The Power Supply

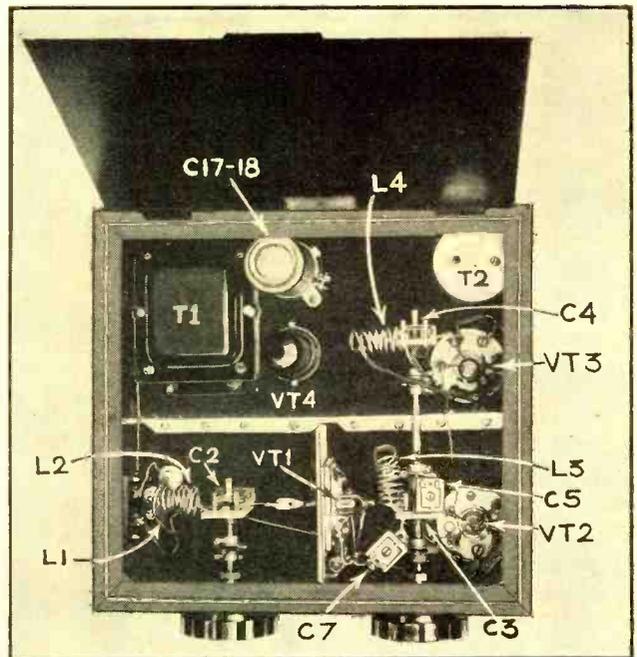The power supply unit is conventional. The filter circuit shown was used in the case of the original unit as the transformer voltage was too high. R7 then served the double purpose of drop-



THE CHASSIS LAYOUT

The r.f. and mixer stages are each shielded from each other and from the oscillator by partitions. On one of these the r.f. tube (Vt-1) and socket are mounted.


ping the d.c. plate voltage to 250 and acting as a filter section. A conventional "pi" filter may be used if the terminal voltage is not greater than 250 under load. Filter design will depend on the transformer used.

The mechanical layout of the converter is evident from the illustrations. Considerable leeway is permissible in actual layout if r.f. leads and by-passing connections are short. Partition shielding as illustrated seems ample for complete stability. A National SW-3 cabinet and shelf were used for the housing of the original unit. Any (Turn to page 56)

Antennas are Important

WILBERT T. GOLSON, Official RADIO NEWS Broadcast-Band Listening Post Observer for Louisiana, located at Baton Rouge, has installed an antenna for DX reception as illustrated herewith. The information on this system is herewith passed along to other DX'ers who may have plenty of space in which to erect their "sky-wires."

As shown in the illustration, the system consists of four separate antennas, each 100 feet long, supported from a center pole 50 feet high. The far ends may be supported from buildings, trees or additional poles. The four wires extend to the four points of the compass. Separate down leads are brought off the inside end of each wire and these leads terminate at a four-pole switch the arm of which is con-

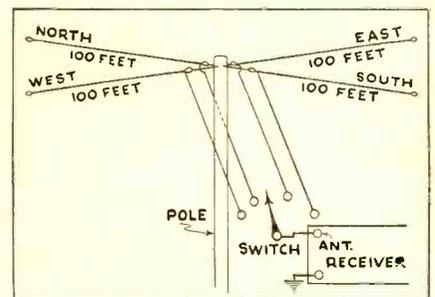


nected to the antenna post of the receiver.

When any station is tuned in, the switch is rotated to connect the antenna that provides the best signal from this particular station, thus taking advantage of the best directional effect.

It may be that in some instances greater signal strength may be obtained by using a combination of two of the four wires. In fact, this system lends itself to various experiments in an effort to obtain maximum signal strength from any given station.

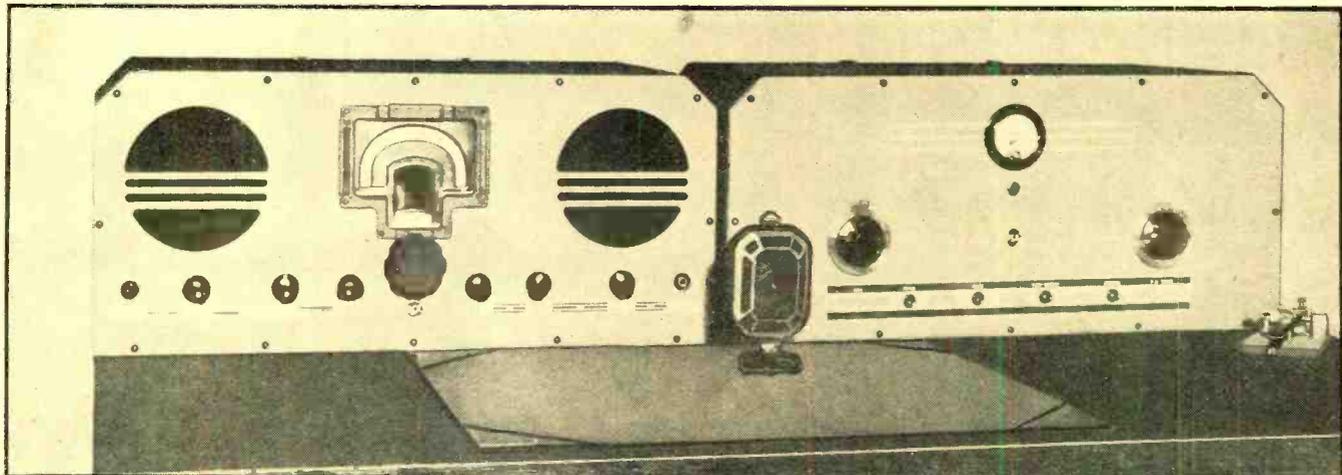Observer Golson has found this system highly effective and has adopted it for permanent use in his DX activities.



THE TEST SET-UP AT W2MW

The new RCA companion units, the ACR-155 receiver at the left, and the ACT-20 transmitter at the right, as they were used at the author's "ham" station, W2MW, during the tests described in this article.

Testing a Multi-Band "Ham" Transmitter

(The RCA Model ACT-20)

By Everett M. Walker

READY-BUILT transmitters are becoming more popular with amateurs. A few years ago there were practically none available to the amateur who wanted to buy his equipment, but the last few years have witnessed the inception of many ready-built units.

It cannot be denied that a factory built job from an appearance standpoint can be made much neater than most amateurs can turn out due in most cases to the lack of the necessary tools for handling the modern type of construction of rack and panel, metal cabinets and metal chassis.

One thing an amateur gets when he buys a transmitter is the assurance that the design is right—that each tube will receive its proper voltages and each piece of apparatus will have been either designed or selected to go with the circuit and tubes employed. Further, if it is a c.w. transmitter, it will be designed to give a good d.c. signal; if it is a 'phone transmitter, a good quality voice signal.

One of the most recent transmitters offered the amateur is the ACT-20 made by the RCA Manufacturing Company, Inc., of Camden, N. J. This is a low powered 'phone c.w. transmitter that incorporates many interesting features. It is capable of operating on any of the amateur bands from 1,715

to 30,000 kilocycles and will deliver 20 watts on c.w. and 16 watts on 'phone (normal) to the antenna.

One of its interesting features is that it employs the latest types of tubes in both the radio-frequency and audio circuits. It, of course, is crystal controlled, and uses an RCA-807 oscillator, an 802

buffer or doubler and another 807 in the radio-frequency amplifier. The 807 is the new beam power tube designed for transmitting circuits and when used in a properly designed circuit is capable of high outputs with small amounts of excitation.



Plate-Screen Modulation

The audio circuit consists of a high gain speech amplifier using a 6F5 and 6F6 which in turn drives a pair of 6L6s in a push-pull modulator stage that is transformer coupled to the r.f. amplifier and modulates both the plate and screen.

Mounted in a two-tone gray wrinkle cabinet, the transmitter is extremely compact. It is 24³/₄ inches long, 11¹/₂ inches high and 12¹/₂ inches deep. All necessary controls are on the front panel. These include a gain control for the speech amplifier, a tuning control for the tank circuit of the r.f. amplifier, a power switch, plate switch, an O-150 milli-ampere ammeter and switch for measuring either the plate current of the buffer-doubler or the r.f. amplifier and a "Phone-C.W." switch.

The transmitter is designed to operate either from 110 or 120 volt a.c. mains, provision being made for adjustment for either voltage. Provision is made for using a double button

(Turn to page 50)

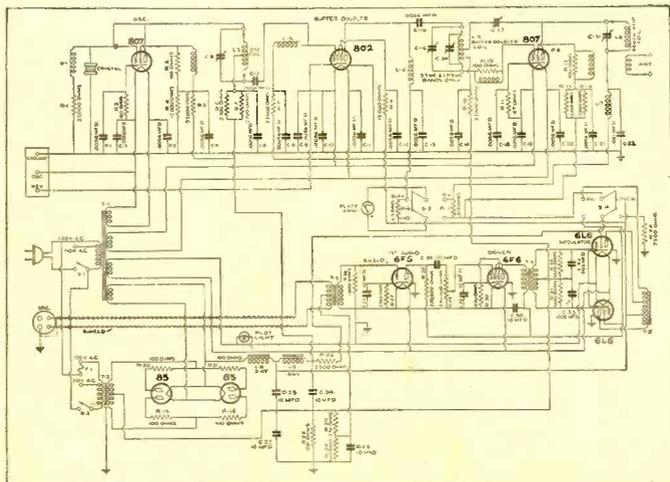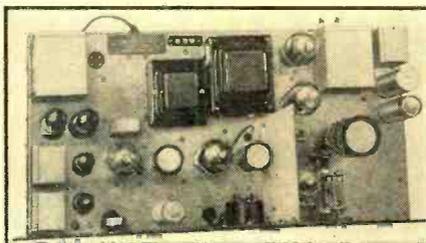

SHORT-WAVE STATION LIST

Arranged by Countries and Cities

NORTH AMERICA

Canada				
Location	Call	Kc.	Meters	Class
Calgary, Alberta	VE9CA	6030	49.75	B
Rossland, B. C.	CFUJ	5705	52.59	P, B
Vancouver, B. C.	VE9BK	4795	62.56	B
Vancouver, B. C.	VE9CS	6070	49.43	B
Winnipeg, Manitoba	CJRO	6150	48.70	B
Winnipeg, Manitoba	CJRX	11730	25.57	B
Winnipeg, Manitoba	VE9CL	6150	48.78	B
Halifax, N. S.	VE9HX	6110	49.10	B
Drummondville, Quebec	CGA3	13285	22.58	P
Drummondville, Quebec	CFA2	4465	67.19	B
Montreal, Quebec	CFGX	6005	49.96	B
Montreal, Quebec	VE9DN	6005	49.96	B
Toronto, Ontario	CFRX	6070	49.42	B
Toronto, Ontario	CRCX	11810	25.40	B
Toronto, Ontario	CRCN	6090	49.26	B

Mexico				
Location	Call	Kc.	Meters	Class
Guadalajara, Jalisco	XECU	6115	49.06	B
Guadalajara, Jalisco	XEDO	9480	31.65	B
Hermosillo, Sonora	XEBR	11830	25.36	B
Mazatlan, Sinaloa	XERM	15420	19.45	B
Mazatlan, Sinaloa	XEBQ	6030	49.75	B
Merida, Yucatan	XEME	9520	31.51	B
Mexico, D. F.	XEBT	6003	49.97	B
Mexico, D. F.	XECR	7380	40.65	B
Mexico, D. F.	XEPW	6120	49.02	B
Mexico, D. F.	XETV	6045	49.62	B
Mexico, D. F.	XEUZ	6117	49.04	B
Mexico, D. F.	XEWI	11900	25.21	B
Mexico, D. F.	XEWI	6015	49.88	B
Mexico, D. F.	XEXA	11880	25.25	B
Mexico, D. F.	XEXA	6133	48.91	B
Mexico, D. F.	XEXF	6050	49.59	B
Mexico, D. F.	XEXR	11895	25.22	B
Mexico, D. F.	XEXR	6065	49.46	B
Mexico, D. F.	XEXS	6200	48.39	B
Veracruz, Ver.	XEFT	9493	31.60	B
Veracruz, Ver.	XEFT	6120	49.02	B
Veracruz, Ver.	XEUW	6020	49.83	B

United States				
Location	Call	Kc.	Meters	Class
Bolinas, Calif.	KEC	5105	58.76	P
Bolinas, Calif.	KEF	6710	44.71	P
Bolinas, Calif.	KEI	9490	31.61	P
Bolinas, Calif.	KEL	6860	43.73	P
Bolinas, Calif.	KEM	15490	19.37	P
Bolinas, Calif.	KES	10410	28.82	P
Bolinas, Calif.	KET	9480	31.65	P
Bolinas, Calif.	KIKB	5110	58.71	P
Bolinas, Calif.	KKL	15475	19.39	P
Bolinas, Calif.	KKQ	11950	25.11	P
Bolinas, Calif.	KKZ	13690	21.91	P
Bolinas, Calif.	KMM	20780	14.44	P
Bolinas, Calif.	KOJ	18020	16.65	P
Bolinas, Calif.	KOR	18040	16.63	P
Bolinas, Calif.	KOZ	17980	16.69	P
Bolinas, Calif.	KSS	20820	14.41	P
Dixon, Calif.	KEZ	10400	28.85	P
Dixon, Calif.	KWN	21060	14.25	P
Dixon, Calif.	KWO	15420	19.45	P
Dixon, Calif.	KWU	15355	19.54	P
Dixon, Calif.	KWV	10840	27.68	P
San Francisco, Calif.	NPG	12885	23.28	T
Storrs, Conn.	W1XEG	400.000	0.75	E
Hialeah, Fla.	WND	4097	73.23	P
Miami Beach, Fla.	W4XB	6040	49.67	B
Chicago, Ill.	W9XAA	17780	16.87	E
Chicago, Ill.	W9XAA	11830	25.36	B
Chicago, Ill.	W9XAA	6080	49.34	B
Chicago, Ill.	W9XF	11880	25.25	B
Chicago, Ill.	W9XF	6100	49.18	B
Beltsville, Md.	WWV	15000	20.00	F
Beltsville, Md.	WWV	10000	30.00	F
Beltsville, Md.	WWV	5000	60.00	F
Boston, Mass.	W1XAL	21460	13.98	B
Boston, Mass.	W1XAL	15250	19.67	B
Boston, Mass.	W1XAL	11790	25.45	B
Boston, Mass.	W1XAL	6040	49.67	B
Chicopee Falls, Mass.	W1XKA	31600	9.50	E
Millis, Mass.	W1XK	9570	31.35	B
Detroit, Mich.	W8XWJ	31600	9.49	E
St. Louis, Mo.	W9XPD	31600	9.49	E
Bound Brook, N. J.	W3XAL	17780	16.87	B
Bound Brook, N. J.	W3XAL	6100	49.18	B
Bound Brook, N. J.	W3XL	17310	17.33	E
Bound Brook, N. J.	W3XL	6425	46.69	E
Lawrenceville, N. J.	WKA	21060	14.25	P
Lawrenceville, N. J.	WKF	19220	15.61	P
Lawrenceville, N. J.	WKK	21420	14.01	P
Lawrenceville, N. J.	WKN	19820	15.14	P
Lawrenceville, N. J.	WLA	18340	16.36	P
Lawrenceville, N. J.	W1LK	16270	18.44	P
Lawrenceville, N. J.	WMN	14590	20.56	P
Lawrenceville, N. J.	WOY	4753	63.11	P
Ocean Gate, N. J.	WOO	4753	63.11	P
Wayne, N. J.	W2NE	21520	13.94	B
Wayne, N. J.	W2NE	17760	16.89	B
Wayne, N. J.	W2NE	15270	19.65	B
Wayne, N. J.	W2NE	11830	25.36	B
Wayne, N. J.	W2NE	6120	49.02	B
N. York, N. Y.	W2NG	41000	7.32	E
Rochester, N. Y.	W8XAI	31600	9.49	E
Rocky Point, N. Y.	WEA	10610	28.28	E
Rocky Point, N. Y.	WEF	10620	28.25	P
Rocky Point, N. Y.	WEF	9490	31.61	P

Location	Call	Kc.	Meters	Class
Rocky Point, N. Y.	WEG	7415	40.45	P
Rocky Point, N. Y.	WKM	18860	15.91	P
Rocky Point, N. Y.	WQB-W2XBJ	17940	16.72	P
Rocky Point, N. Y.	WQF	17920	16.74	P
Schenectady, N. Y.	W2NAD	15330	19.57	B
Schenectady, N. Y.	W2NAF	9530	31.48	B
Cincinnati, Ohio	W8XAI	6060	49.50	B
Philadelphia, Pa.	W3XAU	9590	31.28	B
Philadelphia, Pa.	W3XAU	6060	49.50	B
Philadelphia, Pa.	W3XKA	31600	9.49	E
Pittsburgh, Pa.	W8XK	21540	13.93	B
Pittsburgh, Pa.	W8XK	17780	16.87	B
Pittsburgh, Pa.	W8XK	15210	19.72	B
Pittsburgh, Pa.	W8XK	11870	25.27	B
Pittsburgh, Pa.	W8XK	6140	48.86	B
Pittsburgh, Pa.	W8XKA	60500	4.96	E
Pittsburgh, Pa.	W8XKA	55500	5.41	E
Pittsburgh, Pa.	W8XKA	31600	9.49	E
Arlington, Va.	NAA	16820	17.84	T
Arlington, Va.	NAA	12630	23.75	T
Arlington, Va.	NAA	9425	31.83	T
Arlington, Va.	NAA	9250	32.43	T
Arlington, Va.	NAA	4390	68.34	T
Milwaukee, Wis.	W9XAZ	26400	11.36	E

CENTRAL AMERICA

Costa Rica				
Location	Call	Kc.	Meters	Class
Heredia	T14NRH	9670	31.02	B
Puntarenas	T18VS	7550	39.74	B
San Jose	T1EP	6687	44.86	B
San Jose	T1FA	6360	47.17	B
San Jose	T1GPH	5830	51.46	B
San Jose	T1PG	6410	46.80	B
San Jose	T1RCC	6550	45.80	B
San Jose	T1X2	5830	51.46	B
San Ramon	T15HH	5500	54.55	B

Guatemala				
Location	Call	Kc.	Meters	Class
Guatemala City	TGS	5713	52.51	B
Guatemala City	TGWA	9450	31.75	E
Guatemala City	TGWA	6000	50.00	B
Guatemala City	TG2X	5940	50.50	B

Honduras				
Location	Call	Kc.	Meters	Class
La Ceiba	HRD	6235	48.11	B
La Ceiba	HRW-HRY	11040	27.17	P
La Ceiba	HRW-HRY	8290	36.19	P
La Ceiba	HRW-HRY	6520	46.01	P
La Ceiba	HRW-HRY	6375	47.10	P
La Ceiba	HRW-HRY	5170	58.03	P
La Ceiba	HRW-HRY	4605	65.16	P
San Pedro Sula	HRP1	6357	47.20	B
Tegucigalpa	HRN	5875	51.06	B

Nicaragua				
Location	Call	Kc.	Meters	Class
Boom	YNH6	6350	47.24	P
Boom	YNH6	4610	65.08	P
Boom	YNH6	3175	94.48	P
Granada	YNLAT	7315	41.01	B
Managua	YNA	14480	20.72	P
Managua	YNAM	7200	41.67	A, B
Managua	YNGU	9300	32.26	B
Managua	YNLF	7560	39.68	B
Managua	YNLG	8505	35.27	B
Managua	YNOP	5758	52.10	B
Managua	YNIGG	6540	45.87	B
Puerto Cabezas	YNE	12680	23.66	P
Puerto Cabezas	YNE	11430	26.25	P
Puerto Cabezas	YNE	9220	32.54	P
Puerto Cabezas	YNE	7810	38.41	P
Puerto Cabezas	YNE	6340	47.32	P
Puerto Cabezas	YNE	5555	54.00	P
Puerto Cabezas	YNE	4610	65.08	P
Puerto Cabezas	YNE	3170	94.48	P
Wapam	YNJ7	6350	47.24	P
Wapam	YNJ7	4610	65.08	P
Wapam	YNJ7	3175	94.48	P
Waspoock	YNJ5	6350	47.24	P
Waspoock	YNJ5	4610	65.08	P
Waspoock	YNJ5	3175	94.48	P

Panama				
Location	Call	Kc.	Meters	Class
Aguadulce	HP51	11895	25.22	B
Colon	HP5F	6075	49.38	B
Colon	HP5K	5990	50.08	B
David	HP5L	11740	25.55	B
Panama	HP5B	6030	49.75	B
Panama	HP5J	9605	31.23	B
Panama	HP5Z	6120	49.02	B
Panama	HP5S	9565	31.36	B

El Salvador				
Location	Call	Kc.	Meters	Class
San Salvador	YSL	14985	20.02	P
San Salvador	YSL	14960	20.05	P

SOUTH AMERICA

Argentina				
Location	Call	Kc.	Meters	Class
Buenos Aires	LRU1	15280	19.63	B
Buenos Aires	LRN	9660	31.06	B
Hurlingham	LSK3	10250	29.27	P
Hurlingham	LSL1	7901	37.98	P
Hurlingham	LSL2	10300	29.13	P
Hurlingham	LSL3	15810	18.97	P
Hurlingham	LSL4	21160	14.19	P

Location	Call	Kc.	Meters	Class	Location	Call	Kc.	Meters	Class
Hurlingham	LSM2	14500	20.69	P	Maracay	VVQ	6672	44.96	P
Hurlingham	LSM3	19140	15.68	P	Maracay	VV4RD	6300	47.62	B
Hurlingham	LSN1	14530	20.65	P	Maracay	VV15RV	5917	50.71	B
Hurlingham	LSN2	9890	30.32	P	San Cristobal	VV2RA	5710	52.54	B
Hurlingham	LSN6	21020	14.27	P	Valencia	VV4RB	6520	46.01	B
Monte Grande	LSF	19600	15.31	P	Valencia	VV4RH	5917	50.71	B
Monte Grande	LSH	5435	55.19	P	Valera	VV1RG	6230	48.15	B
Monte Grande	LSX	10350	28.98	P, B					
Monte Grande	LSY	10410	28.82	P					
Bolivia					WEST INDIES				
La Paz	CP5	6080	49.34	B	Bermuda				
La Paz	CP7	15300	19.60	P	Hamilton	ZFA	5025	59.70	P
Brazil					St. George	ZFB	10055	29.84	P
Marapicu	PSA	21080	14.23	P, B	St. George	ZFD	10335	29.03	P
Marapicu	PSB	20910	14.35	P	Cuba				
Marapicu	PSD	15070	19.91	P	Camaguey	CO9JQ	8665	34.62	B
Marapicu	PSE	14935	20.09	P, B	Havana	CMA3	15505	19.35	E
Marapicu	PSF	14690	20.42	P, B	Havana	COCD	6130	48.94	B
Marapicu	PSH	10220	29.35	P, B	Havana	COCH	9428	31.82	B
Marapicu	PSJ	9660	31.06	P, B	Havana	COCQ	6010	49.92	B
Marapicu	PSK	8185	36.65	P, B	Havana	COCQ	9740	30.80	B
Rio de Janeiro	PRF5	9500	31.58	B	Havana	COCX	11435	26.24	B
Sepetiba	PPM	10310	29.10	P	Sancti Spiritus]	COHB	6280	47.77	B
Sepetiba	PPQ	11670	25.71	P	Santiago	COKG	6200	48.39	B
Sepetiba	PPU	19260	15.58	P					
Sepetiba	PPZ	18165	16.51	P	Dominican Republic				
Chile					La Romana	HI3C	6730	43.48	B
Antofagasta	CED	10230	29.33	P, B	San Pedro de Macoris	HIH	6775	44.38	B
Antofagasta	CED	8035	37.34	P	San Pedro de Macoris	HIJ	5865	51.15	B
La Granja	CEC	15865	18.91	P	Santiago de los Caballeros	HI1A	6190	48.47	B
La Granja	CEC	10670	28.12	P	Santiago de los Caballeros	HI1S	6420	46.73	B
La Granja	CEC	7740	38.76	P	Santiago de los Caballeros	HI1N	6150	48.78	B
Santiago	CB615	6150	48.78	B	Santiago de los Caballeros	HI9B	6040	49.57	B
Santiago	CB960	9600	31.25	B	Ciudad Trujillo	HIG	6280	47.77	B
Colombia					Ciudad Trujillo	HIL	6500	46.15	B
Armenia	HJ4ABH	9520	31.51	B	Ciudad Trujillo	HIN	11280	26.50	B
Barranquilla	HJ4A	3376	88.83	P	Ciudad Trujillo	HIN	6243	48.05	B
Barranquilla	HJ1ABB	9559	31.38	B	Ciudad Trujillo	HIT	6630	45.25	B
Barranquilla	HJ1ABB	6115	49.06	B	Ciudad Trujillo	HIX	6340	47.32	B
Barranquilla	HJ1ABG	6042	49.65	B	Ciudad Trujillo	HIX	5980	50.17	B
Bogota	HKV	8795	34.11	B	Ciudad Trujillo	HIZ	6310	47.54	B
Bogota	HJN	5955	50.38	B	Ciudad Trujillo	HI2D	6900	43.48	B
Bogota	HJ3ABD	6050	49.59	B	Ciudad Trujillo	HI4D	6555	45.76	B
Bogota	HJ3ABF	6070	49.42	B	Ciudad Trujillo	HI4V	6477	46.33	B
Bogota	HJ3ABH	6012	49.90	B	Ciudad Trujillo	HI7P	6805	44.07	B
Bogota	HJ3ABX	6122	49.01	B	Ciudad Trujillo	HI8A	6479	46.31	B
Bucaramanga	HJ2ABD	5990	50.08	B	Ciudad Trujillo	HI8Q	6198	48.08	B
Buenaventura	HJU	9510	31.58	B	French West Indies				
Cali	HJ5ABD	6085	49.30	B	Fort de France, Martinique		9360	32.05	B
Cartagena	HJ1ABE	9500	31.58	B	Haiti				
Cartagena	HJ1ABP	9618	31.18	B	Port-au-Prince	HH2S	5925	50.64	B
Cucuta	HJ2ABC	9575	31.34	B	Port-au-Prince	HH2V	9551	31.41	B
Ibague	HJ4ABC	6451	49.26	B	Port-au-Prince	HH3W	9645	31.10	B
Manizales	HJ4ABB	6108	49.11	B	Jamaica				
Medellin	HJ4ABD	5780	51.90	B	Stony Hill	VRR4	11595	25.88	P
Medellin	HJ4ABE	6097	49.20	B	EUROPE				
Medellin	HJ4ABP	6033	49.72	B	Austria				
Pereira	HJ4ABU	6150	48.78	B	Vienna	OER2	11801	25.42	B
Quibdo	HJ1ABC	6000	50.00	B	Azores				
Santa Marta	HJ1ABJ	6025	49.79	B	San Miguel	CT2AJ	4002	74.77	A, B
British Guiana					Belgium				
Georgetown	VP3BG	6130	48.94	B	Ruysselede	ORG	19200	15.62	P
Georgetown	VP3MR	6010	49.92	A, B	Ruysselede	ORK	10330	29.03	B
Dutch Guiana					Bulgaria				
Paramaribo	PZH	7000	42.86	B	Sofia	LZA	14970	20.04	B
Ecuador					Czechoslovakia				
Ambato	HCVT	6578	45.60	B	Podebrady	OLR2A	6010	49.92	B
Guayaquil	HC2CW	8400	35.71	B	Podebrady	OLR2B	6030	49.75	B
Guayaquil	HC2EBA	9441	31.78	B	Podebrady	OLR2C	6115	49.06	B
Guayaquil	HC2ET	4600	65.22	B	Podebrady	OLR3A	9550	31.41	B
Guayaquil	HC2JSB	7854	38.20	B	Podebrady	OLR3B	9504	31.57	B
Guayaquil	HC2RL	6635	45.22	B	Podebrady	OLR4A	11840	25.34	B
Quito	HCETC	6970	43.04	B	Podebrady	OLR4B	11760	25.51	B
Quito	HCJB	8948	33.53	B	Podebrady	OLR4C	11875	25.26	B
Quito	HCJB	4107	73.05	B	Podebrady	OLR4D	11900	25.21	B
Quito	HCJPM	5735	52.31	B	Podebrady	OLR5A	15230	19.70	B
Riobamba	PRADO	6620	45.32	B	Podebrady	OLR5B	15320	19.58	B
Paraguay					Podebrady	OLR5C	15160	19.79	B
Asuncion	ZP10	8300	36.14	B	Podebrady	OLR6A	21450	13.99	B
Asuncion	ZP11	3800	78.95	B	Denmark				
Peru					Skamlebaek	OXY	6060	49.50	B
Arequipa	OAN6A	6122	49.01	B	France				
Chiclayo	OAX1B	6164	48.67	B	Paris	FYB	10578	28.36	T
Cuzco	OAX7A	6128	48.96	B	Pontoise	TPA2	15243	19.68	B
Huancayo	OAX4P	6122	49.01	B	Pontoise	TPA3	11880	25.25	B
Ica	OAX5A	1804	25.42	B	Pontoise	TPA4	11720	25.60	B
Lima	OAX4D	5780	51.90	B	Pontoise	TYA	12215	24.56	P
Lima	OAX4G	6260	47.92	B	Pontoise	TYA2	9040	33.19	P
Lima	OAX4I	9330	32.15	B	Pontoise	TYB	12250	24.49	P
Lima	OAX4K	6425	46.67	B	Pontoise	TYE	18090	16.58	P
Lima	OCI	18670	16.08	P	Pontoise	TYE2	13760	21.80	P
Uruguay					Pontoise	TYE3	10430	28.76	P
Cerrito	CWH	13140	22.83	P	St. Assise	FTK	15880	18.89	P
Montevideo	CWD	5830	51.46	P	S.S. Ile de France	FNTQ	8830	33.96	P
Montevideo	CXA4	6125	48.98	B	S.S. Normandie	FNSK	8830	33.96	P
Venezuela					S.S. Paris	FNSM	8830	33.96	P
Barquisimeto	YV3RA	5899	50.84	B	Germany				
Caracas	YV5RC	5800	51.72	B	Koenigs Wusterhausen	DOT	14410	20.82	P
Caracas	YV5RD	6156	48.73	B	Koenigs Wusterhausen	DON	10128	29.62	P
Caracas	YV5RF	6380	47.02	B	Koenigs Wusterhausen	DOF	5255	57.09	P
Caracas	YV5RH	6400	46.88	B	Koenigs Wusterhausen	DOG	5335	56.23	P
Caracas	YV5RJ	6250	48.00	B	Nauen	DFT	7812	38.40	P
Caracas	YV5RP	6270	47.84	B	Nauen	DGU	9650	31.09	P
Ciudad Bolivar	YV6RB	6545	45.84	B	Nauen	DGM	9920	30.24	P
Coro	YV1RI	6205	48.35	B	Nauen	DGD	10210	29.38	P
Maracaibo	YV1RM	6500	46.15	B	Nauen	DGH	10440	28.74	P
Maracaibo	YV1RB	5850	51.28	B					
Maracaibo	YV1RD	6075	49.38	B					
Maracaibo	YV1RH	6365	47.14	B					
Maracay	YVQ	13337	22.47	P					

Location	Call	Kc.	Meters	Class	Location	Call	Kc.	Meters	Class
Nauen	DFL	10850	27.65	P	Norway				
Nauen	DGL	12035	24.93	P	Jeloy	LKJ1	9530	31.48	B
Nauen	DFC	12985	23.10	P	Jeloy	LKJ1	6130	48.94	B
Nauen	DGG	13180	22.76	P	Jeloy	LKJ1	4100	73.17	E
Nauen	DGZ	14605	20.54	P	Poland				
Nauen	DFD	14665	20.46	P	Warsaw	SPW	13635	22.00	B
Nauen	DGR	17341	17.30	P	Portugal				
Nauen	DFB	17520	17.12	P	Lisbon	CSW	11040	27.17	B
Nauen	DFQ	18700	16.04	P	Lisbon	CSW	9940	30.18	B
Nauen	DFM	19460	15.42	P	Lisbon	CT1AA	9665	31.04	B
Nauen	DFJ	19700	15.23	P	Parede	CT1GO	11900	25.21	B
Nauen	DFJ	19700	14.90	P	Parede	CT1GO	6132	48.92	B
Nauen	DGW	20020	14.90	P	Rumania				
Nauen	DGW	20140	14.90	P	Bucharest	YOI	6000	50.00	B
Nauen	DGS	20500	14.63	P	Spain				
Nauen	DGT	23350	12.85	P	Barcelona	ECN1	7220	41.55	B
Nauen	DGV	23350	12.35	P	Barcelona	EGP1	7020	42.73	B
Nauen	DGX	26800	11.19	P	Caramaca	EAJ33	10350	28.98	B
Nauen	DCE	27400	10.95	P	Madrid	EAQ	19720	15.21	P
Nauen	DGF	27800	10.79	P	Madrid	EAQ	9860	30.43	B
Norddeich	DAF	4400	68.18	P	Madrid	EAR	9480	31.65	B
Norddeich	DAF	5670	52.91	P	Madrid	EDN	10070	29.79	E
Norddeich	DAF	6600	45.45	P	Madrid	EHV	20860	14.37	P
Norddeich	DAF	8765	34.23	P	San Sebastian	7200	41.67	B
Norddeich	DAF	11340	26.46	P	Valencia	7165	41.87	B
Norddeich	DAF	13100	22.90	P	Sweden				
Norddeich	DAF	13275	22.60	P	Motala	SBG	11705	25.63	E
Norddeich	DAF	17265	17.30	P	Motala	SBG	6060	49.50	E
Rehmate	DLC	7332	40.92	P	Stockholm	SM5SD	7281	41.20	B
Rehmate	DLO	19947	15.04	P	Stockholm	SM5SX	11705	25.63	B
Ruegen	DAS	4500	66.67	P	Switzerland				
Ruegen	DAS	5635	53.24	P	Basle	HB9B	3770	79.56	B
Ruegen	DAS	8330	36.01	P	Lausanne	HB9AQ	3525	85.11	B
Zeesen	DJA	9560	31.38	B	Prangins	HBH	18480	16.23	P
Zeesen	DJB	15200	19.74	B	Prangins	HBJ	14535	20.64	P
Zeesen	DJC	6020	49.83	B	Prangins	HBO	11385	26.35	B
Zeesen	DJD	11770	25.49	B	Prangins	HBL	9595	31.27	B
Zeesen	DJE	17760	16.89	B	Prangins	HBP	7797	38.47	B
Zeesen	DJL	15110	19.85	B	United Kingdom				
Zeesen	DJM	6079	49.35	B	Daventry	GSA	6050	49.59	B
Zeesen	DJN	9540	31.45	B	Daventry	GSB	9510	31.55	B
Zeesen	DJO	11795	25.43	B	Daventry	GSC	9580	31.32	B
Zeesen	DJP	11855	25.31	B	Daventry	GSD	11750	25.53	B
Zeesen	DJQ	15280	19.63	B	Daventry	GSE	11860	25.30	B
Zeesen	DJR	15340	19.56	B	Daventry	GSF	15140	19.81	B
Zeesen	DZA	9675	31.01	P	Daventry	GSG	17790	16.86	B
Zeesen	DZB	10042	29.87	P	Daventry	GSH	21470	13.97	B
Zeesen	DZC	10290	29.16	P	Daventry	GSI	15260	19.66	B
Zeesen	DZE	12130	24.73	P	Daventry	GSJ	21530	13.93	B
Zeesen	DZG	15360	19.53	P	Daventry	GSK	26100	11.49	B
Zeesen	DZH	14460	20.75	P	Daventry	GSL	6110	49.10	B
S.S. Adolph Woermann	DHAK				Daventry	GSN	11820	25.38	B
S.S. Bremen/DOAH	DOAH				Daventry	GSO	15180	19.76	B
S.S. Cap Arcona	DHDL				Daventry	GSP	15310	19.60	B
S.S. Columbus	DOBX				Rugby	GAU	18620	16.11	P
S.S. Deutschland/DJNB	DJNB				Rugby	GBB	13585	22.08	P
S.S. Europa/DOAI	DOAI				Rugby	GBC	4975	60.30	P
S.S. Gneisenau	DOQY				Rugby	GBS	12150	24.69	P
S.S. Hamburg/DHJZ	DHJZ				Rugby	GBU	12290	24.41	P
S.S. Hansa/DHAO	DHAO				Rugby	GBW	14440	20.78	P
S.S. Jan Wellem	DIAE				Rugby	GCP	10770	27.86	P
S.S. Milwaukee/DIDP	DIDP				Rugby	GDW	4820	62.24	P
S.S. New York/DJNY	DJNY				S.S. Queen Mary	GBTT			
S.S. Njassa	DHRR				S.S. Berengaria	GBZW			
S.S. Ostmark	DORM	4050	74.07	P	S.S. Homeric	GDLJ	17640	17.00	P
S.S. Potsdam	DOQS	4285	40.01	P	S.S. Majestic	CFWV	13320	22.70	P
S.S. Pretoria	DJSG	8470	35.42	P	S.S. Aquitania	GLRZ	8830	33.96	P
S.S. Reliance/DHTV	DHTV	11140	26.93	P	U. S. S. R.				
S.S. Scharnhorst	DOOQ	12325	24.34	P	Baku	RIO	10170	29.48	P
S.S. Schwabenland	DOFW	12600	23.81	P	Moscow	RAN	9600	31.25	B
S.S. St. Louis/DIFG	DIFG	16665	18.00	P	Moscow	RKI	15040	19.95	B
S.S. Tanganjika	DHXE				Moscow	RV59	12000	25.00	B, P
S.S. Ubena	DHYE				Moscow	RV59	6000	50.00	B
S.S. Usambara	DHYM				Tiflis	RIR	10080	29.76	P
S.S. Usaramo	DHYN				Vatican City				
S.S. Ussukuma	DHYO				Vatican City	HVJ	15123	19.84	B
S.S. Wadai	DHYZ				Vatican City	HVJ	5969	50.26	B
S.S. Wahehe	DHYD				Yugoslavia				
S.S. Wangoni	DHZM				Belgrade	YTC	6100	49.20	B
S.S. Watussi	DHZP				Hungary				
S.S. Westfalen	DODB				Szekesfehervar	HAS3	15370	19.52	B
					Szekesfehervar	HAS5	17130	17.51	B
					Szekesfehervar	HAT4	9125	32.87	B
					Iceland				
					Reykjavik	TFJ	12235	24.52	B
					Italy				
					Coltano	IAC	17750	16.90	P
					Coltano	IAC	12795	23.44	P
					Coltano	IAC	4355	68.89	P
					Rome	IRW	19520	15.37	P
					Rome	IRY	16120	18.61	P
					Rome	I2R03	9635	31.14	B
					Rome	I2R04	11810	25.40	B
					S.S. Rex	ICEJ	13050	22.99	P
					S.S. Conte di Savoia	IBLI	13050	22.99	P
					S.S. Conte Rosso	IBEI	13050	22.99	P
					S.S. Conte Verde	IBGI	13050	22.99	P
					Madeira				
					Funchal	CT3AQ	4000	75.00	B, E
					Netherlands				
					Dordrecht	PIIJ	7082	42.36	A, B
					Huizen	PCJ	15220	19.71	E
					Huizen	PCJ	9590	31.28	E, B
					Huizen	PHI	17770	16.88	B
					Huizen	PHI	11730	25.57	B
					Kootwijk	PCK	18405	16.30	P
					Kootwijk	PCL	16305	18.40	P
					Kootwijk	PCM	18545	16.18	P
					Kootwijk	PKD	10410	28.82	P
					Kootwijk	PDM	18600	16.13	P
					Kootwijk	PDV	12060	24.88	P
					Kootwijk	PGA	7830	38.31	P

All ships on all of the following frequencies:

All ships on all of the following frequencies:

Abbreviations for Class Column

- A—Amateur
- B—Broadcast
- E—Experimental
- F—Frequency
- P—Phone
- T—Time Signals

CZECH OBSERVER

This is the Listening Post of Short-Wave Observer Ferry Friedle, who states (and we believe him) he gets a lot of fun out of short-wave DX'ing.





THE RUGBY STATION

Listening post observers from all over the world have reported hearing the Rugby transmissions and this photograph shows the layout of the transmitters in the telephony building.


THE fifty-second installment of the DX Corner for Short Waves contains the World Short-Wave Time-Table for 24-hour use all over the world and Official Observers' reports of stations heard this month. Consult these two items regularly and make your all-wave set pay big dividends!

Credit Where It Is Due

In carrying out our policy of giving credit for extra fine reports from Listening Posts, our commendations go out to the following Observers: Alfred, Howald, Ralat, Geneve, Partner, Shamleffer, Dressler, Gallagher and Doyle. We are glad to see that there are some new ones on the list this month. Congratulations! Also, we are glad to acknowledge the source of all of the verification cards that appeared on last month's attractive cover. They were sent in by Observer Hugo Richter of Zurich, Switzerland. This cover has been mentioned favorably in many of the letters from readers.

DX Corner Membership

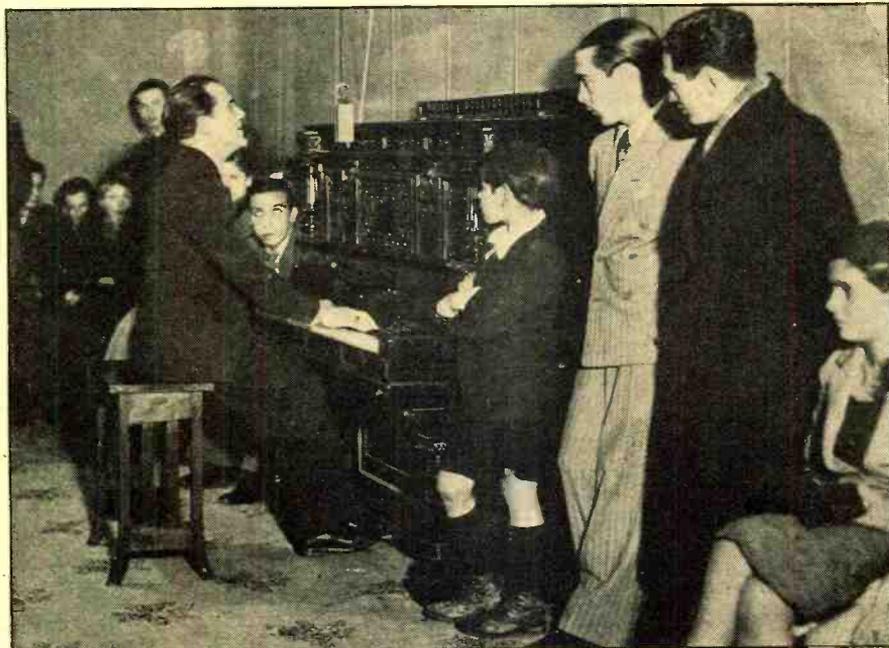Reporting progress for the year 1937, it is noted that our Listening Post Observer membership has increased during the past



The DX for the

Conducted by

Laurence

six months by leaps and bounds. In a quick check-up of Listening Posts, the figures indicate in rough numbers 800 members in good standing. This list will be published complete in the August issue. Our members will be happy to know that we now have Official Observers in 43 States in our own country and in 58 foreign countries scattered all over the earth. The information received in short-wave reports from these Observers is doing much to make the Short-Wave DX Corner a general headquarters for short-wave information for listeners all over the world.

Reports of Listening Post Observers and Other Short-Wave Readers of the DX Corner

LISTED in the following columns is this month's consolidated reports of short-wave stations heard by our worldwide listening posts. Each item is credited with the Observer's surname. This allows our readers to note who obtained the information. If any of our readers can supply Actual Time Schedules, Correct Wavelengths, Correct Frequencies and any other Important Information (in paragraphs as recommended), the DX Editor, as well as our readers, will be grateful for the information. On the other hand, readers seeing these reports can try their skill in pulling in the stations logged and in trying to get complete information on these transmissions. The report for

this month, containing the best information available to date, follows:

Europe

OLR, Prague, Czechoslovakia, 11,840 kc., Sunday 11 p.m.-12:05 a.m., (Lopez, Jensen), 9550 kc., Monday and Thursday 8-10 p.m., (Augustine, Harris), 11,760 kc., (Carton, Fallon, Geneve, Coover, Wittig.)

OLR3A, Prague, Czechoslovakia, 9550 kc., 8-10 p.m. (from ann.), (Partner), Monday and Thursday 8-10 p.m. (from ann.), (Dressler, Shamleffer), 9560 kc. (Alfred, Law), 8640 kc., 9:30-10 p.m. (Wittig, Ralat, Hedgeland).

OLR2A, Prague, Czechoslovakia, 6010 kc., 10-11 p.m., (from ann.), (Partner).

OLR4A, Prague, Czechoslovakia, 11,840 kc., (from ann.), (Partner), Monday and Thursday 10-11 p.m., (Dressler, Alfred), 9560 kc. sing with church bells, (Howald), wants reports (Wittig), 15,230 kc., daily 2-2:15 p.m., (Herzog, Hedgeland, Hare, Staley, Beckemeyer, DeLaet).

OLR5A, Prague, Czechoslovakia, 15,230 kc., (from ann.), (Partner), Monday and Thursday 8-10 p.m., daily 7:55-9:50 a.m., 11,840 kc., (Herzog, Hare), daily 1-2:15 p.m., (De Laet).

OLR4C, Prague, Czechoslovakia, 11,875 kc. (from ann.), (Partner), 9:15 p.m., (Ralat).

DJG, Zeesen, Germany, 15,200 kc., (Jaime), 15,280 kc., (Alfred, Shamleffer), 7-11 a.m., (Herzog), 9540 kc., (Cartin), 9 a.m.-11 p.m., (Howald).

DJN, Zeesen, Germany, 9540 kc., 12:05-4 a.m., (Alfred), 9480 kc., (Wittig), daily 7-9 p.m., (Wollenschlager, Shamleffer).

DJL, Zeesen, Germany, 15,110 kc., 4:50-10:45 p.m., (Alfred, Hartman), from noon on, (Howald), daily 8-9 a.m. (Sigundson).

DJA, Zeesen, Germany, 9560 kc., (Jaime), 12:05-4 a.m., (Alfred, Cartin, Herzog, Shamleffer).

DJB, Zeesen, Germany, 15,200 kc., (Jaime, Alfred), 2-2:30 p.m., (Herzog, Shamleffer, Cartin), 9 a.m.-11 p.m., (Howald), daily 7-9 p.m., (Wollenschlager, Herzog, Ryan, Sigundson, Coover).

DJC, Zeesen, Germany, 6020 kc., 4:50-10:45 p.m., (Alfred, Cartin).

DJD, Zeesen, Germany, 17,770 kc., 7 p.m., (Coover), 4:50-10:45 p.m., (Alfred, Law, Shamleffer, Eramo, Sutker), 11 p.m.-3 p.m., (Cartin, Sprague), daily from noon, (Howald),

STUDIO SCENE AT HJ3ABD

Jose Bohr enthalls guests at this popular South American station, which operates on 6050 kc.

Corner SHORT WAVES

M. Cockaday

Sprague), daily 7-9 p.m., (Wollenschlager, Wacker, Herzog, Ryan, Sigurdson, Wittig, Pylate).

DJR, Zeesen, Germany, 15,340 kc., 8-9 a.m., (Doyle, Kemp).

DJP, Zeesen, Germany, 11,885 kc., (Law), 11,795 kc., Thursday 2:30-2:50 p.m., (Shamleffer), daily 9 p.m., 12:30 a.m., (Pylate).

DZH, Zeesen, Germany, 14,460 kc., daily relaying DJD and DJO, (Herzog).

DJM, Zeesen, Germany, 6079 kc., 5:30 p.m., (Ralat, Hedgeland).

DZA, Zeesen, Germany, 9675 kc., irregular, (Doyle).

DJE, Zeesen, Germany, 17,760 kc., 12 a.m., and on, (Howald, Doyle, Kemp).

DFL, Nauen, Germany, 10,850 kc., 8:30 p.m., relaying DJB and DJD, (Herzog).

TPA4, Paris, France, 25.6 meters, 11:30 p.m., (Weikal, "Radio Colonial," (Fallon), 19.6 meters, daily 7 a.m., (Hendry), 11,720 kc., 4:45 a.m.-2:30 p.m., (Cartin, Howald, Kemp, Ryan, Wittig, Ralat).

TPA2, Paris, France, 15,245 kc., 6 a.m., (Alfred, Randle, Kemp).

TPA3, Pontoise, France, 11,885 kc., 6:35 p.m., (Eramo, Kemp), 11:15 p.m., (Ryan).

Pontoise, France, no call letters given, 9040 kc., 2:30 a.m., (from veri), (Gallagher).

I2RO, Rome, Italy, 9635 kc., 6 p.m., (Coover), 5-7 p.m., (Lopez), 11,810 kc., (Eramo), Sunday 10 a.m.-12:15 p.m., (Cartin, Sprague), Wednesday 7-9 p.m. (Wollenschlager, Ralat, Ruppert, Black, Ryan).

I2RO3, Rome, Italy, 9635 kc., 12:30-7:30 p.m., daily (Alfred), 9610 kc., (Ryan, Stillman).

I2RO4, Rome, Italy, 11,810 kc., 7-11:20 a.m., (Alfred, Stillman).

"Radio Milan," Milan, Italy, 28 meters, irregular, (Ralat).

HVJ, Vatican City, 15,121 kc., 10:30-10:45 a.m., 5969 kc., 2-2:15 p.m., Sunday and Holidays, 5969 kc., 5 a.m., (from veri), (Foshay, Cartin).

GSA, Daventry, England, 6059 kc., 6-11 p.m., (Cartin), 6-9 p.m., (Pylate, Doyle, Kemp).

GSB, Daventry, England, 9510 kc., daily 4-5:45 p.m., 6-8 p.m., (Alfred, Fallon, Shamleffer, Weiss, Dressler, Ryan).

GSC, Daventry, England, 9580 kc., 5 p.m., (Coover), daily 9-11 p.m., (Dressler, Cartin, Howald, Wollenschlager).

GSF, Daventry, England, 15,140 kc., 6-8:30 a.m., 9-12 a.m., (Dressler), daily 4-5:45 p.m., (Alfred, Law, Shamleffer), 6-8 p.m., (Herzog, Fallon), 9-12 p.m., (Howald, Doyle).

GSG, Daventry, England, 17,790 kc., 6-8:30 a.m., 9-12 a.m., (Dressler), 4-5 p.m., (Herzog, Doyle, Beck).

GSH, Daventry, England, 21,470 kc., 6-8:30 a.m., 9-12 a.m., (Dressler, Howald).

GSD, Daventry, England, 11,750 kc., daily 9-11 p.m., (Dressler), daily 4-5:45 p.m., 6-8 p.m., (Alfred, Law, Cartin, Fallon, Howald, Wollenschlager, Kemp, Ryan, Coover, Pylate).

GSN, Daventry, England, 11,820 kc., daily 7-9 p.m., (Wollenschlager, Doyle).

GSO, Daventry, England, 15,180 kc., daily 7-9 p.m., (Wollenschlager), daily 6:20-8:30 p.m., 4-6 p.m., (Dressler).

GSK, London, England, 26,100 kc., new station, (Partner).


GSI, London, England, 15,260 kc., 12:15-3:45 p.m., (Doyle).

GSP, London, England, 15,310 kc., (Doyle), daily 6:20-8:30 p.m., (Dressler), 9:45 p.m., (Pylate).

GSW, Daventry, England, 9790 kc., testing 8:15 p.m., new station, (Ryan).

SPW, Warsaw, Poland, 13,630 kc., 8 p.m., (Coover, Herzog, Partner), 13,050 kc., Friday 12:30-1:30 p.m., (Doyle).

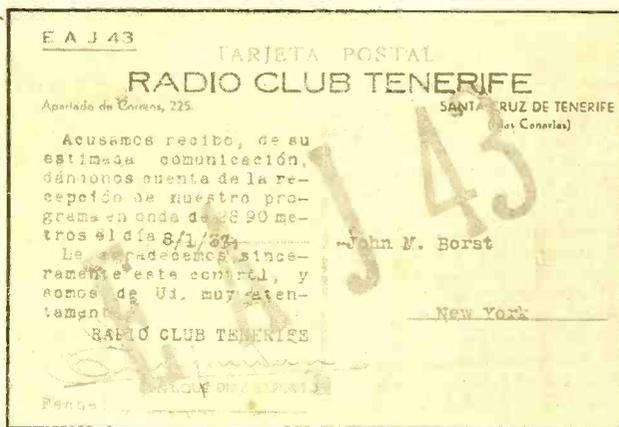PCJ, Hilversum, Holland, 9590 kc., 7 p.m., (Coover), Sunday 7-8 p.m., (Dressler), 31,280 kc., (Jaime), requests reports, (Randle), 15,220 kc., Tuesday, 4:30-6 a.m., Wednesday 8-11 a.m., (Piorko, Herzog, Shamleffer, DeMent, Cartin, Ralat, Foshay, How-



A PRIZE VERIFICATION

Not many listeners have been fortunate enough to receive this "veri" from the Radio Club Tenerife. Suppose you try for it.

ald, DeLaet, Black, Doyle, Kemp), Slogan: "Philips Radio," Address: Hilversum, Holland.

PIIJ, Dordrecht, Holland, 7088 kc., 14,164 kc., 11:10-11:50 a.m., 12:00-12:30 p.m., Saturdays, (from ann.), (Hamilton).

PHI, Huizen, Holland, 17,775 and 11,730 kc., (Herzog), 7 a.m.-2 p.m., Monday, Tuesday and Friday 8-9:30 a.m., Saturday, 8-10 a.m., (Bower, Doyle, Kemp, Atherton, Beck), rebroadcasted a Jugoslavian program, (Shamleffer).

LKJ1, Jeloy, Norway, 9530 kc., Wednesday 7-8 p.m., (Weiss, Partner, Beck).

SM5SX, Stockholm, Sweden, 17,710 kc., Saturday and Sunday, 11 a.m.-5 p.m., (Doyle).

"Radio Beograd," Belgrade, Yugoslavia, 6100 kc., daily 1 a.m.-5 p.m., (Foshay), Wednesday 7-9 p.m., 9590 kc., (Shamleffer).

TFJ, Reykjavik, Iceland, 12,235 kc., Sunday 1:40-2 p.m., (Alfred, Law, Hare, Sprague), Sunday 2-2:30 p.m., (Geneve, Kemp, Sigurdson), Address: State Broadcasting Service, Box 547.


LZA, Sofia, Bulgaria, 14,915 kc., Sunday 1:30-2 a.m., 3:30-4 a.m., (Alfred), 1-3 a.m., 6:30-8:30 a.m., noon-2 p.m., 2:40-5 p.m., except Saturday and Sunday, (Geneve).

ON4VR, Namur, Belgium, 6690 kc., testing 10:15-11 a.m., Sunday (From-
(Turn to page 32)

THE TENERIFE STUDIO

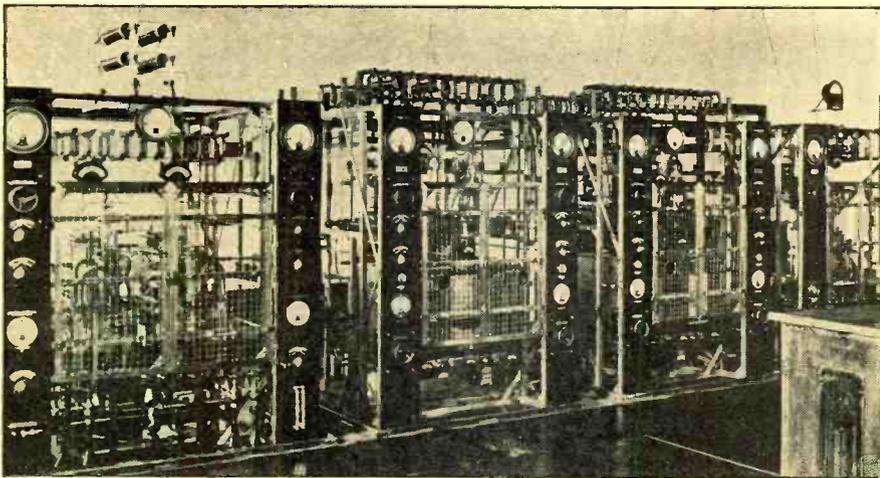This is the broadcasting studio of EAJ43, whose verification card is shown elsewhere on this page.





The DX Corner (Short Waves)

(Continued from page 29)

ann.), (Geneve), Address: 66 Rue Malevey, St. Servais, Namur.

OER2, Vienna, Austria, 11,800 kc., (Ruppert), 11,780 kc., (Hedgeland), daily except Saturday 9 a.m.-5 p.m., Saturday 9 a.m.-6 p.m., (from veri.), (Foshay, Geneve, Partner, Doyle, Stevens).

HAT4, Budapest, Hungary, 9125 kc., Sunday 6-8 p.m., (Dressler, Alfred, Cindel, Hartmann, Hartzell, Doyle, Geneve, Ralat).

HAT3, Budapest, Hungary, 9120 kc., 12:30 a.m.-5:30 p.m., (Cartin, Doyle).

HAS3, Budapest, Hungary, 15,370 kc., 9-10 a.m., (Doyle, Partner, Doyle).

OXY, Skamlebaek, Denmark, 6050 kc., testing 4-5 p.m., (Lueth).

ERGU, Barcelona, Spain, 7150 kc., 5 p.m., (Betances), Slogan: "Radio Esquena."

"Radio Nobi," Moroso Column, Milicias Alicante, Spain, 7130 kc., 4:15 p.m., (Betances).

EA4TSD, Madrid, Spain, 7190 kc., 9 p.m., (Ralat), Slogan: "Emisora del Partido Socialista Espanol."

EA1VL, Pontevedra, Spain, 7275 kc., 5 p.m., (Betances), Slogan: "Radio Pontenedra."

EA4CL, Madrid, Spain, 7020 kc., (Betances).

UDD, Dunute, Aragon Front, Spain, 7150 kc., irregular, (Betances).

EAH, Valleras, Spain, 9480 kc., 11:15-11:45 p.m., (Beck).

ECN1, Barcelona, Spain, 6996 kc., daily 5 p.m., (Betances), Slogan: "Radio Esquerra."

"Falange #1," **ECE1**, Valladolid, Spain, 7010 kc., irregular and 5 p.m., (Betances), rebel station, daily 5-6:30 p.m., (Kober), 7200 kc., Sunday 7 p.m., (Ralat).

EAJ8, Bilbao, Spain, 67.4 meters, 8:25 p.m., desires reports, (Randle).

EARR, Madrid, Spain, 14,500 kc., 4-5 p.m., official rebel army station, (Geneve, Stevens).

"Radio Requete," San Sebastian, Guipuzcoa, Spain, 7200 kc., daily 5-8 p.m., (Ralat), 7100 kc., (Betances).

EAQ, Madrid, Spain, 9860 kc., 9 p.m., (Coover), 5:30-7 p.m., (Lopez) 9500 kc., desires reports, (Dressler, Alfred, Harris, Herzog, De Ment, Ralat, Beckemeyer, Shamleffer, Cartin, Fallon, Hays, Chambers, Sprague, Wollenschlager, Atherton, Tate,

THE TRANSMITTER AT ROME

Listeners hearing the 12RO transmissions will be interested in this photograph of the Marconi transmitters employed at that station.

Hedgeland, Coover, Beckemeyer, Kemp, Doyle, Hare, Ryan, Wittig, Beck, Unger, Gossett), Address: P. O. Box 951.

MEET OBSERVER PIORKO

Poland is now well-represented by Observer P. Piorko, shown below seated in his DX Corner.



HAVE YOU THIS ONE?

Mr. Gustave A. Magnuson of Providence, R. I. is the lucky recipient of this verification from Sweden. We owe Observer Magnuson and his daughter an apology for a recent photograph showing Miss Magnuson as the *XYL* rather than the daughter.

EAQ2, Madrid, Spain, 9480 kc., 9:30 p.m., (Markuson), daily 6:30-7:30 p.m., (Shamleffer), Tuesday and Friday, 7:45-9:30 p.m., (Cindel, Weikal), requests reports, (Alfred, Schrock, Messer, Ralat, Atkinson, Harris, Hedgeland, De Ment, Fallon, Beckemeyer, Herzog, Wacker, Wilson, Beck, Ortiz, Jensen, Murphy, Tate, Lopez, Hurley, Kernan, Dressler, Black, Kemp, Buchanan, Staley, Kentzel, Coover, Murray), Slogan: "The Voice of Spain," Address: P. O. Box 951.

"Radio Nacional," Spain, 14,000 kc., 2-2:45 p.m., (Hamilton).

CSW, Lisbon, Portugal, 9940 kc., 7 p.m., (Coover), 11,040 kc.-6 p.m., (from veri.), (Betances), daily 9 a.m.-2 p.m., (Smith, Jaime, Alfred, Hedgeland), noon-6 p.m., (Herzog, Dressler, Shamleffer), 6-8 p.m., 9940 kc., noon-6 p.m., (11,040 kc.), (Lueth, Ralat, Doyle, Kemp, Ryan, Buchanan, Kernan), Address: Rua do Quelhas, Lisbon.

CT1AA, Lisbon, Portugal, 9650 kc., (Jaime), Tuesday, Thursday and Saturdays 4-7 p.m., Sundays until 8:15 p.m., (Alfred, Randle, Sporn), 9663 kc., (Buchanan).

CSL, Lisbon, Portugal, 6150 kc., 7-9 a.m., (Cartin).

Lisbon, Portugal, 5970 kc., 2-5:30 p.m., Catholic station. (Geneve).

RKI, Moscow, U.S.S.R., 15,080 kc., 2 p.m., (Atherton, Kemp).

RNE, Moscow, U.S.S.R., 12,000 kc., (Gallagher), Sunday and Wednesday, 6-7 a.m., Sunday 10-11 a.m., (Atherton, Alfred), Sunday 4-5 p.m., (from veri.), (Law, Hedgeland, Herzog), Monday, Wednesday and Friday 4-5 p.m., (from veri.), Foshay, Hartzell, Blanchard, Hedgeland), 12,190 kc., wants reports, (Fallon, Kemp, Buchanan).

RAN, Moscow, U.S.S.R., 9600 kc., 6-7 p.m., (Lopez), daily 7-9:15 p.m., (Atherton, Fallon, Alfred, Law), 9520 kc., (Wittig, Foshay, Hartzell, Doyle, Blanchard, Dressler, Shamleffer, Ryan, Kentzel, Randle, Howald, Herzog), Address: Radio Centre, Moscow.

RV59, Moscow, U.S.S.R., Sunday, Monday, Wednesday and Friday, 4-5 p.m., (Atherton), 5996 kc., (Alfred), daily 7-9:15 p.m., (from veri.), (Law, Herzog, Blanchard, Spain).

HBO, Geneva, Switzerland, 11,402 kc., (from ann.), (Alfred), until 8:05 p.m., (Shamleffer), Saturday 7:25 p.m., (Dressler, Ralat), 9340 kc., (Beck).

HBJ, Geneva, Switzerland, 14,535

(Turn to page 46)

ROYAL TECHNICAL UNIVERSITY, STOCKHOLM

SWEDEN

RADIO *Herr Gustave A. Magnuson* 11,705

WE HAVE RECEIVED YOUR REPORT CONCERNING OUR *MC/S*

rundradio TRANSMISSION ON *Jan 1st 1937* AT *1214-2210* GMT

SM5SX

RECEIVER	TRANSMITTER	ANTENNA
10-TUBE SUPERHET	CRYSTAL-CONTROLLED PLATE-MODULATED 204-A IN FINAL STAGE	2 X E-W 400 W OUTPUT

MANY THANKS AND 73

H. Stadel
OP



"OPEN"—FOR BUSINESS!

The closet-door work-bench opened up for use, with the extension lamp in place and all tools handy.

FOR many years it was my fond hope to have a Work Bench for my own exclusive use. In common with many other home experimenters it was my misfortune to have only the kitchen table available to work on. It always seemed to me that the minute my work became most interesting I would have to remove my apparatus and clear the table for some meal. This meant that the apparatus and tools would have to be carried back and forth to the closet which was allotted as a storeroom.

Becoming disgusted with the continual interruptions, it was decided that a permanent Work Bench was needed to

A "Closet-Door" RADIO WORK Bench

By Walter L. Linde


HERE is the ideal Work Bench for the small apartment. Due to the ease with which it can be folded out of sight it meets with the hearty approval of the most critical housewife!

keep peace in the home. An agreement was reached with the family to build a bench provided that it did not destroy the appearance of the room used.

After a careful survey of the available space it seemed that a bench in the closet used for storage would suit the requirements, but this had the objection of being cramped to work at because it was necessary to sit within the doorway when working at the bench. After several variations the bench had evolved itself into a simple drop-leaf attached to the inside of the closet door which opened into my bedroom. While this was satisfactory to work at the inaccessibility

COMPREHENSIVE TOOL CHEST

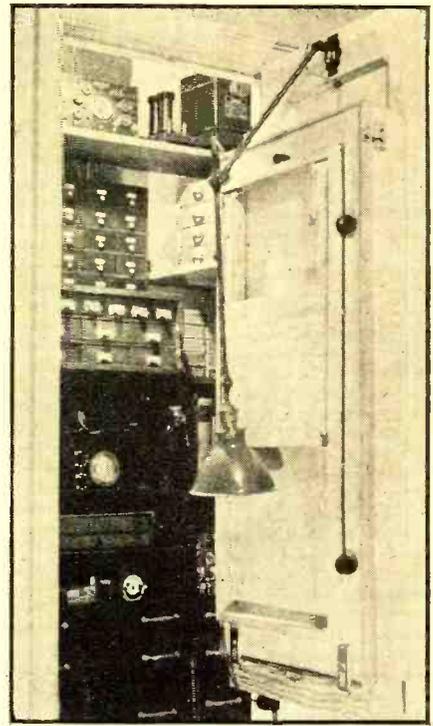Below, at left: View of the tool-box ready for instant use. At right: Close-up of the installation with the drill holders sawing out in handy position.





"CLOSED"—FOR LUNCH!

The work-bench is shown here folded up against the door, which, when slammed, cleans up the room.

of tools was a stiff problem. The final design brought about a combination tool-rack and drop-leaf work table.

The plans called for a rectangular box, the cover of which was to be used as the drop-leaf, work-table. The size was determined by both the door and the fact that a standard sized 48 by 48 inch 5-ply veneer panel would supply all the main lumber without any waste. The overall size of the cabinet when closed is 48 inches high, 21 inches wide and 6½ inches deep. The back of the cabinet and the drop-lid are both 45 inches by 21 inches. The sides are 3 inches wide by 48 inches long and are mounted on the face of the back (Turn to page 60)

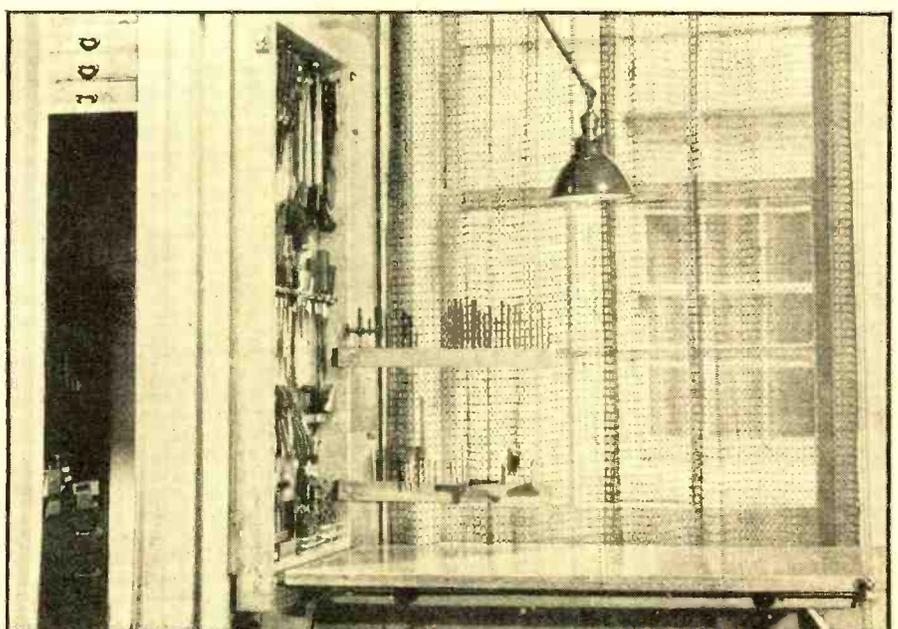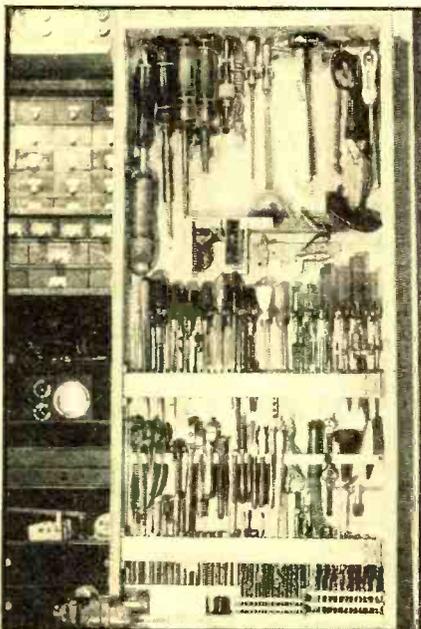

The
**RADIO
WORKSHOP**

Items of interest for beginners, ex-
perimenters and radio constructors.


Conducted by The Associate Editor

Kinks For Every Experimenter

The following hints are of use to all radio experimenters and set builders. The devices described are easily made and are time savers in all kinds of radio testing.

The first is a handy connecting lead of No. 18 stranded push-back wire with large spade type lugs at each end. For my use I made a half dozen leads of 6-inch length, and the same number of 12-inch length. The drawing for this kink is self-explanatory.

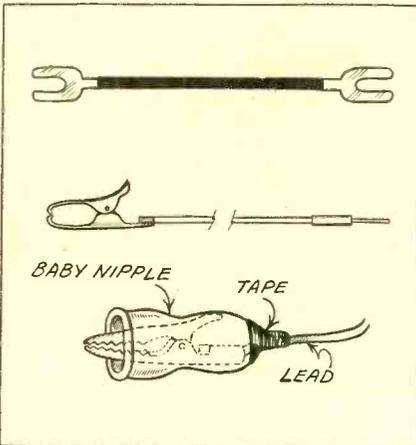The second device is also a connecting lead, but it makes use of a Muller or Morse clip and a phone tip. Number 18 stranded rubber and cotton-covered wire is used for



this lead. After the covering has been removed about 3/4 of an inch at each end of the lead, clean, twist, and tin the wires. Set the phone tip in a vise and fill with solder, then push the lead into the tip and allow to cool. The other end can be made fast to the clip by pushing the lead through the sleeve and hole at the end of the clip. For a neat and lasting job, it is important that you use electrician's rubber tape for binding the ends.


The third makes use of a baby's nipple and if you are a family man and have such things in the house, you can use discarded nipples to advantage for this idea. Cut a 3/4-inch hole at the tip and stretch over the clip, tape as shown, and you have an insulated clip, neat in appearance and safe to use for those "hot" connections.

RICHARD FEENEY,
New York City, N. Y.

**Antenna Kink for Motor
Car Radios**

The signal strength of an automobile set using any type of roof or car top antenna can be increased from 20 to 40 percent by

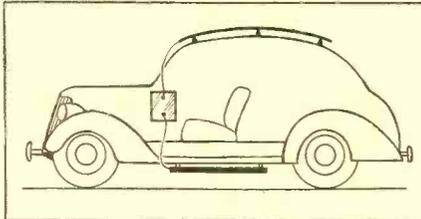using a counterpoise antenna as shown in the accompanying illustration. The counterpoise can be mounted under the car chassis or under the running board and for this purpose a standard under-car aerial is used




or an improvised antenna can be made from two or three continuous spans of No. 18 insulated wire fastened to any of the projecting bolts on the chassis at the front and rear of the car.

To make this item work, it is first necessary to perform a slight operation on the primary winding of the antenna coil. One end of this winding is connected to the aerial, while the other end, in most receivers, is connected to the ground end of the secondary winding thus completing the ground circuit. Now this end of the primary winding should be disconnected from the secondary and brought out to the counterpoise aerial under the car. Try this kink and you will be surprised at the increased pick-up.

Save Old Alarm Clocks

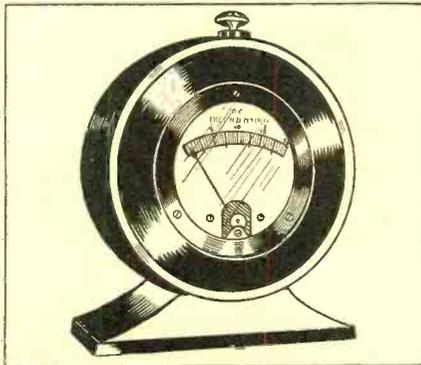This little kink uses the case of a broken alarm clock as a mounting for a meter. The alarm clock happened to have a pedes-



tal mounting and fortunately was of the larger size. The glass and works were removed from the clock and a piece of bakelite cut to the size of the glass and inserted in its place. A hole was cut in the middle of the bakelite disc and the meter mounted


in the usual way with three machine screws. The metal alarm clock case was then painted a dull black.

CHARLES FELSTEAD,
Los Angeles, Cal.

Saves Time

Fellow experimenters will agree with me, that there are some makes of metal tubes that require a good weather-eye to distinguish the type number. In some cases the number is merely stamped in the metal envelope and in others the white filler employed is inadequate for the purpose.

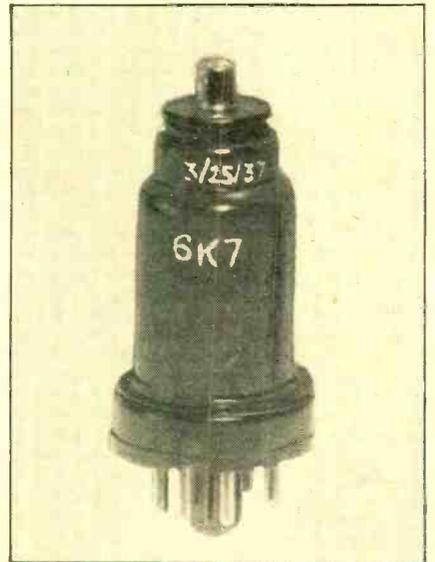Tubes of this sort I re-mark with china white as illustrated in the photo. You will find this idea of material assistance for quickly selecting different tubes for the requirements at hand. While you are at this job of marking, put the date on the collar of the tube, it can be the day the




tube went into service or the purchase date.

Before marking the tube, clean the metal with a little ammonia to take off the grease. After marking, coat with shellac or other fixative.

HERMAN GERTZ,
New York, N. Y.

**A Contact-Spring Adjusting
Tool**

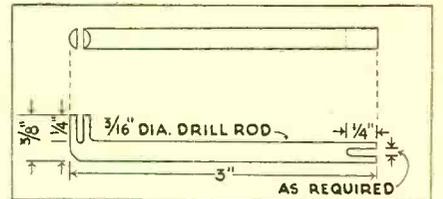This little tool is used for adjusting or tensioning the contact springs of head-set



jacks, radio switches, the spring rotor contact of variable condensers and similar apparatus. The ordinary pliers and tweezers are generally too unhandy for this work. The radio serviceman will find that several "spring benders" of the kind shown in the appended sketch will greatly expedite such adjustments.

The tool (at least two should be made) is made of a piece of 3/16-inch diameter steel rod about 3 1/2 inches long. One end of the rod is bent at a right angle about 3/8 inch from the end. Both ends of the tool are slotted to a depth of 1/4 inch by means of a hacksaw. The slots should be slightly wider than the thickness of the contact springs upon which the tool will be used. After the slots are cut, both ends of the tools should be hardened and tem-

Cash for Kinks


EVERY experimenter, from time to time, works out some simple idea or kink that could be profitably passed along to his fellow experimenters through the "Radio Workshop", a department which caters especially to the exchange of such ideas. Send your ideas to the Workshop Editor, and wherever possible include a simple but clear drawing or a photograph. All ideas published will be paid for at regular space-rates.

pered, but this is not absolutely essential. To bend or tension a spring, one of the tools is applied to the spring at the point where the latter is to be bent, with the spring held in the slot at one end of the tool. A second tool is placed upon the spring in like manner, close to the first. By holding one tool in one hand and manipulating the second tool with the other hand, the spring may be readily bent and tensioned as desired.

P. A. STARCK,
Sioux City, Iowa.

Rack for Radio Manuals

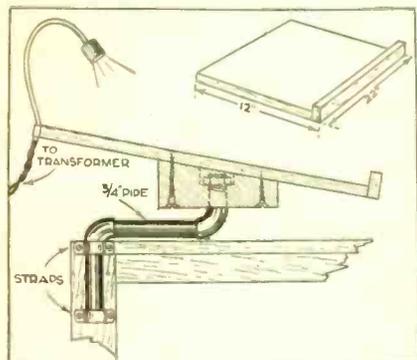It is the general experience of anyone connected with a service shop or laboratory, that after ten minutes work, the bench even though it be a large one, is covered with various parts, test equipment, tools



and whatnot and there is no place for the service manual or text book which one requires for the job at hand.

The accompanying drawing shows a book rack arrangement which I use and have found extremely helpful. It is no job to construct and mount this rack and the builder will find the drawing complete with all dimensions. For the book rest itself I use 3/4 inch pine and for its swivel support I employed 3/4 inch standard conduit. The most convenient place for mounting the rack is the front corner of the bench.

The light and bracket are made from an auto-fender guide. A coil shield from an old Readrite oscillator, came in handy as a reflector. A regular filament transformer operating from the 110 volt 60 cycle a.c. line, furnishes 6.3 volts for the dial lamp. Painting the inside of the coil shield with a flat white improves the reflection. The rack can be swung clear and away from the bench when it is not in use.

J. HARRY GERRISH,
Watertown, New York.

Simple Laboratory Output Meter

An easily constructed output meter with a very low frequency error can be made with a type 6H6 rectifier tube used in conjunction with either a 1-milliampere or a 200-microampere meter as shown in the accompanying drawing and illustration.



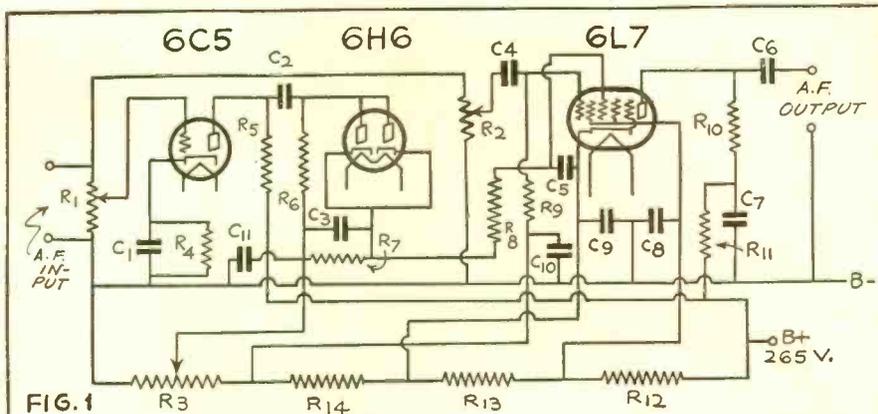
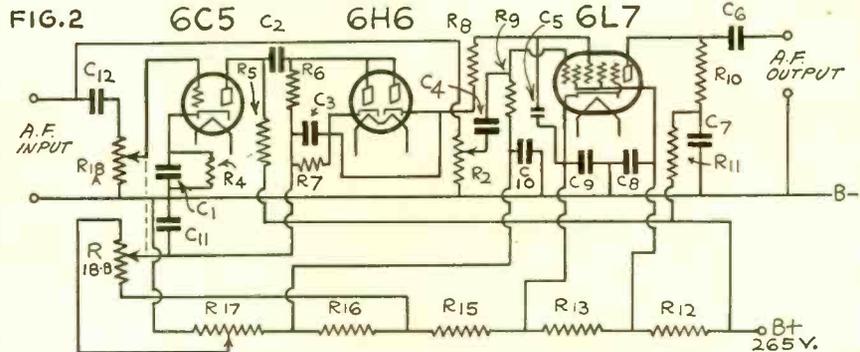


FIG. 1

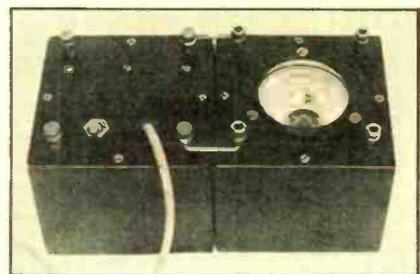

- | | | | |
|----------------------------|-------------------------------|--------------------|----------------------|
| R1 - 1 MEG. EXP. CONT. | R10 - 100,000 OHMS | C1 - .5 MFD. 200V. | C10 - 10 MFD. 25V. |
| R2 - 1 MEG. VOL. CONT. | R11 - 10,000 OHMS | C2 - .1 MFD. 400V. | C11 - 10 MFD. 25V. |
| R3 - 500 OHMS - BIAS CONT. | R12 - 15,000 OHMS - 5W. | C3 - .5 MFD. 200V. | C12 - .01 MFD. 200V. |
| R4 - 10,000 OHMS | R13 - 10,000 OHMS - 5W. | C4 - .1 MFD. 200V. | |
| R5 - 100,000 OHMS | R14 - 1,000 OHMS | C5 - .5 MFD. 200V. | |
| R6 - 100,000 OHMS | R15 - 300 OHMS | C6 - .1 MFD. 400V. | |
| R7 - 250,000 OHMS | R16 - 850 OHMS | C7 - .4 MFD. 300V. | |
| R8 - 500,000 OHMS | R17 - 1,000 OHMS - BIAS CONT. | C8 - .4 MFD. 300V. | |
| R9 - 1 MEG. | R18A 500,000 OHMS EXP. CONT. | C9 - 10 MFD. 50V. | |
| | R18B 5,000 OHMS | | |

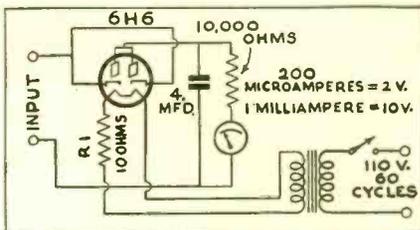The instrument has been tested up to 20,000 cycles with less than 5 percent error. To use it, simply connect the input leads across the voice coil. The 10-ohm resistor, R1, is utilized to reduce the filament voltage, thereby decreasing the contact (no signal) emission to less than 5 microamperes. An inexpensive transformer with a 6-volt wind-



ing is used to furnish the filament voltage. Referring to the illustration, the box at the left contains the filament transformer, tube, switch, resistors and condenser; the second box, as shown, houses the meter. The boxes are 4 inches square. The experimenter can set up this equipment to suit his individual convenience.

K. A. CONSTANT,
New York City, N. Y.

An Improved Volume Expander

The standard volume expander, Figure 1, operates by increasing the gain from a very low value to maximum, as the i.f. input increases. When the degree of expansion is reduced (by applying a smaller portion of the input voltage to the buffer tube), the available maximum gain is also reduced; at zero expansion the 6L7 third grid is at minus 13 volts and the gain is minimum. The ordinary expansion control acts, in other words, to reduce not only the expansion, but also the average gain. As the degree of expansion is changed, then, it becomes necessary to readjust the volume control in order to maintain a comparable output level.


This condition may be materially improved by using a dual potentiometer as compensated expansion control as in Figure 2. The first section (R18a) controls the buffer input as usual. The second section (R18b) makes the return of the 6L7 third grid less negative as expansion is reduced; at full expansion it is -13, as usual, and at zero expansion it is -3, providing full gain. This improvement, while allowing full control of expansion, maintains maximum gain about constant. Some readjustment of the volume control may still be necessary, but in general the effect is to separate the functions of volume control and expansion control, a highly desirable improvement. A dual 500,000-5000-ohm potentiometer is produced by the Yaxley Company. If a 1-megohm, 5000-ohm unit is obtainable, use it and omit C12.

EUGENE WILLIAMS,
New York City, N. Y.

Improved Condenser Tester

My neon condenser tester, as originally connected in Figure A, falsely indicated leak-

(Turn to page 63)

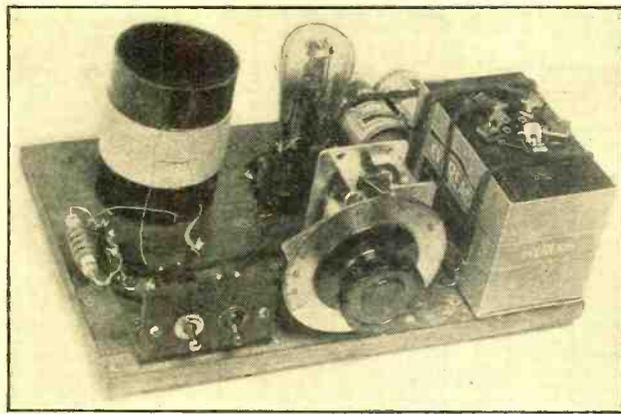

THE SIMPLE TEST OSCILLATOR

A 2-band oscillator which covers the range of 176 to 1550 kilocycles and offers the advantages of low cost, simplicity and wide utility.


EVERY experimenter and set constructor needs a test oscillator and some form of output meter or indicator. These devices are indispensable in accurately aligning both r.f. and i.f. circuits in receivers, and for calibrating receiver tuning dials, checking such calibrations, etc. The present article is therefore devoted to a description of the simplest possible instruments needed for this work. The next article of this series will be a constructional description of a superheterodyne receiver and those who construct that receiver will find the test equipment described this month invaluable in adjusting the receiver for maximum results.

A TEST oscillator is nothing but a miniature broadcasting station, which can be tuned to any frequency within the desired radio-frequency or intermediate-frequency ranges. The one presented here is of a simpler type which will serve to excellent advantage for alignment work, and for many other test purposes.

There are several possible oscillator circuits to choose from as the reader learned in the previous installment. The one selected here is the "series-feed Hartley" circuit. It has the advantage of requiring only one coil (for each range) and being easier to make oscillate all over the range.

Two Ranges Needed

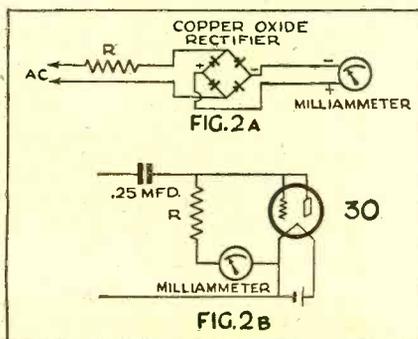The oscillator must cover the entire broadcast band and the intermediate frequency region (our super employs 456 kc.). It is not practical to cover these in a single range, therefore two ranges are provided, necessitating the use of two coils and a switch. This



circuit is illustrated in Figure 1. A careful study of the diagram should enable the reader to add more ranges if he desires by adding more coils and employing a two-gang multi-point switch.

The instrument was made battery operated for the sake of simplicity, easy portability and avoidance of difficulties due to the inter-connection between receiver and oscillator through the power line.

Modulation

In order that the oscillator shall produce an audible signal which is necessary for certain applications, it has to be modulated. The system of modulation employed here utilizes the grid-blocking method. This is nothing more than a grid leak and condenser combination wherein the condenser or leak or both are higher than normal. A large condenser receives a large charge during the periods when the grid becomes positive. This charge must leak off through the resistor. If the resistance is so high that the charge cannot leak off fast enough, the charge accumulates making the grid more and more negative until oscillation stops, allowing the charge to leak off. As soon as the condenser is sufficiently discharged, oscillations start again and the cycle repeats. The interruption occurs at audio-frequencies and the pitch of the note depends on the sizes of grid

leak and condenser. This type of modulation produces a somewhat raucous note, but it is satisfactory as an audible signal.



When it is desired to use the oscillator unmodulated, the grid condenser C2 should be changed to .00025 mfd. and the resistance R2, to 50000 ohms. If desired, a switch could be used to change from the one to the other.


Construction

The layout and wiring should be easy for followers of this series. Condenser C1 is a variable condenser, while the dial, together with the socket, tube and batteries, can be salvaged from the first single-tube set.

The broadcast band coil is home-made, wound on a 2½-inch bakelite form; 3 inches in length. It requires 60 turns of No. 30 d.c.c. magnet wire, with the tap at the 30th turn. Coil L2 is made from a Hammarlund r.f. choke, type CHX. This choke consists of five sections or "pies"; the tap is taken between the first and second pie. When making this tap, one must proceed carefully so as not to ruin the coil. The connecting wire between the two pies goes from the inside of one to the outside of the next. Unwind the wire, on the outside for several turns without cutting it. Then cut near the outside end, and unwind the short end several turns more so as to provide two leads each about 2 inches in length. Clean the ends by carefully scraping away both the covering and the enamel. The two ends can then be soldered together and to the center terminal of the terminal strip.

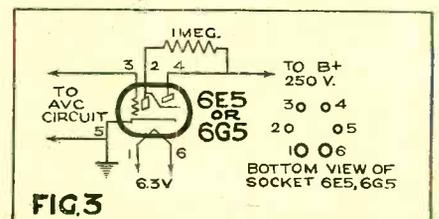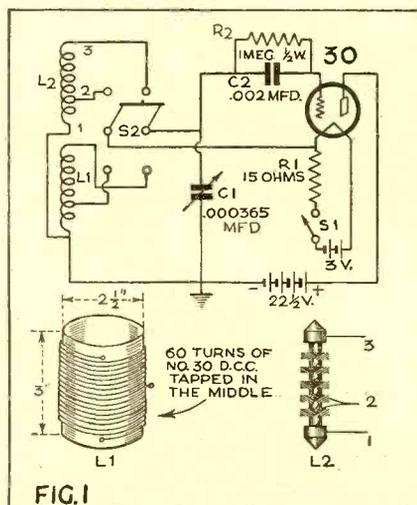The whole unit, batteries and all, has been mounted on a base-board, not employing a panel. A small strip of bakelite supports the switches and an indicator for the dial is made of a piece of wire fastened to C1. Those who have a condenser with a (Turn to page 61)



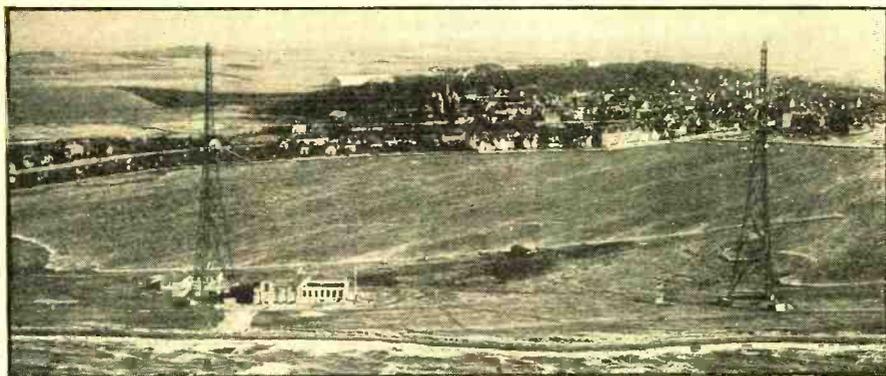

OSP, KALUNDBORG, DENMARK
An airplane view of this famous Danish station which operates on 240 kc. with 60 kw. power. The scenic beauty of the view leaves little to be desired.

THE DX CORNER

(For Broadcast Waves)

S. GORDON TAYLOR

A NOT-TOO-FAVORABLE DX season during which the noise level has remained high almost constantly, has drawn to a conclusion. Much of the DX which has been accomplished has been possible only because of the increased power used this season for the first time by many foreign and domestic stations.

Personal observations and an analysis of Observers' reports for the past three years show that DX has apparently been on a decline. This seems to bear out the theory of the sun-spot cycle and its effect on broadcast-band DX. Other factors are likewise involved, of course, but there can be little question that as the sun-spot area increases the long-distance transmission of signals decreases. Whether this is because noise increases or because signal strength decreases is unimportant because poor DX is the result in either case.

We are approaching the sun-spot peak of the present 11-year cycle. The actual peak is expected during 1938 and after that sun spots will gradually decrease, reaching a minimum in 1943. All of this appears discouraging for the DX'er as it indicates that the next two seasons are likely to be worse than the one just past. Then we will again start on the up-grade, probably reaching the peak of DX in 1943, with reception conditions approximating those of 1933.

It is not the purpose of this discussion to be unduly pessimistic, but on the other hand it is felt that DX'ers in general may as well face the facts. We can use better receivers, and transmitters are constantly increasing their power, but even these can only partially overcome the obstacles which nature is throwing in the path of the DX'er.

Lest we be accused of being a calamity-howler and a "tearer-downer" we hasten to suggest some possibilities of interest to those who have grown discouraged in their DX hobby.

Short-wave broadcast reception has held up beautifully during the years since 1934 when long-wave DX started slipping. Therefore, this suggests itself as one line of activity which the BCB DX'er may select. Another, and one which many listeners are finding of more absorbing interest than short-wave broadcast reception, is that of DX'ing on the amateur phone bands. In many respects the "ham" ranges are among the choicest for DX reception because the average amateur station employs power in the order of a few watts. On 75 meters, for instance, reception of a 25-watt "ham" phone from the opposite coast is a real bit of DX, and reception of such phones from across the Pacific is a feat which will test the perseverance and ability of any listener.

On the 20-meter amateur phone band real DX is again made possible by the low power in common use, although round-the-world reception is not so unusual on this band. The 10-meter band is perhaps of less interest to the DX'er because when this band is "open" there is almost no limit to the distance at which stations can be heard, even those with insignificant power.

The still lower waves extending from 10 meters to 5 meters constitute an entirely new field of activity for DX. Not so long ago these waves were considered to be good only for local transmission and reception but some of the "apex," high-fidelity stations in the U. S. have been authentically heard in Australia and New Zealand, and are commonly heard in Europe. British

VETERAN L.P.O.'s

Maynard J. Lonis of Hannibal, N. Y. (left) is no stranger to Trans-Pacific reception. He reported 13 such stations during the month of March. At the right is Herman E. Rebensdorf of Harvard, Ill., who likewise reports reception of TP's frequently, although lacking electric light lines he is forced to depend on battery power supply.

television transmissions on 6.5 meters have been picked up (and reports verified) in South Africa and U. S. amateur signals on 5 meters have been heard frequently in Europe and vice versa.

It is becoming more apparent that the DX'er who is going to obtain the maximum enjoyment from his hobby is the one who goes in for all-wave activity. During the daytime, in Summer, and during the period of the sun-spot cycle when broadcast-band DX is less attractive, then the short and ultra-short waves offer excellent possibilities for DX. Many veteran BB DX'ers who have felt that DX on the short waves was child's play have learned different during the past few months when they have really given it a fling, with the result that many such are now among the most rabid of the s.w. listeners.

AN ENGLISH DX'ER REPORTS


AN English listener once reported reception on his crystal set of an American broadcast band station. Naturally his claim was not universally believed. But when reception conditions are favorable, it is easily possible to hear such stations on a 2-tube receiver. The radio used by the average English DX'er has from 3 to 7 tubes, but it must be remembered that many of these tubes are of the compound types such as the double diode-triode, double diode-pentode, etc.

North American signals are strongest during November, December, and January, although good reception, depending upon conditions, is possible from September to May. Reception of sorts is sometimes obtained even in the summer months. Stations have been received as early as 9:30 p. m. (4:30 p. m., E. S. T.) and as late as 9 a. m. (4 a. m., E. S. T.) but the best listening period varies from 11:30 p. m. to 6 a. m. in mid-winter to 2:30 a. m. to 3:30 a. m. in mid-summer.

Among the United States stations
 (Turn to page 63)



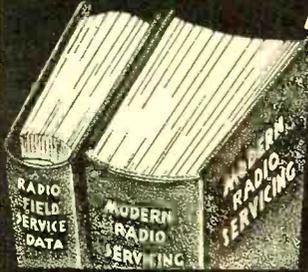They give you the **417** THINGS YOU NEED TO KNOW ABOUT



MODERN RADIO Service Work
1736 Pages 813 Illus.

These two **GHIRARDI** books explain clearly EVERYTHING about radio servicing—everything there is to know! **SUPPLEMENTS** supplied for the Data book several times a year keep it up to the minute. Essential equipment for your shop. Get these great books Now!

- **TEST INSTRUMENTS**—Complete explanations and descriptions of the latest commercial models of test instruments (with circuit diagrams). Construction data, etc.
- **SERVICING METHODS**—Every latest test and repair method clearly explained. Receiver analysis. Repairing individual components. Aligning sets (including latest Cathode-Ray Oscilloscope methods), AVC and QAVC circuits, etc.
- **SPECIAL SERVICING PROBLEMS**—in Auto Radio, All-Wave, High-Fidelity sets, etc., all explained.
- **FIELD DATA**—“Case Histories” of over 1,500 receivers, with trouble symptoms and remedies for each. I.F.’s for 5,424 superhets. Over 25 other charts and tables.

\$6 With Money-Back Guarantee

RADIO & TECHNICAL PUBL. CO.
45 Astor Place, New York, Dept. RN-77
 Each, and \$6 for both servicing books, including Jan. and June '37 Supplements to Data Book, postpaid. (Foreign \$6.50)
 Please send free Circular "CO".

Name.....
Address.....

Fill Out - Tear Off - and Mail!

TRIAD

INVITES THE TRADE
TO VISIT BOOTH NO. 102
NATIONAL TRADE SHOW
RADIO PARTS MANUFACTURERS
at STEVENS HOTEL, CHICAGO
June 10-13 Inc., 1937

TRIAD MANUFACTURING CO., Inc.
PAWTUCKET RHODE ISLAND

THE QUALITY NAME IN RADIO TUBES

QUALITY recommends

Condensers by **SOLAR**

WET... DRY
PAPER
MICA... TRIMMER



Please Write for Details

SOLAR MFG. CORP. 599-601 Broadway New York City



FIGURE 5
A "business card" on wheels, with a sales argument on both sides!

THE SERVICE BENCH

(Continued from page 12)

considerable value in routine testing. A slight over-drain usually indicates a short-circuited by-pass in a plate or screen circuit. If the needle swings quickly to full scale, this is practically always an indication of a short-circuited filter. Low wattage indicates an electrolytic that is low in filtering effect. All this takes only a few minutes and often gives a pretty good idea of where to look for trouble.

"Volts times amperes" do not give a.c. watts except in purely resistive circuits. The value of the volt-amperes must be multiplied by the power factor which, in the case of small transformers under full load, is about 90%. That is, the value of volts times amperes will run around 10% higher than the actual wattage, and allowance should be made for this apparent excess. Also, the power factor will vary with the load, and the load will change with different troubles—the lower the load the lower the power factor. Thus a drop in current will indicate a more than proportionately I² drop in power. Probably the wattmeter is the best arrangement, although as Mr. Olson points out, the ammeter-voltmeter layout has its advantages.


Stewart-Warner Model R-142-A

"This set was dead—plenty. The 110-volt power switch had failed, short-circuiting to the volume-control case and

grounding. Net result, one burned-out power transformer, two filter condensers and a bias resistor in the return lead. A 6X5 rectifier tube was not available, but an extra 5-volt winding on a new Stancor power transformer allowed the change to a 5Z4 with satisfactory results. This repair is obviously of a general nature, and applies to many receivers. However, the specific diagrams tell the general story and A and B of Figure 3 are the 'before-and-after' circuits respectively."—Louis E. Jones, Ace Radio Service, Ohley, West Va.

Dewald 506R

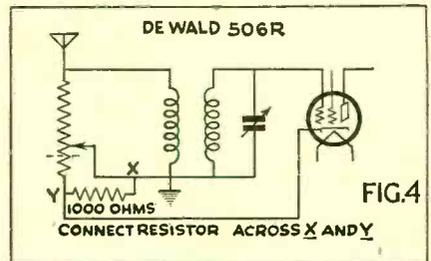
Vernon D. Hobbs, of Vern's Service Bench, West Lafayette, Ind., operating in Purdue University's home town, gets plenty of midgets! "This baby midget came in



with the usual complaint—hum and bad distortion. Replaced the complete filter block, although the double 5's were O.K. This chassis is too small for two blocks. This cleaned up the hum, but the distortion persisted. All voltages and the volume control checked correctly. I finally connected a 1000-ohm resistor between the cathode of the 6C6 and the chassis, as shown between Points X and Y in Figure 4. This job employs an antenna-bias, volume-control system, and the mutual conductance of the circuit is not decreased sufficiently when the volume is on 'low.' If a new control is to be used, be sure to replace with one having a minimum-bias control already included. This has an external adjustment and with a little cut-and-try it seems to work out well on all antenna-bias systems."

Selling Sound

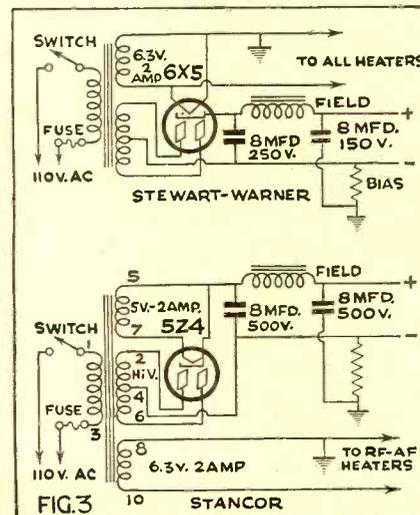The photo of Figure 5 is the reverse side of the standard-size business card handed out by the Ruddell Sound Systems, Seattle, Washington. The other side carries the (Turn to page 45)



**RCA ALL
THE WAY**

RCA Radio News

RCA Manufacturing Company, Inc. • Camden, New Jersey
A Service of the Radio Corporation of America

**EVERYTHING IN
RADIO-MICROPHONE
TO LOUDSPEAKER**

To the consumer, RCA means high quality performance at low cost... To the radio man, RCA means easier selling, higher profits

ENJOY NEW RADIO THRILL!

*Thousands Getting New Pleasure
from Radio that's RCA All The Way!*

The air is full of thrills! Every hour of every day finds colorful, exciting programs being broadcast for you to hear—to enjoy!


As fine as these programs are—it's up to you to get the thrill of radio that's RCA All the Way—perfect performance beginning with the RCA microphone in the studio and coming to you with equal perfection from your RCA Victor receiver. Only by owning an RCA Victor radio can you get this thrill.

They Cost as Little as \$20

You can enjoy radio that's RCA All the Way at low cost with one of RCA Victor's new 1937 models! They are now on display at your RCA Victor dealer's store. Designed for every purse they cost as little as \$20. Among the many models priced below \$100 are several with RCA Victor's Magic Brain, Magic Eye, Metal Tubes. Every chassis is housed in a beautiful cabinet—and there is a large variety of cabinet styles—one of which is sure to catch your eye. At slightly higher prices are the fine models which feature RCA Victor's latest triumph—the Magic Voice.

But visit your dealer. See and hear these superb radios. Take particular notice of their thrilling performance. Then match them against any other radios of equal price—and RCA will win you!

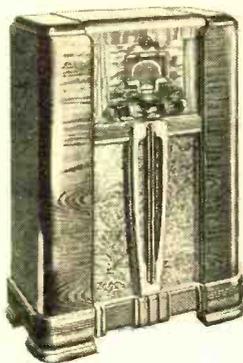RCA Victor Console Model 9K3... with Magic Voice, Magic Brain, Magic Eye, Metal Tubes, 530 to 22,000 kcs. Beam Power Amplification, Selector Dial, 9 tubes, \$134.95.



New Tube Manual!

The RC-13 Manual on RCA Radio Tubes gives service men complete information on all receiving tube types including Metal and G-Series tubes. Get your copy from your RCA tube distributor.

RCA Radiotron Check-up Restores Radio's Pep and Power

Radios, like anything else that's constantly in use, eventually tire and lose the efficiency which gave you outstanding performance when the set was new.

You can restore your radio's original pep and power—give it new life and “new set” tone by having your radio service man administer the cure-all of an RCA Radiotron check-up.

This check-up consists of 10 testing, cleaning and adjusting steps which cost you only \$1.50.

Get More Service Jobs— Push the Check-Up

If you're a service man you will discover, as hundreds of other men in your business have, that the RCA Radiotron Check-up Plan not only gives you additional service jobs but in addition, helps you sell parts, new sets and other appliances that you have for sale.

You will find the RCA check-up an easy service to sell. Because there's nothing unusual about check-ups in American life. People are accustomed to check-ups of all sorts. They know the value of check-ups. Therefore, a radio check-up is quite acceptable.

You get selling help, too, direct from RCA Radiotron. For full column advertisements are running in the Saturday Evening Post and Collier's every other week... newspaper ads are appearing in over 100 cities... the check-up is being featured with commercial announcements on a full hour Sunday radio program. And in every one of these advertising efforts RCA Radiotron is featuring you as the man to perform this check-up service. In addition, RCA Radiotron also offers you mailing pieces for your own use—mailing pieces that will include your own name and address and which will bring you directly to the attention of all your prospects. Secure yours today. Use them. Get behind this check-up service—and profit! You can get full details from your jobber, who will also be glad to tell you about the new RCA Radiotron Auto Radio Check-up.

This is P. A. Time— The Time to Cash In!


Warm weather and bright sunshine are here. And that means it's P.A. time—and the time for you to cash in on installations of public address systems.

Your prospects? There are many. This season of the year is ideal for outdoor installations such as in amusement parks, athletic fields, camps, resorts, swimming pools and “garden” night clubs.

The best way for you to get your share of this P.A. business is to offer prospects RCA equipment. Public address systems bearing the RCA trademark provide real quality. And that's only natural. For behind them are the years of experience RCA has gained as the world's leading maker of sound products.


RCA offers these portable P.A. models that will cover all your needs for the type of equipment. Both give you the sales advantage of the RCA name. All are literally packed with performance features that help make them easy to sell. All sell at modest cost—yet assure you good profits.

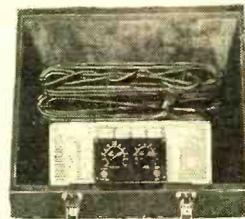Get after the P.A. market today. Get your share of the profits that are in it. Push the RCA public address systems shown here—and win many installation jobs! Write us for free details.



RCA Portable Sound System PG-98... provides volume for audiences up to 1600 persons. 12 watts. RCA Velocity Microphone. Two Electro Dynamic Speakers. Easily accessible controls. Comes complete with six RCA Radiotrons.

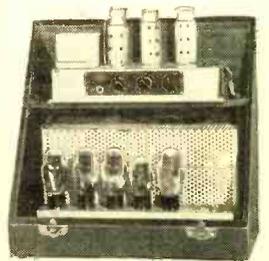RCA Portable Sound System PG-62-E... provides volume for audiences up to 3,000 persons. 20 watts. RCA Velocity Microphone with adjustable banquet stand. Two special Electro Dynamic Speakers. Provides for mixing voice with musical background. Comes complete with seven RCA Radiotrons.



In addition to these two systems shown above, RCA also offers another Portable Sound System, the PG-63-B—a 6-watt system providing volume for audiences up to 600 persons.

RADIO PHYSICS COURSE

ALFRED A. GHIRARDI

Lesson 63—Filters

IN designing a band-pass filter we usually have three things given: The impedance the filter is to work out of, or into, and the upper and lower cut-off frequencies. With this data, the capacitances and inductances are found by the following formulas:

$$C_1 = \frac{f_1 + f_2}{4\pi f_1 f_2 Z} \text{ (farads)}$$

$$C_2 = \frac{f_1 + f_2}{\pi f_2 (f_2 - f_1) Z} \text{ (farads)}$$

$$L_2 = \frac{f_1 + f_2}{4\pi f_1 f_2} \text{ (henries)}$$

C_1 and C_2 are the capacitances in farads, as indicated in the conventional band-pass filter shown in Figure 1, L_2 is the inductance of each coil in henries, f_2 is the higher cut-off frequency in cycles per sec-

110 kc. It is to be terminated at one end by a resistor of 50,000 ohms which is in the plate circuit of a 227 type vacuum tube having a plate impedance of 10,000 ohms; at the other end it is terminated by a variable grid leak which is adjusted to match the impedance of the filter.

Solution: Impedance R, of the parallel circuit feeding into the filter:

$$\frac{1}{R} = \frac{1}{50,000} + \frac{1}{10,000} \text{ or } R = 8350 \text{ ohms (approx.)}$$

$$C_3 = \frac{f_1 + f_2}{4\pi f_1 f_2 Z} = \frac{f_1 + f_2}{100,000 + 110,000} =$$

$$\frac{4\pi \times 100,000 \times 110,000 \times 8350}{.000182 \text{ microfarads}}$$

$$C_2 = \frac{f_1 + f_2}{\pi f_2 (f_2 - f_1) Z} =$$

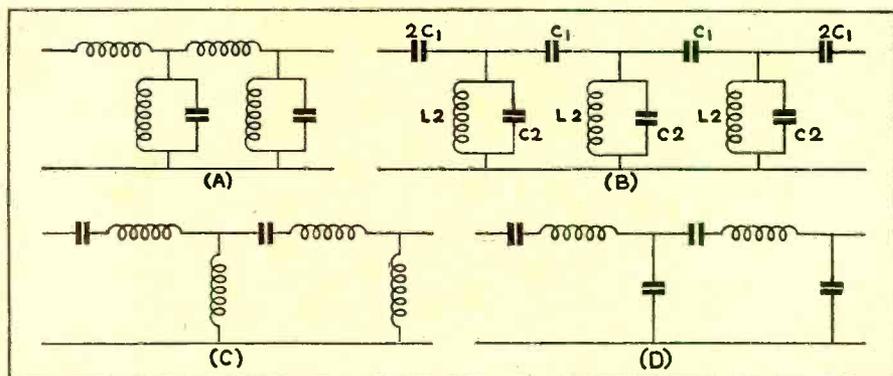


Figure 1. Conventional Band-Pass Filters

ond f_1 is the lower cut-off frequency, Z is the characteristic impedance of the filter. As with the other filters described, Z should be made as nearly equal to the impedance of the source and load as practical. In practice, the impedance selected is usually that of the line, for some frequency near the middle of the pass-band. The use of these formulas may be illustrated by the following example:

Example: It is desired to make a band-pass filter for a superheterodyne receiver; the filter is to pass a band 10 kc. wide and is to have its cut-off frequencies at 100 and

$$\frac{100,000}{3.14 \times 110,000 \times 10,000 \times 8350} = .003467 \text{ microfarads}$$

$$L_2 = \frac{f_1 + f_2}{4\pi f_1 f_2} = \frac{100,000 + 110,000}{4\pi \times 100,000 \times 110,000} = .0006 \text{ henries}$$

Note: In the above solutions C_1 and C_2 have been changed to mfd. by multiplying the answers given by the formulas by the conversion factor 1,000,000.

New Tubes

NEW YORK, N. Y.—Three new cathode-ray tuning indicator tubes have been introduced; these are the 6AB5, 6T5, and 6U5. The 6T5 is cathode-ray indicators of a new type; instead of a narrowing dark sector, the whole luminous ring becomes wider when a station is tuned in. This effect is obtained by a different arrangement of the electrodes. The 6T5 is designed for a plate supply of 250 volts and requires 22 volts on the grid for maximum illumination of the target. The 6U5 is similar to the 6G5 except for the dimensions of the bulb. The 6U5 is mounted in a T-9 bulb, which has an overall length of 4 3/16 inch and a maximum diameter of 1 3/16 inch.

The 6AB5 is a cathode-ray indicator tube somewhat similar to a 6U5 but for a maximum voltage supply of 135 volts. The requested grid bias for a shadow angle of 0° is 7.5 volts.

More G-Tubes


New York, N. Y.—Several new G-tubes with octal bases have been released by Sylvania. The 6C8G is a twin-triode tube, somewhat similar to the 79 but having individual cathodes for the two sections. The tube is recommended as a two stage amplifier or as phase-inverter. The 6U7G is a variable-mu pentode, similar to the 6D6 but supplied with an octal base. The 6V7G is an octal base tube, similar in characteristics to type 85.

"We USED CENTRALAB SINCE THE PIONEER DAYS"



—says
MR. FRANCIS D. WARDNER

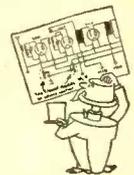of the WARDNER RADIO ELECTRIC CO. of St. Paul, Minn. Thanks, Mr. Wardner, and because we understand you are one of the outstanding service men in the Northwest, we are doubly proud of your testimonial of confidence in Centralab. Since radio's pioneer days CENTRALAB has been building an outstanding "quality" control.



Service men everywhere are following Mr. Wardner's plan by staying with CENTRALAB for ALL replacements.

Centralab

GET THE NEW VOLUME CONTROL GUIDE FROM YOUR JOBBER
DIVISION OF GLOBE UNION, INC.
MILWAUKEE, WIS.
British Centralab, Ltd. French Centralab Co., 118 Avenue Ledru-Rollin, Paris XI, France
Canterbury Rd., Kilburn London N. W. 6, England

HERE'S THE "KEY TO SUCCESSFUL SERVICING"

ADVANCED HOME STUDY TRAINING FOR "SERVICE MECHANICS" WHO WANT TO BECOME SERVICE SPECIALISTS

Actually it is not a case of WANTING to become a "Service Specialist"—it is a NECESSITY! New developments and changes in circuit designs make it urgent for you to keep pace with the progress of Radio. The serviceman who lacks the necessary training is eliminating himself from a better position and better pay.
START TRAINING NOW FOR THE FUTURE RSI training in Radio Service and Public Address work gives you thorough, basic knowledge of how complex circuits work and what goes into modern receivers. Write today and learn all the facts.

FREE BOOKLET!
You'll want to read every page of "The Key to Successful Servicing". Write at once.

RADIO SERVICE INSTITUTE
Subsidiary CREI
Dept. RN-7

3308 14th St., N. W., Wash., D. C.

SERVICEMEN!
THE SWING IS TO INTERCOMMUNICATORS

Privacy is essential. No installation complete without individual phones. Investigate at once.

Write Dept R-2

TRIMM
RADIO MFG. CO.
1770 W. Berteau Ave., Chicago, Ill.

The "Ham" Shack

(Continued from page 21)

higher than the simpler wood affairs usually used. However, their construction is considerably more difficult, and unless the amateur is a good carpenter, require the help of an expert.

Many stations have flagpoles or discarded telephone poles. These average in height to about 50 feet. In some sections of the country the telephone and power companies will sell second-hand poles at small cost. The problem is to erect them. Poles of this type require at least a 7-foot hole in the ground. To erect them it is necessary to use a gin pole about one-third the height of the mast, a block and tackle and to have the help of a number of persons. But once a mast of this type is erected, it is "up-to-stay!"

There are a few important rules to be followed in erecting any type of antenna mast. First the part that is to go into the ground must be painted with some material that will prevent rotting. Asphalt paint is excellent. Three or four coats should be applied. The mast itself should be fairly rigid; that is, it should not "bow" too much when one end is lifted. If it is too flexible it will be difficult to erect and probably will not stay there long, once it is up. A good grade of guy wire should be used. Nothing smaller than No. 10 B & S gauge galvanized wire should be used. No. 8 will last a long while and will hold a heavy load. Galvanized cable is not recommended because once it starts to rust each strand rusts simultaneously, and it will not take long before it will break through, whereas, solid wire will eventually rust on the surface, but will have a solid core for a long while after it starts rusting.

Also when a mast is being put up, as many persons as possible should be around to help—never less than four. Two should be assigned to hold the side guy wires to keep it straight. No one under any circumstances should stand under the mast unless he is pushing with a ladder, and then the ladder should be kept in a position so it will support the pole should the pusher weaken.

CALLS HEARD

By Private James P. Clarke, U. S. Army Air Corps, Headquarters detachment, Nichols Field, P. I., on 20 meter phone: W1DIC, W1GBE, W1GJX, W1IFD, W1JMP, W2ETI, W3ABN, W3APQ, W3AXT, W3DQ, W3EWW, W4TO, W5BEV, W6AH, W6BOY, W6CFI, W6DEP, W6EJC, W6IRX, W6ISH, W6ITH, W6KM, W6LR, W6LYP, W6MLG, W6OCH, W7ALZ, W7AMO, W7AOF, W7DMV, W7FU, W8CKZ, W9EVC, W9RUK, W9VXZ, VE1HE, VE5ES, W1AMP, W1ANQ, W1AXA, W1AXX, W1BFT, W1BE, W1BPP, W1CDX, W1CH, W1CUX, W1DMX, W1DP, W1DUK, W1EPA, W1ELR, W1FAU, W1FDN, W1FKS, W1FN, W1FUY, W1GCG, W1GJ, W1GJZ, W1HOU, W1HRJ, W1JCA, W1JCI, W1JL, W1JL, W1JSC, W1JSD, W1JX, W1JPW, W1JNL, W1JPP, W1MP, W1OX, W1TW, W1ZW, W2AWE, W2ADQ, W2ATR, W2BER, W2COL, W2CJM, W2CSI, W2DOE, W2FHI, W2GJF, W2FGG, W2FMR, W2GWF, W2IKZ, W2IRV, W2JVO, W2JPI, W2JPI, W2JVL, W2JKQ, W2OA, W2OZ, W2GOZ, W2FVL, W2BCK, W2CYS, W2BYK, W2HVQ, W2CPA, W2FEG, W2ELD, W2HJ, W2SE, W2JME, W2FAR, W2CDM, W2CTC, W2FDK, W2LA, W2HJ, W2HSB, W2DNB, W2HCM, W2OC, W2KBA, W2JOZ, W3FKK, W3GHD, W3ENX, W3FLH, W3DGS, W3FNB, W3GAP, W3BQL, W3KD, W3AVJ, W3BQP, W3DYU, W3FLD, W3EE, W4EG, W4DFO, W4TR, W5BUX, W5FFW, W5KC, W5QV, W5LP, W5CRS, W5EUL, W6ABB, W6AC, W6ACL, W6AFH, W6ATJ, W6BAM, W6BAW, W6BHP, W6BNU, W6CEM, W6CSI, W6DFO, W6DJV, W6FMF, W6FMH, W6FMY, W6FKZ, W6FZE, W6FZL, W6GCX, W6GK, W6GPP, W6HAS, W6HCF, W6ICW, W6JH, W6IOI, W6IPH, W6ITY, W6LYN, W6JAC, W6JRO, W6JGO, W6JSG, W6KBD, W6KQL, W6KRI, W6KRS, W6KU, W6KUT, W6KWB, W6KWC, W6LCP, W6LDJ, W6LEA, W6LER, W6LIV, W6LPB.

(Turn to page 45)

CUT RATE OUTLETS

... are places where
National Union Radio Tubes
AIN'T!

A nice comfortable feeling! We mean that secure, clean cut feeling a National Union Service Specialist has when he installs N. U. tubes. He knows he's gotten a fair price for premium quality merchandise. He's rendered a genuine service to a set owner and he's not going to be embarrassed by having his customer see N. U. tubes advertised in some gyp joint down the street as a loss leader.

No, Sir! National Union has kept the market clean for you. National Union tubes are not listed in cut price mail order catalogs. You won't find them in price slashing chain stores or department stores.

Your profit margin is reasonable when you sell at established list prices and

National Union has always felt that you are entitled to protection on it.

Remember these facts . . . the boys who are selling N. U. tubes are selling them with complete confidence . . . they're not running a chance of customer ill-will . . . because the set owner will never see N. U. tubes offered for sale with the heart cut out of the price!

This business of keeping the market clean for the Service Industry is only one of the reasons that N. U. is such an overwhelming favorite in the service field . . . Have you ever heard the entire National Union sales story? It will pay you handsome dividends to be tied up with N. U.

Find out why . . . send the coupon below . . . NOW.

MEET US at the NATIONAL RADIO PARTS TRADE SHOW
Booths 104-105—Hotel Stevens—CHICAGO—June 10, 11, 12, 13

CLIP! . . . MAIL!

NATIONAL UNION RADIO CORP. of N. Y.,
570 Lexington Avenue, New York, N. Y.

RN-737

Who is the nearest N. U. distributor? I want to find out what N. U. can do for me.

Name

Street

City




FREE New 1938 Standard Brands Radio Catalog

Listing more than 500 home electric sets, auto and boat sets, farm and camp sets. We carry only Nationally known makes, such as R.C.A.—PHILCO—G.E.—ZENITH—DELCO—BOSCH—MOTOROLA—EMERSON—DETROLA—FADA—GRUNOW and others. You save up to 50% from manufacturers' prices. Remember every set is brand new, guaranteed perfect and shipped in original sealed cartons. Write to nearest office, Dept. G-3.

Modells - Wholesale Radio Division
Since 1889
New York, N. Y. Chicago, Ill. Atlanta, Ga.
58 Cortlandt St. 156 W. Washington St. 75 Forsyth St.

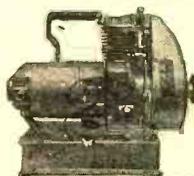Become Our Representative in your territory. We are Headquarters for Servicemen and agents.



110 VOLTS A. C.

Anytime! Anywhere! With **KATOLIGHT PLANTS**
350 watt 110 v. 60 cycle AC \$89.50
300 watt 33 volt DC plant 78.40
15 amp. 12 volt charger... 59.95
25 amp. 6 volt charger... 49.95
AC & DC Generators... Rotary
Converters 32 Volt 800 Watt
Wind Plant... \$141.00
Write For Details.

KATO ENGINEERING CO.,
Mankato, Minnesota, U. S. A.

RADIO ENGINEERING


RCA Institutes offer an intensive course of high standard embracing all phases of Radio. Practical training with modern equipment at New York and Chicago schools. Also specialized courses and Home Study Courses under "No obligation" plan. Catalog Dept. RN-37.

RCA INSTITUTES, Inc.

75 Varick St., New York 1154 Merchandise Mart, Chicago
Recognized Standard in Radio Instruction Since 1909

Aladdin
REG. U. S. PAT. OFF.

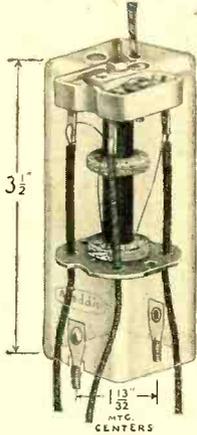ALADDIN quality and performance combined with economy of design



Type S Fixed-Coupling Mica Tuned i-f transformers.

Conventional design, tuned with compression type variable mica condensers, uses ALADDIN Polyiron giving high gain and selectivity—greater signal to noise ratio. Adjustments made from the top of shield.


Type	Gain	List Price
S 101 465 kc. converter	90	\$2.50
S 200 465 kc. diode	108.2	2.50

Aluminum shield 1 3/4" square x 3 1/2" high

SEND FOR 536 TECHNICAL BULLETIN WITH NEW SUPPLEMENT

ALADDIN RADIO INDUSTRIES, INC.

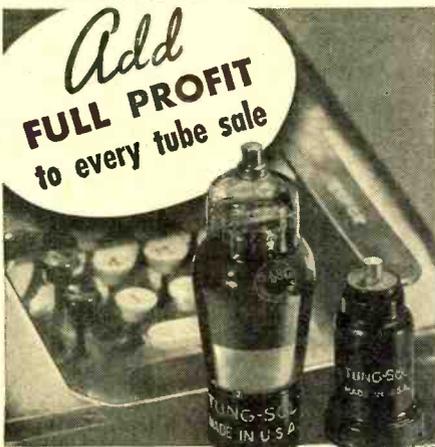466n West Superior Street Chicago, Illinois
Licensee of Johnson Laboratories, Inc.




Under the TUNG-SOL CONSIGNMENT PLAN there's no subtraction of investment expense, no repeated outlay to keep stock complete, no loss through lowered prices or obsolescence. A full profit shows up for every tube sold. And under this plan, 8000 dealers throughout the United States have joined the Tung-Sol partnership.

Desirable locations are still available for established, reputable dealers who can qualify. Write for name of your nearest Tung-Sol wholesaler.

TUNG-SOL

Flow radio Tubes

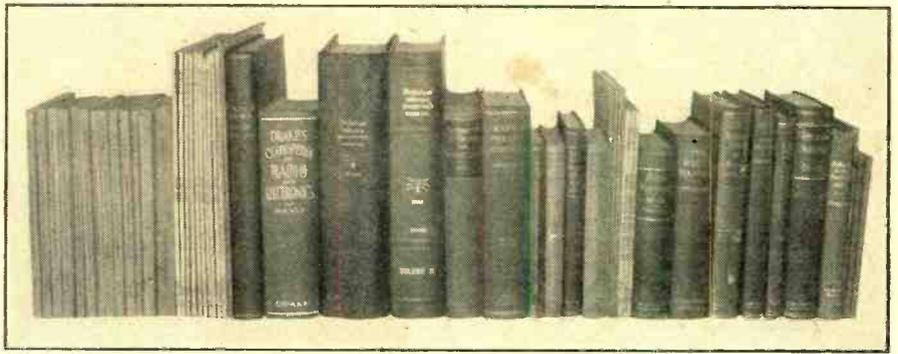TUNG-SOL LAMP WORKS, INC.
Radio Tube Division, NEWARK, N. J.



THE TECHNICAL REVIEW

CONDUCTED BY THE TECHNICAL EDITOR

Alternating Currents in Radio Receivers, by John F. Rider, published by John F. Rider, 1937. This is another one in the series of books under the general title "An Hour a Day with Rider." Many servicemen have only a very hazy conception of alternating currents, electron motion, sine waves, complex waves, and phase differences. Yet, modern receivers are employing new circuits which cannot very well be understood without a thorough knowledge of the above subjects. Therefore, this book should fill a definite need among servicemen. The author discusses in a non-mathematical manner, the alternating current phenomena so that the reader can visualize them. The chapter headings are: I, Introduction (how the electrons move, how fast, and what distance), II, Cycle and Frequency, III, Values of Alternating Current and Voltage, IV, Sine Waves, V, Phase relation in a. c. Circuits; VI, Complex waves; VII, Modulated and Unmodulated waves; VIII, Alternating Currents in Radio Receivers.

Two Hundred Meters and Down, by Clinton B. DeSoto, American Radio Relay League, 1936. A history of amateur activities from the beginning till the present and also a history of the development of radio in general. The amateurs take pride in recalling the role they played in pioneering and how many of the older amateurs made important discoveries and are now among the foremost radio authorities.

Part one of the book describes this early time of pioneering and gives an interesting story from Faraday to Marconi and beyond. The first regulations are described and how the amateurs were pushed below 200 meters. The second part recalls the period after the war, the sudden birth and boom of broadcasting, the spanning of the Atlantic by amateurs on waves below 200 meters. In the third part the later accomplishments are described; short waves, emergencies, expeditions.

Review of the Proceedings of the Institute of Radio Engineers for April, 1937

Characteristics of American Broadcast Receivers as Related to the Power and Frequency of Transmitters, by Arthur Van Dyck and Dudley E. Foster. The characteristics of American broadcast receivers now in use have been investigated to determine the permissible input and frequency separation for freedom from cross talk, heterodyne beats, and flutter effects. Seven types of interference are described separately in the data on the susceptibility of present receivers to each type.

Multiple Amplifier, by L. A. Kubetsky, The development, by the author, of ampli-

fying tubes utilizing secondary emission is discussed. The latest type is described as possessing the quality of small dimensions, high sensitivity (10-100 amperes per lumen), high over-all amplification (10⁶), high voltage output, minimization of noise, absence of microphonics.

Alternating-Current Resistance of Rectangular Conductors, by S. J. Haefner. New experimental data are presented for conductors having ratios of width to thickness of 1 to 1 to 2400 to 1 for frequencies up to eight kilocycles.

The Production of Rochelle Salt Piezoelectric Resonators Having A Pure Longitudinal Mode of Vibration, by Norman C. Stamford. The correct orientation of specimens cut from Rochelle salt crystals for use as piezoelectric resonators having a pure longitudinal mode of vibration is developed from Voigt's theory of piezoelectricity, and the frequency of resonance of these specimens is derived from the constants of the material. Practical details are given regarding the growing of the crystals and grinding of the specimens.

Review of Contemporary Literature

THE following are reviews of articles appearing in recent issues of technical magazines; the name of the magazine and its date are given after the title of each article. Copies of these articles are not included under the "Free Booklets"—they are available from your book-dealer or direct from the publishers. Addresses of publishers will be furnished on request.

Practical Feedback Amplifiers, by J. R. Day and J. B. Russell, Electronics, April 1937. Data and complete information on three practical amplifiers employing inverse feedback.

Electronics Engineers' Library, Electronics, April 1937. A list of books for students and engineers, covering mathematics, physics, Engineering, Communications and Electronics. A short note indicates how much previous education is needed to benefit from each book.

Distortion in Diode Detector Circuits, by A. W. Barker, Radio Engineering, April 1937. Some little known causes of distortion in diode circuits and what may be done about them.

Distortion measurements in the broadcasting station; The General Radio Experimenter, April 1937. Description of a distortion and noise meter for use at broadcast stations.

Factors Relating to faithful Reproduction, by C. M. Sennett; Proceedings of the Radio Club of America, March 1937. Technical description of automatic tone com-

pensating circuit and volume expander in a new RCA Victor phonograph.

Automobile Receiver Design, by J. C. Smith, RCA Review, April 1937. The author discusses the problems of vibrators, antennas and ignition interference suppression.

Horn Loudspeakers, by H. F. Olson, RCA Review, April 1937. A theoretical discussion of horns, their impedance and directional characteristics.

A new Form of Interference—External Cross-modulation, by D. E. Foster. Any corroded joints in antenna or ground system or in nearby metallic objects may act as rectifiers and cause cross-modulation external to the receiver.

Air-Wave Bending of Ultra-High-Frequency Waves, by Ross A. Hull, part one; QST, May 1937. An outline of the result of observations by the author during the last 2½ years.

The Use of Oil Condensers in Amateur Transmitters; Aerovox Research Worker, March 1937. Discussion of the design of high-voltage power supplies for amateur transmitters.

The Broadcasting and Postal Lottery Statutes, by Andrew G. Haley, Air Law Review, October 1936. A statement of the statute and an interpretation of its meaning; i. e. what is considered a lottery and what is not.

Free Bulletins New House Organ

The Clough-Brengle Company recently published the first copy of an interesting little publication called "Instrument Topics." This new folder should receive wide interest from all users of electronic instruments, as many of its pages will be devoted to outlining authentic methods of test procedure. This is to be published periodically and is free to servicemen, radio engineers, and others in the industry. In applying for the folder it will be necessary to make a separate request on your card or letterhead or show the firm with which you are employed and your official title. Send request to RADIO NEWS, 461 Eighth Avenue, New York City, N. Y.



For Servicemen and Dealers

The Triplett Electrical Instrument Company just brought out a new catalog listing their complete line of radio testing instruments and a folder with special information on the model 666 pocket volt-ohm-milliammeter. To obtain free copies of these, write to RADIO NEWS, 461 Eighth Avenue, New York City.

Special Catalog

The Aerovox Corporation recently published a new supplementary catalog on industrial capacitor replacements for use in electrical refrigerators, oil burners and other motor driven equipment. It is offered free to servicemen interested in any of these fields. Send your requests to RADIO NEWS, 461 Eighth Avenue, New York City.


Catalog of Theatre Sound-Equipment

The Wholesale Radio Service Company announce the new Lafayette catalog on

"Facsimile-Tone" theatre sound systems. It is an 8-page booklet containing information on powerful wide-range sound reproducing systems, sound heads, speakers and accessories. The book is offered free to sound engineers and prospective users of this equipment. Address requests to RADIO NEWS, 461 Eighth Avenue, New York City.

Latest Parts Catalog

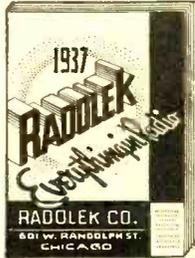"Everything in Radio" is an appropriate name for the new Radolek 1937 catalog. It is a 164-page book, listing home and motor car receivers, radio parts, tools, testing equipment, and many other items. Free copies are available to bona-fide servicemen and dealers. Send your request to RADIO NEWS, 461 Eighth Avenue, New York City, N. Y.



For Dealers and Servicemen

Here is the latest RCA catalog on test equipment, replacement parts, receivers, transmitters and accessories. It contains a convenient cross-indexed guide for all important replacement parts. Through the courtesy of this company, RADIO NEWS is able to offer this finely illustrated bulletin to bona fide servicemen and dealers. Send in your request to RADIO NEWS, 461 Eighth Avenue, New York City.

RADIO NEWS Booklet Offers Repeated

For the benefit of our readers, we are repeating below a list of valuable. FREE technical booklets and manufacturers' catalog offers, which were described in detail in the March, April, May and June, 1937, issues. The majority of these booklets are still available to all readers. Simply ask for them by their code designations and send your request to RADIO NEWS, 461 Eighth Avenue, New York, N. Y. The literature marked with an asterisk is available only to bonafide servicemen, dealers, and engineers. In applying for these folders it is necessary to send in your request on your card or letterhead. If you are an amateur give call letters. The list follows:


- Mh2—Test Equipment Catalog. Clough-Brengle Co.
- Mh3—Engineering Bulletin on 6L6 Tube, Ken-Rad Tube and Lamp Corp.*
- A11—36 page Catalog. Montgomery Ward & Co.
- A12—Parts Catalog. Hammarlund Mfg. Co.
- A13—McGraw-Hill Publishing Co., General catalog listing radio text books.
- My1—Service booklet. Readrite Meter Works.
- My2—Folder on small motor-driven "Handee" tool. Chicago Wheel & Mfg. Co.
- My3—Resistor catalog. International Resistance Co.
- My4—Instrument manual. Supreme Instruments Corp.
- My5—D. Van Nostrand Company's general book catalog.
- My6—Volume control guide. Central Radio Laboratory.
- My7—Latest parts catalog. Wholesale Radio Service Co.
- My8—Condenser catalog. Solar Manufacturing Company.
- Je1—Circulars on power equipment. Pioneer Gen-E-Motor Corp.
- Je2—Parts Catalog. Allied Radio Corp.
- Je3—Radio Receiver Catalog. Modell's.*
- Je4—Catalog on P. A. equipment. United Sound Engineering Co.*
- Je5—Tube Chart. Arcturus Radio Tube Co.*

J. W. Collins on W2XAD-W2XAF

SCHENECTADY, N. Y.—Mr. J. W. Collins, O. B. E., trade and tourist commissioner for New Zealand, will speak over W2XAD and W2XAF on June 19. Mr. Collins will speak from midnight to 12:30 a. m. EST and again at 6 o'clock the same morning. Each transmission is on both short wave stations.


TALKING ABOUT P. A. WE'RE WILDCATS ABOUT REPUTATION

THE important thing in these days of hectic competition in the P. A. field is your reputation for quality merchandise. LAFAYETTE, realizing this, places emphasis on high quality components in every P. A. system which it designs, manufactures and sells. In thus protecting its own reputation, LAFAYETTE doubly secures the reputation of the engineer who sells and installs LAFAYETTE P. A. Systems. Only by the use of quality merchandise can the sound engineer insure his prestige. When you install P. A. be sure it's LAFAYETTE.

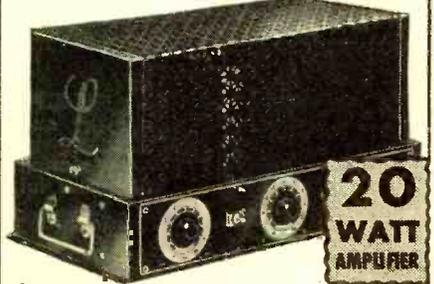

AGAIN LAFAYETTE engineers have produced a "year ahead" De Luxe amplifier! This system establishes a new "high" in fidelity of reproduction—a new "low" in price for a system of this type. "Highlights" include reverse feedback, automatic equalization, the new "Neo-Dial" (you can operate it in the dark), photo-cell input, and many other features. Model 131-A—Less tubes, and screen. **\$29.50** YOUR COST

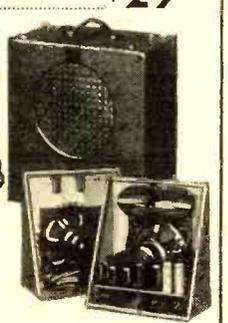20 WATT PORTABLE SYSTEM
Complete with Tubes, Mike, Slip-in Case
\$82.95 READY TO OPERATE



HERE'S a compact portable P. A. system that will speedily earn its cost in rentals. Amplifier can be removed from case, enabling speakers to be hung or placed anywhere—ample power for large assemblages. Model 860-P... your cost complete with tubes and LAFAYETTE velocity mike, ready to operate, **\$82.95** NOTHING ELSE TO BUY!

Send for copy of FREE Catalog listing a full range of sound systems, radios, auto sets and 1001 other bargains. You cannot afford to be without it. Use coupon.

WHOLESALE RADIO SERVICE CO. INC.
NEW YORK, N. Y. • CHICAGO, ILL. • ATLANTA, GA.
100 SIXTH AVENUE • 401 W. JACKSON BLVD. • 430 W. PEACHTREE ST. N. W.
BRONX, N. Y. • NEWARK, N. J. • JAMAICA, L. I.
342 E. FORDHAM RD. • 210 CENTRAL AVE. • 90-08 164TH STREET
SERVICES 8-2321

WHOLESALE RADIO SERVICE CO., Inc.
100 Sixth Avenue, New York, N. Y.

Rush FREE catalog No. 68-2G7
Rush FREE HAM catalog No. 66-2G7

Name.....
Address.....
City..... State.....

MIDWEST.
FACTORY TO YOU
SAVES 50%



18 TUBES For the Price of **10**

Why be content with an ordinary 6, 8, 10, or 12-tube set when you can buy an 18-tube deluxe Midwest for the same money... direct from the factory, at half the cost! Not a cut-price set, but a more powerful super-performing radio in a big, exquisitely designed cabinet.

Only **\$39.95** AND UP
(LESS TUBES)



ZIP and your station flashes in!

Your radio enjoyment is doubled with Dial-A-Matic Tuning* (optional), the amazing new Midwest feature that makes this radio practically tune itself. Zip! . . . Zip! . . . Zip! . . . stations come in instantly, automatically, perfectly . . . as fast as you can push buttons.

30 DAYS FREE TRIAL
You have a year to pay . . . terms as low as 10c a day . . . you secure privilege of 30 days free trial in your own home.

SEND FOR FREE 40-PAGE CATALOG
Dept. R-11, Midwest Radio Corp., Cin'ti, O.
MIDWEST RADIO CORPORATION
DEPT. R-11 CINCINNATI, OHIO
Send me your new FREE 40-page catalog.

Name.....
Address.....
Town..... State.....
User-Agents Make Easy Extra Money. Check Here for details.

ELECTRICITY

"LEARN BY DOING"
12 weeks training

Send Coupon for Details of My "Pay After Graduation Plan"

My Big Free Book tells you how we train you in 12 weeks—to start in the growing field of Electricity by actual shopwork on real electrical machinery—not by books or correspondence. Amazing plan enables many to get training first . . . then take 18 Months to pay in small monthly payments starting 5 Months from date you start school. Experience or advanced education not needed. Many Earn White Learning. Free lifetime employment service. Diesel Engines, Electric Refrigeration and Air Conditioning instruction included. MAIL COUPON for FREE BOOK and all Facts.

H. C. LEWIS, President, COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. B7-87, Chicago, Ill.
Send Big Free Book with facts on Coyne training and tell me about your "Pay-Tuition-After-Graduation" Plan.

NAME..... AGE.....
ADDRESS.....
CITY..... STATE.....

CODE—TAPES FOR EVERY NEED



For Example: Airways Tapes
You can easily learn or improve your Radio or Morse Code—typical messages are sent you by the INSTRUCTOGRAPH at any speed. Senior model with 10 tapes and Book of Instructions—\$20.25 (rented at low cost.) Junior model with 5 tapes and Book of Instructions—\$12.00 (Not rented). Complete oscillator equipment, less battery, \$9.20. Send for full information today to:

INSTRUCTOGRAPH CO., Dept. NR-7, 912 Lakeside Pl., Chicago, Ill. Representatives for Canada: Radio College of Canada, 863 Bay St., Toronto.

We Also Handle—
HALLICRAFTER and R.M.E. SHORT WAVE RECEIVERS—MICROPHONES—VIBROPLEXES—TAYLOR TUBES. Cash or Terms.



QRD? QRD? QRD?

CONDUCTED BY GY

NOW that we have been on the West Coast for a while, it seems that East Coast news and info is being neglected a bit. The small bones being thrown to our sleuth-hounds haven't enough juice within them fit to print. Shall we then use "Rumors" to satiate the appetite of our readers? This column does not advocate using the type of information that cannot be substantiated. Not that we fear libel suits, but primarily because we prefer printing the unadulterated truth, and nothing But.

RADIO at sea has grown to unthought of heights. To prove its merit, it is interesting to note a small item which appeared in one of the daily newspapers. Captain Kahlbetzer of the Red Star liner *Westernland* hove his ship alongside the *Manchester Producer*, 200 miles east of Newfoundland, in a tumultuous sea, for the purpose of transferring an injured seaman for an operation. It was part payment of an obligation contracted by Kahlbetzer when he almost lost his life in the Behring Straits some twenty-five years ago, but for the providential arrival of a Russian freighter. He now pays tribute to radio and radio operators for the part they are playing in this noble work. During his time there was no such thing.

Brother Karl Baarslag has again hit the front pages with the publication of his new book, "Coast Guard to the Rescue," which, as the name implies, portrays the important part played by the Coast Guard in rescue work. It is vividly written in the same style of his former saga of the sea, "SOS to the Rescue." "Coast Guard to the Rescue" should be included in the library of all seagoing radio men as completing the annals of "rescuing ships at sea." We know this book will meet with the same enthusiastic response and interest merited by Baarslag's former saga. Just another radiop who is stepping out and ahead.

Disaster at sea! Radio operators in times of emergency stick to their duty without thought of personal risk. Photo in our heading shows a view of a French film depicting operator of the fateful S.S. *Titanic* with the cabin awash. But, don't get excited—it's only a movie!

We now refer to a column some months back advising ops who have been out of the game for a few years and who wish to

try their hand at operating again, not to travel to any of the coastal ports in the hope of securing assignments. In the first place, the cost of travel is prohibitive and, in the second place, it is depressing to find a number of First Class men occupying the beach because of the lack of billets to go 'round. It is very discouraging to start out with hopes of obtaining an assignment, only to find so many others waiting ahead of you. It is best to write for assignments, stating qualifications, to the various hiring agencies such as Radiomarine, Mackay, etc. The addresses of these and others can be had on request.

We pull a paragraph from a letter written by one of the men who recently resigned from ARTA. "It is a far easier matter to clean house in a union than it is to build up a new union and tear the old one down, even if the task does look formidable. However, I will admit circumstances alter cases and that there may be times when a dual union is the only solution. For years the U. S. Post Office clerks could get nowhere with their boss-controlled union, but finally a handful started a National Federation of Post Office Clerks in Chicago, in 1917. They had a hard time for years. I helped to build Local 251 in Brooklyn, then considered a hopeless stronghold of the reactionary U.N.A.P.O.C. In fact, it was as much as one's job was worth to be a Federation man. But slowly and surely we tore out the old phony and the local is today one of the strongest locals in the N.F.P.O.C. which is a power in the A.F.L. The old U.N.A.P.O.C. consists of a handful of old diehards. In this case dual unionism did work and was the only solution, although for years it was hampered by the old outfit at Washington in obtaining better wages and improved working conditions."

It seems the placid Pacific has been the scene of some of our most recent ship disasters, caused by fire and storm. The U.S. Navy strutted its stuff in a big way when the Light Cruiser Louisville went to the aid of the stricken fire-ridden British *M.S. Silverlarch*, 500 miles off Honolulu. The eight passengers were rescued and, the fire being confined to a few of the holds, the *Silverlarch* was escorted to port, where the fire was extinguished with live steam. Radio relayed the dread SOS transmitted by the *S.S. Volunteer*, via the *President Harrison*, to the *Fresno City*, which battled heavy seas to reach the wallowing freighter off the Japanese coast. The *Volunteer* was reported "out of control and water coming in too fast for the pumps."

Add disasters: The Navy came to the rescue again with the aid of an injured engineer off the tunafisher *Cabrillo* by the *U.S.S. Omaha* off the coast of South America. She rushed him to a Panamanian hospital for an operation. . . . The *S.S. Fijian* had a gasoline explosion aboard and part of the crew left the ship. No message was transmitted about their plight except for a request to ships in their vicinity to stand by. They got the first blaze under control shortly thereafter and the crew returned. Then a new radio message reported fire, out of control and sinking. The crew was saved by the timely arrival of the N.Y.K. steamer *Shinko Maru*. . . . The *President Coolidge*, bound for the Orient out of San Francisco, collided terrifically with the incoming freighter *Frank H. Buck* in the Golden Gate Channel, in a pea-soup fog that would have made London blush with shame. The *Buck* was badly damaged but its entire crew was picked up by the *Coolidge*, which was able to proceed on her way. So, in spite of its name, *Pacific*, all is not always quiet on the Western Front.

And so, brethren of the glass wrist, we come to the end of another chapter in the affairs of radiops and ships at sea and, although dissension is flying about, new methods of procedure and operation continually being invented to harass and dis-gruntle us, there is still humor in the sun shining through the clouds. There is more shipping, better wages and working conditions are gradually improving. So with hopes for continued betterment, cheerio, ge . . . 73 . . . GY.

The "Ham" Shack

(Continued from page 41)

W6LWH, W6LYM, W6MEK, W6MFM, W6MJJ, W6MNT, W6MUB, W6MVO, W6MZY, W6NDB, W6NHA, W6NHC, W6NIQ, W6NSW, W6ODD, W6ZAA, W6AL, W6AON, W6BYR, W6CNW, W6IJA, W6KLB, W6AIN, W6ASV, W6AYZ, W6BKC, W6BNI, W6RVX, W6CD, W6EXO, W6EXA, W6EMV, W6GRE, W6GPN, W6HLH, W6IZU, W6JOH, W6KYO, W6LEV, W6LRH, W6NCM, W6NKZ, W6NNR, W6OE, W6QL, W6TI, W6TT, W6UD, W6VB, W7AHS, W7AVR, W7AVV, W7AWL, W7AYO, W7BNE, W7BRT, W7BTR, W7BTZ, W7BVI, W7CFJ, W6CRD, W7DDU, W7DSZ, W7EGE, W7EHL, W7EHT, W7EK, W7EKA, W7FOR, W7ERA, W7ETN, W7EUV, W7FCD, W7FED, W7FOO, W7FPY, W7FWD, W7GP, W7MB, W7OC, W7VQ, W7WL, W7DZL, W7BTG, W7BD, W7ANZ, W7AYJ, W7AMX, W7DGY, W7FME, W7FTJ, W8AKC, W8ANB, W8APB, W8AU, W8AKB, W8APD, W8AZG, W8BWC, W8BTI, W8BQJ, W8CRA, W8CTE, W8CNX, W8CJI, W8CGL, W8DVA, W8DFH, W8DLD, W8DNE, W8DNI, W8DPS, W8DCE, W8DRS, W8EMV, W8ERZ, W8EUV, W8ENL, W8FOB, W8FGX, W8FMH, W8HJN, W8HII, W8IKR, W8JPB, W8JMP, W8KOL, W8KVN, W8KWI, W8KKR, W8LDR, W8LJ, W8LZF, W8NBI, W8NNT, W8OOF, W8OIZ, W8OMA, W8OAW, W8PNE, W8PZB, W8PKE, W8PZF, W8PAJ, W8PVO, W8YA, W8ZY, W9APY, W9ALV, W9FFJ, W9BUL, W9PGS, W9TB, W9UCJ, W9UMA, W9TII, W9RKN, W9TPI, W9DIJ, W9KCN, W9UIQ, W9VITW, W9ADN,

W9LKZ, W9EAG, W9KOV, W9DNP, W9RUP, W9FS, W9VXV, W9WEL, W9IQZ, W9LW, W9PTV.

On 40 meter C. W. W5EXR, W6ALQ, W6ANQ, W6BVC, W6HXU, W6CUZ, W6DH, W6EUE, W6FMD, W6ITY, W6IUZ, W6LPZ, W6MFF, W6MIGZ, W6MNA, W6MNI, W6MPK, W6MRP, W6NCI, W6BSV, W6BTM, W6KPY, W6KRI, W6LJE, W6NDM, W6NSL, W7AIB, W7FNO, W7FVJ, W7KZ, W7CYQ, W9EBU, W9WUW.

By Rodney Newkirk, 1517 Fargo Avenue, Chicago, Ill., on 20-meter phone: CO7HF, CO2KC, CO2WZ, CO2EG, CO2OK, CO2ON, CO2MH, CO2ON, CO2OO, CO2KL, CO8YB, CO8OG, CO8AE, CO2WV, CO2HC, CO2KY, CO2NF, XE2AH, XE1AX, XE2W, XE2N, VK2JU, LU2BJ, LU2CA, LU1QA, VP2BC, VP6FO, VP6YB, VP9R, VP9G, VP3BG, VP7NA, CPIAA, PY8AD, K5AA, CE3DW, HK1ABM, HK1GK, HK1BM, HK3JA, HK3RC, HK4EA, HK5OBC, TI2IR, TI2DC, TI2RC, TI2EA, HI3X, HI7G, HI7P, HC1JW, HC1JB, SU1CH, F8KW, G2XV, G5IO, G5ML, G5NI, G5ZG, G6LK, HH2B, K6JLV, K6NTV, VO1G, VO1I, VO1P, VO2N, VO2Z, YN1HS, OA4AB, OA4AG, OA4AK, K4TG, YV5AA, YV5AZ, YV5AP, YV5AN, YV5ABE, YV5AE, YV3AE, YV3AD.

The Service Bench

(Continued from page 38)

sales message of—"Sales, Rentals, Service, Sound Cars, Office Call Systems, Laboratory Measurements." Larry Ruddell, proprietor, writes us: "The sound projector on the roof of the car may be of interest to RADIO NEWS readers. It can be raised and lowered, and pointed in any direction from within the car. It is outlined in green neon tubing operated from the car's battery through a revamped Ford spark coil. A built-in metal shutter protects the speaker cone from the elements. Together with a crystal pick-up, flat characteristic amplifiers built and measured in our laboratory, and adjustable high and low-frequency compensation, it affords reproduction not customarily associated with mobile installations. Overall sound-pressure measurements, from crystal pick-up through the speaker are excellent to past 7000 cycles, barring a few minor speaker peaks.

"A 12-volt dynamotor supplies 400 volts plate power to either of two 30-watt resistance-coupled amplifiers, which also contain a.c. power packs. A 350-watt, 110-volt a.c. fan-belt generator is employed as a stand-by power supply. Grandstand crowds of 4000 people have been covered easily without setting up any additional speakers. The truck is painted light green, with darker green fenders and molding."

Service Sales Promotion

Not exactly a pretty ad, but certainly an effective one, is that illustrated in Figure 6. A toothsome bit, one might say, and

GRIND Over This One!.....



Why does Your RADIO Resemble False Teeth?

Both have to be working right for proper digestion (of "prob" and your favorite programs)

Rattling and clicking in both cases cause great discomfort, and

In both cases these troubles can be remedied by proficient attention.

MASTICATE THE ABOVE THOROUGHLY AND SNAP AT THE CHANCE TO HAVE YOUR RADIO SERVICED BY

R. A. WHITE

TAKE YOUR TEETH SOMEWHERE ELSE !!

bound to attract attention. Our only criticism is that the word RADIO should be in larger type so that the advertisement is not taken for what it isn't—a dental ad. (Turn to page 62)



Profits from Those Tough Ones

You can't give your customers their money's worth and make profits from those "hard-to-fix" radio repair jobs without good equipment and knowledge of modern methods.

Competent authorities estimate 34,000,000 radio sets will be in use during this summer.

Be prepared to get your share of the profits from servicing these receivers by using the BEST equipment available -- C-B instruments.



MODEL 88 Vacuum-Tube Voltmeter

Invaluable for automatic frequency control adjustments, gain and impedance measurements, checking oscillator stages, amplifier performance, and other difficult measuring problems. MODEL 88 Vacuum-Tube Voltmeter, complete \$45.50

Use the C-B Easy Payment Plan—only \$5.50 down and ten monthly payments of \$4.57.

Free

Write for our new technical bulletin



telling all about the Vacuum-Tube Voltmeter and what it does.

Mail Coupon Now

Please send additional information on the MODEL 88 Vacuum-Tube Voltmeter.

Name


Address

City State

The CLOUGH-BREngle CO.

2813 W. 19th St., Chicago, Ill.

DEPENDABLE ECONOMICAL MODERN

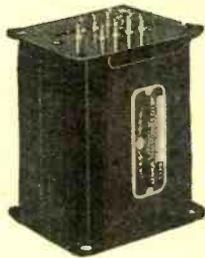

KEN-O-TAP

THE PRACTICAL SOLUTION TO
THE MODULATION PROBLEM

KEN-O-DRIVE

THE MODERN ANSWER TO
CRITICAL DRIVER OPERATION

KEN-O-DYNE

THE PRECISION METHOD OF
MATCHING OUTPUT TUBES TO
SPEAKERS

KEN-O-LINE


THE EFFICIENT COUPLING DE-
VICE FROM UNIVERSAL LINE

Ask your dealer for a free copy of our revised 16 page T line catalog. Contains a large selection of modern audio circuits ranging in power output from four to 120 watts. These circuits feature Beam Power Tubes, Inverse Feed-Back and Cathode Drivers which provide the ultimate in audio design.

KENYON TRANSFORMER CO., INC.
840 Barry Street, New York, N. Y.
Export Department: 25 Warren St., New York, N. Y.
Cable Address: Simonrice, N. Y.



VITREOUS
ENAMEL
RESISTORS

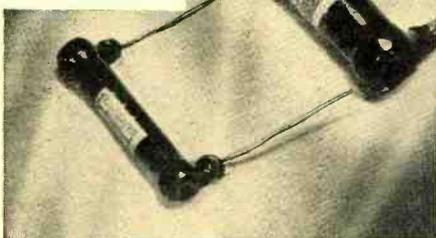

for all

REPLACEMENT REQUIREMENTS

Here's a longer lasting resistor—carefully wound by UTAH, so you know it's right. The entire unit is porcelain covered—right down to the long leads. All sizes from 10 watt to 200 watt are available from stock. Values to cover all requirements.


UTAH has a complete line of variable and fixed resistances every serviceman should find out about. Write Dept. RN-7.

UTAH RADIO PRODUCTS CO.
CHICAGO, U. S. A.

TORONTO
ONTARIO, CANADA

BUENOS AIRES
(UCOA RADIO PRODUCTS CO.)

"15 YEARS OF LEADERSHIP"

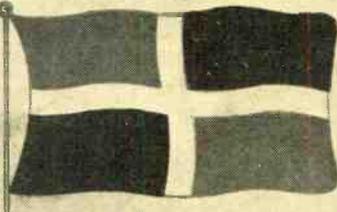

RADIODIFUSORA
"LA VOZ DEL YAQUE"
P. O. Box 423 Teléfono 423
SANTIAGO DE LOS CABALLEROS
REPUBLICA DOMINICANA
W. I.

Potencia 50 Watts Frecuencia 6185Kc.
Power Frequency

En el aire 12 a 2 p. m. 8 a 10 p. m. todos los días
On the air Every day

Local time. 20 minutes in advance E. S. T.

Esta Estación ha sido reportada desde toda América, Europa, La India y desde el lejano oriente Japon.
We have report from all America, Europe, India and Japan.

H-1-A

The DX Corner (Short Waves)

(Continued from page 32)

kc., (from ann.), (Alfred, Shamleffer, Atherton), Saturday 7-8:20 p.m., (Fallon, Herzog, Gallagher, Kentzel).

HBP, Geneva, Switzerland, 7797 kc., (Jaime), Saturday 5:30-6 p.m., (from ann.), (Alfred, Shamleffer, De Ment, Sprague, Kemp, Doyle, Ralat), Address: 12 Quai de la Poste, Geneva.

HBL, Geneva, Switzerland, 9595 kc., and 9345 kc., Saturday 5:30-6 p.m., (Alfred, De Ment, Cartin, Weiss, Kemp), Address: same as HBP.

HBQ, Geneva, Switzerland, 6675 kc., (from ann.), (Alfred).

HBU, Geneva, Switzerland, 14,535 kc., (Sprague).

Africa

EAJ, Tenerife, Canary Islands, 28.9 meters, 8:06-8:15 p.m., (Liljegren).

EA8AK, Tenerife, Canary Islands, 7,140 kc., 9:30 p.m. (Betances).

CR7BH, CR7AA, (6137kc.), CR7BA, Lourenço Marques, Mozambique, Africa, 11,718 kc, 9:30-11 a.m., Herzog, Craston, Sporn,) Weekdays 6:45-7:30 a.m., 10:30 a.m.-12:30 p.m., 1:30-5 p.m., Sunday 12-1 p.m., 4-5 p.m., (Beckemeyer, Partner, Sakely), 11,720 kc., (Howald, Beck, Kernan, Hamilton, Weiss, Gallagher).

EAJ43, Santa Cruz de Tenerife, Canary Islands, 10,360 kc., 28.90 meters, 4 kw., from 3 veris (Geneve, Shamleffer, Kernan, Ralat, Gallagher), Schedule 19:15-21 GMT and 23-2GMT wants reports, EA8AB not working letter from station to Editor). Slogan "Radio Club de Tenerife" Address, P. O. Box 225.

CR6AA, Lobito, Angola, 9,660 kc., 3:45-5:30 p.m. (Herzog).

FIU, Tananarive, Madagascar, 31.2 meters, daily 10-10:45 a.m. (Westman).

OPM, Leopoldville, Belgian Congo, 10,140 kc., daily 7:10 a.m. (Craston).

EHZ, Tenerife, Canary Islands, Africa, 10,370 kc., 7:20 and 8:20 p.m. (Kernan), Poste Bizertin, Bizerte, Tunisia, 6,160 kc., 5-7 p.m. without call letters, (Beckemeyer, Craston).

IUC, Addis Ababa, Ethiopia, 11,950 kc., 11:36 p.m. (Chambers).

SUZ, Cairo, Egypt, 13,830 kc., 2:55 a.m., (Chambers), 14,001 kc., Sunday

LA VOS DEL YAQUE

Verification card of H11A sent in for picturization by Observer Sahlbach. Another good one to try for.

5:30 p.m. (Murray, Kemp).

Algiers, Algeria, 24,75 meters, daily 4 p.m.-1 a.m. (Hedgeland).

VQ7LO, Nairobi, Kenya, 6,080 kc., Sunday 11 a.m.-2 p.m., Saturday 11 a.m.-3 p.m., (Hare), Monday through Saturday, 6-6:30 a.m. (from veri) (Stevens).

YBG, Medan, Sumatra, 10,430 kc., (Craston).

EA9AH, Tetuan, Spanish Morocco, 7,020 kc., 14,030 kc., (Geneve, Herzog, Craston Betances, Kentzel) Address: P. O. Box 124.

ZTJ, Johannesburg, South Africa, 6,097 kc., Wednesday, 5 p.m. (Weiss) heard daily 11:45 p.m., 1:30 a.m., 3:15-7 p.m., 11 a.m.-1:30 p.m., 12-5:15 p.m.—News bulletins and dance music (Sigundson).

Radio Tunis, Tunis, Tunisia, 7,265 kc., 7:30 p.m. Interval signal is one stroke of gong, 8:20-9 a.m. and 4-5 p.m. (Bower).

Asia

JZK, Nazaki, Japan, 15,160 kc., signed 10 p.m., (Howald), Monday and Thursday, 4-5 p.m., (Doyle)

JZG, Nazaki, Japan, 6350 kc., 7 a.m., (Gallagher).

JVT, Nazaki, Japan, 6750 kc., 4:10-7:40 a.m., (Doyle)

JVF, Nazaki, Japan, 15,620 kc., daily 6-7 p.m., (Doyle).

JVJ, Nazaki, Japan, 11,660 kc., 6-7 p.m., (Pylute).

JZI, Nazaki, Japan, 11,800 kc., daily 9-10 a.m., (Weissal), daily 12-1 a.m., (Howald), desires reports, (Markuson), daily 2:30-3:30 p.m., (Piorko, Westman, Hedgeland), daily 4-5 p.m., (Hartzell, Dodge, Emerson, Partner, Black, Hare, Gallagher, Keemp, Doyle, Sakely, Kashimoto, Pylute), chimes used.

JVP, Nazaki, Japan, 7510 kc., Sunday 12:30 p.m., (Hiljegren), daily 4-5 p.m., (from veri) (Herzog, Dressler, Fallon, Sakely), daily 2:30-8:30 p.m., (Hamilton).

JVM, Nazaki, Japan, 10,740 kc., daily 4 a.m., (Alfred), daily 2:30-3:30 p.m., (Piorko, Hedgeland), 4-5 p.m., (from veri), (Herzog, Dressler, Ryan, Hare, Randle, Fallon, Sakely, Kashimoto), chimes used.

JVD, Nazaki, Japan, 15,860 kc., all hours, (Gallagher), irregular, (Doyle)

JVU, Nazaki, Japan, 13,370 kc., 9 a.m., (Gallagher).

JVE, Nazaki, Japan, 15,720 kc., 11 p.m., (Gallagher), 15,660 kc., 3:35 a.m., (Chambers), 9-10 p.m., (Doyle)

JIB, Tyureki, Formosa, 10,530 kc., 2 and 10 a.m., (Gallagher, Markuson).

JVH, Nazaki, Japan, 14,600 kc., 6 p.m., (Gallagher), 5-6 p.m., 9-10 p.m., (Howald), 14,640 kc., replaces JVM at 4 a.m. and on. (Alfred, Herzog, Dressler), 12-1 a.m., (Pylate, Staley, Fallon, Sakely)

JVN, Nazaki, Japan, 10,660 kc., around mid-

night, (Gallagher, Hiljegren), daily 4 a.m., (Alfred), daily 2-8 a.m., (Munz), daily 4-5 a.m., (Hartzell, Herzog, Dressler, Dodge, Partner, Black, Howald, Hare, Kemp, Fallon, Sakely, Kashimoto).

TDE, Shinkyo, Manchukuo, Asia, 10,065 kc., daily 1-2 a.m., (from veri.), (Sporn), 1-7 a.m., (Craston).

JZI, Nazaki, Japan, 9530 kc., 9 a.m., (Gallagher), daily 9-10 a.m., (Weikal, Howald), 2:30-3:30 p.m., (McCartin, Westman, Dressier, Partner, Black, Hare, Herzog, Kashimoto), daily 2:30-3:30 p.m., (Hamilton).

XGN, Shanghai, China, 17,640 kc., 6 p.m., (Gallagher).

XGW, Shanghai, China, 10,420 kc., 10 a.m., (Gallagher).

XGOX, Nanking, China, 6820 kc., 10 a.m., (Gallagher), 6848 kc., (Weisz), 5:30-7 a.m., (Doyle).

ZBW3, Hong Kong, China, 9525 kc., daily after 7 a.m., (Alfred, Adams), daily except Saturday 11:30 p.m.-1:30 a.m., 3-10 a.m., Saturday 3-11 a.m., 9 p.m.-1:30 a.m., (Beckemeyer, Black).

CQN, Macao, China, 10,020 kc., Monday and Friday, 7-8:30 a.m., (Craston, Sprague), 10-10:05 kc., (White).

FZR, Saigon, French Indo-China, 31.5 meters, daily 8-11 a.m., (Sporn, Westman).

ZBW2, Hong Kong, China, 6000 kc., daily 1-4:30 a.m., (Sporn).

ZBW4, Hong Kong, China, 15,190 kc., irregular, (Partner), 11:30 p.m. to 1:15 a.m., (Doyle).

ZBW5, Hong Kong, China, 17,755 kc., daily 4-10 a.m., (Doyle).

PLV, Bandoeng, Java, 9420 kc., 7 and 9 a.m., (Gallagher, Partner), 9:45-10:30 a.m., (Sakely).

PMH, Bandoeng, Java, 6729 kc., daily, (Gallagher), daily 10 a.m., (Markuson, Howald).

PMN, Bandoeng, Java, 10,260 kc., daily 5-7:30 a.m., (Alfred), daily 5:30-11 a.m., (Hartzell, Partner, Black, Gallagher, Sakely).

PMY, Bandoeng, Java, 5150 kc., 9 a.m., (Gallagher).

PLP, Bandoeng, Java, 11000 kc., daily 5-7:30 a.m., (Alfred, Ralat), 5:30-11 a.m. daily, (Hartzell, Partner, Black, Kemp, Doyle, Beckemeyer, Sakely).

YDB, Sourabaya, Java, 9610 kc., daily until 10 a.m., (Markuson), 9650 kc., daily 5:30-11 a.m., (Hartzell, Howard).

PLE, Bandoeng, Java, 18,830 kc., 8:30 p.m., (Craston).

YDC, Bandoeng, Java, 15,150 kc., signed 10 p.m., (Howald).

HS8P, Bangkok, Siam, 9350 kc., 9 a.m., (Gallagher), Friday 8-9 a.m., (McCartin), 19,020 kc., Monday 2-3 a.m., (Sporn, Howald).

RW15, RV15, Khabarovsk, Siberia, 4275 kc., 9 a.m., (Howald, Sporn, Sakely).

VUB, Bombay, India, 9565 kc., new transmitter is being erected. (Beckemeyer).

Oceania

VK3ME, Melbourne, Australia, 9500 kc., daily 5-7 a.m., signed with "God Save the King", (Alfred, Ralat, Dressler, DeLaet, Ryan, Kenn).

VK3LR, Melbourne, Australia, 9500 kc., signs at 9:45 a.m., except Sunday. (Howald); daily 6:30-7 a.m. (Dressler); Kookaburra laugh with announcement. (Olivier, Beckemeyer, Sakely, Kentzel, Kemp, Randle).

VK2ME, Sydney, Australia, 9590 kc., Sunday 1-3 a.m., 5-11 a.m. (Munz, Markuson, Dressler, DeLaet, Randle).

VK6ME, Perth, Australia, 9590 kc., 6-7 a.m., (Herzog, DeMent, Craston, Tate); daily except Sunday 6:30-7:30 a.m., (Lueth, Hamilton).

VK9MI, Australia, 6040 kc., 6:30-7:30 a.m., announcements with chimes and whistles, (Sporn, Kernan).

W10XGY, Yacht "Elano", Pearl Walter Harbor, 12900 kc., 2 p.m., (Herzog).

VPD2, Suva, Fiji Islands, 9540 kc., daily except Sunday 5:30-7 a.m., (Hartzell, Lueth, Partner).

ZLT, Wellington, New Zealand, 11000 kc., 1 a.m., on (Howald, Gallagher, Kemp).

KIO, Kahuku, Hawaii, 11860 kc., 12:40 a.m., (Howald); 11690 kc., 1 a.m., (Gallagher).

KKH, Kahuku, Hawaii, 7520 kc., 1:15-11:30 a.m., (Gallagher).

Central America

HP5F, Colon, Panama, 6080 kc., 8:30-9:15 p.m. (Beck, Law). Slogan: "La Voz de Colon". Address: Carleton Hotel, P. O. Box No. 405.

HP5B, Panama City, Panama, 6030 kc., 7-10:30 a.m., (Doyle, Coover).

HP5H, Panama City, Panama, 9650 kc., Sunday 10 a.m., wants reports. (Burokowski).

HP5K, Colon, Panama, 6000 kc., 10:30 p.m. (Unger); uses bugles 3 tone chimes and gong, 8:30-9:30 p.m. (Beck). Slogan: "La Voz de la Vitor". Address: P. O. Box No. 33.

HP5I, Aguadulce, Panama, 11895 kc., daily 7:30-9:30 p.m., (Jaime, Atherton, Schrock); 11900 kc. (Alfred); three gong stroke three times. (Beck, Craston, Ralat, Partner). Slogan: "La Voz del Interior".

HP5L, David, Panama, 11740 kc., irregularly. (Alfred); 7 p.m. (Partner).

HP5J, Panama City, Panama, 9590 kc., daily 6-10 p. m. (from announcement). (Dressler).

TGWA, Guatemala City, Guatemala, 9450



"Imitation is the most sincere form of flattery." Leadership is always copied. That's why many sound systems are appearing on the market which look like Wards. But that doesn't mean they perform like Wards Amplifiers. Wards pioneered in the field of Sound Systems, introducing streamline styling to amplifiers, new operating conveniences, and new quality features of construction. This pioneering has made

Wards the largest distributors of Sound Systems in the U. S. Wards will continue to pioneer in Sound Systems . . . will continue to bring the newest and best to you. And remember, no matter how much others may try to copy, they can't duplicate Wards quality. Send today to nearest Ward House, Dept. RN 8, for your Free copy of Wards 1937 Radio Catalog. All Sound Systems sold on Wards Monthly Payment Plan!

MONTGOMERY WARD

Largest Distributors of Sound Systems in U.S.

CHICAGO • BALTIMORE • ALBANY • KANSAS CITY • ST. PAUL • DENVER • PORTLAND • OAKLAND • FT. WORTH • JACKSONVILLE

Be a RADIO EXPERT - Learn AT HOME

RADIO SPECIALISTS NEEDED

Modern receivers with their complicated circuit systems have knocked out the old time cut-and-try radio fixer. Trained men with up-to-the-minute knowledge are needed to service these new sets.

HERE IS YOUR OPPORTUNITY

Your possibilities of making money and getting ahead are limited only by your ability and skill—but you must know more than the other fellow. You must be a radio service specialist, as R.T.A. can train you.

PRACTICAL TRAINING AT HOME

Our home study course is practical "shop and bench" training combined with a thorough set of practical lessons prepared by an experienced Radio service engineer. Four working outfits are also furnished.

MAKE SPARE TIME MONEY

Our training is complete and practical. We show you how to make money almost from the start. The course can easily be made to pay its own way. Investigate now, write for free book of details.

WHAT R.T.A. STUDENTS SAY

Norwood, Ohio.
I have connected with a large firm as Radio Service Manager and wish to extend my thanks for your help.
Joseph Rapten, Jr.

Yorkville, Ohio.
From Aug. 1 to Dec. 7, 1936, I repaired 163 radios and put up 43 aerials which is very good for part time work while studying your course.
Chas. Koerber.




FREE OF EXTRA COST

To start you making money without delay we equip you with this Circuit Analyzer and Point to Point Resistance Tester.

RADIO TRAINING ASS'N OF AMERICA
4525 Ravenswood Ave., Dept RN-77, Chicago, Ill.

HOW TO LEARN CODE

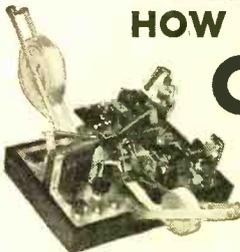

Whether you wish to enter radio as a career or merely add another valuable and fascinating accomplishment to your achievements, the All Electric Master Teleplex Code Teaching Machine will show you how. Teleplex records your sending in visible dots and dashes on a specially prepared waxed paper tape and then sends back to you at any speed you desire. It does not merely show you code. It is code. No experience needed. Beginners, amateurs, experienced ops. get ahead faster this better way. We furnish you complete course, including practice messages, the All Electric Master Teleplex, plus a personal service on a MONEY BACK GUARANTEE. Low cost. Easy terms. Without obligation write for booklet "RN7."

TELEPLEX CO.

72-76 Cortlandt St. New York City



American DYNAMIC

- Excellent Frequency Response
- Freedom from Wind Noise
- High Output
- Immune to Temperature Changes
- Consistency of response characteristic of all units

THE D-5-T 10,000 ohms High Impedance
List \$32.50

THE D-5 50 ohms Low Impedance
List \$27.50

Both equipped with 25' Shielded Cable and Plug.
Write for Free Catalogue on DYNAMIC, CRYSTAL, CARBON, and CONDENSER MICROPHONES, STANDS AND ACCESSORIES.

AMERICAN MICROPHONE CO., INC., LTD.
1915 S. Western Ave. Los Angeles, Calif.

SUCCESSFUL in
PERFORMANCE.. DESIGN..
CONSTRUCTION.. SALES..
say leading P.R. men

AMPERITE VELOCITY

**ACHIEVES
 UNIQUE RECORD
 IN ACTUAL USE**



Featuring..

1. Output increased 6 DB.
2. Triple shielded — against all RF or magnetic fields, entirely eliminating hum pickup.
3. Eliminates feedback troubles.
4. Excellent for close talking and distant pickup.
5. Acoustically designed to eliminate any possibility of cavity resonance.
6. Fitted with switch and cable clamp.

NEW! MODELS RBHn (High Impedance): RBMn (200 ohms), with Cable Connector and Switch — **\$42.00 LIST**

NEW! MODELS RBSn, RSHn, streamline; slightly lower output and frequency range than above, with switch only — **\$32.00 LIST**

Models RAL (200 ohms): RAH (2000 ohms). Built to Amperite standards: No peaks. Flat response. Triple shielded. Shock absorber. Swivel bracket. — **\$22.00 LIST**

Finishes: All microphones have the new standard Gunmetal Finish. Available in Chrome, extra. \$1.00 List.

FREE WINDOW DECAL advertising your SOUND SERVICE. Four-color design. 5 1/4 x 9 1/4. Write for it now.

AMPERITE Co. Cable Address: Aikem, New York
 561 BROADWAY NEW YORK

AMPERITE Velocity **MICROPHONE**

Amazing New Gadgets
Speedup YOUR SERVICE WORK

GHIRARDI'S NEW POCKET TROUBLE SHOOTERS
SAVE TIME • SAVE LABOR • SAVE MONEY!

The author of "RADIO PHYSICS COURSE" & "MODERN RADIO SERVICING" now gives you 2 NEW "GADGETS" — evoletted, pocket-size TROUBLE-SHOOTER CARDS that list all common radio set troubles — tell you exactly what tests to make — give quick remedies for every case!

Cleverest, handiest, trouble-finders ever conceived!

You'll marvel at the genius and simplicity of these wonderful "lightning" trouble finders. Just a flip of a card and the problem's solved!



FOR "HOME" AND "AUTO" SETS

Each gadget for its type of set gives all common trouble symptoms — "Hum", "Weak", "Noisy", "Inoperative", "Intermittent", "Fading", "Oscillating", "Distortion" — with instant tests and remedies.

50c PER COPY

The "Twin Gadgets" may pay you TEN TIMES their cost on the first service call.

MONEY BACK IN 5 DAYS IF NOT SATISFIED!

RUSH THIS COUPON NOW!

Radio & Technical Publ. Co., Dept. RN-77
 45 Astor Place, New York, N. Y.

Enclosed find \$..... Rush the "Gadgets" checked below at 50c each. If not satisfied, I am privileged to return them within 5 days, and get my money back.

"HOME RADIO" GADGET "AUTO RADIO" GADGET

Name.....
 Address.....
 City.....
 State.....

These new Gadgets will be ready for shipment June 21st.

kc., schedule: daily 6-8 a.m., 2-6 p.m., Sunday 1-5 a.m. (Alfred, Jaime, Beck, Fallon). Slogan: "Radiofusora Nacional".

TGWI, Guatemala City, Guatemala, 11850 kc., midnight. (Alfred).

TGI, Guatemala City, Guatemala, 6230 kc., requests reports, 12:12:30 a.m., (Alfred); 6300 kc. (Gallagher).

TG2, Guatemala City, Guatemala, 6250 kc., requests reports, 12:12:30 a.m. (Alfred, Murphy); 6300 kc. (Gallagher).

TG2X, Guatemala City, Guatemala, 5940 kc. (Lopez); requests reports. (Beck).

TIEP, San Jose, Costa Rica, 6700 kc., 9 p.m. (Coover); daily 11-12 p.m., 7-8 a.m. (from veri) (Adams, Sporn, Herzog). Slogan: "La Voz del Tropico". Address: P. O. Box No. 257.

TILS, San Jose, Costa Rica, 5903 kc., signed at 11 p.m. (Alfred); 5800 kc., (Jaime); 11810 kc. (Schrock, Atherton). Address: P. O. Box No. 3.

TI4NRH, Heredia, Costa Rica, 9670 kc., 9:45 p.m. (Ralatt); 9610 kc., signed at 12 a.m., with chimes; reports requested (from announcement) (Wittig); Tuesday 9:20-10 p.m. (Kernan); 14428 kc. (Fallon); schedule: 11:30-midnight, 12:12:40 a.m. (Kernan). Slogan: "The Voice of Costa Rica".

TIPG, San Jose, Costa Rica, 6410 kc. (Herzog); schedule: 7-9 a.m., 12-2 p.m., 4-11:30 p.m. (from veri) (Stillman, Lopez). Slogan: "La Voz de la Victor". Address: Perry Girtton, P. O. Box No. 225.

TIMS, Puntarenas, Costa Rica, 5900 kc. (Chiang); schedule: daily 6-10 p.m. (from announcement) (Beck). Slogan: "Radio Tims".

TIGPH, San Jose, Costa Rica, 5820 kc., 7-11 p.m. (Cartin).

TI9GP3, San Jose, Costa Rica, 5380 kc. (Beck). Slogan: "La Reina del Aire". Address: P. O. Box No. 800.

TI5HH, San Ramon, Costa Rica, 3:30-4 p.m., (Beck). Slogan: "La Voz de San Ramon". Address: R. Herrera O.

YMC, Managua, Nicaragua, 9750 kc., schedule: week days 7-9 p.m. (Lindberg).

YNOP, Managua, Nicaragua, 5758 kc., irregularly and 8-10 p.m. (Alfred). Slogan: "Radiofusora Boyer".

YNLG, Managua, Nicaragua, 8500 kc., schedule: 12-1:30 p.m., 6:30-9 p.m. (Lopez, Alfred). Slogan: "Ruben Dario". "La Voz de la Pilot".

YN1PR, Nicaragua, 8000 kc. (Jaime).

HRD, La Ceiba, Honduras, 6235 kc., 8 p.m. (Coover); daily 7-10 p.m. (from veri) (Munz). Slogan: "La Voz de Atlantido".

South America

YV1RL, Maracaibo, Venezuela, 5930 kc., reports requested. (Gallagher, Jaime, Schrock, Chiang, Randle); chimes with announcements. (Burakowski, Gossett). Slogan: "Radio Popular". Address: P. O. Box No. 247.

YV1RD, Valencia, Venezuela, 6520 kc. (Jaime); 6075 kc., 5-10 p.m. (Law); 6070 kc. (Gallagher).

YV4RG, Maracay, Venezuela, 6300 kc. (Jaime).

YV5RB, Caracas, Venezuela, 6158 kc., 7:30 p.m. (Ralat).

YV4RA, Varenara, Venezuela, 6520 kc. (Liljegren).

YV1RA, YV1RB, Maracaibo, Venezuela, 5850 kc. (Foshay, Lopez). Slogan: "Ecos del Zulia".

YV3RA, Barquisimeto, Venezuela, 50.9 meters, 7:15 p.m. (Randle); 8 p.m. (Coover). Slogan: "La Voz de Lara".

YV5RI, YV1RI, Coro, Venezuela, 6210 kc. (Ruppert, Chiang); Saturday. (Shamleffer, Ralat); 8:30-10:30 p.m. (Beck). Slogan: "Radio Corro".

YV2RA, San Cristobal, Venezuela, 5720 kc. (Herzog).

YV5RG, Caracas, Venezuela, 6400 kc., 5:30 p.m. (Ralat).

YV5RD, Caracas, Venezuela, 6160 kc., 12-2 a.m. (Sporn).

YV1RC, Valencia, Venezuela, 6230 kc. (Betances). Slogan: "Radio Valera".

YV4RB, Valencia, Venezuela, 6520 kc., 6 p.m. (Ralat). Slogan: "La Voz de Carabobo".

YV4RD, Maracay, Venezuela, 6300 kc. (Beck, Burakowski); 5:45 p.m. (Ralatt). Slogan: "La Voz de Oragua".

YV5RP, Caracas, Venezuela, 6270 kc., relays YV5RO. (Beck); daily 10-12 p.m., 9-11 a.m. (from veri) (Sporn). Slogan: "La Voz de la Philco". Address: P. O. Box 508.

YV1AP, Maracaibo, Venezuela (Samson). Address: P. O. Box No. 261.


YV5RC, YV5RA, Caracas, Venezuela, 5800 kc., 7:30-9:30 p.m. (Emerson, Foshay, Coover).

YV4RH, Valencia, Venezuela, 5910 kc. (Chiang); 5920 kc., irregularly. (Fallon).

YV1RH, Maracaibo, Venezuela, 6360 kc., schedule: 6-7:30 a.m., 11 a.m.-2 p.m., 5-11 p.m. (from veri) (Herzog, Coover); wants reports. (Unger, Ralat). Slogan: "Ondas del Logo". Address: P. O. Box 261.

YV4RB, Valencia, 6520 kc., 6-10 p.m. (Cartin).

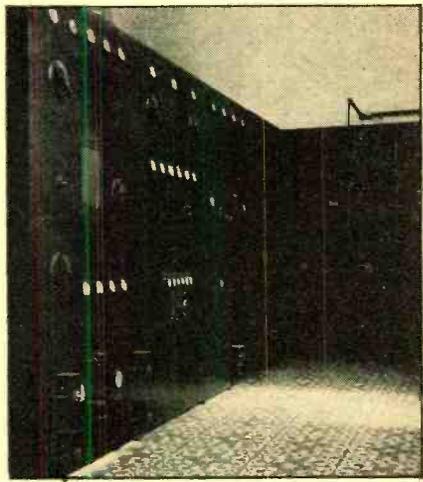HJ1ABE, Cartagena, Colombia, 9500 kc., Monday 10-10:30 p.m. (Shamleffer, Jaime, Weikal); except Sunday 6-10:30 p.m., Sunday 9 a.m.-3 p.m. (from veri.) (Schrock, Alfred, Beck, Staley, Ryan, Herzog, Stillman, Ralat,



CUBAN STATION TRANSMITTER
This is the transmitter set-up of Station COCH, Havana, Cuba.

Wittig). Slogan: "Lo Voz de los Laboratorios Fuentes". Address: P. O. Box 31.

HJ1ABG, Barranquilla, Colombia, 6040 kc. (Jaime, Liljegren); 6025 kc., signed at 11 p.m. (Alfred); 9:30-10:15 p.m. (Wittig). Slogan: "Emisora Atlantico".

HJ1ABP, Cartagena, Colombia, 9600 kc. (Liljegren); Saturday 10-11 p.m. (Weikal); 9620 kc., 7 a.m. (Hartzell, Alfred, Shamleffer, Emerson); signed 8 p.m. Sunday. (Atherton, Coover, Murray, Ralat); uses chimes (Beck). Slogan: "Radio Cartagena". Address: P. O. Box 37.

HJ1ABB, Barranquilla, Colombia, 6135 kc., 8-9 p.m. (Alfred); 9535 kc., 3 p.m. (Ralat); 3 p.m. on, 4780 kc. (Betances). Slogan: "La Voz de Barranquilla". Address: P. O. Box 715.

HJ1ABC, Quibdo, Choco, Colombia, 6000 kc. (from veri.). (Adams). Slogan: "La Voz del Choco".

HJ1ABJ, Santa Marta, Colombia, 6025 kc., daily 8-10:30 a.m. (Sporn).

HJ2ABH, HJ4ABA, Armenia, Colombia, 9520 kc. (Liljegren); daily 7-10:30 p.m.; signs with "Indian Love Call". (Alfred, Shamleffer, Fallon, Welpel, Kemp, Ralat, Wittig.) Slogan: "La Voz de Colombia".

HJ1ABP, Medellin, Colombia, 6030 kc., until 10:45 p.m. (Alfred, Kemp, Atherton). Slogan: "Emisora Philco", "Emisora General Electric".

HJ4ABB, Manizales, Colombia, 6105 kc., Tuesday 8:15 p.m. (Ralat, Kemp).

HJ4ABF, Ibagua, Colombia. (Foshay).

HJ4ABF, Bogota, Colombia, 6069 kc. (Law).

HJ3ABD, Bogota, Colombia, 6050 kc., 6:45 p.m. (Ralat).

HJ3ABB, Bogota, Colombia, 12000 kc., 7:45 p.m. (Ralat). Slogan: "Emisora Nueva Granada".

HJ3ABX, Bogota, Colombia, 6122 kc., 11:30 p.m. (Ralat). Slogan: "La Voz de Colombia".

HJ2ABC, Cucuta, Colombia, 9270 kc., sign at 10 p.m. (Shamleffer, Jaime); 9575 kc., 5 p.m. (Ralat); 4800 kc., 9-10 p.m. (Kentzel).

HJ5ABD, Cali, Colombia, 6080 kc., 7-11 p.m. (Cartin).

HJU, Buenaventura, Colombia, 9500 kc. (Jaime); 9510 kc., Monday 8-11 p.m. (Alfred); Monday, Wednesday, Friday 8-10:45 p.m. (Fallon). Slogan: "La Voz de Pacifico". Address: National Railroads of Colombia.

HKY, Bogota, Colombia, 8790 kc., 9-10 p.m. (Beck).

LSX, Buenos Aires, Argentina, 10350 kc. (Kemp); Wednesday and Thursday 7-10:30 p.m. (Gossett).

LRU, Buenos Aires, 15290 kc., wants reports. (Gossett, Stillman).

LSN3, Buenos Aires, Argentina, 9900 kc. (Gallagher).

LSL, Buenos Aires, Argentina, 15810 kc. and 21600 kc., 1:30 p.m. (Gallagher, Kemp).

LR47, Buenos Aires, Argentina, 19 meters, 6 p.m. (Alfred). Slogan: "Radio Splendid".

LRX, LRI, Buenos Aires, 9660 kc., daily 6-10:30 p.m. (Alfred, Shamleffer, Partner, Black, Stillman, Lopez). Slogan: "Radio El Mundo". Address: Calle Maipu 555.

OAX4J, Lima, Peru, 9800 kc. (Jaime); daily until 11 p.m. (Alfred, Shamleffer, Ralat); 9340 kc., 8 p.m.-1 a.m. (Partner, Chiang, Kemp, Herzog, Beck, Betances). Slogan: "Radio Nacional". Address: Radio Internacional, Casilla 1166.

OAX4D, Lima, Peru, 5780 kc., Wednesday and Saturday 9-11:30 p.m. (from veri) (Alfred). Address: All American Cables Inc., Casilla 2336.

OAX5A, Ica, Peru, 11800 kc., signed at 1 a.m., (Shamleffer); Saturday 10:45-11:30 p.m. (Kentzel); Uses two-tone whistle. (Beck).

OAX4A, OAX4Z, Lima, Peru, 6080 kc., Sun-

day 7:30 p.m.-11:30 p.m. (from veri) (Foshay). Address: P. O. Box 921.

OAX41, Peru, 1:35 a.m. (Beck).
OAX5B, Ica, Peru, 11:95 kc., 9:30 p.m. (Ralat); daily 4-11:15 p.m. (Black, Beck). Slogan: "Radio Universal".

OCL, Lima, Peru, 10970 kc., musical program at 6:30 p.m. (Gallagher).
OAX4G, Lima, Peru, 48.1 meters, 7-9:30 p.m. (Gossett).

PPQ, Rio de Janeiro, Brazil, 11670 kc., 8-8:30 p.m. (Alfred); daily 7:30-8:15 p.m. (Lueth).
PRF5, Rio de Janeiro, Brazil, 9501 kc. (from announcement), until 9:40 p.m. (Shamleffer); daily 1:45-2:45 p.m. (from veri) (Westman); daily 7-8 p.m. (Sporn, Ryan); 5:30-5:45 p.m. (Fallon).

"Radio Libertad," 9520 kc., 7-8 p.m., signs with "Marseillaise". (Shamleffer).
YV3MR, Georgetown, British Guiana, 6000 kc. (Gossett).

PZH, Paramaribo, Dutch Guiana, 7000 kc., 9 p.m. (Croston).
CEB, CB615, CB123, Santiago, Chile, 12300 kc. (from veri) (Sesma); daily 11 a.m.-1 p.m., 4-8 p.m. (Foshay, Herzog); 11 p.m. (Croston, Ralat, Partner). Slogan: "Radio Service". Address: Bandera 176, Casilla 761.

CB960, Santiago, Chile, 9600 kc. (Beck). Slogan: "Radiofutura Pilot".
PRADO, Riobamba, Ecuador, 6620 kc., 9 p.m. (Coover); Thursday 9-11:30 p.m., (Alfred). Address: P. O. Box 98.

HC2RL, Guayaquil, Ecuador, 6235 kc., (Jaime); Sunday 5:45-7:45 p.m., Tuesday 9:15-11:15 p.m. (Staley).
HC2RA, HC2EBA, Guayaquil, Ecuador, 9445 kc. (Alfred, Chiang); daily 9-10 p.m., Sunday 4-10 p.m. (Lueth, Tate). Slogan: "La Voz de Alma".

HCNA, Ecuador, 9440 kc., 11-11:30 p.m. (Wittig).
HCJB, Quito, Ecuador, 8950 kc., Monday, Wednesday and Saturday 1-3 p.m., 2-4 a.m. (from veri) (Sporn, Murray, Beck).

HC20BA, Guayaquil, Ecuador, 9450 kc., 9-10 p.m. (Beck). Slogan: "La Voz del Alma".
HC2CW, Guayaquil, Ecuador, 8400 kc., (Beck). Slogan: "Ondas del Pacifico". Address: P. O. Box 1166.

HC2ET, Guayaquil, Ecuador, 4600 kc., interval signal 12 chimes. (Beck). Slogan: "Radio Difusora del Telegrafo".
CXA4, Montevideo, Uruguay, 6130 kc., relays CX6. (Beck). Slogan: "Radio Electrico de Montevideo". Address: Mercedes 823.

CP6, La Paz, Bolivia, 9:30-10:30 p.m. (Beck). Address: Casilla 637.

West Indies

Radio Fort De France, Fort de France, Martinique, French W. Indies, 9,450 kc., daily 11:30 a.m.-12:30 p.m., 6:15-7:15 p.m., 9-9 p.m. (Edouard Boulanger, Elis, from veri) (Alfred, Craston, Sakely, Kentzel).

HH2S, Port au Prince, Haiti, 5,910 kc., (Jaime).
HH3W, Port au Prince, Haiti, 9,640 kc., (Jaime) Daily, 1-2 p.m., 7-8 p.m. (Doyle, Shamleffer, Ralat).

HIX, Trujillo City, Dominican Republic, 5,980 kc.
H11X, Trujillo City, Dominican Republic, 15,250 kc., 6,430 kc.

H12X, Trujillo City, Dominican Republic, 11,960 kc.
H13X, Trujillo City, Dominican Republic, 15,280 kc. (from veri), Sunday 7:40-10:40 p.m., Tuesday trio, 12:10-1:10 p.m., 8:10-10:10 p.m., rest of week, 12:10-1:10 p.m. (Alfred, Weikal, Schrock, Messer, Chiang, Wilson, Beck, McCartin, Partner, Tate.) Desires reports—(Coover, Navals, Brown, Tomcak, Buchanan).

H1L, Ciudad Trujillo, 6,500 kc. (Jaime).
H1N, Trujillo City, Dominican Republic, 6,240 kc., 9 p.m. (Coover, Jaime, Randle, Unger), 7:30-9:30 p.m. (Candel), 15,290 kc., (Shamleffer), 12,500 kc., (Herzog, Brown) daily 6-11 p.m. (Kernan, Oliver), 12,480 kc. (Beck, Buchanan).

H18A, Trujillo City, Dominican Republic, 6,479 kc., 9-10 p.m., and 1-2 a.m., (Alfred) Address: P. O. Box 1312.

H1T, Trujillo City, Dominican Republic, 6,630 kc., weekdays 12:30 a.m.-2 p.m., 6-8 p.m., Sunday 11 p.m.-1 a.m. (Alfred, Ralat). Slogan: "La Voz de La R.C.A. Victor". Address: P. O. Box 1105.

H1Z, Trujillo City, Dominican Republic, 6,130 kc. (Jaime). Signed at 9:15 p.m. (Ralat).
H1H, Trujillo City, Dominican Republic, 6,243 kc., (Liljegren), 6,780 kc., (Schrack), (from veri) Westman, 5:45 p.m. (Herzog), signed Sunday 6:45 p.m. (Ralat).

H1S, Puerto Plata, Dominican Republic, 6,450 kc., 7-8 p.m. (Willig), 6,420 kc., 12:15 a.m. (Hartzell, Sprague, Unger). Slogan: "La Voz de Hispaniola".

H1G, Trujillo City, Dominican Republic, 6,280 kc. Signed at 5 p.m. (Ralat).
H12D, Trujillo City, 6,900 kc., 4 p.m. (Ralat). Slogan: "La Voz de la Accion Catolica".

H1P, Trujillo City, Dominican Republic, 6,800 kc., daily 1-2 p.m., 7-9 p.m. (Ralat). Slogan: "Emisora Diario del Comercio".

H16N, Moca, Dominican Republic, 6,150 kc., 7-15 p.m. (Ralat). Slogan: "The Voice of Moca".

COCH, Havana, Cuba, 9,428 kc. (Watson, Low), 11:15 p.m. (Unger), 7 p.m.-1 a.m. (Ralat, Sprague, McCartin, Eramo, Wacker, Weiss.) signs at 10 p.m. (Pressler, Coover).

COCD, Havana, Cuba, 6,180 kc., Sunday until 3 a.m. (Sesma) 5-10 p.m. (McCartin,) 11 p.m. (Eramo).
COCE, La Corona, Havana, 8,823 kc., 11 p.m.-5 a.m. (Doyle).

COHB, Sancti Spiritus, 6,280 kc.
COCN, Havana, Cuba, 11,990 kc., signed at 11:33 p.m. (Brown). address: P. O. Box 38.

COCC, Havana, Cuba, 9,750 kc., 8 p.m. (Coover, Liljegren, Watson, Ranelle, Beck), 6 a.m. (Herzog). Schedule 7 a.m.-1 p.m. (Wacker, Pylete, Doyle, Ryan).

COCX, Havana, Cuba, 11,435 kc., 5:55-8:00 p.m. (Liljegren, Watson, Unger) 10,660 kc., (harmonic?) (Herzog, Coover).

COCO, Havana, Cuba, 12,000 kc., (Wiekal), after 3 a.m. (Hedgeland), 8 p.m. (Unger), 6,000 kc., 3-10 p.m. (McCartin, Welper); 8 a.m.-noon (Wacker, Randle).

North America

XEWI, Mexico City, Mexico, 11,900 kc., Tuesday, 9:30-11 p.m., Friday, 8-11 p.m., also on 6015 kc. (Alfred, Ralat), 11-12 p.m. (Wittig, Black) Saturday, 10-11 p.m. (Shamleffer, Gossett). Slogan: "My Voice to the World from Mexico." Address: P. O. Box 2874.

XEYU, Mexico City, Mexico, 9600 kc., requests reports, signed at 1:32 a.m. (Alfred) Saturday 12 a.m. (Hartzell, Lopez, Gallagher). Address: Nopoli 60, 60 Napoli Street.

XEXA, Mexico City, Mexico, 6180 kc., daily 8-11 p.m. (Howald), reports requested, (Fallon, Sporn), 6132 kc. (Brummund, Sporn), 6160 kc., (Gassett). Address: Dept. of Publicity & Propaganda.

XEBT, Mexico City, Mexico, 6000 kc., 7 p.m.-4 a.m. (McCartin), 6100 kc., (Emerson, Beck), interval signal is three cuckoo calls.

XECR, Mexico City, Mexico, 7380 kc. (Emerson).
XEPW, Mexico City, Mexico, 6110 kc., chimes used. (Beck, Alfred, Fallon, Law), daily except Sunday 8-12 p.m. (Partner, Brummund). Slogan: "La Voz del Aguila Azteca des de Mexico". Address: P. O. Box 8403.

XEFO, Mexico City, Mexico, 6120 kc., (from ann.) (Beck) 9400 kc. (Alfred). Address: P. O. Box 2641.

XEUW, Veracruz, Mexico, 6020 kc., (Jaime, Sesina).
XEUZ, Mexico City, Mexico, 6120 kc., (from veri), 2:15 a.m. (Alfred, Jaime, Law, Sakely). Slogan: "Cadena Radio Nacional." Address: Same as XEFO.

XEBR, Hermosillo, Sonora, Mexico, 11,820 kc., Chimes at intervals (Beck), daily 9-10 p.m. (Alfred, Atkinson, Chiang, Brown, Lopez). Slogan: "Herald of Sonora". Address: P. O. Box 68.

XEDQ, Guadalajara, Mexico, 9480 kc., (from veri), 10-12 p.m. (Alfred) 9520 kc. (Jaime, Sesina, Black, Beck). Cuckoo calls, chimes and sirens. Slogan: "Radio Fonografica de Guadalajara". P. O. Box 197.

XEME, Merida, Yucatan, 9520 kc., 2:30-3 a.m. (Alfred). Address: Calle 59, 517.

XEBM, Mazatlan, Sinaloa, Mexico, 15,440 kc., (Beck), uses bugle calls, siren, and chimes. Slogan: "El Pragonero del Pacifico". Address: P. O. Box 50.

XECU, Mexico D.F. Mexico, 6075 kc., 5-10 p.m. (Law).
XERY, Mexico, D.F. Mexico, 5920 kc., (Beck). Slogan: "Alente de Bravo".

CFRX, Toronto, Canada, 6070 kc., relays CFRB.
CRCX, Toronto, Canada, 6090 kc., daily 5-11:30 p.m. (Sporn).

CFRB, Toronto, Canada, 6900 kc., 6-11 p.m. (Alfred, Howald, Sesina), 11:20 kc. (Law, Chiang, Wittig, Unger). Address: Roger-Majestic Corp.

VE9HX, Halifax, N. S., Canada, 6130 kc., 1-1:30 a.m. (Alfred), schedule: 10 a.m.-2 p.m., 6 p.m.-12 midnight, daily except Saturday, Sunday, and Friday; Saturday 2-4 p.m., Sunday only 3 p.m.-midnight (from veri) (Herzog, Kemp).


CJRO, Winnipeg, Canada, 6159 kc. (Jaime), 11-11:30 p.m. (Sprague).
CJRX, Winnipeg, Canada, 11,720 kc., 11-11:30 p.m. (Sprague).

CFCX, Montreal, Canada, 6000 kc., 5-11 p.m. (McCartin, Sprague).
VE9CS, Vancouver, B. C., Canada, 6075 kc., relays CFHC. (Law).

VE9EM, Vancouver, B. C., 4800 kc., heard testing. (Kemp).
W1XX, Springfield, Mass., 9570 kc., (Jaime, Watson, Randle), 6 a.m., (Wittig, Hurley).

W1XAL, Boston, Mass., 4:55 p.m. (Randle), 11,790 kc., 4:30-5:30 p.m. (Liljegren), 15,250 kc., 10-11 a.m. (Shamleffer, Hare), Tuesday and Friday, 7:30-9:15 p.m., Monday through Friday, 7-9 p.m., Saturday 4-7 p.m., Sunday, 10-12 a.m., and 5-7 p.m. (White).

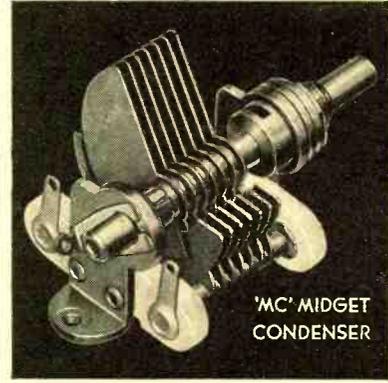W3XAL, Bound Brook, N. J., 17,780 kc., (Liljegren), 6100 kc., 16,843 kc., 5:15 p.m. (Randle), 6-11 p.m. (McCartin, Sigurdson), 17,850 kc., Monday, Wednesday, and Saturday 5 p.m.-12 p.m., 6100 kc., daily 9 a.m.-5 p.m. (Ryan), requests reports (Unger).



MC MIDGET CONDENSER

**BETTER CONDENSERS
for BEST RESULTS**

SINCE introduction, Hammarlund precision variable condensers have been the constant favorite of critical engineers, amateurs, operators, and set builders, for their exacting and diversified needs in quality receivers and transmitters!

Every Hammarlund condenser, designed for peak electrical and mechanical performance, has wide capacity ratios, vibration-proof construction, noise-free operation, quality insulation, and selected metals—all with an eye to dependable, trouble-free, long lasting service. For instance, the MC midget condenser, illustrated above, uses Isolantite insulation, a new noiseless silver-plated Beryllium wiping contact; wide split type rear bearing; a wide special front bearing; cadmium plated soldered brass plates, etc.

A wide variety of condensers are made for every need—such as single and split-stator midget and micro variable condensers (44 sizes—20 to 320 mmf.); single and split-stator transmitting condensers (38 sizes—20 to 1000 mmf., 1000 to 12000 volts); the star midget condensers (7 sizes—15 to 140 mmf.); famous midline condensers (3 sizes, 250 to 500 mmf.); trimming and padding condensers (23 types, 3 to 1000 mmf., single and dual, Isolantite and bakelite bases), etc.

This extensive group of condensers with their special design and construction makes them ideally suited for compensating, vernier, regeneration, neutralizing and general broadcast tuning applications as well as air craft, police car and marine work and laboratory and test equipment in general.

If you want the best results, use Hammarlund condensers—they'll never fail you!

The complete line of Hammarlund condensers is thoroughly described and profusely illustrated in the new 1937 catalog. The coupon below will bring you your copy free of charge.

Mail Coupon Now!



HAMMARLUND MFG. CO., INC.
424-438 W. 33rd St., N. Y. City
Please send me the new "37"
HAMMARLUND catalog

Name.....
Address.....
City..... State.....RN-7



Learn RADIO from REAL RADIO ENGINEERS!

HERE THEY ARE



Kenneth Clough
Chief Engineer,
Clough-Brengle
Company.
E. E. Gramer
Vice President
in Charge of
Engineering,
Standard Trans-
former Co.
Karl E. Hassel
Chief Research
Engineer,
Zenith Radio
Corp.
F. H. Schnell
Radio Engineer,
Grinow Radio
Dr. G. M.
Blackburn
Production Dept.,
P. R. Mallory
and Co.

Many R-T-I Trained Men Earn up to \$75 a Week and More

These industry appointed engineers, who work for large radio manufacturers, will supervise your training at home, and get you ready for good-pay jobs in Radio Broadcasting, Installation, Servicing, Public Address System and Photo Electric Cell work. Also for coming activity in Television. Opportunities for properly trained men better than ever before. Earn while you learn. Some make \$5 and \$10 a week extra in spare time one to two weeks after starting. Many earn up to \$75 a week in full time jobs, or their own business. Some even more. No other training like mine. Get the facts if you want a better job. Write now for my free book.

RAY D. SMITH, President.

RADIO AND TELEVISION INSTITUTE
Dept. 4-B, 2150 Lawrence Avenue, Chicago, Ill.

MAIL COUPON FOR FREE BOOK


RAY D. SMITH, President
Radio and Television Institute (R-T-I)
2150 Lawrence Ave., Dept. 4-B, Chicago, Ill.

Without obligating me, send me FREE Book about spare-time and full-time Radio opportunities and how I can train for them at home.

Name.....

Address.....


City..... State.....

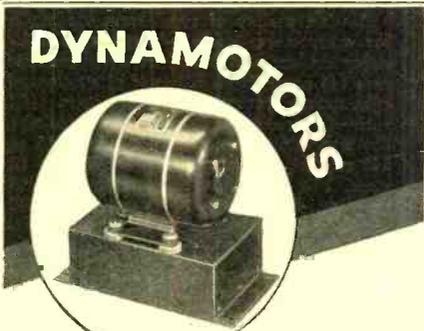

A DEPENDABLE POWER SUPPLY

Dynamotors, gen-e-motors and converters produced by this pioneer manufacturer of power supply units afford the last word in this equipment for aircraft, police, marine and auto radios and public address systems. Compact and light weight. Sturdily constructed to assure long, dependable service. For complete information address

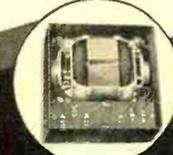PIONEER GEN-E-MOTOR CORPORATION
Dept. No. R-3G, 466 West Superior Street
Chicago, Ill.



GEN-E-MOTORS

- W6XKG, Los Angeles, Calif., (Randle), 25950 kc., has 24 hour schedule, (Schrock), 26400 kc. (Law, Atkinson, Atherton, Wacker, Sesina, Rheiner, Murphy), requests reports, (Randle, Hamilton).
- KEI, Bolinas, Calif., 9490 kc., 11:30 p.m. (Cox).
- KCJ, Bolinas, Calif., 9000 kc., 11-11:05 p.m. (Pylate).
- KKO, Bolinas, Calif., 11950 kc., 9 p.m. (Alfred).
- W3XAU, Philadelphia, Pa., 9580 kc., 6060 kc., 8-11 p.m. (McCartin, Law, Weiss, Sprague).
- W8XK, Pittsburgh, Pa., 15200 kc., 11800 kc., (Jaime, Watson), 6140 kc., 7-12 p.m., 21500 kc., 6:30 a.m., daily (Pylate), daily 9 a.m.-7 p.m. (Ryan).
- W9XAA, Chicago, Ill., 6080 kc., 9:15 a.m., (Eramo, Weiss).
- W9XF, Chicago, Ill., 6100 kc., (Jaime, Watson, Herzog).
- WX9PD, St. Louis, Mo., 31600 kc., requests reports, (Randle).
- W8XWJ, Detroit, Mich., 31600 kc., requests reports, (Randle, Sigundson).
- W2XGB, Long Island, N. Y., 12860 kc., 1-2 a.m. (Beck).
- W2XE, New York, 15270 kc., 17700 kc., (Jaime, Liljengren), 21520 kc., 7:30 a.m. and on (Randle), 17760 kc., (Atkinson).
- W2XAF, New York, N. Y., 9530 kc., (Jaime, Liljengren, Hare, Watson).
- W2XAD, New York, N. Y., 15300 kc., (Jaime) 15330 kc., (Liljengren, Hare), schedule 10 a.m.-6 p.m., (Randle, Sigundson, Ryan, Hamilton, Beck).
- W8XAL, Cincinnati, Ohio, 6600 kc., (Jaime, Randle, Weiss) 6060 kc., (Sprague).
- W3XES, Baltimore, Md., 35600 kc., schedule 9 a.m.-5 p.m. (from veri.), (Randle).
- W9XAZ, Milwaukee, Wis., 26400 kc., 4:45 p.m., (Randle, Law), week days 1-12 p.m., Sundays, 1-5:30 p.m. (Wacker).



SWISS LISTENING POST
Listening post of Observer Hugo W. Richter with his pet Tom cat, "Pete", who resents CW interference.

Brown, Archwell L. Bower, Jack Thomas, Art. E. MacLean, Lee Meade Williams, Leslie Maxwell, Michael Waser, Jr., Ray D. Brown, W. J. Lander, Earl W. Jones, I. M. Sears, A. E. Milby, Edward Treadwell, Marvin Pylate, Irving Sporn, B. W. Southwell, Thomas Fallon, Jr., Joseph A. Ryan, Wayne Wicks, August Brodrecht, R. C. Messer, Louis Margolis, P. L. Stiles, Paul J. Mraz, E. J. Wacker, A. Androk, M. J. Markuson, R. C. Messer, W. F. Herzog, John Eramo, Wede L. Jacobs, H. E. Goleby, George Hare, Fletcher, W. Hartman, Grace M. Beck, L. Weiss, Claude H. Roberts, Dan T. Wollenschlager, Irving Goodeve, C. V. Hays, A. Kosynsky, Abraham Sutker, Elizabeth Ritter, Walter J. Dustin, Wade Chambers, Jorge Ralat, Harry Lueth, Wilbur Croston, R. F. Shamleffer, Anton J. Cindel, James Doyle, Barry Sesma, Zane Sprague, C. R. Wilson, Manuel Betances, Michael Hedgeland, Peyton Black, J. Wendell Partner, K. D. Beckemeyer, John Kernan, Howard W. Oliver, E. Geneve, John L. Tate, Kenneth Dressler, Floyd M. Murphy, Fred Atherton, J. A. Lindebert, Jr., Arthur B. Coover, Orville Brown, Troy Welper, M. Rheimer, Albert Emerson, F. W. Dodge, Manuel Ortiz, C. V. Hays, Fred Cox, Clair D. Van Meter, Mike Janyon, David Hurley, Jr., N. Hendry, Virgil Gossett, B. Kashimoto, Frank Sakely, H. F. Hamilton, J. R. Solodim, Joe Novak, Burnell Unger, C. Hays, G. C. Gallagher, Morgan Foshay, Simon M. Cartin, Elmer Samson, L. M. Jensen, William Peterson, Fred W. Alfred, Kenneth Futrell, D. Mason Gledhill, Lyle M. Nelson, Arthur Hamilton, C. H. Williams, A. W. Brummond, I. H. Burakowski, Jack Staley, H. Kemp, Harry E. Kentzel, George Hare, William Buchanan, John Tomcak, Li Chi Chiang, Sherry Adams, J. Atkinson, P. Piorko, Gilbert L. Harris, W. G. Umstead, Arthur Immicke, Carl & Anne Eder, Albert Augustine, James E. Moore, Jr., R. B. Oxrieder, R. W. Sahlbach, Leslie Mott, E. de Cottignies.

Readers Who Are Awarded "Honorable Mention" for Their Work in Connection with This Month's Short-Wave Report

Jaro Kober, Ernest W. Law, Herman Rupert, Eric W. Watson, Olof Liljengren, Luis Diez, Hugo W. Richter, Donald Robinson, Roy E. Chisholm, Jose Lopez, Clyde Crissell, Steve Gorykowski, Max Hausdorff, Edward Peterson, Robert Muguet, H. Westman, Charles W. Egenweiler, A. Sigundson, Thomas Walczak, Pete Chagaris, Leslie W. Orlon, A. Clyde Fisher, Oscar Jaime, Jr., P. J. Cawsey, Harold E. Schrock, J. C. Innes, Troy Welper, Roy Chisholm, Simon Nodell, Louis C. Sciez, M. E. Packman, Jr., Clarence Hartzell, W. Labega, W. J. Stillman, Herman E. Wittig, Howard N. Schmidt, Richard Connes, Roy E. DeMent, Werner Howald, Thaddeus L. Grabek, T. Burnell Unger, Juan Manuel Salazar, Charles Mourmouris, Armand A. Boussy, Wong Tit, L. F. Gallagher, Paul B. Silver, Adam J. Eckert, Jr., Vincent M. Poll, James Rubard, John C. Sibbin, N. C. Smith, Albert Marcus, Ed. Nowak, Jr., George J. Munz, Joseph Zajchowski, A. Yamamoto, Thomas Randle, Tony Pettigean, Lorimer W. MacAlister, William Buchanan, Wilbur

"Ham" Transmitter

(Continued from page 24)

carbon microphone for voice transmission, although the transmitter is arranged so other types of microphones may be used if desired.

The power supply delivers 325 volts to the plates of the tubes with dropping resistors in other circuits to reduce this value to the ratings of the respective tubes. More than ample current is available through the use of two type 83 rectifier tubes in parallel.


Plug in coils are used. Operation on all amateur bands requires fifteen coils. Three are used at a time, one in the oscillator circuit, one in the buffer and a third in the r.f. amplifier. One of the interesting features is the method of providing flexibility and quick changeover from one band to another. This is the semi-fixed tuning arrangement for the oscillator and buffer circuits. For instance, the oscillator coil is adjusted by means of a trimmer condenser mounted through the chassis. If the trimmer is properly adjusted for the highest

frequency crystal to be used in any band up to and including the 7,000 kilocycle band, another crystal may be substituted in this same band without retuning. However in the 14,000 k.c. band the trimmer will require readjustment when the crystal is changed. It was found the oscillator may be tuned easily when a neon lamp is used to indicate r.f. It is held near the oscillator coil.

The buffer circuit also is tuned by means of a trimmer condenser and adjustment is made in the same manner as in the oscillator stage. The 802 is operated at below normal voltage and draws small plate current, but provides adequate excitation for the r.f. amplifier.

Tuning of the r.f. amplifier is done by means of the control on the front panel. Adjustment of course is for minimum plate current on this tube. The r.f. amplifier plate coil also has an antenna coil wound at the "cold" end, providing for connection to either a "Zeppelin" or matched impedance type of antenna. A Marconi type antenna may be used on the lower frequencies.

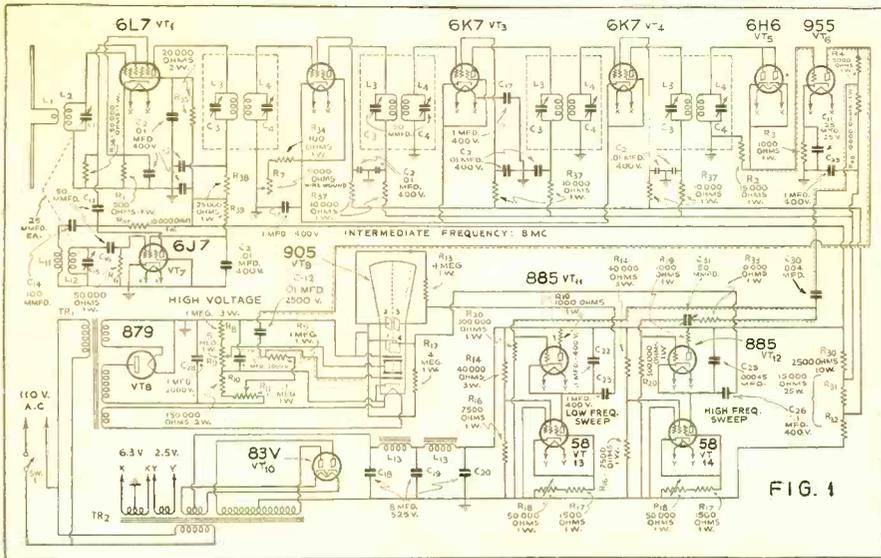Another interesting feature is the method of adjusting the coils for the two lower frequency amateur bands. These coils con-



LATEST DATA ON DON LEE TELEVISION RECEIVER

Constructors should use this diagram when wiring the television receiver described in the May issue. Wiring changes have been made to resistors R19 and R36; Value changes in C23, C12, R9, R30, R31, R32. When and if other improvements make their appearance, these will be incorporated in new diagrams from time to time.

tain their own trimmers which connect in parallel with those already in the set.

Neutralizing voltage for the r.f. amplifier is obtained from the plate circuit of the buffer stage by means of two taps on this coil. The neutralizing condenser for the 807 consists of a nut attached to the end of a screw that may be adjusted to obtain the proper capacity. Only a few micromicrofarads are needed.

Parasitic Filters

Parasitic filters are used in both the screen and grid circuits of the power amplifier and the screen circuit of the oscillator. These consist of 100 ohm resistors shunted by small r.f. choke coils.

Voltage for the carbon microphone is obtained from the power supply, and is approximately 5¾ volts. The modulation transformer is cut in or out of the circuit by means of the "phone—C.W." switch on the front panel. In the c.w. position the switch, which is a double-pole-double-throw affair, disconnects the plate voltage of the two speech amplifier tubes as well as the screen voltage on the 6L6's and substitutes a bleeder resistor. The resistor prevents the rectified voltage from reaching a value endangering the filter condensers when the key is in the "up" position. With the screen voltage removed from the 6L6's they draw no plate current, even though plate voltage is still applied.

Keying the Rig

An insulated strip containing three terminals is provided for connecting the key. By using two of these it is possible to key both the buffer and r.f. amplifier simultaneously while the oscillator continues to operate, or by using two other terminals, the oscillator and amplifier stages may be keyed simultaneously.

Some fixed bias is provided in addition to the grid-leak bias for the protection of the r.f. power amplifier. However, this is not sufficient to prevent high dissipation in the r.f. amplifier should excitation be removed. Therefore, the manufacturer does not recommend the oscillator be keyed alone. However, for frequencies up to and including the 7,000 band it is possible to key the oscillator simultaneously with the other stages.

The transmitter was put on the air at W2MW for tests. Despite its small power surprising results were obtained. On the 20 meter 'phone band five stations were worked in a row and reports varied from R6 to R9. These stations ranged in distance from 500 to 1,000 miles. One interesting test was made with a station in Atlanta, Ga. (W4CFD). He was worked three times during the day at different hours. He reported the signal R7 to 8 on all occasions, but some interference from a powerful mid-Western station. The transmitter was switched from 'phone to c.w. and it was possible to compete with the powerful interference. Later, as a test, the normal 400-watt transmitter at W2MW was put on the air and he reported he noticed very little difference in signal strength, and that interference affected the more powerful signal about as much as that from the low-powered transmitter.

Operating Tests

The transmitter was tested at 10 meters, but unfortunately conditions on the band at the time were nil, so that it was impossible to determine its effectiveness. However, output obtained seemed to be about the same as that on 20 meters and, normally, when the 10 meter band is functioning 16 watts of carrier on 'phone is about as effective as a half-kilowatt.

The transmitter was tested on the 75 meter 'phone band with an antenna that normally has from 500 to 1,000 watts behind it. In the short space of an hour five stations were worked. The tests were made in the late afternoon when the interference on this band is quite heavy. The first station worked (W2CET) was about forty miles airline from the transmitter and reported the signals QSA5 R8 and 100 per cent through all of the QRM. The second station (W8EMV) at Medina, Ohio, was close to 400 miles from the transmitter. He reported the signals QSA4 R7 due to some rather heavy QRM. The next station contacted was W3CKD at Monton, Pa. who reported the signal QSA5 R7 to R8. Two other contacts were had with second district stations within ten miles of the transmitter and both reports were QSA5 R9.

*Handy...and
for 1000 Uses*

Size:
3 1/16" x
5 7/8" x 2 1/8"



Completely Insulated

Model 666

Dealer Price \$15.00

Pocket Volt-Ohm-Milliammeter

For laboratory, shop or field use. Handy pocket size yet sturdy and precision built.

Uses Large 3" Sq. Triplet Instrument.

A.C.-D.C. Voltage Scales Read: 10-50-250-500-1000 volts at 1000 ohms per volt.
D.C. Milliampere Scale Reads: 1-10-50-250.

Ohms Scales Read: Low ½-300; High 250,000.

Black Molded Case and Panel.

Low Loss Selector Switch.

Complete with Alligator Clips, Battery and Test Leads.

A complete instrument for all servicing needs. Can be used for all A.C.-D.C. voltage, current and resistance analyses. Leather Carrying Case, Model 669, supplied extra. Very attractive. Of black, heavy leather with finished edges and strap.

DEALER PRICE. \$3.00

Remember Booth 79, Radio Parts Show, Hotel Stevens. Many New Items in the Ever-Enlarging Triplet Line Will Be Displayed.

WRITE FOR CATALOG



The Triplet Electrical Instrument Co.
157 Harmon Ave., Bluffton, Ohio

Without obligation please send me

More information on Model 666.

I am also interested in.....

Name.....


Address.....

City..... State.....

The NEW SUEDE CABINET


Made of steel, yet having a soft Suede finish that is delightful to the eye and touch, these cabinets are causing the sensation they are entitled to.

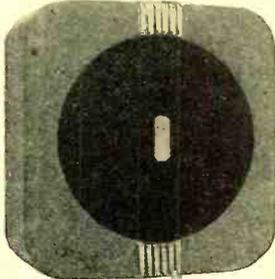Equipped with the famous Nokoil Speakers, they are perfect for hotels, apartments, houses, call systems, automobiles, "Talk-Bak" systems, etc., etc.



The 8" Suede Vehicle Cabinet with its taupe finish and black grille enhanced by the bright polished ornaments.

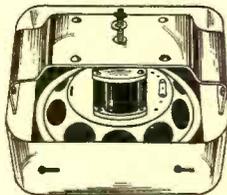See how adaptable it is. Either base or single stud mounting, yet no bolt is screwed into the Speaker pot to throw the pole piece off center.



Wall cabinets are finished in taupe with a light brown grille which blends perfectly. Our new novel method of fastening the cabinet to the wall makes it unremovable without a special tool.

Write for complete information on our Suede Cabinets with Nokoil Speakers. Wright-DeCoster distributors are always anxious to cooperate.

WRIGHT-DeCOSTER, INC.

2255 University Avenue St. Paul, Minn.
Export Dept.: M. Simons & Son Co., New York
Cable Address: "Simontree".

Canadian Office: Associated Sales Co., Guelph, Ont.

I Will Teach YOU to be a Fast, Capable RADIO OPERATOR

At Home

Quick Results When You PRACTICE RIGHT!



Code skill is not a special gift of nature to be enjoyed by a few. It is the natural result of proper training and can be acquired by anyone within a few weeks, with the CANDLER system. Code champion McElroy teaches the CANDLER system at Harvard college. It is the easiest, most inexpensive and surest way to learn good code. Ask any skilled operator. Whether you are a beginner, or want to improve your speed and technique, CANDLER'S personalized and scientific system assures success. Don't postpone your future in code work. Write today!

Send for FREE Book of Facts

CANDLER SYSTEM CO.

Asheville Dept. N-7 North Carolina

RADIOS..SAVE UP TO 50%

DEAL DIRECT...FACTORY PRICES! Many models to select from: AC-DC; All-Wave; Farm sets that operate like city radios! Your name and address on postcard brings you NEW Bargain Catalog in colors FREE. Get details of 30-DAY TRIAL Plan and agent-user proposition! GOLDENTONE RADIO CO. Dept. A-7, DEARBORN, MICHIGAN

Free Catalog

30 DAY TRIAL \$6.98 UP

RADIO ENGINEERING,

broadcasting, aviation and police radio, servicing, marine radio, telegraphy and telephony, Morse telegraphy and railway accounting taught thoroughly. Engineering course of nine months' duration equivalent to three years of college radio work. School established 1874. All expenses low. Catalog free.

Dodge's Institute, Oak St., Valparaiso, Indiana

WHAT'S NEW IN RADIO

WILLIAM C. DORF

(Continued from page 9)

and a saver of time when drivers become confused on strange roads.

Two easy ways are provided for mounting the compass: by a bracket fastened by vacuum cup to the windshield, or by a bracket screwed to header board.

Ideal For Sound Truck Use


Here is the Montgomery-Ward complete 20-watt mobile sound system that should have unusual possibilities for both rental and sale. It can operate from either a 6-volt storage battery or 110-volt a.c. line supply. It is equipped with a mixer con-



trol, regulating microphone, phonograph or radio input. The amplifier consists of 4 stages; one 6C6, two 76's, three 6A6's, and one 83 type rectifier.

Constant Impedance Control

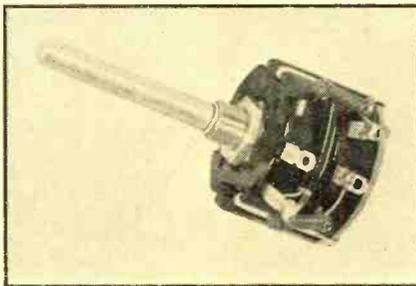Using an old principle of design, the "bridged-T" network in a new application has enabled Centralab to offer a true constant impedance control at little more than the cost of a good potentiometer. Known as the "Delta-T Pad" these new units are



designed to be used in all conventional low-impedance attenuator and series-mixer circuits.

New Tube Checker


The Weston Electrical Instrument Corporation recently announced the new model No. 773 tube tester, available with carrying case, for special counter mounting (shown in the illustration) or as a matched companion unit for their model No. 772 analyzer. The checker features the same "anti-obsolescence" circuit and switching system first introduced in the model 770 tube checker two years ago—a system designed to test the newest tubes without adapters. A new feature of the unit is the "noise-test" jack, wherein headphones or an amplifying unit can be plugged to check on possible sputtering, "frying" or other tube noise in any or all



electrode circuits. A hot-cathode leakage test is provided, and the neon short check can be quickly made while the tube is hot to catch intermittent shorts. The 4½ inch meter scale has a color-band marking, differentiating between good and bad tubes.

Microphone Stand Contest

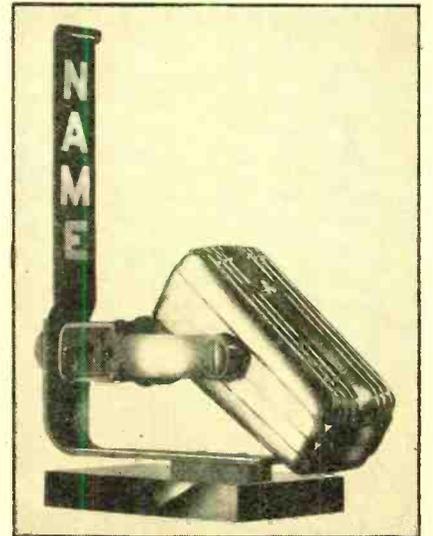The Amperite Company invites our readers to submit a name for their new "mike" desk stand. The person submitting the best name receives the first prize of a microphone and stand. Those submitting




the ten next best names will be awarded a stand. The contest closes July first and the judges are John F. Rider, publisher, and Joseph Kautman, of the National Radio Institute.

One of the features of the new stand, is with the microphone placed horizontally, the center of gravity is lowered, making the unit unusually stable. The leaf spring suspension acts as an excellent shock absorber.

Dial Tells Complete Story

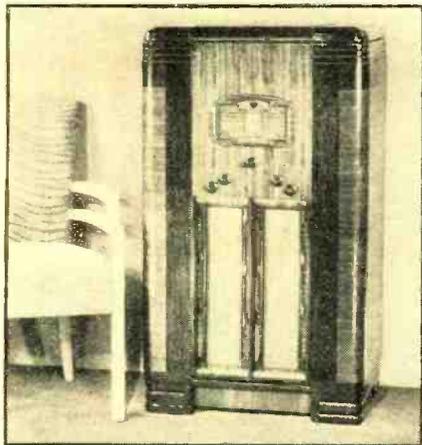
At first glance the most apparent refinement of the new Stromberg-Carlson model 145 SP ten-tube Labyrinth type high-fidelity receiver and automatic phonograph is the de luxe index type dial with tri-focal tuning indicator, micrometer sub-dial, volume indicator and other features all grouped in one attractive unit. Additional advances include tuning range 145 to 18,000



kc., automatic antenna selector new full floating pickup mounting, etc.

New Electrical Accessories

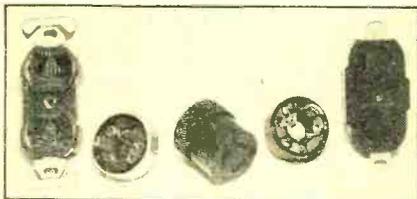
The Harvey Hubbell Company, specialists in all kinds of electrical wiring accessories, has just announced the following



new products, of interest to servicemen and radio dealers as well as electricians. Viewing the illustration from left to right, the first item is a new duplex-outlet for side wiring. It is finished with a bakelite face and will take the double "T" blade cord-grip plug shown next to it. The blades of the plug are a combination of tandem and parallel, riveted and key-locked together. The next three items are the new "twist-lock" devices; a 3 wire polarized bakelite connector and cap, and a duplex-flush receptacle for same.

Latest Farm Radio


This is the new RCA 5-tube, three-band superheterodyne, especially designed for use on the farm and in those districts without benefit of power lines. This model may be operated as a 2-volt set, using the following batteries: one Air-Cell or 2-volt storage battery; three 45 volt "B" batteries; one 7½ volt "C" battery or it can also be easily converted to 6-volt operation by employing the new RCA model CV-8 "Pak-O-Powr". This unit and a 6-volt storage battery are the only power supplies needed. The set has a tuning range from 530 to 1720 kilocycles.

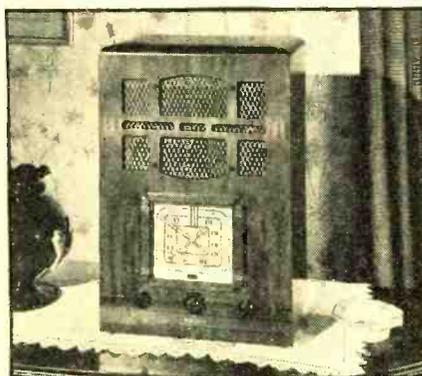

equipment comprises one 1C6, one 1A4, one 1F6, one 30 and one 19 type power tube.

Dynamic Microphone

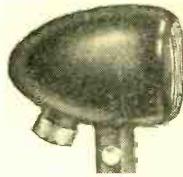
The moving coil, permanent magnet type microphone shown in the accompanying illustration, is made by the American Microphone Company. The new instrument is available with either high or low-impedance output. It is an all-purpose



"mike" of rugged construction, designed to be semi-directional, to have minimum feedback, and to provide high-quality.

Another Profitable Side Line

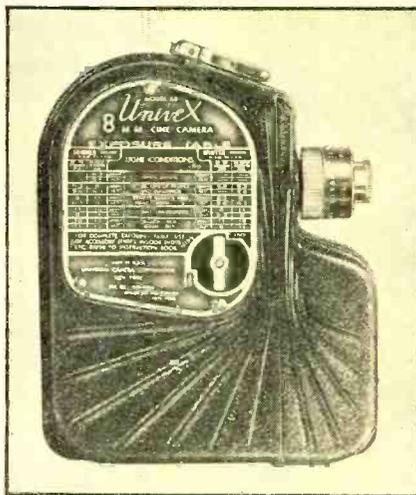
For extra sales and profits many radio stores are now handling home movie equipment. Dealers and servicemen in this business will be interested in the new Univex Cine low-cost movie camera. This instru-



ment employs 8 mm. film and there is a companion projector, model No. P8.

Constant-Impedance Output Attenuator

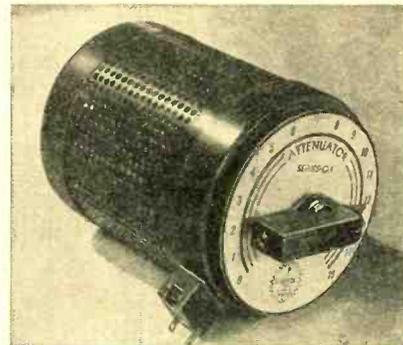This is the new series CIA constant-impedance attenuator announced by the



Clarostat Manufacturing Company. It is recommended as an output level control for power amplifiers, or as an input attenuator for individual loud-speakers in a public address system. It is made to dissipate 25 watts of power continuously, regardless of setting, and has a minimum insertion loss of 1.3 decibels. Standard surge or input impedances available are 8, 15, 50, 200, 250 and 500 ohms.

The control is linear up to 45 decibels, in steps of 3 decibels with an end position of infinite attenuation. Impedance from load end is approximately three times the line value.


(Turn to page 64)

AMAZINGLY NEW, MIDLANDS GREAT "COLOR-CODED"

RADIO TELEVISION EXTENSION TRAINING

Originated and developed by experienced engineers and educators. Backed by the resources and modern facilities of nationally known, 5000-watt Columbia basic network broadcasting station, KMBC. "Color-Coded" training fits you for better jobs in radio—prepares for future television opportunities. Graduates qualified to take Government operator's license exams. Lifetime employment service. Get the facts without delay.

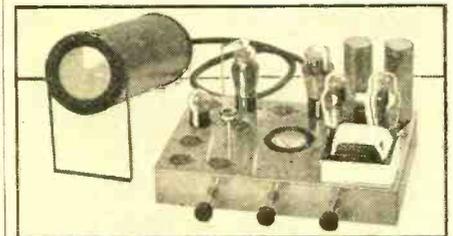WE SEND ALL NECESSARY EQUIPMENT FOR YOUR "HOME LABORATORY" EXPERIMENTS



You will build this modern oscilloscope. And it will be yours to keep.

You get 90 modern "color-coded," illustrated lessons, 10 attractive "Home Laboratory" manuals; 10 big shipments of experimental equipment including 3-inch Cathode Ray tube—necessary tools. Then, after completing your "home training," you get a bus ticket to Kansas City and 4 weeks' intensive training in our fine school laboratories. WE ARE NOT CONNECTED WITH ANY OTHER RADIO OR TELEVISION SCHOOL.

MIDLAND TELEVISION, Inc.

29th Floor, Kansas City Power & Light Bldg. 110 W. 14th St., Kansas City, Mo.

IT'S Free **FORTUNES IN FORESIGHT**
Get the Facts Before you Act! Send for your copy today.

MAIL COUPON TODAY

MIDLAND TELEVISION, Inc. (Mail in 29th Floor, Kansas City, Mo. envelope or paste on postcard)
110 W. 14th St., Kansas City, Mo.
Without obligating me, send your new FREE book about the Radio-Television profession, "FORTUNES in FORESIGHT."
Name..... Age.....
Address.....
City..... State.....

ELECTROLYTICS
for your every
CIRCUIT
REQUIREMENT



There is no electrolytic replacement required for the servicing of the modern A.C.-D.C. receiver that cannot be successfully accommodated by either the types KR or JR dry electrolytic capacitors.

The type KR series is enclosed in aluminum containers with convenient wire leads and the type JR series is available in containers with wire leads and mounting feet. Both the type KR and JR series is available in single, dual and multiple capacity combinations.

For a neat, profitable job and complete customer satisfaction standardize on C-D electrolytics. Complete catalog free on request.

MICA • DYKANOL • PAPER
WET AND DRY ELECTROLYTICS
CORNELL-DUBILIER CORPORATION
1018 Hamilton Blvd., So. Plainfield, N. J.



RADIO
ENGINEERING
DEGREE
IN 2 YEARS

Complete Radio Engineering course in 96 weeks. Bachelor of Science Degree. Radio (television, talking pictures and the vast electronic field) offers unusual opportunities for trained radio engineers. Courses also in Civil, Electrical, Mechanical, Chemical, Aeronautical Engineering; Business Administration and Accounting. Also short diploma courses in Surveying (36 weeks), Drafting (36 weeks). Low tuition, low living costs. World famous for technical two-year courses. Those who lack high school may make up work. Students from all parts of the world. 54th year. Enter June, September, January, March. Write for catalog.

1677 College Ave. Angola, Ind.
TRI-STATE COLLEGE

CORWICO
On broadcast as well as shortwave frequencies, in any location, you can eliminate "man-made" static with
NOISE MASTER
ALL-WAVE ANTENNA
Send for complete literature.
CORNISH WIRE CO., 30 CHURCH STREET, NEW YORK CITY

Inter-Office Call Systems

(Continued from page 11)

master unit can be used either in a multiple arrangement or it may be employed with the "Call and Reply System" where it is used in connection with a number of loudspeakers placed at various points.

The Bullet-Phone

THE Transducer Corp. announces three new call systems offering the advantages of 2-way, and multi-station communication. The "Bullet-Phone" unit (see No. 7) functions both as a loudspeaker and microphone. It is modern in appearance and it takes up less space than the regular telephone instrument. The amplifier is compactly designed and can be mounted on the wall or on the side of the desk the same as a telephone bell box. The number and type of tubes employed include one 6J7, one 25L6 and one 25Z6. The manufacturer advises that conversations over the "Bullet-Phone" may be carried on in a normal tone of voice with the instrument placed anywhere on the desk. Its directional characteristics reduce to a minimum such background noises as typewriters, adding machines, etc.

Features Quality Reproduction


THE Operadio model 135 call system (see No. 12) employs connecting wires between stations and is designed to operate from 110 volt alternating or direct current. The response of the amplifier is so designed as to complement the frequency response of the speaker when used as a microphone, as well as a speaker, so that the overall result, as far as quality is concerned is the same as when using a separate microphone in conjunction with any good P.A. system.

The Operadio model 111 paging system (see No. 8) is designed especially for use in factories, hotels, public buildings, etc. The system is supplied complete with contact type crystal microphone, a special amplifier which mounts on the wall at some convenient place near the microphone; a foot switch for use when talking; and four permanent-magnet dynamic speakers in attractive steel wall cabinets. Speakers are connected in parallel through a two wire system.

Can Handle Ten Stations

NO. 16 shows the new Webster Company's model OCM inter-office communication instrument. This is a multiple system designed to accommodate up to ten stations. It features a circuit arrangement whereby a number of simultaneous conversations can be carried on at the same time. The instrument is housed in a strikingly-attractive, highly-polished, wooden cabinet with an ebony finish. They make four different models all operating from either alternating or direct current and employing connecting wires between sub-stations.

NO. 16

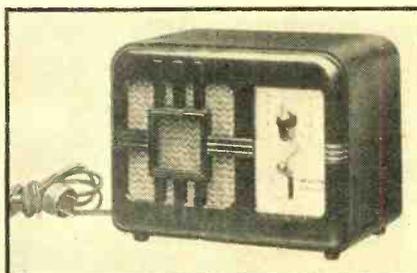

NO. 17

Unusual interest has been displayed in their new factory call system. No. 17 shows the operator seated at the switchboard and communicating to the different departments.

Operates from Alternating or Direct Current

THE Wholesale Radio Service Company's "Auburn" intercommunication systems (see No. 11) feature easy installation, simple operation and attractive appearance. Both systems furnish an efficient and fast means of holding direct 2-way amplified communication between two or more persons or departments. The selective system offers direct communication with any one of five different points, or with all five simultaneously. The second, a "common call" system is similar to the selector type of system, except that it does not incorporate a selector switch. Also, it is limited to the addition of three additional sub-stations, as compared to five in the selector system. Both systems are of the wired type. Completely assembled cables with plugs are available in 50 foot or 100 foot lengths.

"Duo-Matic"


THE Dictograph Products Company, pioneers in the inter-communication field, announce the Duo-Matic call-system featuring loudspeaking, simultaneous 2-way communication. It operates 8 to 12 months on a few dry cell batteries, uses current only when operating, is silent when not in use and all staff stations may call the master station at any time promptly and privately. This system is really telephone equipment. (The master station and the staff telephone hand set are shown in Nos. 13 and 14). This company is also producing a call-system for use in trailers. With this instrument the driver can talk and listen without taking his eyes off the road or his hands from the wheel.

P.D.Q. Two-Way System

THE new Turner inter-communication system (see No. 15), furnished complete with simple diagrams and instructions, is designed to be installed in a few minutes time. A 2-station system consists of one automatic central unit, two walnut station cabinets and the necessary plugs, tubes, and hook-up wire. Additional stations can be added at any time, as no changes are necessary in the original system.

"Intercommunicator"

THE new Sound Systems, Inc., "Inter-communicator" call-system (see No. 18) is designed along ultra-modern lines to harmonize with modern desk accessories. It

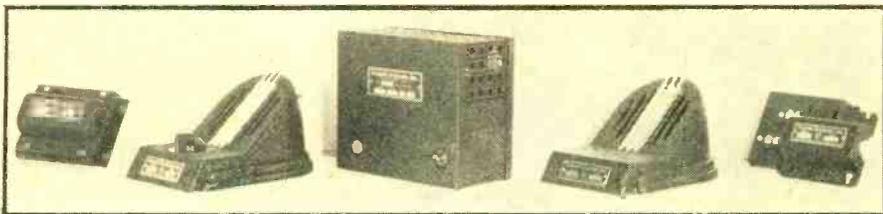

NO. 18

is no larger than the ordinary telephone set. The combination speaker microphone unit is enclosed in a small aluminum casting 4 by 5 by 7 inches mounted at a 45-degree angle. The Intercommunicator is so designed that from 1 to 18 units may be used with one central amplifier. This system uses connecting wires between stations.

Communo-Phone

FIVE different models, three "wired" and two "wireless" type complete the Bogen "Communo-Phone" series of call systems. All models operate from either 110 volt direct or alternating current. The model 5SC station (see No. 10) houses a 4-tube amplifier and is provided with selective controls to enable conversation with any or all of the other stations on the system, either independently or simultaneously. The tubes used are: one 6J7, one 6C5, one 25A6, one 25Z6 and 1-25 watt, 120 volt bulb.

Information from the manufacturer points out that the model 5W system, (a wired-wireless type) has an external control which permits frequency selection so that several systems may be used independently in the same building. A 6-tube unit is used in each station and communication is possible between points over 1000 feet apart. They further advise that no jumper condensers are required at fuse boxes, even though stations are operating from entirely different branches of the power line.

"Vocophone"

THE Miles Reproducer Company, Inc. specializes in all kinds of communication



equipment. Their "Vocophone" (shown in No. 19) and "Socket-Phone" systems are available for multiple station operation with and without inter-connecting lines. They work from either alternating or direct current. A control is provided at each master station for volume and tone adjustment. This company also manufactures portable private phone systems, 1-way announcing systems, and paging systems, for hotels, restaurants, etc.

Specialists in Communication Systems

The "Teletalk" line of inter-office communication equipment made by the Webster Electric Company includes selective type

systems, master station models, paging systems, and confidential models to afford privacy in conversation. They feature a new circuit arrangement to reduce line current drain whereby the tube filaments are kept hot and the high voltages are used only when talking.

"Talk-Bak"

The Wright-DeCoster Company, Inc., well known loudspeaker manufacturer, has just introduced a special 5-inch "Nokoil" speaker, for combination use as a microphone and speaker with all kinds of inter-




communication systems. The "Talk-Bak" speaker, as it is known, is shown in a suggested type of cabinet. This company is in



a position to supply schematic diagrams, including information regarding the equalizer, the suggested type of amplifier and several different types of "Talk-Bak" installations.

"Cal-Fon"

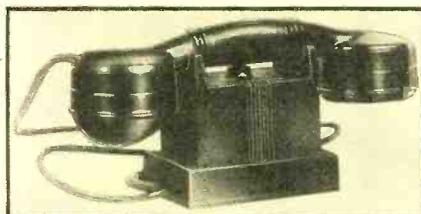The Universal Microphone Company introduces the "Cal-Fon" private phone system. The assembly constitutes a complete French hand-set. The housing also contains the buzzer, and the transformer, so that any number of phones can be used on one circuit by coding the rings for the office or individual being called. The system operates



on four dry cells or one 6-volt battery. This company will also adapt the new type of "Cal-Fon" for use on automobile trailers with the new model used for installation in the trailer itself, and an inter-communicating phone in the driver's compartment.

"Port-A-Fone"

The Electronic Devices, Inc., announce a new inter-communication system called the (Turn to page 62)

IT HELPS ME
ON ALMOST
EVERY JOB!

Are you one of the thousands of service men getting help from the new Sylvania Technical Manual? Get on the "band wagon" now!

If you knew how many thousands of service men are using this new Sylvania Technical Manual on almost every job—you'd realize what a whale of a value it is for 15c!

This handy pocket manual contains 184 pages listing 193 tube types with important circuit application information on each—all about glass, metal and "G" type tubes as well as those for Majestic receivers... and full information on Sylvania "Ballast Tubes". Don't be without it! It's one of the handiest tools you could carry! Send the coupon and 15c—we'll do the rest.

SYLVANIA

SET-TESTED RADIO TUBES

Hygrade Sylvania Corporation, Emporium, Pa. RN-77

I enclose 15c, for which please send me a copy of the new Sylvania Technical Manual. I am (check below).

Experimenter ; Amateur ; Call ; Serviceman ; Employed by dealer ; Independent Member Service Organization.....

Name

Address

City..... State.....

Name of jobber.....

Address

AUTO RADIO
WITH
Safety Tuning

See this amazing new G-E Auto Radio with Automatic Frequency Control. You concentrate on driving the car while this G-E Auto Radio model practically tunes itself for perfect Focused Tone reception.

**MANY EXCLUSIVE FEATURES
SUPER-PERFORMANCE
EASILY INSTALLED**

"Custom-built" Controls for all makes of cars

**GENERAL ELECTRIC
AUTO RADIO**

THROUGH THE
EYES OF AN
ENGINEER!"

"LOOK

Do you have a thorough working knowledge of the operation of modern equipment with new types of circuits and vacuum tubes? The CRFI home-study course in Practical Radio Engineering enables you to look at a transmitter or receiver with the eyes of the engineers who design them, so that you can fully appreciate the results they are trying to obtain and realize the possibilities and limitations. CRFI can give you the ability to progress from the mechanic stage into the ranks of trained engineers. A post card brings you all details.

FREE!
New illustrated
Tested Plan for a
Future in Prac-
tice "Engineering," on re-
quest.

RIGHT NOW -- WRITE NOW!

CAPITOL RADIO ENGINEERING INSTITUTE
Dept. RN-7, 14th & Park Rd. N.W., Washington, D.C.

**TOUGH RADIO JOBS
DON'T STUMP ME
I SOLVE ALL MY PROBLEMS WITH
KINK-AIDS**

More than 3000 filed and indexed service kinks to repair those hard-to-fix home and auto radios. Just pull out the card corresponding to the name and model of the set you are repairing, and there you have listed the service troubles found in that radio and how to fix them.

\$1.95

Sent complete with metal box, only.....
FREE—Write for Bulletin RN-7 and sample cards.
AKRAD PRODUCTS COMPANY
362 Wooster Ave. Akron, Ohio



200 Meters And Down
CHICAGO, ILL.—The illustration shows a scene in the studio of WMAQ, NBC station, during one of the Saturday Midnight dramatizations of important events in amateur radio. The programs were sponsored by William J. Halligan, W9WZE, president of The Hallicrafters, Inc. They were built from material in DeSoto's book, "200

Meters and Down," and from records in the files of the A. R. R. L. The scene illustrated here was a re-enactment of the holdup of Dr. Philip Weintraub, W9SZW, a prominent Chicago dentist and amateur radio operator. Dr. Weintraub was saved due to the presence of a transmitter in his office. Seated all the way at the right is the sponsor, Mr. W. J. Halligan.

5-Meter Converter

(Continued from page 23)

box of similar size will serve. Considerable time and trouble will be saved if the unit is made on a standard chassis, with standard panel and cabinet. The r.f. socket is mounted on the partition between the i.f. and detector compartments. The detector and oscillator sockets are mounted on the chassis. The detector plate lead is thereby isolated from the r.f. circuits.

The alignment of this unit is not difficult. Connect the output terminals to the input terminals of the receiver to be used as the i.f. amplifier with twisted pair. Tune the receiver to 1,600 kilocycles. Now adjust the output transformer trimmer on the converter for maximum noise (hiss). This "hiss" is generated in the 954 converter plate circuit. The best method of aligning the detector appears to be as follows:

1. Connect an ordinary buzzer to a battery and place it somewhere near the converter.
2. Vary the detector trimmer until the noise is at maximum. Make sure the detector is on the low frequency side of the oscillator. (If the detector blocks as you decrease the trimmer capacity from the point of maximum noise you are on the low frequency side.) Do the aligning in the middle of the band.
3. The r.f. tuning is not ganged and therefore no trimming is necessary.

This converter has been tested on several types of receivers and the following facts have been observed:

1. The ideal receiver to use as an i.f. amplifier would include such features as variable selectivity, good a.v.c. action, a good tuning or "R" meter, automatic frequency control on its own oscillator and a manually adjusted noise silencer.
2. Tests made on the Hammarlund Super-Pro as an i.f. amplifier indicated that maximum selectivity (about 3 kc. band width) could be used with ease on crystal controlled signals in the five-meter band. The variable selectivity feature of this receiver allowed its use on good M. O. P. A. signals and well adjusted rod oscillators.

3. The use of a receiver with automatic frequency control simplified tuning tremendously as it held on to signals which drifted out without the control in use.
4. The signal to noise ratio was superior (regardless of the receiver used as the i.f. channel) to any 5-meter receiver yet tested by the author.
5. When using the Super-Pro, c.w. signals from crystal-controlled 5-meter transmitters as well as commercial harmonics were copied with ease.
6. If greater band width is required, to permit understandable reception of some of the less stable transmitters, a t.r.f. receiver will serve well as the i.f. portion. Such sets may be picked up today for a song. They will not, however, allow maximum selectivity on stable signals.

In conclusion, I feel a final word of warning is in order. This is an advanced piece of 5-meter equipment and only the advanced amateur should tackle it. Units made from the same set of plans by different people will often differ in performance. The advanced "ham" can easily correct the discrepancies himself. The novice is not in a position to do this.

List of Parts

- C1—50-100 mmfd., midget variable condenser
- C2, C3, C4—20 mmfd., midget variable condenser
- C5, C7,—3-30 mmfd., midget mica trimmer condenser
- C6—150 mmfd., mica trimmer condenser
- C8—.005 mfd., 200 volt, paper condenser
- C9—included with National XMA socket
- C10, C13, C15, C16—.00025 mfd., midget mica condenser
- C11—.005 mfd., paper condenser, 400 v.
- C12—.05 mfd., paper condenser, 200 v.
- C14, C19—.01 mfd., paper condenser, 400 v.
- C17, 18—dual 8-8 mfd., 400 v., electrolytic condensers
- L1—7 t., spiral wound No. 18 push-back wire, dipped in Duco cement
- L2, L3, L4—7 t., 1/8 inch diam., spaced 2 X diam., No. 16 tinned copper wire
- L5—National R-100 r.f. choke
- R1—1500 ohms, 1/4 watt
- R2, R4—100,000 ohms, 1/2 watt
- R3—2000 ohms, 1/4 watt
- R5—50,000 ohms, 1/4 watt
- R6—20,000 ohms, 25 watts
- R7—2000 ohms, 10 watts
- R8—150,000 ohms, 1/2 watt
- T1—small power transformer, 300 v. each side e.t., 6.3 v. fil. winding
- T2—1600 kc., transformer (See text)
- S1—snap switch
- VT1—954 acorn pentode
- VT2—954 acorn pentode
- VT3—955 acorn triode
- VT4—5V4 rectifier

Auto Radio Servicing

(Continued from page 13)

in this article to indicate more than a handful of typical conditions. The individual serviceman should experiment with the types of auto radios which he will be called upon most often to service. The general procedure will be the same in all cases.

Connect the high side of the vertical plates in the cathode-ray oscilloscope, through the usual amplifier, to one side of the primary of the power transformer. Connect the ground side of the oscilloscope to the chassis of the auto radio receiver. Adjust the amplifier gain control for satisfactory vertical deflection, and the horizontal sweep circuit for synchronization at one-half or one-third the vibrator frequency to obtain two or three waves on the screen.

If difficulty is experienced in obtaining a stationary image, this is *prima facie* evidence of vibrator trouble. Two types of moving wave-forms may be experienced. Voltage fluctuations will show vertical instability, as indicated in the oscillogram of Figure 4. This is an RCA synchronous vibrator with burned rectifying points. Frequency instability will be evident in an erratic horizontal movement of the pattern, and will usually be caused by dirty or burned vibrator points.

The technique of experimentation should be carried out as follows: First investigate the wave-form of a perfect vibrator. Using an Arvin 17A, the vibrator curve, if in perfect condition, will appear on the screen as indicated in Figures 1, 2 and 3, and as in "a" of Figure 5. Bend one stationary contact so that it is at a greater distance from the operating reed. This may alter the frequency slightly, necessitating resynchronization. Note the distortion produced in the curve. Press the contact too close and again observe the curve. Resetting the operating contact to its normal position, make similar tests with one of the rectifying contacts—in the case of a synchronous rectifier. Contacts can be opened by inserting a piece of paper between vibrating and stationary contacts. Remove the buffer condensers—two .02 mf. condensers with a common ground in the case of the Arvin. Note the wave-form. Replace one condenser and again observe the pattern on the screen. A further observation should be made with excess capacity buffers. *During this experimenting, remember high voltage is developed in the secondary circuit, so take care to avoid shocks.*

Most of these tests can be effected with the suggested oscilloscopic connections in the primary power circuit. Where the secondary circuit is affected, the load variations will be reflected in the primary circuit, thus making a change of set-up unnecessary, and facilitating the work of routine servicing.

Returning to Figure 5: Oscillograms "a" through "h" were made on the Arvin. Curve "b" shows one contact too close; "c", the other contact too close; "d", one contact open; "e", no buffer condensers; "f", one buffer condenser; and "g" shows too much buffer capacity. At "h" is shown the output of the 84 with the filter connected, but observed on the tube side of the filter. Figures 5-i-j-k-l were made with a Philco non-synchronous vibrator under different conditions, showing correct and maloperation. Oscillogram "i" indicates correct adjustment; "j" with the

Designed to Withstand
**ROUGH
FIELD
SERVICING**
**RANGER
EXAMINER**



MODEL 740

PRECISION
BUILT
\$1860

● FOR THAT DUPLICATE SET OF SERVICING INSTRUMENTS ADVOCATED BY LEADING SERVICEMEN

● Model 740 Volt-Ohm-Milliammeter has 3" Square Triplett Precision Instrument. Scale readings: 10-50-250-500-1000 A.C. and D.C. Volts at 1000 Ohms per Volt (D.C. Accuracy 2%; A.C. 5%); 1-10-50-250 D.C. M.A.; 0-300 low ohms; High Ohms to 250,000 at 1½ Volts. (Rheostat adjustment for 13½ volts for Ohm readings to 2½ Megohms.) Batteries may be added permitting such readings in 250,000 ohm steps. Low Ohms to ½ Ohm with 25 Ohms in center of scale. Backup circuit used. Current draw is only 1 M.A.

VOLT-OHM-MILLIAMMETER NO EXTRA CASES TO BUY

Readrite Meter Works
715 College Dr., Bluffton, Ohio
 Please send me more information on Model 740.
 I am also interested in.....
Name.....
Address.....
City..... State.....

One Dime Brings You The Valuable 1936 RADIO DATA BOOK

This large 8" by 11" book—with over 120 illustrations, charts and hook-ups—has 48 pages crammed full of information of value to every radio man. It includes constructional details for the RADIO NEWS Trap-Circuit Tenatuner, Short-Wave Converter and Ultra-Sensitive V. T. Voltmeter—how-to-build articles on short-wave receivers, amateur transmitters, and servicing instruments—many hints and kinks for radio experimenters—reception aids for short-wave fans—and plenty of other worthwhile information and valuable charts.

Get Your Copy Now!

Over 14,000 copies of this book have already been distributed and only a limited supply remains. Make sure you get a copy by sending 10c (Canada & Foreign 15c) today!

Dept. 377a

Radio News

461 Eighth Ave. New York, N. Y.

Train for ELECTRICITY IN 12 WEEKS AT COYNE

The Big Coyne Shops in Chicago have a world-wide reputation for training ambitious fellows for their start in this big-pay field in only 12 weeks. Then you get **lifetime graduate employment service.** By my new plan YOU can take advantage of our wonderful method of learning-by-doing NOW—no need to lose time and money while you strive and save to raise the necessary tuition.

"ARRANGE TO FINANCE YOUR TUITION"

I have a plan where many get training first. Then they have over a year to pay for their training in easy monthly payments starting 5 months from the day they start school. If you will write to me at once I will send you complete details of this sensational new plan, together with the Big Free illustrated Book telling all about COYNE and how many earn while learning and training you can get there without book study or useless theory.



COYNE ELECTRICAL SCHOOL
500 S. Paulina Street, Dept. B7-81, Chicago, Illinois

MR. H. C. LEWIS, President
Dpt. B7-81, 500 S. Paulina St., Chicago, Ill.
Send me all details of your "pay-tuition-after-graduation" plan and your big FREE catalog.

NAME.....
ADDRESS.....
CITY..... STATE.....

PARTS PRICES SLASHED!

Complete stock of fine-quality replacements for Short Wave—P. A.—Ham and Service work at big savings. Why carry expensive stocks? Use our RUSH shipment plan.

BOND RADIO COMPANY
13137 Hamilton Ave., Detroit, Michigan



- ★ Available in ratings from 500 to 7000 v. DC. Capacities of .00004 to .1 mfd.
- ★ 13 types to choose from. Tiny "postage stamp" molded unit to metal-case units, and everything between.
- ★ Popular Type 1455 shown. Ideal for stacking or grouping. Insulated terminals and mounting holes.

DATA: Latest catalog covers a complete mica line as well as other types of condensers and essential resistors. Copy on request.




FREE BOOK of Opportunity
Instructive facts about
TELEVISION
RADIO
SOUND RECORDING
Complete, practical instruction. Earn room and board while learning. Coach railroad fare allowed to Los Angeles.

NATIONAL SCHOOLS
National Schools, Dept. 7-RN,
4000 So. Figueroa St., Los Angeles, Calif.

NAME..... AGE.....
ADDRESS.....
CITY..... STATE.....

NEW 1938 DELUXE MAC KEY

\$9.50
net

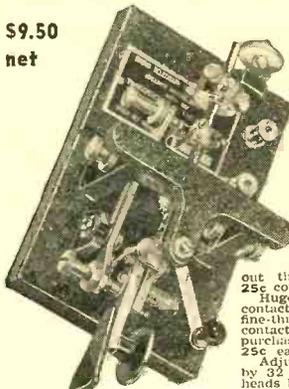

Equipped with my new "dot stabilizer" which is the most remarkable feature ever offered operators on a speed key. (The "dot stabilizer" may be purchased separately for any speed key at 50c.)

Main spring selected as you all know with great care (these main springs likewise may be purchased by unfortunate operators having those "speed keys" that won't work right without the right spring at 25c complete with rivets).
Tuge 3/16th fine silver contacts mounted on 1/4" fine-threaded dot and dash contact screws (may be purchased separately at 25c each).
Adjustment screws 1/4 by 32 screws. All screw-heads knurled and slotted.
Insulating washers, bushings bakelite. Dash

button, dot paddle bakelite. Bearing pins and screws oversized case hardened steel. Note also pigtails for electrical connections instead of depending on bearings.
All parts above base beautifully chromium plated. Same gigantic solid one-piece cast base but how breath-takingly gorgeously finished like a piece of polished black marble with light veins running through.

T. R. McELROY, 175 Congress St., Boston, Mass.

starting contact too close; "k", the other contact too close; "l", contacts too far apart. Figures 5-m and 5-n show respectively a Radiart 3313 replacement for the RCA synchronous vibrator (shown faulty in Figure 4) and a Radiart 3320 replacement in a Philco—normal operation being indicated in both instances.

By synchronizing with the output wave of the filter system, and then connecting the oscilloscope to the output of the set, it can be determined if any "hash" is being fed into the r-f system, and thence to the audio circuits. Sometimes this is not audible as "hash", but is evident as distortion when a signal is being received—the modulated carrier riding the "hash" wave. A modulated oscillator—400 cycles—should be employed in making this test, and the "hash" will be disclosed as a distorted envelope. Radio-frequency chokes in the hot "a" lead and adequate by-pass condensers can then be added to filter the disturbance.

The layout in Figure 3 shows, in addition to the Arvin receiver, a National Union oscilloscope, with the RCA TMV-97-A oscillator at the left. The National Union "wobulator", atop the oscilloscope, is not used in vibrator servicing, but is employed, of course, in lining up both home and auto radios.

V-T Voltmeter

(Continued from page 15)

rise to a value that would endanger the meter. During measurements the switch is kept closed.

When measuring d.c. or low-frequency a.c. it is most convenient to have the 75 tube plugged in the panel socket. For r.f. measurements, however, the cap of the 75 tube must be brought to the point where the voltage measurement is desired. This is accomplished by using the goose-neck adapter, shown in the photograph of the instrument.

The adapter consists of a 6-wire cable terminating at one end in a 6-pin tube cable connector socket. Each cable lead from the tube base connects to the corresponding panel socket prong. In addition, a .05-mfd., 400-volt condenser, connected with as short leads as possible between the cathode and plate prongs of the cable connector socket, is required to keep the 75 tube from oscillating at some ultra-high frequency.

No detailed constructional data will be given, since every constructor will have his own idea of the proper layout and mechanical construction, and there is no reason why these personal preferences should not be indulged as long as the constants of the individual parts are not changed. For this reason, also small hardware, chassis parts, tube sockets, etc., are not specified on the parts list.

The accuracy of measurement will depend on the accuracy of the reference voltmeter so that it will pay to obtain a high-grade instrument and accurate multiplying resistors for this purpose. However, the values of the condensers and other resistors specified are not critical. It is essential that the paper dielectric by-pass condensers have very low leakage.

Before the vacuum-tube voltmeter can be used, it must be properly balanced to obtain the proper bridge action. No difficulty will be encountered if the following procedure is used:

1. Turn the balance indicator sensitivity switch (SW3) to "Low." This connects the 30,000-ohm resistor (R6) in series with the milliammeter and prevents the possi-

bility of damage from excessive current during the balancing operation.

2. Short input to voltmeter by clipping ground lead to cap of 75 tube.

3. Plug in the power cord, turn on the instrument and allow it to warm up for at least one minute.

4. Set bias-selector switch (SW1) to point 2 (0-10 v. range) and turn potentiometer 1 to the 10-volt position.

5. Turn switch 3 to "High."

6. Adjust bridge balance control (P6) until balance indicator reads 0.

7. Return balance-bias selector switch (SW2) to position 1 ("0" bias voltage).

8. Adjust voltmeter tube bias (P5) until a reading of approximately 1/10 ma. is obtained on the balance indicator. This adjustment is not critical. If difficulty is found in reducing the plate current to .1 ma., try another type 37 tube. Some have "remote cut-off" and are unsatisfactory for this purpose. The instrument is now ready to be used.

When connecting the voltmeter it must be remembered that a d.c. path must be provided to close the grid circuit. In measuring across coils and resistors, the return path can be the voltage source. On the other hand, when measuring a.c. voltages through a capacity, as would be required for eliminating the d.c. component in a circuit where both a.c. and d.c. are flowing, or because of the nature of the circuit, a separate d.c. path must be provided. This can easily be accomplished by connecting a high resistance (2 to 5 megohms) between the 75 tube cap and the voltmeter ground wire. The ground wire should also be attached to the low-potential point of the circuit. When measuring d.c. voltages, the 75 grid cap connects to the positive side of the voltage source, the voltmeter ground to the negative.

Using the Vacuum-Tube Voltmeter

Where approximate value of voltage is known:

1. Set reference voltmeter range switch (SW1) at a point sufficiently high to cover the maximum voltage which might be encountered (i.e., to measure a voltage having a value between 25 and 50 volts, set the reference voltmeter range switch so that 50 volts can be measured).

2. Set the bias selector switch (SW2) to cover the desired range.

3. Connect the vacuum-tube voltmeter input leads across the voltage source to be measured.

4. Slowly retard bias potentiometer until indication is found on balance indicator, and pointer returns to a position between 0 and the original setting, 1/10 ma.

5. Read peak voltage as indicated on reference meter.

Where voltage to be measured is unknown:

1. Set SW1 to highest position.

2. Set SW2 to highest position.

3. Slowly retard bias potentiometer 4.

4. If no indication of null point is found, move back one position on both the reference voltmeter range switch and the bias selector switch. Then, slowly retard bias potentiometer 3, noting balance indicator action. If no indication is found, repeat these operations on each preceding range until the null point is found. Then read peak voltage on reference meter.

Detailed notes on applications will appear in an article to follow.

Parts List

C1, C2—Mallory HS693 8 mfd., 600 v. condensers
C3, C4—Mallory RN242 8 mfd., 450 v. condensers
C5, C6, C7—Mallory TP443 1 mfd., 200 v by-pass condensers
C8—2 mfd. 600 v. paper dielectric condenser
CH1, CH2—Midget filter chokes, 12 to 30 henry, 35 ma.

- CT1, CT2—Yaxley 864C center-tapped resistors, 64 ohm
 - P1—Yaxley M1MP 1,000-ohm linear wire-wound potentiometer
 - P2—Yaxley M4MP 4,000-ohm linear wire-wound potentiometer
 - P3—Yaxley M20MP 20,000-ohm linear wire-wound potentiometer
 - P4—Yaxley M25MP 25,000-ohm linear wire-wound potentiometer
 - P5—Yaxley M1MP 1,000-ohm linear wire-wound potentiometer
 - P6—Yaxley M70MP 70,000-ohm linear wire-wound potentiometer
 - R1—100,000-ohm 1 watt carbon resistor
 - R2—10,000-ohm, 10 watt wire-wound resistor
 - R3—250,000-ohm, 1 watt carbon resistor
 - R4—1,000-ohm, 5 watt wire wound resistor
 - R5—25,000-ohm, 5 watt wire wound resistor
 - R6—30,000-ohm, 1 watt carbon resistor
 - R7—10,000-ohm, 5 watt wire-wound resistor
 - R8—10,000-ohm, 5 watt wire-wound resistor
 - SW1—Yaxley 1316 single-circuit 6 point switch, with type 374 dial plate
 - SW2—Yaxley 1316 single circuit 6 point switch with type 375 etched dial plate
 - SW3—Yaxley midjet jack switch No. 10
 - SW5—On-off switch for 110 volts
 - T1—Power transformer, midjet receiver type: pri. 115 v 60 cycles, secondaries 700 v., c. t.; 5 v. at 2a.; 6.3 v. at .3a
 - T2—Power transformer, midjet receiver type, pri. 115 v. 60 cycles, secondaries 600 v., c. t.; 5 v. at 2a.; 6.3 at .3a
 - 2 Milliammeters, 0-1 ma.
- One set of resistance multipliers for one of above meters to give voltage readings with the following ranges, 0-10 volts, 0-50 volts, 0-250 volts and 0-500 volts. If desired a high-grade three range 0-500 volt high resistance voltmeter can be substituted for one of the milliammeters and the set of multipliers
- 1 type 75 tube
 - 1 type 37 tube
 - 1 type 80 tube

Television Operators Wanted

(Continued from page 15)

the human organ of sight is essential. The eye is very complex, but all future developments and improvements will undoubtedly be based on this organ. All of the properties of the eye should be studied, with particular attention to the *persistence of vision*, the secret of television and motion pictures.

The future engineer or operator must also have an extensive knowledge of optics, lenses, and the properties of light. He must be familiar with the electron theory, and electronic properties and action, as correlated with the structure of matter. He must be well-grounded in the elements and principles of electricity and radio.

All of these underlying principles are basic fundamentals of television, and must be thoroughly understood. With these principles in mind their direct application to television can be specifically defined.

The future television engineer and operator must have an extensive knowledge of audio- and video-amplifiers, including a comprehensive understanding of their related circuits. He should be familiar with commercial electron tubes, and practical commercial amplification and attenuation circuits. He must be well-versed in the use and operation of the photo-electric cell. Since all television transmission will be accomplished with the very short waves, a thorough understanding of radio-frequency transmission with ultra-high-frequency oscillators is very necessary. The operator should be familiar with the theory, operation and use of the cathode-ray tube in modern installations.

It is generally believed that television in the future will take place through non-mechanical, non-moving circuits. Experimental receivers now being prepared by two leading set manufacturers have no moving parts, or scanning discs. However, it would be desirable to have a knowledge of the scanning disc, electric motor, and associated equipment. Synchronization in

television is very important. This is performed either by use of motors, or by "relaxation" circuits designed for this work; both methods should be familiar to the television operator or engineer.

Much of the early television broadcasting will be done by means of the motion-picture. This will be necessary because of the radical change imposed upon commercial broadcasting and the adaptability of the motion-picture to television transmission. Therefore the television engineer or operator should be familiar with the operation, use, and care of commercial motion-picture projectors and their related use to television.

A study of the Kerr Cell should also be considered. This important, though little-known, tube is used for obtaining large clear-white images, by action of the polarizing light which is in proportion to the impressed magnetic signal.

The potential television engineer, technician, operator or serviceman should keep constantly in touch with all new developments in the television field, through leading radio magazines and technical journals. Experimentation with television probably leads all other fields of research at the present time, and it is highly necessary to be well informed on new developments. It would be wise to construct and experiment with all types of smaller television receivers and transmitters, in order to become familiar with their operation, peculiarities and characteristics.

When television does arrive commercially it will be on a large scale and there will be an ever-increasing demand for competent, efficient, trained engineers, operators and technicians. The trained man will find himself very much in demand only if he has been well-trained and is thoroughly familiar with the various phases of television. There is probably no one technical school, college, or other institution where all of this necessary training can be obtained. Only by patient personal study and application can the future engineer or operator completely master the many diversified complexities involved in the transmission and reception of television radio signals. Television will revolutionize broadcasting and radio transmission and reception. The industry will eventually discover that it has a large demand for competent men, but a very small supply actually existing.

P. A. Equipment

(Continued from page 19)

The chief feature of this new amplifier is in the use of a "reverse or negative feedback circuit," which permits high-power output with minimum distortion and improved frequency response. This circuit is the latest method for achieving these results.

Automatic equalization made possible by the negative-feedback circuit, is a means whereby the gain of the amplifier is automatically controlled so that amplification of various frequencies is compensated for, according to their strength.

The circuit, shown in Figure 1, consists of five stages, using two 6J7 type tubes as voltage amplifiers, one 6N7 for the mixer stage, one 6N7 as a phase inverter and driver tube, and two 6L6's for the output stage. A type 5V4G is employed for rectification.

The frequency response of the amplifier is rated 1 db. from 50 to 10,000 cycles. The technical specifications show the maximum available gain to be 138 db. (with 5 megohms. input) and the rated output into a 500 ohm. line, 20 watts, and peak power output, 30 watts.

Top Quality - ALWAYS!



You take no chances with Raytheon tubes. When you make a replacement with Raytheons — you can forget them! Every Raytheon tube is top quality! Every one is precision engineered... built to give clear, true-toned reception, and extra long life. They won't bounce back! And every customer will be a permanent satisfied customer.

Because of their top quality, you'll find Raytheons practically everywhere! In U. S. Army, Navy and Aviation Communications. In major broadcasting chains. In thousands of amateur radio transmitters and receivers. In millions of home radio sets as original equipment. In leading auto radios, because of their sturdiness, uniformity and ability to withstand continuous shocks and rough usage. On thousands of dealers' and servicemen's shelves... and so on down the line.


So — when you handle or use Raytheons, you're not only in good company — but you know you're taking no chances.

ASK YOUR JOBBER



RAYTHEON PRODUCTION CORPORATION
 420 Lexington Ave. 55 Chapel Street
 New York, N. Y. Newton, Mass.
 445 Lake Shore Drive 555 Howard Street
 Chicago, Illinois San Francisco, Cal.
 415 Peachtree St., N. E.
 Atlanta, Ga.

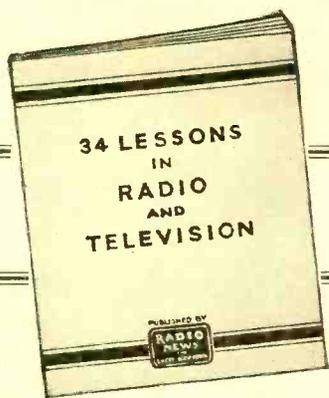RAYTHEON IS THE MOST COMPLETE LINE—ALL TYPES OF GLASS, OCTAL BASE, METAL, RESISTANCE AND AMATEUR TRANSMITTER TUBES.



10,000 RADIO MEN

Can't Be Wrong!

Ten thousand radio men already have copies of "34 Lessons In Radio and Television"—and they praise it highly! You, too, will want a copy! It guides you, in easy-to-understand language, from the fundamentals of radio and electricity to the intricate problems involved in constructing modern radio receivers. It covers radio from crystal sets to television! And you can get a copy free!

List of Contents

This book tells you how to build crystal, diode, triode, regenerative and tuned radio-frequency receivers and includes lessons on: Electricity—Vacuum Tubes—Radio Waves—Radio Symbols and Circuits—R. F. and A. F. Amplification—Regeneration—T. R. F. and Superhets—Automatic Volume Control—Antennas—Photocells—Learning the Code—History of Television—Scanning-Disk Television—Cathode-Ray Tubes—Cathode-Ray Television—Television Receiver Design—and Present-Day Television. It is crammed full of valuable reference data and worthwhile information.

Our Special Offer

Place a new or renewal subscription today for 11 issues of RADIO NEWS at only \$2, and we will send you "34 Lessons In Radio and Television" FREE! Act now—the supply is limited!

Mail This Coupon Now!

RADIO NEWS, Dept. 377
461 Eighth Ave., New York, N. Y.

Enclosed find \$2. Send me RADIO NEWS for 11 months and rush a copy of "34 Lessons in Radio and Television" to me free of charge. (Canada and Foreign \$2.50).

Name.....
Address.....
City..... State.....

(If a Radio Serviceman, check here)

The amplifier is equipped with four input channels, two of which can accommodate any of the low-level high-impedance microphones, including the "Velotron" and "Velophone" types, as well as photo-cells input devices. The input circuit also has provisions for a radio tuner or phonograph pick-up. Complete mixing and fading facilities are provided whereby any two or four inputs can be mixed at a time.

A feature that will prove popular is the new "Neo" illuminated dial. Up to now it has never been practicable to watch, on a darkened stage, the adjustment of volume and tone control settings, and have the audience unaware of what was being done. The necessity for throwing light against the control dials, in order to see them, made it difficult to operate according to cues pre-determined at rehearsal, and still preserve that illusion of effortless ease which is the basis of good showmanship. The new Neo-dials, however, glow too dimly to be visible when the amplifier is placed back to audience, yet shine with a bright neon red to be easily seen by an orchestra leader or other person who faces them. Thus the leader, or master of ceremonies, or drummer if desired, can operate this small but powerful amplifier in full view of the audience, without the audience knowing there is an amplifier on the stage at all.

Twenty-four watts of field excitation are available for several speaker fields, the resistance of which totals 5000 ohms. Versatility in use is increased by a wide range of voice output impedance, running from 35 to 500 ohms., and including eleven choices of impedance within that range.

The dimensions of the amplifier are 6¾ by 8¾ by 17 inches, and its shipping weight is 30 pounds.

Closet-Door Work Bench

(Continued from page 33)

panel, even with the edges, extending 3 inches below the bottom. The top and bottom are 3 inches wide by 19½ inches long and fit between the sides, just even with the back edges. To have a firm support for the drop-leaf hinges, a piece of pine 2 inches by 3 inches by 19½ inches is fastened between the extended sides at the bottom.

To reinforce the plywood table-top a rectangular frame, made from 1 by 2 inch pine is attached to the underside. The legs are made of hard 1½ by 1½ inch pine and hinged to this frame with card-table hinges. A piece of 3-ply veneer, 12 inches high is fastened across both legs to reinforce them and prevent wobbling. Adjustable screw type levels are countersunk into the bottom of the legs to compensate for uneven flooring.

The bench-top is covered with Good-year rubber flooring which is thoroughly cemented down to prevent bulging when the lid is closed. The entire edge of the bench is finished with 1 inch wide flat moulding. Two strong, flat, inside-shutter hooks are placed near the top of the sides to hold the lid closed, while the legs are held folded in place inside the lid frame by means of two brass turn-buttons. The most suitable lid hinges are the refrigerator door type. Wood screws are used exclusively in the assembly of the cabinet so as to insure greatest strength.

The cabinet is a complete assembly in itself and is attached to the heavy part of the door by six long wood screws. When it is desired to remove the cabinet to an-

other location it is only necessary to take out these six screws and the entire unit is then portable. Five convenient outlets are wired along the three outer sides of the lid frame, current being secured through a heavy flexible cord from a base outlet in the closet.

When the bench is opened to working position it is directly in front of a window. Ample light for night-work is available from an adjustable lamp which also folds out of the way against the closed cabinet. Clips are used to hold all handle-type tools, while others hang from rods or hooks. Two standard drill-stands accommodate a full set of twist drills. A pair of hinged 1 by 2 inch pine arms fold out of the open cabinet and are drilled with holes to hold an assortment of files and small tools.

The completed cabinet and Work Bench has proven so practical that several of my friends copied the design with slight modifications to suit their own special requirements. In one case several drawers were added, while in another the cabinet has been made deeper to accommodate an amateur receiver and transmitter. The basic idea of design can be altered to suit any individual requirement and to provide for a personal working space in the smallest of homes.

Empire State Television

(Continued from page 8)

tion. The difficulties of making apparatus function outside the laboratory are being surmounted. The technical fundamentals of our system have been confirmed. Theory has been put into practice, and the experience gained thereby is enabling the laboratories to chart the needs of a practical television service.

"A major problem in television is that of network program distribution. The present facilities for distributing sound broadcasting cover the vast area of the United States and serve its 128,000,000 people. Similar coverage for television programs in the present state of the television art would require a multiplicity of transmitters and network interconnections by wire or by radio facilities still to be developed.

"The field tests are not completed, but the capabilities of the RCA television system are being constantly expanded, and we are moving toward ultimate realization of satisfactory high-definition television for public service."

In addition to the technical phases of television progress, NBC has been concerned with program development for the sight-and-sound shows that may soon be a commonplace on the airlines. Continuity, make-up, costuming and other important production phases are being experimented with so that there will be no "guinea pig" era when the commercial launching of the new art takes place.

Miss Betty Goodwin, formerly of the press department, has been named the network's first "regular television announcer."

(Editor's Note: The audio and video signals from the Empire State are regularly received up through Connecticut and as far as Massachusetts, by amateurs, according to a representative of RADIO NEWS who interviewed many amateurs at a recent Amateur Convention in Middletown. At times when DX conditions prevailed on the ultra-high frequencies these signals came in with tremendous volume, exceeding that of locals. Just what this means in terms of interference between television

stations using frequencies in other cities remains a question of controversy.)

The following bibliography is appended for those readers anxious for popular and technical research on RCA-NBC television progress:

"Television." RCA Institute Technical Press. July, 1936.

"Television Radio Delay." RCA Review. October, 1936.

"Equipment Used In the Current RCA Television Field Tests." RCA Review. January, 1937. (This issue also contains other relative papers.)

"Seeing's Believing." RADIO NEWS. July, 1936.

"The Next Ten Years Will Be Television." RADIO NEWS. February, 1937.

The Radio Beginner

(Continued from page 36)

$\frac{3}{8}$ -inch shaft will need a shaft reducer if the dial is for a $\frac{1}{4}$ -inch shaft. The batteries are simply fastened with wood screws with insulated wires. The filament leads are soldered to the flashlight cells. First file or sandpaper a clean spot on the battery terminals, then tin the spot, tin the wire, and solder the wire to the batteries. Do not heat the batteries too much.

Calibration

When the wiring is finished, it is necessary to calibrate the oscillator. The broadcast band can be calibrated by comparing with broadcast stations, picking up both the broadcast station and the oscillator on a receiver. Set the oscillator somewhere in the room (no connections needed), tune in a broadcast station of known frequency and turn the dial of the oscillator until it too is heard. When the oscillator signal is broad, move the instrument farther away from the aerial or reduce sensitivity on the receiver. Note at what point of the dial this known frequency was obtained. Repeat the procedure with other stations and make a curve for the oscillator, plotting dial setting against frequency. Thereafter it is possible to obtain a signal at any desired frequency by referring to this curve.

To calibrate the i.f. band, harmonics must be used. Disconnect the aerial from the receiver, run a wire from the antenna post to the oscillator—just lay it near the instrument. Set the oscillator dial to 100 (C1 fully meshed) and search for the signal on the receiver, this will probably come in somewhere near 710 kc. and again at about 880. The actual frequency is now the difference between the two. To get it more exact, divide the difference into 880, which will give about 5. The exact frequency is $880/5$. By reading the frequencies accurately, the result will be very close to the exact frequency. This method can be used to determine frequencies at other spots on the dial. Again a curve should be made of dial setting vs. frequency, so that an exact setting for 456 kc. can be obtained. The model constructed in the RADIO NEWS laboratory had ranges from 176-550 kc. and 540-1550 kc. Those who wish to cover 175 kc. and lower, can connect a fixed condenser of .00025 mfd. in parallel with C1, or across L2, which will cover this band adequately.

Output Indicators

When aligning circuits for maximum response, the ear may be used and the best adjustment found by listening, this requires a modulated oscillator. However, the ear is not very sensitive to small changes in sound intensity. A sharper indication is obtained by means of some measuring in-

strument. Lamps or neon tubes have been used but these aren't any better than listening tests because the eye is just as inaccurate as the ear.

The first type of "output meter" is some form of a.c. voltmeter. A low-reading a.c. voltmeter can be used, connected across the voice coil. This may have a range of 0-5 volts or 0-10 volts. The second type consists of a d.c. milliammeter with a rectifier. Rectifier-type voltmeters are on the market, but they can be made from a d.c. milliammeter by the addition of a rectifier as shown in Figure 2a. The rectifier used can be one of the copper oxide type, available from radio supply houses, or a tube as in Figure 2b. Some have used a carborundum crystal successfully. The resistance R determines the range of the voltmeter. If the milliammeter in Figure 2a has a 1-ma. range, the resistance R should be 850 ohms. per volt. So for a 100-volt range R would be 85000 ohms; for a 10-volt range, 8500 ohms, etc. For a milliammeter with a range of 5 ma., divide the above values by 5.

In the case of Figure 2b, the resistor should be 20000 ohms to 50000 ohms, and a rather sensitive meter is required, 0-5 ma. or 0-1 ma. All the systems described so far, require a modulated oscillator.

A simple milliammeter, having a range of 0-15 ma. or less can be used in receivers equipped with a.v.c. The meter is simply placed in series with the plate lead of one or more of the controlled tubes. If the range of the meter is 0-15 ma., the current of two controlled tubes, should be sent through it. Meters with ranges of 0-10 ma. or less should receive the current of but one tube. If the range of the meter is less than 0-7 ma., it may be necessary to shunt it with a rheostat of 0-30 ohms., adjusting the resistance for full-scale deflection when no signal is coming in.

This type of meter will show a decreased current when a signal is tuned in and all adjustments are made for minimum current. Also, the oscillator may either be modulated or unmodulated; in the case of unmodulated signals sharper indications are obtained and the speaker is silent.

Finally, it is possible to get an indication without a measuring instrument by the use of a tuning indicator tube like the 6E5, 6G5, etc. These are used by RCA under the trade name "Magic Eye." The tube is cheaper than a good milliammeter and the associated equipment is inexpensive. Figure 3 shows how it should be connected. The tube is a miniature cathode-ray tube with a triode amplifier in one envelope. When in operation, the tube shows a luminous ring with a dark sector. This dark sector narrows down when a negative voltage is applied to the grid. Thus the grid can be connected to the a.v.c. circuit for alignment purposes. This again does not require a modulated signal. The tube requires a 6.3 volt filament supply and 250 volts plate supply at very low drain; all power can be taken from the receiver.

Parts List

- C1—single gang variable condenser, .000365 mfd.
- C2—Solar mica condenser, .002 mfd. (for unmodulated oscillator, .00025 mfd.)
- L1—see text and Figure 1
- L2—Hammarlund r.f. choke, type CHX, prepared as described in text
- R1—15 ohm wire wound resistor
- R2—IRC carbon resistor, 1 meg., $\frac{1}{2}$ watt (for unmodulated oscillator: 50000 ohms, $\frac{1}{2}$ watt)
- S1—Single-pole-single-throw toggle switch
- S2—Double-pole-double-throw toggle switch
- 1—Eby base mounting socket, 4-prong
- 1—Bud tuning dial, type 713
- 3 inches bakelite tubing, $2\frac{1}{4}$ inches diameter, for L1
- 2—Eveready flashlight cells, type 950
- 1—Eveready 22 $\frac{1}{2}$ volt battery, type 763
- 1—Type 30 tube
- Baseboard 9 x 6 inches



ALLIED'S 156-PAGE CATALOG SCOOPS THE RADIO FIELD!

Here's a new book—a complete book—a book that makes all other catalogs obsolete! Packed with Everything in Radio that's months-ahead. It includes more than 10,000 exact duplicate and replacement parts; latest test instruments—tube checkers, analyzers, oscillographs, meters, set-testers, etc.; 53 new Super-Value Knight Radios; Amateur gear; new Sound Systems; dozens of Set-Builders' kits; books, tools, etc. See what's new—see what's important in Radio!—Send coupon for this great book today!

FASTEST SERVICE—LOWEST PRICES!

You save more—get more—profit more—when you order from ALLIED! Our complete stocks, central location, efficient buying and selling methods, and speedy shipping department mean faster service, lower prices and greater values for you. Make ALLIED—Radio's Leading Supply House—your single dependable source for high-grade radio supplies!



FREE Catalog

ALLIED RADIO Corp.

833 W. JACKSON BLVD., Dept. 1-G
CHICAGO, ILLINOIS.

Send me your new 1937 Radio Catalog.

Name.....
Address.....
City.....

COMPLETE STANCOR KIT

- 4 OSCILLATORS
 - Straight Pentode
 - Tritet
 - Jones
 - Bi-Push
- 2 BUFFER DOUBLERS
 - Triode
 - Dual Triode
- 4 AMPLIFIERS
 - Single Triode (T20 or Type 10)
 - Push-Pull Triode (T20 or Type 10)
 - Single Pentode (RK-39 etc.)
 - Push-Pull Pentode (Bi-Push)
- Forty-Eight Combinations




48 CIRCUIT COMBINATIONS FOR \$49⁹⁵

Here's a natural for the medium-power amateur. 4 Oscillators... 2 Buffer-Doublers... and 4 Amplifiers... \$5 to \$20 watts input... ALL FROM A SINGLE KIT. The kit includes circuits on the most recently released tubes... and circuits on older types of tubes that you probably have in your shack.

The new Stancor "48-C" Kit contains all the parts you need FOR EVERY CIRCUIT—less crystal, tubes and meter.

COMPLETE SCHEMATIC BLUE PRINTS FREE WITH EVERY KIT

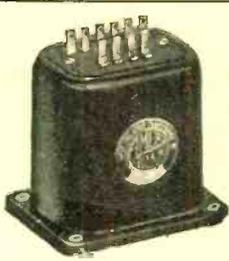STANDARD TRANSFORMER CORPORATION
850 BLACKHAWK STREET • CHICAGO



Record of RESULTS

ASK the earliest of amateurs. They all knew you had to have an Amer-Tran Transformer to get clear, natural amplification. Ask today's experienced engineers and you learn that Amer-Tran's record of results is still the *record*. Only the highest quality of materials and the highest order of craftsmanship could produce transformers so reliable.



AMERICAN TRANSFORMER CO.
178 Emmet Street Newark, N. J.



CRYSTAL HEAD PHONES

SOUND CELL MICROPHONES

Information on request
THE BRUSH DEVELOPMENT CO.
3311 PERKINS AVE. CLEVELAND, OHIO

HANDEE

Tool of 1001 Uses

A whole shop full of tools in one. Does away with slow hand work. Plugs in any light socket AC or DC, 110 v 13,000 r.p.m. Uses 200 different accessories—grinds, polishes, routs, drills, cuts, carves, sands, saws, sharpens, engraves.



Get A Demonstration at Hardware, Dept. Stores, Tool Dealers or order on 10 Day Money-Back Trial. \$10.75 and up postpaid. 3 Accessories Free. DeLuxe Model \$18.50, with 6 Accessories. Catalog Free.

For Faster Better Jobs
New CRAFTSMAN Project Book
"Pleasure and Profit with a Handee." Easy working plans for making many interesting and unusual projects 25c, stamps or coin.


ELECTRICAL ENGINEERING
For those who can't afford the time and expense of a 4-year college course, Bliss offers a condensed **ONE YEAR** residence training, combining essential Theory and Practice. 45th year. **CATALOG ON REQUEST!**
BLISS ELECTRICAL SCHOOL
477 Takoma Ave., Washington, D.C.

Small bakelite panel 2 x 3 inches, 1/4 inch thick
1—lug terminal strip, 3 lugs
5—angle brackets

Inter-Office Call Systems

(Continued from page 55)

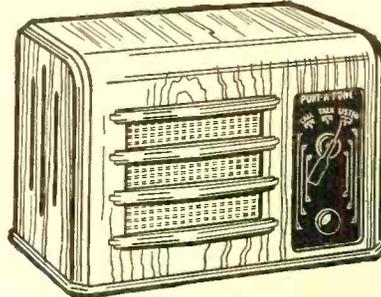"Port-A-Fone" which transmits the speech frequencies over the electric light lines. To operate, it is only necessary to plug the instrument into the nearest electric light socket, press the calling signal, flick the



indicator to "talk," speak in a normal conversational tone, and your voice is carried over the power wires to another station. The instrument weighs only 8 pounds.

The Service Bench

(Continued from page 45)

Service Notes

A lot of the lads tell us that Rider's new book on Philcos out-Philcos—*and that it's what they have been waiting for a long time.* We'll review it next month. RCA has just issued a new parts catalog which is more than worth the trouble of

securing through your jobber. In it are pictured and described replacement parts, test and measuring equipment, tubes, radio accessories and amateur apparatus. A handy cross-reference replacement guide for RCA Victor lines up the corresponding models of G. E., Graybar and Westinghouse.

Speaking of RCA, the folks down in Camden have brought out two new popular-priced record players, the R-93-A, listing for \$18.50, and the R-94, with a suggested list price of \$28.95. While there is a nice profit selling these items themselves, the real money is in building up a record business which runs on and on long after the turntable and pick-up unit is sold. Razor companies don't make money on razors—it's the blades they sell that counts!

Wonder who'll be running around in the sound truck shown in Figure 7? Just



FIGURE 7

The name of some serviceman reader of RADIO NEWS is probably on this truck by now. Alongside are Eddie Riedel and Earl Dietrich of Raytheon, who is giving away the truck.

about the time this is published Raytheon is giving away this elaborately-equipped "ballyhoo wagon" to some lucky serviceman!

Take a tip from Sylvania and decorate your shop or store with the display shown in Figure 8. The large one fits a window

INDEX TO ADVERTISERS

Aerovox Corporation.....	58	Models	41
Akrad Products Company.....	56	Montgomery Ward.....	47
Aladdin Radio Industries, Inc.....	42	National Radio Institute.....	1
Allied Radio Corporation.....	61	National Schools.....	58
American Microphone Co., Inc.....	47	National Union Radio Corp.....	41
American Transformer Company.....	62	New York Y.M.C.A. Schools.....	63
Amperite Corporation.....	48	Pioneer Gen-E-Motor Corporation.....	50
Bliss Electrical School.....	62	RCA Institutes, Inc.....	41
Bond Radio Company.....	57	RCA Manufacturing Company.....	39
Brush Development Co., The.....	62	Radio City Products Company.....	63
Cameradio Company.....	64	Radio Service Institute.....	40
Candler System Co., The.....	52	Radio & Technical Publishing Company.....	38, 48
Capitol Radio Engineering Institute.....	56	Radio & Television Institute.....	50
Central Radio Laboratories.....	40	Radio Training Ass'n of America.....	47
Chicago Wheel & Mfg. Company.....	62	Radolek Company, The.....	63
Classified Ads.....	63	Raytheon Production Corporation.....	59
Clough-Brengle Company.....	45	Readrite Meter Works.....	57
Cornell-Dubilier Corporation.....	54	Rider, John F.....	63
Cornish Wire Company, Inc.....	54	Scott Radio Labs., Inc. E. H.....	3
Coyne Electrical School.....	44, 57	Silver Corporation, McMurdo.....	Inside Back Cover
Dodges Institute.....	52	Solar Mfg. Corporation.....	38
General Electric Company.....	56	Sprayberry Academy of Radio.....	64
Goldentone Radio Company.....	52	Standard Transformer Corporation.....	61
Hallcrafters, Inc.....	Back Cover	Teleplex Company.....	47
Hammarlund Mfg. Company.....	49	Triad Mfg. Company, Inc.....	38
Hygrade-Sylvania Corporation.....	55	Trimm Radio Mfg. Company.....	40
Instructograph Company.....	44	Triplet Electrical Instrument Company.....	51
Kato Engineering Company.....	41	Tri State College.....	54
Kenyon Transformer Company, Inc.....	46	Tung-Sol Lamp Works, Inc.....	42
Lincoln Engineering School.....	63	United Sound Engineering Company.....	64
McElroy, T. R.....	58	Utah Radio Products Company.....	46
Mallory & Company, P. R.....	6	Weston Electrical Instruments Corporation.....	Inside Front Cover
Midland Television, Inc.....	53	Wholesale Radio Service Company.....	43
Midwest Radio Corporation.....	44	Wright-DeCoster Company, Inc.....	52
Million Radio & Television Laboratory.....	64		

WHY PAY MORE?

... when Radio City Products Co. offers you better testing equipment at far lower cost?

SEE YOUR JOBBER •
WRITE TO DEPT. N FOR CATALOG

RADIO CITY PRODUCTS CO.

88 PARK PLACE NEW YORK CITY "DEPEND ON DEPENDABLE"

RADIO COURSES

RADIO OPERATING: Prepare for Gov't License Exam. • RADIO SERVICING: Including Short Wave • AMATEUR CODE • ELECTRONICS • TELEVISION •

Day and Evening Classes—Booklet Upon Request

NEW YORK Y.M.C.A. SCHOOLS
7 W. 63rd Street, New York City

RADIO EXPERIMENTERS' HANDBOOK

This handy manual is crammed full of useful data for the radio experimenter. Includes: Laboratory and Shop Notes—Antenna Experiments—Experimental Circuits in Radio and Electronics—Principles of Short-Wave Reception—Equipment for Photo-Electric Work—Miscellaneous Measurements—Experimental Television Data—and Circuit Design Data. Get your copy now—send 10c to: Dept. 377a, RADIO NEWS, 461 8th Ave., N. Y. C. (Canada & Foreign 15c).

10¢

A 136-PAGE BOOK—ONLY

Correspondence Courses in RADIO and ELECTRICAL ENGINEERING

ELECTRICAL ENGINEERING Get good electrical field. Prepare yourself, at Low Cost, for secure future. Modern course. So simplified anyone can understand quickly.

RADIO ENGINEERING Extra line course in radio, public address, photo-electric work. Trains you to be super-service man, real vacuum tube technician. Experimental kits furnished. Diploma on completion. Tuition, ONLY \$25, either course. Deferred payment plan available.

FREE! Send name quick for free copies of school catalogs, student magazines, complete details. SEND NOW!

LINCOLN ENGINEERING SCHOOL, Box 931-30, Lincoln, Nebr.

Read Classified Advertising—It Pays

Advertisements in this section sixteen cents a word for each insertion. Name and address must be included at the above rate. Cash should accompany all classified advertisements unless placed by an accredited advertising agency. No advertisements for less than 10 words accepted. Objectionable or misleading advertisements not accepted. Advertisements for these columns should reach us not later than 3rd of 2d month preceding issue.

TECK PUBLICATIONS, INC.
461 Eighth Ave. New York, N. Y.

Correspondence Courses

USED Correspondence Courses and Educational Books sold or rented. Inexpensive. Money-back guarantee. Write for Free Catalog listing 4000 bargains. (Courses Bought.) Lee Mountain, Fishah, Alabama.

BIG BARGAIN Catalogue Courses 10c. Hanfling, P-799 Broadway, New York.

Patent Attorneys

PATENTS. Instruction "How to Establish Your Rights" and form, "Evidence of Conception" sent Free! Lancaster, Allwine & Rommel, 414 Bowen Building, Washington, D. C.

PATENTS—Advice and booklet free. Highest references. Best results. Promptness assured. Watson E. Coleman, Patent Lawyer, 724 9th Street, Washington, D. C.

Patents and Inventions Wanted

INVENTIONS COMMERCIALIZED. Patented or unpatented. Write Adam Fisher Company, 278 Enright, St. Louis, Missouri.

Radio Instruction

AMATEUR RADIO. Commercial Radiotelephone and Radiotelegraph licenses, complete training. Resident and correspondence courses. Every graduate a licensed operator. N. Y. Wireless School, 1123 Broadway, New York.

Short Wave Listeners

SEND us one dollar for 100 snappy Short Wave Listeners cards printed with your name and address. sent postpaid, W1BEF, 16 Stockbridge Ave., Lowell, Mass.



FIGURE 8
Two attractive Sylvania displays.

and flashes, while the small replica is counter size without flasher. Distribution through Sylvania jobbers.


Midwest Builds Service Organization

The Midwest Radio Corporation announces that they will engage competent servicemen all over the country to install and service Midwest radios in their respective neighborhoods. Midwest will pay for such original installations on a fee basis. Servicemen who are interested in taking on this extra business should write immediately to the Midwest Radio Corporation, Cincinnati, Ohio, for complete details.

The Radio Workshop

(Continued from page 35)

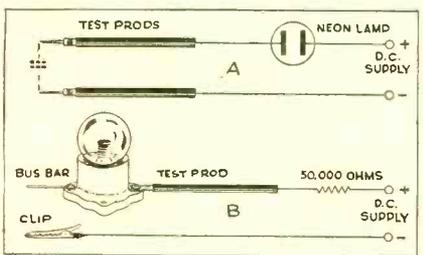age in several good condensers. This condition was brought about by minute leakage through the insulation of the test leads, creating a high resistance path through the hands and the body. To remedy this condition I connected the neon tube at the



end of the test handle as shown in Figure B. In this method any possible leakage across the leads can not go through the neon tube.

An alligator clip forms a convenient negative test lead, also facilitates testing. With the clip connected to one side of the condenser under test there will be only one hand in the circuit and therefore no circuit through the body. Also, both tube and prod are constantly in view, so you will not miss the quick flash produced by a small condenser and think it open. Using 90 to 250 volts, I find a quarter-watt neon tube with 50,000 ohms in series, an ideal combination. For 300 volts and higher, use 100,000 ohms in series to protect the tube in case of a short.

W. E. KEEVER,
Detroit, Michigan.

The DX Corner

(Continued from page 37)

best heard in England are: WJSV, WAAB,

RIDER BOOKS

for
**SERVICEMEN
AMATEURS
EXPERIMENTERS**

- NEW**
- ALIGNING PHILCO RECEIVERS**—New! Authentic instructions for aligning ANY of the 8,000,000 Philcos. Over 160 pp. Only \$1.00
 - SERVICING SUPERHETS** Revised edition just published shows how to make superheterodyne repairs quickly. 288 pp., \$1.00
 - CATHODE-RAY TUBE AT WORK**—Complete, practical, written for servicemen. Information on Oscillograph, etc. \$2.50 336 pp. 450 ill.
 - "AN HOUR A DAY WITH RIDER" BOOKS**
 - ON AUTOMATIC VOLUME CONTROL** will speed up your AVC work. 96 pp.—65 ill.—hard cover—60c
 - ON RESONANCE & ALIGNMENT.** You need this! 96 pp.—48 ill.—hard cover—60c
 - ON D-C VOLTAGE DISTRIBUTION IN RADIO RECEIVERS.** How d-c voltages are led to tube elements, etc. 96 pp.—69 ill.—hard cover—60c
 - ON ALTERNATING CURRENTS IN RADIO RECEIVERS**—Out in March—60c
- ORDER YOUR COPIES TODAY•**
- 1440 Broadway,
JOHN F. RIDER, Publisher New York City

by the Publisher of

RIDER MANUALS

NOW IN SEVEN VOLUMES

the RADOLEK

Most Complete Radio BUYING GUIDE FREE!

Everything in Radio

The completely revised Summer and Early Fall edition of the 1937 Radolek Profit Guide is just off the press. Over 1000 NEW ITEMS plus an ADVANCE SHOWING OF 1938 RECEIVER MODELS. 164 Pages of valuable, detailed radio buying information... contains the most complete replacement parts listings of volume controls, condensers, transformers and vibrators. OVER 12,000 REPAIR PARTS—THE RIGHT REPLACEMENT ITEMS FOR EVERY RADIO THAT YOU WILL SERVICE. Radolek specializes in giving the radio man what he wants, when he wants it, and at the right price. Send for your Profit Guide NOW!

RADOLEK

601 W. Randolph, Chicago, Dept B-7

Send me the Radolek Radio Profit Guide FREE.

Name.....

Address.....

Serviceman? Dealer? Experimenter?



"I'll show you how to get the jobs that other Radio men can't handle"

MAKE \$40-\$60 a WEEK

with this New Kind of Radio Training

It Actually Sets You Up In Business!

Now there's a new kind of Radio training every man should know about if he wants to get on the money end of the Radio industry. Men taking my training right now are actually earning \$10, \$15, \$20 a week and more in spare time—while they learn. Men who have graduated are holding down jobs paying \$60 a week and up.

Make More Money Quick

My course is arranged so that you get practical lessons right at the start. Quickly, you are ready to begin servicing sets. Useful, simple job sheets show you every step to take. And you have the equipment to handle these jobs properly. Time and time again my students write in to tell me they are handling jobs other Radio men couldn't handle. That's because my easy to understand lessons and professional equipment make you a real Radio expert.

No Experience Needed

Old-timers and new-comers are taking this new kind of training and making real money in Radio. If you are a Radio man now, you know now is the time to get extra training and bigger pay. If you are just about to enter Radio, now is the time to start taking this thorough, easily-learned course. Everything is clear. Everything practical. You learn business methods, gain self-confidence, get the satisfaction that nothing but quick cash in the pocket can give you.

Get the Facts

Your future in Radio can be rich and happy if you get started on the right track, get the kind of instruction that puts you ahead of others from the start. My new book, entitled "MORE MONEY IN RADIO" tells about Radio's spare-time and full-time opportunities, tells you about my unusual new type of practical Radio training. Shows you letters from men who have found success this way, shows how YOU can do the same. Send for this book today and get the facts. Act now! Fill in and mail this coupon below.



Course Worth Many Times Price
"Took your Course while going to high school. Soon I built up a large Radio Service Business. Sold over 300 tubes between January and May. Your Course is worth many times the price." Henry Reynolds, Reynoldsville, Pa.

Big Professional Outfit Sent

Because I'm a practical Radio man, I have developed this practical training. While you learn at home, in your spare time, you train on real Radio parts with real professional tools and implements. I send them to you as part of your course. This big professional outfit is practically an entire Radio shop in itself—it sets you up in business. Mail coupon for complete information today.



GET FREE BOOK

Mail Coupon Now

Sprayberry Academy of Radio,
F. L. Sprayberry, President,
Office No. 25-H
University Place, N. W.,
Washington, D. C.

Please send me, without obligation, "More Money in Radio" and complete facts about your new type of training.

Name..... Age.....

Address.....

City..... State.....


Paste this coupon on a penny postcard and mail TODAY.



For Sound Trucks

The U.S.E. Type

20-E Amplifier

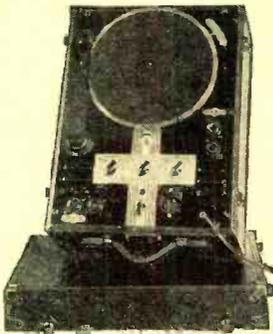

Operates on car battery or 110 volts a.c.

20 Watts output. Dual mike input. Electric-eye Monitor.

U.S.E.'s new 16-page catalog lists complete Sound Truck Systems using the 20-E Amplifier.

Write for Catalog No. 107 and proposition.



United Sound Engineering Co.
Manufacturers of Electronic Equipment

2237 University Ave.
St. Paul, Minnesota

Licensed by arrangement with E.R.P.I. under patents owned and controlled by A. T. & T. and Western Elec. Co., Inc.

MILLION

DC VOLT-OHM MILLIAMMETER



3" square meter. 0-3-30-300-900 volts D.C. at 1000 ohms per volt. 0-1-3-30-300 M.A. D.C. 0-3000-300,000 ohms. ALL connections made by single switch. Zero adjuster and durable test leads.

Model V O (Illustrated)
AC-DC-Volts 7.5 megohms—
—200 microamperes
5000 ohms
per volt..... \$19.95

MODEL A
\$9.95
NET

MILLION RADIO AND TELEVISION LABORATORIES
577 N. UNION ST., CHICAGO, ILL.

OUR NEW HOME

THREE BIG FLOORS
THE ENTIRE BUILDING
With the Largest Stock of
STANDARD RADIO PARTS & EQUIPMENT
IN PENNA.-OHIO-W. VA.

Write for new 1937 catalog

CAMERADIO

963 LIBERTY AVE., PITTSBURGH, PA.
Established 1919

WIOD, WNAC, WCAU, WHAM, WPG, KMOX, WBT, WTIC, WHN, WBZ, WABC, WJZ, WOR, WEA, and WEEI. Just which is the pick of this bunch has been the cause of much argument, but it is noticeable that even those DX'ers who believe WTIC, WBZ or WOR to be best usually admit WCAU to be second best, and the Philadelphia station is placed first by many. It will be observed that this list of well heard stations contains the names of several small broadcasters. The little 'uns who are received fairly consistently are, with the possible exception of WFBL, all situated on the Atlantic coast. However, when conditions are extra good, low-powered stations, even 100-watters, may be received from all parts of the States. Three of the best veries held by English listeners are from KDB, KERN, and KBPS.

There is a deep-rooted belief among English DX'ers that North American signals are strongest at the full moon, and weakest at the new moon. In practice this theory proves by no means 100 percent correct, but is near enough to cause the ardent listener to book a date with his radio when the moon is roundest.

WLW, KDKA, and WGY are three broadcasters associated with little mysteries. WLW, while testing as W8XO, was receivable at really good volume, but since dropping the experimental call has rarely approached its old form. Ten years ago KDKA and WGY shared No. 1 position as Atlantic crossers. Today WGY is only moderately well heard, and KDKA hardly at all.


R. A. STANSFIELD,
Newark Road,
Ripley, Woking, England.

What's New in Radio

(Continued from page 53)


Program Distribution System for Schools

The Holtzer-Cabot Electric Company introduces a complete sound distribution system especially planned for schools. It is designed to provide radio, phonograph, and microphone programs with sufficient power to operate up to 60 loudspeakers. The phonograph reproducer is of the automatic record ejector type. The system is equipped with two all-wave, high-fidelity superheterodynes. A special feature provides two-way communication between the control cabinet and the classroom by using the classroom loudspeaker as a microphone.

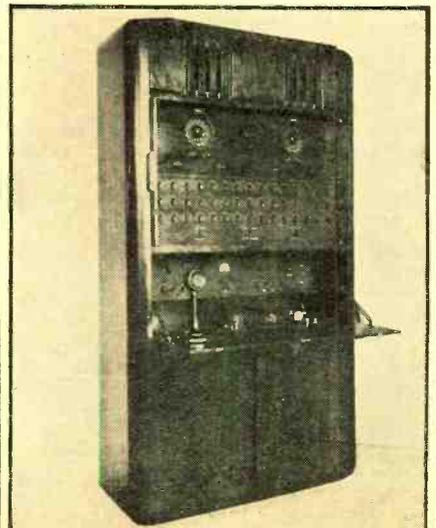

Another Polar Expedition Chooses

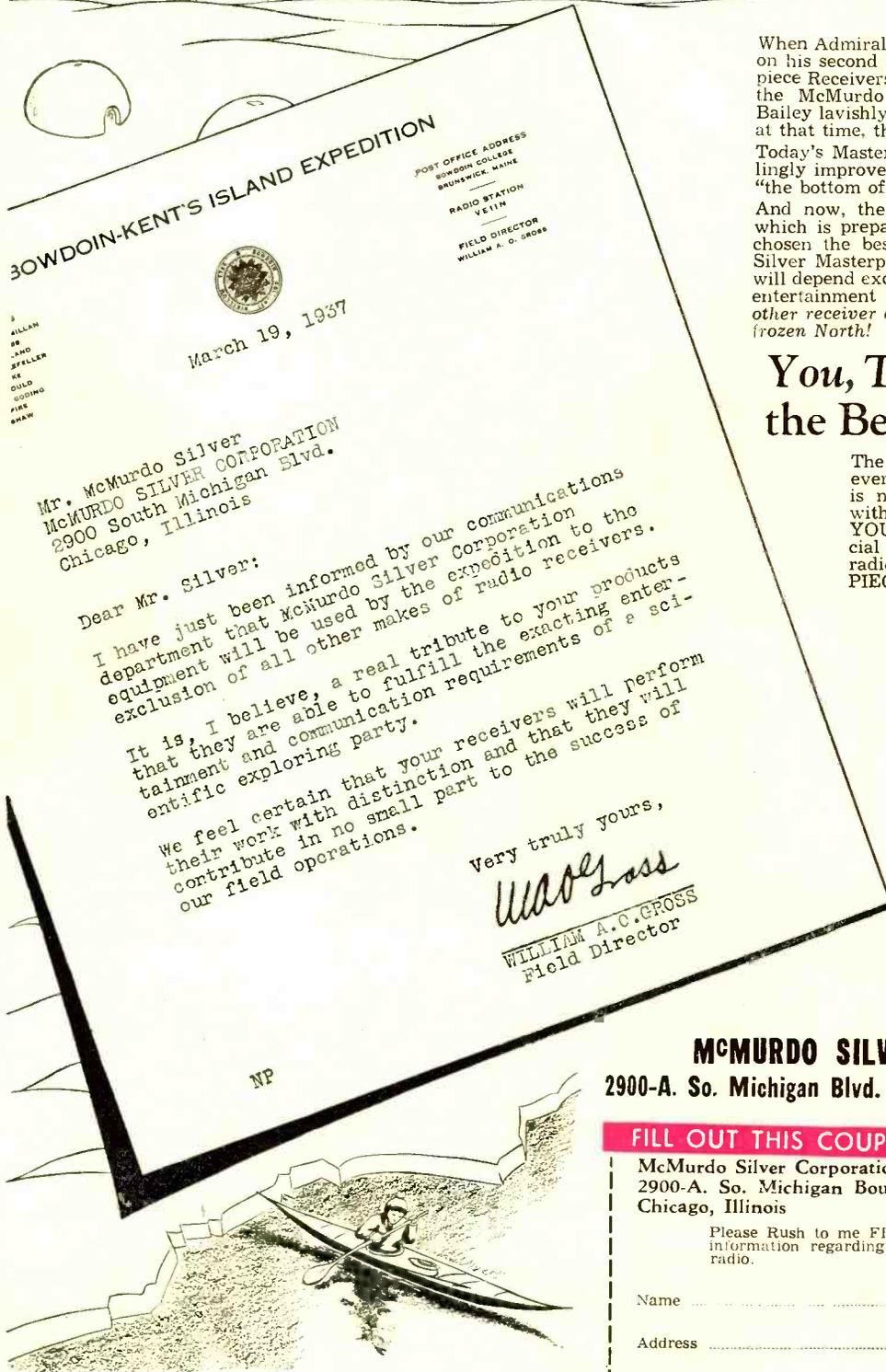The **McMURDO SILVER** MASTERPIECE RECEIVER!



When Admiral Byrd went to Little America, in 1934, on his second South Pole Expedition, four Masterpiece Receivers went with him. There are letters in the McMurdo Silver files from Chief Operator Bailey lavishly praising the Masterpiece which was, at that time, the world's best radio.

Today's Masterpiece is still the best, though startlingly improved over the Masterpiece that went to "the bottom of the world".

And now, the Bowdoin-Kent's Island Expedition which is preparing to sail for the Arctic has also chosen the best and most reliable—the McMurdo Silver Masterpiece. This scientific exploring party will depend exclusively on the Masterpiece for total entertainment and communication reception. No other receiver accompanies this expedition into the frozen North!

You, Too, Should Have the Best in the World!

The MASTERPIECE can be owned by everyone who wants the very best. It is not priced so high that it is only within the reach of the millionaires. YOU, almost regardless of your financial circumstances, if you demand fine radio reception, can own the MASTERPIECE.

Remember!

You can Buy the
World's Best Radio
On Small Monthly Payments

Write for Illustrated Literature

The McMurdo Silver laboratories have just fathered spectacular new developments in the radio art. Features never dreamed of before—and not found in any other radio receiver! Just fill out the coupon NOW and we will explain clearly the reasons why the Masterpiece is the world's best radio. TRULY CUSTOM-BUILT FOR YOUR INDIVIDUAL NEEDS.

McMURDO SILVER CORPORATION

2900-A. So. Michigan Blvd.

Chicago, Illinois

FILL OUT THIS COUPON AND MAIL TODAY!

McMurdo Silver Corporation
2900-A. So. Michigan Boulevard
Chicago, Illinois

Please Rush to me FREE illustrated literature, complete information regarding the newest, improved Masterpiece radio.



Name

Address

City..... State.....

"THE WORLD'S FINEST CUSTOM-BUILT RADIO"

Announcing

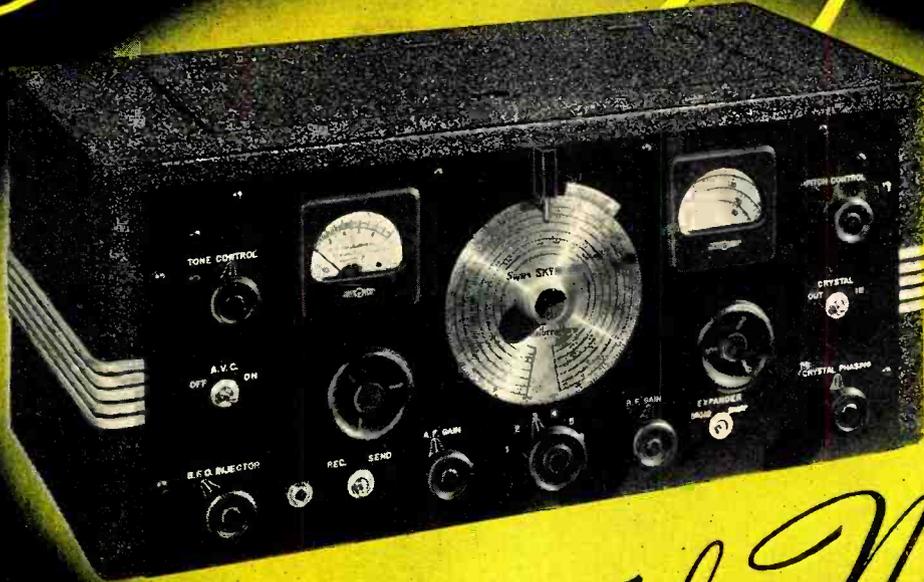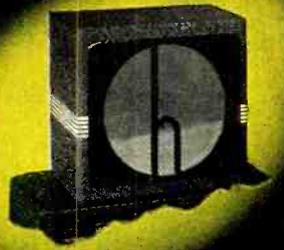

The New 1938

SUPER SKY RIDER

Leading Radio Columnist
HANDS AN ORCHID
to the Super Sky Rider†

Visited by Diplomats

On Wednesday evening I was honored to entertain B. P. Stoyanovitch, Consul General of Yugoslavia, and his staff while we listened to a special broadcast up among the megacycles from Belgrade.

With a battery of five communications receivers which had been warming up for hours, I sat down full of confidence and started spinning dials. Well, maybe not confidence, exactly, but hope, anyway. But imagine my embarrassment when minutes passed and we logged practically everything in the world except Belgrade.

However, at the end of about fifteen minutes we dragged in a speech in an unfamiliar language, and immediately Mr. Stoyanovitch burst forth in happy smiles. It was the voice of the Prime Minister of Yugoslavia and the receiver that did the trick was the old reliable SX11 superskyrider. After trying for a few minutes to log the program on the other receivers, just by way of something to fall back on in case of emergency, but having no luck, we turned off the others and sat back to listen. And if you don't think a terrible weight was lifted from my brow when the skyrider did its stuff, then you never had eleven officials of a foreign nation standing skeptically by while you try to produce results in short wave radio reception.

†Reproduced from Ted Rogers' Radio Column, New York World-Telegram, April 17, 1937

THE HALLICRAFTERS' GREATEST ACHIEVEMENT

Imagine a receiver that gives you complete coverage from 5 to 550 meters, taking in everything from the 5 meter band to the top of the broadcast band—with wide range variable selectivity (single signal razor-sharpness to true high fidelity*)—with an ingenious, new, electrical band-spreading device** that provides 1000° of band spread—an "S" meter that works on weak signals—with improved image and signal-to-noise ratio, and a dozen other outstanding features. Now you can listen to two-way police communications on 7½ meters—to the interesting and active new 5 meter band—in fact to everything on short waves and the broadcast band as well.

Imagine all this on one receiver—there's not another feature the amateur or short wave listener could possibly desire. It's absolutely revolutionary in performance and scope. It's the New 1938 Super Sky Rider, now on display at your dealer's, at an amazingly low price for so much value. Available on Hallicrafters' liberal Time Payment Plan. See it today!

*R. M. A. has defined High Fidelity as 7000 cycles at 20 D. B. down.

**Patent applied for.

FEATURES

5 to 550 Meters Coverage.

6 Bands.

11 Tubes.

Wide Range Variable Selectivity.

Better than One Microvolt Average Sensitivity on all bands.

1000° Electrical Band Spread.

"S" Meter.

13 Watt Undistorted Output.

Air-Trimmed R. F. Circuit.

Improved Expanding I. F. Transformers.

Improved Crystal Filter Control.

See the New 1938 Super Sky Rider at your dealer's or write for complete information.

the hallicrafters inc.

2603 Indiana Avenue, Chicago, Ill. • Cable Address "Hallicraft" Chicago
America's Leading Manufacturer of Communications Receivers