# SHORT-WAVE

VOL. XXIX

OCTOBER, 1971

NUMBER 8





full information on the great new all band solid state
Trio communications receiver Model

Ask at your local dealer or send for full information on the JR-599 receiver £185.00 and all other Trio models including: TS-510 transceiver and PS-510 power supply £180.00 (the pair); VFO-5D (Variable Frequency Oscillator for TS-510) £25.00; 9R-59DS receiver £47.50; JR-310 receiver £77.50; SP-5D speaker £4.38 and HS-4 headphones £5.98.



exclusive United Kingdom distributors b.h.morris and co.(radio) limited

84.88 Nelson Street, London E.1 2DY. TEL: 01.790 4824

**MUNICATIONS** 



# World-wide leading manufacturer for the Radio Amateur

Long established to give you reliable service EXPERT FREE ADVICE DIRECT FROM THE MANUFACTURER

All Equipment available through accredited agents

# 2 Great Transceivers KW2000B 10-160 metres Two-speed VFO drive SSB TRANSCEIVER: 180 watts Improved VFO Read-out PEP 10-160 metres, complete with A.C. P.S.U., VOX P.T.T., New, precise metering Attractive panel lavout I.R.T./I.T.T. . D.C. P.S.U. for mobile Break-in c.w. Carriage extra 1111 1111 11111 11111 11111 11111 11111 manning in KW ATLANTA 10 - 80 metres Extremely good audio (crystal filters fitted) £200 500 watt PEP SSB Transceiver Operation on all amateur bands from 10 to 80 metres A.N.L. and A.L.C. carriage extra 100 kHz Crystal Calibrator. KW Atlanta and Two speed VFO drive A.C. P.S.U. Built in speaker. Both transceivers available with remote VFO unit

KW offers a complete range of equipment ensure your investment in equipment pays dividends—buy KW\*

\*KW equipment holds its value longer—compare "trade-in" prices for 1-5 year old equipment, with other makes. Spares, for all KW equipment stocked for a minimum of 5 years—this is well worth considering.

# NEW KW PRODUCTS

KW202 RECEIVER, 10-160 metres SSB/AM/CW, with Mechanical Filter, built-in 'Q' Multiplier (Peak & Null), 500 kHz VFO covering all Bands. Two-Speed VFO Drive. Excellent Sig./Noise and sensitivity performance. Very attractive (similar in appearance to KW2000B). 100 kHz Crystal Calibrator price £140 carriage extra. KW204 TRANSMITTER. 10-160 metres SSB/ AM /CW. Successor to the famous KW "Vesna" -Perfectly matches the KW202 Receiver and is similar in appearance. 180 watts p.e.p. from trustworthy 6146's. Built-in Power Supply. Provides "side tone" cw monitoring. A beautiful compact efficient unit. Price £142 carriage extra. 101—Standing-Wave-Ratio meter £9.25\*. KW 103 SWR/Power meter 0-100 & 0-1000 watts £12-50\*. KW 103 with Dummy Load and Coax Lead £20.50\*. KW 105 Antenna Tuning System including E-Z Match, SWR Ind., Dummy Load. Antenna Switch, 5 position, £36-90\*. Also KW Trap Dipole with twin feeder and 4 other types (only the original Trap from KW is good enough for you). KW E-Z Match ATV, KW Low Pass Filters, KW & HZP Baluns, etc.

KW for HY-GAIN, MOSLEY, G-WHIP, POLYQUAD, WEBSTER, HUSTLER ANTENNAS. SHURE Microphones, CDR Rotators. VIBROPLEX Keys, etc.

Write for details today

# K. W. ELECTRONICS LIMITED

1 HEATH STREET, DARTFORD, KENT Telephone: Dartford 25574 Cables: Kaydublew Dartford



# SERVICE (with a capital 'S') BEGINS WITH WESTERN ELECTRONICS

24hr. Delivery! We guarantee delivery within 24 hours. (48 hrs. to remote parts of Scotland) of cash sales of items which are in stock. The cost of this special service if £1 per parcel and applies to all TRANSCEIVERS, ROTATORS, and certain AERIALS. 10% DEPOSIT ONLY ON H.P. You will find our Interest Rates are about the cheapest too.

You'll be doing yourself a favour, as well as us, if you buy all your equipment, KW, CDR, HY-GAIN, etc. through "WESTERN ELECTRONICS"



# ETIM

Price #230.00

Denosit £23.00

Now available with 160m.

Price 4745.00

Deposit 474.50

● 10 FET's, 3 IC's, 31 TR and 38 diodes.

- Highly advanced computer-type plug in modules.
- 240w. p.e.p. 3·5-30 MHz.
- 12. D.C. and 100/240v. A.C. supplies built-in
- Break-in C.W. keying (180w.)
- lacktriangle Dual gate Mosfet's for 0-3  $\mu$ V sensitivity for 10 dB S/S + N ratio.
- ★ Noise Blanker is standard.
- ★ Built-in WWV band.
- ♣ Built-in speaker.
- ★ 25 and 100 xtal calibrator.
- \* Comes complete with microphone.

All this for our low PRICE of £230 (carr. £2).

YAESU/SOMMERKAMP 12 month Guarantee backed by full Service and Spares.
FT101/277 Transceiver ... £230.00 FV200 Remote VFO ..
FT101 CW Filter ... ... £11.90 FR400/500 Receiver ... FT101/277 Transceiver FT101 CW Filter ... £36.00 FT560/747 Transceiver FT101 CW Filter ... FV101 Remote VFO SP101 Speaker ... FT200/250 Transceiver FP200/250 A.C. Supply DECEMBER 1. £120-£160 ... £215.00 FT401 Fitted CW Filter ... FV401S Remote VFO ... FL400/500 Transmitter £36.00 ... £36.00 ... ... SP400 Speaker FF50DX Low Pass Filter ... £6·20 ... £10.00 £10.00 FL2000B Linear I-2 KW YD844 Table Mic. ... £118.00 ... £36.00 FL2500 Linear 2 KW ... FT2F 2m. Transceiver ... YD846 H and Mic. ... FP2AC A.C. p.s.u. for FT2F ... ... £80·00 ... £25.00 ...

DIGITAL 500. This transceiver is a highly advanced digital read-out high power transceiver using semiconductors and tubes. There are 28 IC's and 10 Tr. in the counter alone, £298 (see July advert).

K.W. We are now South coast distributors of K.W. equipment. Ex stock Alanta Mk. II, £203 (carriage £2). KW2000B, £240 (carriage £2). E-Z match £13.50 (40p). Dummy Loads Z 50Ω each. £7 (25p).

LIV CAIN (						TA32 Jnr., £22•
HY-GAIN (carriage extra). Verticals: Tri-Band Beams:		vertical £19·00 n., 6 ele. £85·00	18v., 10–80m, vert LC80Q, 80m, loadi TH3K3, 10–20m, 3	ing coil £6.70 ele £68.00	12AVQ., 10-2 18AVT/WB, 1 TH3 Jnr., 10-2	0m. vertical £16. 0-80, vertical £33. 20m. 3 ele £47.
Mono Band Beams:	Hy-Quad, 10-20m 204BA, 20m. 4 ele 103BA, 10m. 3 ele Balun BN86	£69·50 £14·50	DB10-15, 10 and 1 203BA, 20m. 3 ele. LAI Lightning arre	£67·00	153BA, 15m. 3	3 ele £33•
J BEAM (ex-stock, carriage p 2/4Y, 2m. 4 ele 2/6Y, 6 ele 2/8Y, 2m. 8 ele 2/10Y, 2m. 10 ele. 2/4P, 2m. 14 ele	£2.65 £3.20 £3.80 £8.20	2/10XY, 2m. C 2/100V, 2m. O 2/8, 2m. 4 over 2/12, 2m. 6 ove 2/16, 2m. 8 ove	mni/bi-directional 4 er 6	£6.50 2 £4.60 70 £6.15 70 £7.65 70	HO, 2m. Halo /HM, 2m. Halo/mast //16, 70 cm., 8 over 8 //14Y, 70 cms. 14 ele. //18P, 70 cms. 18 ele. //BM/46, 70 cms., 46	£1.
G. WHIPS (ex-stock, carriag Tri-bander 10, 15 and 20m. LF40, 40m. coil LF80, 80m. coil LF160, 160m. coil Telescopic section for LF co	£9·45 £4·00 £4·00 £4·00	Multimobile 71 MM40, 40m. co MM80, 80m. co MM160, 160m.	oil oil	£4.00 T	ase mounts hread adaptor AE for leaflet please.	
WE QUAD 10-20m. "boon	nless" type. Cas	t aluminium centre	e. bamboos, etc. £23•	00, carriage paid.		
<b>NEW W.E</b> . Trapped dipoles f relief.	or 10-80m. All are Type S, 5 Type P w	e fitted with resin end 100 watts, £11+50; Ty rith a special copper/t		igh quality commer	_	mbly with cable str
BANTEX. Fibreglass whips.	BM 2m. 🕯 wav	e vert., £2·75.	B5, 2m. § wave, £4.35	. Magnetic	Mounts, £4.95.	
ROTATORS (carriage extra) ARIO, £18.00 (carr, 40p),		00 (65p). TR44	I. <b>£40·00</b> (75 <sub>0</sub> ). I	HAM-M. £70-00 (8	Op). Hv-Gain 4	100, <b>£98·00</b> (80 <sub>D</sub> ),

LONDON AGENT—Roger Wilkins. Tel.: 01-845 6290 After 6.0 p.m. Hours of business Mon.-Fri. 9-1 p.m. 2-5.30 p.m. Saturday by appointment.

\*Your "one stop" single source of towers mast antennas etc.

\*Money saving "package deal \*Largest range in the U.K. on purchase of mast, rotator and antenna.

## **ELECTRONICS** WESTERN (U.K.) LTD.

OSBOURNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND. TEL.: TOTTON 4930 and 2785. CABLES: 'AERIAL' SOUTHAMPTON.

# THE SENATOR CRYSTAL BANK

# G3UGY

Phone 01-769 1639

# CRYSTALS FROM STOCK AT KEEN PRICES

SENATOR CRYSTALS proven record shows them to be the field-leaders in the art of catering for crystal requirements. Upon review, it becomes fairly obvious why this should be. At SENATOR, prior to despatch, every crystal is tested on internationally approved test-sets in conjunction with frequency counters, thereby eliminating error and assuring that every crystal unit is despatched in perfect working order.

55,000 BRAND NEW, modern crystals under our control and actually in our own stock-rooms, is sufficient reason for our customers, who range from amateurs to the Post Office government departments, universities and leading electronics manufacturers, to order from SENATOR time and time again, particularly when they need crystals in a hurry.

Here are just a few of the popular frequencies actually in STOCK

100 kHz in HCII/U	£2.50	26-500 MHz in HC18/U*	£1.60			
I-00 MHz in HC6/U	£1.75	30-000 MHz in HC6/U .	£1.60			
2.000 MHz in HC6/U	£1.50	32 500 MHz in HC18/U*	£1.60			
3.500 MHz in HC6/U	£1.75	34 000 MHz in HC18/U*	£1.60			
5.000 MHz in HC25/U*	£1.50	34 500 MHz in HC18/U*	£1.60			
7.000 MHz in HC6/U	£1.50	35 000 MHz in HC18/U*	£1.75			
9-000 MHz in HC6/U	£1.50	35-500 MHz in HC18/U*	£1 .75			
10:000 MHz in HC6/U	£1.50	38-666 MHz in HC18/U*	£1.35			
11-000 MHz in HC6/U	£1.50	40-000 MHz in HC18/U*	£1 .60			
19-500 MHz in HC6/U	£1.60	70-000 MHz in HC18/U*	£2.00			
24-500 MHz in HCI8/U*	£1.60	71-000 MHz in HC18/U*	£2.00			
25:000 MHz in HC6/U	£1.60					
* Also queilable in MCCIII						

\*---Also available in HC6/U.

And here's our STOCK range of BRAND NEW HC6/U 8 MHz for 2M:

8.007 8.012 8.018 8.021 8.032 8.041 8.043 8.047 8.048 8.0555 8.058 8.061 8.070 8.031 8.092 8.100 8.104 8.107

All at £1.25 each, post free. These crystals will pull well if used in a VXO.

Here are some popular frequencies for VHF, home station, mobile channels and R.A.E.N., ALL IN STOCK:

8·0555 MHz in HC6/U for TX x 18 to 145·000 MHz 2M Mobile Channel ... ... ... ... ... ... ... £1·25
44·7666 MHz in HC6/U for RX x 3 + 10·7 MHz to 145·000 MHz 2M Mobile Channel ... ... ... ... ... £1·80
8·100 MHz in HC6/U for TX x 18 to 145·800 MHz 2M RAEN

12:0933 MHz in HC6/U for TX × 12 to 145:000 MHz 2M Mobile Channel ... ... ... ... £1:60 8:7825 MHz in HC6/U for TX × 8 to 70:260 MHz 4M Mobile

Channel ... ... ... ... ... ... £1.60
You'll find the above frequencies may be suitable for your PYE
Cambridge, Ranger, Vanguard and other makes of ex-commercial

R/T gear for the now popular and well-used mobile call channels. Check up with crystal multiplication data in equipment manuals for suitability.

For IOM walkie-talkies with I.F. of 455 kHz to transceive on 28:500 MHz, we have in STOCK 28:500 MHz (TX) and 28:045 MHz (RX), at £1:60 each.

AVAILABLE SOON:

6746-667 kHz for PYE Ranger to receive on 70:260 MHz (4M Mobile Call Channel).

11.710 MHz for transmitters multiplying  $\times$  6 to 70.260 MHz.

72:500 MHz for  $\times$  2 to 145:000 MHz (useful for walkie-talkie projects, etc.).

CLUB and other GROUP projects: If your club or group is contemplating a constructional project requiring crystals, we can offer real keen prices for quantity orders.

Also, 200 kHz, 500 kHz, 8797-190 kHz for R.A.E.N., most crystals for G2DAF and other designs, and crystals for every amateur band always In stock. There are so many 1,000's more useful frequencies in the Bank that to list them all would take too long.

in the Bank that to list them all would take too long.

Why not telephone or write your enquiry to us? Experience proves that we are sure to have something very close to—if not spot-on—the frequency you require from 50 kHz thru 132 MHz in stock.

When telephoning, you can be assured of a speedy answer to your enquiry. All our stock is recorded (no computers—just hardworking staff).

Should you require crystals made to order—no problem. We can supply as follows: (PLEASE NOTE however, our crystals can only be as accurate as your specification).

3rd, 5th and 7th OVERTONE to an adjustment tolerance of  $\pm 0.005\%$  will hold 50ppm from -20 to + 70 deg. C. Available in HC6/U, 18/U and 25/U:

in HC6/U, 18/U and 25/U:
175 MHz to 200:0 MHz £12.00 60 MHz to 109:9 MHz £3.25
140 MHz to 179:9 MHz £8.75 17 MHz to 59:9 MHz ... £2.50
110 MHz to 139:9 MHz £7.00

FUNDAMENTAL MODE to an adjustment tolerance of ±0.005% available in HC6/U, 18/U and 25/U:
11.5 MHz to 20.00 MHz £2.50 4.0 MHz to 11.49 MHz... £2.50

The following in HC6/U only ±0.005% tolerance:

1-4 MHz to 3-9 MHz
£3-00

1-0 MHz to 1-39 MHz
£3-20

The following to ±0.01% tolerance:

500 kHz to 999 kHz in

150 kHz to 449 kHz in

Types available: Flexural Mode; NT Elements; J Plate; Duplex Elements.

SENATOR can supply crystal units to British and U.S.A. Defence specs.

Now you've read this advertisements, we naturally hope that you are "hooked" on SENATOR CRYSTALS; however, if you are not, deal with us once and we are sure that you will be. SENATOR know-how and 55,000 units actually in stock practically assures this.

Mail Order SENATOR CRYSTALS Dept. SW. 36 Valleyfield Road, S.W.16.

G3 X K F

G3×KF

# MINITENNA COMMUNICATIONS

Make your signal really heard with the NEW ALANDO

Compressor—Amplifier

Gain up to 2 S points and really add the talk power.

★ PP.3. 9v. operation.
★ Five Transistors
★ Input and output controls
★ Black crackle cabinet
★ Size 7" × 4" × 2" high

Each unit built and tested on the premises

Immediate delivery

Price: £11.25 P.P.25p

J. SHARRATT 8 PEBBLEMOOR, EDLESBOROUGH, DUNSTABLE, BEDS Tel. Eaton Bray 297

# The Amateur Radio Shop

# RIO COMMUNICATION RECEIVERS



PS-510 - TS-510 - VFO-5D

TS-510 SSB Transceiver covers all ham bands from 3.5-29.7 MHz Emission SSB (A3J), CW (AI) Input 160W at 3.5-21 MHz; 120W at 28 MHz. Antenna input imp. 50-70 ohms. Uses 14 valves, 2 FET's, 13 transistors, and 29 diodes. Circuits include YOX, PTT, amp. AGC, RIT, CAL, switching multimeter indicates 1p, RF, HV, ALC and signal strength. AGC switch terminals for external VFO, ALC and receiver input and output terminals. Size: 13 x 7 x 13\frac{x}{2}. PS-510 power supply for TS-510. Incorporates 6\frac{x}{2} communications speaker. Frequency response 150-5,000 Hz. Size: 7\frac{x}{2} x 8\frac{1}{2} x 11\frac{x}{2}. VFO-5D Variable Frequency Oscillator. Frequency range. Bands, 3:5-29.7 MHz. Oscillation frequency 49-55 MHz. Output voltage 1v. Power: A.C. 12.6v. 8-mA; D.C. 150v. 30 mA. Size: 7\frac{1}{2} x 8\frac{1}{2} x 7\frac{1}{2}.

Lasky's Price, TS-510 & PS-510, £180.00 (the pair), Post £2.50 VFO-5D, £25.00 Post 750



JR.310 SSB receiver. Frequency range: 3·5 MHz-29·1 MHz in 7 bands. Output SSB CW. Power supply A.C 110-120v,/220-240v., 6 valves, 6 transistors, 2 (FET's) and 19 diodes. Crystal controlled BFO for SSB reception 9 meter, ANL and calibrator circuit switch are provided, RIT circuit. Power output Iw max. Size:  $13 \times 7\frac{1}{16} \times 12\frac{1}{16}$ .

Lasky's Price £77.50 Post FREE

JR.500SE communications Rx. We have two only of this excellent model, S/H but perfect at £50 each from our Cavell Street address only.



9R-59DS 9R-59DS
9R-59DS SSB receiver. Frequency ranges: 550-1000 kHz: 1-6-4-8 MHz; 10-3-30 MHz. Bandspread: 3-5 MHz 80m-28 MHz 10m. Audio output 1-5 watts. Power A.C. I15/230v. Circuits ANL; AVC. Headphone jack. Size: 7 x 15 x 10".

Lasky's Price £47.50 Post FREE



JR-599 SSB receiver. All solid state. Frequency range: 1-8 MHz-29-1. MHz in 8 bands. Reception SSB, CW, AM and FM. Antenna input imp. 50-75 n.AF output more than lw. 10 FET's, 1 IC, 30 transistors, 37 diodes, A.C. 110/117/220/240v. 50/60 Hz. D.C. 12-15v. Size: 10½ x5½ x 12 7/32" Lasky's Price £185 Post FREE

Ask for full information on the above, and all other TRIO models and accessories.

# **ACCESSORIES**

TRIO HS-4 Headphones	£5·98
TRIO SP-5D Communications speaker	£4·38
Leson TW-205A Base station mic	£7.95
TTC G-1120 Head set/boom mic	£6.75
TTC H-1010 Wireless code practise	
oscillator	£1.50
TTC F-1003 Morse code practise set	£1.40
TTC F-1001 Key	45p
TTC F-1005 Semi-automatic bug key	£4.50
TTC F-1009 Code practise set	£1.20
TTC S-1020 Antenna selector	95 <sub>D</sub>
	£2.75
TTC C-3041 Field strength meter	EZ.13
	64 DE
meter	£4.25
TTC C-3005 SWR and power meter	£7·25
TTC H-1011 De luxe 5 band field	
strength meter	£3.95
TTC R-1014 A.CD.C. converter	£2·95
TTC R-2500 A.CD.C. converter	£3.95
Post 15p on all above	

Full range of JOYSTICK aerials available from stock (see separate advertisement).

# AIRCRAFT CONVERTER Model VHF 105

An item for the radio enthusiast bringing instant reception o the ground-to-air, air-to-ground waveband, for use with any standard AM or FM radio covering 535-1600 KHz, 88-108 MHz respectively—with no electrical conversion or connection required. The VHF 105 is self powered by one 9v, batt. placed close to the receiving set, volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the volume controls of each. Black plastic cabinet with brushed metal front panel. 18" chrome telescopic antenna. Size only  $4 \times 2\frac{7}{8} \times 2\frac{3}{8}$ ". Comp. with batt.



LASKY'S PRICE £3.60 Post 10p

# MIDLAND 10-406 AM/AIRCRAFT

The first pocket size receiver of its type allowing you to Into tirst pocket size receiver of its type allowing you to tune-in to the entire air communications band covered by 108–137 MHz in addition to full AM medium wave intermediate frequencies. AM 455 KHz: VHF 10-7 mc/s. Output power: 200 mV.  $2\frac{1}{2}$  P.D. 8 ohm speaker. A built-in ferrite rod aerial is provided for AM reception. The 10–406 is finished in blue with chrome trim. Chrome telescopic antenna. Size:  $6\frac{1}{8} \times 3\frac{3}{8} \times 1\frac{7}{8}$ . Comp. with batts. and magnetic earphone.



LASKY'S PRICE £8.35 Post 13p

# MAIL ORDERS TO: 3-15 CAVELL ST. LONDON E1 2BN 01-790 4821

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605 Open all day, 9 a.m.-6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833 Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42:45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01:580 2573 Open all day, 9 a.m. - 6 p.m. Monday to Saturday

# NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812 Open all day Thursday, early closing 1 p.m. Saturday

## T. & I. ELECTRONICS LTD.

where equipment is fully overhauled

			-	•	
TRIO TS510 & PS5					 £159.00 (£2.00)
EDDYSTONE 888					 £85.00 (£1.50)
KW2000A and A.C. STAR SR200					 £175.00 (£2.00) £40.00 (£1.25)
EDDYSTONE S640		•••			 £25.00 (£1.50)
EDDYSTONE EB3					 £45.00 (£1.25)
KW VESPA Mk. II			p.s.u.		 £105.00 (£2.00)
HEATHKIT "MOI		"			 £35.00 (£1.00) £28.00 (£1.25)
LAFAYETTE KT320 HEATHKIT RG-1	<b>.</b>		•••		 £33.00 (£1.25)
EDDYSTONE 6802	· · · ·				 £85.00 (£2.00)
LAFAYETTE HE-8					 £48.00 (£1.25)
EDDYSTONE EAL	2				 £150.00 (£2.00)
R.C.A. AR88LF TRIO 9R-59-DE		• • • •	• • • •	• • • •	 £50.00 (£2.00) £38.00 (£1.00)
KW-201					 £90.00 (£1.50)
HALLICRAFTERS					 £100.00 (£1.50)
HEATHKIT RA-I					 £35-00 (£1-25)

WE CAN ALSO SUPPLY ANY MAKE OF NEW EQUIPMENT—and have pleasure in giving a few examples which are normally in stock:—

WE CAN ALSO SUPPLY ANY MAKE OF NEW EQUIPMENT—and have pleasure in giving a few examples which are normally in stock:—

ANGLIA, 2 metre converters (state I.F. required), £15-00 (30p).

AVOMETERS, Model 7, Mk. 2, £37-60; Model 8, Mk. 4, £40-90; Model 9, Mk. 4, £40-90; Model 40, Mk. 2, £37-60; Model 8, Mk. 4, £40-90; Model 40, Mk. 2, £37-60; Model mk. 4, £40-90; Model 40, Mk. 2, £37-60; Model mk. 4, £40-90; Model 40, Mk. 2, £37-60; Model mk. 4, £40-90; Model 40, Mk. 2, £37-60; Model mk. 4, £40-90; Model 40; Standard leather carrying case (Models 7, 8, 9, 40), £6-50; Every-Ready (ILL), £150; Model EA113 Electronic Avo. £62-00. All above post free in U.K. Trade and Educational enquiries invited.

S. G. BROWN'S HEADPHONDES, Type "F" 120 ohms, 2,000 ohms, 4,000 ohms, £4-95 (25p); Rubber earpads for same, £5p epr pair (5p). Type 3C/1100 Noise excluding (with superb fitting), high quality, electrodynamic, £7-35 (25p); Standard Jack Plugs, 22p (4p). EDDYSTONE EQUIPMENT, Receivers, £307, £372-75; EA12, £205-00; EC10/2, £74-50; EC10/1, £64-50; 924 A.C. mains p.s.u., £7-75 (30p); General Purpose Speaker, 935, £371 (40p); Edometer, 902 Mk. 2, £29-50 (50p); Telescopic Aerial, Lp.3126, £2-50 (25p); Diecast Boxes, from £5p (10p). Brochure on request. (CODAR EQUIPMENT, ATS, £19-50 (35p); Edometer, 902 Mk. 2, £9-30 (55p); Elecast Boxes, from £5p (10p). Brochure on request. (CODAR EQUIPMENT, ATS, £19-50 (35p); PR30X, £9-30 (35p); Eleaflets on request. (PARTRIDGE "107STICKS.") New. Lightweight, £13-30 (40p); "107MATCH" LO-Z, £13-30 (30p); SM, £10-00 (30p); 3A, £4-20 (25p); TR, £9-67 (30p). Licerature on request.

PARTRIDGE "107STICKS." New. Lightweight, £13-30 (40p); "107MATCH" LO-Z, £13-30 (30p); SM, £10-00 (30p); 3A, £4-20 (25p); TR, £9-67 (30p). Licerature on request.

PARTRIDGE "107STICKS." New. Lightweight, £13-30 (40p); "107MATCH" LO-Z, £13-30 (30p); SM, £10-00 (30p); 3A, £4-20 (35p); TR, £9-67 (30p). Licerature on request.

PARTRIDGE "107STICKS." New. Lightweight, £13-30 (40p); 3A, £4-20 (40p); 24-20 (40p); 24-20 (40p); 24-2

At R.T. & I.

We have full H.P. facilities Part exchanges are a pleasure

We purchase for cash We offer a first-class overhaul service for your electronic equipment, whether

you are an amateur or professional user We have EASY Parking facilities

We welcome your enquiries for specific items which, although not advertised, may very well be in stock.

• • TRIO EQUIPMENT, Transceiver, TS-510 + PS-510 a.c. p.s.u., £180.00 (£2.00); VFC-5D for above, £32.00 (50p); Receivers, JR-559, £185.00 (£1.00); JR-310, £77.50 (£1.00); JR-500.5£, £65.00 (£1.00); 9R-59-DS £47.50 (50p); SP-5D Loudspeaker, £4.37 (40p); Headphones, HS-4, £5.97 (20p). NEW TR-599 TRANSMITTER (to match JR-599), £185.00 (£2.00). Leaflets available.
SHURE MICROPHONES, 444T, £15.00 (40p); 444, £13.00 (40p); 401A, £6.50 (30p); 201, £5.40 (30p). Full details on request. KEYNECTORS, piano key mains connector unit, £2.75 (25p). VALVES. Please state your requirements.

# OFFICIALLY APPOINTED K.W. AGENTS

KW EQ UIPMENT, KW2000B + A.C. p.s.u., £240-00 (£2-00); D.C. p.s.u. for KW2000B, £44-00 (50p); KW2000B only, £200-00 (£1-50); KW ATLANTA + A.C. p.s.u., £200-00 (£2-00); Remote V.F.O. for Atlanta, £34-00 (50p); VOX unit for Atlanta, £7-50 (25p); Remote V.F.O. for 2000B, £36-00 (50p); KW1000 Linear amplifier, £135-00 (£1-50); KW200 Receiver - crystal cal., £111-00 (£1-50); KW VESPA Mk. 2, + A.C. p.s.u., £135-00 (£2-00); KW202 Receiver with calibrator, £140-00 (£1-50); KW 202 Matching Spkr., £8-00 (80p); KW204 Transmitter, £142-00 (£2-00); KW105 combined E-Z Match; VSWR indicator, dummy load, and ant. switch (4 outlets) \$52 or 75 ohms, £30-00 (\$50p); KW103, VSWR and power meter, \$52 ohms, £12-50 (45p); KW101, VSWR meter, \$2 or 75 ohms, £92-55 (30p); also E-Z match, dummy load, trap dipoles, etc., etc. Details on request.

# R. T. & I. ELECTRONICS LTD.

Ashville Old Hall, Ashville Road, London, E.11

# AT LAST. - A '24' HOUR DIGITAL

OF TOP QUALITY AT A PRICE THAT WON'T BREAK THE BANK The Radio Amateurs' and S.W. Listeners' dream. Made by the famous COPAL/CASLON Company

**JUST LOOK AT THESE FEATURES** 

Incredible accuracy. 18 pole motor operating at low speed for long service life.

24 and 12 hour versions available.

Diffused lighting built in.


Available in 5 attractive colours-(White, Charcoal, Red, Lime and Purple).

Small, compact with beautiful 70's styling.

12 month guarantee.

ONLY **£8-25** 

 with free postage, packing and insurance.



Undoubtedly these clocks are the best value you have ever been offered. However, should you also require Day, Date, etc., you need the 601 or 602.

JUST LOOK AT THESE PRICES :-

COPAL/CASLON 601—Aluminium case, 12 or 24 hour 602—Same as 601 but super modern wood case £16.50 FREE—Post, Packing and Insurance on all clocks

Please Note: -Every single clock is carefully checked and tested by us. If after 10 days you are not completely happy, just return it for a full refund, without question.

DON'T DELAY - SEND TODAY - YOUR ORDER WILL RECEIVE IMMEDIATE ATTENTION.

AERO & GENERAL SUPPLIES, NANAIMO HOUSE, 2 RINGWOOD AVENUE, LEEDS, LS14 1AJ, ENGLAND. TEL.: 658568 TEL.: 658568

# NORTH WEST ELECTRICS

769, STOCKPORT ROAD,

LEVENSHULME.

MANCHESTER, 19.

Phone: 061-224 4911

# **G3MAX**

EDDYSTONE AND TRIO RECEIVERS. DIECAST BOXES.
JACKSON CAPACITORS AND DRIVES. DENCO COILS.
"RADIOSPARES" TRANSFORMERS AND COMPONENTS.
"O" MAX CUTTERS.

R209 Mk. II PORTABLE/MOBILE RECEIVER. I to 20 Mc/s. 12 volt D.C. operation. AM/CW/FM. Internal speaker. Ideal for caravan or small boat enthusiast. Checked and tested before despatch, £15, carriage £1. (Please add 50p for Irish orders.)

24 HOUR ELECTRIC CLOCK. COPAL 222. Very readable figures, ½" high. Front measures 5" x 2½". £8.75, P.P. 25p.

**CONTROL BOX.** 6"  $\times$  5"  $\times$  3". Contains 500ua  $1\frac{1}{4}$ " Meter. Desyn Res 180° travel, 4 rotary sws. 500 and 1k var res. the desyn will match our indicators by using 2 to 1 ratio on the drive, 87 $\frac{1}{2}$ p, P.P. 24p.

132ft. COPPER AERIAL WIRE. 7 strand 26 swg. fitted with 4 sets Bakelite chain insulators. 10ft. insulated lead in wire, supplied on 8" cable drum, 86½p, post 35p.

POLYPROPYLENE ROPE. 500lb. strain. 100 yd. reel, £1, post 15p.

MODULATOR, TYPE 105. Ex-TR 1986 series. 2-6C4 in push pull. EF92 Mic amp. EL91 driver. New, boxed with circuit, 75p, post 25p.

HEAVY DUTY WIRE-WOUND RESISTOR. 332 ohm .74 amp., 37½p, post 15p.

**SMALL POWER TRANSFORMERS.** Drop through Mtg.  $3'' \times 2\frac{1}{2}'' \times 2\frac{1}{2}''$ . Above chassis, post  $27\frac{1}{2}p$  each. 240v. 100mA. 6·3v. 2A. LT, £1·25, 180v. 40mA. 6·3v. 2A. LT,  $87\frac{1}{2}p$ . 180v. 25mA. 6·3v. 2A LT, 70p.

COAX LINK LEAD. 8' 6" cable with 2 Burndept/Londex coax plugs, 35p each, post 15p. (50  $\Omega$  impedance).

AR88 MAINS ON/OFF C.W. SWITCHES. New Boxed, 32½ p. post 5p.

VIBRATORS. 12 volt synchronous. Type No. 12SR7, 50p each. Special offer 3 for £1, postage 15p.

CONVERTER CHASSIS. New spares for transistorised UHF tuner. Contains 4 gang min. var. cap. 4 tube trimmers, in screened sections, 25p, post 15p.

JACKSONS 6/36 slow motion dial and drive, £1.55, post 15p.

CATHODE RAY TUBE 5FP7A. Brand new. Boxed, £1-25, post 25p.

WE WOULD BE PLEASED TO RECEIVE QSL CARD FOR DISPLAY

BROWN BROS. Twin lever paddle. The best for the CW enthusiast, £7-50, post paid in G.B.

VARICAP DIODES. SGS. BBY10-6-8pF, BBY11-10pF, BBY12-12pF, 25p each, post 5p.

RECEIVER UNIT R3673 20 to 90 Mc/s. Size 13" x 8" x 8". 10 channel. Motor selected. High quality converter unit into 7:5 Mc/s. IF strip. 19 valves. (13 EF91, 3 EB91, 1 EL91, 1 616, 1 EAC 91.) Small blower, 2 relays. Supplied with circuit and modifications, £3-50, plus postage £1. All tested before despatch. (Pease add extra 50p for Irish orders.)

CV416 (6F17) VALVE, 30p each, post 5p, or 4 for £1-20, post paid.

PLEASE NOTE OUR NEW PREMISES ARE OPEN FOR BUSINESS AND THEY ARE MUCH IMPROVED FOR DISPLAY AND SALES.

WE ARE ABLE TO OFFER BETTER FACILITIES AS REGARDS RECEIVER DEMONSTRATIONS.

NO PARKING RESTRICTIONS.
NO INCREASE IN PRICES.

5" DESYN INDICATOR, 75p, post 25.p

3" DESYN INDICATOR. 62½p, post 20p. Compass degrees and corrector on 5" Desyn only.

200 + 200 + 100 mfd. 350v. D.C. wkg.,  $4\frac{1}{2}$ " x  $1\frac{3}{4}$ ",  $37\frac{1}{4}$ p each, post  $12\frac{1}{2}$ p. 10 for £3·00 post 25p. Ideal for high voltage psu. 10 in series makes 50 mfd. 3·5 Kv.

MAINS TRANSFORMER FOR AR88LF. Brand new, £2.00, post 50p.

Business Hours: Tues.-Fri., 9.30 a.m. to 6.30 p.m. SATURDAY: 9 a.m.-5 p.m. OPEN ALL DAY. CLOSED ALL DAY MONDAY.

WE WELCOME ALL ENQUIRIES HOWEVER SMALL Stamped addressed envelope please.

## **HY-GAIN PRODUCTS FROM RADIO SHACK** VERTICAL ANTENNAS and ACCESSORIES HIGH PERFORMANCE MONO-BAND BEAMS 4 Flement 20 metre Beam ... £68·50 6 thru 80 metre Vertical "Hy-204B A IRHT €89.50 203BA 3 Element 20 metre Beam ... £66.50 Tower" 10 thru 20 metre Vertical 3 Flement 15 metre Beam ... £32.00 I SSRA 12 AVO Trapped Antenna ... €15.50 103BA 3 Element 10 metre Beam £23.00 14 AVQ/WB 10 thru 40 metre Vertical HAMCAT MOBILE ANTENNAS Trapped Antenna ... ... 18 AVT/WB 10 thru 80 metre Vertical €18.50 Mobile Mast with foldover hinge and swivel base £8.50 80 metre Coil and Tip Rod Trapped Antenna .. £32.50 252 £9.75 10 thru 80 metre Vertical 40 metre Coil and Tip Rod ... 20 metre Coil and Tip Rod ... IR V 256 €8.75 £9.75 255 £8.00 Antenna Roof Mounting Kit for 12 AVO 15 metre Coil and Tip Rod 254 12 RMO £8.50 £6.50 253 £5.50 14 RMO Roof Mounting Kit for 14 10 metre Coil and Tip Rod Coil and Tip Rod Spring AVO/WB €9.75 492 £1.50 ... LC 80O 80 metre Loading Coil for 14 499 Flush Body Mount £4.75 ANTENNA ACCESSORIES and COAX AVO/WB £6.50 TE 7-01 Omega-T Systems Antenna TRI-BAND BEAMS and QUADS Noise Bridge. I-100 MHz ... TH6DXX Super Thunderbird 6 Element £13.50 Omega-T Systems Antenna 10-15-20m. Beam TE 7-02 £84.00 Noise Bridge. I-300 MHz ... Thunderbird 3 Element 10-15-TH3MK3 £19.50 20m. Beam £67.50 **BN 86** Broadband Ferrite Balun for use TH31R 3 Element 10-15-20m. Beam. €7.75 with any beam 600W PEP rating £46.50 RG-8A/U Heavy Duty 52 ohm Coaxial Cable ... 37p TH2MK3 Thunderbird 2 Element 10-15-Cable ... ... per yd. Connectors for RG-8A/U Cable PL-259 20m. Beam ... £48.00 35p HY-OUAD 3 Band 2 Element Cubical Ouad. PL-258 Adaptors for joining two PL-259 Sgl. Feed Line 461.00 Connectors ... 90p DB10-15A 10 and 15 metre Duo-Band Beam £50.00 LA-I Lightning Arrestor £14.25 ... In-Line Lightning Arrestor Carriage extra on all items LA-2 £2.50 182 BROADHURST GARDENS. LONDON, NW6 3AY. TELEPHONE 01-624 7174 CABLES: RADIOSHACK LONDON NW6 3AY GIRO ACCOUNT NUMBER 588 7151

# **AMATEUR ELECTRONICS**

BIRMINGHAM 021-327 1497 021-327 6313

WE URGENTLY REQUIRE all types of quality used equipment with a particular emphasis on top name gear, i.e., Collins Drake, etc., etc., and where necessary we can arrange collection and provide an immediate cash settlement. We have a requirement for high quality general coverage Receivers of British and American manufacture with particular reference to the more sophisticated types.

Below we show our current stock position, demonstration facilities for which are available for the caller and all items on offer may be tried on our premises without any obligation whatsoever on the part of the prospective purchaser. This facility, of course, also applies to new gear available from stock, i.e., Trio, KW, and Yaesu Musen and we would point out we have good stocks of the JR-310 Receiver which received such an excellent write-up in the last issue of "Radio Communication".



the state of the s	Wilco-up II	Telle last issue of italio communication :	
	£	<b>▼</b>	
COLLINS 51-J4 GENERAL COVERAGE RECEIVER. Fitted all filters, superb performance and a delight to handle.		TRIO 9R59DE RECEIVERS. Several in stock in first-class	38.00
Slight superficial external marks	252 - 50	unmarked condition EDDYSTONE 740 RECEIVER. Externally poor but FB for	38.00
COLLINS 75-A2 AMATEUR BAND RECEIVER. Again	232.30	its paid the 740 RECEIVER. Externally poor but PB for	31.00
typically Collins in performance and condition similar to above	137 - 50	EAGLE SR-165 RECEIVER. General coverage with band	21.00
NATIONAL NCI83D RECEIVER. General coverage with	137.30	EAGLE SR-103 RECEIVER. General coverage with band	
excellent amateur band spread. A most interesting Receiver		EDDYSTONE ECIO RECEIVERS. Several Mark I's in stock	35.00
excellent anateur band spread. A most interesting Receiver	87 - 50	EDDTS TO NE ECTO RECEIVERS. Several Mark I's in stock	
in unusually good condition EDDYSTONE 940 RECEIVER. Too well-known to describe	87.50	rrom	45 - 00
but this one is in absolutely mint condition	110.00	TRIO VFO-5D EXTERNAL VFO. Good condition	16.00
HEATHKIT SB300 RECEIVER, complete with SB610	110.00	NATIONAL NC-190 RECEIVER. Unmarked and first-class	47 - 50
Monitor scope, both in immaculate condition	135.00	HEATHKIT SB-300 RECEIVER. Unmarked and mint	95.00
SOMMERKAMP FR-100B and FL-200B SEPARATES.		TRIO JR-500SE RECEIVER. Further supplies are now avail-	73.00
Both in exceptional unmarked condition, the Receiver		The state of the s	
covering top band also	165-00	able of used sets in mint condition with 3 months warranty	55 - 00
SOMMERKAMP FR-100B RECEIVER, unmarked	70.00	AR88LF and AR88D RECEIVERS. Further supplies of used	
KW2000 TRANSCEIVER excellent clean condition	120.00	sets now en route from	45.00
EDDYSTONE 750 RECEIVER. Average condition externally,	120.00	Full details upon request.	
excellent performance	40.00	AR88D CERAMIC WAVE CHANGE SWITCHES, as	
EDDYSTONE 840C RECEIVER. Just arrived, well above	40.00	previously advertised	I · 25
average	46.50	BC221 FREQUENCY METERS. First-class fully tested con-	
EDDYSTONE EAI2 RECEIVER. Just arrived, absolutely	40.30	dition, complete with correct charts	22.50
EDDISIONE EAIL RECEIVER. Just arrived, absolutely	150.00	MEDCO FILTERS. Belling Lee connector, 75 ohm models	
immaculate SWAN 350 TRANSCEIVER. Complete with 220 A.C. p.s.u.	150-00	available ex stock but our apologies for the delay with all	
SWAIN 330 INANSCEIVER. Complete With 220 A.C. p.s.u.		types using UHF connectors due to production difficulties.	
Very nice condition, fully air tested	155-00	G-WHIP MOBILE ANTENNAE. All models available	
HAMMARLUND HQ145 RECEIVER. Typical Hammarlund		ex stock.	
construction and performance, good condition HEATHKIT HW-I2 80 metre TRANSCEIVER. Complete	65 - 00	KW ACCESSORIES. All items available ex stock.	
MEATINE DIV-12 OU METE I KANSCEIVER. Complete	67 - 50	TTC C3042 50 ohm SWR BRIDGES each	4.50
with HP-23A p.s.u. HEATHKIT DXI00 TRANSMITTER, fairly clean condition	39.50	TTC C3005 50 ohm SWR BRIDGES but with twin meters each	7.50
HEATHKIT DX100 TRANSMITTER with SB-10U SSB	37.30		7.30
	55.00	TTC PTT Fist mikes. Metal body excellent communication	
		microphone earh	3 · 5
REMEMBER! All items listed are priced to include carriage	and our ne	ew credit terms, as announced last month, require a deposit of Ino	/- only

ER! All items listed are priced to include carriage and our new credit terms, as announced last month, require a deposit of of the published price, with the balance spread to suit your own requirements.

PLEASE NOTE an S.A.E. with your enquiry will ensure a prompt reply.

ELECTRON HOUSE, 518-520 ALUM ROCK ROAD, BIRMINGHAM 8

# The Outstanding Heathkit SB-303



Kit K/SB-303 £175. Carr. 70p.

# the "303" . . . the new standard of performance in receivers

■ State-of-the-art solid-state circuit using 27 silicon transistors including 4 dual-gate, diode protected MOS-FET'S plus I IC Heath factory assembled solid-state Linear Master Oscillator for instant warmup, improved stability & more accurate tracking A unique Heath design using 9 modular plug-in circuit boards ■ Receives USB, LSB, AM, CW & RTTY ■ Complete 80-10 M coverage plus 15 MHz WWV for exact calibration ■ 25 kHz & 100 kHz calibration markers Front panel selection of antenna & power connections for up to two VHF converters with rear panel jacks built-in Fast & Slow AGC selectable from front panel Front panel selection of built-in 2.1 kHz SSB crystal filter or optional AM & CW crystal filters Built-in extremely stable solid-state power supply with circuit breaker protection 

Speaker and/or headphone selection from front panel 

Handsome SSB-Series styling in a smaller package than the famed SB-301 Easy, enjoyable assembly with the famous Heathkit manual.

# PROFESSIONAL SHORTWAVE, SB-310 KIT

Frequency range (MHz) 3:5-4:0; 5:7-6:2; 7:0-7:5; 9:5-10:00; 11:5-12:0; 14:0-14:5; 15:0-15:5; 17:5-18:0; 26:9-27.4; (cabar accessed) 27-4; (other options). Less than 100 Hz drift. Selectivity 5.0 kHz at 6 dB-15 kHz at 60 dB.



SB-310 £125 Carriage 70p

# DE-LUXE SHORTWAVE, GR-54 KIT

2 MHz to 30 MHz plus 550 kHz to 1550 kHz, 180 kHz to 420 kHz. Tuned RF. Crystal filter. Product detector. AM/ SSB/CW. Noise limiter. Sleek styling. Charcoal grey metal cabinet. 120-240v. A.C.



GR-54 £53 Carriage 60p

# LOW COST 4-BAND, GR-64 KIT


3 shortwave bands cover I MHz to 30 MHz, plus 550 kHz to 1620 kHz. Built-in 5" speaker. 7" slide rule dial 4-valve superhet circuit. Handsome styling. 110-240v.



GR-64 £25 Carriage 50p
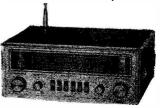
# SOLID-STATE GENERAL COVERAGE. GR-78 KIT

Tunes from 190 kHz to 30 MHz in six bands. Double conversion above 18 MHz. AM/CW/SSB. Nickel Cadmium Battery charges from 240v. A.C. or 12-15v. D.C. Modular construction. Durable construction charcoal and matching



GR\_78 660 Carriage 45p

The new credit t	erms are a	s follows
Total cash value inc. carriage	minimum deposit	Period of repayment
up to £15 r	no credit te	rms
£15—£50	10%	12 months
£50—£100	10%	12 or 24 months
over £100	20%	12, 24, 36 months

GR-76 £69 Carriage 43p
Please send me free catalogue  Tick here.
Please send me specification sheets for models
Name
Address
Post Code
Attractive Credit Facilities available
HEATH (Gloucester) LTD. GLOUCESTER, GL2-6EE



A Schlumberger Company

56/10



# "LISTEN TO THE WORLD WITH EDDYSTONE"

# Your local Eddystone dealer is:

# **CHESHIRE**

The Transistor Centre (Wilmslow) Ltd. Green Lane Wilmslow 24766

# CORNWALL

R. V. Heming Ltd (Peter Heming G3WBW). Cliff Road, Newquay.

Newquay 2191

.S.B. Products (Norman Birkett G3EKX)
7 Little Castle Street

Devoran 862575

# DERBYSHIRE

J. & A. Tweedy (Electronic Supplies) Ltd 64 Lordsmill Street Chesterfield 4982

# DEVON

Graham Newbery (Reg Ward G 2BSW) Axminster Axminster 3163

# **ESSEX**

F. E. Smith 184 Moulsham Street Chelmsford Chelmsford 54594

Unique Radio Ltd. 6 The Facade, High Road Goodmayes, Ilford 01 590 8277

# HAMPSHIRE

Southern Marine Radio Solent House, Town Quay Town Quay 22721

Wireless Supplies Unlimited 264-266 Old Christchurch Road Bournemouth Bournemouth 24567

# **IRELAND**

John F. MacMahon 10, Church Street, Enniskillen, Co. Fermanagh, N. Ireland Enniskillen 2055

# ISLE OF WIGHT

Sherratt & Son 81-82-83 High Street, Newport Newport 3358-9

# KENT

G. T. & R. Wilson 12-14-16 Queen Street Gravesend Gravesend 63527/8

# LANCASHIRE

Stephen-James Ltd 70 Priory Road, Anfield Liverpool L4 2RZ 051-263 7829

North West Electrics 769 Stockport Road Levenshulme, Manchester 19 061-224 4911

Croftfilm Ltd 46 Friargate
Preston PRI-2AT Preston 55244

# LEICESTERSHIRE.

A. K. Davey Ltd New Street, Hinckley Hinckley 2173 and 4288

Hardie 542 George Street Aberdeen Aberdeen 20113

Cosh and Hammond

29 Beach Road, Littlehampton

Littlehampton 4477 or 4478

SCOTLAND

# SUSSEX LONDON

Imhofs (Retail) Ltd 112-116 New Oxford Street W.C.1 01-636 7878

R. T. & I. Electronics Ltd Ashville Old Hall Ashville Road Leytonstone, E.11 01-539 4986

Radio Shack Ltd 182 Broadhurst Gardens London, N.W.6 01-624 7174

# WALES

Holt High Fidelity Picton Arcade, Swansea Swansea 53254

Holt High Fidelity 8 Portland Street, Swansea Swansea 41032

# WARWICKSHIRE

Chas. H. Young Ltd 170/172 Corporation Street Birmingham 4 021-236 1635

# **YORKSHIRE**

Philip Cann Ltd Chapel Walk, Fargate Sheffield S1 1GJ Sheffield 29225/6

Short Wave (Hull) 24a Newland Avenue Hull, HU5 3AF Hull 408953

# NORFOLK

The Record Shop 157 King Street Great Yarmouth

NORTHUMBERLAND

Newcastle upon Tyne 26729

Aitken Bros & Company 35 High Bridge Newcastle upon Tyne NE1 1EW

# RADIO COMMUNICATION HANDBOOK

Fourth Edition of the Original RSGB "Amateur Radio Handbook"

Price £3.15

(+ post and packing 35p.) Available from stock

Order from

PUBLICATIONS DEPT. SHORT WAVE MAGAZINE LTD., 55 VICTORIA STREET, LONDON, S.W.1

# **GUIDE TO BROADCASTING STATIONS**

16th Edition

Illiffe & Son Ltd. 164 bages.

58p (inclusive of p & p.)

CONTENTS

Long- and Medium-Wave European Stations: Some L.W. and M.W. Stations outside Europe : Short-Wave Stations of the World. Stations outside Europe: Short-Wave Stations of the World: Map of Broadcasting Regions: European Standard Frequency Transmitters: Short Wave Broadcasting Bands: Wavelength and Frequency Conversion: European Television Stations: European VHF Sound Broadcasting Stations: Internationally Allocated Call Signs.

Available from stock

PUBLICATIONS DEPT.

SHORT WAVE MAGAZINE 55 VICTORIA STREET, LONDON, S.W.I

# **ELECTRONICS** LOWE

# 119 CAVENDISH ROAD, MATLOCK, DERBYSHIRE.

Matlock 2817 (2430 evenings)

Bill G3UBO

Alan G3MME

# **AGENTS**

(evenings & weekends only)

John

16 Harvard Road, Ringmer, Lewes, Sussex.

G3.IVG

Ringmer 8071

Cim

19 Ellismuir Road, Baillieston, Nr. Glasgow.

**GM3SAN** 

041-771 0364

## CAVEAT EMPTOR

We are the authorised Yaesu Musen Co. Ltd. distributor for the U.K. and guarantee all Yaesu products sold by us for 12 months. We do not and cannot guarantee Yaesu products sold from sources other than ourselves, so if there is any doubt as to the validity of guarantee and after-sales service, you are advised to check with us.

I don't like to have to print the above, but I just have to in self defence. I would be the last person to tell you where to buy your gear and if you can get it from another source closer to you, maybe get it a bob or two cheaper, maybe get it a bit quicker, jolly good luck to 'ee, sir, nobody can blame you. ONLY DON'T EXPECT US TO PROVIDE SERVICE AND SPARES.

## NEW EQUIPMENT

Yaesu:

FTdx560 560W p.e.p. transceiver, £195.

260W p.e.p. mobile/fixed station transistorised transceiver, £230. FT\_IOI

FT\_200

260W p.e.p. transceiver, £132 (p.s.u. speaker, £35). Receiver. Super de luxe version with FM FRdx400

discriminator, four true mechanical filters and two VHF converters, £160.

FLdx400 Matching transmitter, £140.

FL-2000B Matching linear, £130. FT-2F 2m FM mobile transceiver, £80.

Matching speakers, £10. External VFO's, £35.

New Model: FT-401

Not yet officially available on the European market. The factory policy is to give a new rig a jolly good whirl on the Far East market before exporting to the States or Europe. Get any bugs out of it first. Not a bad policy (as owners of the very early FT-101's will readily testify!!). Same remarks apply to the 2m. transverter which I'm told is available in the Far East. You please yourself, but personally I'll hang on a bit until I'm quite sure about it.

# Inque :

New Model: 1C-20

Restyled IC-2F retaining all the valuable features with one or two minor improve-

ments, £80.

We have just received a batch of IC-700R We have just received a back of it—fluor receivers—these are the solid state amateur band receivers with the top quality 9 MHz crystal filter at a reduced price of 275. At the old price they were a best buy, and at this price they are an absolute

F.E.: FE-600 200W p.e.p. transceiver. Excellent value at a rock bottom price. A ready-built 80-10 200W p.e.p. (2 x 6146B's) transceiver with built-in p.s.u., VOX, MOX, PTT, RIT, etc. Everybody thinks there's a catch-it

can't be any good at such a low price. Nonsense, gentlemen—just listen to them on the air or come along and try one at our QTH. Convince yourself. The daftest thing I ever did was to underprice them in the first place. However, let's see if I can move 'em at £130 (And if anyone wanting a low priced rig misses this then they want their nut examining!).

1500W p.e.p. linear. Excellent value, 5-6KD6's, electronically regulated screen voltage, built-in L.P.F. and S.W.R. meter, £100. FE-3500

Digital 500D Yeah man. £275.

Street new stuff includes the YD846 mike at £5 (this is the one supplied with the FT-I01—sound nice, don't they?) and the de luxe table mike YD844 at £10. Keys £1, EK-9X keyers, £8.20, low impedance padded headsets, £2.50 without plug, £2.60 with stereo plug, 12 hour digital clocks, £5.80. Crystal filters KVG XF-9A, B, C, D and M all in stock, as well as the TEW and Kokusai. Fresh batch of Asahi dual meter SWR meters, £6.80. Power meters/dummy loads, these are a very superior job, switchable 20 or 120 watts, VSWR 1.2 or better. 50 ohms 3-500 MHz, £32 75 ohms 3-150 MHz, £30.

VHF men-at last a decent piece of gear at a reasonable price. VHF mobile whips: the G-whip & vertical at £4·10 plus 15p postage—just the job for the mobile IC-2F, IC-20 or FT-2F.

All prices post free except where stated.

# SECOND-HAND EQUIPMENT

Receivers :

JR-310, **£55.** JR-500. £45.

FR-100B, £80. NC-190, £45. Star SR-700, £60.

Transmitters: Viceroy II, £55. FL-200B, £85. FL-500, £100. Star ST-700, £75. мисн MORE STOCK

Transceivers: Swan 350, £130.

Trio 510, £135. KW2000A LESS p.s.u., £120.

# SERVICE

In order to give an even better deal to our customers, we have appointed the following part-time (evenings and weekends) Regional Service Representatives :-

Dave Dryden, G3BKQ Alan Bartlett, GW3YSA 205 Main Street, Thornton, Leics.

35 Pen-y-Waun, Efail Isaf, Nr. Pontypridd, Glam.

Tel. Newton Llantwit 3809

Peter Ward, G3XWX

47 Radstock Avenue, Ward End, Birmingham, B36 8HD.

Naturally, if you can get your gear to Matlock we would be delighted to see you and of course our Northern and Southern Agents, Sim and John are very adept at fixing gear in a hurry, but possibly there is an authorised Regional Service Rep. nearer to you who can sort out your problems in double-quick time. In which case, it may pay you to take your gear to him for prompt attention at low cost. Please drop us a line enclosing s.a.e. and we will send you all our guff.

Hours: Tuesday to Saturday 9-5.30 (closed for lunch 1-2 and all day Monday).

73 de Alan and Bill

# BUILT IN MECHANICAL FILTER 8 TUBES COMMUNICATION RECEIVER 9R-59DS



# TRIO'S 9R-59DS FOR SELECTIVE SUPERIORITY


The thrills of amateur short wave communication can be a joy forever. With TRIO's 9R-59DS communications receiver you can be assured of repeated adventure. TRIO's modern engineering techniques are especially apparent in its mechanical filter which achieves amazingly superior selectivity. For the thrill of a lifetime tune in with TRIO's 9R-59DS.
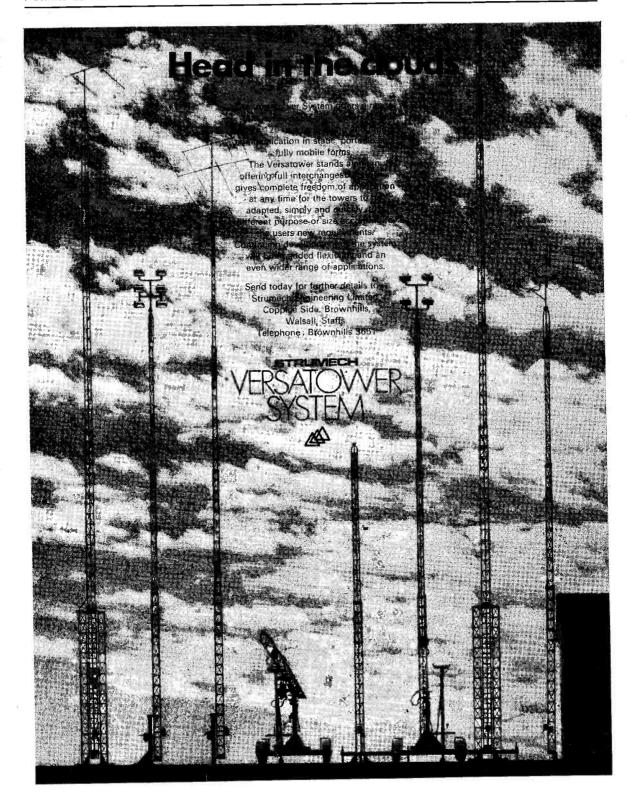
# SPECIFICATIONS:

• Frequency Ranges: Band A 550-1600KHz, B 1.6-4.8MHz, C 4.8-14.5MHz, D 10.5-30MHz, • Sensitivity: 2µV for 10dB S/N Ratio (at 10MHz) • Selectivity ± 5KHz at −50dB • Power Consumption: 45 watts • Audio Power Output; 1.5 watts • Tube & Diode Complement: 6BA6 × 3, 6BE6 × 2, 6AQ8 × 2, 6AQ5, SW-05S × 2, SW-05 × 2, IN60 × 2. • Dimensions: Width 15", Height 7", Depth 10".







# **Technical Books and Manuals**

(ENGLISH AND AMERICAN)

AERIAL INFORMATION	HANDBOOKS AND MANUALS
AERIAL INFORMATION  ABC of Antennas	Amateur Radio DX Handbook £2.15  Electronic Circuit Handbook, Vol. 1 £1.40  Electronic Circuit Handbook, Vol. 2 £1.40  Mobile Handbook, CQ £1.38  Mobile Manual, ARRL £1.38  New RTTY Handbook £1.78  New Sideband Handbook, CQ £1.43  Novice Handbook Tx & Rx £1.80  Radio Amateur Handbook 1971 (ARRL) £2.80  Radio Amateur Handbook 1971 (ARRL)
	(Hard Cover) £3.60 Radio Communication Handbook ( <i>RSGB</i> ) £3.50 Radio Handbook, W.I. Orr (18th) . • • • • • • • • • • • • • • • • • •
BOOKS FOR THE BEGINNER  Amateur Radio (Rayer)	Radio Handbook, W.I. Orr (18th) O/P Rtty A-Z (CQ Tech. Series) £2.23 Surplus Conversion Handbook . £1·35 Transistor Substitution Handbook . 98p  USEFUL REFERENCE BOOKS
Beginners Guide to Electronics (N.E.)  Beginners Guide to Transistors	Amateur Radio SSB Guide £1.57 Amateur Radio Techniques (N/E) £1.13 Amateur Radio Construction Projects £1.10 Amateur Radio Circuit Book 70p Elements of Radio Engineering O/P Guide to Amateur Radio 47p Engineers' Pocket Book 80p 'G' Call Book 1971 52p Hams' Interpreter 55p Hints & Kinks, Vol. 8 (ARRL) 60p Radio Amateur Examination Manual 31p Operating an Amateur Radio Stat. 16p Radio Amateur Operator's Handbook O/P Radio Data Reference Book (2nd Edition) Radio, Valve and Transistor Data (Iliffe) 9th Edition 75p
GENERAL  Easibinder	Radio Engineer's Pocket Book Service Valve & Semiconductors Equivalents Ients Single Sideband for the Radio Amateur (ARRL) 4th Edition Single Sideband for the Radio Amateur (ARRL) 5th Edition Sun, Earth & Radio by J. A. Ratcliffe Sun, Earth & Radio by J. A. Ratcliffe Surplus Schematics (CQ) Transistor Pocket Book Transistor Pocket Book A on Audio A A on Electronics Sun & A on Transistors (3rd Edit.)  VHF PUBLICATIONS
Television Explained Vol. I	VHF Handbook, Wm. I. Orr       £1 · 77         VHF Manual (ARRL)       £1 · 35         VHF/UHF Manual (RSGB) N/E       . £1 · 75

The above prices include increased postage rates and packing.

Delivery is from stock.

(O|P = out of print)

# Available from

# SHORT WAVE MAGAZINE

Publications Dept., 55 Victoria St., London S.W.1

01-222 5341

(Counter Service. 9.30-5.15. Mon. to Fri.)

(Nearest Station: St. James's Park)

(GIRO A/C. No. 547 6151)



Our New 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 272 pages, fully illustrated and detailing thousands of items at bargain prices.

SEND NOW! STILL ONLY 37 to P&P 10p.

TRIO TS 510 AMATEUR TRANSCEIVER with speaker and mains P.S.U., £180. TRIO JR310 AMATEUR BAND 10-80 Metre Receiver, £77-50.

## ADMIRALTY 62B RECEIVERS



High quality 10 valve receiver manufactured by Murphy, Five bands 150-300 Kc/s.; 560 Kc/s.

1-15 Mc/s.; 3-9-30-5 Mc/s.; Incorporates 2 R.F. and 3 i.F. stages band-

R.F. and a i.i. stages, band-limiter, crystal stages, band-pass filter, noise limiter, crystal controlled B.F.O. calibrator, I.F. output, etc. Built-in speaker, out-put for phones. Operation 150/230 volt A.C. Size 19½" x 13½" x 16". Weight 114 lbs. Offered in good working condition, £22-50. Carr. £1-50. With circuit diagram. Also available B41 L.F. version of above. 15 Kc/s.—700 Kc/s. £17-50. Carr. £1-50.

DUMMY LOAD RESISTORS

Carbon 30 Ω 35w., 27+p. P.P. 7+p

# CRYSTAL CALIBRATOR No. 10



Small portable crystal controlled wavemeter. Size 7" x 7½" x 4". Frequency range 500 Kc/s.-10

# **MULTI-METERS**

Model TE-300. 30,000 O.P.V. Mirror scale, overload protection 0:-6/3/15/60/300/1/200v. D.C. 0/6/30/120/600/1/200v. A.C. 0/30uA/6mA/60mA/300mA/600mA. 0/8K/80K/80K/8 meg. ohm-20 to + 63 dB., £5.97½, P.P. 15p.

Model TE-90. 50.000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200v. D.C. 0/6/ 30/120/300/1,200v. D.C. 03/6/60/600 mA. D.C. 16K/16K/1-6/16 MEGΩ. —20 to +63 dB., £7-50, P.P. 15p.

# UR-II SOLID STATE COMMUNICATION RECEIVER



4 bands covering 550 Kc/s.-30 Mc/s. continuous. Special features are use of FET transistors, S Meter, built-inspeaker, variable BFO for SSS reception, noise limiter, bandspread control, sensitivity control. Output for low imdepance head-phones. Operation 220-240v. A.C. or 12v. D.C. Size: 12½" × 4½" × 7". Excellent value. Only £24-00. Carr. 37½p.

# CLASS D WAVEMETERS



A crystal controlled heterodynefrequency meter covering 1:7-8 Mc/s. Operation on 6 voits D.C. Ideal for amateur used condition, and condition of 55.97±. Carr. 37‡p or brand new, £7.97½. Carr. 37‡p.

# TEI5 TRANSISTORISED GRID DIP METERS





HANSEN SWR-3 BRIDGE Impedance 52 ohms. Also operates as field strength indicator, complete with telescopic aerial, £3-47½ each. P.P. 17½p. PL259 plugs to suit 37½p each.

CODAR EQUI	MENT
CR.70 Receiver	£22·50
CR.45 Receiver	£14-50
	£11.50
PR.30 Preselector	£7·50
PR.30X (Built in P.S.	
RQ.10 Q Multiplier	
RQ.10X (Built in P.S.	
AT.5 MK.II Transmit	
T.28 Receiver	£17·50
12/MS Mobile P.S.U.	£11.50
12/RC Control Unit	£2.50
ATS Mains P.S.U.	£11.00
Mini Clipper Kit	£2·95

LAFAYETTE HA.800 SOLID STATE AMATEUR COMMU-NICATION RECEIVER SIX BANDS 3-5-4, 7-7-3, 14-14-35, 21-45, 28-29.7, 50-54 Mc/s.

Dual conversion on all bands. 2 x 455 Kc/s. mechanical filters. Product detector Variable B.F.O. 100 Kc/s. crystal calibrator. "5" meter Huge slide rule dial. Operation 230v. AC or 12v. DC. Size 15" x 9½" x 8½". Complete with instruction manual, £50-50. Carr. paid (100 Kc/s. Crystal £1-97½ extra).



# UNR-30. 4 BAND COMMUNICATION PECEIVER

Covering 550 Kc/s.-30 Mc/s. Incorporates variable FOB for CW/SSB reception. Built-in speaker and phone jack. Metal cabinet. Operation 220/240v. A.C. supplied brandnew, guaranteed with instructions, £15-75. Carr. 37-jp.

TRIO 9R59DS

4 band covering 550 Kc/s. to 30 Mc/s. continuous and electrical bandspread on 10, 15, 20, 40, and 80 metras. 8 valve plus 7 diode circuit 56/50 when the second seco

TRIO COMMUNICATION TYPE HEADPHONES. £5.97½, our price £3.75 if purchased with receiver. Normally



97‡, our price £3-75 if purchased with receiver.

NEW LAFAYETTE SOLID STATE HA600 RECEIVER
5 Band AM/CW/SSB amateur
and short wave 50 Kc/s.-400 Kc/s.
and 50 Kc/s.-30 Mc/s.
F.E.T. front end. 2 Mechanical filters.
Huge Dial. Product detector.
Variable BFO. Noise limiter, S Meter.
24\* Bandspread. 230v. A.C.//2v.
D.C. Neg. earth operation. R gain
control. Size: 15" x 92" x 82".
Carr. 50p.

# TRIO JR-500SE AMATEUR RECEIVER



TRIO JR-500SE AMATEUR RECEIVER
7 separate ranges between 3·5 and 29·7
Mc/s. 7 valves, 2 transistors and 5
diodes plus 8 crystals: output 8 and
500 ohm and 5000 ohm phone jack.
Crystal controlled oscillator.
Variable BFO. VFO. AVC. ANL.
S meter . SSB-CW . Stand-by
switch . special double gear dial
drive socket for connection to a
transmitter. I15/250v. A.C. Mains.
SFD speaker and HS4 headphone, £69·50.

EDDYSTONE VHF RECEIVERS.

EDDYSTONE VHF RECEIVERS
Model 770R, 19–165 Mc/s. Excellent
condition, £150-00.

B.C.221 FREQUENCY METERS
Latest release 125 kHz-20 MHz.
Excellent condition. Fully tested
and checked and complete with
calibrator charts, £27-50 each.
Core 500. Carr. 50p.

HAMGEAR PRESELECTORS
Mains operated 7-5-30 Mc/s.
£7-50, P.P. 20p.

AR88 MAINS TRANSFORMERS Brand new, boxed, £2-97½, P.P. 25p.

JOYSTICK AERIALS
Full range of Aerials and Tuners
in stock.

# CLEAR PLASTIC PANEL METERS

First grade quality, Moving Coil panel meters, available ex-stock, S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows. Type MR.38P. 1 21/32in. square fronts.



50 ± 50 100 vs. 1 pp 1 100 ps. 4 1.87 ± 100 ps. 4 1.87 ± 100 ps. 4 1.87 ± 100 ps. 4 1.75 ± 200 ps. 4 1.75 ± 500 ps. 4 1.37 ± 1.00 ps. 4 1.37 ± 5 ms. 4 1.37 ± 10 ms. 4 1.37 ± 750 ms. £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ £1 · 37 ½ I amp 2 amp 5 amp 20mA 50mA 150mA 200mA 300mA 300mA 500mA 300 DC 10v DC 20v DC

FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET.

27 TOTTENHAM CT. RD. LONDON, W.1 3 LISLE STREET, LONDON, W.C.2 34 LISLE STREET, LONDON, W.C.2 311 EDGWARE ROAD, LONDON, W.2 OPEN 9-6 MONDAY TO SATURDAY

Tel: 01-636 3715 Tel: 01-437 8204 Tel: 01-437 9155 Tel: 01-262 0387

All Mail Orders to 11-12, Paddington Gro London, W.2 Tel: 01-262 6562 (Trade supplied)

# AMERICAN TITLES FROM FOULSHAM-SAMS

## ARC's OF ANTENNAS

The introductory chapters cover the fundamentals of radio-wave propagation and basic antenna characteristics. The remainder of the book is then devoted to a discussion of the various types of of the book is then devoted to a discussion of the various types of antennas and their uses. Antennas for radio, television and two-way communications are included. Business radio, amateur, both mobile and fixed-station operation, are covered. The final chapter should be particularly appealing to those interested in microwave uses and radio-navigational systems. A perusal of this book will provide any student with an excellent foundation for more advanced study in antenna design.

# ABC's of SHORT-WAVE LISTENING

ABC's of SHORT-WAVE LISTENING Have you ever listened to a radio and thought how enjoyable it would be to hear broadcasts from faraway places, such as Toronto, Berlin, and Tokyo, as well as signals from ships at sea and satellites in space. All these broadcasts can be at your fingertips, offering a

in space. All these broadcasts can be at your tingertips, offering a fascinating hobby.

ABC's of Short-Wave Listening a non-technical guide, will help you get started, or give you added pointers if you are now engaged in this hobby. The mysteries of radio waves are revealed in a manner that anyone can understand, providing priceless knowledge about the ever-expanding world of short-wave radio.

ABC's of RADIO & TV BROADCASTING
This is a book for those who want to know what goes on at the transmitting end in radio and television broadcasting. It explains how the radio and television signals are formed, built up, and transmitted. In addition to the discussion of basic transmitter circuits, information is provided concerning metering and monitor-

ing circuits and procedures.

The author has avoided a detailed mathematical treatment. keeping the text basic and the essentials in view. Review questions are included at the end of each of the twelve chapters. The answers are given in the back of the book.

£1-13

# AMATEUR SSB RADIO GUIDE

AMATEUR SS RADIO GUIDE
Single-sideband receivers, transmitters, and transceivers are now available which have higher frequency stability and are much easier to tune than the early models. In this book, the author presents a guide to single-sideband and single-sideband equipment, which will be useful to any amateur considering or already operating SSB.

By WATYH

# AMATEUR RADIO CONSTRUCTION PROJECTS

Amateur radio is a rewarding and enjoyable hobby. For many hams the greatest thrill comes from constructing and operating their own "home-brew" rigs. There is something about being able to lean back and say, "I built it myself," that isn't engendered by owner-

rean pack and say, "Tourist myself, 'that isn't engendered by ownership of a commercial unit.

Amateur Radio Construction Projects is a book for every amateur, whether he wants to build all his equipment or just a unit or two to supplement what he already owns. Starting with many helpful construction hints (some of which will benefit the "old-timer"), the book progresses from simple projects to more complicated ones. Each chapter contains a complete circuit description, chassis layout tuning procedure and operating instructions quasile. layout, tuning procedure, and operating instructions, supplemented by schematic and pictorial diagrams and complete parts lists

By W6NJV

£1.10

# BUILDING YOUR AMATEUR RADIO NOVICE STATION This book is the first "completely detailed" construction manual for

building an amateur novice radio station. Nothing is overlooked in building the station from scratch to the actual on-the-air operation. The transmitter and receiver are distinctly professional in performance quality and appearance.

The book is primarily directed to the novice radio ham, it contains many novel and valuable construction hints and tips for amateurs in any licence class. As a finished touch to the projects a complete "rollaway ham shack for hams with limited space (apartment dwellers, etc.) is featured and fully described.

By W70E

HAM ANTENNA CONSTRUCTION PROJECTS

Besides full details on many useful and interesting types of aerials, Ham Antenna Construction Projects includes complete information on long-lasting construction methods, as well as how to position your antenna to achieve maximum distance with a given radiation pattern. In addition, much easy-to-understand technical information on tuning antennas and the use of test equipment is presented.

# PRACTICAL HAM RADIO PROJECTS

The projects described in this book include: all-band 500-watt linear amplifier. 2-metre SSB mixer and linear amplifier all-band 500-watt antenna tuner. electronic automatic keyer. deluxe 6-metre mobile transmitter. universal transistor mobile band 500-watt antenna tuner electronic automatic Keyer deluxe 6-metre mobile transmitter universal transistor mobile modulator and power supply universal transistor 2-metre superhet receiver VFO for 6, 2, and 1.25 metres universal transistor dip oscillator universal transistor of the station universal transistor 6-metre transceiver for mobile or fixed station universitor 6-metre handie-talkie monitor scope for SSB and AM. Just about all that is needed for a complete amateur station!

# SWL ANTENNA CONSTRUCTION PROJECTS

Two chapters cover the basic principles of antennae and the Two chapters cover the basic principles of antennae and the knowledge necessary for construction of the projects which are given in the following pages. The antenna projects themselves are divided into six classes. First are the dipole aerials such as segmented and inverted types. Following them are the vertical antennae, including array and beam types. Then horizontal beam systems (Yagis) are considered. Various low- and high-band and multiband triangle antennae are also discussed. The next section multipand triangle antennae are also discussed. The next section deals with long-wire antennae, such as vee beams and rhombics, for those SWL'ers with a sizeable plot of land available. For SWL'ers without land, indoor antennas, which are included in the final section, may be a solution. Three useful appendices are provided at the end of the book.

# TRANSISTOR FUNDAMENTALS Vol. I

This book is a carefully planned programmed introduction to semi-conductors and the basic electrical circuits. It begins with a brief description of transistors and later devotes an entire chapter to an explanation of transistor principles. Sandwiched between these chapters are explanations of voltage, current, and resistance; and the all-important Ohm's Law and Kirchhoff's laws. The book also looks at the more complicated nature of inductance, capacitance, and resistance in AC circuits.

TRANSISTOR FUNDAMENTALS Vol. 2
This volume describes transistors and how they are used in semiconductor circuits. Simple circuits illustrate the basic principles conductor circuits. Simple circuits illustrate the basic principles involved, and the more complicated circuits found in amplifiers and oscillators help to show how the basic operations are applied. Later, some recent semi-conductor developments are discussed. Details descriptions of four new transistor devices are given and how they are being used.

# TRANSISTOR FUNDAMENTALS Vol.

TRANSISTOR FUNDAMENTALS Vol. 3
This book covers circuits used in audio, radio, and television equipment. The reader is given a basic explanation of block and schematic diagrams, and operating principles of input and output devices, such as microphones and speakers. Numerous "X-ray" illustrations highlight the descriptions of these devices. Also discussed are the uses of the oscilloscope, radio-frequency and audio generators, and the vacuum-tube voltmeter. Throughout the book the reader will learn to recognise trouble symptoms and to use logical troubleshooting methods to narrow down troubles to specific circuits or stages in the unit under test.

The Books described here are American in origin.

The above prices include postage & packing.

Delivery is from stock.

# Available from

# SHORT WAVE MAGAZINE

Publications Dept., 55 Victoria St., London S.W.1

01-222 5341

(Counter Service, 9.30-5.15, Mon. to Fri.)

(GIRO A/C. No. 547 6151)

(Nearest Station: St. James's Park)

# ADVERTISERS INDEX

	PAGE
Aero and General Supplies	452
Amateur Electronics (G3FIK	) 454
Belding & Bennett (Morse)	512
J. Birkett	508
Burns Electronics	510
City of Birmingham Police	503
Derwent Radio	507
<b>Echelford Communications</b>	503
Eddystone Agents	456
Emsac	504
G D Grigg	506
G.W.M. Radio	511
Hamgear Electronics	508
Heath (Gloucester) Ltd	455
Imhofs	509
K.W. Electronics inside fro	nt cover
Lasky's Radio inside back co	
Lowe Electronics	457
LST Electronic Components	i
Ltd	503
Ltd May (Leicester) Ltd	503
Minitenna Communications	450
Ltd front co	over, 511
Mosley	464
B. H. Morris & Co. (Radio) Ltd front co. Mosley Newbery, Graham	510
NOTH West Electrics	453
New Forest Printing Co.,	
Ltd	506
Photo Electronic Services	506
Radio Shack, Ltd	454
R.T. & I. Electronics Ltd.	452
Senator Crystals	450
Small Advertisements	507-512
Smith, G. W. (Radio)	461
Solid State Modules inside be	
Spacemark, Ltd	
SSB Products Stephens-James, Ltd.	504
Stephens-James, Ltd. inside ba	
inside od	450 500
Strumech Engineering	439, 309
Strumech Engineering S.W.M. Publications bace 456, 460, 462, 503, 5	<i>ck cover</i> ,
430, 400, 402, 303, 3	506, 507
Taurus Electrical Services	505
Telecomms (G3SED)	505
Telecomms (G3SED) The Amateur Radio Shop	450
Trio Electronics	458
Weller Electric Co. Ltd	
Western Electronics	
Chas. H. Young	506

# SHORT WAVE MAGAZINE

(GB3SWM)

<del>_</del>	CONTENT	C				
	CONTENT					Page
Editorial— <i>Market</i>			•••	•••	•••	46:
Communication and D	X News, by A. J. L	Devon		•••		46
"Sun, Earth and Rad	io"—Book Review	•••	•••	•••		472
813's in Linear.						
by D. P. Nicholls,	G3ZVZ, and M. W.	Smith,	<i>G3UAF</i>	•••	• • •	47.
R.A.E. Courses-Fina	l List	•••		•••	• • •	47
Transmitting Antennae	for Small Gardens, by	y <b>J</b> . S. C	ushing,	G3KH	<i>[C</i>	47:
Adjustable HT Supply	, by F. G. Rayer, A.I.	E.R.E.	G30GF	₹	•••	47
Vehicle Noise Suppres by D. C. Arigho,	ssion for Mobile Ope	ration,				47
Beam Direction Indica	ator by I M Orton					48
Personal Portable for	Two Metres, by J. R.	Hev. M	f.S.E.R.	T., G3	TDZ	48
Pictures from the Mo	hile Rallies	,	•••	·		48
VHF Bands, by A. H	L. Dormer, G3DAH	•••				48
The Other Man's Sta	tion—G3YWS					49
The Month with The	Clubs—From Report	·s	•••			49
Rules Magazit	ie Top Band Club	Conte	st, MC	'C		49
Chib Identifica	tion Codes, MCC		•••			50
Zones and Sco	ring, MCC					50
New OTH's				•••		50

Published at 55 Victoria Street, London, S.W.I, on the last Friday of the month, dated the month following.

Telephone: 01-222 5341 & 5342

Annual Subscription:

Home: £2.50 (£2.75 first class) post paid Overseas: £2.50 (\$7.00 U.S.), post free surface mail

Editorial Address:

Short Wave Magazine, BUCKINGHAM, England

# **AUTHORS' MSS**

Articles submitted for Editorial consideration must be typed double-spaced with wide margins on one side only of quarto or foolscap sheets. Photographs should be lightly identified in pencil on the back with details on a separate sheet. All drawings and diagrams should also be shown separately, and tables of values prepared in accordance with our normal setting convention—see any issue. Payment is made for all material used, and it is a condition of acceptance that full copyright passes to the Short Wave Magazine, Ltd., on publication.

(C) Short Wave Magazine Ltd.

# ARE YOU READY?— WE ARE—FOR THE DX SEASON. Buy Now Before The Rush

TRAP MASTER

BACK BRITAIN
Manufactured 100% in England

MUSTANG	D1-2
ATLAS	SWL-7
ELAN	RD-5
TA-33 Jr.	A-315
TA-32 Jr.	A-215
TA-3i Jr.	A-310
VTD-3 Jr.	A-210
TD-3 Jr.	

MUSTANG

Mosley U.S.A. types are of course also available

Rotators, Towers, Polythene cord and rope, Coax cable, Control cable, Twin feeder.

Send for HANDBOOK/CATALOGUE containing full details and prices of Antennae and technical information, 25 pages, 15p refundable on purchase of an Antenna.

Vasley Electronics. Ltd. 40, Valley Road, New. Costessey, Norwich, Norfolk Nor. 26K

# **Special Offer—Weller**

Every year at the RSGB Show Weller have made new friends and welcomed old friends. Because there is no Show this year we are making our usual offer to our friends—by post—to buy one of our renowned temperature controlled tools at very keen prices. These tools have been out on demonstrations, in displays and on exhibition stands and so they don't look their best. However, THE FULL SIX MONTH GUARANTEE STILL APPLIES, so these are still first-class buys.

There is not an unlimited stock so send your order in right away to avoid disappointment. Please send your remittance with your order to avoid delay, with postage and packing.

TCP-1, 24v., fitted with PTCC7 and PU-1D (Power Unit 220/240v.) Postage and packing (UK only) Overseas: allow for 2 kilo parcel post from UK to your address	UK Industrial List Price £10·10	<b>Offered at £6.00</b> 50p	Weller Electric
Tips: PTCC7, PTAA6, PTDD8 Set of three (one of each) Postage and packing	£1·50	<b>£1⋅00</b> 25p	<b>Limited</b> Redkiln Way
W60D Mains voltage iron (220/240) with Bench Holder BH4LL Postage and packing	£7·60	<b>£4⋅75</b> 50p	Horsham, RH13 5QL Sussex, England

# The SHORT-WAVE Magazine

# FDITORIAL

Whether one is or is not in favour of the U.K. joining the European Economic Community ("Common Market") it is interesting to consider the implications for us in the Amateur Radio context. The first fact to emerge is that the Six are relatively under-populated in the radio amateur sense—a check from the latest available IARU figures (end 1970) with an adjustment to allow for the probable growth of licensing since, shows that France, Germany, Italy, Belgium, Holland and Luxembourg have together only 29,700 licensed AT-stations.

The U.K. total is 16,500. Our entry would make it 46,200 for the Seven and the U.K. proportion of the whole 28%. As the U.K. rate of amateur-station licensing appears to be rather higher than in the six countries, this proportion would likely increase as time went on. Not only would the U.K. be the dominant partner in terms of AT-stations licensed (no one country has more than we have, though Germany has approximately equal numbers) but Britain would also be the only member with an indigenous industry manufacturing for the Amateur Radio market—of course, relatively a very small part of the electronics complex as a whole, but nevertheless efficient, well-established and already doing world-wide business.

In the strictly Amateur Radio context, there would not appear to be any advantage, one way or the other, by the U.K. either joining the Market or staying out of it. The possible exception to this is in the long term, when an Amateur Radio Federation of the Seven (as it would then be if we went in) might be formed as a strong organisation within the Community. This would really be essential for the proper conduct of affairs because the existing IARU Region I set-up—being composed of 36 countries, many of which are politically opposed to the Common Market and its aspirations—could not be an entirely satisfactory organisation through which to handle Amateur Radio affairs within the Seven. And, of course, by the time such an "A.R.F. of the Seven" has been formed, the Community itself would probably have been enlarged by the joining of the fringe-countries of Northern Europe, from the EFTA group.

Quite apart from any Amateur Radio consideration and the possibilities outlined in the foregoing, it would seem that the U.K. would in the end do better by remaining outside the Common Market altogether—but that will be for Parliament to decide, in due course.

Aus hin bodyh.

# **COMMUNICATION and DX NEWS**

A. J. Devon

JUST as this issue was due for press, most unhappily Paul Essery, became too ill for any work. So the contribution this time has been compiled by another hand—that, in fact, of none other than A. J. Devon who, roused from his slumbers, was handed a peremptory brief by the Editor saying, in effect, "Get on with it, let's have it on time and try to make it good". So herewith A.J.D. does his best to keep the fire in for G3KFE...

\* \*

General opinion is that the seasonal improvement in HF-band conditions is undoubtedly beginning to show-the evidence for this is in the 21 MHz band, which is getting much livelier. With a truly-resonant dipole showing an SWR of 1:1.1 (better than which you could not expect to see) and 150 watts it is possible to find something interesting to work any day. As the season goes on, this will relieve the heavy pressure on Twenty and may permit a little more real DX to be worked more easily on that band-for it is our 14 MHz frequency area that is the best, in terms of propagation potential, for any part of the world. The only trouble is the QRM!

Forty, for DX, is used mainly by the specialists, who have attenuators in their Rx inputs and can be on towards midnight or very early in the morning, when the QRM reduces to fairly tolerable proportions.

The 80m situation is that while conditions are improving for DX (which is there and is workable by the dab-hands) the congestion and the general slap-happy operating does make things very difficult. Eighty is probably at its quietest and most urbane on weekday mornings, when the regular "retired gentlemen's nets" can be heard gently discussing affairs of absolutely no importance.

Top Band is, as always, in a category of its own. With conditions improving steadily some extraordinary DX is being worked, having

regard to the frequency. We have reports of W1BB, MP4BJI and KV4FZ being heard regularly in the U.K. and, on the American side, the said KV4FZ made a 160m. WAC in 24 hours during August, the U.K. station involved being GW3AEC. (Astounding, says Stew Perry, W1BB, and we can only concur.)

# Contest Programme

There are several important events coming off during the next few months, of which we should apprise you. Unfortunately, there are so many that we cannot possibly print the rules for each, even in an attenuated form-but full details can be obtained from the addresses given (except that the VK/ZL affair is right on us). In general, the exchanges are on the usual signal report + serial number basis. The point is that high activity can be expected during the periods shown; it is possible to join in (even if not intending to send in an entry) by first listening round for a few minutes to see what the form is, and making QSO's accordingly; then sorting out the paper-work

afterwards, when there has been time to get the detailed rules.

VK/ZL—Oceania: Phone section, 1000z Oct. 2 to 1000z Oct. 3. CW session, 1000z Oct. 9 to 1000z Oct. 10. Paper-work from, and logs to (by Jan. 30, '72): W.I.A., Federal Contest Committee, Box N1002, G.P.O. Perth, 6001, Western Australia.

"CQ" World-Wide DX: Phone section, Oct. 30-31. CW section, November 27-28. Rules and log forms from: Contest Dept., CQ Magazine, 14 Vanderventer Avenue, Port Washington, Long Island, N.Y., 11050, U.S.A.

ARRL Sweepstakes: *Phone* session, Nov. 13-14. *CW* leg, Nov. 20-21. Paper-work from: ARRL, 228 Main Street, Newington, Conn., 06111, U.S.A.

ARRL 160-Metre Contest: December 11-12. Logs, etc., as above.

"CQ" World-Wide Top Band CW: January 29-30. Contest entry address as given.

Foregoing are the big events, open to all on a world-wide basis. When



Showing the Hungarian callsign allocation, by districts indicated by the first letter after the prefix, e.g. HA2G - - Kaposvar and HAØD - - Debrecen. All stations in the district of the capital, Budapest, are prefixed HA5. The total of licensed HA's is about 700.

Map acknowledgement "DL-OTC", August,

sending for the rules, log forms, etc., use airmail and enclose at least two IRC's for return postage.

There are, between times, many other contests of local or lesser import, which it is not possible to list here. You find them going on as you tour the bands and your QSO will always be welcomed by the participants.

# Top Band Test Series


These are always of great interest to U.K. stations, with a high level of participation. The Trans-Atlantic Tests are on (GMT dates) Nov. 28. Dec. 26, Jan. 9 and 23, and Feb. 13, 0500-0730z each day, with the W/VE stations on 1800-1810 kHz and Europeans (which means us) using 1823-1830 kHz. Call "CO DX Test" at 5-min, intervals, our times being 0505, 0515 et sea, the W/VE's calling at 0500, 0510 and so on. Note that this implies not only accurate timekeeping, but cross-frequency working -vou will be more than somewhat unpopular if you are heard calling a W station on his frequency; anyway, he propably won't hear you because he will be searching for Europe over 1823-1830 kHz. The calling-listening periods can, of course, be broken if a OSO is started—which remember. should be kept strictly cross-frequency. (The idea of this is, of course, to minimise mutual QRM locally.)

There is another—but for us a good deal more difficult—160-metre test event on Nov. 6 and 20, Dec. 4 and 18, Jan. 1 and 15, and Feb. 13, when the W/VE's try to work across the Pacific, in particular to JA, ZL and VK. There is one period when it could be worth trying from where we are—0730-1000z on those dates, when the JA's will be on 1907.5-1912-5 kHz, the VK's on 1802-1805 kHz and the ZL's on 1876 kHz. We should keep to 1823-1830 kHz.

Reports from U.K. stations taking part, for coverage in this feature, would be greatly appreciated.
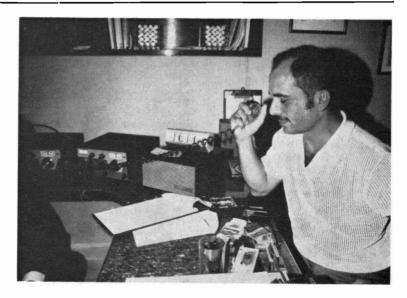
# Items of News

ZL4JF/A, Campbell Is., has been heard working EU's on 3798 kHz..... W6AM now has a kilowatt mobile rig in his Cadillac, for which the battery leads are of No. 2g. copper, more than a \(\frac{1}{2}\)in. in diameter; he will be signing W6AM/M on 14025 kHz CW (phew!).....



JY1, Amman, H.M. King Hussein of Jordan, at the operating position in his study at the Palace—well known on the HF bands as a courteous and efficient operator and very conscientious about his QSL'ing. He has worked many U.K. stations (nobody need write in to us any more about this!) and spends a little time on the air almost every day.

KF4SJ is a genuine call, to do with the founding anniversary of San Juan, Puerto Rico . . . . Same goes for VA2UN, which is a special c/s issued to McGill University. Montreal, for operation on all bands till the end of the year . . . . . G5ZT, of SS/TV fame (see p.405, Sept.) has now had slow-scan television contacts with 15 countries. all two-way on 20 metres, some of the more interesting being KL7DRZ. VK6ES, ZL1DW and 4X4VB, with more than 50 U.S. stations pictured ..... 4X4NJ has obtained special permission to operate over 1800-1830 and 1870-1900 kHz "during contests only"; his present xtal frequency is 1827.5 kHz . . . . . G3ZNZ worked JY1 recently and when he asked if he could speak to Princess Muna, H.M. put her on; the gear used at both ends is British K.W. equipment . . . . . G2NJ has again found YO4ASG/MM, on 7 MHz, whom he has worked before on s.s. Moldova; and by about now G5NX/LA/MM aboard m.v. Torrens should be home again . . . . . . G3ZYY, H.M.S. Cleopatra, is off on tour to the Far East and will be looking up VS6DO to find out who-and-what he really has worked on 160m.; the ship will be visiting a number of DX localities

and G3ZYY hopes to go reciprocal at least in 9V1 and VS6 . . . . . G3ZOJ, our "Other Man's Station" subject in the August issue, would like to report, and us to record, an instance of considerate and gentlemanly behaviour on 20m.: He called "CQ VK" at 1545 clock on Sept. 1 (when of course the band was full of first-skip Europeans) and back came VK6OV—a nice response if ever there was one; every one of the EU's on the channel held off and gave G3ZOJ/VK6OV a clear frequency for a good 579 CW contact . . . . . You would probably never have known it but between Norway and Sweden there is a small, independent territory called Morokulien, which is an international refugee area; for it, the prefixes LG and SK9 have been specially issued, with LG5GL and SK9WL regularly active; the QSL address is P.O. Box 1, N.2242/S 67 044, Morokulien. Scandinavia . . . . . Our inside information is that stations using the BY prefix and giving Chinese locations are likely to be genuine; they will QSL through Hong Kong .... Other interesting, and genuine, calls heard recently or about to appear are: AC3PT, ET3ZU/A, HKØAA, KC6RS,

SVØWXX (Crete), VK3UV/9 (Solomon Is.) and ZL3PO/C (Chatham Is.)..... The ET3's (and there are now several of them) can be QSL'd via P.O. 379, Asmara, Ethiopia.

# Individual Reports

As always, there has been a good intake of mail from the correspondents who provide the hard-core background for this feature. Though it is possible to some limited extent to make bricks without straw when reporting activity on the amateur bands, one does need to know what the real practitioners of the art are doing.

One of these is Jack Drudge-Coates, G2DC (Ringwood, Hants.) who has not only been touring the DX bands for the best part of 40 years but also, nowadays retired, is able to keep almost a daily check on what is happening on 10-15-20-40-80m., and occasionally he looks at Top Band, too. G2DC (whose ground-wave on the HF bands is within range of where A.J.D. listens) is not only a very competent and experienced CW operator but also expert at winkling out the difficult stuff. His report for this month covers a wide range of CW/ SSB DX on all the HF bands. among the most interesting being ZD6CW, worked out of the blue at 599 both ways on an otherwisedead 10m, band, and a flock of PY's on 80m.

G3ZXZ (Wakefield, Yorks.) says he "neglects all bands except 15 and 80m."—he is now working SSB with a Heath HW-100, and got ZL2LE on Eighty; he has a two-element Quad for 15m., and has been quite successful with CW/SSB DX on that band.

G3NOF (Yeovil, Som.) is another of our regulars who searches all bands and always comes in with factual information. With him. Ten has been the poorest in terms of workable DX since he started in 1959. Fifteen is much more forthcoming, with the Far East there in the mornings and Asia in the afternoons, though the band has been closing early. As regards Twenty, G3NOF agrees that mornings after about 0730 clock is the best time for working the DX-why, you may ask? Answer is that around 0730 our time is when the EU's start going to work and the QRM A.J.D. has noticeably lessens!


found this, too, as he searches for the rarer stuff in the UA9, UA $\emptyset$  areas; as a matter of fact, much interesting Far East DX can be worked on 20m. by picking out the right stations, always glad to be called by somebody different from the usual run of Mittel-Europa countries—and you can be sure that, in due time, you will get a QSL.

G3DNF (Leeds) writes to say he has come to life again, with an interesting record of stations worked on the 7-14-21 MHz bands. We pick out UA9CAO on Forty, H18MMA on Twenty and G3TZL/MM on Fifteen. G3DNF is working his antenna to get low-angle radiation on 7 MHz, trying a sloping

wire, feeling like \(\frac{3}{3}\)-wave against a good earth connection. He says "at last I can hear the DX, and seem to be able to work it". Well, there you are—there's an idea for a simple aerial

For years, A.J.D. has been using closely-resonant dipoles for all bands 10 to 80m. and, within the usual limitations of band conditions and QRM, can be reasonably sure of working anything that the Rx can hear. GW3AHN (Cardiff), one of our king-pin DX operators, has worked 328 countries on 15 metres alone, using no more than a rotary dipole.

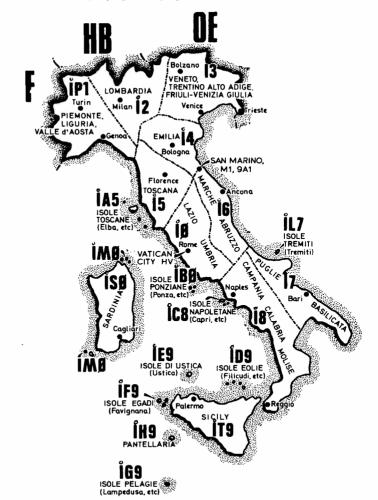G3VLX, now of Chislehurst, Kent, started on the air five years ago when, as he says, he was "very green".



Sorting out the Italian prefix system. Not all I's are obliged to use this and some keep to their original callsigns—which only adds to the confusion.

Map acknowledgement August "Region I News", G2BVN.

and described how he had buried a 60-gal. water tank for an earth. He feels that this is almost where he came in—because at the new QTH he has just buried another 60-gal. water-tank for an earth! (And he can't go wrong!—Editor).

For G8HX (Mansfield), the R. & D. department of Rediffusion. Ltd. have made a considerable effort and have at last rid him of the TVI he was causing—by reason of the 7 MHz pass-band in their system, for which he was held not to blame by the Post Office. It has taken about a year and many hours of testing, but always on a completely amicable basis; success was celebrated by a session at the local, for which the firm paid! G8HX runs a DX-100U, CW only, and a dipole (balanced feeder through a balun) on 40m, and has worked some nice run-of-the-mill DX. Particularly interested in one of the German awards, he has worked more than 330 W. German stations, with a QSL return of no less than 62%. He notices a lot of difference in the quality of signal as between West and East German stations, the latter being markedly inferior.

GM3JDR (Wick), another of the stalwarts behind this feature, also



G3ZBA is Dr. Sidney Sefton, 8 Sandmoor Avenue, Leeds, LS17-7DW, who runs K.W. gear on the Tx side and an Eddystone 830/7 receiver—a nice range of modern British equipment, with which he has got more than 150 countries confirmed. Being a doctor of medicine he is strictly a "non-professional radio amateur".

keeps to 7 MHz and has an impressive worked-list; he has three antennae cut for that band—a dipole, a delta loop and a bobtail curtain and finds that by switching them he can not only pick his direction but also cut back a lot of the EU QRM.

W4WFL/1 (Hartford, Conn.) who is a member of the ARRL Hq. staff and likewise a regular correspondent, mentions that he is modifying his Drake 2-B for 160m., à la G6LX's article in the March issue of SHORT WAVE MAGAZINE. He gives us another ET QSL address-Telecoms. A.R.C., P.O. Box 1047, Addis Ababa, Ethiopia, though this does not apply to all ET3's or 9E3's: best thing is to ask where the card is to be sent when in QSO. For C31EF, cards go to W4WFL himself, at BM/W4WFL, London, W.C.1. (which is a Monomark address, and quite sufficient). Over in Ipswich, G3DCS is still working away with antennae and

Over in Ipswich, G3DCS is still working away with antennae and has a balun-connected rectangle (somewhat as G6LX suggested in the June issue, one presumes) and shows a good CW/DX list using it on 15-20m. with a KW-2000.

G3YRR (Grimsby) had some rewarding sessions on 15m., though he remarks that "one terrible evening on 15 I heard ZP, CE, PZ and just about the whole S. American firmament without getting a bite". That's how it goes!

# Ten Metres

Though we have heard little anough of anything in the way of DX happenings on Ten, this band should not be neglected—hence the heading to itself. For one thing, it is ideal for local net working and



John Sainsbury, 9J2HE (Box 696, Kitwe) was first licensed in 1937 as G8HV. He has been in Zambia for the last seven years and the shack is actually a 4-wheel caravan trailer. John has also operated from ZE6, VQ1, VQ3, VQ4, SX5 and VS9. His pre-War U.K. recollections go back to the time when G3CY first started listening to those mysterious noises from outer space on a home built Rx in his father's garage—G3CY is now Sir Martin Ryle, the eminent scientist and radio astronomer at Cambridge University.

should be used much more for that purpose when it is in the doldrums in the DX context, and for another it can spring the odd surprise.

Some years ago, we used to run Activity Periods on 10 metres, just to stir things up and see what could happen. The results were always extremely interesting and proved two things: One that activity generated more occupancy, and the other that G's on ground-wave could be heard up to 100 miles or \$0.

# The Tabular Matter

There is none again this month because of course G3KFE holds all the details and it was not possible in the time available for A.J.D. to get the Tables together.

# Apologia

It is only too well appreciated that this offering of CDXN is scant compared with what we usually get from G3KFE—but not only did A.J.D. come to the job stone-cold, as the saying is, but he had less than two days in which to do it.

Anyway, it is much to be hoped that Paul Essery will be back on his beat by next time.

# Deadline

And for next time, the closing date for this feature will be Monday, October 11, addressed CDXN, SHORT WAVE MAGAZINE, BUCKINGHAM. Keep the bands busy, es 73 de A.J.D.

Station set-up, G4ACF, of the Worcs. Army Cadet Force, Rubery Troop, Callowbridge, Rubery, Birmingham. Main operating interest is 80m. SSB working on Monday and Thursday evenings. They would particularly like to contact, or to hear from, any other amateur station directly connected with the Army Cadet Force.



The Yugoslavs have about 2,000 licensed AT-stations, distributed as shown here.

Map acknowledgement August "Region I News," G2BVN.



# "THE HAM'S INTERPRETER"

This is a radio amateur phrase book in ten languages (including English and Esperanto) which translates the usual phraseology—for instance, Thank you very much for this QSO or I hope to meet you again in the near future under better conditions—into any one of the nine other languages, from French or Spanish to Yugo-Slav or Russian. The book also contains sections on correct pronunciation, in phonetic spelling, e.g., the letter Z is tse in Russian or tset in German, also a translation of numbers from 0 (zero) to 1000, which is hiljada in Yugo-Slav (you say it just like that). There is an extensive glossary of terms usual in radio parlance, like kantoaalto, which is "carrier-wave" in Finnish, or "effective height", which sounds like evektivnaja visota when you (try to) say it in Russian.

The cost of this very useful and practical little book—which, apart from its applications to the every-day European contact, makes instructive reading for anyone interested in what radio amateurs talk about over the air—is but 55p, post free ex-stock, from the Publications Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1. Over the years, we have sold 1000's of copies of the *Ham's Interpreter*, from the time it only covered five languages to the ten interpreted in the current issue.

# **OUR BOOK DEPARTMENT**

Regular readers will not have failed to notice that each month we offer an extensive range of book titles covering (as far as we know) every aspect of the art and practice of Amateur Radio. We are constantly looking for new books of Amateur Radio interest—like Ratcliffe's Sun, Earth and Radio, now available. We do a considerable business through our Book and Publications Dept.—probably in our field the largest in the U.K.

What matters for our customers is that every title we advertise—and there are nearly 150 of them!—is in stock for immediate delivery. All prices shown are post free and orders are usually despatched on the day of receipt—slight blurb in support of the devoted staff who look after the Publications Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.I. (If you buy at the counter, we knock off the postage charge.)

# FOR ANYTHING FOR SALE OR WANTED

In the radio amateur field, always use the Small Adv. pages of Short Wave Magazine. For nearly 25 years, our Small Adv. columns have been establishing, by the law of supply and demand, the re-sale value of a very wide range of branded equipment, of whatever origin. (There are today some "surplus" items commanding a higher price than they did many years ago—we would not mention them, for fear of forcing the price even higher!)

Through our Readers' Small Advertising columns, many £1,000's-worth of equipment change hands every month—in the September issue alone, nearly £3,000-worth of gear was being offered For Sale, this taking no account of the "Wanted" or "Exchange Offer" Advs.

While we do not suggest that you can sell any old junk by advertising it in Short Wave Magazine, what

we do say is that if you have an interesting piece of gear at a reasonable price, you are pretty certain of being able to get immediate cash for it.

We can check this quite easily for ourselves: In each issue there is a certain proportion of Box No. advertisements. The replies to all these must come through us to be sent on to the addressees. It is therefore easy to evaluate Advs. having the greatest appeal—it is always those items offered at a realistic second-hand price. (Of course, we do not open the envelopes, which are sent on immediately as received.) But if we get 37 for Box No. XYZ and only five for Box No. ABC, it is easy to see what are the attractive items from the point of view of the reader willing to lay out his cash.

We have been in this business of Amateur Radio for more than 25 years and the cost of our Small Advertising is cheap enough—2½p per word, minimum charge to readers 50p, payable with order. Copy to: Advertising Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

# GOING BACK A BIT

Anent the picture on p.275 of the July issue of Short Wave Magazine, one of our well-known SWL correspondents, E. J. Boyle (London, S.E.19), writes that during the Kaiser's War he was in the old R.F.C. as a W/T opr. and himself operated a Tx of that type in a BE-8 artillery spotter aircraft over the Ypres area. The receiver which went with it was a two-crystal job (you had a switch to select the one with the most sensitive spot) followed by a valve amplifier using the famous R-type bright-emitter valves. Hallowed days—hallowed memories.

# CITIZENS' BAND-U.S.A.

The American FCC (Federal Communications Commission) has recently published the results of a two-year survey on what is happening over there on what is known as the "Citizens' Band", categorised as Class-D Licensing for personal transceiver operation around 27 MHz. The most interesting fact emerging from this survey (according to Auto-Call, July) is that 74% of the 900,000 individuals licensed are actually making full use of the facility (talking to one another) though it does mean some over-crowding of the 23 available channels, allocated on a regional basis. Apparently, there is a large body of what are called "hard-core violators"-people who pay no licence fee and buy equipment running far over the CB licensed power of 5 watts. There is also an interesting problem due to skip under anomalous propagation conditionslike when we can hear the 27 MHz CB stations over here.

In the U.S., amateurs have a band, apparently little used (and unknown over here) at 220-225 MHz. The proposal is that 2 MHz of this band be given over to the CB service, making some 80 CC/FM channels available, to be allocated on a regional basis.

The underlying difficulty about the whole situation is the fact that the FCC has totally insufficient funds to enforce the CB rules as they stand—not much could be done anyway about anonymous "hard-core violators"—while against them they have a powerful segment of the electronics industry eager to sell more transceivers to more people.

# SCOUT INTERNATIONAL EVENT

Once again, there will be a large number of U.K. stations on for J-O-T-A, the Scout Radio Jamboree over the weekend October 16-17, 0001-2359, effectively midnight Friday to midnight on Sunday, a 48-hour period. Of course, few stations will be able to keep going for such a long stretch but a little calculation with the 24-hour clock will show how the time can be used under the band conditions that normally can be expected to catch DX from anywhere in the world, e.g., 40 metres early Sat./Sun. morning; 20m. during the late evening and early morning; 80m. mid-morning and early afternoon Sat./Sun. for contacts with other U.K. Scout groups; and Sunday morning for the same on Top Band and the working of locals. The other two bands, 10-15m. may not be of much use at any time, though it is always worth checking 15 metres for DX, especially from the Near East and North Africa.

We shall be glad to have, for a write-up in the December issue, J-O-T-A reports from any stations participating. Details required are: Callsign and location; Scout group entertained or involved; bands worked; total of actual J-O-T-A contacts made; best Scout DX and/or most interesting J-O-T-A station worked; a general comment on conditions and experiences—also, where possible, a good picture of the station and visitors—all to be addressed to: JOTA, SHORT WAVE MAGAZINE, BUCKINGHAM, to arrive on or before October 30. All photographs we can use will be paid for on appearance, in the usual way.

# KEEP TO THE UNOFFICIAL RULES

Though any U.K. amateur station is entitled to use any mode he wishes on any frequency within the bands for which he is licensed, there are certain unofficial rules which have been drawn up for the comfort and convenience of all concerned and they are meant to apply throughout the Region I area—in the common interest, they should be observed. Transgressors do not lay themselves open to any official penalty, because there is none—but they will certainly attract the obloquy of other users of a band, an attitude that can show itself in a number of ways, mainly unpleasant.

The Region I IARU Band Plan—with which we are in full agreement and which we entirely support as being in the general interest—can be summarised as follows:

For CW-only Operation: 3500-3600 kHz; 7000-7040 kHz; 14000-14100 kHz; 21-0-21-15 MHz; and 28-00 to 28-20 MHz. What all this comes to is that CW working should be confined to the LF areas of the DX bands.

For Phone-only Working, the limits are: 3600-3800 kHz; 7040-7100 kHz; 14100-14350 kHz; 21·15-21·45 MHz; and 28·20-29·70 MHz.

International RTTY (radio teleprinter operation) should be kept around 14090 kHz. Two other narrow frequency bands agreed for inter-Continental DX are 3500-3510 kHz for CW and 3790-3800 kHz for Phone.

There is no difficulty about any of the foregoing. The great majority of amateur stations conform. If you are one of those who do not, you cannot complain if you are trodden on. You will not be breaking any official rules but you will certainly be behaving in an anti-social fashion.

# "SUN. EARTH and RADIO"

It is an odd thought that though the ionosphere and its changes are the key to all radio communication, it is the phenomena least understood by amateurs, and also the most simplified part of the R.A.E., to be covered in the course of a couple of hours of lecture.

This book of Ratcliffe's is a demonstration of just now much over-simplified the ionosphere can be and gives a good idea of the speed at which science is learning, modifying and discarding theories in the light of experimental evidence. It is also very much a proof of the practical value of scientific space satellites.

What are you going to get for your money? Not a book to read in bed, certainly. Sun, Earth and Radio is aimed at students seeking the facts on the subject and intelligent general readers who just want to know. Thus, there is an introductory historical discussion, further material covering the area out to about 1000 kilometres, and then some chapters dealing with later advances and consolidation of existing theories which the space era brought into the field.

All this is linked up to a discussion of the practical implications in terms of radio communications. In this final part there are some surprises in store for the average reader who is a practising HF-band radio amateur. Finally there are a couple of appendices, the first one of which gives a brief but adequate coverage of basic physical matters which are relevant, e.g., frequency, phase, magnetic fields, photons, Doppler-effect, temperature-measurement and so on, making it possible for an intelligent reader to come to the book "cold." The second appendix gives the last-minute developments between completion of the main work and publication, emphasising once more the speed with which the experts are moving ahead. To round-off, there is a very useful bibliography, with a heading to the effect that in all additional reading the date of publication is of the utmost importance—and, of course, an adequate index. There are fifteen photographic plates and 83 two-colour diagrams, all drawn originally by the author.

One is not involved in mathematics beyond the ability to read a graph. The style of writing is very direct and the numerous two-colour graphs and diagrams help in bringing home the various points. The caption-writing associated with the diagrams is particularly good and clear.

Summing-up, one cannot imagine a better treatment on the ionosphere and magnetosphere than this, to be read and referred to again. One feels that it will become the standard text against which all other works on the subject will be compared—and it is certainly a valuable addition to your reviewer's shelves.

Of the author, Dr. J. A. Ratcliffe, FRS, it is enough to say that he was for six years the director of the Govt. Radio & Space Research Station and is recognised as a world authority on radio propagation and the problems of the ionosphere.

His book, of more than 250 pages, copiously illutrated and called *Sum*, *Earth and Radio* costs 89p post free and is obtainable, from stock, of our Publications Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.I.

E.P.E.

# 813's IN LINEAR

# DESIGN FOR ALL HF BANDS

D. P. NICHOLLS, M.B., Ch.B. (G3ZVZ) M. W. SMITH, M.B., Ch.B. (G3UAF)

MANY amateurs now own transceivers giving 90-200w. p.e.p. output, but would like to run 400w. output for greater advantage in DX working. However, commercial linear RF amplifiers are still quite expensive. This article describes a cheap and reliable linear, capable of delivering the legal power limit with ease. Full constructional details are not given, as it is assumed that many constructors will keep the price down by using available parts, i.e., their junk-boxes. In this way, it should be possible to build the amplifier for under £20.

The linear uses two 813 valves in parallel grounded-grid mode. This has the advantages of good linearity without neutralisation (except perhaps on 10 metres). No complex test procedures are required, and no bias supplies are used. The output from most modern transceivers is more than ample to drive it to full output. (As used to be said of the 813 "you have only to breathe on its grid to get 400 watts RF output"—a pair of them can be pushed to a kilowatt with about 10 mA of drive—Editor.)

# Power Supply Unit-Fig. 1

For maximum efficiency, a plate voltage of 2-2.5 kV is used. This is supplied from a 1000-0-1000v, transformer, rated at 250 mA. A lower current rating may result in core saturation on peaks and diminished output. This is, of course, a lethal voltage, and appropriate safety precautions must be taken, including a good earth. The "third pin" of the mains should not be relied upon. Something like 20 to 40  $\mu$ F of smoothing is recommended, with bleeder resistors across each capacitor. The large value of resistor used results in long discharge time; thus, high voltage can remain in the linear for several minutes after switching off. Therefore, always ground the HT line with a large, well insulated screwdriver before touching anything inside! The HT and heater transformers should have separate switches; switching the HT off first will decrease the discharge time.

In this context, we should mention the medical treatment of anyone who has received a severe electric shock. Although the victim may appear to be dead, it is well worth while continuing artificial respiration and heart massage for over an hour in such cases, as they could well come round again.

To those more concerned with the longevity of the valves than of the operator, this may be considerably increased by testing and tuning on reduced plate voltage. A Variac or large choke in the mains primary will reduce the voltage, but grounding the centre-tap of the transformer secondary winding does not work. Blower cooling of the valves is a luxury but not a necessity.

The rectifier is a full-wave bridge arrangement, using four or five silicons per limb, mounted on tagboard.

Types such as RAS-310AF are superior to the BY-100 in current rating, but note that in this case the connections are *opposite* to the BY-100. All the capacitors should be isolated in plastic tubing, and the smoothing choke should be of large dimensions. The power pack is screened, but the anode choke L3 and its decoupler C7 (Fig. 2) are contained in the PA compartment. Anode chokes are notoriously difficult to make, and often burn out due to parasitics. It is best to buy a commercial type intended for high-power operation.

# RF Amplifier—Fig. 2 (p.474)

Although the design of the power-pack is not critical (if may even be built as a separate unit), much more care should be taken with the layout of the amplifier. Leads should be only of the minimum length necessary, and the unit built strong and rigid. The input and output circuits must be screened. It may be convenient to incorporate a heavy-duty aerial change-over relay on the output side of the linear.

The exciter input is fed through a capacitor, C1 which works well in many cases, but better matching is obtained with a pi-network. The bifilar heater choke is made from about twelve double turns of 16g. insulated copper wire close wound on  $\frac{3}{8}$  in. ferrite rod, and bound. The anode parasitic chokes L1, L2 are about three or four turns of 16g. copper,  $\frac{1}{2}$  in. i.d., over a 47-ohm carbon resistor (not wire-wound). This may have to be altered if the standing current is excessive, indicating parasitics; normal standing current is about 80 mA.

The *pi*-tank design will vary considerably according to the components available. The tune capacitor C8, C9 must be wide-spaced and heavy-duty, but the load condenser need not be so bulky. For the tune condenser, try 50 pF, with 100-150 pF to switch in parallel for 80m. and 40m. A large split-stator condenser, such as Eddystone used to make, is ideal. Plates may be removed from both sections and the larger portion switched in

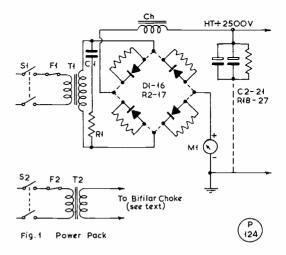


Fig. 1. Suitable PSU for the 813 Linear discussed in the text. C1, 500  $\,\mu\mu\mathrm{F}$ , 3 kV.; C2-C21, 60 + 250  $\,\mu\mathrm{F}$ , electrolytic, 350v. working, ten in series-parallel; R1, 1.5K, 5w.; R2-R17, 470K, ½w., 4 in series across each diode; R18-R27, 470K, ten in series; Ch., 5-25 Hy, rated 250 mA+; D1-D16, see text; T1, 1000-0-1000v. at 250 mA; T2, 10v. at 10 amps for 813 heaters.

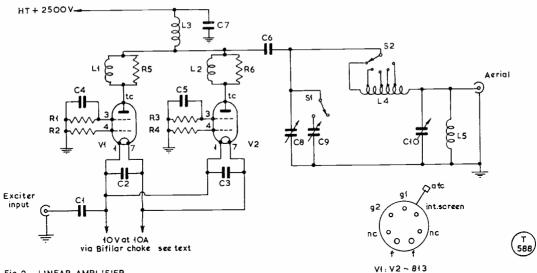


Fig. 2 LINEAR AMPLIFIER

Fig. 2. The parallel-813 Linear Amplifier. Values should be C1, .02  $\mu$ F; C2, C3, .005  $\mu$ F; C4, C5, .001  $\mu$ F; C6, .001-002  $\mu$ F, 20 kV working; C7, .01  $\mu$ F, 5 kV; C8, C9, 50+150  $\mu$  $\mu$ F wide-spaced variable; C10, .001  $\mu$ F variable; R1-R4, 15 ohms,  $\frac{1}{2}$ w.; R5, R6, 47 ohms, carbon, 2w. Valves are 813 and coils are explained in text. The RFC L3 should be designed for the job—see text.

for 80m, and 40m, only,

Two coils are fitted in series at L4 and a heavy-duty ceramic switch used. For 20m., 15m. and 10m. the tappings are on a self-supporting coil of light copper tube, internal dia. 21 in., over 8 turns in 3 in. The 80 m. and 40m, coils are on a braced winding of 16g, copper wire, 3½in. int. diameter, 2½in. long at 7 t.p.i. The exact tapping points should be found by experiment, aiming for current dip in the mid-range of the plate tune condenser.

It is of course necessary to have an aerial presenting a favourable SWR-otherwise RF may appear in the outer braiding of the coaxial feeder. This can result in TVI. parasitics or even RF burns from contact with the chassis. (It is also a sure indication that power "up the spout" is being lost).

# Results

This linear has been driven to full output with three different exciters: KW-200, Trio TS-510, and more recently a Sommerkamp FT-101. With a simple groundplane antenna, it yielded good results on 15m. and 20m., making 2-3 S-points difference in VK. It also works on 10m, with a ZL-Special. Recently, it has been used extensively on 80m, into a modified Windom, with a long-wire of 600 feet. So far, 104 countries have been worked, with good reports from VE, VO, ZL, PY, YV and other South American areas.

# R.A.E. COURSES-FINAL LIST

The following notifications were received too late for the September listings on p.430. In most cases, the Course will already have started, so application to the College or Evening Institute concerned should be made immediately.

Eastbourne: At College of Further Education, St. Anne's Road, evenings Tuesday (Theory) and Thursday (Practical), with P. Simmons, G3XUS, in charge.

Farnborough: At Cove Further Education Centre, Secondary School, St. John's Road—apply Principal.

London (Acton): At the Technical College, opposite Town Hall, on Wednesday evenings. Course lecturer W. G. Dyer, G3GEH. Apply to the College immediately for registration.

London (Islington): At De Beavoir Evening Institute, Balls Pond Road, Tottenham Road, N.1, on Tuesday and Thursday evenings—instructor F. Barns, G3AGP, enrolment immediately.

London (Wembley): At the Evening Institute, High Road, on Monday evenings, with A. Bayliss, B.Sc., G8PD, in charge. He has a long record of success in R.A.E. tuition.

Slough: At College of Technology, William Street, on Thursday evenings, with G3FVC and G3WQC in charge. Apply right away to the College, which also operates its own station G3XPL as part of the

Welwyn Garden City: At the College of Further Education, apply Principal. or G3IOZ, QTHR.

# TRANSMITTING ANTENNAE FOR SMALL GARDENS

INTERESTING HELICAL SYSTEM
ON TOP BAND

# J. S. CUSHING (G3KHC)

ONE of the problems many amateurs have to solve is how to radiate a reasonable signal from a small garden. The QTH where the aerial systems described here are installed has a garden just over 40 feet long, so elaborate layouts are impossible. A major handicap is the difficulties involved if masts of any height are installed. Obviously, siting and guying even one mast of more than 25 feet is not easy, while if a taller mast is somehow contrived there is always a risk of damage to a neighbour's property. On the principle that good neighbourly relations are more important than an extra S-point with a W2, only one mast about 20 feet high is used. This is near the end of the garden and by using the rear of the house in place of a second mast, a maximum top length of just over 30 feet is possible.

Aerials made by folding about 70 feet of wire into the space available radiate a good enough signal on 160 and 80 metres to allow plenty of contacts, though mostly only local ones result. A very much folded 140 feet has also been tried but this maze of wire gave only slightly better results.

On 20 metres with either of these aerials results were very poor even though all indications suggested they were taking power. But as soon as a simple dipole was put up contacts with European countries became easy. Such an aerial at 20 feet will not open the door to DX working, but on the other hand contacts up to 1500 miles are regularly and easily made with reports up to 5-and-9, and sometimes W's are worked with no great effort—this with an *input* of less than 50 watts p.e.p. The reason for these results is easy to understand if azimuthal radiation pattern diagrams for simple aerials are studied. For a height of about 20 feet—with a 20-metre aerial—radiation will be mostly at high angles, hence the ease in working Continentals.

Practical advice seems to be: Get the aerial up to about 20 feet and plenty of QSO's should result. DX contacts will be very few, but recalling how fierce competition can be, it may be argued very little is being missed.

Having made some progress with 20 metres attention was returned to 160 and 80m. Operation on these bands was possible by the common expedient of straping inner and outer of the coax feeder to the dipole.

# Another Approach


At this point it seemed no further progress could easily be made when brief mention of a helically wound aerial suitable for Top Band was noticed in the '69 ARRL Handbook. Briefly, the idea is to wind 250 feet of wire on a wooden pole 15 to 20 feet high. This is fed with 70-ohm coax which may be taken straight to the Tx


as no ATU is needed. For a vertical radiator less than 20 feet high, which can be placed in any convenient spot, results are very good and lively interest was shown by some stations contacted. If Fig. 1 is referred to the general idea should easily be visualised The mast is about 20 feet high and one or two inches in diameter. It must of course be non-metallic so a short wooden scaffold pole, a couple of stout 10 foot bamboos (suitably joined) or thick dowelling are suggested. Uniformly wound over the length of the mast, except for a couple of feet at the bottom, is 250 feet or wire. This should resonate at 2.0 MHz or a little above and to bring the system to resonance in Top Band a tapped inductance is connected between the inner of the coax feeder and the bottom of the helix. The outer of the coax is earthed below the mast.

Turning to constructional aspects the point to keep in mind is there seems to be nothing very critical about dimensions. The *Handbook* does not lay down any rigid data and, as will be seen later, data for this aerial departs a good deal from recommendations in the *Handbook*.
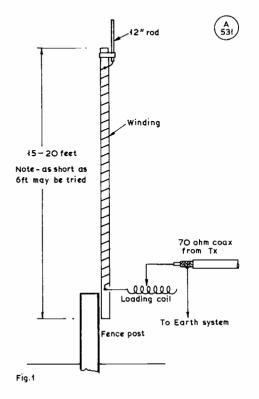
# Construction

A mast was made by joining two 9-foot lengths of one-inch diameter wooden poles, these being joined as shown in Fig. 2 with a halving joint. This joint is not the strongest possible, but should be no problem to anyone with a modicum of skill in woodwork and needs no special tools other than a small handsaw. Three 2BA screws and nuts secure the joint and the small amount of



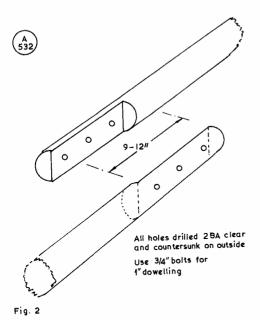

metal seems to have no ill effect. Having joined the two sections a couple of coats of varnish are applied as weather proofing. Winding 250 feet of wire on to the mast comes next. This should be done carefully so the winding is reasonably regular. Making this winding is rather tedious and takes some time so is best started when time is available to work steadily and get the job done in one go. If a thicker mast or a different length of winding is used, frustration will be avoided if a little figuring is done first mainly to determine the number of turns per inch. Any join in the mast may be covered with a layer of black insulating tape to provide a smooth surface for the winding.

When complete, the winding should be liberally doped with more varnish to fix the turns in place. Once the helix is finished the remainder of the job is easy enough. A fence post or something similar is sunk two or three feet in the ground with the mast fixed to it with home made clamps of thick sheet aluminium. The tapped coil is housed in a plastic box and waterproofed with black *Bostik*.

There remains an earth system. Buried radials are recommended, but several earth rods will do instead. For initial trials one earth rod will suffice.

# Testing

To check resonance of the system, feed "full" output from a signal generator into the coax feeder and place a field-strength meter close to the mast. The meter (which should be of the aperiodic type) will peak as the generator is tuned through the resonant frequency. If different taps are selected optimum taps for various parts of 160m. can be found. (No doubt a GDO could be used instead, though this was not tried.)

When it came to on-the-air testing, a pleasant surprise resulted. It had been assumed in view of the low height and small size that only very local contacts would be possible—but early contacts proved, it was radiating very well and several stations commented on the strength of the signal, and were much interested when told of the nature of the aerial.

# Results


Sufficient QSO's have now been made to establish its performance with some certainty. There seems little doubt that a strong ground-wave goes out with a maximum range of 25 to 30 miles. Nearby contacts are S9+, at 10 miles generally S9 and at 20 miles usually S8. Beyond 20 miles the signal weakens rapidly and ground-wave contacts in excess of 30 miles have not been possible. These figures are across open country. Contacts across heavily built-up areas are not so good—but compared with a folded 70 feet of wire, results are considered very good.

At greater distances performance has been less easily determined, but the following serves as a guide: Up to about 200 miles reports are poor, but beyond this they improve—R5/S5 has been given at 250 miles and R4/S5 at 500 miles. Again, other aerials tried have never produced even these results.

It is, of course, a Top Band-only system and will not work on other bands. If an ATU was placed at the bottom of the helix other bands might perhaps be used. This has not been tried so no comment can be offered.

Reception of Top Band signals is also very satisfactory. In the S.E. of England, GW, GI and GM stations are often heard. Harmonics from TV time-bases, which are so often troublesome, are considerably attenuated—the effect is quite noticeable and this system could be recommended on these grounds alone.

The manner in which this aerial works is not very clear. It does not function as a half-wave (250 feet is approximately a half-wave on 160 metres). It rather acts as a vertical quarter-wave and the ARRL Handbook does mention this. This is borne out indirectly by remembering the feed impedance of a vertical quarter-wave is 50 or 60 ohms and that the ordinary 60/70 ohm coax used makes a good feeder. Low readings on a SWR Bridge tend to confirm the above.

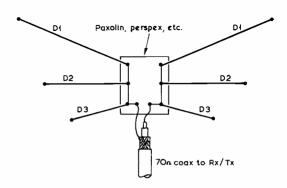

Di: 20 metre aerial, total length about 33 feet

D2: For 15 metres, 22 feet

D3: 10 metres 161/2 feet approx.

Fig. 3



These two aerials then, erected in a small garden, have given superior results if compared with a short wire aerial and have produced many enjoyable QSO's. The chance to work DX only occurs rarely but when worked is perhaps more satisfying for that reason. There is, by the way, no need to keep to 160 and 20 metres. The helical can be wound for 80 or 40m. instead and a 15 or 10-metre dipole used in place of a 20-metre one—or perhaps the idea in Fig. 3 could be tried, if all HF bands are to be used. Construction data for the 160 metre aerial is given herewith. If it is checked against that in the *Handbook*, several differences will be noticed, suggesting there is nothing critical about the design. Probably the only important factor is the length of wire used. This was in fact measured fairly carefully and must

have been within a foot or two of the required length of 250 feet.

## Aerial

Length of mast 17ft. 3in.; diameter of mast one inch; length of wire 250ft.; length of winding 13ft. 6in.; pitch of winding 6 t.p.i.; gauge of wire 28g., or heavier.

# Tapped Inductance

100 turns close wound, 18g. on 1½in. former, taps every 5-10 turns.

Three or four light guy lines are advised if a one-inch

# ADJUSTABLE HT SUPPLY

FOR TRANSMITTERS—SIMPLE CIRCUIT DEVICE

F. G. RAYER, A.LE.R.E. (G3OGR)

SOMETIMES, as when running valves at maximum ratings, it is necessary to have some way of varying the HT voltage over a moderate range. To the best of the writer's knowledge the method shown here has never appeared in the literature, and it was suggested to him some years ago by GW3OXE.

In the diagram, T1 is the usual mains transformer, in this case with two semi-conductor rectifiers, with limiting resistors R1 and R2. C1, C2 and the choke are the customary smoothing components.

If C1 is connected in the usual way, a capacitor input circuit is in use. If C1 is disconnected, choke input gives a substantially lower HT output voltage. With VR1 included as shown, a smooth control over HT output from the capacitor input to the choke input conditions is available.


# Voltages Obtained

The range of adjustment actually secured depends on the choke inductance and resistance, rectifiers, R1 and R2, and effective supply resistance of the windings of T1, as well as upon C1. In such a circuit intended for the supply of early stages of a transmitter, adjustment range was from 225v. to 300v. at 100 mA, using a 300-0-300v. 120 mA transformer.

The maximum voltage output is of course that which would be obtained with the usual capacitor input, VR1 giving a reduction from this level.


In the case of a 500v. HT secondary, approximately 420v. was obtained at 50 mA to 125 mA, with VR1 at maximum value. With VR1 at minimum, the HT voltage was about 520v. at 50 mA, falling to around 500v. when loaded to 125 mA.

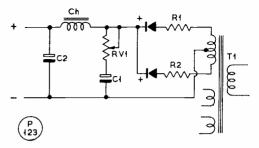For maximum HT output, R1 and R2 are of the lowest value for making up the total effective supply resistance to the minimum safe value for the rectifiers, for a specified value at C1. The choke also needs to be of low DC resistance. However, placing VR1 in circuit



will allow the voltage to be reduced with any capacitor input circuit. The method is most suitable for equipment imposing a steady HT load.

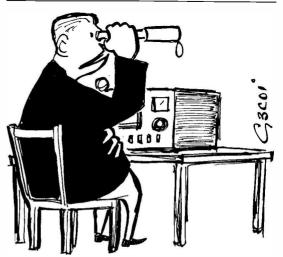In using this circuit it becomes apparent that VR1 needs to be quite a large wire-wound component—to carry the watts. A value of 2K was used, but 1.5K to 2.5K should be suitable. After setting operating conditions for the required output voltage, the portion of VR1 in circuit could be measured, and a fixed resistor of similar value permanently substituted for VR1.



"... Using a remote-reading field strength meter here, OM ..."

# VEHICLE NOISE SUPPRESSION FOR MOBILE OPERATION

DEALING WITH A MORRIS 1000

D. G. ARIGHO (G3NVM)

Based on material appearing originally in the July 1971 issue of "Mobile News", the approach and methods suggested by G3NVM would obviously be applicable to almost any make of car requiring rigorous noise suppression treatment.—Editor.

Having recently installed 160/80 metre transmitting and receiving equipment in my Morris 1000 for mobile operation, I found various interference problems had to be overcome before satisfactory mobile operation was possible. Whilst I do not claim that the following notes are original, they are an accumulation of various hints and articles which were perused in the effort to find a cure for my own particular interference problem.

## Mobile Installation

The equipment being used consists of a home-built Tx and a Codar T.28 Receiver. The transmitter is located directly over the transmission shaft and below the heater outlet. The receiver is just under the driver's glove compartment. The antenna is a 9-ft. centre-loaded whip with an adjustable capacity hat on the high end of the coil and resonates in the 160-metre band. The aerial mounting is on the rear bumper (driver's side) and a coaxial lead taken through the luggage boot under carpets to the front of the vehicle to the transmitter.

# The Dynamo

The first mobile trials were not very encouraging as the interference whine from the dynamo was equivalent to an S8/9 signal on the receiver so it was virtually impossible for contacts to be made when the vehicle was moving.

This was tackled first; a standard car suppressor  $(0.1~\mu F)$  was fitted between the dynamo output and the casing and this improved reception as the dynamo noise level was considerably reduced. The next step was to remove the dynamo and examine the state of the commutator and brushes. The commutator was found to be very dirty and the brush wear was uneven. The commutator was well cleaned up and a new set of brushes bedded in. The possibility of physically mounting the dynamo suppressor capacitors directly on the brushes and inside the dynamo case was investigated and eventually a  $0.1~\mu F$  and a 1,000~pF were wired in parallel across the brush holders.

The first test proved that there was not a trace of dynamo interference at various engine speeds and reception was possible on 160/80 metres. However, now that the dynamo trouble was cleared up, I was permitted to hear interference from the distributor (ignition interference), this was bearable but it was decided to try and eliminate it. The first thing was to fit standard plug

suppressors to all the plugs leads (these can be purchased through most Lucas agents) and a cut lead suppressor to the HT lead to the coil. This modification was tried with a noticeable improvement. The next step was to fit a  $0.1~\mu F$  capacitor to the LT side of the coil (SW)—and again there was an improvement.

# Wheels and Tyres

Then it was discovered that now either wheel or brake static was evident and at S9-plus, making it virtually impossible to copy anything at all. Back to the square one. A quick jab at the brakes confirmed that it was not brake static as it did not disappear when the brake was applied, so it must be a combination of wheel and tyre static.

A rethink and a reread of various manuals dealing with interference disclosed a number of solutions. The first one was to inject anti-static powder into the tyres. Great! But have you ever tried getting any anti-static powder? . . . every tyre distributor I inquired at said "Never heard of it."

The BMC people in Cambridge said there had been a kit of anti-static brushes for a Morris 1000 but they were no longer being manufactured. I had an idea of what would be necessary for these brushes, so I decided to make and fit my own interpretation of them.

Make sure that all the grease is removed from the contact area before refitting the hub cap otherwise you will be wasting effort. The rear wheels not having the removable hub caps required a rethink, and eventually it was decided to drill the rear brake drum and mount a phosphor bronze spring in each rear wheel, so that when the brake drums were refitted they would make contact against the springs and "ground" the wheel to the axle.

# **Final Triumph**

When the modifications were complete and the mobile equipment tested on the road on 160/80 metres a marked reduction was evident. The ignition interference was well below the noise level and the tyre/wheel static had virtually disappeared. As a last refinement a tin of tyre wall paint (obtainable from Halfords) was bought and a mixture of 25% powdered graphite and the tyre wall paint was made up. This was then painted on to the outside walls of the tyres; a retest was arranged and *presto*, no sign of any tyre or wheel static was evident at all.

# Bonding

It should be mentioned that after this exercise was complete about two days were spent underneath the car taking resistance measurements between various parts of the framework. The results were surprising, as much as 20 ohms appearing between some panels and the overall chassis. Thick, heavy wire was used to bond most of the chassis items to the various panels where these large resistances were encountered. I cannot say that this has at all helped with the *interference* suppression but the signal strength on both transmit and receive has improved remarkably!

One other point worth mentioning which might interest Morris 1000 owners is that the front and rear wheel suspensions are connected to the chassis through rubber bushes, so theoretically the front wheels are insulated from the chassis by these rubber suspension (cont'd. p.480)


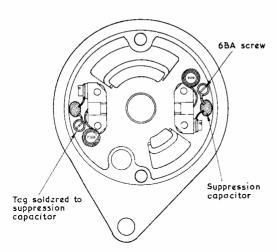


Fig.1 Dynamo End Plate

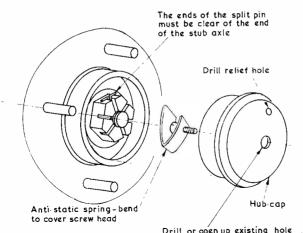

Drill or open up existing hole to clear 4BA screw (No. 25 drill) The hole must be in exact centre of cap

Fig 2. Fitting Anti-static Spring to Hub cap.

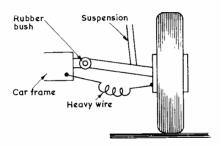


Fig.3 Grounding Front Suspension

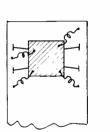


Fig. 4 Engine mounting grounding points


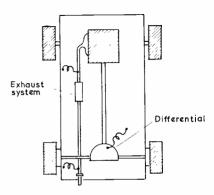


Fig. 5 Additional grounding points

 



Hub casing————— Anti-static spring
Fig. 6 Fitting of Anti-static Bracket to Brake Shoe

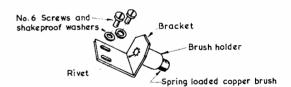


Fig.7 Commercial anti-static spring

bushes. Both front wheels were grounded to the chassis with a short length of heavy flexible cable, the grounding points being from the rear of the front-wheel brake drums direct to the chassis; enough slack grounding cable must be left to allow for the steering linkage, otherwise every time you turn a corner the grounding cable will snap. The rear suspension and exhaust system were grounded from the differential casing to the chassis, also with a short length of heavy lead.

# Conclusion

Perhaps one final comment: During the past few months or so attending various Mobile Rallies and talking with a multitude of Morris 1000 owners everyone had the same comment—in their opinion the Morris 1000 was the worst car they had experienced for ignition and wheel static interference! So, if you're seriously thinking of going mobile, unless you are prepared to do a lot of painstaking work buy another car, one which has a good reputation for interference-free reception from the outset.

# BEAM DIRECTION INDICATOR

FOR REMOTE READING AT OPERATING POSITION


# J. M. ORTON (G8CHP)

A FTER constructing a rotator for a 2-metre Yagi, the writer had to decide upon a suitable means of determining the direction in which the beam was aimed. Various methods were considered, but the best, it was decided, would be to arrange for one rotation of the aerial to perform about \(\frac{1}{3}\)-turn of a wirewound potentiometer, which would form one leg of a resistance bridge. When the rotator turned, the alteration in resistance so caused, would unbalance the bridge, and cause a deflection on the meter—see diagram.

The writer's rotator was constructed so that when the North heading was reached, a micro-switch broke the motor circuit for that direction (to avoid coax cable tangling) and the potentiometer from being turned past its end stop. Micro-switches were fitted both fully clockwise and fully anticlockwise, although only the actual indicator is dealt with here.

The gearing down of the potentiometer from the rotator drive spindle was achieved quite simply by a 3in. slow motion drive wheel on the potentiometer, friction driving against a one-inch grommet on the rotator spindle; when the slot in the wheel was engaged with same in the grommet, a reliable drive was made, which did not slip, even after continued use.

In the writer's prototype, the meter was set up to read "N" (north) at the zero point on the meter, when the aerial was fully anticlockwise, and "N" at full-scale meter reading, when the aerial was fully clockwise. Thus, the meter read "N-E-S-W-N" left to right. As the rotator motor supply was 50v., it was considered convenient to use this for the bridge supply voltage. Setting up the meter swing was easily done by adjusting

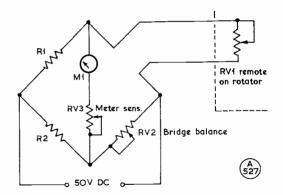

Circuit of the beam direction indicator described by G8CHP, for mounting at the operating position. Values are: R1, R2, 10K; RV2, 470 obms; RV3, 5K; meter 0-1 mA. RV1 is a 470-ohm potentiometer activated by the rotator, mounted in some convenient manner to obtain drive—see text.

RV2 for bridge balance with the rotator fully anticlockwise, then rotating the aerial fully clockwise, and adjusting RV3 (meter sensitivity) to full scale reading. If a linear wirewound potentiometer is used, it will be found that the compass points are equally spaced across the scale.

# POINTS OF INTEREST

Those concerned about calibration accuracy should remember that Rugby, MSF, transmits standard frequency and time signals on 60 kHz and 2·5, 5·0 and 10·0 MHz—the LW signal is 24-hour and the HF-band transmissions are for 12 hours daily.

It is announced that WWV, Fort Collins, Colorado, U.S.A., no longer uses any Morse in its transmitting sequence. Frequency, time and audio tone signals (440, 500 and 600 Hz) are radiated on 2.5, 5.0, 10.0, 15.0, 20.0 and 25.0 MHz. For the U.K., the 15 MHz transmission is probably the most useful.

A number of South African stations—ZS's 2BZ, 2CC, 2DD, 2GE, 2GZ and 2OW—are working RTTY on the 50 MHz (6-metre) band. There is no allocation for this band in the U.K.—however, previous experience suggests that they could be receivable here when ten metres is open to the *States*, during which periods the MUF can go high enough for ZS signals on 6 metres to be heard in the U.K. (it has happened) thus making a cross-band RTTY contact G/ZS possible.

For the last R.A.E. in South Africa, basically the same as ours, 55 candidates sat of whom 48 passed, with a best top mark of 89%.

For the forthcoming J-O-T-A during October 16-17, the representative station for South Africa will be ZS6JAM, Mafeking, scene of the famous siege during the Boer War when the late Lord Baden-Powell, founder of the Scout movement, was in command.

# PERSONAL PORTABLE FOR TWO METRES


CAPABLE OF

INTERESTING

RESULTS — DESIGN

AND

CONSTRUCTION

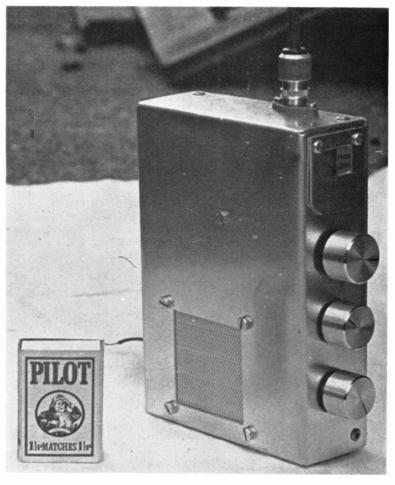

General appearance of the completed two-metre personal portable, as designed and constructed by G3TDZ, with a size comparison. The speaker is behind the grille. The Tx runs two watts and more than 100 stations have been worked using simple antennae.

# J. R. HEY, M.S.E.R.T. (G3TDZ)

FOR some time policemen have been wandering around with a radio station in their top pockets, so why cannot radio amateurs who have had more experience?

At the risk of someone saying, "Not another portable from old 'TDZ', a suggested design is offered which will enable our VHF fraternity to take their hobby with them anywhere they wish.

The realisation of the availability of certain useful components prompted this design. A miniature 3-gang capacitor is advertised by two well known dealers at only 25p; a Mullard TAD110, 14 pin dual-in-line IC with a matching ceramic 465 kHz IF filter were bought for £1·19 and 77p respectively. With just a small handful of extra components the second conversion stage or tunable IF could be designed. A fairly conventional converter section or front-end could then be added, so producing a small receiver of adequate performance.

A number of firms offer miniature high-frequency crystals at reasonable prices which means that both the converter oscillator chain and transmitter can be designed economically.

# Receiver Side

Using Mullards published data on their TAD100 and TAD110 IC's, a basic receiver was lashed up in bird's-nest form and evaluated. It was decided that 12v. operation was going to be the most useful choice and the whole circuit was designed around this voltage, a small stabiliser being included to provide 6v. for the IC. The only remaining transistors necessary were the two output devices, AC188 and AC187, but as a pair of AC128/AC176's were waving from the junk box, these were substituted.

Within the single IC are mixer, oscillator, IF, detector, AGC and audio stages up to output level. It was found, however, that the internal oscillator when tuning 14·5-16·5 MHz was insufficiently stable, the drift experienced being quite unacceptable. A separate Clapp oscillator and emitter-follower was tried, injecting into the mixer base available at pin 13 of the IC; this proved most

satisfactory—in fact the emitter follower was omitted in the final design.

The LP1175 ceramic IF filter overcomes the need for careful IF alignment before anything else can be tested, as in more usual circuits.

In order to avoid conversion birdies, the second-conversion oscillator frequency must be chosen with care. An oscillator covering, for example, 18·4-20·4 MHz would be a good choice in that the nearest the 8th harmonic would come is 1·2 MHz above 146 MHz and the closest the 7th harmonic would be is 1·2 MHz below 144 MHz. It could be argued that it might be better to suffer one odd birdie than sacrifice oscillator stability by operating so high; this is up to the individual and more to the point, what crystal is available. An odd harmonic like an 11th or 13th might not be too drastic.


For this unit a 64.5 MHz crystal was obtained at modest cost, thus fixing the injection at 129 MHz which meant an IF of 15-17 MHz. The oscillator must run either 15.465 to 17.465 MHz or 14.535 to 16.535 MHz, and in practice the upper one is used plonking a nasty

9th in the band, causing a couple of noticeable responses in the lower half. (Oh well, you can't win 'em all.)

A double-tuned critically coupled pair of coils as intermediate IF was considered adequate, and with 35 pF trimmers added to the 14.5 pF swing of the 3-gang, only 19 turns of wire was needed on the standard 3/16in. dust-cored formers. Later, one of these was adjusted to 17 turns and the other increased to 21 turns to make tracking easier.

The two formers are placed 0.4in. apart, which gives the desired coupling, also making it easy to connect to the 3-gang. On top of the secondary winding five turns are wound as a link to feed the mixer in the IC.

Again, the front end or converter design was dictated by component availability. Two Japanese FET's, 2SK19, were to hand and these were to be used in a cascode RF stage. With these had come a planar bipolar transistor 2SC785, recommended for use as mixer in VHF domestic radios and TV's. Perhaps another FET might have been better but beggars should not be so choosey. Whilst this arrangement has proved to be very

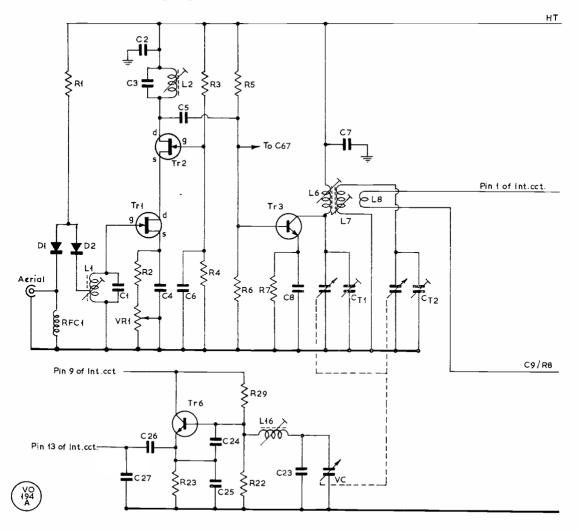

good, obviously the S2K19's could be replaced by 2N3819's or UC734's, etc. For those wishing to be more "with it", one of the new dual-gate Mosfets such as 40673 or 40820 should make a lively RF stage.

A straightforward overtone circuit using a BC109 was wired for the crystal followed by a 2N918 doubler; injection is made to the mixer base through a 1.5 pF capacitor.


Earlier experiences have indicated the desirability of an RF gain control; a 10K pot. is wired in series with the RF stage source resistor and is a most effective addition. A slight trace of RF instability was cured by simply earthing the brass slug in the drain tuning coil. A gold-plated lead wire from a transistor was heated and pushed through the plastic coil former and soldered to the earth track of the printed board, the slug when re-fitted being earthed.

Now jumping to the other end of the IC: The AF

output transistors were pushed into a double heat clip and the thermistors recommended for biasing the bases of the Class-B outputs replaced by a single NKT279A diode. The reason for this was not particularly because of the argument that a diode provides better regulation against supply variations but that sheer meanness guided the writer towards the junk box rather than the shop.

A slight modification to the driver load resistor values and the biasing resistors of one side of the differential was made to allow the full 12v. to be applied to the audio output and retain equal clipping.

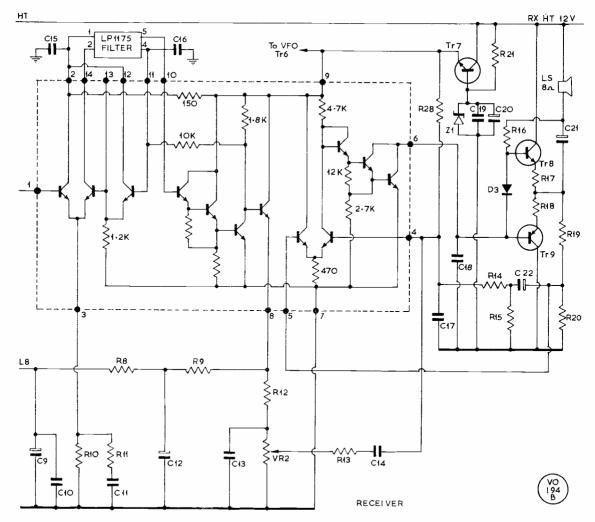The simple stabilised source consists of a medium power TO5 transistor as series element with a 6.8v. zener in its base. The zener is actually an old planar transistor using only its base-emitter junction connected backwards. This is a handy way of obtaining low power zener diodes around 5-11v. as general-purpose planar transistors are much cheaper than pukka diodes. A



Receiver Circuit, G3TDZ Personal Portable — read from left, opposite page. Table of Values overleaf.

 $\cdot$ 001  $\mu$ F ceramic and an 80  $\mu$ F electrolytic are placed in parallel across the zener, the latter being amplified by the gain of the transistor provides good decoupling whilst the small capacitor overcomes the noise sometimes generated by zener diodes.

Screening plates were fitted between RF and mixer and between oscillator and doubler. Nothing much can be done about the IC, one must trust providence.

#### The Transmitter

Apower of two watts was considered the wisest choice between economy and effectiveness. The BLY33 seemed to be the best choice for the PA as many RF power tranictors are not at their best at only 12 volts.

A 72 MHz crystal is wired in an overtone circuit, a capacitive tap coupling its output to the doubler. The oscillator uses a BC109 transistor whilst the doubler is happier with a 2N918.

As the input capacity of the RF power devices is as high as 100 pF and outputs in the order of 10-12 pF, simple parallel tuned circuits and *pi*-couplers are not much use. It was decided to use L-*pi* coupling between driver and PA, and again between PA and the 75-ohm aerial outlet.

For the driver, which develops about 40 mW, a 2N3553 or BLY33 is recommended.

In order to tune out the huge input capacity of the driver, a  $1\frac{1}{2}$  turn 0.06  $\mu$ H coil, L11, is placed in series with the base and resonated by 22 pF to the top of which the resonating capacitor of the doubler is connected. The doubler does in effect use a parallel tuned circuit,

its 4-turn coil L10 connecting to a well-decoupled HT. The DC return rath for the driver base is *via* a small RF choke consisting of two turns wound on an FX1115 ferrite bead.

Emitter leads of both driver and PA must be very short as lengths greater than 2 mm, can cause instability.

The driver collector goes to a diode tap across the modulation transformer through another two-turn RF choke on a ferrite bead. The internal capacity of this transistor, allowing a loaded Q of 10, means the  $0.63~\mu H$  collector coil L12 requires only 1.8~pF for resonance. Like the driver the PA base is tuned by a  $1\frac{1}{2}$ -turn coil and 22 pF capacitor. In circuits where each resonating capacitor is of similar order in value, these may be lumped together and a suitable trimmer used. However, 1.8~and~22~pF are a bit off and are therefore wired in a series-divider configuration. In the finished unit, these values has to be adjusted a little; the 1.8~pF became 2.2~pF and the 2.2~pF reduced to 15~pF.

The output stage L-pi network is somewhat simpler as input and output impedances are closer. We know we must aim at 75 ohms for the aerial output, the PA transistor looking like 36 ohms with 9-10 pF. The first section has a Q of 10 and the second a Q or 15 which means a loading capacitor of 28.5 pF (a 30 pF trimmer being used) with a centre resonating capacitor lumped into 8.7 pF, or a 10 pF trimmer.

A large diode is inserted in series with the last coil before the HT choke and blocking capacitor. This forms part of the solid-state aerial switching and being in the DC path as well as the RF path, appears as a low

# Table of Values For the G3TDZ Personal Portable

```
R1 = 6.8K

R2 = 220 ohms

R3 = 39K

R4 = 39K

R5 = 12K

R6 = 5.6K

R7 = 2.7K
                                                                                                    R41 = 680 ohms

R42 = 4.7K

R43 = 560 ohms

R44 = 1K

R45 = 2.2K

R46 = 100 ohms

R47 = 100 ohms
                                                                                                                                                                                                                                   330 pF ceram.
330pF ceram.
1000pF ceram.
                                                                                                                                                                                                                                                                                                                  Tr1 = 2SK19.
                                                                                                                                                                                                                                                                                                                                                                  2N3819.
                                                                                                                                                                                                             C25
                                                                                                                                                                                                                          _
                                                                                                                                                                                                                                                                                                                                      UC734,
2SK19,
UC734,
                                                                                                                                                                                                                                                                                                                                                                 etc.
2N3819
                                                                                                                                                                                                             C26
                                                                                                                                                                                                                                                                                                                  Tr2 =
                                                                                                                                                                                                                                   330 pF ceram.

0·01 μF foil

0·047 μF foil
                                                                                                                                                                                                                          ----
                                                                                                                                                                                                                                                                                                                                      2SC785, BF220
BC109
2N918
2N918
                                                                                                                                                                                                                                  0-01 μF foil

0-047 μF foil

33 pF SM

82 pF SM

0-022 μF foil

12 pF SM

22 pF SM

2000 pF disc

2·2 PF SM

18 pF SM

2000 pF disc

2000 pF deram
                                                                                                                                                                                                                                                                                                                  Tr3
                                                                                                     R46
R47
R48
R49
                                                                                                                           100 ohms
100 ohms
                                                                                                                                                                                                             C29
C30
                                                                                                                                                                                                                                                                                                                             =
                                                                                                                                                                                                                                                                                                                  Tr5
Tr6
                                                                                                                  22 ohms
47K
15K
680 ohms
    R8 =
                       8.2K
                                                                                                                                                                                                             C31
C32
                       8.2K
                                                                                                                                                                                                                                                                                                                                      BC441, BFX51,
NKT0028
AC176, AC187
AC128, AC153,
R10 = 820 ohms
R11 = 150 ohms
R12 = 390 ohms
R13 = 1K
R14 = 10K
R15 = 120 ohms
                                                                                                    R50
R51
R52
R53
                                                                                                                                                                                                             C33
                                                                                                                                                                                                            C33
C34
C35
C36
C37
C38
C39
                                                                                                                           68 ohms
560 ohms
10K 1in.
                                                                                                                                                                                                                                                                                                                  Tr9
                                                                                                                                                                                                                                                                                                                               =
                                                                                                                                                                                                                                                                                                                                       AC188
BC109
                                                                                                    VR1
VR2
                                                                                                                                                                                                                                                                                                               Tr10
                                                                                                                           5K log.
10K pre-set
                                                                                                                   ==
                       680 ohms
2-2 ohms
2-2 ohms
22K
R16
R17
                                                                                                                                                                                                                                   2000 pF ceram.
                                                                                                                                                                                                                                                                                                                                       BLY33,
2N3535
                                                                                                                                                                                                                                                                                                               Tr12
                                                                                                                                                                                                                                                                                                                                                                  2N3553
                                                                                                                         10K pre-set

5K pre-set

12pF SM

1000pF disc

12pF SM

0·01μF foil

10pF SM

0·01μF foil

0·01μF foil

0·01μF foil
                                                                                                                                                                                                                                  2000 pF ceram

0·1 \muF foil

100 pF ceram.

10 \muF 16v.

10 \muF 16v.

80 \muF 10v.
                                                                                                    TR2
                                                                                                                   _
                                                                                                                                                                                                            C40
C41
C42
C43
C44
C45
C46
C47
C48
R18
R19
                                                                                                                                                                                                                                                                                                               Tr13
Tr14
Tr15
                                                                                                                                                                                                                                                                                                                                       BLY33
BC109
                                                                                                                   _
                       10K
                                                                                                                                                                                                                                                                                                                                       BC179
R21
R22
                       4.7K
                                                                                                        C4
C5
              ---
                                                                                                                   _
                                                                                                                                                                                                                                                                                                              Tr16
Tr17
Tr18
                                                                                                                                                                                                                                                                                                                                       BC108
                       12K
1·2K
27K
                                                                                                                                                                                                                                                                                                                               -
                                                                                                                                                                                                                                  4 μF 10v.
200 μF 10v.
                                                                                                                                                                                                                                                                                                                                       BC108
R23
R24
R25
              _
                                                                                                        C6
C7
                                                                                                                                                                                                                                200 μF 10v.

100 pF ceram.

25 μF 25v.

400 μF 10v.

0-1 μF foil

0-01 μF foil

39 pF SM

0-01 μF foil

15 pF SM

470 pF ceram.

0-01 μF poly.

1-5 pF SM

35 pF trimmer

15 pF trimmer

10 pF trimmer

10 pF trimmer

30 pF trimmer

30 pR trimmer

30 pR trimmer
                                                                                                                                                                                                                                                                                                                               _
                                                                                                                                                                                                                                                                                                                                       BC178
                                                                                                                   =
                                                                                                        C8
C9
                                                                                                                          0·01μF foil
10μF 16v.
                       15K
                                                                                                                         0-01 μF foil
10 μF 16v.
0-1 μF foil
0-047 μF foil
0 μF 16v.
0-1 μF foil
0-22 μF foil
0-22 μF foil
0-01 μF foil
1000 μF foil
1000 μF foil
                                                                                                                                                                                                                                                                                                              Tr20
R26
R27
R28
                       680 ohms
22 ohms
27K
                                                                                                                   =
                                                                                                                                                                                                            C49
C50
                                                                                                                                                                                                                                                                                                                             = TAD110, TAD100

= BA141, BA101,

BA102

= BA141, BA101,

BA102

= BA114, D914,


1N914, 1N4148,
                                                                                                    C11
C12
C13
C14
C15
              =
R29
R30
                     510K*
27 ohms
33 ohms
                                                                                                                                                                                                           C53
C54
C55
             -
R31
R32
                                                                                                                  _
                                                                                                                                                                                                                                                                                                                  D3
                     33 of
1M
330K
27K
15K
150K
4.7K
56K
R32
R33
R34
R35
R36
R37
                                                                                                    C16
C17
C18
C19
                                                                                                                                                                                                            C56
             = 10D2, PL4003,
1N4003, OA202
= BZY88/7V or
                                                                                                                                                                                                          CT1
CT2
                                                                                                                                                                                                                         ==
                                                                                                                 =
                                                                                                                          80 μF 16v.
400 μF 10
4 μF 10v.
                                                                                                    C20
                                                                                                                                                                                                                        =
                                                                                                                                                                                                           CT3
R38
R39
                                                                                                                                                                                                                                                                                                                                         transistor*
                                                                                                                  =
                                                                                                                                                                                                                                 3 gang 18 pF
                       47
                                                                                                                           43 pF 5%SM
```

resistance when conducting during transmission but very high when on "receive," isolating the receiver from the PA tuned circuits. The PA HT feed is again *via* an FX1115 bead choke to the modulation transformer, their junction well by-passed close to the choke.

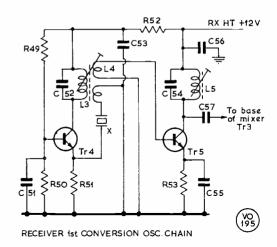
#### The Modulator

To obtain the necessary voltage swing from a complementary output circuit working at 12v., a step-up transformer of about 3:1 ratio is required. This means the output transistors are seeing only 4 ohms and large peak currents are possible. Transistors capable of 2A minimum are advisable and BD131/BD132 were found to fit the bill. These are very small opoxy types and being capable of 11w. each do not need heat sinks at low power.


The complementary output pair are driven by complementary drivers BC108/BC178, these being preceded by a further BC108 pre-drive with a p.n.p. BC179 voltage amplifier. Overall NFB is applied as in all the best Hi-Fi circuits, a very splendid audio waveform appearing across the modulation transformer, even with



Rx 1st Conversion Oscillator Chain.

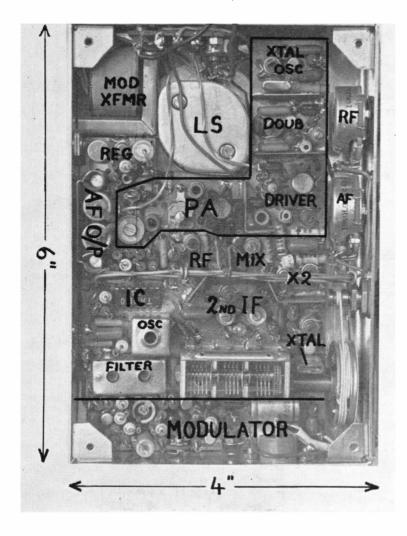

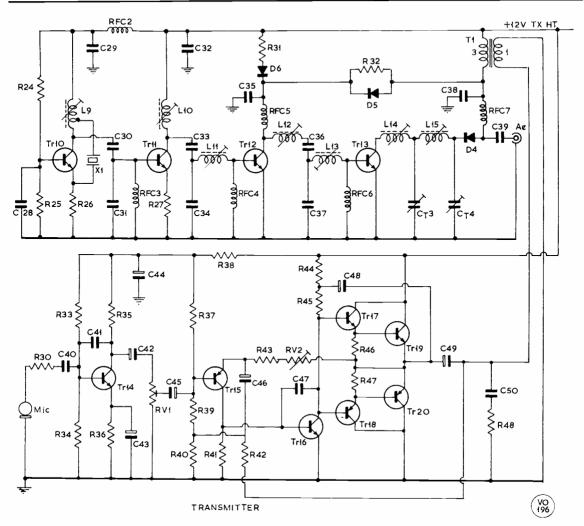Showing general layout inside the chassis with main sections of the circuit identified—compare with circuit diagram The size of 6in, by 4in. would be quite comfortable for hand-held operation.



The G3TDZ Two-Watt Transmitter Circuit.

#### TABLE OF COIL DATA

4 turns, 22g. TC, spaced ½in., tap 1½ turns up, ferrite slug.
4 turns, 22g. TC, spaced ½in. brass slug.
5 turns, 22g. TC, spaced ½in., tap 1 turn down from cold end or wind 1 turn PVC link over main winding.
2 turns, 22g. TC PVC wound on top of L3.
4 turns, 22g. TC, spaced ½in., ferrite slug.
21 turns, 26. enam., close wound, ferrite slug.
5 turns, 26g. enam., close wound, ferrite slug.
5 turns, 26g. enam., wound on top of L7, insulated 1 layer paper.
5 turns, 22g. TC, spaced ½in. tap 1 turn from cold and

L4 L5 L6 L7

1.8

L9

L12

1.14

paper.

5 turns, 22g. TC, spaced §in., tap 1 turn from cold end, ferrite slug.

6 4 turns, 22g. TC, spaced §in., ferrite slug.

7 2 turns, 22g. TC, spaced §in., brass slug.

8 12 turns, 24g. enam., close wound, ferrite slug.

9 turns, 24g. enam., close wound, no slug.

9 turns, 24g. enam., close wound, no slug.

10 turns, 24g. enam., close wound, no slug.

11 turns, 24g. enam., close wound, ferrite slug.

12 turns, 26g. enam., close wound, ferrite slug.

13 turns, 26g. enam., ferrite beads FXIII5.

140 turns approx., tetrafillar wound: see text.

= 120 turns approx., tetrafillar wound; see text.

Notes: All formers are fain. diameter. TC indicates tinned copper wire. Ferrite slugs must be of a material suitable for VHF use. Coil values may require adjustment, depending upon layout, and should be regarded as for guidance only.

RF on load. A further BC109 microphone pre-amp is necessary; a small skeleton pre-set pot, is included to regulate the modulation depth.

(To be concluded)

#### THE EI/GI CONVENTION CANCELLED

It is with much regret that, consequent upon the present troubled situation in Ireland, we have been asked to announce that the normally very happy and successful EI/GI Convention has had to be cancelled for this year. Our authority for this dolorous announcement is W. McIlwaine, EI9F, secretary, I.R.T.S., who sent us the notice appearing under "Points of Interest" on p.424 of the September issue of SHORT WAVE MAGAZINE. The president of the Irish Radio Transmitters Society is A. D. Patterson, EI4BC/GI3KYP-who at one time served a term as president of the RSGB.

#### PICTURES FROM THE MOBILE RALLIES



Having a person-to-person QSO at the Derby event were, left to right: G3XMI, G3XGP, G8CVR (all from Birmingham), G8BFV (Portsmouth) and G8CLY (Chelmsford).





(Above) At the recent White Rose Rally, left to right, Mr. and Mrs. G6QO, Mr. and Mrs. G3IJC and Mr. and Mrs. G6AU. At right, the two-metre talk-in station, signing G3XEP/A and operated by G3ZTU when this picture was taken.




Another group caught at the Derby Rally—left to right: G3XOC, VK6KK, G4JW, G5ATB and G3YOA, who came from parts far and near for the occasion.
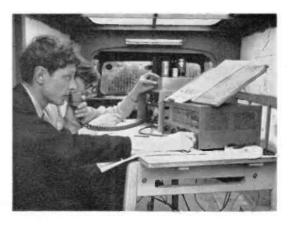
#### MORE RALLY PICTURES



Those concerned with the mounting and organisation of the recent White Rose Rally in Leeds included, left to right: G3XUD, G3YFP, G3YEE, G8DSW and G3ZKH. They put on a very good and successful show.



The Top Band talk-in station for the Derby Mobile Rally, signing G3ERD/A (one of the Derby Club's own callsigns) operated by G3UQV, with G3ZYD reading the map and doing the logging.



For the Derby & District Amateur Radio Society Mobile Rally, the 14th in their series of these events, once again there was a large attendance with "numerous attractions for all comers"—some of whom are pictured here waiting for the next item to be offered in the monster Junk Sale, always one of the main Rally interests at Derby.

"Short Wave Magazine" covers the whole field of Amateur Radio and should be obtainable to order through any newsagent.

A PART from those openings mentioned last month, the remainder of August was fairly quiet on all the VHF bands. Best days were August 16/17 which saw a good 2m, lift to PAO, and the 18th, when 70 cm, was wide open to PAØ and DL, but little G activity to be heard. Your conductor worked six PAØ and two DL off one CO (the PAØ beacon was at 5 & 9) and asked each of them if there was other G activity to be heard but the answer was-none. Odd! The necessary tropo, was there to enable the G3BA/G3BHT/G3URV expedition to LX to make many G contacts before, during and after VHF/NFD at the start of September. Stations well down into France and to the East were also audible at good strength late on the afternoon of September 5. GW to East Coast G was also good on the night of September 3. September 6 produced some reasonable DX on 70 cm, although the other bands were quiet at the time, and GM was worked from Herne Bay on September 6, 7 and 8. During the contact with GM8BRM/P in Aberdeenshire on the 7th, Iain mentioned that he had had 37 Continental contacts that evening, so there was certainly a path from the North to the South East! The Angus beacon was being heard in the South on these two nights at good level, and on the following day DLØPR was at 5 & 9 at 0933z, although signal strengths had dropped appreciably an hour later. G3ZPZ worked GM8CUW/A in Yell in the Shetlands and got 5 & 9 on September 8. The Islander, an ex-Leeds man, runs 10 watts on 145.62 MHz. So September has come in like a lion, and it remains to be seen how it exists As elaborated below, conditions during VHF/NFD were above par.

#### VHF NFD

Weather conditions were splendid for this event, and were almost matched by propagation conditions, which were showing a welcome lift on all the VHF bands. On 4m., the propagation appeared to be up in pretty well all directions, with GM, EI and GI all workable from the South. The Cornish stations were being worked in the North, and the Welsh portables were heard well in

# WHI BANDS

A. H. DORMER, G3DAH

the South and East. On 2m., the best DX axis was undoubtedly to the South and South-East at the start of the contest, but swung round somewhat towards the end. when DL and PAØ were plentiful. HB, LX, OE2 and EA were all worked from Kent on this band. No reports have been received of reception of SM or OZ, and this year, there was no aurora to help. 70 cm. was not nearly so productive of DX as were the lower-frequency bands, 200 miles or so being considered good, and no Continental contest activity to help swell the totals.

Traffic on all bands seemed to be a bit up on last year, but the slightly less favourable propagation restricted some of the scores heard. Nevertheless, there were some pretty useful totals being passed. On 2m., DL2OM was giving 409S at the end: GW3NUE/P (Brecon) passed 305S at 1630z, and that should mean a fair number of points, since most of these must have been at good range; G2JF has 225 contacts, of which some 80% were Continentals. An early score noted was that of GC3ZXR/P in Alderney who gave 241S at 1145z, so he should be up above the 300 mark, with some good long-haul stuff into the South and West of France from the C.I. To give some idea of the scoring rates on two metres, G3WIR/P near Stokenchurch passed 151S at 1115z and 180S at 1640z-29 stations in 5½ hours. G3SDS/P near Bridport

gave 128S at 1150z and 166S at 1615z making it 38S worked in 4 ½ hours, so the going was not all that easy.

Scoring rates on 4m, were also slowish, with little CW activity to help the DX along. Several stations were over the 90 mark, but the top score will probably be something around 130. Activity on 70 cm. was apparently higher in the North of the country, where propagation was also better. G8AWS/P near Buxton for example, had got over the 100S by midday on Sunday, including EI, but in the South, apart from the well-sited portables on the Coast, it all seemed a bit of a struggle, and this ties in with the customary picture of activity levels in the two areas

There was a distinct lull in the proceedings around 1600z, and several stations were heard calling "CQ Contest" after 1800z, presumably because contradictory times had been published. The official times coincided with the IARU Region I event, i.e., 1800z September 4 to 1800z September 5.

Inevitably, it seems, there were some pretty dreadful signals around, some on 4m, and 70 cm., but the majority were among the 2m. portables again. Bad quality modulation was the most prevalent fault, followed by generator hash and There was the usual instability. overcrowding at the LF end of the band regardless of the Band Plan. although VFO's were being used more intelligently, and therefore socially, than on some previous occasions, and it was noted that stations operating on fixed frequencies, or using the VFO but rarely, were doing equally as well as the "here, there and everywhere" gentlemen. To quote but one example, in terms of quality, signal strength and generally intelligent operating, newcomers to VHF NFD might well emulate the example of G8APH/P, operating from north of Winchester, who was doing all the right things. Surely, the time has now come to do something more positive about disqualifying persistent offenders. To rely upon other operators writing in to complain, is but to scratch at the problem, and it is suggested that a team of impartial, voluntary adjudicators, located strategically around the

country for the specific purpose of monitoring the bands for poor transmissions, and with the power to recommend immediate disqualification in flagrant cases, would be much more effective. They need not be members of the Contest Committee, and cross-checking their reports would provide a safeguard if anyone wished to question their probity.

So there it is until next year.

#### Contests

Conditions were very patchy for the 70 MHz contest on August 15. and appear to have been rather more reliable and productive of DX in the North and Midlands than in the South, although even there, propagation tailed off considerably towards the end. G3OHH and G3RLE, to quote but two stations who normally do pretty well in these events, were passing scores of 35 and 26 respectively at the finish and your scribe could only manage 25, possibly due in part at least to the systemic shock of having to get up in what appeared to be the middle of the night to be in on the GC3WMR/P was a good start! signal in the South and up into the Midlands for the first couple of hours or so, and then was never heard again, although G3TTG/P in Cornwall was there most of the G3UVR/P was located in Cardigan, but in spite of his attractive location only worked G3TTG/P and G3ZVK in Kidderminster. Checking around afterwards, it seemed that the choice of the timing was not particularly welcomed by many operators with TVI problems and/or large, local, immigrant populations and University-of-the-Air students, since they were unable to transmit during the time these programmes were being radiated on Sunday morning. There still seems to be a good case for the longer contest, rather than the abbreviated five hours of this event, taking in a large part of the time between midnight and say nine in the morning. It's only two or three times a year, after all. However, as G3DAH knows from personal experience of organising these events, you can't please all the people all of the time, and indeed very few for even part of the time!

Forthcoming events are the UHF/

SHF contests over the weekend of October 2/3, which coincide with a similar IARU Region I event; the first of the 70 MHz Cumulatives on October 13 and 27; and the 432 MHz fixed contest over the weekend October 30/31.

#### Meteor Scatter

Many two-metre operators must have heard the 30 w.p.m. CW at the low end of the band recently, and even if they have not been able to hear the other end of the contact, may have deciphered the call as being that of Johnny Stace, G3CCH (Scunthorpe, Lincs.), in contact with

TF3EA, with whom he has been running random meteor skeds on Thursday evenings between 2100z and 2130z. To date, they have had 23 OSO's, and this has encouraged them to have a go at M/S on 432 At present, only G3CCH transmits, and TF3EA listens. Several "pings" have been heard in Iceland, with occasional, barely perceptible, signals of much longer However, efforts are duration. being made to improve the circuit with bigger and better aerials and higher power. The skeds are on Saturday evenings between 2000z and 2100z at the bottom end of the

# THREE BAND ANNUAL VHF TABLE January to December, 1971

Station	FOUR Counties	METRES Countries	TWO I	METRES Countries	70 CENT Counties	IMETRES Countries	TOTAL pts.
G3COJ	34	4	63	16	29	7	153
G3OHH	47	7	55	5	24	3	141
G3DAH	31	3	58	12	25	5	134
G5DF	17	2	55	11	29	5	119
G3ZYC	41	4	26	5	33	7	116
GD2HDZ	23	4	48	8	19	4	106
G8ATS	_	_	45	8	39	5	97
G3JXN	27	2	57	9		_	95
G3ZPZ		_	78	13	_		91
G8BCA	_		49	6	31	4	90
G2AXI	24	3	39	4	8	2	80
G3EKP	22	6	19	5	6	6	64
G3FIJ	4	1	44	8	5	2	64
G2JF	_	_	51	9	_	_	60
G3IAR	31	3	21	4	_	_	59
EI6AS	15	5	30	6	1	1	58
G8BKR	_		41	5	10	2	58
G8ECK	_	-	46	9	_	_	55
G8BWW	<u> </u>	_	32	5	6	4	47
G8CBU	_	_	36	5	3	1	45
G8DLJ			32	8		_	40
G8AUN	_	-	30	3	3	2	38
G8CVD	_	_	32	5	_	_	37
GM3EOJ		_	18	10	3	1	32
PA9LY	_	-	13	6	_	_	19
G8CYN	<u> </u>	_	13	2	<u> </u>		15

Just a reminder that the Tables go through to December 31st, 1971. The Three Band Annual Tables show claims to date for the year commencing January 1st, 1971. Claims should be sent to Short Wave Magazine, Buckingham, Bucks.

hand

Far from random was Johnny's two-metre QSO with LZ1BW during the *Perseids* shower on August 12/13, a carefully planned and executed operation which resulted in a 2230 km contact to give 'CCH (and probably LZ1BW) his best DX to date.

Fine achievement though this can be seen to be, it is perhaps all the more praise-worthy, since Johnny does not have access to the vast laboratories available to some amateurs, and is not engaged professionally in radio. His gear is home-designed and constructed. One recalls an article of his which appeared in the *Magazine* many years ago, in which he described the construction of a dish for E-M-E working. So, congratulations.

And in another area of Europe, EA4AO of Madrid, well-known to many M/S operators in this country, also got in on the *Perseids* shower. After a phone call from PAØVVH, skeds were arranged for 0900z to 1100z on 144-150 MHz over the period, and on the 13th, a QSO resulted within 60 minutes with good signals both ways and long bursts. At the conclusion of the contact, PAØJMV came on the frequency, and signal strengths of 7 & 8 were exchanged, and this without a previously arranged sked.

To give some idea of the gear required to participate in this particular form of communication, PAØVVH runs 100 watts from a QQV06-40A to a ten-ele Yagi; PAØJMV has 600 watts input to a 4X150A and an 18-ele long-Yagi; EA4AO has 500 watts output from a pair of 4CX250's into a 10-ele Yagi.

#### Beacons

GB3SX is still off the air at the time of writing, but it is hoped to have it on again very shortly. The trouble appears to have been that the power increase to 120 watts (to an 829B) and an increase in the ambient temperature, caused it to give up the ghost.

Permission has now been granted for the installation of a new beacon in Lerwick on a frequency of 50·1 MHz with the object of promoting the study of auroral and sporadic-E effects. The Tx will be transistorised and is of the same general form as



On a recent Verulam (St. Albans) Club occasion se see, left to right: G8BJK, G3DAH, PAØLSC, G3COJ and G3POI. G3COJ is well-known on VHF and he and G3POI work PAØLSC regularly, the latter's father being PAØCSL, also very active on the VHF bands.

the TF3EA job, both the brain children of G3JVL. Although not in the amateur frequency allocation, this beacon will provide a useful guide to propagation on 70 MHz.

Happily, the Wrotham 2m, beacon is back in form, although the transmission cycle now omits the long dash, and lining up converters still remains a problem if this transmission is used in lieu of a signal generator. GB3GEC on 70 cm. is still off the air, and likely to remain so for some time, if not indefinitely, which deprives not only the U.K. amateur of a very useful service, but also the many Continental stations who used the beacon as an indicator of propagation in the U.K. direction. So valuable was this beacon to them, that its presence was given as one of the reasons for setting-up the Dutch beacon. PAØVD. True, the new installation at Durham, when it becomes operative, will partly fill this gap, although the proposed antenna headings are not particularly favourable for Continental Europe. Even better would be the installation of a 70 cm. beacon at, say, the site of the projected 23 cm. job at Shooters Hill in Kent, to radiate medium power from an omni-directional antenna. A further beacon in the South-West, beaming North-East, would, with GB3SC, then complete the coverage very satisfactorily. The case has obviously been made for such a system on 2m., and presumably, the arguments are equally

applicable to the higher frequency band, if not more so, in view of the lower levels of activity on 432 MHz.

Further to the information given last month re the new French beacon. F7THF, installed at "Ballon d'Alsace" in QRA DH75, the complete cycle is as follows:-(1) The start signal consisting of a musical tone, (2) The call letters in - A2, (3) The temperature in degrees Celsius, defined by one pip for each degree, preceded by a long dash if the figure is below zero, (4) The local pressure in millibars with a pip for each millibar above 950 and up to 1,000. (The low starting point is dictated by the fact that the site is at 1520m. a.s.l.), (5) A 1,000 Hz note for tuning purposes, (6) A 600 Hz note for tuning purposes, but this time on NBFM with a deviation of 1.5 kHz, (7) A report on reception of "Checkpoint Charlie" just below the band edge, and in QRA DK63j, with nine pips indicating excellent reception, and a lesser number for lower states, (8) A report on the amount of sunshine on site, but this is unlikely to interest us very much!

Plans are in hand to duplicate this beacon information on 70 cm. Reports will be welcomed by Radio Club de Belfort, 7 rue de la Claichiere, 90, Bavilliers, France.

Reception in this country of the German beacon on 70 cm., DL7HGA in Berlin, has yet to be confirmed, although it has been heard out as far as 300 km. in Germany itself.

It appears to be a remarkably stable device, as frequency measurements over last few months have shown it to have varied by as little as 30 Hz about the allotted frequency of 433.485 MHz. This is, unlike the beacons in this country, a venture" installation. "nrivate operated by DL7HG, who has to accede to requests to switch it off when weak DX is around the frequency, in order to keep the peace with his neighbouring amateurs, and in this respect, it operates at a disadvantage compared remotely and officially controlled beacon transmitters, but nevertheless, it can still be a useful, if not permanent, aid to the determination of propagation conditions on 70 cm. Reception reports would welcomed by Peter Brumm. Berlin 37, Claszeile 23,

It is reported that a new German beacon has been set up 20 miles NE of Hamburg. Callsign DJ8XOA, and frequency 432·0 mHz.

#### VHFCC Awards

Only one claim has been received this month for the VHFCC Award. This came from Geoff Monks. G8ENL (Horsforth, Leeds) who gains Certificate No. 111 for two Geoff is obviously no metres slouch, since he was first licensed in January 1971, and has now worked 800+ stations in 38 counties and 8 countries. He runs a QQV06-40A in the PA with 40 watts of NBFM to a 10-ele Yagi at 30ft. a.g.l. on a site 550ft, a.s.l. The converter is a DL6SW and the main receiver an SP600JX.

#### Club and Society Activity

G3ZKH sends some details of the operations of the White Rose Radio Society which has been giving a good account of itself under the callsign G3XEP/P during recent contests. They normally use a site some 950ft. a.s.l. 15 km. north of Leeds, which has a clear take-off in all directions except to the West, where a little affair called the Pennines intervenes. The Tx runs between 25 and 35 watts on two metres to one, or two, 10-ele Skybeams, and on occasions, to a 14-ele Parabeam. Main receivers are either an EC-10 or a Trio JR-500SE, with alternatively a Mosfet converter or a nuvistor job. On 4m., they have

10 watts with a 6-ele beam. One has the feeling that we will hear a lot more of them in the not too distant future.

The Reading Amateur Radio Club held their VHF picnic again in July, with talk-in stations, junk sale and raffle, and it is hoped that this will become an annual event. This sounds a congenial occasion which Club secretaries may wish to investigate further, in which case they should contact G3NBU, QTHR, for further details. The South Bucks. Club, whose meetings are regularly reported in this Column. have arranged a talk on UHF equipment by Arnold Mynett G3HBW, for October 5, and a film on transistors on November 3. Details of these and other meetings may be obtained from the Secretary. G3XPB, OTHR.

Another activity which has much to commend it for those who like a day in the country is a foxhunt, and yet this does not seem to have achieved the same popularity in this country as it has on the Continent. The Ovingham & District Society Amateur Radio Northumberland held theirs August 1, with the fox at Mootlaw, 832ft, a.s.l. and the winner, G4LA, took just over the hour to find him. The point about these contests is that they can be shared with the family, and XYL ORM is therefore less likely than with a fixed station Michael Stott, G8BGU, event

organised this one, and Club secretaries might like to contact him, QTHR, to get further details of the organisation behind it.

The South East UHF/VHF Group meets at Wye College, University of London, nr. Ashford, Kent, on October 15 at 7.30 p.m., when Arnold Mynett, G3HBW, will be talking about VHF transceivers. Details of this and subsequent meetings may be obtained from the secretary, G3DAH, *QTHR*.

The "Radelec 71" jamboree, (if that is the right word for this particular aspect of Scouting activity) takes place over the weekend of October 1/2 at Gilwell Park near Chingford, Essex, easily reached by train from Liverpool Street station or by road. Talks on ultrasonics, tape recording, RTTY and antennae have been arranged, and all Scouts with an interest in Amateur Radio are welcome. If as many turn up as last year, there should be some 100 there. Further details from G8CBU, OTHR.

#### Four-Metre News

Nothing further seems to have been heard from TF3EA or TF3VHF on 4m. since the sporadic-E openings reported last month, except for a brief appearance on M/S on August 11 when the Manchester station, G3VSA, heard quite long bursts, although no contact was made at that time.

G3VPK logged ZB2VHF on 70.26



The legendary Cairn O' Mount site in Aberdeenshire has been used by many VHF/P expeditions. On the Aberdeenskincardine border, the elevation is 1,488ft. GM3DAH/M found it a wonderful spot when on a holiday trip up there.

MHz at 2100z on August 7, but as this date coincided with the latest Apollo splashdown TV pictures, perhaps many of us missed the opening! G30HH reports hearing the station on August 21 between 1938z and 1944z, but signals were very weak. All in all, the openings to ZB2 have been very poor this year—perhaps some of the experts can offer a credible explanation?

G3FDW, one of the star operators on the 4-metre band, is moving OTH within the Nottingham area. and will be QRT until December. G3WOS of Rugby is now to be heard on 4m. on SSB. He runs a FET VFO and OOV06-40A PA: he is planning an all-mode set-up to give him A1, A3, F3 and A3J: the antenna is a 4-ele at 33ft, a.g.l., but a 25-ele (!) with a calculated gain of 13+ dB is planned for contest working. He is also building for 432 MHz. Heard on 4m. recently: An operator with a severe case of the "RF feedbacks" in QSO with another station who reported that the feedback was much worse on 70.36 MHz than it was on 70.26 MHz. Some feedback-the carrier was on 70:47 MHz!

# Two-Metre and 70 Cm. News

A newish signal from the South-West-and the Lizard is about as far South-West as one can get in this country without going to the Scillies-comes from G3IUD, who is to be heard most evenings on CW around 144.03 MHz. He is a refugee from Wilmslow in Cheshire, from whence he transmitted on all bands from 4m. to 3 cm. currently has 120 watts to an 8-ele beam. He has a nightly sked with G2JT in Oldham, and they rarely seem to miss. He can also be heard working G3DAH most evenings when conditions are right, at 2320z. He is planning to come back on to four metres again soon.

G8BMI of Keighley, Yorks, is now equipped for teletype reception. Moving QTH has held up further progress in this direction, since it has involved the fabrication of a special console for all the gear. He is to be heard on 2m. AM though. Brian Flynn, GM3BJF, well-known on 70 cm. in Edinburgh, is to be congratulated on his B.Sc., (Hons.) degree; he is staying on at the University to take his Ph.D.



Left to right: G3ZGR, G4LA and G8AGN, winners in a recent fox-hunt on two metres organised by the Ovingham (Northumberland) Amateur Radio Club. The Tx frequency was 145.1 MHz and G4LA got there first.

When GM8BRS was portable in South West Scotland recently, they had a good contact with GD2HDZ, Laxey, I.o.M. to give the latter his first GM on 70 cm. The Tx ran 100 watts, and 30 watts on two metres.

#### News Items

The live A/TV demonstration at Woburn Rally attracted the attention of many visitors, and the following details may be of interest: G6AFK/T and G6AGE/T, with vocal assistance from G8CBU, looked after the transmission side from the car park Dunstable Downs, G6AEV/T and G6AGX/T were in the marquee at the rally. transmitting equipment consisted of a hybrid Tx winding up with ten watts input and a 18-ele Parabeam at 16ft. a.g.l. (the site was 800ft. a.s.l.!), the home-built camera equipment having been constructed by G6AFK/T-see p.369, September SHORT WAVE MAGAZINE. At Woburn, a transistor TV tuner. suitably pulled to 70 cm., fed into an ex-rental TV set, with the antenna an 18-ele Parabeam on a Strumech tower up at 60ft. Both sound and vision were transmitted in the 70 cm. band with 3.5 MHz spacing, and very good noise-free pictures were received during the two-hour long programme.

G8BCL, Halifax, Yorks, is looking for contacts on 23 cm. He has a xtal-controlled Tx on 1297 MHz

with a 2C39 tripler/PA giving 5-6 watts out to the 32 ele Yagi. At least, it should have been a 32-ele Yagi, but Howard says that an extra director crep' in by mistake. and it is now a 33-ele job! The converter is the K6KXN model. Skeds can be arranged (OTHR, with s.a.e.). Incidentally, many listeners will have heard the early-morning skeds between G8BCL and G5DF in Reading, around 0900 hrs. local time on two metres. These have been running since April 1 this year. and they have never missed due to propagation conditions over this 170-mile path.

Some interesting DX is reported by EA4AO in Madrid. During the recent 2m. contest in Spain, contacts were made with Palma de Mallorca over a distance of 2150 km. The Canary group were up at 2,200 metres and were running a OOV03-12 in the final, so this looks like a spot of Es. They were using an abbreviated form of procedure, with just the last letters of the call, and this caused some amateurs, who were copying them at 5 & 9, to think that it was the local police net breaking through. (There must be a lesson to be learned here about using callsigns correctly.) EA4AO makes the point that these sort of conditions are possibly more prevalent than is imagined, and it can only be regretted that there is often insufficient activity to pinpoint them. We could do with a bit of this

propagation at this latitude!

Dave Stockley, G8ELP (Whitstable, Kent) was involved in a nasty car smash recently, but this has not prevented him from coming on the two-metre air from his hospital bed. The local lads have fitted him up with an NBFM Tx/Rx and a halo antenna (of which both the matron and the visiting Padre approve!) and he is thus able to while away the long weeks by keeping in touch with the outside world via Amateur Radio.

Alan Wheeler, G3RHF was also laid low in hospital at the end of last month, and was able to get on 2m. with the help of an Echelcom-2 Tx and a Rx designed and built by G8EDL, Derek Holding. Once again, the antenna was a halo, although the best antenna for general listening purposes turned out to be the hospital earth system!

We wish a speedy recovery to them both.

#### Ernie Dedman-G2NH

It is with deep regret that we have

to announce the sudden death, at the age of 57, of Ernie Dedman, G2NH. of New Malden, Surrey. It was immediately after his return from the VHF/NFD site on Sunday. September 5, that this unhappy event occurred, and one cannot help thinking that this might be the way that Ernie himself would have wished it. First licensed in 1927, he has always taken a full and active part in amateur activities on all bands, from HF, through 5 metres, to VHF, and will be remembered by many, who did not have the fortune to know him personally, as the moving spirit behind the Quartz Crystal Company. which in the 1930's must have provided most of the "rocks" for the amateur fraternity. While not neglecting the HF bands, his recent interest had centred on two-metre SSB, and he was to be heard on the air most Monday evenings either working the DX or ready with helpful advice for the newcomerhe was by no means just a "5 & 9pse OSL" man. The sympathy of so many of us goes to his family.

#### Deadline

Deadline for the next issue is October 9 and the address for news, views, claims and comment is: "VHF Bands", SHORT WAVE MAGAZINE, BUCKINGHAM. Cheers for now, and 73 de G3DAH.

#### Stop Press

The results of the 1969 IARU Region I Contest in September of that year have now been issued officially by the Czech authorities. U.K. placings are as follows:

144 MHz Fixed: 3rd G2JF, 360th G8BWF.

144 MHz Portable: 23rd GD3VXK /P, 40th GW3BA/P, 63rd GM3TGL/P, 145th G3FZL/P.

432 MHz Fixed: No U.K. entry. 432 MHz Portable: 1st GW3HAZ/P, 3rd GD3WMS/P.

1296 MHz Fixed: No U.K. entry. 1296 MHz Portable: 2nd GW3HAZ /P.

#### ADDRESSES FOR RECIPROCAL LICENSING

Following is the latest Region I IARU list for applications for reciprocal licences in the countries named, covering also /M permits (where these are allowed to foreigners). Short-term licences are usually free or are issued at nominal cost. In most European countries Top Band is not permitted. In the first instance, make a straightforward typed request with a photostat copy of your licence—and allow ample time for the business to go through.

Austria: Generaldirektion der Post und Telegraphenverwaltung, Abt. 15F (Funk), Vienna (or the capital city of the province of residence).

Belgium: Monsieur le Directeur-Général des Radiocommunications de la RTT, Place Madou 1, B-1030, Bruxelles.

Eire: Dept. of Posts & Telegraphs, Experimental Radio Section, Hamman Buildings, O'Connell Street, Dublin.

Finland: Suomen Radioamatooriliitto r.y., P.O. Box 10316, Helsinki 10.

France: P.T.T., Direction des Services Radio Electriques, 5 Rue Froidevaux, F-75, Paris XIV. (Also for Andorra.) Luxembourg: Administration des P. & T., Hotel des Postes, Luxembourg-Ville.

Netherlands: Radio Controledienst P.T.T., Kortenaer-kade 12, The Hague.

Norway: Teledirektoratet, Universitetsgt. 2, Oslo, 1.

Portugal: Administracao General dos C.T.T., Direcçao dos Servicos Radioeletricos, 1A Reparticao, Rua General Sinel de Cordes 9-5°, Lisboa 1.


Sweden: Central Administration of Swedish Telecommunications, Radio Development Section, S-123 86 Farsta.

Switzerland: Generaldirektion P.T.T., Radio und Ferneshabteilung, CH-3000, Berne.


United Kingdom: Ministry of Posts & Telecommunications, Amateur Licensing Branch, T & RRD, Waterloo Bridge House, Waterloo Bridge Road, London, S.E.1.

United States: Federal Communications Commission, Washington, D.C.

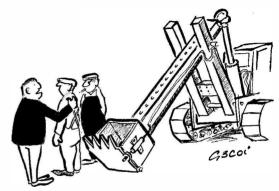The U.K. address is given for the convenience of overseas amateurs who may wish to operate in this country. The U.S.A. is not in Region I, but is included for completeness.



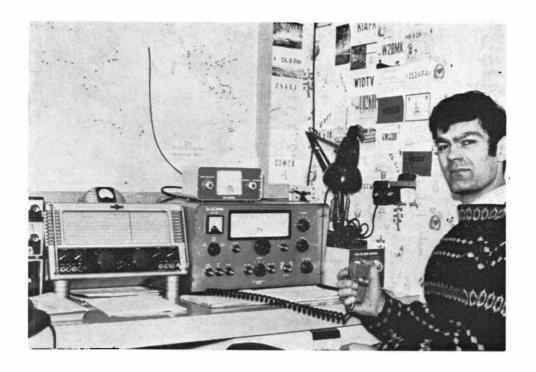"... Come over here and I'll show you where to dig out for the radials ..."



# THE OTHER MAN'S STATION

**G3YWS** 

J. M. SMITH, 16 Woodlands, Winthorpe, Newark, Notts., put G3YWS on the air in November 1969—though in fact he became interested in Amateur Radio fifteen years ago, while still at school. The force of various circumstances—such as working for professional qualifications (he is a lecturer at Newark Technical College), and marriage—held up a serious approach until some years later.

He is now in a house-and-garden carefully chosen with Amateur Radio in view, enabling him to have a good aerial system in a quiet location—antennae consist of a Mosley TA-33Jr., a 132-ft. wire and a 5-ele beam for two metres.

Gear at present in use is, as HF-band Tx, a K.W. Viceroy for CW/SSB operation, an Eddystone 888A as main receiver, a Codar A.T.5 for Top Band and a small two-metre Tx modulated and powered by the A.T.5, with the appropriate 144-146 MHz converter for reception.

Thus, operation from G3YWS is possible on all bands two metres to 160m., with the main interest DX working on 21 MHz. The score at the moment stands at 154C, with 84 countries confirmed.

Activity on two metres was started comparatively recently, in order to join in with the locals who, we are told, use that band extensively—but VHF/DX is also being raised, thanks to an excellent QTH.

Latterly, G3YWS has been busy setting up G3ZWV, the recently-licensed AT-station at the Technical College, with a KW-2000 transceiver and the ancillaries. It is hoped in due time to institute a course for the R,A,E.

Finally, he remarks that he "has a very tolerant XYL and a 2½-year-old junior op. who could say 'CQ' before he could say 'Daddy' "! Well, we don't know . . .!

But we would remark that the operator of G3YWS, now just 31 years of age and with plenty of time in prospect, strikes us as one of those radio amateurs who have made a rational step-by-step approach to Amateur Radio—we wish him and his family well for the years to come.

#### APOLOGY FOR ERROR

In that caption on p.275 of the July issue, we in-advertently described the spark Tx as being an "R.A.F.-type of 1916 vintage"—of course, it should have been R.F.C., because the R.A.F. did not exist at that time. Also, it should have been mentioned that the Tx itself is a replica in full working order built by W4ZM to the original Sterling Radio specification, for the Antique Wireless Association, who have a remarkable collection of early radio apparatus.

# THE MONTH WITH THE CLUBS

# By "Club Secretary"

(Deadline for November issue: October 8)

(Please address all reports for this feature to "Club Secretary," SHORT WAVE MAGAZINE, Buckingham.)

ONCE again the merry-go-round starts to spin, covering reports from Clubs far and wide—and most of them seem to be preparing to do battle in MCC, Rules for which appear herewith. Suffice it to say that while they are basically the same as last year, the formula having met with general approval, the Ident. Codes are different. Thus, if you make a last-minute decision to run a station, it is no good, and can do positive harm, to operate using last year's Ident. Yes, we know it sounds a bit odd—but it has happened!

For more than 25 years now, MCC has been the annual competitive event for Clubs who are really on the air, and have enough CW operators to put in an entry.

This is what makes the interest in MCC—and the fact that your Club is competing primarily with the others in your own Zone. In addition to the main placelist, we also show the first two in each Zone, these being the lead stations in their own area; see p.688, January 1971 SHORT WAVE MAGAZINE for the local Club situation last year.

Also to be remarked here—as has been explained in previous years—the Contest is closely invigilated. This is *not* with the idea of looking for people to disqualify but rather to make sure that all concerned play to the Rules—see, in particular, Rule 8, p.497, which will be strictly enforced. What we do *not* want to hear are loud-and-dirty noises from over-driven transceivers!

All necessary information for making an entry is given herewith. Any Club omitted from the Identification Code list (and there can't be many!) should let us know forthwith ("Club Secretary", SHORT WAVE MAGAZINE, BUCKINGHAM) so that if necessary a supplementary Ident. Code list can be published next month—though we are hoping that this year it will not be required and that there will be no last-minute panics about getting a code.

#### FULL DETAILS FOR MCC

Appear in this issue. Rules are much as last year but Identification Codes are changed. Any Club not included and wanting a code should write in straight away. Dates for the event are November 6/7, and the report and results will appear in the January issue.

#### The Reports

Straight down this time, for a change from the Regional approach of recent months.

Midland appear at the top of the pile; they have their being in the Midland Institute, Margaret Street, Birmingham, 3. In the calendar for October we notice Tuesdays are the ones—October 1 for an extra Natter session, and the 19th for the Annual General Meeting.

Thames Valley are booked in at the "Three Pigeons," Portsmouth Road, Long Ditton, on the first Wednesday of every month; October's evening will be devoted to modifying for 70 and 144 MHz a certain popular type of business-radio equipment, both from a theoretical and a practical point of view.

Up at North Notts, the lads are having an "odd day" extra this time, visiting Newark Club to meet Fred Ward, G2CVV. Normal sessions are on Thursday, and October 7 is particularly noted for a "Forum," with experts to answer any question you care to throw them. For the venue, and any other details, contact G3OZN, as Panel p.498.

The Richmond Terrace buildings of Brighton Technical College will soon be ringing with radio amateur noises when the lads have their fortnightly sessions, and maybe put G3TCB on the air. Any interested folk who would like to visit or join, should get in touch with G2CMH at the address in the Panel for details and dates.

Sad to say, **Bristol** will be losing their Secretary, G3RKH at the end of September, which means a special farewell evening in the skittle-alley of the Ship Inn, Redcliffe, on September 30. Then the normal meetings at 41 Ducie Road, Barton Hill, Bristol, must still go on; there is a Film Show on October 14, and the AGM to be dealt with on October 28.

Hq. for the **Hereford** chaps is at the County Control, Civil Defence Headquarters, Goal Street, Hereford; they are here on October 1 for a talk and demonstration by Geoff Tibbetts, G3NUE, of Worcester, "by radio and land-line." Then on October 15, there is the last trip for this year working /P on 144 MHz, weather, of course, permitting—it it doesn't then it is back to Hq. to operate from there.

A change of venue is afoot for the White Rose lads, who apparently have found themselves an old house to be converted into a permanent home; this probably means that the main interest for the next few months will be in paint-pots and brushes! Because of this, it is suggested that if you want the latest information you contact G3YEE, as Panel.

October 7 is the date for **South Birmingham**, and a most important date at that, because it is the AGM. This will be dealt with at Hampstead House, Fairfax Road, West Heath, Birmingham, starting at 8.0 p.m. sharp.

Unfortunately, Worcester's calendar, printed in the

copy of the *Newsletter* to hand, stops at the end of September; but from it we learn that the venue is the Crown, Broad Street, and the meeting is set on a Saturday evening. For the rest, we must refer you to the hon. secretary—see Panel overleaf.

For **Bedford**, in their place in the Dolphin, Broadway, October seems a full month; on the 7th, Joe Farley is to give a scientific lecture, and on the 14th G3RFG takes the floor to tell all about his Multi-band vertical aerial. This takes us to October 21, and G4AHE, whose theme will be the development of trends in receiver design using Integrated Circuits. Finally, there is the Annual General Meeting on October 28.

'Tis quite a while since last we heard noises from Otley, but they are loud and clear this month, and sound as though they are thriving. They have an Annual Open Night on October 26, with a trade stand, visitors welcome from 7.30 p.m. onwards, and refreshments available, at the Club premises, 14 Back of Court House Street, Otley.

Spen Valley seem to be away more than at home in October! On the 7th, there is to be an evening of music, put on by Richard Allen Radio, Ltd., followed by a visit to Basinghall telephone exchange on the 14th; they also have a look round the Yorkshire Post Newspapers Ltd. set-up, starting at 7.0 p.m. The home meetings are always at the Grammar School, High Street, Heckmondwike.

Thursdays it is for **Redditch**, at the Old People's Centre, Park Road. This month sees the October 14 date filled by a talk by G3HZG, who used to be better-known at VR2FT on Fiji, his topic being life in that DX-otic spot, illustrated by slides. Then there is October 28, when the club's own HW-100 will be in action for a night-on-the-air.

At Marle Place, Leylands Road, Burgess Hill, you can find the Mid-Sussex lads twice each month. For October, it rather looks like the second and fourth Thursday by extrapolating from the calendar given for the earlier months in the *Newsletters* to hand; however, it would probably be a good idea to check with the hon. secretary, address as Panel, p.498.

Wirral are now safely into their new place at the Drill Hall, Grange Road West, Birkenhead, where on October 6 they have the Annual General Meeting, followed by a film show on the 20th.

There is a clubroom built on to the back of the "Jack o' Newbury" pub at Binfield, just outside Bracknell, and this is the place to find the Bracknell boys on the second and fourth Mondays in each month. From the way he wrote, it is rather gathered the scribe has been hustled into the job at the march of events, so at this stage he could not advise of the programme; but like most groups, they no doubt have something laid on.

Chippenham have been assembling every week at the Boys' High School, Hardenhuish Lane, for years now; any Tuesday you can find them there. For October, the particular high spots are the Rowde Hamfest on October 5, with talk-in on Top Band to the George and Dragon, Rowde, near Devizes. Kick-off at 8.0 p.m. and refreshments will be available at modest charges—all, of course, welcome. The other event is the film show,

# MCC—TWENTY-SIXTH ANNUAL TOP BAND CLUB TRANSMITTING CONTEST

#### RULES

- 1. *Duration:* Saturday, November 6, and Sunday, November 7; on both days between the hours of 1700 and 2100 GMT (eight operating hours in all).
- Frequency and Power: All contacts to be made in the 1800-2000 kHz band, using CW, with a power input not exceeding ten watts to the final stage.
- 3. Call-Signs: Where a Club has its own call-sign, that is to be used; if no club call-sign is held, the call of a nominated member may be used.
- 4. Scoring: Other Club stations may be worked once in each session, the contacts counting three points each time. Non-club stations may be worked once in each session, to count for one point each time.
- Contest Exchanges: Inter-Club contacts will take the form of an exchange of RST plus the allocated Club Ident. Code. (See p.500). Nonclub contacts to be an exchange of RST and QTH.
- 6. Logs: The contest logs are to be legibly set out as follows: One side only of quarto or foolscap sheets should be ruled into nine columns, with the Club name and call-sign on every sheet. Col. 1, Date and Time; Col. 2, Call of station worked; Col. 3, Outgoing exchange; Col. 4, Incoming exchange; Col. 5, Outgoing RST (non-club); Col. 6, Incoming RST (non-club). Col. 7, QTH of non-club station. Col. 8, QSO Points, Col. 9, Points claimed after multiplier applied.
- 7. Final Tabulation: To each Club contact, apply the correct Zone multiplier. To each non-club contact, regardless of distance, apply a multiplier of ten. Total the points claimed after multiplying to obtain final score. This, together with a declaration that the station was operated within the rules and spirit of the Contest, and comments on the Rules, equipment used, experiences, and so on, should be on the front sheet of the entry (Multiplier table on p.501).
- 8. Disqualification: This is at the discretion of the invigilators, and reasons will be given. Typically, disqualification could result from a consistently rough signal, deliberate interference with other stations, over-driving of a transceiver producing strong key-clicks or a spread of spurii, unnecessarily long CQ calls or abbreviated callsigns.
- Contest Call: Call "CQ MCC" only. Shortened c/s must not be used.
- 10. Entries: Logs, addressed to "Club Secretary", SHORT WAVE MAGAZINE, BUCKINGHAM, must be posted to arrive not later than Friday, November 19. Results will appear in the January 1972 issue of SHORT WAVE MAGAZINE, due out on December 31. The Editor's decision is final on all matters affecting the Contest.

at Hq., to be presented on October 26 by G8BXG.

A new Hq. is the gist of the Clacton report; it seems they have a fine place with the Sea Scouts in Sadds Yard, Skelmersdale Road, which is about 100 yards from the main railway station. It is a year since they re-formed, and members now total 41—which is pretty healthy

progress. All are asked to take particular note of the date for the AGM: October 12, at Hu., starting at 1930 promptly.

Bristol Shirehampton's secretary writes in from Polperro to say that the summer break for the Club ends after September, and from then it will be "business as usual." G35XY should be home by the time you read this, so contact him for all the doings—see Panel.

At Torbay we are specially asked to announce that the meeting of October 30 is to be a Junk Sale and Extra-Ordinary Meeting, so please make a special effort to be there.

The RAIBC Radial for this month carries a good article on his North American trip by G5CP, and an interesting exposition of the help the Club can give, through the "supporters," to the blind and invalid full members, particularly in relation to the question of how much it really means to them.

Saltash has to cancel their proposed Mobile Rally of September 5, but are still going—and going strongly, at that—on alternate Fridays at Burraton Toc-H. Details of the talks are not, at the time of writing, firm, but we are assured that there will be something definite fixed up.

Derby can be found on Wednesday evenings at Room 4, 119 Green Lane, as well as at other times for different activities. October, for example, mentions a

UHF/SHF NFD: October 6, for a junk sale, and the 13th for film show. A Natter Night on the 20th is followed by the monthly VHF group meeting; then on the 24th there is a D/F contest with a trophy to be won. All this leads us to October 27, when there will be a Hi-Fi demonstration. Every month seems to be as busy as this!

**BEA** have now formed their own Amateur Radio Club, with Hg, at the BEA Training Centre, Heston, on the last Wednesday in each month—but if you want to visit, please contact G3OUF first—his address and phone are in the Panel. Moves are also afoot to set up a permanent Club station at Northolt, at the BEA Trident Club there.

At Wolverhampton the lads have Neachells Cottage, Stockwell End. Tettenhall, for an Hg., where they can be found on Mondays. A particular date to be noticed is October 4, when the AGM is taken.

Yeovil are pleased to report a couple of their lads have obtained licences; members can be found assembled at the Youth Centre, 31 Park Lodge, any Thursday, we understand.

One always notices the distinctive colour-scheme of the cover of the Cornish Newsletter, and there is usually something interesting inside, this month being no exception. The main meeting is at the SWEB Clubroom, Pool, Camborne, on the first Thursday in the month. However, at this time we do not have any details of the

NORTH NOTTS: E. W. Badger, G3OZN, 20 Tennyson Drive,

#### Names and Addresses of Club Secretaries reporting in this issue:

ACTON, BRENTFORD & CHISWICK: W. G. Dyer, G3GEH, 188 Gunnersbury Avenue, London, W3-8LB.
BASINGSTOKE: P. Sterry, G3CBU, Ashley, Orchard Road, Salisbury Gardens, Basingstoke.
BEDFORD: J. Bennett, G3FWA, 47 Ibbett Close, Kempston (2022). Bedford. BEDFORD: J. Bennett, G3PWA, 4/ IDDEIT CLOSE, NELLIPSION (2427), Bedford.

BICESTER: T. Shaw, G8EWS, 5 Langford Gardens, Bicester. BRACKNELL: S. Jewell, G8EMY, 108 Highfield Park, Wargrave (2800), Reading, Berks.

BRIGHTON (Technical College): R. J. Henley, G2CMH, 35 Wilmington Way, Brighton, BN1-8TH, Sussex.

BRISTOL: R. W. Thompson, G3TKF, Stapledown, Hill Drive, Failand Bristol BRISTOL: R. W. Inompson, USIKF, Staptedown, Am. 2010., Failand, Bristol.
BRISTOL (Shirehampton): E. J. Davis, G3SXY, 72 North View, Westbury Park, Bristol (33284), B86-7PZ.
BRISTOL (University): C. Elliott, G8ADP, 37 Seymour Road, Bristol (421864), BS7-9HS.
CAMBRIDGE (University): D. Field, G3XTT, Selwyn College, Cambridge Cambridge.

CHELTENHAM: E. Janes, G2FWA, Hillside, Bushcombe Lane, Woodmancote, Cheltenham (Bishops Cleeve 2229).

CHIPPENHAM: P. J. Tuck, 186 St. Edith's Marsh, Bromham (274), Chippenham, Wilts.

CLACTON: T. Mills, G3YAI, 75 Lymington Avenue, Clactonon-Sea (21664), CO15-4PL, Essex.

CORNISH: J. Farrar, G3UCQ, Elm Cottage, Ventonleague, Hayle, Cornwall. COVENTRY: C. Jaynes, 20 Belgrave Road, Wyken, Coventry, Warks.
CRAY VALLEY: P. Vella, G3WVP, 78 Hurst Road, Sidcup.
CRYSTAL PALACE: G. M. C. Stone, G3FZL, 11 Liphook
Crescent, London, SE23-3BM (01-699 6940).
DERBY: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover,
Derby (21931), DE3-7GE.
ECHELFORD: R. Hewes, G3TDR, 24 Brightside Avenue,
Laleham-on-Thames (Staines 56513), Middlesex.
HEREFORD: S. Jesson, 181 Kings Acre Road, Hereford.
HULL: Mrs. M. Longson, 4 Chester Road, Hull, HU5-5QE.
MANSFIELD: F. N. F. Bewley, G8HX, 116 Westfield Lane,
Mansfield (25208), Notts.
MIDLAND: N. Gutteridge, G8BHE, 68 Max Road, Quinton,
Birmingham, 32. Birmingham, 32.

MID-SUSSEX: E. J. Letts, G3RXJ, 87 Meadow Lane, Burgess Hill (3552), Sussex.

NIGERIAN: E. A. Lomax, 5N2ABG, P.O. Box 68, Kaduna, Nigeria.
NORTH KENT: L. Randall, G4ACQ, 118 Brook Street, Erith

Worksop, Netts.

OTLEY: H. S. Johnstone, 12 Rumple Croft, Newall Carr, Otley, Yorks, LS21-2RE.

OXFORD: D. R. Ward, 2 Lincoln Road, Oxford (77471), OXI-4TB.
PLYMOUTH: S. E. Martin, 32 East Park Avenue, Mutley, PLYMOUTH: S. E. Martin, 32 East Park Avenue, Mutley, Plymouth, PL4-6PF, Devon.
R.A.I.B.C.: Mrs. F. Woolley, G3LWY, 331 Wigan Lane, Wigan.
REDDITCH: R. J. Mutton, G3EVT, Summerhayes, Mill Lane, Oversley Green, Alcester (2041).
SALTASH: J. A. Ennis, G3XWA, 19 Coombe Road, Saltash, (3551), Cornwall, PL12-4ER.
SHEFFORD: A. Sullivan, G2DGF, 12 Glebe Road, Letchworth, Herts Herts.
SILVER WING (B.E.A.): D. Evans, G3OUF, 2 Meadow Drive, Amersham (3257), Bucks.
SOLIHULL: J. Burnie, G8BYM, 12 Buryfield Road, Solihull (021-705 4565), Warks.
SOUTH BIRMINGHAM: R. J. Thompson, 23 Fox Hill, Selly Oak, Birmingham, 29.
SOUTHGATE: A. Hydes, G3XSV, 6 Glenbrook North, Cotswold Way, Enfield (01-363 8747).
SOUTH MANCHESTER: D. Holland, G3WFT, 7 Alcester Road, Sale, M33-3GW.
SPEN VALLEY: J. Milnes, G8DSB, 19 Cliffe Road, Staincliffe, Batley, Yorks. (Heckmondwike 2433).
THAMES VALLEY: C. Seaman, G3ATF, 40 Park Road, Ashford, Middx. Handes Valley: C. Seaman, G3ATF, 40 Park Road, Ashford, Middx.

TORBAY: Mrs. G. L. Western, G3NQD, 110 Truro Avenue, Hele, Torquay.

VERULAM: H. Young, G3YHY, 93 Leaford Crescent, Watford, WD2-5JQ.

WEST OF SCOTLAND (Glasgow): V. T. Budas, GM3VTB, 28 Kelvinside Gardens, Glasgow, N.W.

WHITE ROSE: R. Short, G3YEE, 10 Tyersal Grove, Bradford 4 (664-220), Yorkshire.

WIRRAL: A. Fisher, G3WSD, 34 Glenmore Road, Oxton, Birkenhead, Cheshire (051-652 5078).

WOLVERHAMPTON: J. Burden, G3UBX, 28 Coalway Road, Wolverhampton, WV3-7LX.

WORCESTER: G. Spink, G3WUI, 1 Belvoir Bank, North Malvern, Worcs. (Malvern 3088).

YEOVIL: D. L. MacLean, G3NOF, 9 Cedar Grove, Yeovil, Somerset.

YORK: J. A. Rainbow, G8BOK, 14 Temple Road, Bishop-thorpe, York, YO2-1QN.

#### SHORT CLUB NOTICES

CLUB Name	HEADQUARTERS LOCATION	MEETING DAY MONTHLY
Acton, Brentford and Chiswick	66 High Road, Chiswick	October 19
Bicester	11 Stoneburg Cres., Bicester	Fridays
Bristol University	Dept. of Physics, Royal Fort, Tyndall Park Road	Saturdays, 2.30 p.m.
Cambridge University	King's College	October 12
Coventry	121 St. Nicholas Street, Radford Road	Fridays (AGM October 1)
Cray Valley	Congregational Church Hall, Court Road, S.E.9	October 7, October 21
Crystal Palace	Emmanual Church Hall, Barry Road, S.E.22	October 16
Echelford	The Hall, St. Martins Court, Ashford, Middx.	October 29 (away)
Hull	592, Hessle Road	Fridays
Mansfield	New Inn, Westgate	1st Friday
North Kent	Not quoted	October 14 October 28
Oxford	Cherwell Hotel, Watereaton Road	2nd and 4th Wednesdays
Plymouth	Virginia House, Bretonside	1st and 3rd Tuesdays
Shefford	Church Hall, Ampthill Road	Thursdays
Southgate	Civil Defence Hut, opp. Arnos Grove Tube	2nd Thursday
South Manchester	Sale Moor Community Centre, Norris Road, Sale	Fridays
York	British Legion, 61 Micklegate	Thursdays

N.B.—In each case, secretary's name and address appears in Panel, p.498.



" . . . getting a bit more through the spout here, OM . . . "

programme, for which you are referred to G3UCQ, as in Panel opposite.

Chineham House, Shakespeare Road, Popley, is the place where the Basingstoke chaps foregather. October 2 is booked for station operation and construction, and on the 16th, they have a constructional competition—an event which nearly always throws up something of interest.

Most months we have something to report from the Nigerian group, by way of their NARS News—and it is of interest to be told that they have had some enquiries about the Club as a direct result. Of course, they are not just a local group but a full-blown National Society as well—a fact which tends to put a savour into the



We might almost call this a Puzzle Picture—but in fact it illustrates part of the Leeds Radio Society project to construct, on a Club basis, a number of small portable two-metre Tx/Rx units which can be easily carried about to meetings (think of the QRM!) and outdoor field events. The printed-circuit layout for each section is photographed and from these, board diagrams are prepared for distribution to members wishing to build up a sophisticated rig involving bi-polars, PET's and the readily obtainable IC's.

# IDENTIFICATION CODES FOR CLUBS IN "MCC"

Zone A—Scotland	d	Sheffield (University)		Sutton Coldfield	C72	Crystal Palace	F56
Aberdeen	A2	Southport	B66	Wirral	C73	Culham	F57
Ardeer	A3	S. Shields	B67	Wolverhampton	C74	Dartford Heath D/F	F58
Border	A4	Spen Valley	B68	Worcester	C75	Dorking	F59 F62
Dundee (Tech. Coll.)	A5	Star (Leeds)	B69 B72			Dunstable Downs Dursley	F63
Falkirk Group	A6	Sunderland Thornton Claveleys	<b>B</b> /2	Zone D-Eastern	1	Ealing	F64
Glasgow Univ.	A7	Thornton Cleveleys (Lancs.)	<b>B</b> 73	D G( E11	D.3	East Barnet	F65
Glenrothes	A8	Tyneside	B74	Bury St. Edmunds	D2 D3	East Kent	F66
Greenock	A9	Wakefield	B75	Cambridge Cambridge (Univ.)	D3 D4	Echelford	F67
Heriot-Watt Univ.	A22	Westmorland	B76	Digby R.A.F.	D5	Edgware	F68
Inverness Lothians	A23 A24	West Riding Contest		Grimsby	D6	Fareham	F69
Mid-Lanarkshire	A24	White Rose	<i>B</i> 78	Grimsby (Wheatsheaf		Fareham (Group)	F72
Group -	A25	York (Bradford)	<b>B</b> 79	Haverill	D8	Fawley	F73
Moray Firth	A26			Ipswich	D9	Finchley	F74
Pentlands	A27	Zone C-Midland	1.	Lincoln	D22	G. Kent, Ltd. (Luton)	F75
Radio Club of		Zone C-Widiano	15	Lowestoft	D23	Gosport	F76
Scotland	A28	Ashton-u-Lyme	C2	Norfolk	D24	Government Comms.	E77
Spey Valley	A29	Bromsgrove	<i>C3</i>	Pye (Cambridge)	D25	(Cheltenham)	F77 F78
West of Scotland	A32	Burslem	C4	Scunthorpe	D26	Grafton Greenford	F79
Zone B—Northern En	aland	Cannock Chase	C5	Skegness	D27	Guildford	F82
	_	Chapel Green Countr		Spalding	D28 D29	Harlow	F83
Ainsdale	B2	Chester	<i>C7</i>	Stowmarket Wattisham R.A.F.	D29 D32	Harrow	F84
Billingham	B3	Chesterfield	C8	Wymondham	D32 D33	Havering	F85
Bishops Rawsthorne	B4 B5	Coventry	C9 C22	vv ymondnam	<i>D33</i>	Hemel Hempstead	F86
Blackpool and Fylde Bolton	В3 В6	Derby Derby (Nunsfield)	C23			Henley G.S.	F87
Bradford	B0 B7	Dudley	C23	Zone F (L)—South	ern	High Wycombe	F88
Bury and Rossendale		Four Counties	C25	Acton, Brentford and		Hillingdon	F89
Carlisle	B9	Henley-in-Arden	C26	Chiswick	F2	Horsham	F92
Chorley	$\vec{B22}$	Hereford	C27	Addiscombe	F3	Isle of Wight	F93
Cleveland	B23	Keele (University)	C28	AERE, Harwell	F4	Kingston	F94
Culceth, Liverpool	B24	Kings Norton Contest	t <i>C29</i>	Ampfield Contest	F5	Leyton and	F95
Cumberland	B25	Leicester	C32	Ariel (BBC)	F6	Walthamstow Loughton	F95
Dial House, Salford		Lichfield	C33	Axe Vale	F7	Luton	F97
East Lancs.	B27	Macclesfield	C34	Baden-Powell House		Maidenhead	F98
Eccles	B28	Magnus, Newark	C35	(London)	F8	Maidstone YMCA	F99
Fulford Fylingdales	B29 B32	Mansfield	C36	Barking	F9	Marconi Apprentices	
Halifax	B32 B33	Melton Mowbray Mid-Cheshire	C37 C38	Basildon Basingstoke	F22 F23	(Chelmsford)	L2
Hallamshire	B33 B34	Midland	C39	Basingstoke Bedford	F23 F24	Medway	L3
Hartlepools	B35	Mid-Warwicks	C42	Bicester	F25	Mid-Herts	L4
Hull	B36	Newark	C43	Bishops Stortford	F26	Mid-Sussex	L5
Leeds	B37	Northampton	0.10	Bracknell	F27	Minehead	L6
Leyland Hundred	B38	Short Wave	C44	Brighton	/	Nailsworth	L7
Lindholme R.A.F.	B39	North Notts	C45	(Technical Coll.)	F28	Newbury	L8
Liverpool	<b>B42</b>	North Staffs.	C46	Brighton		Newham	L9
Liverpool (University)		North Staffs.		(Coll. of Tech.)	F29	North Bucks,	L22 L23
Manchester Group	B44	(Polytechnic)	C47	Bristol	F32	Northern Poly North Kent	L23
Manchester	D 45	Nottingham	C48	Bristol	F2.2		L25
(University) Manchester Institute	B45	Nottingham (Univ.) Nuneaton	C49 C52	(Shirehampton)	F33		L26
of Science and		Painton	C32	Bristol (University) Brunel University	F34 F35		L27
Technology)	B46	(Northampton)	C53	Burnham Beeches	F36		L28
Mexborough	B47	Peterborough	C54	Burnham-on-Sea	F37	Racal	L29
Morpeth	B48	Redditch	C55	Chelmsford	F38		L32
Newcastle-on-Tyne		Rugby	C56	Cheltenham G.S.	F39		L33
(University)	<b>B</b> 49	Salop	C57	Cheltenham	F42		L34
Northern Heights	<b>B</b> 52	Sealand R.A.F.	C58	Cheltenham Group	F43		L35
North Liverpool	B53	Slade	C59	Chesham	F44	Royal Marines,	T 26
Northumbria	B54	Solihull	C62	Cheshunt	F45	Portsmouth	L36
N.W. Durham	B55	South Birmingham	C63	Chichester	F46	Royal Navy,	1 27
Ovingham Otley	B56 B57	South Manchester	C64	Chiltern	F47	Petersfield	L37
Preston	B58	Stafford (Coll. of Tech.)	C65	Chippenham	F48 F49	Royal Signals	L38
Rotherham	B59	Stockport	C66	Clacton Clifton	F49 F52	R.A.F. A.R.S., Locking	1.30
St. Helens	B62	Stoke-on-Trent	C67	Colchester	F53 F53	Salisbury	L39 L42
Scarborough	B63	Stourbridge	C68	Crawley	F54	Shefford	L43
Sheffield	B64	Stratford-on-Avon	C69	Cray Valley	F55	Silverthorn	L44
				,	-		•

Silver Wing (BEA) S. Langton School	L45 L46	Vange, Basildon Verulam	L72 L74	Zone H—All GW Co	ounties	Univ. College, Cardiff	H33
Southampton	L47	Veteran Operators	$\overline{L}75$	Bangor	H2	Univ. College,	1133
Southampton		Wanstead and		Bangor	***	Swansea	H34
(University)	L48	Woodford	L76	(Univ. College)	H3	Welsh	H35
South Bucks. Contest	L49	Wessex	L77	Barry (Coll. of Furth	er		1100
Southdown	L52	West Kent	L78	Education)	H4	7 1	
Southend-on-Sea	L53	Wimbledon	L79	Blackwood	H5	Zone J—	
Southgate	L54	Winchester	L82	Cardiff	H6	Ireland and Isle o	f Man
Speedbird (BOAC)	L55	Worthing	L83	Chepstow	<i>H</i> 7	Ballymena	<b>J</b> 2
STC, Harlow	L56	Yeovil	L84	Conway Valley	H8	Bangor	J2 J2
Stevenage	L57			Flint	H9	City of Belfast	J2 J4
Stroud	L58	Zone G—South-We	estern	Haverfordwest	H22	IRTS Region 1	J4 J5
Surrey	L59 L62	C4 I		Llanelli G.S.	H23	Isle of Man	J6
Sussex University Sutton and Cheam	L62 L63	St. Lawrence's,	C)	Maesteg	H24	Limerick	J7
Swindon	L63 L64	Bodmin Cornish	G2	Pembroke	H25	South-East EI	18
Taunton	L65	Exeter	G3 G4	Port Talbot	H26		•
Thanet	L66	North Devon	G5	Rhyl Rhondda	H27 H28		
Thames Valley	L67	Plymouth	G6	Sully	п26 H29	Zone K—Channel	Isles
Thornbury	L68	Saltash	G7	Swansea Telephone	П29	Guarnaari	W3
University of Essex	L69	Torbay	G8	Area	H32	Guernsey	K2
or Essen		10104	30	Aica	1132	Jersey	K3

#### THE MCC ZONES

The Zone in which a Club is located is indicated by the initial letter of the Ident. Code. The multiplier for a contact with another Club is defined by the Zone letter sent and received, and will be the same for both stations (see Scoring Table). The Zones are as follows: Zone A: All Scottish counties.

Zone B: Northern England—Northumberland, Durham, Cumberland, Westmorland, Lancashire and Yorkshire.

Zone C: The Midlands—Cheshire, Derby, Shropshire, Stafford, Hereford, Worcester, Warwick, Nottingham, Leicester, Rutland, Northampton, and Huntingdon.

Zone D: Eastern—Cambridge, Norfolk, Suffolk and Lincolnshire.

The South—Somerset, Dorset, Gloucester, Wilts, Berks, (or L) Hants, Oxford, Bucks, Herts, Middlesex, Surrey, Sussex, Kent, Essex, London and Bedford.

Zone G: South-Western—Devon and Cornwall.

Zone K: All EJ/GJ/GD.

Zone K: All EJ/GJ/GD.

Zone H: Zone J: Zone K:

Channel Isles

#### Scoring Table

#### Multipliers to be applied to Club Contacts.

Contact with own Zone, multiplier 10

Contact between		Contact between	
Zones A and B(V)	11	Zones C(X) and H	11
A " C(X)	13	C(X) ,, $J$	13
4 " D`'	14	C/V\ E	15
	15	D E(I)	îĭ
A C.	17	D "C'"	15
A ,, G	12		
Ą " Ħ	13		12
	15	D ,, J	15
A	20	D " K	15
B(V) , $C(X)$	11	F(L) ,, G	11
B(V) ,, D	13	F(L) ,, H	11
B(V) , $F(L)$	13	F(L) ,, J	15
B(V) ,, G	15	E(I) V	15
R(V) II	13	G H	îĩ
RÁVÝ T	13	Ć " ī	15
B(V) ,, K	20		12
	20		12
$\mathbf{C}(\mathbf{X})$ ,, $\mathbf{D}$	11	н "ј	11
$\mathbf{C}(\mathbf{X})$ ,, $\mathbf{F}(\mathbf{L})$	H	н "к	12
C(X) G	12	.J K	12

Contact with non-Club station, regardless of location, attracts multiplier of 10.

N.B. Letters (V) and (X) to accommodate late-entry stations in B and C Zones.

#### EXAMPLES FOR OPERATING

Coventry works Derby and sends 579C9, receives 579C22; Aberdeen works Jersey and sends 559A2, receiving 549K3.

#### EXAMPLES FOR SCORING

Coventry works Derby. Each claims three points x multiplier of Aberdeen works Jersey. Each station claims three points x multiplier of twenty, equals sixty points.

Newsletter editorial comment on occasion.

Cheltenham are having a Sale of Surplus Equipment on October 7, at the "Royal Crescent" in Clarence Street, Cheltenham.

There are two get-togethers at Solihull in October. That on October 5 is in the rear bar of the Malt Shovel in High Street. On October 19 things are a little more formal-it is the Annual General Meeting, at the Manor House, High Street, starting at 7.30 p.m.

Now to Verulam, who have the Council Chamber of St. Albans Town Hall for their regular evening sessions. On October 20, G3SBA is coming along to talk about some HF Design and Construction Projects.

Up in Glasgow, West of Scotland (Amateur Radio Society) have got through their AGM, with new elections for 1971-'72— and it is noteworthy that on August 27 they had a record attendance of 96 members. October 8 they are being hosts to the Ayrshire group. This very active Glasgow group, with more than 100 members after only one year's existence, now have their own callsign, GM4AGG, running K.W. gear on the HF bands and an IC-2F for two metres.

#### Deadline

This is one of those blessed (to us, anyway!) months when we have a little more time between issues—the deadline for November is Friday, October 8, with all "Clubs" material addressed to: Club Secretary, SHORT WAVE MAGAZINE, BUCKINGHAM. For December issue, it will be November 5—but we are not giving you a date for the January, 1972, issue because the Clubs space in that will be devoted to a full report on MCC, the annual Magazine Club Contest on Top Band, taking place during the weekend November 6-7, for which we hope to have a record entry. All gen. herewith!

# NEW QTH's

This space is available for the publication of the addresses of all holders of new U.K. callsigns, as issued, or changes of address of transmitters already licensed. All addresses published here are reprinted in the U.K. section of the "RADIO AMATEUR CALL BOOK" in preparation. QTH's are inserted as they are received, up to the limit of the space allowance each month. Please write clearly and address on a separate slip to OTH Section.

- G3GUE, A. F. Dowling, Laburnum,
  Clearway, Addington, Maidstone,
  Kent. (re-issue). (Tel. West Malling 2557.)
  G3ZVW, S. White, 262 Princes
- G3ZVW, S. White, 262 Princes Avenue, Palmers Green, London, N13-6HN.
- G3ZZO, M. J. Miller, 94-A High Street, Orpington, Kent, BR6-OJY.
- GM4AAF, Kingsway Technical College Amateur Radio Club, Kingsway Technical College, Old Glamis Road, Dundee.
- **G4ABS**, D. Bedford, 19 Havacre Lane, Coseley, Bilston, Staffs.
- GM4AGG, The West of Scotland Amateur Radio Society, 81 Virginia Street, Glasgow, C.1.
- GM4AGS, J. N. S. Miller, Ingleby, West Road, Newport-on-Tay, Fife, DD6-8HP.
- G4AHO, K. M. Jones, c/o Diplomatic Wireless Service, E.M.R.S., Limassol, Cyprus.
- GW4AHV, H. Lewis, 1 Western Road, Portardawe, Swansea, SA8-4A I
- G4AIR, D. A. Bieber, The Chapel House, Warfield Street, Bracknell, Berks.
- G4AJM, B. Smith (ex-G8CSG), 1 Back Street, Mundesley, Norwich, Norfolk, NOR.33-Y.
- G4AKJ, T. G. Abrahams, 73 Boston Road, Bristol, BS7-OHD. (Tel. Bristol 46612.)
- G4AKQ, M. Bernard (ex-DL5XW), 23 Tovil Road, Maidstone, Kent. (Tel. Maidstone 64623.)
- G4AKV, T. H. Allen, 4 Leonards Lane, Feltwell, Thetford, Norfolk.
- G4ALG, S. A. Rawlings, 7 Winch-combe Road, Twyford, Reading, Berkshire. RG10 OAS.
- G4AMH, J. W. Stratton (ex-G8DFL/ZC4JW), 11 Bondfield Avenue, Northampton, NN2-7RD.
- G8DFW, K. R. W. Swift, 10 Barnhill Close, Marlow, Bucks., SL7-3HA
- **G8EZD**, D Gifford, Roecliffe, Sandpits Road, Ludlow, Salop.
- G8EZH, M. A. Smith, 52 Rockhurst Drive, Eastbourne, Sussex. G8FAJ, J. Everett, Marloes, Comp Lane, St. Mary's Platt, Sevenoaks,

- Kent. (Tel. Borough Green 3329.) G8FAO, M.H. Tunau, 87 Leigham Vale, London, S.W.16, 2.IG
- **G8FBB,** J. H. Lloyd, 70 Heath Drive, Ware, Herts.
- G8FBL, G. Benson, 2 Saxon Walk, Lichfield, Staffs., WS13-8AJ. (Tel. Lichfield 3919.)
- **G8FBN**, M. Stevens, 72 Firgrove Road, Freemantle, Southampton, Hants., SO1-3EP. (*Tel. Southamp-ton 71856*.)
- **G8FBO,** R. B. Stockwell, 20 Grange Road, Little Cransley, Kettering, Northants.
- GW8FBU, P. S. Murray, 146 Sandy Road, Llanelli, Carms.
- **G8FEO**, S. E. Lowe, 59 Lyndhurst Road, Exmouth, Devon, EX8-3DS. (*Tel. Exmouth 6203*.)

#### CHANGE OF ADDRESS

- G3AIU, K. A. H. Rogers, The Manor Hotel, Titchwell, Brancaster, Norfolk.
- G3HKQ, L. V. Westmoreland, Endeavour, Hayton Smeath, Retford, Notts. (Tel. Retford 4597.)
- G3KVV, V. Bridport, BM/G3KVV, London, W.C.1.
- G3MBK, D. W. Underdown, Kimberley, Anchor Hill, Knaphill, Woking, Surrey.
- G3NGF, Rev. A. W. Shepherd, WAMRAC Headquarters, The Manse, Kendal Road, Tebay, Penrith, Cumberland. (*Tel. Orton 275*.)
- G3NJB, WAMRAC Headquarters, The Manse, Kendal Road, Tebay, Penrith, Cumberland. (*Tel. Orton* 275.)
- G3NZT, A. Hodgkinson, L.D.S., V.U.M., Stone-Beck, Fell Foot, Newby Bridge, Ulverston, Lancs. (Tel. Newby Bridge 550.)
- G3NZT/A, A. Hodgkinson, L.D.S., V.U.M., East Lynne, Millans Park, Ambleside, Westmorland. (Tel. Ambleside 2544.)
- **G3PMR**, A. H. Jubb, 5 York Close, Chippenham, Wilts. (*Tel. Chippenham*, 50275.)
- GI3RPT, M. O'Boyle, 26 Townview Avenue South, Omagh, Co. Tyrone. (Tel. Omagh 3785.)

- G3UJU, M. Haslam, Lynchetts, Upper Lambourne, Berks.
- GM3VEY, F. Baxter, 10 Buddon Drive, Monifieth, Angus, DD5-4TH.
- G3XYG, Dr. M. George (ex-GM3XYG), Northfield Cottage, Northfield Lane, Barnstaple, N. Devon. (Tel. Barnstaple 2967.)
- G3YMP, P. A. Lovell, c/o Timberley, Trefusis Terrace, Redruth, Cornwall.
- G3YSG, M. Taylor, 54 Rectory Road, Upton-on-Severn, Worcs. (Tel. Upton-upon-Severn 2564.)
- G3YTS, R. W. Ferguson, 6 Cambridge Grove, Kippax, Leeds, Yorkshire, LS25-7JF. (*Tel. Garforth 3576.*)
- GM3YVX, D. W. Coupar, 32 Gillies Place. Broughty Ferry, Dundee.
- G3YWZ, K. Buksh, 5 Broadfield Avenue, Blackpool, Lancs., FY4-3RA.
- G3ZPG, R. Shipman, 29 Holmfield Road, Leicester.
- G5APC, J. H. Garrett, c/o Seiscom Limited, Tubs Hill House, Sevenoaks, Kent.
- GISACY, C. J. Champion, 37 Dundron Drive, Old Warren II, Lisburn, Co. Antrim.
- **G8CEZ**, R. A. Fuller, 35 Chichester Walk, Oakley Garden Village, Wimborne, Dorset.
- G8CRD, D. Gibbon, 9 Queen Street, Kingswood, Bristol, BS15-2BA. (Tel. 0272-673346.)
- **G8DDB**, W. F. Kirby, c/o Sgts' Mess, R.A.F. Coningsby, Lincs.
- G8DDW, S. C. Fletcher, 90 Westcombe Park Road, Blackheath, London, S.E.3-7OS.
- **G8DHP**, R. A. Hood, Broombank, Nutley, Uckfield, Sussex.
- G8DJU, R. Frisby, 4 Westfield Walk, Waltham Cross, Herts. (Tel. Waltham Cross 31584.)
- G8DKA, S. Westlake, 20 Max Road, Quinton, Birmingham, 32.
- **G8DRY**, E. C. Jones, 7 Forton, Montford Bridge, Shrewsbury, Salop.
- G8RY, F. E. Wyer, 31 Princess Avenue, Knaresborough, Yorkshire, HG5-OAW.

CALL BOOKS
INTERNATIONAL: RADIO AMATEUR CALL BOOK ("Fall" Edition)
"DX Listings" £3." "U.S. Listings" £4." The two together, covering the
World £6⋅1
"G's" only
MAPS
AMATEUR RADIO MAP OF WORLD  Mercator Projection — Much DX Information — in colour. Second
Edition 60
DX ZONE MAP (GREAT CIRCLE) In colour with Country/Prefix Supplement Revised to Dec. 1970
1970
U.S.A. AND NORTH AMERICA State boundaries and prefixes, size 24" by 30", paper 60
RADIO AMATEUR'S WORLD ATLAS In booklet form, Mercator projec-
tion, for desk use. Gives Zones and Prefixes 85
LOG BOOKS
Standard Log (New Glossy Cover) . 56
Log and VHF Contest Log 40
Receiving Station Log 43
ARRL. Log (Spiral) 70
(The above prices include increased postage rates and packing).  Delivery is from stock.
MORSE COURSES
G3HSC Rhythm Method of Morse Tuition Complete Course with three 3

G3HSC Rhythm Method of Morse	Tuition
Complete Course with three 3 speed L.P. records with books	£4·50
Beginner's Course with two 3 speed L.P. records with book.	£3·30
Single 12" L.P. Beginner's with book	£2·75
Single, 12" L.P. Advanced with book	£2·75
Three speed simulated GPO test. 7" d.s. E.P. record	85p
Ex.Gov. Heavy Duty Morse Keys	95p
Prices include postage, packing and ins	urance

Available from

# SHORT WAVE MAGAZINE

Publications Dept., 55 Victoria Street, London, S.W.1 . 01-222 5341

(Counter Service, 9.30-5.15, Mon. to Fri.) (Nearest Station: St. James's Park) (GIRO A/C No. 547 6151)

# Echelford Communications 32 FELTHAM HILL RD., ASHFORD, MIDDX.

Tel.: ASHford 55265

Our Winter 71/72 list is now being printed, and may be obtained from us by sending a  $9'' \times 4''$  S.A.E.

Many bargains and new lines.

I wish to thank the many well wishers at the August rallies and the shop, during my enforced four week stay in the local hospital.

ALLAN G. WHEELER, G3RHF

# CITY OF BIRMINGHAM Police Department WIRELESS TECHNICIAN

Salary: £1,059—£1,416 per annum (Technical Grades 2/3) according to ability, experience and qualifications.

Wireless Technicians are required for the repair and maintenance of mobile and personal radio sets used by Birmingham Police, Fire and Ambulance and other Departments.

Applicants should be familiar with principles of transmitter and receiver design and experienced in fault-finding techniques. Interesting and worthwhile work with a 37½ hour week.

Applications should be received within 14 days addressed to: STAFF APPOINTMENTS, P.O. BOX 29, Council House, Birmingham, BI IBB.

PLEASE STATE REFERENCE NUMBER 43/W/T/1/8 ON LETTER AND

(V 9148)

XTALS G3ACQ OFFERS: I-8 to 30 MHz Amateur Bands and VHF 9-12-16-35-48-70-80 MHz. All at 63p post paid. LUCKY DIP XTALS 10 mixed freqs. £1.13 post paid. TRIO TS510, JR599, GR59DS, JR310 Tech. GDO. JOYSTICKS, S.W. Bridges, Sig. Gen., etc. All in stock. SOLID STATE MODULES VHF Converters 2m.—4m.—70 cm., £13-75. These are superb, I can highly recommend them. New 24 Hour Digital Clocks £8-95.

# S. MAY (Leicester) LTD.

12/14 CHURCHGATE, CITY CENTRE, LEICESTER.

Tel. Leicester 58662

# TOO MUCH STOCK!!

-to list on one advertisement!

Yes, LST would need most of this magazine to show their full range.

But 5p for postage will bring you our FREE components catalogue. 44 pages of semiconductors, integrated circuits, passive components, tools, kits, etc., etc.

Write to:

LST ELECTRONIC COMPONENTS LTD.,
MAIL ORDER DEPT. SWM,
7 COPTFOLD ROAD,
BRENTWOOD, ESSEX.

OUR RETAIL COUNTER (same address) is open Monday-Saturday (Thursday early closing) under the auspices of G3LRL (Dick) who will be pleased to see you

### G3EKX S.S.B. PRODUCTS G3EKX NEW EQUIPMENT! READY FOR DESPATCH! NEW EQUIPMENT! READY FOR DEDDYSTONE EB35 Mk. 2 with V.H.F. EDDYSTONE Cabinet Speaker (grey) EDDYSTONE EC10 Mk. 2. The very latest EDDYSTONE 924 Pack TRIO Ham Receiver JR599 ... TRIO Ham Receiver, JR310 and PS510 TRIO Transceiver, TS510 and PS510 TRIO TRIO HAT PS507 Speaker SP5D £90.00 £3.70 £79.00 £7.75 £185.00 £77.50 £180.00 £4.37 TRIO 9R59DS. New stock £47.50 XTALS! XTALS! XTALS! STATE YOUR REQUIREMENTS. Send no money just an S.A.E. THOUSANDS!! New metal-cased Xtals (not ex-Govt.) 2 to 7 me, 50p, 12 mc upwards -110 mc, 50p each. 26-28 mc. miniature. We might have it 2 at 50p plus 5p P. and P. S.A.E. pse. PYRAMID 800 WATT 80-10m. LINEAR KITS 448.00 68.50 ATTENTION PLEASE! ALL KINDS OF RECEIVERS AND TRANSMITTERS REQUIRED FOR IMMEDIATE CASH OR PART EXCHANGE. SEND DETAILS NOW! S.A.E. HELPS CLASS "D" WAVEMETERS. (Untested) offered with brand new dual xtal (tested). Handbook and phones at only ... ... ... (75p) 15.75 + or 240v, A.C. input. Fully tested, Reconditioned (75p) £10.75 \* BUY NOW WHILE STOCK LASTS ! ! \* 7 LITTLE CASTLE STREET, TRURO Tel. DEVORAN 862575 CORNWALL

#### **EMSAC CRYSTAL SERVICE**

We have produced new lists of crystals in stock here as well as lists of the large stocks held by a well known American manufacturer. We aim to deliver by return for our own crystals and within 3 weeks on the overseas lists. However, please bear in mind that these are subject to the vagaries of importation in general! As a new service we offer FT243 crystals at £1.05 including postage ground to within 1 kHz at any frequency between 8 and 8-111 MHz. Our delivery target is 3 weeks after receipt of order. We also have the popular 38-666 in HC18/U per return delivery at £1-25. Grinding kits in stock £3.

Send an s.a.e. for our lists, including grinding prices, or telephone your requirements to West Kingsdown 2344: our telephone is manned between 9 a.m. to 6 p.m. 6 days a week.

# **EMSAC EQUIPMENT**

The large range of EMSAC equipment now available includes the following:—CN1, CN2 two metre converters; any IF supplied, £9.75 and £15.35. CN3, CN4 four metre converters, £9.75 and £15.35. CN5 Top Band converter to MW car radio, £8.75. PRI High gain iglet pre-amp for two metres, £4.75. TX4 Four metre TX, with AM, FM, CW, 6 valves £28.85. FX2 two metre TX, with AM, FM, CW, 6 valves £28.85. FX ITX2 two metre TX, with AM, FM, CW, 6 valves £28.85. FSI mains p.s.u. for converters, £3.75. PS2 mains p.s.u. for converters, £3.75. PS2 mains p.s.u. for converters, £3.75. FS2 mains p.s.u. for converters, £3.75. EV3 mains p.s.u. for converters, £3.75. DS2 mains p.s.u. for converters, £3.75. DS3 mains p.s.u. for converters, £3.75. DS3 mains p.s.u. for converters, £3.75. DS3 mains p.s.u. for converters, £3.75. GV1 General purpose vertical antenna, all band £5. GD1, GD2, SRV type wire dipole all band antennas, £4.25 and £3.25. Demonstrations of all equipment arranged. J. beams stocked. All prices include postage and packing.

New comprehensive lists available. Send large s.a.e. or Telephone : West Kingsdown 2344

#### G31AR

ELECTRONIC & MECHANICAL SUB-ASSEMBLY Co. Ltd. Highfield House, West Kingsdown, Nr. Sevenoaks, Kent

# "CALLBOOK"

"FALL" EDITION

Please order early to ensure your copy, available early October.

Known the world over as the CALLBOOK, this comprehensive reférence lists about 300,000 licensed radio amateurs in the United States Directory and 160,000 or more in the rest of the world (contained in the "DX Section"). The entries grow with every issue! In the U.S. Section, licence classifications are now shown. Each issue is an entirely new book with revised listings of new licences, names and addresses. The CALLBOOK also includes much incidental DX information. Every amateur operator and SWL needs the latest CALLBOOK to get the most out of Amateur Radio.

The CALLBOOK has a new look—the directory pages are now easier to read—upper and lower case print, a much desired improvement and one we are all accustomed to reading.

DX Listings £3:10

US Listings £4'10

The two together, covering the World, £6'80

The above prices include increased postal rates and packing.

Available only from
Publications Dept.,
SHORT WAVE MAGAZINE

55 Victoria Street, London, S.W.I 01-222 5341

# WORLD RADIO/TV HANDBOOK 1971

(From Stock)

The World's only complete reference guide to International Radio & Television Broadcasting Stations. It includes: Frequencies, time schedules, announcements, personnel, slogans, interval signals and much more.

Lists all International short-wave stations, including frequencies, for each country; foreign broadcasts, long and medium wave stations (AM broadcast Band), TV stations and domestic programmes. Long recognised as the established authority by broadcasters and listeners. It is the only publication that enables you to identify BC stations quickly and easily. Enables you to fill more pages in your log book on the SW BC bands and helps you add more BC-station QSL cards to your collection.

€2 · 25

(The above prices include increased postal rates and packing).

from:

SHORT WAVE MAGAZINE
55 Victoria Street, London, S.W.I

#### ALL ABOUT CUBICAL QUAD ANTENNAS by William I. Orr, W6SAI

This world-famous book, which has become a classic in its field, discusses the theory, design, construction and operation of Cubical Ouad antennas. It covers the Quad's history, operation and characteristics: multi-element and concentric Quads; the X-Q Quad with 3 dB gain over normal design; the new Tri-Gamma match; new, improved feed systems; new, sturdier construction; true angle of radiation; antenna tuning and maintenance. Contains data never before published! All you need to know about Quads! 96 pages £1.78 post free

# BEAM ANTENNA HANDBOOK by William I. Orr, W6SAI; 3rd edition

This completely revised 3rd edition of Bill Orr's popular book covers beam antenna theory, design, construction, installation. and adjustment. Includes ionosphere theory; transmission lines: matching devices; new Inducto-match system; parasitic beams; all-metal arrays: multiband beams: wire beams; 20 and 40 metre compact beams: design charts and SWR curves for beams-six to forty metres; how to evaluate your beam; test instruments and how to use them; different types of installation. A "must" for the serious DXer whether he buys or builds his beam. 200 pages £2.08 post free

Publications Dept.

Short Wave Magazine Ltd., 55 Victoria Street, London, S.W.1. (01-222 5341/2)

#### **TAURUS ELECTRICAL SERVICES**

(Prop.: G3TED)	
1392 RECEIVERS. 100-150 Mc/s. Complete with full mods.	
for 2 metres coverage Carr. baid	£7·50
NEW MODERN GEIGER COUNTERS S145 Carr. paid	£6.50
MAINS TRANSFORMER. O/P 250v. at 200 mA, 6·3 at 3·5 amps Care, paid	£2-10
spindle Post paid	20p
MAINS SMALL MOTORS. 2½ r.p.m. Power full Post paid	50p
SPECIAL OFFER of QQV03-10's. Tested Post paid	55p
New 6CL6's, Tested Post haid	55p
6L6's. Ruggadised. New Post paid	80p
TELEPHONE HANDSETS Post paid Per pair	£1.00
EX. G.P.O. TELEPHONES Post poid E180CC valves Post poid	£1.25
NEW VHF AERIAL CHANGE OVER RELAY. Tested.	25p
	£1.70
METERS:	£1.70
2½" round 50-0-50 Microamp Meters Post paid	80p
2½" round 0-300 A.C. meters Post paid	£1.25
SPEAKERS—New. 1½" 40 \( \Omega \) Post poid	35p
3673 AIRCRAFT RECEIVERS. 19 valves, complete Post paid	68.00
NEW 80 WATT POWER TRANSISTORS 2G221 Post baid	30p
NEW TEXAS 2N2537. N.P.N. High Freq. med. power 250	ээр
megs Post baid	60p
BY100's. Tested Post paid 15p ea. £1-1	
MIXED COMPUTER PANELS (min, of 30 transistors) Post paid	50p
144 Kc/s. TRANSCEIVERS. Less valves Carr. paid With valves (15) Carr. paid	£3.00 £5.00
TRANS CALL UNITS (mains intercoms). Complete with valves Carr, baid	€2.20
MIXED PARCELS. Resistors, components, etc. Large bags	
Post poid	£1 · 50
SMALL VARIABLE CONDENSERS. Air spaced. Long shafts (3 different types) Post poid per 3	50p
	эvр
CREED 7B's	
Al Tested condition, £25. Delivered.	
A2 Untested, complete average condition. £11. Delivered	
Spares (incomplete 7B's) 7 tons to shift at £6 per 100 lbs. Dol	ivered.
Sproket Paper O.K. for friction feed as well. Box 10 pads, Delivered.	£1.70
Pink/yellow reperf rolls. Box 20 pads, £2.70. Delivered.	
Same price Box 30 pads. £3.50. Delivered.	
Box 50 pads, £5.00. Delivered.  CREED AUTO TXS (Tape Readers), £8.50. Delivered.	
CREED AUTO TXS (Tape Readers), £8-50. Delivered. CREED 7TR Reperforators, £8-50. Delivered.	
handbook, £7.50. Delivered.	
Few only new transistorised Keyer units with handbook new	boxed,
£8-50, post paid. Extra hand books £1-25. This is modern Amequipment.	ne <i>r</i> ican

26/28 NOTTINGHAM ROAD, LOUGHBOROUGH

Telephone 5131

# TELECOMMS G3SFD

AMATEUR COMMUNICATIONS—ELECTRONIC COMPONENTS SALES AND SERVICE

TRIO TS510 transceiver with PS510 po		ibbla			£186
TRIO JR310 SSB receiver, Ham band of	nly				£77 - 50
TRIO JR500 Communications receiver		•••			£69.50
TRIO 9R59DS All band receiver	• • • •	• • • •	•		£42 · 50
TRIO JR599 Transistor/FET Ham band	receiv	ег			£18!
TRIO HS-4 Padded headphones					£5 · 35
SP-5D Communications speaker					£4-60
CW FILTER for TS510  10AZ Mechanical filter for JR310  25 kHz marker unit for JR310 (less area)					£14.67
25 kHz marker unit for JR310 (less crys		•••			£14·67
100 kHz Calibration Crystal HCI6U					£3 · 18
OA2 Mains Voltage Stabiliser		•••			67 p
BIO16/C Hand held Communication TS510 transceiver				TRIO	£3.38
LESSON TW205A Table Standing mic	rophor 	1e w	ith b	attery	£7.95
preampliner					HONE

#### (Turner) Desk Microphone

Chrome satin finish, with PTT facility. High impedance dynamic mic., specially suited for communications purposes.

PRICE £6 plus 50p P. & P.



#### MORSE KEYS

New ex-govt, morse keys with jack plug and lead. Fully adjustable contact spacing and spring tension. PRICE 49p plus 15p P. & P.

#### SPECIAL OFFER! PRINTED CIRCUIT BOARD

S.R.B.P. Copper laminate board, sizes cut to your requirements.

(max. size 4ft. by 3ft.) ... ... PRICE 12-p per sq. ft. Fibre glass laminate board ... (max. size 3ft. by 2ft.)
Allow plenty of postage—excess will be refunded. PRICE 15p per sq. ft.

ADMIRALTY PATTERN MORSE KEYS. Few only of these popular "Brass Pounders." Base size 6" by 3½". Price 75p, post and packing 15p

NEW BOXED SIFAM METI	ERS	(Special	Price	e)	
Type M25 0–250v. 2⅓″ sq.				(P.P. 12p)	£1 · 50
Type M312 0—500v. 3 3 " sq.				(P.P. 12p)	£1.20
Type M303 0300 m/A 3 3 g sq.				(P.P. 12p)	£1.20
Type M303 0—250 m/A 3 3 " sq.				(P.P. 12p)	£1.20
Type M303 0— 50 m/A 3 3 " sq.				(P.P. 12 <sub>p</sub> )	£1-20

#### NEW AEI TRANSFORMERS (Standard mains primary)

Type I 0-310v. at 180 m/A., 170v. at 30 m/A., 6·3v. at 3·2A. Price 75p plus 25p post

Type 2 0-320v. at 60 m/A., 10·5-0-10·5v. at 3A., 6·3v. at 1A. Price 75p plus 25p post

Type 3 370–0–370v. at 80 mA., 3·15–0–3·15v. at 3A., 6·3v. at 1A.
Price 95p plus 25p post

Type 4 ALBION :—0-2-5v., 0-15-26v. both at 1½A.
Price 60p plus 12p post Type 5 Reading :—400–0–400v. at 200 m/A., 6·3v. at 3A., 5v. at 2A. Price 41·50 plus 25p post

Type 6 WODEN:—0-20-22-5-25-27-5-30-32-5v, at 15A 200v. at 50 m/A., 5v. at 2A., 6-3v. at 1A. Price £4 plus 60p post

DUBLIER Nitrogel capacitors (Block paper) 8 mfd. at 800v. ... WRITE NOW FOR OUR LATEST COMPONENTS LISTS For the caller we have a comprehensive range of components at competitive prices.

Shop Hours: Mon. to Sat. 10 a.m.-7 p.m. Half day closing Thursday. Tel.: PORTSMOUTH (0705) 60036 Terms: Cash with Order.

73's From 73 TWYFORD AVENUE, STAMSHAW, PORTSMOUTH, HANTS.

# YOUR MIDLAND STOCKISTS

EQUIPMENT

#### AERIAL EQUIPMENT

Full range of "J" BEAMS in stock. 2 Mtr. and 70 cm. Please allow 50p for carr.

SUPER AERAXIAL CABLE 75 ohm, very low loss, 13p per yd. Also 50 ohm 300W, 25p per yd. P. and p. either 24p.

RIBBED CERAMIC INSULATORS, 12+p. DIPOLE CENTRE PIECE, 12+p. TRANSPOSITION BLOCKS, 5p. P. and p. 12+p.

COPPER AERIAL WIRE H/D 14G and 7/-029 Stranded, also 40/-0076 covered, 140ft., £1-87; 70ft., 95p. Other lengths pro rata. (Lengths approx., sold by weight). P. and p. 24p.

TOUGH POLYTHENE LINE 100 lb. B/S ML1, 63p. 100 yds. 200 lb. B/S ML2, £1-25 100 yds. 400 lb. B/S ML4, ½p per yd. P. and p. (any quantity) 12½p.

CHAS. H. YOUNG LTD.

A FACILIATIA	
EDDYSTONE ECIO	
Mark II	£79.00
TRIO 9R59DS	£47.50
TRIO 9R59DS with Cal.	£50.00
TRIO JR500SE	£48.00
TRIO JR310	£77.00
KW2000B	£240.00
KW 202R X	£140.00
KW 204TX	£142.00
KW 105 MATCHING	21.12.00
UNIT	£36.00
KW 103 VSWR UNIT	£12.50
KW EZEE MATCH	£13.50
TRIO SPSD SPEAKER	
TRIO HEADPHONES	
HS4	£6.00
CODAR ATS TX	£19.50
CODAR PR30X	217.30
Pre-selector	£8.50
RAYMART SUPER BA	
CHECKER I-8-35 M/c	
All above items carriage	ovtro 04
An above itellis calliage	CALIA AL

#### AERIAL EQUIPMENT

HALSON WHIPS, £6.87—COILS ONLY, £3.87.

G WHIPS RANGE EX STOCK—LIST.

AR22 ROTATOR, £25-00. Carr. 50p AR10 ROTATOR, £18-00. Carr. 40p AR44 ROTATOR, £40-00. Carr. 50p

KW TRAP DIPOLE, £12-75 KW TRAPS and INS., £4-00.

#### HI GAIN I4AVQ VERTICAL £19.50

75 ohm FEEDER, 4p. per yd. or 100 yd. DRUM, £2.50. P. and p. 20p. 300 ohm FLAT TWIN, 4p. per yd. P. and p. 20p. KW BALUNS, £1.75; HIGH PASS FILTERS, £1.37.

FULL RANGE OF DIE-CAST BOXES, CHASSIS, PUNCHES, METERS, PLUGS, SOCKETS. S.A.E. WITH ENQUIRIES PLEASE.

TEUR RADIO

The Widest Range of Components in the Midlands

Fast Mail Order CHAS. H.

CHAS. H. YOUNG LTD

FV

170-172 Corporation Street, Birmingham B4 6UD

At your service G2AK, G3LAY & G3VFV

Please print your address. No C.O.D. under £1.

'phone 021-236 1635

#### A 2 METRE TX WITH A DIFFERENCE

We are pleased to announce our new 2m. F.M. transmitter, suitable for home station, mobile, or portable, with the following features:—

- All semiconductor, which means instant warmup and no D.C. inverter required when mobile or portable.
- 12 volt D.C. operation at approx. I amp.
- FM by means of phase modulation, with suitable correction, giving a max. deviation of 5 kHz.
- Audio circuit incorporates A.V.C. together with low distortion logarithmic compression.
- All multiplier stages use bandpass coupled circuits for the reduction of spurious outputs.
- Built to a professional specification.
- 10 watts D.C. input to the final power transistor.
- RF output indicator.
- 12 meg. xtal.
- Built in an Imhof case 9" x 7" x 5" with hammer finish in blue and grey.
- Price : £55·25.

Hear this Tx. on the air from G2YH on 144-0686 MHz.

PHOTO ELECTRONIC SERVICES
FOUR WINDS,
ORGANFORD,

POOLE,

**DORSET** 

#### **QSL CARDS**

Designed by specialists Log Books — Reports, etc.

S.A.E. for samples:

NEW FOREST PRINTING CO. LTD.
31 Palfrey Place, Kennington, London, S.W.8.
Telephone 01-735 2020

#### 2 METRE CONVERTERS

A.F.239 R.F. Stage. 2N5245 F.E.T. Mixer Xtal controlled Multiplier Chain. Size  $4'' \times 3'' \times 1\frac{1}{2}''$ . f.F.'s: 4-6, 24-26, 28-30 Mc/s. £10-50 each.

G. R. GRIGG, G3PRX
72 ELMSTONE ROAD, RAINHAM, KENT.
Telephone: Medway 361433

# "DX ZONE MAP"

In four colours, on durable paper for wall mounting, 35in. wide by 25in. deep. Giving essential DX information—bearing and distance of all parts of the world relative to the U.K., the 40 Zone areas into which the world is divided for Amateur Radio purposes, with major prefixes listed separately. Distance scale in miles and kilometres. Time scale in GMT. Marking of Lat./Long. close enough for accurate plotting. Hundreds of place names, mainly the usual ones, and most of the rare islands.

With new revised Prefix List

Price 85p

including postage and special packing in postal tube to avoid damage in transit.

Publications Dept.

Short Wave Magazine Ltd., 55 Victoria Street, London, S.W.1. (01-222 5341/2.)

#### SMALL ADVERTISEMENTS

("SITUATIONS" AND "TRADE")

5p per word, minimum charge £1.00. No series discount. All charges payable with order. Insertions of radio interest only accepted. Add 50% for Bold Face (Heavy Type). Box Numbers 121p extra. No responsibility accepted for transcription errors. Replies to Box Numbers should be addressed to The Short Wave Magazine, 55 Victoria Street. London, S.W.1.

QSL Cards and Log Books, GPO approved, cheapest and best. Prompt delivery.—Samples from Atkinson Bros., Printers, Looe, Cornwall.

TRIO EQUIPMENT: All models and accessories in TRIO EQUIPMENT: All models and accessories in stock for immediate delivery. No-deposit credit can be arranged, with payment spread over two years. Cameras and such taken in part-exchange. We also stock Codar equipment, Joystick antennae and G-Whips for superior Mobile performance. Good commercial amateur-band gear taken in exchange for Cameras or Hi-Fi stereo appartus.—York Photo-Audio Centre, Fossgate, York. (Tel: 56176.)

TRIO JR.500 with Top Band and Calibrator Unit. new, £65.00. Slightly marked, £55.00. Twelve months guarantee. Send s.a.e. for copy "Short Wave Magazine" review.—HOLDINGS Photo-Audio Centre, 39.41 Mincing Lane, Blackburn, BB2.2AF. (Closed on Thursdays). Tel.: Blackburn 59595/6.

OSL Cards for Tx and SWL, Send s.a.e. for samples Stating which type required.—Beaumont, G5YV, Ashfield Avenue, Morley, Leeds. LS27-0QD.

QSL Cards. Two-colour, attractive design, variable features from £3·15 per 1,000 (inclusive). Send foolscap s.a.e. for samples.—ARA Press, 46 Moat Avenue, Green Lane, Coventry.

QSL Cards for Tx, SWL. One to four-colour designs. Good selection. Large s.a.e. for samples.—
Pennington, 100 Ryden Avenue, Leyland, Lancs. PR5-2ZL

NOVEMBER Issue: Appears October 29. Single-copy orders 25p, post free, to reach us by Wednesday, October 27, for posting on October 28.—Circulation Dept., Short Wave Magazine Ltd., 55 Victoria Street, London, S.W.1.

OVERNMENT Surplus Wireless Equipment Handbook: Contains circuits, data, illustrations and valuable information on British and American receivers, transmitters and trans/receivers. Includes modification data for sets and test equipment, also surplus/commercial cross referenced valve and transistor guide. Price £2.85, post/packing 15p.—Myers, 112 Stainburn Crescent, Leeds, 17.

#### READERS ADVERTISEMENTS

2½p per word, minimum charge 50p payable with order. Add 25% for Bold Face (Heavy Type). Please write clearly, using full punctuation and recognised abbreviations. No responsibility accepted for transcription errors. Box Numbers 121p extra. Replies to Box Numbers should be addressed to The Short Wave Magazine, 55 Victoria Street, London, S.W.1.

BARGAINS, Shack Clearance: Heathkit SB-401 transmitter, at £130. R.C.A. 8516L Rx, £130, Heathkit Audio Generator, Type AG-9U, £15. Tiltable lattice tower, 50ft., Ham-M rotator, four-position Aeremote switch with three-band Quad, price £155 delivered U.K. Heathkit VHF FM 4U, £10. LM-14 signal generator, £12. Many other items, send s.a.e. for list. Carriage extra.—Brown, G3JBF, QTHR. Tel. Penkridge (Staffs.) 2912.

#### DERWENT RADIO SCA

SHOWKOOM, 5 COLUMBO	
	S RAVINE, SCARBOROUGH
KW Atlanta VFO £32.00	Codar AT-5 tx £19-50
KW2000B with AC p.s.u. £240-00	Codar T-28 rx £17.50
KW s.w.r. bridge £8-10 Wightraps, pair £2-50 Wightraps hi power £3-50 Hallicrafters SX 133 £145-00 Yaesu FT101 £240-00 Yaesu FL400 £130-00	Codar 250/S mains psu £11.00
Wightness, pair £2.50	Codar 12/KC £2.50
Wightraps of power £3.50	
Yangu ETINI £143.00	Codar PR30 X £9.50
Yaesu FL400 £130-00	Codar CR70A £22.50
Yaesu 200 D.C. p.s.u £45.00	Lafayette HA600 £45.00 Lafayette HA800 £57.00
Yaesu FR500S £145-00	Jackson 4103 dial £1-20
Yangu FT200 4180.00	Jackson 25 pfd variable 22p
Trio JR599 £170.00	Jackson 4103 dial
Trio 9R59DS. New model £47.00	TTC s.w.r. bridge 64.20
Trio JR500Se £65.00	TTC s.w.r. bridge £4-20 TTC s.w.r. bridge £7-20
Trio JR310 £77.00	Amphenol PL259 ptfe 30p
Trio TS510 transceiver £180.00	Amphenol SO 239 25p
Trio SP5D speaker £4.00 Trio HS 4 Headset £5.50	Amphenol reducers 5p
Trio HS 4 Headset £5.50	Amphenol \$O239A ptfe 30p
G Whip 160/80 £9-00 G Whip Tribander £9-00 G Whip Multimobile £15-50	RCA 6LQ6 £2.60
G Whip Tribander £9.00	RCA 6GK6 95p RCA MOSFET 3N 140 85p
G Whip Multimobile £15-50 G Whip basemount £1-50 Unica UR-IA rx £25-00 Halson mobile whip £7-50	KCA MOSFET 3N 140 85p
Unica UR-IA rx £25.00	
Halson mobile whip £7.50	
Halson extra coils £4-40	
Antex 15w, solder iron #1.40	
Antex soldering kit . £2.45	50 misc. diodes 12p
Xtal mics. from £1.35	HC6U xtal sockets 5p
2 way intercom £2.75	HC6U xtal sockets 5p
750 ohm carbon not 1E-	Shure 201 £5.50
RSGB Handbook £3-15	
RSGB Logbook 45p	Shure 444 £12.00
RGSB Callbook 45p	ACOS MIC 43 £1+10
All RSGB Publications in	Magazine binders 72p
stock. Xta <sup>1</sup> s 38.666 MHz £1•40	Egg type insulators 3p
Xta's 38.666 MHz £1-40 Xtals 38.888 MHz 75p	Valve and Transistor Data 75p
Xtals 38.888 MHz 75p Xtals 1000 kHz 75p	Transistor Equivalents 40p Guide to B/cast Stations 50p
Xtals 1000 kHz 75p Eddystone ECI0 Mk. II £74-00	Guide to B /cast Stations 50p
EC10 mains psu £7-75	2ft. telescopic aerial 35p Hammerite. All colours 18p
Codar CRos cabinets £1.30	Hammerite. All colours 18p
Chokes 18H 50 ma 20p Aiwa ARI58 mains/batt. £38-90	All RCA publications in stock : Tx valve manual £1-00
Aiwa ARI58 mains/batt. £38-90	Rx valve manual £1-25
Silver mica, mixed bar 20n	Transistor manual £1-30
Ceramic capacitors mix 20p	Transistor manual £1-30 Transistor servicing £1-79 Hobby ccts manual £1-85
Wirewould resistors mix 30n	
Diecast boxes from 80p	S.C.R. manual 75p
	J.C.N. Manual /3p
Adcola Invader Iron £1.70	S.C.R. manual 75p Power transistors £1.00
Johnson roller coaster 60p	I.C. applications (1.30
Johnson roller coaster 60p	I.C. applications (1.30
Johnson roller coaster 60p	I.C. applications (1.30
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or p	Power transistors £1-99 I.C. applications £1-30 to hear about your trade-in equip- tw, Eddystone, and TW items in adio equipment in part exchange.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or p	Power transistors £1-99 I.C. applications £1-30 to hear about your trade-in equip- tw, Eddystone, and TW items in adio equipment in part exchange.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or a Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MJ	Power transistors £1-69 i.C. applications £1-30 to hear about your trade-in equip- W. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 6066-25, 6054-44 Hz. 36 M Hz. 37 M Hz. 27142. 77190.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over (25 in value /	Flower transistors £1-69 L.C. applications £1-30 e hear about your trade-in equip- W. Eddystone, and TW items radio equipment in part exchange. 6021-11, 6076-67, 606-25, 6054-24 Hz, 36 M Hz, 37 M Hz, 27142, 27120.
Jonnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or: Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office	Fower transistors £1-90 I.C. applications £1-30 e hear about your trade-in equip- iw, Eddystone, and TW items in addio equipment in part exchange 6021-11, 6076-67, 6066-25, 6034-44 Hz, 36 MHz, 37 MHz, 27142, 27120. Due third deposit and up to two years clim. You may also place your orders.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04	Fower transistors £1-90 I.C. applications £1-30 e hear about your trade-in equip- iw, Eddystone, and TW items in addio equipment in part exchange 6021-11, 6076-67, 6066-25, 6034-44 Hz, 36 MHz, 37 MHz, 27142, 27120. Due third deposit and up to two years clim. You may also place your orders.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04	Fower transistors £1-30 L.C. applications £1-30 the hear about your trade-in equip- ity, Eddystone, and TW items radio equipment in part exchange. . 6021-11, 6076-67, 6066-25, 6034-44 Hz, 36 MHz, 37 MHz, 27142, 27120. One third deposit and up to two years (Giro. You may also place your orders 1 0006.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or a Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-09	Fower transistors £1-30 L.C. applications £1-30 the hear about your trade-in equip- ity, Eddystone, and TW items radio equipment in part exchange. . 6021-11, 6076-67, 6066-25, 6034-44 Hz, 36 MHz, 37 MHz, 27142, 27120. One third deposit and up to two years (Giro. You may also place your orders 1 0006.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or r Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 Oct Trie 9759De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00	Fower transistors £1-30 L.C. applications £1-30 the hear about your trade-in equip- ity, Eddystone, and TW items radio equipment in part exchange. . 6021-11, 6076-67, 6066-25, 6034-44 Hz, 36 MHz, 37 MHz, 27142, 27120. One third deposit and up to two years (Giro. You may also place your orders 1 0006.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or I Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Trio JRS00Se £55-00	Fower transistors £1-30 L.C. applications £1-30 the hear about your trade-in equip- ity, Eddystone, and TW items radio equipment in part exchange. . 6021-11, 6076-67, 6066-25, 6034-44 Hz, 36 MHz, 37 MHz, 27142, 27120. One third deposit and up to two years (Giro. You may also place your orders 1 0006.
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or a Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9r59De £35-09 Codar AT5 £14-00 Pye base receiver low £55-00 Trio JRS00Se £55-00 Hallicrafters \$214 £35-00	Fower transistors £1-30  e. hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 6066-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27142, 27120.  One third deposit and up to two years (siro. You may also place your orders 10006.  Trio 9R59DS £38-00  Eddystone 840A £35-00  Heath RG I £27-00  KW 2000B and ad p.s.u. £185-00  KW 2000B and ad p.s.u. £185-00  KW Atlanta and p.s.u £165-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or I Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-00 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Hallicrafters \$214 £35-00 T\$510 as new £160-00	Power transistors £1-30  L.C. applications £1-31  e hear about your trade-in equip- inv. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 606-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27/42, 27/20.  Due third deposit and up to two years Giro. You may also place your orders 10006.  Trio 9R59DS £18-00  Eddystone 840A £15-0e  Heath RG I £27-0e  KW 2000B and ad p.s.u. £185-00  KW 2000B and ad p.s.u. £165-00  KW Atlanta and p.s.u. £165-00  Eddystone EC10 £40-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or I Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-00 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Hallicrafters \$214 £35-00 T\$510 as new £160-00	Fower transistors £1-69  I.C. applications £1-30  e hear about your trade-in equip- iw, Eddystone, and TW items in addio equipment in part exchange.  6021-11, 6076-67, 6066-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27142, 27120.  The third deposit and up to two years (orio. You may also place your orders (0006.  Trio 9R59DS £18-00  Eddystone 840A £15-09  Heath RG I £27-09  KW 2000B and ad p.s.u. £165-00  Eddystone ECIO p.s.u. £165-00  Eddystone ECIO p.s.u. £165-00  Eddystone ECIO p.s.u. £165-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or I Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-00 Codar AT5 £14-00 Pye base receiver low £5-00 Trio JRS0OSe £55-00 Hallicrafters \$214 £35-00 Star \$R550 £30-00 Star \$R550 £30-00	Power transistors £1.08  I.C. applications £1.30  e hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 606-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27142, 27120.  Due third deposit and up to two years Giro. You may also place your orders 10006.  Trio 9R99DS £18-00  Eddystone 840A £15-0e  Heath RG I £27-0e  KW 2000B and ad p.s.u. £185-00  KW 4tlanta and p.s.u. £165-00  Eddystone ECI0 £40-00  Sommerkamp FT150 £155-00  Lafayette HA350 £55-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good k particular. We can offer cash, or: Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9r59De £14-00 Pye base receiver low £5-00 Trio JR \$100Se £160-00 Star \$R550 £160-00 Star \$R550 £20-00 Trio JR \$10 mint £25-00 Trio JR \$10 mint £25-00 Trio JR \$10 mint £25-00	Power transistors £1.08  I.C. applications £1.30  e hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 606-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27142, 27120.  Due third deposit and up to two years Giro. You may also place your orders 10006.  Trio 9R99DS £18-00  Eddystone 840A £15-0e  Heath RG I £27-0e  KW 2000B and ad p.s.u. £185-00  KW 4tlanta and p.s.u. £165-00  Eddystone ECI0 £40-00  Sommerkamp FT150 £155-00  Lafayette HA350 £55-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value, C to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 97-59De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Trio JR300se £36-00 Star \$R550 £30-00 Star \$R550 £25-00 Trio JR 310 mint £65-00 Pye base receiver hi band £5-00	Power transistors £1-09  I.C. applications £1-30  e hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange.  6021-11, 6076-67, 606-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27/142, 27/20.  Due third deposit and up to two years Giro. You may also place your orders 10006.  Trio 9R99DS £25-09  Eddystone 840A. £25-09  Hatt RG 1  KW 2000B and ad p.s.u. £15-00  KW 2000B and ad p.s.u. £165-00  KW 2000B and ad p.s.u. £165-00  KW 2000B and ad p.s.u. £155-00  Sommerkamp F1150 £55-00  KW 41santa and p.s.u. £28-00  Sommerkamp F1200B £200-00  Sommerkamp F1200B £200-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value, C to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 97-59De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Trio JR300se £36-00 Star \$R550 £30-00 Star \$R550 £25-00 Trio JR 310 mint £65-00 Pye base receiver hi band £5-00	Power transistors £1-30 e. hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 6066-25, 6054-44 Hz, 36 M Hz, 37 M Hz, 27142, 27120. One third deposit and up to two years Giro. You may also place your orders 1 0006. Trio 9R59DS £38-00 Eddystone 840A £35-00 Eddystone 840A £35-00 KW 2000B and ad p.s.u. £185-00 KW 41041ata and p.s.u. £185-00 Eddystone EC10 £40-30 Sommerkamp FT150 £155-00 Lafayette HA350 KW 41040-151-161-161-161-161-161-161-161-161-161
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value, C to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 97-59De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Trio JR300se £36-00 Star \$R550 £30-00 Star \$R550 £25-00 Trio JR 310 mint £65-00 Pye base receiver hi band £5-00	Fower transistors £1-30  a. L.C. applications £1-30  b. hear about your trade-in equip- i.W. Eddystone, and TW items in radio equipment in part exchange.  6021-11, 6076-67, 606-25, 6054-24, 27120.  Due third deposit and up to two years  Ciro. You may also place your orders 10006.  Trio 9R59DS £38-00  Eddystone 840A £15-09  KW 2000B and ad p.s.u. £165-00  KW Atlanta and p.s.u. £165-00  Eddystone Eddystone £15-00  KW Atlanta and p.s.u. £165-00  Eddystone FTD £155-00  LGW Atlanta and p.s.u. £165-00  Eddystone Eddystone £155-00  KW Atlanta and p.s.u. £165-00  Sommerkamp FTD £155-00  LGW Atlanta FTD £155-00  LGW Atlanta FTD £155-00  LGW Atlanta FTD £155-00  LGW Atlanta FTD £155-00  LGW ATLANTE £150-00  Sommerkamp FTD £150-00  Sommerkamp FTD £155-00  Sommerkamp FTD £150-00  Sommerkamp FR100B £20-00  Sommerkamp FR100B £20-00  Sommerkamp FR100B £20-00  Sommerkamp FR100B £20-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good k particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9r59De £35-00 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Trio JR \$300 £25-00 Trio JR \$30 £25-00 Trio JR \$310 mint £65-00 Ranger p.s.u./mod. unit £3-00 RCA panadaptor £20-00 Pye 4 channel rx £60-00 Pye 4 channel rx £60-00 Pye 50 Pyersity switch £30-00 CGRE Diversity switch £30-00	Fower transistors £1-30  a. L.C. applications £1-30  b. hear about your trade-in equip- i.W. Eddystone, and TW items in radio equipment in part exchange.  6021-11, 6076-67, 606-25, 6054-24, 27120.  Due third deposit and up to two years  Ciro. You may also place your orders 10006.  Trio 9R59DS £38-00  Eddystone 840A £15-09  KW 2000B and ad p.s.u. £165-00  KW Atlanta and p.s.u. £165-00  Eddystone Eddystone £15-00  KW Atlanta and p.s.u. £165-00  Eddystone FTD £155-00  LGW Atlanta and p.s.u. £165-00  Eddystone Eddystone £155-00  KW Atlanta and p.s.u. £165-00  Sommerkamp FTD £155-00  LGW Atlanta FTD £155-00  LGW Atlanta FTD £155-00  LGW Atlanta FTD £155-00  LGW Atlanta FTD £155-00  LGW ATLANTE £150-00  Sommerkamp FTD £150-00  Sommerkamp FTD £155-00  Sommerkamp FTD £150-00  Sommerkamp FR100B £20-00  Sommerkamp FR100B £20-00  Sommerkamp FR100B £20-00  Sommerkamp FR100B £20-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value, C to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trio 97-59be £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Hallicrafters \$214 £35-00 Star \$R550 £30-00 Star \$R550 £30-00 Star \$R550 £25-00 Trio JR 310 mint £65-00 Pye base receiver hi band £5-00 RCA panadaptor £20-00 RCA panadaptor £20-00 GCARE Devarity switch £7-00	Power transistors £1.68  I.C. applications £1.38  e hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 606-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27/42, 27/20.  Due third deposit and up to two years Giro. You may also place your orders 10006.  Trio 9R59DS £18-00  Eddystone 840A. £15-0e  Heath RG I £27-0e  KW 2000B and ad p.s.u. £185-00  KW 2000B and ad p.s.u. £185-00  KW 41anta and p.s.u. £165-00  KW 44tanta and p.s.u. £165-00  Sommerkamp F1150 £55-00  KW Vanguard 160-10m £28-00  Sommerkamp F12008 £90-00  Sommerkamp F1008 £90-00  Sommerkamp F1008 £90-00  Swan Cygnet £170-00  Eddystone 680X £65-00  Eddystone 680X £65-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good k particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. 6 to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 97-99De £35-00 Codar ATS £35-00 Codar ATS £35-00 Trio JRS00Se £35-00 Trio JRS00Se £35-00 TS510 as new £160-00 Star SR550 £10-00 Eagle Rx 80 £25-00 Trio JR 310 mint £65-00 Pye base receiver hi band £5-00 Ranger p.su./mod. unit £1-00 RCA panadaptor £20-00 GCRE Diversity switch £3-00 Codar PR0X £4-00 Codar PR0X £4-00	Fower transistors £1-09  I.C. applications £1-30  e hear about your trade-in equip- i.W. Eddystone, and TW items in radio equipment in part exchange.  6021-11, 6076-67, 606-25, 6054-27, 6054-41, 27120.  Due third deposit and up to two years Giro. You may also place your orders 10006.  Trio 9R59DS £38-00  Eddystone 840A £15-09  Heath RG 1 £27-09  KW 2000B and ad p.s.u. £165-00  Eddystone Eddystone £05-00  Eddystone Eddystone £05-00  Eddystone £05-00  KW Atlanta and p.s.u. £165-00  Eddystone Eddystone £05-00  Sommerkamp F100B £20-00  Sommerkamp F200B £20-00  Sommerkamp F100B £20-00  Sommerkamp F100B £20-00  Swan Cygnet £170-00  Eddystone 680X £65-00  Eddystone 680X £65-00  Radio Cub Tx £28-00  Radio Yenet £65-00  Radio Yenet £65-00  Reddystone 338 rx £12-00  Eddystone 338 rx £12-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good k particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. 6 to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 97-99De £35-00 Codar ATS £35-00 Codar ATS £35-00 Trio JRS00Se £35-00 Trio JRS00Se £35-00 TS510 as new £160-00 Star SR550 £10-00 Eagle Rx 80 £25-00 Trio JR 310 mint £65-00 Pye base receiver hi band £5-00 Ranger p.su./mod. unit £1-00 RCA panadaptor £20-00 GCRE Diversity switch £3-00 Codar PR0X £4-00 Codar PR0X £4-00	Fower transistors £1-80 e. hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 6066-25, 6054-44 Hz, 36 M Hz, 37 M Hz, 27142, 27120. One third deposit and up to two years (siro. You may also place your orders 10006. Trio 9R59DS £38-00 Eddystone 840A £35-00 Heath RG I £27-00 KW 2000B and ad p.s.u. £185-00 KW Atlanta and p.s.u. £185-00 Eddystone ECI0 Sommerkamp FT150 £155-00 Lafayette HA350 £55-00 CW 430-40-40-40-40-40-40-40-40-40-40-40-40-40
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good k particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 Ml H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Trio JR\$30Os £56-00 Star \$R\$50 £36-00 Star \$R\$50 £35-00 Trio JR\$310 mint £65-00 Pye base receiver hi band £5-00 Ranger p.s.u./mod. unit £3-00 RCA panadaptor £20-00 Pye 4 channel rx £4-00 Codar PR\$30X £16-00 Codar PR\$30X £16-00 Codar PR\$300 £16-00 Labgear LG\$300 £16-00 Labgear LG\$300 £16-00 Labgear LG\$300 £16-00 Labgear LG\$300 £16-00 Codar CR45 £9-00	Fower transistors £1-80 e. hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange. 6021-11, 6076-67, 6066-25, 6054-44 Hz, 36 M Hz, 37 M Hz, 27142, 27120. One third deposit and up to two years (siro. You may also place your orders 10006. Trio 9R59DS £38-00 Eddystone 840A £35-00 Heath RG I £27-00 KW 2000B and ad p.s.u. £185-00 KW Atlanta and p.s.u. £185-00 Eddystone ECI0 Sommerkamp FT150 £155-00 Lafayette HA350 £55-00 CW 430-40-40-40-40-40-40-40-40-40-40-40-40-40
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. 6 to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Hillcrafters \$214 £35-00 Hillcrafters \$214 £35-00 Hillcrafters \$214 £35-00 Fig. 18 30 £30-00 Ranger p.su. /mod unit £3-00 Ranger p.su. /mod unit £3-00 RCA panadaptor Pye 4 channel rx £4-00 GCRE Diversity switch £3-00 Codar PR30X £16-00 KW2000A £16-00 Codar CR45 £30-00 Codar CR45 £30-00 Codar CR45 £30-00 Contral Electronics 100y.	Fower transistors £1-30  e. hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange.  6021-11, 6076-67, 6066-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27142, 27120.  One third deposit and up to two years (siro. You may also place your orders 10006.  Trio 9R59DS £38-00  Eddystone 840A £35-00  Heath RG I £27-00  KW 2000B and ad p.s.u. £185-00  KW 42000B and ad p.s.u. £185-00  Eddystone EC10 £40-09  Eddystone EC10 £40-09  Eddystone EC10 £55-00  Lafayette HA350 £55-00  Lafayette HA350 £55-00  Sommerkamp FT150 £155-00  Lafayette G80X £66-00  Sommerkamp FR100B £80-00  Sommerkamp FR100B £80-00  Swan Cygnet £170-00  Eddystone 680X £65-00  Panda Cub Tx £28-00  Panda Cub Tx £28-00  RA16 vbf receiver £65-00  Eddystone 358 rx £12-00  Murphy B40 £15-00  Murphy B40 £15-00  Murphy B40 £15-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 MI H.P. on any items over £25 in value. ( to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 97-59De £35-00 Codar AT5 £14-00 Pye base receiver low £5-00 Hallicrafters \$214 £35-00 Trio JR\$30Os £56-00 Bagle Rx 80 £5-00 Trio JR\$310 mint £65-00 Pye base receiver hi band £5-00 Ranger p.s.u./mod. unit £3-00 RCA panadaptor £5-00 Pye A channel rx £4-00 Codar PR30X £160-00 Codar PR30X £160-00 Codar CR45 £100-00 Codar LG300 £160-00 Codar LG300 £160-00 Codar CR45 £9-00 Central Electronics 100v. am/ssb/fsk/Tx £150-00	Fower transistors £1-30  e. hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange.  6021-11, 6076-67, 6066-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27142, 27120.  One third deposit and up to two years (siro. You may also place your orders 10006.  Trio 9R59DS £38-00  Eddystone 840A £35-00  Heath RG I £27-00  KW 2000B and ad p.s.u. £185-00  KW 42000B and ad p.s.u. £185-00  Eddystone EC10 £40-09  Eddystone EC10 £40-09  Eddystone EC10 £55-00  Lafayette HA350 £55-00  Lafayette HA350 £55-00  Sommerkamp FT150 £155-00  Lafayette G80X £66-00  Sommerkamp FR100B £80-00  Sommerkamp FR100B £80-00  Swan Cygnet £170-00  Eddystone 680X £65-00  Panda Cub Tx £28-00  Panda Cub Tx £28-00  RA16 vbf receiver £65-00  Eddystone 358 rx £12-00  Murphy B40 £15-00  Murphy B40 £15-00  Murphy B40 £15-00
Johnson roller coaster 60p Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Xtals. the following all at 40p each 6400, 6048-9, 7072-92, 7062-5, 100 M H.P. on any items over £25 in value. 6 to pay. Payments may be by Post Office by Giro. Our account number 64 04 Trie 9759De £35-09 Codar AT5 £14-00 Pye base receiver low £5-00 Hillcrafters \$214 £35-00 Hillcrafters \$214 £35-00 Hillcrafters \$214 £35-00 Fig. 18 30 £30-00 Ranger p.su. /mod unit £3-00 Ranger p.su. /mod unit £3-00 RCA panadaptor Pye 4 channel rx £4-00 GCRE Diversity switch £3-00 Codar PR30X £16-00 KW2000A £16-00 Codar CR45 £30-00 Codar CR45 £30-00 Codar CR45 £30-00 Contral Electronics 100y.	Fower transistors £1-80  e. hear about your trade-in equip- iw. Eddystone, and TW items in radio equipment in part exchange.  6021-11, 6076-67, 6066-25, 6054-44  Hz, 36 M Hz, 37 M Hz, 27142, 27120.  One third deposit and up to two years (siro. You may also place your orders 10006.  Trio 9R59DS £38-00  Eddystone 840A £35-00  Heath RG I £27-00  KW 2000B and ad p.s.u. £185-00  KW 42000B and ad p.s.u. £185-00  KW 4200B and ad p.s.u. £185-00  Eddystone EC10 £40-09  Eddystone EC10 £40-09  Eddystone EC10 £55-00  Lafayette HA350 £55-00  Lafayette HA350 £55-00  Sommerkamp FT150 £155-00  Lafayette G80X £66-00  Sommerkamp FR100B £80-00  Sommerkamp FR100B £80-00  Sommerkamp FR100B £80-00  Swan Cygnet £170-00  Eddystone 680X £65-00  Panda Cub Tx £28-00  Panda Cub Tx £28-00  RA16 1974 receiver £15-00  Murphy B40 £15-00  HRO /a.c. p.s.u./gc coils £25-00

Please add extra for carriage. S.A.E. lists. 28 Hillcrest Avenue, Scarborough, Yorks.

TRANSISTOR POCKET BOOK

by R. G. HIBBERD, B.Sc., M.I.E.E., Sen.M.I.E.E.E.

This addition to Newnes series of technical pocket books provides a comprehensive guide on the characteristics and use of the various types of transistor that have come into use in recent years. It is based on the junction transistor, fully taking into account the latest varieties including the epitaxial planar, field effect, metal-oxide silicon and thin film types. Earlier chapters describe the principles of operation, transistor characteristics, equivalent circuits and parameters and establishing suitable D.C. operating conditions. A chapter is included on the manufacture of transistors, so that the effect of the basic methods of fabrication and types of junction on transistor characteristics is clearly understood. The operation and characteristics of associated semiconductor devices used in conjunction with transistors, such as the junction rectifiers used in conjunction with transistors, such as the junction rectifier and phototransistor are also described. Low level, high power and high frequency amplifieration; oscillator, switch and D.C. amplifier circuits; radio receivers and power supply arrangements are all covered in separate chapters, practical circuits complete with transistor types and component values being included for these various applications. The book also includes notes on handling and testing transistors, and a chapter on solid state circuit techniques.

SHORT WAYE MAGAZINE

SHORT WAYE MAGAZINE

55 VICTORIA STREET, LONDON, S.W.I

POWER I.C. for R.F. TRIGGERED C.W. Monitor. 5 for 62p untested with Data Sheets.

TCC MICRO-MIN TANTALUM CAPACITORS. 07uf 20v.w., 5p each 50p doz.

STC SUB-MIN TANTALUM CAPACITORS 33uf 10v.w., 5p each, 50p doz.

STC SUB-MIN TANTALUM CAPACITORS 33uf 10v.w., 5p each, 50p doz.

STC SUB-MIN 5uf 25v.w. TANTALUM CAPACITORS, 5p each, 50p doz.

UNION CARBIDE SUB-MIN TANTALUM CAPACITORS 47uf 6v.w., 5p each, 50p doz.

MULLARD FETS BFW 10 (Similar to 2N 3819), 25p each, 5 for £1.

MULLARD FETS BFW 11 at 25p each.

Transistor Disc Ceramics. 18bf, 3·3pf 50v.w., 4·7uf 100v.w., 10pf 50c.w., 100of 100v.w., 1000pf 50v.w., 0·1uf 18v.w., 0·22uf 18v.w., 0·47uf 12v.w., 1uf 18v.w., 1uf 20v.w., 2·2uf 3v.w. All at 10 for 15p

PHILIPS CONCENTRIC 3-30pf TRIMMERS at 8p each.

RCA 115 watt 15 amp. 35 volt SILICON NPN TRANSISTORS, type 40363 at 30p each.

14 Lead Dual in Line NPN Transistor package containing one matched pair plus 3 single Transistors. All 600 MHz untested with Data, 5 for 50p.

TEXAS TRANSISTOR PNP GM 669A, 500 MHz at 10p.

SUB-MIN AIR SPACED 5pf TRIMMERS at 8p each, 25p doz.

SPECIAL DISC CERAMICS MINIATURE 500pf 8 K.V.W., 20p doz.

SPECIAL DISC CERAMICS MINIATURE 500pf 8 K.V.W., 20p doz.

SPECIAL DISC CERAMICS MINIATURE 500pf 8 K.V.W., 20p doz.

SPECIAL DISC CERAMICS MINIATURE 500pf 8 K.V.W., 20p doz.

SPECIAL PNP TRANSISTOR offer GET 872. 50 for £1 or GT 45, 100 for £1.

GENERAL PURPOSE P CHANNEL M.O.S. FET, 10p each with suggested circuit booklet

# J. BIRKETT

Radio Component Suppliers,

25 THE STRAIT, LINCOLN
Telephone: 20767

# HAMGEAR ELECTRONICS

P.M.II This is a preselector covering 1.8 to 32 Mc/s. complete with a gain of up to 25 dBs. With a built-in antenna coupler this will improve almost any communication receiver/antenna combination, £8.30. Complete with internal mains power pack. Also available with a built-in xtal 1 Mc. Calibrator, £10.25.

**P.M.** III A 160 metre converter, I.F. of 7 Mc/s. using three F.E.T. transistors. Built-in antenna coupler, £9.00.

P.M. IV A I Mc. crystal calibrator with modulation for easy recognition of the marker points, £4.50.

**P.M. V** As the P.M. IV except it has 1 Mc. and 100 kc/s. with modulation, £6.50.

P.M. VI Specification as P.M. II with the addition of a built-in top band transistor converter, £13-50. Also available with a built-in I Mc. calibrator, £16-50.

P.M. VII A cascode preselector giving 18 dBs. gain and covering 12 to 30 Mc/s. using two F.E.T.'s for minimum noise and cross modulation, £7.25.

P.M. VIII A calibrator with I Mc/s, 100 Kc/s, 10 Kc/s and modulation. Zero beat facility. £10-75.

2½p stamp for illustrated leaflets

29 CARLYLE ROAD, NORWICH

SELLING: K.W. Victor AM/CW Tx, 120 watts, £25 TCS-6 transmitter, £10. Converter for 4 metres, £4. Buyers to collect.—Cole, G3OHK, 25 Causeway Road, Seaton, Workington, Cumberland.

YOUR Price Paid for an Eddystone 750 receiver in excellent condition. For Sale: Portable X-Ray unit, £30. Or Exchange Communications Receiver.—Taylor, G3FK, QTHR, or ring Broadstone (Dorset) 2631.

FOR SALE: Heathkit HW-32A, coverage 14.05 to 14.35 MHz, about 12 months old, demonstrated mobile and delivered to within 30 miles of North London, price £40.—Box No. 5034, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

**M**ANUALS: For SP-600, AR-8516L, PTC-2107, Collins J4, £2; B.40, CR-150, RA-17, £1·75; CR-100, CR-300, S.27, S.36A, AR88LF, £1·25.—Brooks, 5 Farrant House, Winstanley Road, London, S.W.11.

SALE: Mosley TA-32Jr. with AR22R rotator, £25 carriage at cost. Any offers for a Jap 9 MHz xtal filter, with matching USB/LSB carrier crystals, brand new, as KVG XF9B specification? (Lincs.).—Box. No. 5035, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SALE: Teleprinter 7B and two auto-transmitters, including spare motors and governors, with other 7B teleprinter spares, all in good condition, £20 The Lot, buyer collects. WANTED: Teleprinter Type 75RP/TK.—Kanaar, 14 Queens Road, Belmont, Sutton, Surrey. (Tel: Vigilant 6415.)

**S**ELLING Up: Variety of good gear including a Lafayette HA-600 in mint condition, Eddystone 898 dials, and such.—Ring Scott, 01-578 0653 (London)

SALE: Heath SB-301E, SSB and AM filters, with SP-600 speaker, £100. Also Mosley TA-31Jr aerial, £6. Prefer buyers to collect.—Williams, 39 Clockhouse Way, Braintree, Essex, CM7-6RD.

FOR SALE: KW-2000B, with AC/PSU, in perfect and unmarked condition, little used as "second rig" on Top Band only, £175, carriage paid. Marconi receiver, HR-24, SSB diversity, offers?—McCaig GM3BQA, Woodlands, Whitekirk Road, North Berwick, East Lothian, Scotland.

SELLING: K.W. Viceroy Mk.II, CW/SSB Tx, with AC/PSU, £45 or near offer—also a Hammarlund HQ-170A receiver at £60 to £70 or near. (London area).—Box No. 5036, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

FOR SALE: Most parts for a Linear, including transformer, Viceroy-type cabinet, two 4CX250B's, with relays, etc., £12. Nombrex Signal Generator, Model 27, £6. German Papst motor, 110v., silent running, good for blower, £1.50. Meters: 0.50v., 75p; 0.1 mA, 75p; 0.150 mA, 75p; 0.80 mA fwd with 0.20 mA negative, 2½in. square, nice job, new, £1.25. Also Mosley A.215 15-metre Beam, 8 months' use, in that time 85 countries worked, could be re-tuned for 10 metres, £11, carriage extra.—Jones, GW3TMP, QTHR.

SELLING: Eddystone S.640 receiver, in good condition, price £22. Also two-metre 10w. CW Tx and PSU, £12. — Smith, 1 Back Street, Mundesley, Norwich, Norfolk, NOR.33Y.

FOR SALE: Eddystone EB.35 receiver, transistorised, coverage 350 kHz to 22 MHz, AM/FM, with 230v. PSU and batteries and Sinclair Q14 speaker, in good condition, £35. — Dring, 3 Newtonside, Burfield Road, Old Windsor, Berks.

**S**ALE: BC-221 frequency meter in good working order, with original calibration charts, £22.—Bell, G3RTB, Watchtower House, The Ridgeway, London, N.W.7. (Tel: 01-959 6773.)

WANTED: Electroniques valve-type front end QP.166, must be in excellent condition.—Ring Baker, Northampton 51865.

FOR SALE: Eddystone EC-10 receiver, with mains and battery units, little used, at £40.—Telford, 16 Cragside Crescent, Kirkstall, Leeds 5, Yorkshire.

LEARANCE At G8BSR: Pye Reporter Tx/Rx, Suitable two metres, good condition, £4. Pye Cambridge RF section on 2m., new, £4. Pye Vanguard RF section with QQV03-20A, working 2m., £6. Two-metre receiver fully tunable 144 to 146 MHz, superb Rx with mains PSU, £11-50. Bendix RA-1B Rx, mains PSU, coverage 50 kHz to 15 MHz, excellent order, £12. B.44 Mk.III, 12-volt, brand new, suitable 4 metres, £8.50. Pair VHF Tx/Rx nortable stations hand sate £8.50. Pair VHF Tx/Rx portable stations, hand-sets suitable for 4m. or 10m., complete with batteries and aerials, £7.50 each. Chinese-copy K.W. Vanguard AM Tx, 60 watts, 10 to 80 metres, 807 PA, pair 807 modr., with mains PSU, £15.—Pugh, G8BSR, QTHR, Tel: Wolverhampton 29201.

SELLING: BC-639A VHF receiver, tunable 80 to 150 MHz; BC-348 Rx, £12; B.46 receiver, £8; National NC-100 receiver, £12; four Hudson transceivers on 72 MHz, £3-50 each; Hudson 72 MHz base station, £8; Pye Ranger 6-channel Tx/Rx on 170 MHz, transistorised PSU but no xtals, £7; Cossor signal generator Type 52A, with charts, £5-10. For Electronic Organ constructors: Enough complete equipment to huild two manual organs, price £40 The Lot. Carbuild two manual organs, price £40 The Lot. Carriage extra, but prefer buyers see and collect.—Sheedy, G8EWO, 24 Thornwood Road, London, Sheedy SE13-5RG.

WANTED: Bandspread coil pack, 20m., for National HRO. Have 40m. and 80m. ditto for Exchange, with cash adjustment if necessary—or would buy if price right.—Smith, 3 Hillbeck Way, Greenford, Middx.

FOR SALE: R.C.A. AR88LF receiver, in good condition, with S-meter, speaker and manual, price £32.50 delivered within 75 miles Bradford.—Knox, Bradford 630266.

WANTED: Fully transistorised Transceiver with integral power supply, to GPO marine specification, for 2182 kHz or 156.8 MHz, AM operation. Details and price.—Box No. 5032, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.


OFFERS INVITED: Seco Antenna Tester, Model 520A with manual. B. & W. electronic switch, Model 250-39. Heathkit factory-built GEO with coils. Dow-Key relays, new, 52-0hm DK60-G, 220v. AC; DK60-2C, 220v. AC; used DK60-G & C, 110v. AC. Hy-Gain traps for 40-80m. Waters Protax coaxial switch Model 375. Waters Compreamp Model 359. Tenna switch, unused. HRO knob, like new. BM-3 crystal mike; Acos-22; Calrad DM-17. 58ft. Belden 8-core cable for Ham-M control. Original manuals for AR88D and SX-101A. Leach (U.S.A.) 110v. antenna shorting relay. Advance (U.S.A.) Type 400 115v. 50-60 Hz relay on ceramic base, beautiful job. Advance 110v. AC 50-60 Hz antenna relay. Weston antenna current meter, dial marked 0.10. Brand new 0-300v. DC meter Model KR-52. Mosley all-band whip antenna. Brand new unused Stolle de luxe rotator and indicator. Grundig tape recorder, Type TK-55.-Box No. 5033, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

FOR SALE: Creed 54 with reperforator, £16. Creed 54, £12·50. Creed 7B, £10. Creed 54 receiver, £7·50. Creed 7TR reperforator, £7·50. Creed 6S/5M auto, £12·50. Siemens T-Loch 15 printing reperforator, £10.—Wigg, G6JF, Yabbacombe Farm, Kingsbridge, South Devon. (Tel: Loddiswell 324.)

WANTED: PCR-3 receiver, in working order; please write in first instance (postage refunded). SEL-LING: R.1475 Rx, with original PSU for 250v. AC or 12v. DC operation, £12. Class-D Wavemeter, modified for mains working, £6.—Dunhill, 16 Fernleigh Close, Blackpool, FY2-OHS, Lancs.



# Listen to the world with **Eddystone**

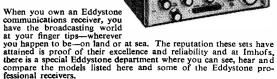

Same day despatch to any part of the world; free delivery in the U.K.; plus after sales service for which Imhofs and Eddystone are world famous.

EDDYSTONE EC10 Mark II transistorised communications receiver. A de-luxe version of this famous design now incorporating "S" meter and limited fine tuner. £79.00.

EDDYSTONE 830/7 wide range communications receiver. A high grade HF/MF receiver covering 300 kHz—30 mHz in 9 ranges with crystal control facilities. Many satisfied users acclaim it as "the best ever". £340.00.

Due to professional commitments the Eddystone range available to the general public is limited for the time being. However, new models are under development—keep an eye on our advertisements for advanced information. Meantime, the EC10 Mark II continues to prove the most popular medium priced receiver ever introduced by



MAIN EDDYSTONE DISTRIBUTORS



Dept: 11/10

112-116 New Oxford Street, London, WC1A 1HJ Tel.: 01-6367878

#### BURNS ELECTRONICS

It is regretted that with effect from November 1, 1971, prices of the Crystal Calibrator, Wavemeter and Frequency Standard will be increased by approximately 10% in order that the present high standard of manufacture can be maintained. However it has been made possible by a Pass Filter, FET Converter and FM Detector constant and to reduce that of the Test Oscillator. All orders received before November I to be at

CRYSTAL CALIBRATOR CC-10. Battery operated solid state using low power integrated circuits to generate 1 MHz, 500 kHz, 100 kHz, 500 kHz, 10 kHz and 5 kHz and harmonics to above 500 MHz. Stability better than ±10ppm stability. Heterodyne wavemeter and Mod monitor functions.

WAVEMETER TC-101. Absorption wavemeter covering 0-8-480 MHz in six overlapping ranges with sensitive meter and detector circuit. Insulated probe. Matching style to calibrator. Price: £16-45

FREQUENCY STANDARD SD-II. Provides separate outputs of I MHz and 10 MHz phase locked to Droitwich 200 kHz transmission. Battery operated, solid state with self contained aerial. Price: £69-45

LOW PASS FILTER FL2/FL4. Reduce BC1/TVI, available 50 or 75 ohms, Passband loss less than † dB, stopband loss 50 dB minimum.
Price: £6-20

FET CONVERTER FC2/FC4. New design using protected dual gate MOSFETS for low noise and high gain. 4-6 MHz and 28-30 MHz standard IP's but any in range 2-30 MHz to order. Operates from 9 volt D.C. supply and has reverse polarity protection. Price: £16-20

TEST OSCILLATOR TO-701. Crystal controlled oscillator in small hand held case for IF alignment, calibration, etc. Any single frequency 100 kHz to 100 MHz. Battery operated. Quantity 5+ Price: £10-00 Quantity 5+ Price: £8-90

FM DETECTOR FMD-1. Add on unit using high gain integrated circuit and low distortion discriminator. Any IF in the range 450 kHz to 1 MHz. Supplied in kit form or made and tested. Kit Price £6-70 Tested Price: £8-20

Many new components added to our stock list. Large S.A.E. for details or cash with order to :

**BURNS ELECTRONICS** THE COTTAGE, 35, BEULAH HILL, LONDON, S.E.19

# GRAHAM NEWBERY

(REG WARD G2BSW)

WE ARE OFF	CIALL	TAP	POIN	TED I	K.W. /	AGEN	TS FOR
THE SOUTH	MF21	(Som	erset,	Dorse	it, Dev	ron, C	ornwail)
KW Atlanta v	with p.s	s.u.					£200-00
Remote VFO							€34.00
KW 2000B wi	th p.s.u						€240.00
Remote VFO			•••				£36.00
KW 202 Rece	iver	•••	•••	•••			£140.00
Matching Spea	ker						£8.00
KW 204 Tran	smitter						£142.00
KW 1000 Line							£135.00
KW 101 VSW		er (52	or 75	opm)			£9.25
KW103 VSWR	Meter	and Co	mbine	d Powe	or Mare		£12.50
KW E-Z Mate	ch. 10	-80m.	ATU			•• •••	£13.50
KW 105 Com	bined	E-Z M	larch.	VSWR	India		213.30
Dummy Loa	d and A	ntenns	Swite	h for A	Outle	ator,	£36.00
KW Trap Dip	ole 70'	75 ohn	n Twin	Feede	Cone		£12.00
KW Trap Dipo	ale 97'	Coavial	Feeds	r			£12.75
				•••••	•••	•••	E12.13
EDDYSTONE							
ECIO Mk. II		•••	•••	•••	•••	•••	£79·00
EA12							£205 · 00
WE ARE	THE D	DISTRIE	BUTO	RS OF	EDDY	STON	E
PROFESSION	NAL R	CEIVE	RS FC	R THE	<b>SOU</b>	TH W	EST.
Trio Equipment	4 Madal	00500	C £47	EA 11	. 4 11-		- 45
			/3 E4/	3U. IT	3 7 me	aapnor	162 ED - 20
SHURE MICR	OPHO	NES					
Model 444	•••		•••				£14.40
Model 201	•••				•••	•••	£6.00
Model 202							66.60

R.C'A. VALVES for KW and Heathkit equipment. 6146, 6146B, 611F5, 6LQ6, 6GE5, 6EA8, 6GW8, 6GK6, 6CM6, 6CL6, 6CB6, 6BN8, 611S6, 6EW6, 12BA6, 12BE6, 12B26, etc. and many other types.

TRADE INS WITH PLEASURE. OUR STOCK OF GOOD SECOND HAND EQUIPMENT CHANGES DAILY - LET US KNOW YOUR REQUIREMENTS.

WE STOCK R.S.G.B. PUBLICATIONS, LOG BOOKS, Etc. HP. TERMS AVAILABLE.

AXMINSTER — DEVON Telephone: 3163

OFFERING: KW-2000B CW/SSB transceiver; Eddvstone 940 receiver; T.C.C. SWR meter.-Dawson, ET5BT, 33 Ardlea Road, Dublin, 5, Eire.

WANTED: In mint condition, AR-8516L receiver. please state details and price, including carriage in suitable parkaging to Holland.—Hendriksen, Lintelestraat 9, Zutphen, Holland.

FOR SALE: Trio 9R-59DE receiver, as new, including voltage stabiliser and built in crystal calibrator, £30. Eagle IP-7 inter-com., complete with two sub-station units, as new. £13 or near offer.—Burrows, 23 Birch Avenue, Ashton-on-Ribble, Preston, PR2-1JU, Lancs.

SALE: Brand new Japanese version Lafayette HA-460 10m. transceiver, 20-watt 2E26 final, crystal or VFO control, complete with p-t-t microphone, 12v. DC and 240v. AC PSU's integral, for fixed or mobile working (vehicle mounting brackets supplied), cost £75 but first £45 will secure. Prefer buyer collects.—

224 Nino Mila Rida Wakingham Barks. Beestin, 334 Nine Mile Ride, Wokingham, Berks. (Tel: Eversley 3674, after 6 p.m.).

WANTED: Cabinet, front panel and base-plate for W Marconi CR-150 receiver; scrap Rx considered if price right. Please give details.—Lang, 4 Lynton Road, Burnham-on-Sea, Somerset.

FOR SALE: Eddystone EA-12 receiver, coverage 10 to 160m. bands, with all facilities, including CW and slot filter, as new, £105 or near offer.—Davis, G3VTR, 49 Watersmeet, Harlow (33084), Essex.

SWL Clearing Shack, has for disposal cabinets, Swith Clearing Shack, has for disposal cabinets, chassis, mains transformers, speakers, vibrator power supplies and such; also back-number volumes "Short Wave Magazine" and "RSGB Bulletin". Callers welcome at weekends or after 6 p.m. evenings.—Lowson, 4 Julia Place, Old Brechin Road, Forfar, Angus, Scotland.

WANTED: Ex-R.A.F. T.1154 transmitter, less PSU, complete and in working order, £5 offered, will pay carriage extra.—Box No. 5037, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

SALE: Hudson AM-108 Mk.II mobile transceiver, with three channels around 70 MHz, working, unmodified, complete with all crystals, handset, mobile mount and manual, price £12.50.—Michaelson, G3RDG, QTHR, or ring 01.455 8831 (London).

SALE: Eddystone S.640 receiver, with S-meter, £20. Codar CR-70A Rx, £15. Codar PR-30 pre-selector, £5. Codar RQ-10 Q-multiplier, £5. Buyers to collect evenings.—Cunningham, 51 Rosemary Lane, Formby (73573), Lancs.

SELLING: VHF Tx for two metres, 70 cm. and 23 cm., rack mounted, PA's 3-20A 45w. for two metres, 3-20A 40w. on 70 cm., 2C39A 60w. on 23 cm. Modulation by pair KT88's; all grids and amodes metered, relay controlled, push-to-talk operation, complete with PSU and all cables, £28. Creed 7B page-printer, motor PSU, terminal unit and paper, £20. Local delivery to 50 miles, or carriage extra.—Woodhall, 5 Summerville Avenue, Staining, Nr. Blackpool, Lancs.

OLLINS 75A-2/4 receiver, the Rolls-Royce for the amateur bands, having been professionally uprated to 75A-4 specification, including fitting two genuine Collins mechanical filters, 2.1 kHz for SSB and 6 kHz for good quality AM signals, at a cost of over £50. This receiver really sorts out the weak DX from the QRM, with its excellent 500 Hz dial read-out and second-to-none specification. Complete with comprehensive workshop manuals for 75A-2 and 75A-4, and Collins speaker. A rare opportunity and an absolute bargain at £145.—Ring Cartwright, G3UCV, Leeds 643788.

WHY Build Your Own Power Supply? Commercially-built variable PSU, available at give-away prices, mains input 200-250v. AC, output continuously variable 6-25v. at 250 mA, fully stabilised, low ripple voltage, in neat metal case 7in. x 6½in. x 4in., ideal for most transistor applications, price £5.50, carriage 50p.—Forbes, G3JKU, 40 Hempshaw Avenue, Woodmansterne, Banstead, Surrey.

SALE: KW-600 linear amplifier, in excellent condition, has just been fitted with a brand new 572B final, price £60, carriage extra.—Box No. 5038, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

OFFERING: Trio 9R-59DE receiver, with matching SP5D speaker and HS4 headset; all in perfect condition, hardly used and with original packing. Offers invited.—Ring Mathews, 01-876 7868 (London).

SALE: National HRO, with miniature valves, all BS coils including 21 MHz and Top Band, stabilised PSU, noise limiter and crystal calibrator, £25. Codar A.T.5 with mains PSU, £18. Carriage extra.—Moser, G3HMR, QTHR.

OFFERING: Sommerkamp FT-100 Transceiver, coverage 10 to 80m. bands, mobile PSU fitted, offers around £125.—Hudson, G3BOR, 21 Hallas Lane, Cullingworth, Bradford, BD13-5BX, Yorkshire. (Ring Bradford 23171, 9 a.m. to 5 p.m.).

SALE: K.W. Vespa Mk.II, in excellent condition, with mains PSU and crystal microphone, price £87.—Ring Glenn, G3YCU, Wilmslow (Cheshire) 25403.

SELLING: Fine example of "G2DAF-type" Rx, with etched front panel and linear VFO; sale at £45 due construction of IC transceiver.—Wiseman, GW3GRY OTHER, or ring Colwyn Bay 56135.

GW3GRY, QTHR, or ring Colwyn Bay 56135.

SALE: Hy-Gain 18-AVQ five-band vertical Ae. for £22-50, buyer to collect.—king Spencer, Shenstone (Staffs) 481202.

EXCHANGE: Brand-new QQV03-20A for QQV06-40A. C. Tyrone, Northern Ireland. (Tel. Omagh 3785 after 6.0 p.m.)

SALE: K.W. Vespa Mk. II with PSU, latest model having 6LQ6 PA, almost new, having had less than 6 hours' use due to business commitments. Cost £135, an absolute gift at £80 in manufacturer's original packing.—Ring Cartwright, G3UCV, Leeds, 643788.

OFFERING: Volumes "Short Wave Magazine" 1959-60, 1960-61, 1961-62, 1962-63, 1963-64, 1964-65—bound and in perfect condition, at £1.50 each, or near offer (includes postage).—Box No. 5039, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

DISPOSING: Two-metre gear, including TW2 Tx and PSU, T.W. Twomobile Rx, 10ft. pole, 4-ele J-Beam, frequency meter, etc. (S.W. London).—Box No. X009, Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

WANTED: Manual or circuit diagram for Marconi AD.108D, for loan to copy, or purchase. Packing and postage refunded to all correspondents. SALE: Heathkit RG-1 receiver, £22.—Day, 38, Woodstock Road, Begbroke, Oxford.

SALE: Emsac CN5 Top Band to MW or car radio converter, self-contained, new and as advertised, £5. Home-built solid-state GC superhet, includes Electroniques GC.166T Qoilpax, MW with five SW bands 1.7 to 30 MHz, RF stage, mixer, follower, oscillator, three IF's, product detector, BFO, S-meter, IC-10 AF amplifier, 898 dial, for mains operation, reasonable appearance, price £15 (dial alone worth £7). Postage extra, but prefer buyers inspect and collect.—Ring Hunter, 01-858 1448 (London).

# TRIO

## Communications Accessories

The following accessories are available for use with Trio Communications Equipment...

		Recom	mended Price				
CW Filter for T\$510	•••		£14·00				
10AZ Mechanical Filter for JR310	,		£14·67				
25kHz Marker Unit for JR310 (les	ss cr	ystal)	£7·34				
100kHz Calibration crystal			£3·18				
0A2 Mains Voltage Stabiliser	•••	•••	67p				
BI016/L Hand Held Communicat Microphone for TS510	ion 	•	£3·38				
Leson TW205A Table Standing Microphone							
with battery pre-amplifier	•••	•••	£7·95				
HS-4 Communication H/Phones	•••	•••	£5·98				
SP-5D Communications speaker matches all Trio receivers			£4·38				



# G. W. M. RADIO LTD.

PORTABLE AERIAL MASTS. Fine quality 48ft. masts by Coubro & Scrutton. 2" dia. aluminium sections, complete with 16 guys, pickets and all fittings. Unused and in "as new" condition in green canvas carrying bag, £20, carriage paid. Also available Erection Derrick kit containing 3 additional mast sections, ropes and pulleys, etc. to enable mast to be erected by fewer personnel, £5, carriage paid.

NEW 19 SET. Aerial Variometer tuners, Mk. III, £1-30, post paid. Control boxes No. I Mk. 2, 50p, post paid.

MARCONI VALVE VOLTMETERS No. 2, TF428B/I, in excellent condition, recently overhauled and in Ministry sealed packing, £5, carriage paid.

CRYSTAL CALIBRATOR CT432. 100 kc/s., 1 Mc/s. and 10 Mc/s. complete with crystals. Facilities for using external crystals of all common base types. 110/250v. A.C., £10, post paid.

AVOMETERS, 47a or 48a. Electrically same as model 40. All ranges checked, £10.00, post paid.

HYGRO METERS. Wet and dry bulb type, new, £1-25, post paid. SINGLE gang 500pf variables new and boxed, 30p, post paid. B40 speakers 600 ohm in ali case, £1-50, post paid. Eddystone 591 2" fluted knobs ‡" spindle, 25p each, 6 for £1-00, post paid. Vibrators 12v. 4-pin, 28p each or three for 68p, post.paid.

TRANSFORMERS. Used "C" core, 200–250v. to 230-0-230v. 260ma, 6-3v. 0-6a., 6-3v. 6-0a., £2 poat paid. Chokes "C" core 10h. 75ma., 50p post paid or 6 for £1-65 post paid. Unused Radiospares "Heavy Duty" 205-245v. to 350-0-350v. 150ma, 6-3v. 2-5a., 6-3. 3a., 6-3v. 2a (capped at 5v. 3-5a), £2, post paid. "Midget Mains" same input to 125-0-125v. 50ma., 6-3v. 1-2a., 75p, post paid. "Midget Output" 50p post. Used "C" core 0-115-180-240v. to 0-24-30-32v. 2a., £1-50, post paid. New Gardner potted 200-250v. to 12-7v. 2-5a., £1, post paid.

CAPACITORS, paper, 8uf 400v., 30p post paid or 6 for £1-05 post paid.

All Receivers and Test Equipment are in working order at time of dispatch.

Carriage charges quoted are for England and Wales only.

Telephone 34897
Terms: Cash with order Early closing Wednesday

40-42 PORTLAND ROAD, WORTHING, SUSSEX

WANTED: Joystick Aerial, complete with precision built variometer.—Leighton, Tangley Cottage, Wonersh, Guildford (66543), Surrey.

WANTED: To buy or hire, manual for Green Electronics 2M1000 Tx, also circuit for Mullard regulated PSU, Type L.153.—McGregor, G8ENH, 2 Roystone Road, Bradford 3, Yorkshire. (Tel: Bradford 664404).

WANTED: Pye F27AM, Cambridge, Bantams, Westwinster, Motaphone. Also wanted, working and unmodified Walkie-Talkies on either 27 or 28.5 MHz.—Kates, G3UHS, QTHR, Caterham (Surrey) 46692.

SALE: Codar A.T.5, £15. 250/PSU, £9. Star SR-200 Rx with Codar Q-multiplier, £44. All "or near offer."—Wickham, G3YWB, 25 Westwood Road, Brunton Park Estate, Newcastle-on-Tyne, NE3-5NN. (Tel: 089-4 2473).

SELLING: B.40D professional communication receiver, coverage 650 kHz to 30.5 MHz in five bands, with crystal calibrator, Osc. trimmer, xtal BFO and many advance features, absolutely first-class, £47 or near offer. Ekco International Short Wave Mariner receiver, nine bands, with world map and guide, as-new condition, £18.50.—3 Dane Road, off Norman Road, Ilford, Essex.

NOVEMBER issue SHORT WAVE MAGAZINE will appear on Friday, October 29. Single copies at 25p post free can be suppled to orders reaching us by Wednesday 27th for despatch on Thursday 28th, the day before publication. Orders with remittance to: Circulation Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, S.W.1.

# The NEW SAMSON ETM-3 **SQUEEZE - KEYER**

is now available!

With SQUEEZE-KEYING you make such characters as C, Q, Y, F, L, AR, SK, etc. with fewer paddle movements.

● 4 Integrated circuits 6 transistors, 2 diodes. ● Use double-paddle for either Squeeze-keying or normal fully-automatic electronic keying as preferred. ● Built-in PSU. ● Constant I:3 dash-dot ratio. ● Weight only 2½ lbs.

RETAINS the star features of the WELL-KNOWN SAMSON ETM-2 -used by coast stations and big ships all over the world :-

● Watchmaker-assembled keying-lever movement. ● Silent reed relay (400v., IA contacts). ● Sidetone. ● TUNE button.

BETTER EVEN THAN THE ETM-2—GET YOURS NOW!

£24.75 post paid U.K.

. . . and still going strong :-

SAMSON ETM-2 electronic keyer, £21 (£22-20 with mercury

SAMSON STA Speaker/Amplifier, for ETM-2/ETM-3, £2.75.

JUNKER PRECISION HAND KEY. Superb German straight Key made for professionals afloat and ashore. Free-standing—needs no fixing to desk. Hinged grey dust cover. Front and back contacts with click-stop gap adjustment. Key-click filter, £8.95.

BAUER KEYING LEVER AND PADDLE UNIT-for your own El-Bug. Compact enough to build in. Gaps/tensions adjustable NEW PRICE, £2.75.

MODEL TTU RTTY CONVERTER/KEYER-All-in-one-box instant send-receive RTTY with a TX/RX and cheap surplus teleprinter, £115.

All items post-paid U.K. Catalogue SP5 describes these and other RTTY, VHF, SSB kits and units.

SPACEMARK LTD. 14 PICCADILLY, MANCHESTER I.

14 PICCADILLY, (Tel.: 061-237 0817)

SELLING: Lafayette KT-340 general coverage receiver, 8 valves, Q-multiplier, 1 microvolt sensitivity, with spare valves and manual, £18.—Hartley, 31 Kings Drive, Middleton, Manchester, M24-4FB.

ALE: In very good condition, Eddystone 940, £90. Also Heathkit SB-301, all filters nearly new, price £130. Must clear.—Cliffe, The Willows, Kings Bromley, Burton-on-Trent, Staffs. (Tel: Yoxall 241, evenings).

WANTED: Hy-Gain 3DB mobile antenna; Pye AC/10PU power unit; TM-1 test meter; reflectometer Type RLF-1.—Pyatt, 141 The Chantries, Coventry, Warwickshire.

ONSIDERABLE Quantity of experimental radio CONSIDERABLE Quantity of capeting cheap parts left by recently deceased amateur, cheap to clear.—Ring 01-804 892 after 6.00 p.m. for appoint-

SELLING: CR-100 receiver, re-valved and realigned, superb, £17·50. R.209, coverage 1·0 to 20 MHz, 12v. DC inverter built in, brand new, £13.—Pugh, G8BSR, 178 Compton Road, Wolverhampton, Staffs.

KW-2000B with AC/PSU, in excellent condition, £175. T.W. Communicator, two-metre, £35. Prefer buyers collect.—Tibbert, G3RKZ, 11 Darwin Road, Mickleover, Derby (511434).

WANTED: By SWL, good communication receiver and equipment. Details and cash price, please; collection arganged.—Knudsden, 38 Pennington Oval, Lymington, Hants.

SELLING: Hallicrafters HT-46 transmitter, as new. coverage 10 to 80m. bands, runs 175w. SSB, 150w. CW. Price £100.—Gibson, 12 Cross Way, Harpenden,

WANTED: Oscilloscope, Hartley Type 13A, also Electroniques front-end Type GC.166. Any condition of either considered.—Hulin, Southview, Station Road, Bramley, near Guildford, Surrey. (Tel: 2279, after 6 p.m.).

FAILED R.A.E.: Selling Trio 510 transceiver with PSU, complete and professionally built linear consisting four PL-504's with PSU, all in one cabinet, in excellent condition, price £180 or near offer, or would separate. — Montgomery, 23 Larkham Lane, Plypton, Plymouth (37003) Devon.

FOR SALE: Drake TR4 transceiver, with AC4 PSU, RV-4 remote VFO, little used and in mint condition, £350.—Barry, 15 Fairlawn Court, London, W4-5EE. (Tel.: 01-994 6931).

FOR SALE: In very good condition, R.C.A. AR88LF receiver, price £35.—Bensley, 25 Wimborn Avenue, Grimsby (2344), Lincs.

# MORSE MADE

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed.

guaranteed.

For details and course C.O.D. ring s.t.d. 01-660 2896 or 01-668
3255 send 4p. stamp for explanatory booklet to:
G3HSC/Box 14, 45 GREEN LANE, PURLEY, SURREY.

#### SOLID STATE MODULES

#### THE SENTINEL DUAL GATE MOSEFT CONVERTERS

- \* Low noise figure of 2dB. Gain 30dB.

- ★ Low noise figure of 2dB. Gain 30dB.
   ★ Excellent overload and cross modulation performance.
   ★ Dual gate MOSFET R.F. amplifier and mixer.
   ★ Compact 2½" x 3" x ½" aluminium case.
   ★ 2 metre IFs stocked: 4-6 MHz, 9-11 MHz, 14-16 MHz, 18-20 MHz, 23-25 MHz, 24-26 MHz, 28-30 MHz.
- ★ 4 metre IFs stocked: 25-25.7 MHz. 28-28.7 MHz. Price: £13.75.

#### SM 70 70cms FET CONVERTER

- ♣ Low noise figure 3:5dB.
- Town lose injure 3-30a.

  If output 144–146 MHz for connection into a 2 metre converter.

  This arrangement means that we can produce a high performance 70cms unit for only £13-75.

#### THE SENTINEL LOW NOISE FET 2 METRE PRE AMPLIFIER

- \* FET and components selected for a low noise figure of IdB.
- Gain of 18dB. Price £6.50.

#### THE SPITFIRE 2 METRE A.M. TRANSMITTER

- ★ 5 watts input. At least 2 watts output.
- 12 volts operation.

  Modulation wave shaping gives good, clean 100% audio.
- Audio modulation monitoring point for headphones. Price £22.00.

#### THE SPITFIRE MODULATOR

\* Same size and appearance as the transmitter. Price £10.00.

# SOLID STATE 9 MHz SSB GENERATOR \*\*Selectable USB, LSB and CW.

- \* 0.2 volts into 80 Ohms output.
- A sound basis for your SSB transmitter.

  Price £11.00 less filter and Carrier crystals.

#### KVG 9 MHz CRYSTAL FILTERS

XF 9A SSB 2.4 kHz, £11.00

XF 9D AM 5 kHz £15:00

XF 9B SSB 2.4 kHz, £16.00 XF 9C AM 3:75 kHz. £15:00

Official KW Agents

KW202. Receiver ... KW204. Transmitter ... KW2000B. Transceiver

KW Atlanta Transceiver W Atlanta. VFO ...

KWI03. VSWR ... KW Antenna Traps pair KW Dummy Load ... KW Low Pass Filter ...

Yaesu/Sommerkamp

FT101. Transceiver ... FT560. Transceiver ... FT200. Transceiver ...

TS510. Transceiver ... TX599. Transmitter ...

HS4. Headphones ...

KW Balun

Trio

G3LRB

KW2000B. Remote VFO £35-00

KW E-Z Match ... £13-50 KW107. Matching unit £40-00 KW103. VSWR ... £12-50

FT200. Transceiver ... £180 FT2F. 2m. Transceiver £80.00

F12F. 2m. Iransceiver £80-00 FL500. Transmitter ... £140 FR500. Receiver £120/£160 FV400. Remote VFO ... £38-00 F400. Loudspeaker ... £10-00 FL2000B. Linear ... £130

| 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185 | 185

XF 9M CW 0.5 kHz, £11.00 Carrier crystals, £1.50 each

Eddystone EC 10 Mk2. Receiver ... £79.00

EC 10 Mk2. Receiver ... £79.00
A.C. Power Unit ... £7.75
Sy8 SM Drive ... £7.75
Full range of diecast boxes.
Hy-Gain Antenna Range
12AVQ. Vertical ... £15.50
14AVQ. Vertical ... £18.50
14AVQ. Wertical ... £33.50
TH6DX. Tribander ... £84.00
TH3MK2. Tribander ... £46.50
TH3JNR. Tribander ... £46.50
TH2 Mk. 3. Tribander ... £46.50
TH2 Mk. 3. Tribander ... £67.50
CL80Q. 80m. coil ... £8.00
LC80Q. 80m. coil ... £8.00
203BA. 20m. 3 element ... £68.50
G Whip Antenna Range
160m. Ranger ... £7.50

160/80m. Duobander ... £7-30
160/180m. Duobander ... £9-00
10-15-20m. Tribander £9-50
Coils for LF bands each £4-00
Coils for LF Bands ... £4-00
Basemounts ... £1-45

160m. Ranger ... ... 160/80m. Duobander ...

Basemounts ... Telescopic for LF Coils

2m. § wavelength.

V.H.F. Beams

2m. 5 element ... 2m. 6 element ...

2m. 8 element ...

4m. 3 element ...

4m. 4 element ... 70cm. 9 element

All equipment advertised should be ex stock but you can ring for confirmation.

63, WOODHEAD ROAD. SOLID, LOCKWOOD, HUDDERSFIELD. Tel. 23991

£140

£142 £240

£200 £32·00

£12.50 £4.00 £7.00

£230

£195

£180

£185

# Sale

JOYSTICK AERIALS AND TUNER UNITS AT ALMOST HALF PRICE. NOW IS YOUR CHANCE TO BUY THE TUNING UNIT THAT YOU WANT. STOCKS ARE LIMITED. DON'T DELAY.

Joymatch type 2A Tuners ....SALE PRICE £2.20 Joymatch type 4 Tuners .....SALE PRICE £2.75 Joymatch type 4H Tuners .... SALE PRICE £2.50 Joymatch Junior Aerials.....£3.25 each

Post and Packing 20p per item extra.

All items offered are new and unused. Stocks are limited so please state second choice when ordering.

Personal callers and Mail Orders to:

#### Laskys Radio Limited, 3/15, Cavell Street, London El 2BN

NOTE—THESE ITEMS ARE ONLY AVAILABLE FROM THE ABOVE ADDRESS AND NOT FROM ANY OF OUR BRANCHES. ALL ITEMS OFFERED SUBJECT TO BEING AVAILABLE.

Codar

Preselectors Preselectors ... Q Multipliers ...

Partridge Electronics

New Lightweight VFA .. TX Tuner ... ... RX Tuner ... ...

...

Eddystone 670A ... £25
FL2000 Linear ... £100-00
KW Viceroy Mk. 2 ... £70-00
Eddystone 680X ... £70-00

Secondhand Equipment Sommerkamp FL500 Tx. Codar Preselector ...

Codar Preselector ... Codar Q Multiplier ...

Antenna Range W.E. Quad ... GEM Quad ...

Lafayette KT320 Swan 500 ... Trio JR310 Codar CR70A

Codar CR70A ... Eddystone 840C

Lafayette HA500

AR88D Trio TS500 KW 2000

Poly Quad

30p

100

#### STEPHENS-JAMES LTD. . LIVERPOOL 70 PRIORY ROAD

4m. Folded Dipole 4m. Folded Dipole ... £1.50
Sentinel 2m. Converters £13.75
Sentinel 4m. Converters £13.75
Sentinel 70cm. Converters £13.75 2m. AM Transmitter 2 Modulator ... ... £22.00 ... £10.00 ... HZP Balun ... pair Wight balun ... £3.00 £2.50

... Dipole T pieces ... 300 ohm twin feeder yd. l3p 75 ohm twin feeder yd. PL259 Plugs 30p

... ٠... Sockets ... Cable reducers

High Pass Filter ... Semi-Auto Bug Keys ... Tunable RF Meters ... £2.40 £4.50 Antenna Rotators

£18.00 to £70.00 50 ohm Coax ... yd. 12p Egg Insulators ... ...

Transistor Checker

Omega Antenna Noise
Bridge ....
Copal 24 Hour Clocks ...
3 Band Aircraft Radio... ... £13·50 £8.95

Stella cabinets. Large S.A.E. will bring all the range of equipment we stock. All RSGB Publications stocked.

...

Complete range of Datum and Eddystone Diecast boxes also

Equipment bought for cash. Carriage/post is extra all items. Shop hours 9.30 till I p.m. 2.15 till 6 p.m. Half day Wednesday.

**G3MCN** 

Telephone 051-263 7829

> ... ... £27.00

£8.50

£10.00

£23.00

4105

€5.00

£5.00

... £26.00 ... £235.00

...

...

£60.00

£15

£35

£135 £120

Lafayette
HA600A. Receiver ... £45.00
HA800. Receiver ... £50.50 Regret no mail order on VHF Beams H.P. and Credit terms can be arranged on all orders over £35. After sales service. Part exchanges.

No parking problems except Saturday afternoons as we are close to the Liverpool and Everton Football grounds.

£7.50

75p

£4.20

£2.50

£4·20 £3·50


£4.00

£3.00

Vertical

...

...

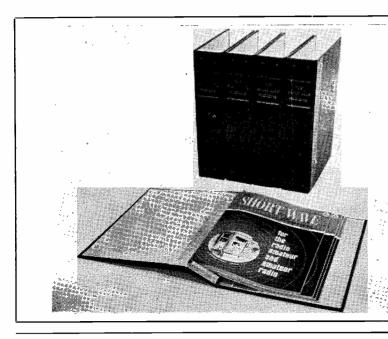

# CREATE YOUR OWN REFERENCE LIBRARY

The "EASIBINDER" is designed to bind 12 copies of the Magazine as you receive them month by month, eventually providing a handsomely

No need to wait until twelve copies No need to wait until twelve copies are assembled. As each copy is received, it is quickly and simply inserted into the binder. Whether partially or completely filled, the binder is equally effective, giving the appearance of a book, with each page opening flat.

Strongly made with stiff covers and attractively bound in maroon Leathercloth and Milskin, the binders have only the title gold blocked on the spine.

Price 88p. post free.

PUBLICATIONS DEPARTMENT SHORT WAVE MAGAZINE 55 VICTORIA STREET LONDON, S.W.I

# Advertising in "Short Wave Magazine" guarantees the largest and most effective coverage of the U.K. radio amateur interest

#### SINGLE SIDEBAND (Theory & Practice) by Harry D. Hooton, W6TYH.

by Harry D. Hooton, W6TYH.

The Origin of Single Sideband
The Derivation of Single-Sideband Signals

Amplitude Modulation—Power Distribution in the AM Signal—Formation of the Sidebands—Transmitter Efficiency—Carrier and Sideband Removal Effects.

Carrier Suppression Techniques
Push-Pull Balanced Modulator—Parallel-Output Balanced Modulator—Vector Analysis—Push-Pull Input and Output—Diode Modulator —Vector Analysis—Push-Pull Input and Output—Diode Modulator —Balanced Modulator Using a Beam Deflection Tube.

Sideband Selection
Filter Method of Sideband Selection—Phase-Shift Sideband Selection.

Carrier Generators

Low-Frequency Generators—Medium Frequency Generators—High-Frequency Generators—Generator Design Precautions.

Speech Amplifiers and Filters

Amplifier Frequency Response—AF Bandpass Filters—Practical Speech-Amplifier Circuits—Commercial Speech-Amplifier Circuits—Speech-Amplifier Circuits—Commercial Speech-Amplifier Circuits—Speech-Amplifier Circuits—Commercial Speech-Amplifier Circuits—Single-Sideband Generators

Bainced Mixers and Converters

Double Conversion—Triode Balanced Mixers—Pentode Mixers—Beam-Deflection Tube Mixer.

Low-Power Single-Sideband Transmitters

Collins 32S-3—The Hammarlund HX-500—Hallicrafters HT-46

Transmitter—R. L. Drake T-4 and T-4X Equipment.

Linear RF Power Amplifiers

Amplifier Classes—Types of Tubes—Basic Circuits—Practical Design—A I,000-watt Amplifier—The Collins 30S-1—Grounded-Grid Class-B—I,000-watt Grounded-Grid Amplifier—Collins 30G-1—Heathkit SSB Amplifier HA-14-SB2-LA Linear Amplifier—The Hammarlund HQ-180—Single-Sideband Conversion—

SSB Receiver Summary.

Single-Sideband Transceivers

Collins KWM-212A—SBE SB-34—EICO 753 Tri-Band Transceiver Kir—Heathkit SB-110—RF-301 Military SSB Transceiver—SB-6FA SSB Transceiver—Beath Programmer Language Power Counter Makayers

Tests and Measurement Methods and Techniques—Hammarlund Forey Counter Makayers

SSB Transceiver.

Tests and Measurements

Frequency Measurement Methods and Techniques—Hammarlund
HX-500—Collins 32S-3—Signal-Level and Power-Output Measurements—Linearity Measurements in Power Amplifiers.

PRICE £3.45p. post free

Available from Publications Dept., SHORT WAVE MAGAZINE 55 Victoria Street, London, S.W.I 01-222 5341 THE RADIO AMATEUR'S HANDBOOK has again been extensively revised and updated by the Headquarters Staff of the American Radio Relay League, Doug DeMaw, WICER, Editor. The 1971 edition of this widely used manual of communications theory, design and construction contains even more new material on state-of-the-art techniques and equipment than last year's 47th edition. The new HANDBOOK continues to fill the need for a standard textbook and reference work for both beginners and advanced amateurs. This Edition is of 688 pages, including catalogue section and index. There are over 1,300 illustrations, many of which have been revised, including 576 valve-base diagrams. Available from stock at £2.80 post free or at £3.60 (post free) for the hardcovered clothbound edition.

Orders to:

PUBLICATIONS DEPT. SHORT WAVE MAGAZINE 55 VICTORIA STREET, LONDON, S.W.I.

01-222-5341/2

Printed by The Courier Printing Co. Ltd., Tunbridge Wells for the Proprietors and Publishers, The Short Wave Magazine Ltd., 55 Victoria Street, London, S.W.I. The Short Wave Magazine is obtainable abroad through the following: Continental Publishers & Distributors, Ltd., William Dawson & Son Ltd.; AUSTRALIA AND NEW ZEALAND — Gordon & Gotch, Ltd.; AMERICA—International News Company, 131 Varick Street, New YORK. Registered for transmission to Canada by Magazine Post. October, 1971.