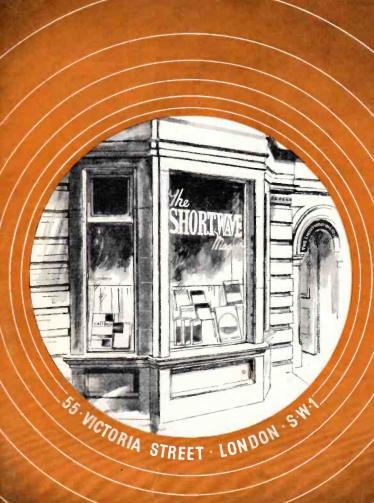


Magazine

VOL. XXX

APRIL, 1972



amateur mateur ii

MULT!-METERS



MODEL 500 30,000 O.P.V. with over-O.P.V. with overload protection in mirror scale 0/15/25/10 / 25 / 100 / 250 / 100 / 250 / 100 / 250 / 100 / 250 / 100 / 1000. 250 / 100 / 1000. 250 / 500 / 1.000v. A.C. 0 / 50µA / 5 / 50 / 500mA. 12 amp. D.C. 0/60/K/6 Meg./60 Meg. Ω, £8.87½ Post paid.



TMK MODELTW-50K
46 ranges, mirror scale,
50K/Vol. D.C.: Volts '125,
25, 125, 25, 50, 100,
A.C. DC.: St, Volt
25, 125, 25, 50, 100,
A.C. Volts: 1.5, 3, 5, 10,
0000v. D.C. Current: 25, 50µA,
25, 50, 250, 500mA, 5, 10 amp.
Resistance: 10K, 100K, 1 Meg.,
10 Meg.,
10 Meg.,
10 Meg., Decibels: —20 to +
81.5 dB, £8.50, P. & P. 17‡p.



MODEL 5025
7 Ranges. Giant
15 in Meter, Polarity Reverse
Switch.
Sensitivity: 50K/
Volt. D.C. 5K/Volt
A.C. D.C. Volts: 125, 51, 125, 51, 125, 55, 125, 520, 500, 1,000v. A.C.
500A, 2:5, 5, 25, 50, 25, 50, 25, 500A, 5, 100K, 1Meg, 10 Meg. Decibels:
-20 to + 85 dB, £12.50. P. & P.



MODEL S-100TR Multimeter/Transistor Tester 100,000 O.P.V. 0.0,000 O.P.V.
Mirror Scale/Over-load Protection. 0/
-12/-6-03/-120/-600v. D.C. 0/6/
30/-120/-600v. D.C. 0/6/
30/-120/-600v. D.C. 0/6/
30/-120/-600v. D.C. 0/10/-12/
300MA/12 AMP D.C. 0/10K/I Meg-20 to +50 dB. 0-01-2

Transistor tester measures Alpha, Beta and Ico. Complete with batteries, instructions and leads, £13-50. P. & P. 25p.

POWER SUPPLY UNITS



output 0-24v.D.C.

up to I amp. Dual scale meter to monitor voltage and current. Input 220/240v. A.C. Size: 185 × 85 x 105mm., £8-97. P. & P. 25p.



PS.1000B Regulated Power Supply. Stoled state. Output 6, 9 or 12 volt D.C. up to 3 amps. Meter to monitor current. Input 220/240v, A.C. Size: 4" x 3\frac{1}{4}" x 6\frac{1}{4}", \frac{1}{4}11-97. P. & P. 25p.

> Small port-

CRYSTAL CALIBRATOR No. 10



able crystal controlled wavemeter. size 7" x 7½" x 4". Frequency range 500 Kc/s.-10

LAFAYETTE HA.800 SOLID STATE AMATEUR COMMU-NICATION RECEIVER SIX BANDS 3-5-4, 7-7-3, 14-14-35, 21-45, 28-29-7, 50-54 Mc/s.

Dual conversion on all bands. 2 x 455 Kc/s. mechanical filters. Product detector Variable B.F.O. 100 Kc/s. crystal calibrator. "S" meter Huge slide rule dial. Operation 230v. AC or 12v. DC. Size 15" x 9\frac{3}{2}" x 8\frac{1}{2}". Complete with instruction manual, £57.50. Carr. paid (100 Kc/s. Crystal £1 · 97\frac{1}{2} extra).



3 🔞

UNR-30. 4 BAND COMMUNICATION RECEIVER

Covering 550 Kc/s.-30 Mc/s. Incorporates variable FOB for CW/SSB reception. Built-in speaker and phone jack. Metal cabinet. Operation 220/240v. A.C. supplied brand new, guaranteed with instructions, 215-73. Carr. 37‡p.


TRIO 9R59DS

TRIO 9R59DS

4 band covering 550 Kc/s, to 30 Mc/s, continuous and electrical bandspread on 10, 15, 20, 40, and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB—CW ANL · Variable BFO · S meter · Sepbandspread dial · IF frequency 455 Kc/s. · audio output i-5w. · Variable RF and AF gain controls 115/250v. A.C. Size : 7" × 13" × 10" with instruction manual, 657-50, Carr. paid. SPECIAL OFFER!

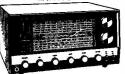SPECIAL OFFER!
Matching SP5D speaker supplied free with above receiver.





STATE HA600 RECEIVER
5 Band AM/CW/SSB amateur
and short wave 50 Kc/s.-400 Kc/s.
and 550 Kc/s.-30 Mc/s.
F.E.T. front end. 2 Mechanical filters,
Huge Dial. Product detector.
Variable BFO. Noise limiter, S Meter.
24" Bandspread. 230v. A.C./12v.
D.C. Neg. earth operation. RF gain
control. Size: 15" x 94"
Vt. 18 lbs. Exceptional value, £50.
Carr. 50p.

TRIO JR-500SE AMATEUR RECEIVER

7 separate ranges between 3·5 and 29·7
Mc/s. 7 valves, 2 transistors and 5
diodes plus 8 crystals: output 8 and
500 ohm and 5000 ohm phone jack.
Crystal controlled oscillator.
Variable BFO · VFO · AVC · ANL ·
S meter · SSB-CW · Stand-by
switch · special double gear dial
drive socket for connection to a
drive socket for connection to a
fransmitter. 115/250v. A.C. Mains.
Size: 7" x 13" x 10" with instruction
manual and service data, 265·00, Carriage paid. Package deal : JR500SE with
SPSD speaker and HS4 headphones, 269-50.

TRIO TS 510 AMATEUR TRANSCEIVER with speaker and mains P.S.U., £180.

TRIO JR310 AMATEUR BAND 10-80 Metre Receiver, £77-50.

B.C.22I FREQUENCY METERS Latest release 125 kHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts, £27-50 each. Carr. 50p.

UR.IA SOLID STATE COMMUNICATION RECEIVER



4 bands covering 550 Kc/s-30 Mc/s. continuous. Special features are use of FET transistors, S Meter, bult-in speaker, variable BFO for SSB reception, noise limiter, bandspread control, sensitivity control. Output for low impedance headphones. Operation 220-240v. A.C. or 12v. D.C. Size: 122" x 44" x 7". Excellent value. Only £25.00. Carr. 37½p.

TEI5 TRANSISTORISED GRID DIP METERS

Six ranges. 440 Kc/s.— 280 Mc/s. Operates on 9v. battery. Full instructions £12-50.



HANSEN SWR-3 BRIDGE Impedance 52 ohms. Also operates as field strength indicator, complete with telescopic aerial, £4-25 each, P.P., 17½p. PL259 plugs to suit 37½p each.

HAMGEAR PRESELECTORS PMIIA £9-20 & PMIIB £8-25, P.P.20p.

Our New 6th edition gives full Our New 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS. TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 272 pages, fully illustrated and detailing thousands of items at bargain prices.

SEND NOW | STILL ONLY 37½p P. & P. 10p.

CLEAR PLASTIC PANEL METERS

First grade quality, Moving Coil panel meters, available ex-stock. Quantity discounts. Type MR.38P. I 21/32in. square fronts.



50μA £2·10 50-0-50μA £1·90 100μA £1·90 100-0-100μA£1·75 200μA £1·75 500μA £1·65 200μA 500μA 500-0-500μA £1.60

£1.60 £1.60 £1.60 £1.60 £1.60 £1.60 ImA I+0-ImA 2mA 5mA 10mA 750mA

150 v DC 300 v DC 500 v DC 750 v DC 15 v AC 150 v AC 150 v AC 300 v AC £1.60 £1.60 £1.60 £1.60 £1.60 £1.60 £1.60 1 amp 2 amp 5 amp 20mA 50mA 100mA 150mA 200mA 300mA 500mA 500mA 10v DC 20v DC l amp £1.60 £1.60 £1.60 £1.60 £1.60 £1.60 £1.60 S meter I mA £1.70 VU meter £2.10

FULL RANGE OF OTHER SIZES IN STOCK, SEND S.A.E. FOR LEAFLET.


OPEN 9-6 MONDAY TO SATURDAY



G.W.SMITH & C 27 TOTTENHAM CT. RD. LONDON, W.1 3 LISLE STREET, LONDON, W.C.2 34 LISLE STREET, LONDON, W.C.2 311 EDGWARE ROAD, LONDON, W.2 OPEN 9:6 MONDOY, TO SATURE

Tel: 01-636 3715 Tel: 01-437 8204

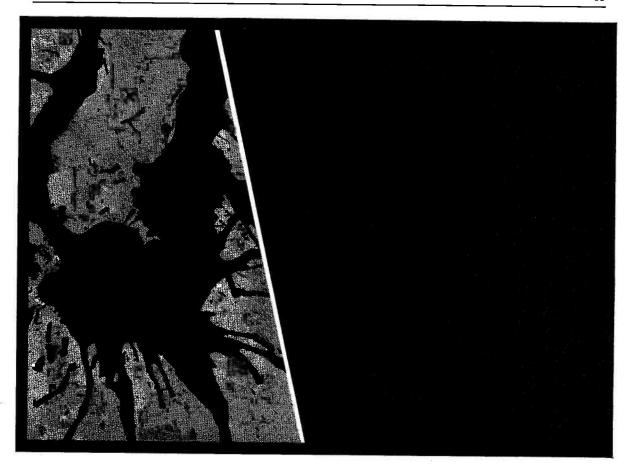All Mail Orders to – 11-12, Paddington Green, London W.2 Tel: 01-262 6562



SSB-er:

increase talk power, cut "splatter"



Our 444 base station microphone not only gives you increased talk power, but cuts "splatter" (and QRM complaints) to an absolute minimum! It has superbly tailored response, with sharp cutoffs below 300 and above 3,000 Hz and a rising response characteristic for maximum intelligibility. The 444's rugged, reliable Controlled Magnetic element has been proved in safety communications, and other tough professional communications applications. It delivers a clean signal to the transmitter at levels as high as crystal units! (And, unlike crystal and ceramic units, the element is totally immune to the effects of temperature and humidity.) The 444 also features an adjustable height stand that makes for comfortable "ragchewing" sessions, an optional-locking bar for push-to-talk or VOX operation, and a practically indestructible Armo-Dur® case. Write:

Shure Electronics Limited 84 Blackfriars Road London SE1 8HA, England



Technical Books and Manuals

(ENGL)	JII AILD	AMERICAN	
AERIAL INFORMATION		ARRL Calculator, Type A	92p
ARC of Antonnae	90p	ARRL Calculator, Type B	72p
ABC of Antennas	00-	Easibinder (to hold 12 copies of Short Wave	
Acrial Handbook (Brigge)	87n	Magazine together)	90p
Aerials (By D. Sjobbema) Aerial Handbook (Briggs) Amateur Radio Antennas (Hooton) Antenna Handbook, Volume 1 Antenna Round-Up, Volume 1 Antenna Round-Up, Volume 2 Antenna Handbook, 12th Edition Beam Antenna Handbook Ham Antenna Construction Projects Quad Antennae S9 Signals	£1.87	Practical Integrated Circuits	
Antonna Handhook Volume 1	£1.77	(Newnes-Butterworth)	€1 · 01
Antonna Pound-Un Volume 1	£1.47	110 Semi-Conductors Projects for the Home	
Antenna Pound-Un Volume 2	£1.77	Constructor (Iliffe)	€1 ∙ 37
Antonna Handhook 19th Edition	£1.40	HANDBOOKS AND MANUALS	
Poem Antonna Handhook	£2.10		€2·17
Ham Antonna Construction Projects	£1.47	Amateur Radio DX Handbook	£1 · 42
Out Antenna Construction Projects	£1.90	Electronic Circuit Handbook, Vol. 1	£1 · 42
Quad Antennae	87p	Electronic Circuit Handbook, Vol. 2	
	01Þ		£1 · 40
73 Vertical, Beam and Triangle Antennas	£2·40	Mobile Manual, ARRL	£1 · 40
(by E. M. Noll)	T.Z.40	New RTTY Handbook	£1 · 80
73 Dipole and Long-Wire Antennas (by E. M. Noll)	£2·20	Radio Amateur Handbook 1972 (ARRL)	£2·85
SWL Antenna Construction Projects	£1.30	Radio Amateur Handbook 19/2 (ARRL) (Haru	
BOOKS FOR THE BEGINNER			€3.62
	£1 · 60	Radio Amateur Operators Handbook, 12th Edition	53p
Amateur Radio (Rayer)	£1.42	Radio Communication Handbook (RSGB)	£3·50
Beginners Guide to Radio (7th Edition)	£1.10	Rtty A-Z (CQ Tech. Series)	£2·25
Beginners Guide to Electronics (N.E.)	E1.10	Surplus Conversion Handbook	£1 · 37
Beginners Guide to Transistors	#1.17	Transistor Substitution Handbook No. 10	£1 · 12
Beginners Guide to Radio (7th Edition) Beginners Guide to Electronics (N.E.) Beginners Guide to Transistors Beginners Guide to Colour TV	02P	USEFUL REFERENCE BOOKS	
Better Short Wave Reception	£1.90		£1 · 59
Course in Radio Fundamentals	62p	Amateur Radio SSB Guide	61.15
Foundations of Wireless and Electronics	£2·02	Amateur Radio Techniques (N/L)	C1 .12
Guide to Amateur Radio	50p	Amateur Radio Construction Projects	705
How to Become a Radio Amateur	59p	Amateur Radio Circuit Book	10p
How to Become a Radio Amateur Morse Code for the Radio Amateur	15p	Guide to Amateur Radio	20 P
Learning the RT Code	27p	Engineers' Pocket Book-bin Edition	£1:40
Radio, by D. Gibson	85p	'G' Call Book 1972	62p
Radio Amateur Examination Manual	45p	Hams' Interpreter	esp esp
Short Wave Listener's Guide (N.E.)	O/P	Hints and Kinks, Vol. 8 (ARRL)	62P
Simple Short Wave Receivers (Data)	89p	Radio Amateur Examination Manual	45P
Radio, by D. Gibson	£1·37	Operating an Amateur Radio Stat.	Zəp
		Amateur Radio Circuit Book Guide to Amateur Radio Engineers' Pocket Book—6th Edition 'G' Call Book 1972 Hams' Interpreter Hints and Kinks, Vol. 8 (ARRL) Radio Amateur Examination Manual Operating an Amateur Radio Stat. Radio Data Reference Book (3rd Edition) Radio. Valve and Transistor Data (Iliffe),	£1.00
GENERAL			
	ois	9th Edition	89p
Guide to Broadcasting Stations (16th Edition)	60p	Service Valve and Semiconductors Equivalents .	35р
How to Listen to the World 1971—Edition	£1 · 37	Single Sideband for the Radio Amateur (ARRL),	
RCA Receiving Tubes Manual RCA Transistor Manual (N.E.) RCA Transmitting Tubes Shop and Shack Shortcuts Television Explained Vol. I Television Explained Vol. II.	£1 · 77		£1 · 67
RCA Transistor Manual (N.E.)	£1 · 75	Single Sideband (Theory & Practice) by H. D. Hooton Sun, Earth and Radio by J. A. Ratcliffe Surplus Schematics (CQ) Transistor Pocket Book Q & A on Audio TRANSISTOR MANUALS	
RCA Transmitting Tubes	£1 · 35	by H. D. Hooton	£3·47
Shop and Shack Shortcuts	£1 · 75	Sun, Earth and Radio by J. A. Ratcliffe	91 p
Television Explained Vol. I	£1 · 35	Surplus Schematics (CQ)	£1 · 22
Television Explained Vol. II.	£1·37	Transistor Pocket Book	£1 · 57
Telecommunications Pocket Book (1, L. Squires)	£1·32	TRANSISTOR MANUALS ABC of Transistors	54p
World Radio and TV Handbook 1972 Edition .	£2·80	TRANSISTOR MANUALS	
ARC of Electronics (by Farl J. Waters)	£1 · 20	ABC of Transistors	£1 · 33
ABC of FET's ABC's of Short Wave Listening	£1 ·35	ABC of Transistors	£2.35
ABC's of Short Wave Listening	£1 · 02	Transistor Fundamentals: Basic Semi-Conductor	
Ruilding Your Amateur Radio Novice Station		and Circuit Principles, Vol. 1	61.02
(by W7OE)	£1.5/	Translator Fundamentales	~ I · 3L
FET Circuits (by Rufus P. Turner)	£1 ·52	Transistor Fundamentals: Basic Transistor Circuits, Vol. 2	C4 . 02
FET Circuits (by Rufus P. Turner) FET Principles, Experiments and Projects	£2·15	Translator Fundamentales	. I · JZ
Having Fun with Transistors Know Your Oscilloscope (by Paul C. Smith)	£1.59	Transistor Fundamentals:	£1 · 92
Know Your Oscilloscope (by Paul C. Smith) .	£1.80		£1.32
110 Integrated Circuit Projects for the notice		Transistor Fundamentals: Student's Workbook	C1.02
Constructor	£1 ·22		£1·12
40 Facy Transistor Projects	£1 · 01		£1·12 £1·77
Practical Ham Radio Projects (by W6NJV)	£1 · 15	comy corporation	~1.11
Practical Transistor Theory	£1.10	VHF PUBLICATIONS	
Practical Wireless Circuits	£1 · 34	VHF Handbook, Wm. I. Orr	£1 · 79
Single Sideband: Theory & Practice		VHF Manual (ARRL)	£1 · 37
(by H. D. Hooton)	£3·47	VHF Handbook, Wm. I. Orr VHF Manual (ARRL) VHF JUHF Manual (RSGB) N /E	£1 · 80

The above prices include postage and packing.

Many of these Titles are American in origin.

Available from SHORT WAVE MAGAZINE Publication Dept., 55 Victoria St., London SW1H OHF . 01-222 5321

(Counter Service, 9.30-5.15. Mon. to Fri.)

(GIRO A/C. No. 547 6151)


(Nearest Station: St. James's Park)

CALL BOOKS INTERNATIONAL: RADIO AMATEUR CALL BOOK "DX Listings" £3.10 "U.S. Listings" £4:10 The two together, covering the World . 46.80 "G's" only 1972 60p MAPS AMATEUR RADIO MAP OF WORLD Mercator Projection - Much DX Information - in colour, Second Edition 65 p DX ZONE MAP (GREAT CIRCLE) In colour with Country/Prefix Supplement Revised to Dec. 1970 85p RADIO AMATEUR MAP OF THE U.S.A. AND NORTH AMERICA State boundaries and prefixes, size 24" by 30", paper a 03 RADIO AMATEUR'S WORLD **ATLAS** In booklet form, Mercator projection, for desk use. Gives Zones and Prefixes 85p LOG BOOKS Standard Log (New Glossy Cover) . 55 p Log and VHF Contest Log . . . 40p Receiving Station Log . . . 45p ARRL. Log (Spiral) 70p (The above prices include postage and packing). Delivery is from stock. MORSE COURSES G3HSC Rhythm Method of Morse Tuition *Complete Course with three 3 speed L.P. records with books £4.50 *Beginner's Course with two 3 speed L.P. records with book . £3·30 Single 12" L.P. Beginner's with book . . £2.75 Single, 12" L.P. Advanced with book £2.75 Three speed simulated GPO test. 7" d.s. E.P. record 85p Ex.Gov. Heavy Duty Morse Keys Fully Shrouded 95p Prices include postage, packing and insurance in U.K. only *Overseas orders + £1.00. Available from

SHORT WAVE MAGAZINE

Publications Dept., 55 Victoria Street, London, SW1H OHF . 01-222 5341

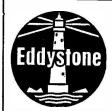(Counter Service, 9.30-5.15, Mon. to Fri.) (Nearest Station: St. James's Park) (GIRO A/C No. 547 6151)



"LISTEN TO THE WORLD WITH EDDYSTONE"

Your local Eddystone dealer is:

CHESHIRE

The Transistor Centre (Wilmslow) Ltd. Green Lane Wilmslow 24766

CORNWALL

R. V. Heming Ltd. (Peter Heming G3WBW) Cliff Road, Newquay Newquay 2191

S.S.B. Products (Norman Birkett G3EKX) 7 Little Castle Street Turo Devoran 862575

DEVON

Graham Newbery (Reg Ward G2BSW) Axminster Axminster 3163

ESSEX

F. E. Smith 184 Moulsham Street Chelmsford Chelmsford 54594

HAMPSHIRE

Southern Marine Radio (Southampton) Ltd Solent House, Town Quay Town Quay 22721

Wireless Supplies Unlimited 264-266 Old Christchurch Road Bournemouth Bournemouth 24567

LANCASHIRE

Holdings Photo Audio Centre Mincing Lane - Darwen Street, Blackburn BB2 2AF Tele, 59595

Stephen-James Ltd 70 Priory Road, Anfield Liverpool L4 2RZ 051-263 7829

North West Electrics 769 Stockport Road Levenshulme, Manchester 19 061-224 4911

Croftfilm Ltd 46 Friargate Preston PRI-2AT Preston 55244

LEICESTERSHIRE

A. K. Davey Ltd New Street, Hinckley Hinckley 2173 and 4288

LONDON

Imhofs (Retail) Ltd 112-116 New Oxford Street W.C.1 01-636 7878 R. T. & I. Electronics Ltd Ashville Old Hall Ashville New Ell 01-539 4986 Radio Shack Ltd

Radio Shack Ltd 182 Broadhurst Gardens London, N.W.6 01-624 7174

NORFOLK

The Record Shop 157 King Street Great Yarmouth

NORTHUMBERL'D

Aitken Bros & Company 35 High Bridge Newcastle upon Tyne NE! IEW Newcastle upon Tyne 26729

IRELAND

John F. MacMahon 10, Church Street, Enniskillen Co. Fermanagh, N. Ireland Enniskillen 2955

ISLE OF WIGHT

Sherratt & Son 81-82-83 High Street, Newport Newport 3358-9

KENT

G. T. & R. Wilson 12-14-16 Queen Street Gravesend Gravesend 63527/8

SCOTLAND

L. Hardie 542 George Street Aberdeen Aberdeen 20113

WALES

Holt High Fidelity Picton Arcade, Swansea Swansea 53254

Holt High Fidelity 8 Portland Street, Swansea Swansea 41032

WARWICKSHIRE

Chas. H. Young Ltd 170/172 Corporation Street Birmingham 4 021-236 1635



WESTERN


When you buy YAESU from their U.K. main distributor you get the best engineering standards in the world and superb performance too. All items carry the YAESU 12 months guarantee. We also do free labour on warranty claims, and carry an excellent stock of spares.

NOW BEAT THIS FOR VALUE! 35p per watt! The YAESU FT560 only £195 (Free 24 hour delivery)

Forget the fact the YAESU is the finest built Forget the fact that YAESU offer greater facilities Forget the multitude of other YAESU advantages

and you will still have to agree that the FT560 transceiver offering 10-80m. with 560w. p.e.p. input is the best buy. Even the cheapest kits cost 88p per watt and offer far less features.

FT560 (Ex Stock)

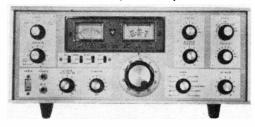

SPECIFICATIONS :

Maximum Input Power : 560 W PEP SSB, 500 W CW.

Sensitivity: 0.5 Microvolt for 20 dB S/N (SSB 14 MC)

Selectivity: 2.3 kHz (6 dB down) 3.7 kHz (60 dB down) six pole crystal filter nominal shape factor 1:6:1. Optional 600 Hz CW filter is available. Frequency Range: 3.5 to 4, 7 to 7.5, 10 to 10.5 WWV, 14 to 14.5, 21 to 21.5, 28 to 30 (Megahertz).

Unwanted Side Band Suppression: 55 dB down (at 1000 Hz).

Carrier Suppression: 50 dB down from full output.

Distortion Products: More than 25 dB down. I.F. and Image Ratio: More than 50 dB down.

Frequency Stability: Less than 100 Hz drift in any 30 minute period after

Antenna Impedance: 50 to 120 Ohm-SWR 2: I or less.

Audio Output: 1.5 watts, 350-2200 Hz, 8/600 Ohm impedance.

Power Source: 117 or 220 volts A.C. 50/60 Hz. Dimensions: $15\frac{3}{4}$ " wide, $6\frac{1}{4}$ " high, $13\frac{3}{4}$ " deep.

Weight: 45 pounds.

Built-in A.C. power supply.

★ Built-in 25/100 kHz calibrator.

★ ! kHz read-out.

★ Built-in VOX.

Built-in WWV band (to check calibration).

* Receiver incremental tuning.

Considered the best buy in amateur equipment available today, the FTdx560 features highpower, super sensitivity, and sharp selectivity, in one complete station package. Except for the addition of a microphone and speaker no other accessories are needed to be "On the air.

De luxe equipment built-in to the FTdx560 at no extra cost includes, A.C. power supply, dual calibrators (100 kHz and 25 kHz), VOX, Break-in CW with sidetone, clarifier, phone patch terminal, and WWV 10 MHz band. Full transceive capability 80 through the complete 10 metre band plus two optional auxiliary bands between 3-5-30 MHz.

The FTdx560 features velvet smooth tuning with zero backlash planetary gear system. Readout to within 300 Hz is easily obtainable when calibrated to the nearest 25 kHz marker. WWV frequency check to crystal calibrator assures "on frequency" operation on all bands.

DUAL TOROID first I.F. stage provides high gain/bandwidth product for double conversion tunable I.F. circuit used in the FTdx560. This system guarantees linear tuning rate plus high image rejection.

Twenty tubes plus forty-two silicon semi-conductors make up the active devices used in the transceiver. The passive crystal filter is of the six pole type designed

The FTdx560 was planned and designed specifically for the World Amateur utilizing standard electronic parts readily available from local sources. Yaesu warranties the FTdx560 for a period of one year following sale. Continuing service is available for your complete satisfaction.

Check the specifications and compare your cost. We believe that the FTdx560 is truly the best buy in the amateur field today.

YAESU PRICE LIST. FREE SECURICOR DELIVERY. MANUFACTURERS I YEAR GUARANTEE.

FT101 fitted 160m £255-00		AM filter FR400 £7.50	YC-305 Frequency counter	£97·50
FT 0 transceiver £249.00	FR400S DX Receiver, 160-2m. £160-00	FT560 Transceiver £195.00		£84.00
FVI01 Remote VFO £38.00 FL2100 Linear Amplifier £135.00	EL400 Transmitton £140.00		FP2AC Ac PSU for FT2F	£25-00
SPIOI Speaker for FTIOI £10.00		FT401 Transceiver £215.00	FP2AC/B AC supply with	
Fan FT101 £8.00	FL2000B Linear amplifier £135-00		batteries	£34.00
FT200 Transceiver £134-00		SP401 Speaker £10.00	Crystals for FT2F	£1-60
FP200 A€ supply for FT200 £38.00	FC2 2m. converter £12.00	FL2500 Linear amplifier £118.00	FP50DX Low pass filter	£6-60
	FC6 6m converter £12-00	YD846 Hand microphone £5.00	Mobile mount FT101	£5.00
FV200 Remote VFO for FT200 £38.00	CW filter FR400 £12.50	YD844 table microphone £12.00	CW filter FT101, FT401, FT560	£15.00


USED EQUIPMENT (3 months guarantee over (45)

Sommerkamp FL500. Excellent £100 Sommerkamp FL2000B. Superb £115 Digital 500. Demo-model £250


ELECTRONICS (UK) LTD



LARGEST STOCKS MASTS & ANTENNAS

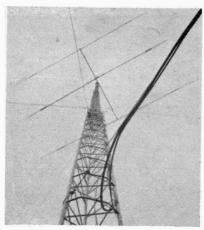

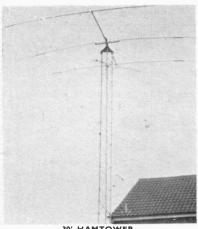The finest value in guyed galvanised steel towers which telescope down to 25ft. with climbing steps. Prices, carr. paid, 42' £72, 57' £93, 79' £121, 101' £161.



30' HAMTOWER

A self-supporting galvanised tower for H.F. band beams. Each 10' side weighs only 22 lbs., so the tower can be erected single-handed, Price 450-15 until April 1st.

TELOMASTS

These galvanised steel masts telescope down to 10'. They can be extended up to 30', 40' or 50' with antennas up to TA33 inn size and can be rotated from the ground. Prices are carr, paid. England and Wales, Scotland plus £1. Channel Isles plus £2.

Mast only	with	fu!l	Rigging	kit
30' £14-40		30'	£19.95	
40' £16⋅50			£25⋅50	
50' £19.50		50'	€31 - 50	

VERSATOWERS

Self-supporting telescopic and tilt over towers complete with head unit for pole extension or rotators 40′ £92, 60′ 80′ £222-30, 85′ £275, 60' £146.50, 120' £380 (guyed).

HY-GAIN 18 AVT/WB THE GREAT NEW WIDE BAND VERTICAL SELF SUPPORTING FOR 10-80M.

Take the wide band, omnidirectional performance of Hy-Gains famous 14AVQ/WB add 80 mtrs. plus extra heavy duty construction and you have the new I8AVT/WB 🛨 True ‡-ware resonance on all bands ★ 52Ω I/P ★ SWR of 2:1 or less at band edges ★ 1 kW (AM) * Radiation pattern has an outstandingly low angle * Roof or ground mounting.

Hy-GAIN (Carr. paid)	
Hy-GAIN (Carr. paid) Hy-Tower, 10-80m. 18V, 10-80m. Vertical	£99.50 £10.50 £16.50 £18.50 £88.00 £88.00 £48.00 £48.00 £48.00 £51.00 £51.00 £51.00 £7.50 £14.50 £14.50 £14.50

MOSLET ANTENNAS (Carr.	paid
Mustang, 3 ele. beam TA-33 Jr., Triband 3 ele. beam, 1½"	

Mustang, 3 ele. beam	アンス・コの
TA-33 Jr., Triband 3 ele, beam, 11"	£33.00
TA-33 Jr.E., As above for 2" mast	£33.50
TA-32 Jr., Triband 2 ele, beam 11"	€23-50
TA-32 Jr.E., As above for 2" mast	£24-90
Atlas, Vert. 10, 15, 20 and 40m.,	
2 Kw p.e.p	£20.00
• •	

WESTERN ELECTRONICS DIPOLES

Type S, Trapped dipole, 10-80m. Type P, Portable version, fitted with our copper terylene braid for ease of coiling up onto	£11.50
winding spools, 75ft. of coax, cord and weights	£14-90
Type HP, High power (I Kw. p.e.p.) version of above	£13-50
W.E., 2 ele. quad kit, complete Bamboos, set of 8, 15' long.	£27·00
Carriage paid	£5.50
Centre assembly, complete	£10.50
Gem Quad, fibreglass arms, 2 ele.	£65·00
Gem Quad, fibreglass arms, 3 ele.	
Gem Quad, fibreglass arms, 4 ele.	

ANTENNA ROTATORS (Ex stock)

CDR AR20 AR22 TR44 Ham-M		(P/P 40p) (P/P 65p) (P/P 75p) (P/P 80p)	£20.00 £25.00 £40.00 £70.00 £98.00
Hy-Gain 400	• • •	•••	£98 · 00

WIGHTRAPS for trapped dipoles

(Çarr.	20p)		
Standard High pow	ver (blue)	þair Þoir	£2.3!

J BEAM ANTENNAS (Carr. paid) -

10/4Y, 10m. 4 ele, array	£21 · 90
4/3Y, 4m, 3 ele, folded dipole	£3-85
4/4Y, 4m, 4 ele. folded dipole	£5-10
PM4/2, Coax harness to match	
2 x 4m	£4-10
2/4Y, 2m, 4 ele, folded dipole	€2.65
2/6Y, 2m, 6 ele. folded dipole	€3.20
2 8Y, 2m. 8 ele. folded dipole	€3 - 80
2/10Y, 2m. 10 ele. folded dipole	€8-20
	£10.50
2/14Y, 2m, 14 element yagi	£13.00
2/14P, 2m. 14 ele. "Parabeam"	€4.20
2/XD, Crossed dipole	24.70
2/10XY, Cross polarised 10 ele.	€11-00
yagi, l‡" boom	
2/0V, Omni or bi-directional	£6.50
2/8, 2m, Double 4 slot fed	£4-60
2/12, 2m. Double 6 slot fed	£6 · 15
2/16, 2m. Double 8 slot fed	£7.65
2/HO, 2m. Halo mobile aerial	£1-30
2/HM, 2m, Halo with #" mast	£1•60
PM2/2. Coax harness to match	
2 x 2m,	£2.60
PM2/4, Coax harness to match	
4 x 2m	£5.50
70/16, 70 cms. Double 8 slot fed 70/14Y, 70 cms. 14 ele. folded	€5-10
70/14Y, 70 cms, 14 ele, folded	£6.45
70/18P, 70 cms. 18 ele. "Parabeam"	£6.50
70/MBM/46 70 cms 46 ele-	
70/MBM/46, 70 cms. 46 ele. "Multibeam"	£9-60
PM/70/2, harness to match	
2 x 70 cm	€2.35
PM70/4 harness to match	
A v. 70 am	€5-25
4 x 70 cm	23.23

BANTEX FIBREGLASS MOBILE

MENIMES (Carr. Joh)	
70/1, 70 MHz 1 wave	£3-00
BGA, 144 MHz Mobile, BTN base,	£6+1!
2 wave 144/‡, 144 MHz Mobile with base,	10.13
# wave	£2.75
B5 144 MHz Mobile with base,	€4+35
Magnetic base for above; extra	24.33
cost in lieu of BTN or BM base	€4.95

MULTI-CORE CABLE (Carr. 40p)

	ype TR44 and the resistance exceed I ohm. O' run only of re is possible, 0076), unless	uire that hall not that a 4 1076) w mp (14)	M-M requi 2 wires sh is means t imp (8)·00 80' of 2 An	HA on I Thi I A or 8
10			ra cores a	
18p			mp. 4 wa	
23p			3 way	8
33p	þer m.		2 way	- 1
20p			mp, 4 co	
24p	per m.		core	
39p	per m.		2 core	
3.P	3/·0076, 7 ×	n		
20-				
28p	per m.		4/10076)	į.
	50' remote			
	E, TR44 and			
	(23/-0076)	10 wa	HAM-M	F
43 p	ber m.			
	per			

CATALOGUE. You ought not be without your copy listing towers, masts, antennas, rotators, Yaesu equipment and a host of other items. Send 15p only (no s.a.e.)

Hours of business: Monday-Friday, 9-5.30 p.m. Saturday, 9-12.30 p.m.

Money saving "package deals" on purchase of mast, rotator and antenna-H.P.—first rate terms 10% deposit, part exchanges and 24 hours delivery most parts of U.K. for £1 most items.

Midlands Agent: ANDY MARTIN, G3UDR, Shipston-on-Stour 61839 after 6 p.m.

Dept. SW4

OSBORNE RD., TOTTON, SOUTHAMPTON, SO4 4DN Rel. TOTTON 4930 or 2785 Cables "AERIAL," SOUTHAMPTON

YOUR MIDLAND **STOCKISTS**

AERIAL EQUIPMENT

Full range of "J" BEAMS in stock. 2 Mtr. and 70 cm. Please allow 50p for carr.

STOLLE ROTATOR. Type 2010, £24.50.

SUPER AERAXIAL CABLE 75 ohm, very low loss, 13p per yd. Also 50 ohm 300W, 25p per yd. P. and p. either 24p.

RIBBED CERAMIC INSULATORS, 12½p. DIPOLE CENTRE PIECE, 12½p. TRANSPOSITION BLOCKS, 5p. P. and p. 12½p.

COPPER AERIAL WIRE H/D 14G and 7/-029 Stranded, also 32/0-2 mm. covered, 140ft., £1-87; 70ft., 95p. Other lengths pro rata. (Lengths approx., sold by weight). P. and p. 24p.

TOUGH POLYTHENE LINE 100 lb. B/S ML1, 63p 100 yds. 200 lb. B/S ML2, £1·25 100 yds. 400 lb. B/S ML4, 21p per yd. P. and p. (any quantity) 12½p.

EQUIPMENT **EDDYSTONE ECIO**

£79.00 Mark II TRIO 9R59DS £57.50 TRIO 9R59DS with Cal. £60.00 TRIO JR310 £83.50 KW2000B £240.00 KW202RX £140.00 KW204TX £145.00 **KW 107 MATCHING** UNIT £40.00 KW 103 VSWR UNIT £12.50 **KW EZEE MATCH** £15.00 TRIO SP5D SPEAKER £4.50 RAYMART SUPER BAND CHECKER 1:8-35 Mc/s. £5.25 P. & p. 25p

CALSON DIGITAL CLOCKS:

£8.00 222 24 hour 601 24 hour £17.65 701 24 hour £13.35

Carriage paid

AERIAL EQUIPMENT

HALSON WHIPS, £7-40-COILS ONLY, £4-40.

G WHIPS RANGE EX STOCK-LIST.

AR22 ROTATOR, £25.45. Carr. 50p ARIO ROTATOR, £18-40. Carr. 40p AR44 ROTATOR, £40.55. Carr. 50p

KW TRAP DIPOLE, £15.00. KW TRAPS and INS., £4.50.

HI GAIN I4AVQ VERTICAL £19-50

300 ohm FEEDER, 4p per yd. 75 ohm FEEDER, 4p per yd. or 100 yd. DRUM, £2.50. P. and p. 20p. KW BALUNS, £1-95; HIGH PASS

FILTERS, £2.50.

FULL RANGE OF DIE-CAST BOXES, CHASSIS, PUNCHES, METERS, PLUGS, SOCKETS. S.A.E. WITH ENQUIRIES PLEASE.



The Widest Range of Components in the Midlands

Fast Mail Order CHAS. H. YOUNG LTD.

170-172 Corporation Street, Birmingham B4 6UD

At your service G2AK, G3LAY & G3VFV

Please print your address. No C.O.D. under £1.

'phone 021-236 1635

COME RAIN — COME SHINE

MOSLEY of England Antennae

Mustang. 3 band 3 elements Elan. 2 band 3 elements

TA-33 Jr. 3 band 3 elements TA-32 Jr. 3 band 2 elements

TA-31 Jr. 3 band dipole

V-3 Jr. 3 band vertical A-310. 10 metre 3 elements

A-315. 15 metre 3 elements

Atlas. 4 band vertical TD-3 Jr. 3 band trap dipole

RD-5. SWL amateur bands SWL-7. SWL broadcast bands

D-4BCa. Base loading coil for ATLAS for 80 metres TW-3X Jr. 20, 40 and 80 metre vertical

VTD-3 Jr. 3 band vertical for difficult locations

MOSLEY U.S.A. types:

MCQ-3B. 10, 15 and 20 metre Quad

MCQ-20, 20 metre Quad

Classic-33. 10, 15 and 20 metre 3 elements


Classic-203. 20 metre 3 elements A-92-S. 2 metre 9 elements

DI-2. 2 metre. Ground plane Other U.S.A. types to special order.

WE ARE THE ANTENNA

ROTATORS, TOWERS, **PEOPLE** CABLES, INSULATORS, ETC. ROTATORS,

THIS IS ANTENNAE TIME

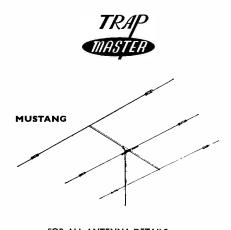

FOR ALL ANTENNA DETAILS:

Send for complete Handbook, containing full details and prices of Antennas and other technical information. 25 pages, 15p

Refundable upon purchase of an Antenna.

V-3 Jr.

Administrative Address only

Vasley Electronics Ltd. 40, Valley Road, New Costessey, Norwich, Norfolk Nor. 26K

Radio Shack Ltd

*

London's Amateur Radio Stockists

Just around the corner from West Hampstead Underground Station

USED EQUIPMENT FROM RADIO SHACK

DRAKE TR-3. Transceiver with P.S.U. and MS-4 Spkr.	£195.00
DRAKE RV-4 Remote VEO	£40.00
DRAKE R-4A. Receiver Hurricane" Transceiver	£140.00
HALLICRAFTERS SR2000 "Hurricane" Transceiver	
with P.S.U HALLICRAFTERS SR400 "Cyclone" Transceiver with	£450.00
HALLICRAFTERS SR400 "Cyclone" Transceiver with	
P.S.U. HALLICRAFTERS SX-122. General Coverage	£395.00
HALLICRAFTERS SX-122. General Coverage	C12F 00
Receiver	£125.00
HAMGEAR PM-I. Preselector	£5.00
HEATHKIT SB-310. Broadcast and Some Amateur	CLUE 00
Bands Receiver	£115.00 -
HEATHKII GR-/8. Transistorised, solid state,	640.00
General Coverage Receiver	C4F 00
HEATHKIT SB-300. Amateur Bands Receiver.	£43.00
10-80m	£95.00
HEATHKIT SB220, Linear Amplifier	£160.00
HEATHKIT SB-301. Amateur Bands Receiver. 3-5-	1100.00
30.0 MHz	£125.00
HEATHKIT. SB-600 Speaker	€10.00
KW VESPA Mk. 2. Transmitter. SSB, CW	£95.00
KW. 160 metre Transmitter	620.00
KAY. 100 metre transmitter	COE 00
KW 1000. Linear Amplifier	
KW ATLANTA with P.S.U. and V.F.O	
KW ATLANTA VFO	
NATIONAL NCX-5. Transceiver, 5 Bands (with	
P.S.U.)	£195.00

NATIONAL NCX-500. Transceiver, 5 Bands (wi	th
P.S.U.) NATIONAL XCU-27. Crystal Calibrator for NCX-	E/
NATIONAL XU-27. Crystal Calibrator for NCX- NCX-500	£9.50
SWAN 270 CYGNET. 5 Band Transceiver, built-	·in
AC and DC power supply	£200.00
AC and DC power supply SWAN 500. Transceiver and P.S.U	£195.00
SWAN 500. Transceiver and P.S.U	£210.00
SWAN 500C. Transceiver and P.S.U	£250.00
SWAN 410. VFO with 22 Adaptor, for Swan 350 or 5	
SWAN VX-I. VOX	£12.50
TRIO JR500SE. Amateur Bands Receiver. 10-80m.	£50.00
SOMMERKAMP FTDX500, 5 Band Receiver wi	th
CW Filter	£175.00
CW Filter	er.
AC/DC	£145.00
SOMMERKAMP FRDX500, Transceiver, 160-2m.	£120.00
SOMMERKAMP FLDX500. Transmitter	
SOMMERKAMP DX2000. Linear	£80.00
EDDYSTONE ECIO	£45.00
BC-1031-A PANADAPTOR. 455 kHz	£35.00
	£20.00
	£5.00
	£25.00
	£60.00
	£95.00
	£75.00
COLLINS 3510-2. Mobile Mount	£50.00
HEATHKIT SB-100. 5 Band Transceiver	£165.00

RADIO SHACK LTD.

182 BROADHURST GARDENS, LONDON, N.W.6.Just around the corner from West Hampstead Underground Station

Telephone: 01-624 7174 Cables: Radio Shack, London, NW6-3AY.
Giro Account No.: 588 7151



KW 107 ANTENNA Tuning SYSTEM



KW 202 RECEIVER, 10-160 metres SSB/AM/CW, with Mechanical Filter, built-in 'Q' Multiplier (Peak & Null),500 kHz VFO covering all Bands.

Two Speed VFO Drive. Excellent Sig./Noise and sensitivity performance. Very attractive (similar in appearance to KW2000B). 100 kHz Crystal Calibrator price £140 carriage extra.

2 Great Transceivers DELIVERY IMMEDIATELY, FROM STOCK

KW2000B 10-160 metres SSB TRANSCEIVER: 180 watts PEP 10-160 metres, complete with A.C. p.s.u., VOX P.T.T., I.R.T./I.T.T.

£240 carriage extra.

KW ATLANTA 10-80 metres. KW Atlanta and A.C. p.s.u.

£210 carriage

or separate units



KW 204 TRANSMITTER. 10-160 metres SSB/AM/CW. Successor to the famous KW "Vespa"—Perfectly matches the KW202 Receiver and is

similar in appearance. 180 watts p.e.p. from trustworthy 6146's. Built-in Power Supply. Provides "side tone" CW monitoring. A beautiful compact efficient unit. Price £145 carriage extra.

Matching KW1000 LINEAR AMPLIFIER for KW 204 and KW 2000B—also available. 1200 wat to pen max. Pair T160L/572B tubes including 2-5kv Power Unit built-in to KW2000B style cabinet £135 carriage extra. KW 101 Standing-Wave-Ratio meter, £9-25. KW 103 SWR/Power meter 0-100 & 0-1000 watts £12-50°. KW103 with Dummy Load and Coax Lead, £20-50°. KW 107 Antenna Tuning System including E-Z Match, SWR Ind., Dummy Load, Antenna Switch, 5 position, £40.00°. Also KW Trap Dipole with twin feeder and 4 other types (only the original Trap from KW is good enough for you). KW E-Z Match ATV, KW Low Pass Filters, KW & HZP Baluns, etc. *Carriage extra.



KW 202

SPEAKER

All Equipment Available through accredited agents

TRADE-IN EQUIPMENT AND MANY IMPORTED ITEMS AVAILABLE WRITE FOR DETAILS TODAY

K.W.ELECTRONICS LIMITED: 1 HEATH STREET, DARTFORD, KENT Tel.: Dartford 25574 Cables: Kaydublew Dartford

EASY TERMS ON EQUIPMENT AVAILABLE OVER 12, 18 OR 24 MONTHS

LOWE ELECTRONICS

119 CAVENDISH ROAD, MATLOCK, DERBYSHIRE, DE4 3HE

Tel. Matlock 2817 or 2430 9 a.m. - 9 p.m.

BILL G3UBO

ALAN G3MME

Service & Sales (evenings & weekends only)


John G3JYG 16 Harvard Road, Ringmer, Lewes, Sussex.

Ringmer 812071

Sim GM3SAN 19 Ellismuir Road, Baillieston, Nr. Glasgow.

041-771 0364

Main YAESU MUSEN CO. LTD. Distributors

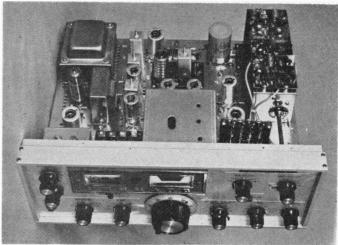

You know what the outside looks like, here's the innards.

FRdx400

Top band to 2m. ½ microvolt sensitivity, 4 true mechanical filters for no compromise. F.M., A.M., S.S.B. and C.W.

F.M. discriminator.

Notch filter.

Super de luxe version with all factory options fitted, £160.00

If you are thinking of a new Amateur Band receiver, you might as well get the best. Yaesu Prices. All equipment ex stock for immediate delivery, carriage paid, by Securicor (who deliver gently, usually in 24 hours).

	8- F	(denter genery, addairy in 21 nours).
	£240.00	FV-101 Remote VFO £38.00
	£10.00	FT-200 Transceiver £134.00
FP-200 A.C. p.s.u. for FT-200 .	£38·00	DC-200 D.C. p.s.u. for FT-200 £45.00
	£38·00	SP-400 Speaker £10.00
FR-400 Super de luxe Receiver .	£160·00	FL-400 Transmitter £140.00
	£135.00	FL2000B Linear Amplifier £135.00
	£215.00	FT-560 Transceiver £195.00
E14 401 B	£38.00	SP_401 Spanker
FT-2F 2m. Transceiver		SP-401 Speaker £10.00
	£5.00	YC-305 Frequency Counter £97.50
FT-101 Fan		YD844 Table Microphone £12.00
		FT-101 Mobile Mount

Coming: Yaesu low price receiver FR-50B and low price transceiver FT-75.

Incidentally, equipment of the calibre of Yaesu is getting awfully sophisticated these days and it needs some pretty sophisticated equipment to service it (to service it properly that is!). So be sure you get your Yaesu gear from someone who has the ability, the test equipment and the spares to do a proper job.

If you want to see what a good service department looks like-come and see ours.

H.P. a pleasure from 10% down and up to 3 years to pay.

Trade-ins. We are always happy to accept good equipment in trade. We are also prepared to buy equipment.

Repairs. The best, at reasonable prices either at Matlock or at any of our Service Agents :

Dave Dryden, G3BKQ

205 Main Street, Thornton, Leics.

Alan Bartlett, GW3YSA Peter Ward, G3XWX

35 Pen-Y-Waun, Efail Isaf, Nr. Pontypridd, Glam.

47 Radstock Avenue, Ward End, Birmingham, B36 8HD



Lowe Electronics

Second-Hand

Just a selection of second-hand items included in the following:—

Receivers:

Heathkit SB30	0 fitted	CW a	nd SSB	filters			£85·00
Lafayette HA-	500 Am	ateur i	Bands				£30.00
KW202		• • • •			•••		£115.00
Trio 9R59DS					•••	•••	£37.00
Eddystone 830	/2				•••		£175.00
Lafayette HA-	350	•••					£50.00
Trio JR-500							£40·00
EC Mk. I		•••					£38.00
Sommerkamp	FR-100	В					£75.00

Transmitters:

Sommerkamp FL-200B		 	 £80.00
Yaesu Musen FL-100	• • •	 	 £65.00

Transceivers

National NCX-5 and p.s.u.			National NC-200 and p.s.u £95.00
National NCX-3 and p.s.u.			Digital 500D (latest model) demonstrator £250.00
KW2000B and A.C. p.s.u.	 	£175·00	FE Super 600 £100.00
KW2000 and p.s.u			KW2000 and p.s.u £100.00
KW2000A and p.s.u			HW100 and p.s.u £105.00
FT-250 and p.s.u	 • • •	£125·00	Codar AT5 T28 mobile p.s.u. and remote switch £35.00

Carriage on second-hand goods £1.75

All our second-hand items are thoroughly guaranteed. They are checked, serviced and aligned where necessary before sale. Prices are very keen and you can thoroughly check the gear both on the bench and on the air before purchase. In addition, you have the protection of a full money-back guarantee.

Antennae Carriage paid.

Asahi 3 band 3-element trap beam £60.00 Asahi 40-10m. vertical £17.50

G-Whip, Tavasu, Diamond, etc.

Write for guff on Antennae

Sundries Carriage Paid.

Digital clocks—our well-known 12 hour Digitor at £5.50 or the 24 hour Copal 222 at £8.50 or the even more exotic 601 at £17.50.

Microphones-DM501 £3.00; Yaesu 846 £5.00; Yaesu 844 stand mike £12.00.

Filters—the well-known Medco L.P. filters 50 and 75 ohms at £6.50 and their equally effective high pass filter at £2.40. Crystal filters—K.V.G. XF-9B £18.00; XF-9C, XF-9D and XF-9M all at £16.00 each. Complete with carrier xtals and holders where applicable.

Dummy Load/Wattmeters. An accurate wattmeter, not to be confused with cheap and cheerful so-called power meters which are frequency conscious. These are a 50 ohm load and wattmeter flat to 500 MHz. Switchable 0-20/0-120 watts giving useful readings down to $\frac{1}{4}$ watt. On occasions, it is worth its weight in gold. If you don't fancy forking out the whole price, join up with a gang and share one, £32.

All the above prices post free

Coax Cable Postage Extra.

Bulk purchase allows us to sell the ever popular 50 ohm UR43 at a rock bottom 8p per yard.

Hours: Tuesday to Saturday 9-5.30 (closed for lunch 1-2 and all day Monday)

73 de Alan and Bill

THE SENATOR CRYSTAL BANK

TO THE POST OF THE

G3UGY

Phone: 01-769 1639

CRYSTALS FROM STOCK AT KEEN PRICES

SENATOR CRYSTALS: the first place to contact when you need good crystals quickly.

Here are just a few of the popular frequencies actually in STOCK now:

kHz		MHz		
100 in HC13/U	 £2.50	28:045 in HC25/U		£1-60
455 in HC6/U	 £1.75	28-500 in HC25/U		£1.60
500 in HC6/U	 £1.75	30-000 in HC6/U		£1-60
MHz		32-500 in HC18/U*	***	£1-60
1-000 in HC6/U	 £1.75	34-000 in HCI8/U*		£1-60
2-000 in HC6/U	 £1-60	34-500 in HC18/U*		£1-60
3-500 in HC6/U	 £1.75	35-000 in HC18/U*		£1.75
5-000 in HC25/U*	 £1-60	35-500 in HC18/U*		£1.75
7-000 in HC6/U	 £1.50	38-666 in HC18/U*		£1-35
7-520 in HC25/U	 £1-80	40.000 in HC18/U*		£1-60
7-755 in HC6/U	 £1-80	42-000 in HC18/U*		£1-60
9-000 in HC6/U	 £1.50	70-000 in HC18/U*		£2.00
10:000 in HC6/U	 £1.50	71-000 in HC18/U*		£2-00
10-245 in HC25/U	 £1-60	72-050 in HC18/U*		£1-75
11-000 in HC6/U	 £1.50	72:425 in HC18/U*		£1.75
19-500 in HC6/U	 £1-60	72-500 in HC25/U*		£1.75
24-500 in HC18/U*	 £1-60	72-525 in HC18/U*		£1.75
25:000 in HC6/U	 £1.60	96-000 in HC6/U		£2.00
26-500 in HC18/U*	 £1-60	116-000 in HC18/U		£2.80
	* = Also	in HC6/U		

TWO more stock frequencies: 454 kHz and 456 kHz in HC6/U, useful for side-band filters etc. at £1-75 each.

And here's our STOCK range of 8RAND NEW HC6/U 8 MHz for 2M: 8.002 8.007 8.012 8.018 8.021 8.0266 8.032 8.041 8.043 8.047 8.048 8.0555 8.058 8.061 8.070 8.081 8.092 8.100 8.104 8.107

All at £1-25 each, post free. These crystals pull well when VXO'd.

Here are some popular frequencies for VHF, home station, mobile channels and R.A.E.N. ALL IN STOCK:

8-0555 MHz in HC6/U for TX × 18 = 145-000 MHz 2M Mobile £1-25 44-7666 MHz in HC6/U for RX × 3 + 10-7 MHz

= 145:000 MHz 2M Mobile £1:80 8-100 MHz in HC6/U for TX × 18 = 145-800 MHz for RAEN £1-25

45-0333 MHz in HC6/U for RX X 3 + 10-7 MHz = 145-800 MHz for RAEN £1-80 12:975 MHz in HC6/U for RX X 12 - 10:7 MHz

= 145.000 MHz 2M Mobile £1.60 11-1916 MHz in HC6/U for RX × 12 + 10-7 MHz

= 145-000 MHz 2M Mobile £1-60 12-0833 MHz in HC6/U for TX x 12 = 145-000 MHz 2M_Mobile_£1-60

8-7825 MHz in HC6/U for TX X 8 = 70-260 MHz 4M Mobile £1-60 29-780 MHz in HC6/U for RX X 2 + 10-7 MHz = 70-260 MHz 4M Mobile £1-65

6-74666 MHz in HC6/U for RX X 12 - 10-7 MHz

= 70.260 MHz 4M Mobile £1.60 11-710 MHz in HC6/U for TX × 6 = 70-260 MHz 4M Mobile £1-60

You'll find the above frequencies may be suitable for your PYE Cambridge, Ranger, Vanguard and other makes of ex-commercial R/T gear for the well-used mobile call channels. Check up with crystal multiplication data and crystal spec. in equipment manuals for suitability.

116:000 MHz in HC18/U NOW IN STOCK at £2:80. Ideal for 2M converter for I.F. 28-30 MHz, thus dispensing with need for osc. multiplication.

160m. modification on the FT-101. See February 1972 Radio Communication, page 84 using 7-520 MHz in HC25/U. In stock at £1-80. PYE Cambridge 2nd oscillator crystal-change. See January 1972 Radio Communication, page 10 using 10:245 MHz in HC25/U. In stock at £1:60. 160m. modification on the JR-310. See December 1971 Short Wave Magazine, page 601 using 7.755 MHz in HC6/U. In stock at £1-80. 70cm. Converter—See December 1971 Short Wave Magazine, page 611 using 96-000 MHz. In stock at £2-00.

AVAILABLE SOON:

140-000 MHz and 130-000 MHz IN HC18/U. IDEAL FOR 2m CONVERTERS FOR I.F. 4-6 MHz and 14-16 MHz, THUS DISPENSING WITH NEED FOR OSCILLATOR MULTIPLICATION.

48-3333 MHz for \times 3 = 145-000 MHz 46-6667 MHz for Converter.

New facility at SENATOR enables us to REDUCE PRICES on many made to order units, as follows:

50 149-9	kHz in HCI3/U	£4-60
150 499	kHz in HC6/U	£3-85
450 500	kHz in HC6/U	£3.50
501 999	kHz in HCI/U	£4-50
1.000- 1.39	MHz in HC6/U	£3.20
1-40 20-00	MHz in HC6/U (18/U & 25/U over 5 MHz)	
20.00 - 59.99	MHz in HC6/U; HC18/U; HC25/U	£2.25**
60.00 - 79.99	MHz in HC6/U ; HC18/U ; HC25/U	£2.50**
80.00 -114.00	MHz in HC6/U; HC18/U; HC25/U	£3.00**
14-00 -140-99	MHz in HC6/U; HC18/U; HC25/U	£7-00
41.00 -175.99	MHz in HC6/U; HC18/U; HC25/U	£8.75
76.00 200.00	MHz in HC6/U · HC18/U · HC25/U	£12.00

Under 1 MHz to .01% tolerance. 1 MHz upwards to .005% tolerance. Closer tolerances by quotation.

Mail Order SENATOR CRYSTALS Dept. S.W., 36 Valleyfield Road, SW16 2HR

CONTROL CONTRO

C. D. TELECOMMS (L'pool)

44 IMPERIAL CHAMBERS 62 DALE STREET, LIVERPOOL, L2 5SX

Radiotelephones. Mobile 15 watts A.M. Part transistorised. Radiotelephones. Mobile 15 watts A.M. Fart transitorised.

12v. DC Transistor supply. Ideal for 4 metres. Complete with control box, cable, speaker, microphone and cct. Few only at giveaway price of £25

Limited number of above, less control box, etc. £20

A.M. Base Stations. Complete with mic and remote control unit. Lo-Band. Type approved. 8 only of these in cabinets.

F.M. Base Station. Complete with handset. Hi-band. One only at ... only at ...

All equipment air tested before despatch. Terms of Business: Cash with order. Callers by appointment. Cheques, P.O.'s made payable to C. D. Telecomms (L'pool) Carriage on mobiles £1.75. Base Stations £3.00.

All orders dealt with in strict rotation

SONTRONICS' sensational BANDSCANNER, the 7 transistor monitor Rx. Covering a wider frequency range than any other unit on the amateur market. The front end comprises a high sensitivity, untuned, wide band cascode RF amplifier covering the entire RF on the amateur market. The front end comprises a high sensitivity, untuned, wide band cascode RF amplifier covering the entire RF spectrum from 50 kHz to 450 MHz. Uses UHF silicon planar transistors. Pocket sized and self-contained in a strong moulded, white plastic case, measuring $4\frac{1}{2}$ " x 3" x $1\frac{1}{2}$ "; complete with telescopic aerial and miniature loudspeaker. Sensitivity preset to receive a 5 watt Tx, whether on Top band or Two, at between 100 and 200 marks. Mealter leads transmissions transmiss the stronger

yards. Monitor local transmissions; remember, the strongest signal predominates.

The demand is zooming, everyone has a use for the Bandscanner, the one and only "electronic ear." Send for the free data sheet—s.a.e. please! Only £8.80 each. P. and p. and insurance 20p. s.a.e. please! Only £8
PP3 battery 14p extra.
Mail Order only.

Official Orders Welcomed.

SONTRONICS 30 ASTBURY AVENUE, POOLE, DORSET, BH12 5DT Telephone: Bournemouth 58211

FROM HEATHKIT

SW-717 SOLID-STATE RECEIVER FOR THE JUNIOR SWL

4 bands 550–1500 kHz; 1·5–4·0 MHz; 4·0–10·0 MHz; 10·0–30·0 MHz. AM–SSB–CW. Int. speaker, Phone socket. Main and bandspread tuning. 240v. A.C. 14½ "w. x 5¾ "h. x 10"d. Weight 7 lb.



Kit SW-717

£31.50 Carriage 70p

GR-78 ADVANCED SOLID-STATE GENERAL COVERAGE RECEIVER

190 kHz-30 MHz in 6 switched bands. II transistors 5 FET's and 7 diodes. 500 kHz cal. AM-SSB-CW • Anl • muting Built in D.E.A.C. and charger. Double S/H above 18 MHz. Sens. 3 uV Built average. Operates 120/ 240v. A.C. or 12/15v. D.C. Int speaker. Bandspread. Size: $6\frac{1}{4}$ "h. x $11\frac{1}{2}$ "w. x 9"d. Weight 11 lb. Kit GR-78



£69.00 Carriage 50p

SB-301 HIGH PERFORMANCE RECEIVER **AMATEUR BANDS 80-10M**

Stab. 100 Hz per hour. Sens. 0.25 uV for 10 dB S/N. SSB filter 2·1 kHz at 6 dB 5·0 kHz at 60 dB (CW and AM options) 10 valves and 7 diodes. For 120/ 240v. A.C. operation. Size: 14½"w. x 6½"h. x 13½"d. Weight 17 lb.



Kit SB-301

£125.00 Carriage 90p

SB-303 LATEST SOLID-STATE ADDITION TO OUR LINE

Even better than the SB-301 but retains all original features using latest design techniques. Uses 27 silicon transistors. (Including 4 dual-gate diode ing 4 dual-gate diode protected MOSFET's). Full RTTY provision. For 120/240v. A.C. Size: operation. Size: 12½"w. x 7½"h, x 14"d. Weight 15½ lb. Kit SB-303



£175.00 Carriage 90p

SB-310 SEMI GC RECEIVER CIRCUIT AS SB-301

Covers 6 SW bands + 80-40-20 Amateur (500 kHz on each band with options). SSB-AM-CW with filter options. Designed for discerning SWL and for professional use. For 120/240v. use. For 120



Kit SB-310

£125.00 Carriage 90p

HR-10B 7 VALVE AMATEUR BANDS **ONLY 80-10 METRES**

SSB-AM-CW. Opt. 100 kHz Cal. R.F. Amp. for extra sensitivity. Int. xtal filter. Sens. I uV at 10 dB. Image rej. 40 dB. Operates from 110/240v. A.C. Require ext. speaker. Size: 13½"w. x 11½"d. x 6½"h. Weight 20 lb.



Kit HR-10B

£44.00 Carriage 80p

Please	send	Heathkit	Catalogue	
--------	------	----------	-----------	--

Name	
Address	

ATTRACTIVE CREDIT FACILITIES AVAILABLE

10% Deposit 12-24-36 Months: Please note that on any credit agreement the service charge will be refunded if you complete payment within 3 months. After 3 months an early settlement discount of 5% on the final outstanding balance is given.



HEATH (Gloucester) LTD., GLOUCESTER GL2 6EE

SW/04/72

a Schlumberger Company

NEW FROM PARTRIDGF

We've all heard about the frustrated apartment dweller who planted his earth lead in a flower pot! (by the way they now use soil-less soil and plastic water pipes, just to complete your frustration). Well, PARTRIDGE solved your AIR SPACE problems over 10 years ago—WE HAVE NOW SOLVED THE OTHER END OF YOUR PROBLEM WITH

THE JOYMATCH ARTIFICIAL EARTH
BANDSWITCHED FOR PROVIDING AN EXTREMELY EFFICIENT INDOOR ARTIFICIAL EARTH. HAS PROVED
ITSELF SUPERIOR ON TEST TO A REALLY EFFICIENT AND ELABORATE "SOGGY" OUTDOOR EARTH. GREATLY IMPROVES RADIATION AND RECEPTION ON ALL AMATEUR AND SHORT WAVE BROADCAST BANDS. COMPRISES SWITCHED BOX, PLUG-IN RADIAL FOR LAYING AROUND THE WALLS OF THE ROOM/ SHACK AND TERMINATED PLUG-IN LEAD FOR CONNECTING TO TRANSMITTER OR RECEIVER. VERÝ ATTRACTIVE APPEARANCE. ONLY £4.50 + 30p P/P.

THE JOYMATCH AERIAL BANDSWITCH ALSO NEW!!

A compact, simple to operate, indoor or outdoor AERIAL SYSTEM suitable for ALL types of RADIO RECEIVERS that tune over the MARINE BAND (2-4 MHz) "TRAWLER" BAND, AMATEUR BANDS (160, 80, 40, 20, 15 and 10 metres) and the World Wide Short Wave Broadcast Bands (75, 49, 41, 31, 25, 19, 16, 13 and 11 metre bands)-COMPLETE SHORT WAVE COVERAGE.

SIMPLE, NON-TECHNICAL OPERATING INSTRUCTIONS are supplied with each JOYMATCH AERIAL BAND-SWITCH comprising the attractive BANDSWITCH BOX, RADIO AERIAL and terminated lead for connecting to SEND ONLY £4.50 + 30p P/P. your RECEIVER.

THESE PRODUCTS ARE NEAT IN APPEARANCE—FOOLPROOF IN OPERATION— BRAND NEW ADDITIONS TO OUR WORLD FAMOUS RANGE

Dept. SE

Send 3p stamp for full details of ALL our SPACE AGE antenna/earth products to:-

Telephone (Thanet) 0843 62535



R. T. & I. ELECTRONICS LTD.

where equipment is fully overhauled

EDDYSTONE ECIO Mk. I			•••		£45.00 (£1.00)
HALLICRAFTERS SX 117	,				£115.00 (£1.50)
HAMMARLUND HQ 170)				£150-00 (£1-50)
LAFAYETTE HA-600					£36.00 (£1.00)
LAFAYETTE HE-80		• • •	•••	•••	£48.00 (£1.50)
	•••	• • •	• • • •	•••	
LAFAYETTE HE-30	•••	•••	• • • •	• • • •	£25.00 (£1.25)
HEATHKIT MOHICAN			•••		£35.00 (£1.25)
NATIONAL NCX-500 Tr		iver	c/w a.	c. p.s.u.	
HAMMARLUND HQ-145	-X				£135-00 (£2-00)
RCA AR88D					£70.00 (£2.00)
LAFAYETTE HA-63					£22.00 (£1.00)
HAMMARLUND HQI80	•••		•••		£150.00 (£2.00)
	• • • •	***		• • • •	
HEATHKIT GR64					£25.00 (£1.00)
EDDYSTONE 840A					£35.00 (£1.50)
KW 201					£90.00 (£1.50)
KW VESPA II c/w p.s.u.					£105.00 (£2.00)
KW 77					& £80.00 (£1.50)
HALLICRAFTERS S 240 a					£35.00 (£1.00)
		,			
EDDYSTONE 940, as new	· · · ·	•••			£135.00 (£1.50)
		. .			

WE CAN ALSO SUPPLY ANY MAKE OF NEW EQUIPMENT—and have pleasure in giving a few examples which are normally in stock:—

ANGLIA, 2 metre converters (state I.F. required), £15.00 (30b).

ANGLIA, 2 metre converters (state I.F. required), £15.00 (30p).

AVOMETERS, Model 7, Mk. 2, £37.60; Model 8, Mk. 4, £49.90; Model 9, Mk. 4, £40.90; Model 40, Mk. 2, £37.60; Model 8, Mk. 4, £40.90; Model 40, Mk. 2, £37.60; Multiminor, Mk. 4, £13.50; Standard leather carrying case (Models 7, 8, 9, 40), £6.50; Every-Ready dicto, £7.40; Multiminor leather case, £3.91; IOKV D.C. Multiplier for Model 8 or 9, £6.10; 30KV D.C. ditto, £9.90; Pair of Long Reach Safety Clips, £1.90; Model EAI 13 Electronic Avo, £82.00. All above post free in U.K. Trade and Educational enquiries invited.

S. G. BROWN'S HEADPHONES, Type "F" 120 ohms, 2,000 ohms, 4,000 ohms, £4.95 (25p); Rubber earpads for same, 45p per pair (5p). Type 3C/1100 Noise excluding (with superb fitting), high quality, electrodynamic, £7.55 (25p). Standard Jack Plugs, 24p (4p).

EDDYSTONE EQUIPMENT, Receivers, 830/7, £372.75; EA12, £205.00; EC10/2, £79.00; EC10/1, £64.50; 924 Ac.C. mains ps.u., £7.75 (50p); Doublet Aerial, 731/1, £5.28 (50p); Plinth Speaker, 906, £6.20 (50p); Ceneral Purpose Speaker, 935, £5.55 (40p); Edometer, 902 Mk. 2, £29.50 (50p); Telescopic Aerial, LP.3126, £2.50 (25p); Diecast Boxes from 45p (10p). Brochure on request.

CODAR EQUIPMENT, ATS Mk. II, £22.50 (50p); PR 40, £8.50 (3p); PR30, £7.50 (25p); PR30x, £9.50 (25p); Leaflets on request.

Our latest list of over 50 receivers, and many other

Our latest list of over 50 receivers, and many other interesting items sent free upon receipt of your sale. Carriage for England, Soutlead and Wales shown in brackets. Terms: C.W.O., Approved Monthly Accounts, Hire Purchase and Part Exchange. Special facilities for export. Enquiries

At R.T. & I. We have full H.P. facilities

Part exchanges are a pleasure We purchase for cash

We offer a first-class overhaul service for your electronic equipment, whether you are an amateur

or professional user
We have EASY Parking facilities

We welcome your enquiries for specific items which, although not advertised, may very well be in stock.

PARTRIDGE "JOYSTICKS," "New Lightweight VFA" £12-99 (30p). "JOYMATCH" III. Aerial Tuning Unit, £12.99 (30p). Literature on

TRIO EQUIPMENT, Transceiver, TS-510 + PS-510 a.c. p.s.u., £180·00 (£2·00); VFO-5D for above, £25·00 (50p); Receivers, JR-599, £185·00 (£1·00); JR-310, £77·50 (£1·00); JR-500-SE, £65·00 (£1·00); PS-59-DS £47·50 (50p); SP-5D Loudspeaker, £4·37 (40p); Headphones, HS-4. £5·97 (20p). NEW TR-599 TRANSMITTER (to match JR-599), £185·00 (£2·00). Leaflets available.

SHURE MICROPHONES, 444T, £15.00 (40p); 444, £13.00 (40p); 401A, £6.50 (30p); 201, £5.40 (30p); 202, £6.00 (30p). Full details on

KEYNECTORS, piano key mains connector units, £2.75 (25p).

VALVES. Please state your requirements.

TMK METERS: TMK500, £8-25 (25p); TW20CB, £10-25 (25p); TP50SN, £5-75 (25p); 700, £16-50 (25p); also leather cases.

PHILIPS PM2403 ELECTRONIC MULTIMETER, £49 (25p).

We also supply PHILIPS and KORTING COLOUR TV TEST EQUIP-MENT, including Colour Bar Generators, Convergators, etc.

MENT, including Colour Bar Generators, Convergators, etc.

KW EQUIPMENT, KW2000B + A.C. p.s.u, £240.00 (£2.00); D.C. p.s.u,
for KW2000B, £44.400 (50p); KW 2000B only, £200.00 (£1.50); KW

ATLANTA + A.C. p.s.u, £200.00 (£2.00); Remote V.F.O. for Atlanta,
£34.400 (50p); YOX unit for Atlanta, £7.50 (25p); Remote V.F.O. for
2000B, £36.00 (50p); KW1000 Linear amplifier, £135.00 (£1.50);
KW202 Receiver with calibrator, £140.00 (£1.50); KW 202 Matching
Spkr., £8.00 (80p); KW204 Transmitter, £142.00 (£2.00); KW105
combined E-Z Match; YSWR indicator, dummy load, and ant. switch
(4 outlets) \$2.015, S0 (45p); KW102, WSWR meter, \$2.015, S0 (45p); KW102, WSWR and power meter,
\$52 ohms, £12.50 (45p); KW101, YSWR meter, \$2.07 75 ohms, £9.25
(30p); KW 107, £40-00 (50p); KWSWR, dummy load, trap dipoles,
etc., etc. Details on request.

R. T. & I. ELECTRONICS LTD.

Ashville Old Hall, Ashville Road, London, E.11 Tel: 01-539 4986

ADVERTISERS INDEX


	PAGE
Amateur Electronics (G3FIK)	120
Relding & Rennett (Morce)	127
J. Birkett "BoomMike"	124
"BoomMike"	127
D T D C	116
TD 1771 - 4	123
C.D. (F-1	
C.D. Telecomms Colomor Electronics, Ltd.	74
Colomor Electronics, Ltd.	121
Derwent Radio	116
E. & E. Services	116
Echelford Communications	122
Eddystone Agents	67
General Merchandise Credit,	
Ltd	117
G.W.M. Radio	122
Hamgear Electronics	126
Heath (Gloucester) Ltd	75
Holdings Photo-Audio Centre	,
(Trio)	127
imnois	125
Johns Radio	128
K.W. Electronics	71
T D - 41 -	123
T 1911	72
3.5 (*)	127
Markham Electronics	121
Minitenna Communications	116
Mosley Newbery, Graham	70
Newbery, Graham	126
North West Electrics	_
inside bac	
P. & P. Developments back	
Partridge Electronics, Ltd.	76
Radio Shack, Ltd R. T. & I. Electronics, Ltd.	71
R. T. & I. Electronics, Ltd.	76
Senator Crystals	74, 127
Shure Electronics	65
	121-127
Smith, G. W. (Radio)	
inside fron	t cover
Solid State Modules	117
Sontronics	74
Spacemark, Ltd	124
SSB Products	117
Stephens-James	120
a	125
Strumech Engineering	123
S.W.M. Publications <i>back</i> 66, 67, 118, 1	<i>c cover</i>
Tours Flortwicel Convices	17, 120
Taurus Electrical Services	116
The Amateur Radio Shop	117
The Trading Post	127
Trio Electronics Inc	78
Western Electronics Ltd	68, 69
Chas. H. Young (Amateur	
Radio) Ltd	65

SHORT WAVE MAGAZINE

(GB3SWM)

Vol. XXX	APRIL	, 1972				No	o. 342
	CONT	ENTS					
							Page
Editorial—Frustrating					•••	•••	79
Communication and DX N		. Esse	ry, G3	KFE	•••	•••	80
The Mobile Scene			•••				87
The HW-17A Modified f by C. P. Howard, G82		Perio	rmance	on T	wo Me	tres,	88
The Eddystone 888A, by I			R.E., C	30GR			90
Points of Interest							92
Transistor Transmitter for	Top Band.	bv R.	Gould.	stone. C	3TAG		93
Miniature Monitor/Oscilla	• '	•					100
The Physics Society Exhi			•••				101
Low Power NBFM for Sev	,		nghluth	. F6AF			102
Tone-Modulated Oscillator	• , .		_			•••	103
VHF Bands, by A. H. Dor	•	•					104
The Month with The Clubs	•		•••		•••		110
New QTH's							115
· · · · · · · · · · · · · · · · · · ·							
Magaging Editor: AU	STIN FOR	RSYT	Н, о.	в.е. (G	6FO/	G3S\	WM)
Adv	vertising: Ma	ıria Gı	reenwo	od			
Published at 55 Victoria Si month, dated the month f				r, on the ne: 01-			
Annual Subscription:	Home Verseas: £2	e: £2·: 75 (\$7·	75 (£3 ·00 U.	·00 firs S.), pos	st class t free s) post urface	paid mail
Editorial Address: S	hort Wave	Magaz	ine, B	UCKIN	IGHAN	И, En	gland
	AUTHO	RS' M	SS				
Articles submitted for Edwith wide margins on one should be lightly identified sheet. All drawings and dof values prepared in accordissue. Payment is made acceptance that full copyrights	side only of quited in pencil of in pencil of ingrams show the office with officer all mates.	uarto o n the o ld also our nor crial u o the S	or fools back v be sho mal se sed, a	cap she with det own sepo tting co nd it	ets. I ails on arately, onventions is a c	Photog a sep and on—se ondition	raphs parate tables e any on of

© Short Wave Magazine Ltd.

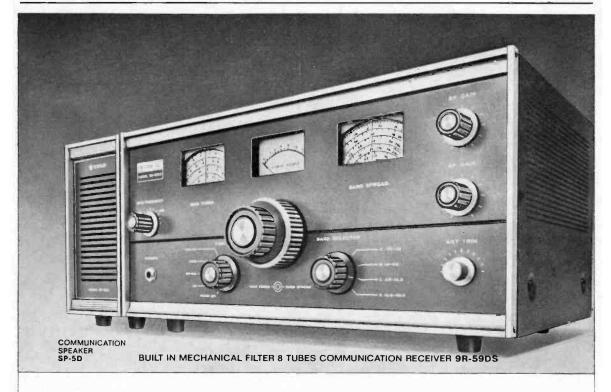

Shortwave Success Always With TRIO's 9R-59DS

TRIO have the complete communications receiver in the 9R-59DS. A true example of the best in professional test equipment, the intrepid amateur can confidently operate this instrument with a 1.5 watt power output. With 8 vacuum tubes and 7 diodes, the 9R-59DS has a power consumption of 45 watts. Rely on full speaker range with the 9R-59DS with its $2\mu V$ sensitivity and optimum selectivity of—50dB. The most modern communications refinements are incorporated in every feature. Total reliability.



SPECIFICATIONS:

• Frequency Ranges: Band: A 550-1600KHz. B 1.6-4.8MHz. C 4.8-14.5MHz. D 10.5-30MHz: • Sensitivity: 2 μV for 10dB S/N Ratio (at 10MHz): • Selectivity: ±5KHz at −50dB • Power Consumption: 45 watts: • Audio Power Output: 1.5 watts: • Tube & Diode Complement: 6BA6×3, 6BE6×2, 6AQ8×2, 6AQ8×2, 6AQ5, SW-05×2, SW-05×2, IN60×2 • Dimensions: Width 15°, Height 7°, Depth 10°.



TRIO ELECTRONICS, INC. 6-5, 1-chome, Shibuya. Shibuya-ku, Tokyo, Japan Sole Agent for the U.K. B.H. MORRIS & CO., (RADIO) LTD. 84/88, Nelson Street, Tower Hamlets, London E.1. Phone: 01-790-4824



EDITORIAL

Frustrating

Last month in this space, we had to explain production difficulties associated with the electricity supply failures.

Since then, we have become involved in another sort of hang-up on the mechanical side—the printing unions are working out a dispute with their managements, which directly or indirectly affects all print production outside the London area. It is neither our purpose nor our function to attempt to inform readers on the issues involved—it is enough to say that any such dispute must lead to what (for us, as for many other periodicals) are considerable difficulties, quite beyond our control, in getting an issue out and also in giving full coverage of all the news reaching us.

The issue now in your hands has been produced in just this situation. To enable us to continue to meet our commitment to get Short Wave Magazine out and on time, readers can do a great deal to help.

In the first place, let all your contacts know (over the air and otherwise) that, for the time being, we are in same position as most periodicals dependent on the normal processes of print.

Secondly, let us have whatever you want to get into the May issue—Activity Feature reports, Club news items, Small Advertisements, and so forth—just as soon as you can. Though in this issue we do give normal deadline dates for the next, in fact they should be regarded as somewhat unrealistic. At the moment of writing, it is not possible to say what, in reality, they ought to be. For instance, for this issue we had to anticipate the production of Editorial material (which means all that goes in the body of the *Magazine*) by a full week, meaning that much in the way of news came in too late, and is now dead for May.

Thirdly, accept our assurance that all concerned with the preparation of Short Wave Magazine for press are doing their utmost to overcome what we all hope will only be a temporary difficulty.

Aus hin boxish, GEFO.

COMMUNICATION and DX NEWS

THIS month, we are starting to write the piece much earlier than usual, because of possible "delays in the system" while a printing dispute is being worked out, which means some regular correspondents may be missing, the piece having left these hands before their letters could be taken in. To such, and to any readers who find the offering somewhat lacking in meat as a result, our apologies—we promise to try and do better next time!

The Bands

Not bad at all, by and large. The falling of the sunspot number has made quite a difference, of course, as it has gone from the eighties down to the low fifties a year later, which will make a noticeable difference. Nonetheless, harder going or not, this time of year invariably sees much of the high activity and the DX QSO's.

Naturally, Ten has fallen away, and Fifteen to a lesser degree, while Twenty is not staying open so late as of yore in the evenings—but the counterbalance is in the improvement in DX conditions on 1.8, 3.5, and 7 MHz caused by the reduction in absorption effects. Indeed, Forty should be yielding something of interest almost round the clock, given a decent aerial system (and appropriate QRM suppressants!) So . . . let's look at it all, as seen through the eyes of the beholders.

Ten Metres

Naturally, a shortage of reports—half the trouble at least with Ten is lack of activity, as most of the big contests seem to demonstrate.

First we hear from W6AM (Long Beach), who mentions QSO's on SSB with CR6IY, HC1RF, ZP5AQ and CP1EU, all around 1800z and all on approximately the same frequency, 28.5 MHz.

Also "over there" is W4WFL/1, although by the time this is being read, Morgan will be operating in Europe under some quite interesting calls, using his modified SBE-33 transceiver for all this; the modifications comprise fitting of a CW

facility and, in addition, coverage of all of the bands 80 to 15 metres. This is not to say W4WFL/1 does not show up on Ten, at least from home—he does, and recently booked in TG9YN and VP2LAT just to prove it.

A new correspondent, and very welcome, too, is G3JFF (Cowplain, Hants.), who runs 150 watts of SSB or CW to a "5RV". Results have been quite good of late, thanks to conditions. Ten CW yielded contacts with EA8BK, ZS3AW, OD5LX, VU2AAA, CR6AI and ZS6OS, with VP2AAA as the prize gotaway.

An HW-101 and a bit of wet string serve as his weapons, but G4AMJ seems to have deployed them well enough, SSB having produced VU2JM and ZE1DI, and CW CT3AS and a string of W1-4 types.

Low sunspot count or no, G2DC reckons there have been several days on which WAC could be made. with an opening as early as 0700z to UL7 and that part of the world, gradually spreading Eastwards, and to Africa, then about noon the first W's coming in and coverage Westwards later to bring in all districts by about 1700. As for conditions to VK, they have been somewhat erratic, but this may have been to some extent the old bogey of activity, since it is nearly always the same VK chaps one runs across. his 10m. contacts were CW, with such as C8CQ (a new one for the band) FG7TG, EP2PR, JA1NW, JA6JML, JA7AT, JH1TGO, KZ5MS, LU8EQI, PY2AME. OX3AB, RAØLAY, TY7ABM, UA9SA, UA9MC, UA9NAD, UA9UAR, UD6AS, UL7GAU, UL7GAN, UL7SAC, UL7PAO, UI8AFI, UH8HAF, VP2AAA, VK5GM, VK6SA, VU2AAA, ZE3JJ, ZS1A, ZS3AW, ZS5NQ, ZS5KI, ZS6KT, ZL1ADD, all W call areas, and VE1-7.

Fifteen

Here pride of place must go to the return of old-stager G8DI

E. P. Essery, G3KFE

(Liverpool) who seems to have stuck to CW with his TR4 by Drake. One notes JY6FC, KR8BY, KH6HGP, 5T5CJ, EP2PR, 6W8AL, EA9OG, VP2LY and HI3JEI all taking the G8DI bait; the escapers numbered among them KR6KC, ZE1JL, XE2BG, KG6ALV, 8P6BU, 3B8RS, and TG9NJ.

Quite a lad is G4AMT (Penzance), one way and another. That Ouad of his blew down, but was eventually re-erected with enough guys, Terry says, to keep the Post Office Tower upright. Rather than leave Fifteen alone while the Quad was down. Terry loaded up the 7 MHz dipole and promptly worked VK6PM and VK6CF, over the top of hills of 200 feet coming within fifty yards of the station, which must act as pretty effective screens. Once the Quad was back in the air, Terry made his first three QSO's by way of FL8MM, JY8JK, and VU2JM! For the rest, there were such as MP4MBC, VU2HLU, JY6FC, W1-5, W8-0 and VE1-3, 9K2BQ, OD5ET, EQ2KH, EQ2SW, EQ2TB, ET3DS, 9M2MN, 5Z4MO, FC9VN, ZC4LC and CT2BG.

For W6AM, the only contact considered worth a mention in his letter was KS6DH, hooked on Fifteen right at the LF end of the Phone area, for an SSB exchange of RS59.

G3JFF found the band quite lively but not as full of interest as Twenty, but his CW tickled the palate of EA9EO, 5T5CJ, EQ2BQ, ZS6OS, ZS6AL and OD5LX.

As for your poor old scribe, his view of the band is simply that every time he goes on it the lesson is rubbed home that he badly needs both a beam and a hefty linear; to which his ambitions have got no further than a cabinet for the linear and a rotator for a beam!

An interesting situation arose for G2HKU (Sheppey) who was working a string of W's on Fifteen, when quite suddenly the band folded up and there was—silence! Just like Ten, even to the 599 signal reports just before the calamity.


Since his operating time has been a bit limited by the slow departure of the screws, G2DC (Ringwood) has not given much attention to the band, saving one spell during the Phone leg of the ARRL shindig, when ninety minutes of SSB operating resulted in 143 W QSO's, just to prove Jack could still show some DX operators a trick or two!

G4AMJ only managed a look at 15m. while he was /A from G4AMT's shack, but in that period he did raise on SSB FL8MM, JY8JK and VU2HLU, which must have encouraged him a bit, since he then went home and worked KP4BCL, also UI8BL, WB4QVG, UK9HAA and a string of Europeans on CW.

Twenty Metres

Sad to say, complains G2HKU, he has not yet found a way of going without sleep-unlike the contest experts!-and the rest of his time is taken with such sordid things as working and other unmentionable necessities. As if that were not bad enough Ted has a very justifiable gripe about some of the I1 stations; one well-known "Eye Wan" was on at the time Ted wrote and he was spreading a measured 18 kHz across the band! It is true most of us go "over the top" at times, but a normal rig will not produce splatter of that magnitude unless it is being overdriven to a point which is painfully evident by a glance at the PA current meter on the linear. G3KFE recalls his operation with the Hallicrafters SR-400: One could literally put volts on the mike socket, but it would not allow itself to be goaded into producing any significantly powered splatter, no matter what. That I1 station was going the right way to wreck his output bottles! On a happier note, Ted managed to find time for a CW QSO with UK9WAA, and SSB chats with JD1ACF (Bonin), UWØIF, ZL1HR, ZL1VN, ZL1WE, ZL2AUX, ZL3FO, ZL3SE and EQ2SW.

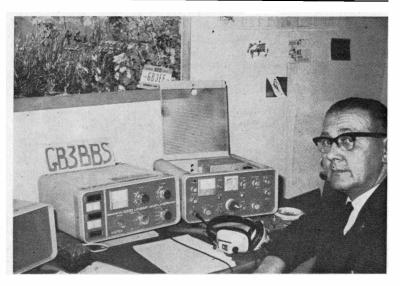Ed at G3XTJ (Palmers Green) has been bashing at the DX again, when he could spare the time from bashing the QRM on Forty, and on Twenty he came up with A2CAE, 5R8AP, DU1DBT, XE2ID, MP4M, 9M2, HS, VK, ZL, VS9, 4S7, 5X5 and 9V1. And he says that anything



G3JPN operating GB3BBS, Bingley Hall, Birmingham, on the occasion of the Boat Show there during February 12-26. The gear shown here is a KW-2000A with a KW linear, which worked into a KW trap dipole on the roof of the Hall. Contacts world-wide were made during the period of the Exhibition, this being the annual M.A.R.S. contribution to the Show.

done away from Forty is a mere sideline!

Still soldiering on, G8DI seems to have had rather mixed luck of late; he notes QSO's with TY1ABE, HK1QQ, FG7TG, 9V1QK, UH8CS, EA9EO, W7OHR, YV5DRN, VP2GLE, UH8CW and FM7AI, but the gotaway list includes 5R8AB, PZ1AP, LX1SN, TU2CV, OY1R, JW6FP, VP2AAA, CN8CF, FG7AA, HK2DP, ZD8JT, OX3AY and KL7CYL.

As has been often said, G4AMT does not like Twenty, but this month Terry admits this is mainly a function of his receiver, which we gather is not so hot; however, he did try the band, to work an assortment of Europeans and HV3SJ.

W4WFL/1 has been having sessions on Twenty, thanks to its later activity with the changing season, his new ones on SSB including CR7GJ, VP2SG, 6W8AL and 9G1WW, while CW also added to the score by way of KS6DY, OD5EJ, 3D6AF, 7Q7AA and 9H3C.

Strange to relate W6AM, who usually seems to devote most time to 20m. only mentions a couple of contacts, with KC4USA, on Sideband, and KC4USP, CW. Incidentally, the latter was the first time your conductor recalls W6AM getting a report worse than 59 on

Twenty—this time he was down to 569. There's hope for the rest of us yet!

Both modes are shown in G3JFF's report. To look at the CW list first, we see VE6VK, VE7EG, VK2EO, VK2BQQ, ZL2AI. ZL2ASM. ZL2AFZ, UH8CS, UA5ØA, ZD9GA. JA3XKJ, TY1ABE. UAØIT. VP8LK. XE1FFY, OX3ZO, ZS6S, ZS6AL, CR6AI, ZL3IS, PY2SO W7PHO, while SSB accounted for 5Z4NM, 5Z4DW, VQ9DM and ZS6XF. As for the gotaways, there TG9NJ, are TI2MV. 7Q7BC. VP2GSY and 9Y4MM on this list.

From SWL Ellis of Guildford, we hear that VK4SU, who has been on six metres exclusively, and has not used Twenty since his spells from October '68 to April '69 and (portable) in late 1969, has been receiving cards which indicate the presence of a pirate on the band—which, rightly, annoys him.

An amusing letter from G5CS (Esher) decries the use of the term "old-timer" in the Amateur Radio sense—after all, Gerry may be 65, but he still likes looking at miniskirts, and driving a Lotus Elan. Anyway, he says, the old-timers generally know a lot less than today's youngsters! Be that as it may, Gerry was on Twenty one day

with a net of eight "doddering old greybeards" which included G6DW, GM5NW, G5CS himself, VK3AD (who is ex-G6TM), VK3OG (ex-G6OH), and a distinguished visitor in the VK3AD shack in the shape of W8GZ of Windom aerial fame. Of this group the "youngest licence" was first issued in 1928, the oldest in 1914; and G2DX was around on channel but did not quite make a QSO, for he would have been able to go back almost to coherer days!

BRIEF DX DATA

Call

Details

XUIAA Operator VO2AH is from Cardiff; QSL's from VE7IR/XU are quite OK for DXCC credit.

WS3VOA Special prefix to commemorate 30 years of VOA broadcasting!

XT2AF SSB signal at S9, 1700 to 2000, 14100-14200 kHz usually; Nil is ex-TJ1AU. QSL to N. Belanger, Box 127, Bobo Dioulasso, Volta Republic.

VR1AA Looks for Europeans, 14027, 0615-0730z, 3504, 3528, 7002 kHz, 0645-0700z.

C2... C21AA, 14 MHz SSB, 1135z; C21DC worked 181PB at 0640z; C21TL, 14312 SSB, 1500z.

ASITY New call for Yonten, was ACSTY; 14195 kHz, around 1700-1800z with 4S7AB as m.c.


W9IGW San Felix. About April 7, /CEØX for four days. CW/SSB operation, all bands including 160m. QSL's via K3RLY.

UA5Ø... Special prefix U.S.S.R.; five stations will visit each Republic in turn, using calls of this form, as, e.g. UF5Ø., between March 1 and e.g. UF5Ø., June 7 in all. Each stop for a week. Award. USSR-50 for 15 QSO's with the special stations, 35 other U.S.S.R. stations, and there will also be trophies to be Mail by June 22.

for QSL's.
14228 kHz, 0630z, S9
SSB signal, QSL to
W50LG, or direct to
Box 1, Adamsville, Pitcairn Island.

to USSR-50, Box N-88,

Moscow, also the address

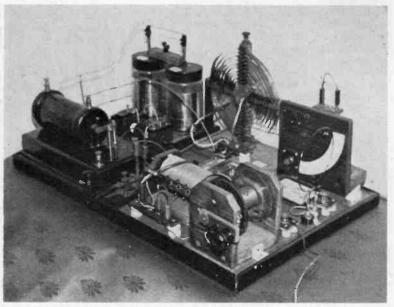

Over in the Black Forest, a group of amateurs including DL1CU (of 'ORV Amateur Radio'', the new German magazine) have as a hobby-interest the rebullding of antique amateur equipment. Here is a model of a very early transmitter, still capable of giving (we are told) a sweet MCW note on the LF bands. The picture opposite is of an early amateur-band station of years later!

As for G2DC, Jack's main pleasure this month lies in his gradual return to the CW ends of the bands. Although various VK's have mentioned that C21TL is active on both CW and SSB, G2DC has not as yet tripped over him-but he did make CW contact with VK2-7, ZL1-4, UAØFD, VK9LV (G5RV, who will soon be returning to the U.K., by way of various odd places) and JD1ACF, while on sideband were accountings with MP4MBC, MP4MBB, MP4MBA, JY8JK, VK4VX, VK4VC, VK6LK, VK6MO, VK6VC, VQ9R, VE8BR (Baffin Is.), 5H3LV, 5X5NA, 9M2DQ, YBØCJ, all W call areas and VE1-8.

G4AMJ (St. Ives) seems to have been hammering Twenty for new countries, and to show G4AMT "the way home!" said countries on SSB included ZF1GC, 8P6CC, HRIRF, FG7XL, VQ9R, ZSITS, 8R1U. MP4MBM, VP8MM. CN8CG, VK9JV, ZB2BL, 9K2AN, LA8YB/4W, HPØLL, EL2T, VP2MY, VP2GAE, DU1MAT, OD5FU, VP2KF, HZ1SH, and OHIJW/OHØ. Other contacts of interest were VP9GE, PZ1AP, various PY/YV, VP9K, VP9AF, HK3LT. JAØBBB. ZP5KA.

HV3SJ, KP4ZC, PJ2CL, LU3AHR/P, LU2FAO, 9K2CI, PZIDR, ZB2RE, VP2VAM, VP2LY, 8P6EK, PZIAN, HKICEY, 4X4HT, VP2LI, LX1RF, DU1ZAC, ZB2CK, OD5GT, OD5GU and CT3AT. As if that were not enough, the man goes on to his CW new countries, with TYIABE, ZP5KA, LU6FA, T12WX and CX4CO, also other CW DX such as PY's, OY4M, HK3AVK, 8P6AE, HK7UL, KV4AA, W5OJZ and W5RM. We wait with bated breath to find what will happen when G4AMT hears about all this, he being busily engaged on building a Quad for G4AMJ!

Points of View

Your conductor recently received a stack of back-numbers of American magazines which had been held up in the dock strike over there. He was brought up sharp by the November 1971 issue of *CQ Magazine*, and its Editorial. This quotes W4BW as being more interested in the present age of the newcomers to Amateur Radio rather than the fall in numbers over there—after all, as he says, 500,000 W's on the air would make the QRM pretty grim, even with 200-cycle filters! However, he goes on to offer the suggestion


that the international Frequency Conference in 1977 is the time for the amateurs of the world to press hard for more bands—as he says, a look at the frequency allocation charts will show how the growth of international cable and satellite communication is significantly easing the pressure in the HF bands, as indeed we have all hoped it would. He therefore goes on to say that proposals should be offered which could lead to more space for amateurs, a suggested range being bands at 10 MHz, 18 MHz and 24 MHz.

Now, just who is this chap? W4BW is the Chief of the Amateur and Citizens Division of the Federal Communications Commission, the U.S. licensing authority.

So much for those who spend their time at Conferences just hoping we will not *lose* too much spectrum-space! All your conductor would add by way of comment is that the easiest way to lose a battle is to think you have lost it, to which the corollary is that attack is far the best form of defence.

QSL Matters

Quite a crop of OSL addresses again. G2HKU mentions JD1ACF, whose cards go to JA1OAF. W4WFL next: Morgan's forthcoming trip to Europe will involve the calls FØAEE/FC and PA9RA, not to mention others not yet to hand, and they all go to him at BM/W4WFL, London WC1V-6XX. Oh, and we forgot, he also has C31EF lined up, as the QSL card (blank, sadly!) on the writer's desk shows. In addition, W4WFL offers 9H3C, to W2FXA; VP2LAT, to WA9UCE; IBØCRW, IL7CRW and IMØCRW, all to DK5KA; 5T5CJ to Box 202, Naukchott, Mauritania; JTØAE to OK1AQW; JTIAW to K4MPE; HB9XJG, HBØXJG and 3AØFN all to either DL4VA via DARC, or to WA4WME. next lot, from G4AMT, VP2VAM, to VE3GMT; LU7TD. to Box 1981, Jujuy, Argentine; CT2BG to WB8ENY, FCØVQ to DJ8UT; FL8MM to Box 574, Djibouti, T.F.A.I.; VU2HLU to WØPAH; HK3LT to Box 584, Bogota, Colombia; 9K2BQ to JA1ZZ; OD5ET to Box 4848, Beirut, Lebanon; JY6FC to Box 11020, Amman, Jordan; 4Z4G to

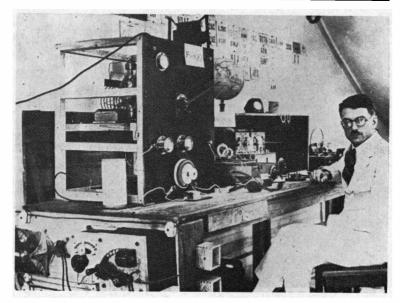

In the last few years, we have been hearing a lot of unhappy Saigon. When this picture was taken, in 1926, Saigon was one of the peaceful, elegant and gracious cities of French Indo-China, and FISQQ was among the locally active amateurs. We have only the picture to go by but we would say that at the time FISQQ was working CW/DX on 45 metres, running about 50 watts into an L-aerial of 66ft. or so, tapped directly on to the tank coil, and his Rx would probably have been a 1-V-1. Happily, M. Richard Jamas is still with us, and now signs FSQQ from Nice, on the DX bands.

W2KF; ET3DS to VE2DCY, and 9H3B to VE3MR.

Bits and Pieces

Various items to be mentioned. First, by way of the RAFARS Newsletter, a note about the Cyprus QSL Bureau. This is incoming only, to Box 216, Famagusta. Anyone who has left Cyprus but may have a few cards coming in, should send a supply of s.a.e.'s for the QSL's to be forwarded.

Now the question of 5B4 stations: 5B4ES is quite valid, we understand, and is held by the English School in Nicosia. This is the only station properly licensed to use the 5B4 prefix; however, there are some UN licensed stations, who *should* sign 5B4UN + call letters, but generally omit the letters UN.

By now, we shall be past the deadline for the CQ WW WPX Contest over the March 25/26 weekend, but it is not too late to say that logs should be timed in GMT, with a separate log for each band, prefixes indicated the first time they are worked, and the logs checked for duplicate QSO's; then add the summary sheet, the category you are entering, which may be single-op, all band; or one-band, multioperator; all-band, single transmitter; or multi-op. multi-transmitter. All entries, postmarked not later than May 1 to CQ WW WPX Contest Committee, 14 Vanderventer Avenue, Port Washington, L.I., N.Y. 11050, U.S.A.

April 22/23 sees the Bermuda Phone Contest, which has been mentioned before, and May 6/7 is the CW leg, when you can brush up your CW, ready for the U.S.S.R. CW Contest the following weekend.

Among the lesser ones, we have some detail on the contest which is being run in conjunction with the 7th World Orchid Conference, which is the world working the HK4 stations, with 5J4LR and 5K4LR also available. It is five points for each HK4, or ten points for 5J4 and 5K4, giving RS plus the usual three-digit number starting at 001. The HK4's pass RS plus a number indicating the power. Same station may be worked on different bands, final score to be QSO points times multiplier for the number of bands worked. Mail to LCRA, Seccional Medtllin, Apartado Aereo 51900, Medellin, Colombia, South America.

On a more domestic level, the

Chiltern Club found their own shindig on Top Band quite popular, and to judge by the logs sent in, at least twenty counties were available to be worked during the morning, although DHJ was by no means strong, which would suggest that conditions were not too good.

By way of QRV Magazine, we have some interesting details on the HV2 operation last year from Castelgandofo, which with the help of HV3SJ, was mounted by a group of DL amateurs, led by DL1CU, which gave CW contacts to about 3000 lucky souls: Brother Ed., HV3SJ is normally a phone-only operator himself, although certainly active enough to please the most hardened DX'er. Enclosed with the data was a picture of the rig, with DL9PF at the operating position a nice business-like station set-up. It is understood that ARRL have been approached regarding the status of an HV2 operation as a separate country for DXCC, but at this time we have no further information as to the outcome.

From BFPO 33 comes an incensed missive—G3YEU has been out of the country for 2½ years now, but is receiving QSL cards from late 1970 onwards, covering all bands on SSB, and, on the face of things, a resident of Nottinghamshire. Barry appeals to anyone who worked this character *please* to stop sending QSL cards, as they hooked a phoney.

Top Band

Rather a thin clip this month. G3VLX (Chislehurst) sends in his entry for the Table with a cryptic comment to the effect we'll be tired

COUNTIES TABLE TOP BAND			
Callsign	CW CW	Counties Phone	Total Score
GM3YOR	56	23	57
G3YPT	44	8	52
G3VLX	18	21	39
GW3WSU	-	32	32
G4ALG	19	6	25
G3DCS	14	_	14
This table will run until December 31 1972. Starting date, January 1, 1972. Any mode goes.			

Reporting the HF Bands

of seeing his short notes—never, it's all grist to the mill!

From W1BB's latest Newsflash, we have various bits of news, perhaps the most important of which is that K1PBW has lost his house and shack, with the 133-foot vertical and eighty radials, all burned to the ground as a result of an overheated stove pipe. Ernie was able to dash in and save the receiver and transmitter. Let us hope he will be able to get everything sorted out and up again in time for next autumn—this was a real disaster, on which we all sympathise.

Also from W1BB, we hear that DL9KR, who used to be DL9KRA. has already managed a WAC from his new apartment-block home. He has put up a 30-foot vertical with an "umbrella" of six wires giving top-loading, plus some two thousand feet of wire on the roof in the form of radials up to seventy feet long. Once this was tuned-up "on the nose" a listen round yielded a first QSO with K2ANR, after which he was called by ZD9BM, for a "First." As if that were not enough, Jan was able to go on in the CQ WW 160 Test, raising 21 countries and making 269 QSO's, including 20 States and Provinces, also such as VP2AAA, 8P6DR, HZ1KE, W4BRB/VP7 (all "Firsts" for DL). Within three days, DL9KR had made a WAC, with EQ2BQ, VK5KO, W5RTQ, K4CIA, KV4FZ and PY1DVG. This should interest the chaps who say DX can't be worked from a small plot.

G2HKU (Sheppey) continues his serene way with the EU/DX, and this month offers PAØPN and PAØINA on SSB, plus CW with E19J, OL1AOH, GD5DZ and GW3UPK.

JH1LKH, Minekazu Sugiyama, has been active on Top Band since 1968, his first DX QSO being with W7DL/T, when JH1LKH had only ten watts of transmitter; this spurred him on, to use higher power, with Drake and, to judge from the photograph W1BB sent over, Yaesu, gear, which has netted him contacts with VK, VS6, and a "First" to VK9, not

to mention CR6, KH6, and regular W6 and W7 working—all of which have generated ambition for European and East Coast W contacts

G4AYZ (Northampton) is now on 160 and 80 metres, with a Codar A.T.5. as a starter. It is interesting to notice that it is a year to the day between his first picking up a copy of Short Wave Magazine to the date when he received the ticket, although it has to be admitted he was a pre-war SWL. He hopes to get on SSB later, but meanwhile he would appreciate reports, SWL and otherwise and promises to QSL any which are of any help at all.

GW3WSU (Llancarfan) comes into the Table, having picked up 32 counties all on Phone; it is interesting to see he is operating from the Decca site, so doubtless he is pretty well clued-up on the ways and means of making RF go off in the desired directions.

GM3YOR (Kirkcaldy) is also in the Table, and at the same time is looking for *CW* QSO's, to make his 98, with the Scillies, Alderney, Guernsey, Armagh, Tyrone, Caithness, Brecon and Montgomery—any offers? On a different tack, Drew has received the QSL for his MP4BJI contact, and John claims this is the first GM/MP4B on Top Band.

G3YPT (Swanage) reports a quiet spell, apart from a session in a recent Top Band contest, when conditions seemed quite fair and GD5DZ, GI3OLJ, GI3SSR, GM3NCS/A and GM3UKG (Banff) were worked, not to mention OK1IDK/P. Paul hopes to be somewhat more active in the counties context during the coming weeks.

And that, it might be added, goes for your conductor, too. There is wire coiled up ready-measured for at least a temporary end-fed aerial to get going again on the band, but . . .


The LF Bands

First G2DC, who confined himself to being on and active at times, between 0300z and 0630, on *Eighty*,

when the band has been good to the West, which meant he was able to work all the W call areas except W6, plus VE1, VE2, VE3 and VE7. As for Forty, it has been quite fair during 2200 and 0330z and again between 0530 and 0730. One morning HKØBKX was there with a nice signal, but after a couple of contacts was mobbed by the EU's to such a degree that the HK just gave up and sent in conclusion that he would be better off in bed! CW accounted for PY2AME, PY7OS, VK3MR, ZL4IE, all W call areas, VE1-5, VE7 and lots of UA9's. Although G4AMJ, as related elsewhere, spent a lot of his time working over Twenty, he did find enough energy to tackle Eighty

UA2UN and WBØFFG/TF. Using a sloping-Vee dipole, with the apex at sixty feet, G4AMT spent quite a lot of effort working Eighty between 0600 and 1000. All this list is 80m. Sideband: VE1FO, VE1IE, VE3FKU, VE3NE, VE3PT. VE3GGS, VE1AVN, VO1JK. W1FVD. W2ZPO, WB2OEU/2, W4JT, WB4JYB, VA2UN, ZL3GQ, ZL3GS, ZL4AV, HR1KAS. HR2GK, CT2AK. XEIKB, PYIHA, CO2FA, VP9AT, 6W8DY and VP2LY. The CW on Forty, in a half-hour stint before going to church one Sunday morning, accounted for all W call areas (apart from W7), 3A2AB, 5Z4JD and FCØVQ.

For G2HKU there was interest in Eighty by working CW to YK10K, W1, W2, W4 and other routine stuff; Forty produced 6Y5SR, and a comment about the way Radio Peking spreads of late, as though the transmitter were out of kilter —a point mentioned, too, by others. In an aside, Ted talks about his "5RV" and 14AVQ aerials; the ground-mounted 14AVQ is well up on the 5RV to U.S.A. on 7 MHz, but not so good to ZL—on the other hand, surprisingly enough, it produces less TVI on any band-

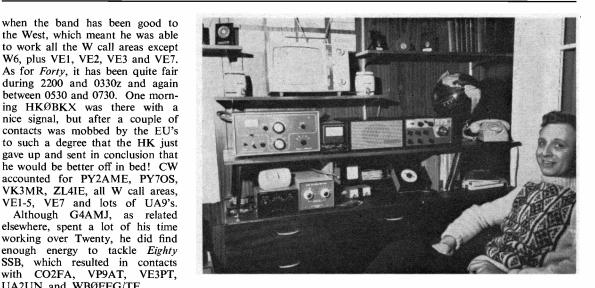

G3UCV, Ron Cartwright, 5 Manston Gardens, Crossgates, Leeds, 15, passed the R.A.E. in 1952 but did not take out his ticket till 13 years later! Since 1965, wide varieties of gear and antennae have been tried and he is now happily settled with a Drake TR-4 transceiver, a linear to go with it, and the necessary ancillaries. His aerials are a trapped mini-Quad for the DX and an inverted dipole for 80m. The shack is an annex off the living room.

being fed through individual ATU's switched at the transmitter-output.

For W6AM, there have been a few interesting QSO's, on CW, including TG9HP, DL3ZM/YV5 and 8R1G, all worked just HF of the U.K. upper frequency limit of 3.8 MHz.

Another "5RV" aerial addict is G3JFF, who used it on Eighty to key his 150 watts with CT2AK, HV3SJ, GB2MT and East Coast W's; Forty produced only Europeans and W3/W4, but created a comment that these transceivers just hate the amount of signal that pounds their front-ends from the BC stations. Very true, and a good argument for an aerial attenuator!

To round off, a letter from G3XTJ (Palmers Green) who has clearly been inspired by all the talk of DX on Forty. He set off to work it, with a Drake R4-A, and registered with FG7TG, JA5FHQ, KP4BNH, PY4BUN/2, PZ1AP. SV1CH, TG9CD. UK8JAD, VP1AV, VP9BK. VP9BO. YV5DRN and 4S7DA-the SV was raised while writing his letter, and takes Ed. up to Country No. 99 on Forty, assuming the JT1AA he worked was OK; and a sked with ZC4KJ could put the "ton" up by the time this reaches the bookstalls.

Conclusion

And there, good people, you have it; as this is going down before time-see Editorial-there may well be more news in the pipeline but it will, sad to say, have to wait till our next. But we haven't forgotten or lost the letters! All being well, the nominal deadline for next month will be April 11, addressed, as always, to CDXN, SHORT WAVE MAGAZINE, BUCKINGHAM. Till then, good luck and good DX. Write in again as soon as you can.

To keep in touch with the world of Amateur Radio, read "Short Wave Magazine" regularly -Independent, Unsubsidised and now in its 30th volume.

ANOTHER MARCONI ANNIVERSARY

In connection with a range of activities—both on the air and off it—arranged for May 13-21 by the Barry College Radio Society in commemoration of the Marconi-Kemp first 'cross-water tests in 1897, from Flatholm in the Bristol Channel, we have received a large amount of detailed information from GW3VBP, the hon. secretary. There is neither time nor space to deal with tall here now, except to mention that the local stations to be on are GB3MKT (Lavernock Pt.), GB3BCT (Flatholm Is.) and G2WS/P (old "Two Walking Suitcases" who started out /P many years ago), on Brean Down, Somerset. We hope we may be able to cover this more fully in the May issue, due out on April 28.

USEFUL NEW PRODUCTS

The first is a neat little instrument box, 4 x 6 x 4in., finished grey, with mounting feet, a chrome handle and detachable aluminium panel. Costing but £1.50 post free, a container of this sort has many obvious applications in the construction of small pieces of apparatus.

Another item is a QSL mounting sleeve in a clear plastic material, designed to take a dozen cards for display, of course with the minimum of marking of the wall on which they are mounted. Ten such strips cost 25p (post 6p), accommodating 120 QSL cards.

Both these items can be obtained from: Derwent Radio, 28 Hillcrest Avenue, Scarborough, Yorkshire.

CORRECTION NOTE—R.A.E. PASSES


As several readers have rightly pointed out, an error was made in that item on the R.A.E. on p.43 March. A pass must be secured in *both* Parts I and II, to the extent of 50% of the marks for each section, in order to obtain the R.A.E. Certificate. While we much regret having perpetrated such an error, in fact it does not in any way affect the tenor of the argument, which is that the pass-rate overall ought to be higher.

NOVICE LICENSING IN AUSTRALIA

The problems of Novice Licensing and the definition, control and examination standards for such a system have become the hot topic for the Wireless Institute of Australia (the VK amateur representative body) and their Amateur Radio. Pages are devoted to correspondence—unedited and in extenso—on the subject and from here the arguments look to be about as broad as they are long (though that may be somewhat over-simplifying the situation). One point emerging that came as news to us is that in Australia their equivalent to our R.A.E. demands 70% of the marks for a pass; in New Zealand it is 50%, as in the U.K.

The present position is that in the light of the discussions since the first Novice Report was published for general consideration, a Supplementary Report on Novice Licensing is to be prepared for submission to the authorities concerned.

Interesting picture showing the effect of a Mullard image intensifier, demonstrated at their Research Laboratories, Redhill, Surrey. The TV camera, fitted with the intensifier, is at one end of a long, dark room, with a lamp directed on to the camera and operator. The picture on the monitor is illuminated only by the stray light reflected from the camera equipment, yet the monitor shows clearly such details as the operator's glasses and his watch.

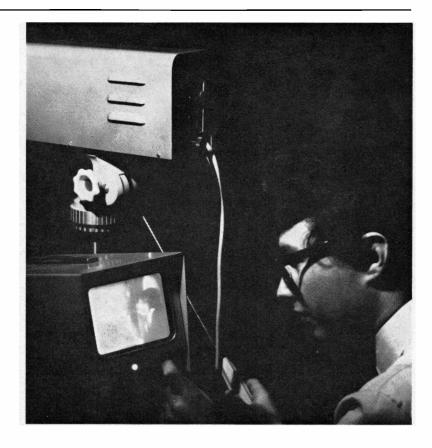

THE MOBILE SCENE

The Rally Calendar has been filling up well during the last two months. All dates notified at the time of writing are given below, with details (where we have them) for the events shortly to take place.

Latest figures show that there are now more than 3,200 U.K. amateurs licensed for mobile operation, of whom about 16% are /M on the VHF bands. These numbers should ensure a large turn-out for the more popular of the Season's Rallies.

With the formation of the Amateur Radio Retailers' Association (see elsewhere this issue) trade participation in Mobile Rallies by A.R.R.A. members is now being handled by H. James, G3MCN (Stephen-James Ltd.), 70 Priory Road, Liverpool L4 2RZ. (Tel: 051-263 7829.) Rally organisers are asked to note this and contact G3MCN direct if they wish for retail trade support at their event.

Incidentally, we understand that A.R.R.A. members are much concerned about the increasing pilferage round the trade stands at Rallies. Measures are being taken to counter this—it is a manifestation of the times of which nobody can be proud. It is the intention of the Association to take the severest action against anyone caught shop-lifting.

Now for the Calendar of Events:

- April 2: White Rose Mobile Rally at Lawnswood High School, Leeds, 6, at junction of the A.660 Leeds-Otley and A.6120 Leeds ring road. Ample car parking, trade representation, bring-and-buy sale, raffle and talk-in on 2m./160m. Contacts are: R. Short, G3YEE (*Tel: Bradford 664220*), or E. Lawley, G8EHV, *QTHR*.
- April 16: Annual North Midlands event at Drayton Manor Park, near Tamworth, Staffs., opening at 12 noon. There will be trade stands, a grand raffle, judging of mobile installations and talk-in on Top Band and Two metres. And if it is a fine day, the Park has many attractions for the family. Details from C. H. Lloyd, G3ZPQ, QTHR (Tel: Coleshill 63092).
- May 7: Spalding Tulip-Time Rally at Surfleet, Lincs., 4 miles north of Spalding on the A.16 Spalding to Boston. The tulip fields should be in full bloom and are a magnificent sight. Pleasant riverside venue, offering overnight camping and caravan facilities, attractions to include trade stands, raffle and bring-and-buy stall. Free admission, and refreshments available on site. Talk-in by G3VPR/P on 1980 kHz, G3MMS/P on 70.26 MHz and G3XBS/P on 145.80 MHz. Maps of the Tulip Fields and further information from: R. Harrison, G3VPR, QTHR.
- May 21: Annual Northern Mobile Rally, at Moor Grange School, Parkstone Avenue, off Ring Road, West Park, Leeds, with all the usual attractions, including trade stands, sale of surplus equipment (bring yours for the stall) and prize draw. Refreshments will be available. Contact for details: D. Binns, G3MGI, QTHR.

- May 28: Chiltern Amateur Radio Club Rally at West Wycombe, Bucks., at the Dashwood home near High Wycombe, on the Oxford road just outside the town. This Rally will coincide with the Steam Rally and the Model World shows. Details from: P. Perkins, G3OUV, Loakes House, Loakes Park, High Wycombe, Bucks.
- May 28: Hull & District Amateur Radio Society first Mobile Rally, in grounds of the East Riding College of Education, Bishops Burton, on the A.1079 York to Beverley. Contact man: L. D. Colley, G3AGX, QTHR. (Further details later.)
- June 18: Anglian Mobile Rally, at the Suffolk Show Ground, Ipswich. Contact: D. W. Thomas, G3ZLN, QTHR. (Further details later.)
- June 25: West of England Mobile Rally, at Longleat, near Warminster, as in previous years. Information from D. Iles, G3COP, QTHR. (Further details later.)
- July 16: Upton-on-Severn Mobile Rally organised by the Worcester & District Amateur Radio Club. Information: B. Jones, G8ASO, QTHR.
- August 13: Torbay Amateur Radio Society Mobile Rally at Newton Abbot Rugby Ground.
- August 13: Annual Derby Mobile Rally at Rykneld Schools, as in previous years. Details from T. Darn, G3FGY, QTHR.
- August 20: Saltash & District Amateur Radio Club Rally at Saltash Grammar School, with all the usual side-shows and activities, most of which can be under cover. Ample free parking on site. Details from: I. Aldridge, G4AJU, 302 St. Peter's Road, Manadon, Plymouth, Devon PL5 3DU.
- August 26-27: Stratford-on-Avon Radio Club Mobile Rally at the National Agricultural Centre, Kenilworth, Warwickshire, Hq. of the Royal Agricultural Society of England. Contact: M. J. W. Webb, G3OOQ, QTHR, or ring Stratford-on-Avon 5973. (Further details later.)
- September 24: Harlow & District Amateur Radio Society annual Rally at Magdalen Laver Village Hall, as in previous years. For details: V. Heard, 106 Vicarage Wood, Harlow, Essex.

Any further information for publication relevant to "The Mobile Scene" should be sent in to SHORT WAVE MAGAZINE, BUCKINGHAM as soon as possible—and on a separate piece of paper, please, not mixed in with other correspondence, nor addressed to our London office!

We are always glad to see good photographs of current Mobile Rally interest. Those we can use are paid for on publication.

THEFT OF GEAR

Over the week ending March 4/5, G3YJE lost, from the boot of his car, a Heathkit HW-30 (known also as the "Two'er"). This must have happened somewhere between Chester and Newby Bridge. The HW-30 itself is somewhat modified, has two scrapes on the front panel, no screws at the back of the cabinet and no control cabling or other ancillaries. Information would be appreciated by P. R. Merriman, G3YJE, OTHR, (or ring 01-953 8088).

THE HW-17A. MODIFIED FOR IMPROVED PERFORMANCE ON TWO METRES

DISCUSSING THE PRACTICAL DETAILS

C. P. HOWARD (G8ANU)

THE Heathkit HW-17A two-metre transceiver kit is no longer listed, having been withdrawn from the U.K. market in January 1971. However, during the time that it was available in its original HW-17 and later HW-17A form a large number of units were sold and are still in use, for both fixed station and also for mobile and portable operation with the accessory HW-17-1 DC inverter power supply from a 12-volt battery.

The transceiver unit is compact (14½in. wide, 8½in. deep and 6½in. high) and weighs 13 pounds. It has a built in 240v. AC/PSU. The receiver section is completely transistorised and the Tx side had three valves and a transistor modulator. Four internal switched crystal sockets are provided and also connectors for the *Heathkit* HG-10 VFO.

Shortcomings of the Original Design

The transmitter circuitry of the HW-17A in general performs tolerably well in the standard form (the original severe lack of PA drive of the HW-17 having been largely eliminated by component changes in the later model) the only remaining transmitter fault being lack of modulation. The receiver is generally considered to be short on sensitivity and to have a tendency to frequency drift due to temperature variations affecting the first oscillator, which is a single tuned transistor arrangement.

The suggested modifications are divided into three sections: (1) Transmitter, (2) Receiver, and (3) Minor general modifications.

The Transmitter

A useful improvement in modulation can be achieved by replacing the ceramic microphone insert in the p-t-t microphone by an *Acos* Mic. 40 crystal insert and dispensing with the paxolin disc and all but the decorative metallic fabric in front of the insert when fitted in the case.

A more substantial increase in depth of modulation was obtained by increasing the value of the PA screen resistor (R115 in the original circuit) from 12K ohms to 22K ohms, a 2-watt resistor being required. This has the effect of reducing the DC input to the PA from 30 watts to about 25 watts and while the reduction in carrier strength is not detectable the available audio produces more modulation.

A final increase in depth of modulation was obtained by replacing the rectifiers supplying the 15-volt DC line (D307, D308, D309, D311 in the handbook circuit) by rather more adequate plastic encapsulated 1N4002 types and by adding a further 2000 μ F capacitor in parallel with the smoothing/reservoir capacity for the

15-volt supply (C325). The effect of these changes was that the 15v. line fell from a no-load of 15 volts to a value of 13·5v. with a sustained loud whistle into the microphone, whereas with the original components the voltage fell to 8·0 volts under the same conditions.

It has been suggested to the writer that substitution of AD149 transistors for the standard audio output transistors (Tr14 and Tr15) could be of benefit but no improvement in modulation could be obtained in this way.

Receiver Modifications

Various attempts were made initially to obtain adequate sensitivity from the receiver section by careful adjustment of the existing circuitry without the addition of pre-amps, or other devices. Reasonable performance was obtained by very carefully following the handbook on "Receiver Alignment" for the IF stages, and carrying out a modified version of the "Tuner Alignment" procedure—this was to align at 144 and 146 MHz instead of as recommended (who needs a flat response from 143.2 to 148.2 MHz?) and by increasing the 2nd oscillator injection by reducing the value of the emitter resistor (R207). The original 680-ohm resistor can be reduced to less than 100 ohms to produce noticeably more gain-but a compromise is needed as too much injection can greatly increase noise; a value of 270 ohms appears to be suitable.

With these preliminary modifications carried out the receiver seemed much more lively, the AVC began to work and hence the squelch, and tuning meter circuits also started to function. But even at that more sensitivity is obviously needed for other than cross-town type contacts.

To obtain further sensitivity more amplification is required. This may take the form of either an additional RF stage or more IF gain. Both alternatives will be described.

RF Pre-Amplifier

Attempts to add a pre-amplifier within the case of the transceiver were unsuccessful due to the limited space available and the most promising solution was an external unit mounted on the right-hand side of the cabinet, the input and output coax and power leads being

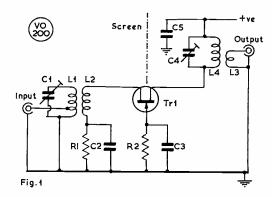


Fig. 1. Pre-amplifier for the HW-17A Rx section. Values can be: Cl, C4, 2-8 pF trimmers; C2, C3, C5, 001 µF feed through; R1, 330 ohms; R2, 100K; L1, L4, 6 turns, \in diameter; L2, L3, single-turn coupling to L1, L4; Tr1, TIS88.

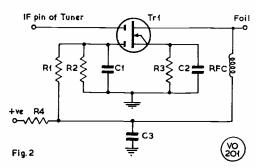


Fig. 2. Circuit of the IF amplifier discussed in the text. C1, C2, C3, .002 µF; R1, 100K; R2, 33K; R3, 120 ohms; R4, 560 ohms; RFC, 19 inches of 30g. enam. wound on 1-megohm resistor as former; transistor Tr1, 40673.

taken through holes in the side of the lower half of the case. A circuit such as that shown in Fig. 1 can be used or a ready-made unit (which must be negative earth!) such as the Solid State Modules Sentinel pre-amplifier would be suitable. The DC supplies may be taken from any suitable earth point (-ve) and from the positive end of C325 on the underside of the receiver partition. The 100 pF disc capacitor should be unsoldered from lug 2 of terminal strip AP (the other end being left connected to the Ant. pin on the underside of the receiver printed circuit board) and the inner of the coax input lead to the pre-amplifier connected to lug 2 of strip AP instead. The inner of the coax output lead from the pre-amplifier should then be taken to the free end of the 100 pF disc capacitor. The two coax braids should be earthed to lug 3 of terminal strip AP. If connections to the preamplifier are made with coax plugs and sockets reassembly of the unit is made easier and it is possible to use an external converter and tunable IF strip with the transmitter and aerial switching of the HW-17A if this should ever be required.

The result of this modification is a really worth-while increase in receiver gain up to the level to be expected from a conventional FET converter and tunable IF arrangement, the tuning meter deflecting to full scale on strong signals, with the AVC and squelch circuits working is a most satisfactory manner. In the "spot" mode the transmitter oscillator produces a half-scale meter reading for netting purposes instead of the previous slight deflection only.

Additional IF Amplifier—Alternative Arrangement

This modification was originally described by WA5PWX as an alternative to the use of a pre-amplifier and its attraction is the small number of components required. The circuit is shown as Fig. 2, above.

The IF pin underneath the tuner section of the receiver printed circuit board is unsoldered from the "island of foil" and insulated from it. Gate 1 of the 40673 is soldered directly to the pin and the drain lead goes to the island of foil originally connected to the pin and the other components are hung on the remaining transistor leads and the adjacent large area of earthy foil below the tuner. (Voltage supplies can be obtained as previously described for the pre-amplifier.) After fitting the amplifier T1 (in the tuner) and L6 require re-alignment as described

in the HW-17A handbook.

Receiver Drift

It was observed that the frequency drift of the receiver, previously mentioned, occurred only when the transmitter was in use and appeared to be due to heating of the tuner unit by radiation from the Tx valves. The rate of drift was greatly reduced by lagging the sides and top of the tuner unit box with the thickest polystyrene foam sheeting which could be accommodated. The foam was cut from ceiling tiles and taped into position.

Minor General Modifications

Other modifications are mainly minor points of detail and are listed briefly:

- (1) A standard *Belling-Lee* coaxial aerial socket can be mounted directly using the original holes provided for the "phono" socket.
- (2) For safety a three-core mains lead should be used with "live" connected to pin 3 of the 11-pin power socket, neutral to pin 10 and earth to pin 8 and a fused plug fitted to the other other end of the lead,
- (3) The VFO position of the crystal switch can be used to connect a further crystal socket mounted on the back wall of the case to provide one crystal which can be changed without removing the top of the case. If one side of the crystal socket is connected to the inner of the VFO input "phono" socket and the other side to the common point for the internal crystal sockets it is possible to use either an external crystal or a VFO as required, (4) The arrangement by which the dial light is switched off in the "Batt. Saver" position of the function switch as well as the valve heaters seems to be carrying economy too far. By joining together lugs 1 and 2 of the function switch the dial light will remain lit as long as the transceiver is switched on—a great convenience when operating mobile or portable at night, (5) If it is desired to add a coaxial aerial change-over relay to replace the diode switching system originally used it will be found that one of the relays available from surplus commercial R/T equipment with a 12-volt, comparatively high-current, operating coil can be wired in series with the HT supply to the anode and screen of the PA stage and will provide superior aerial switching performance,
- (6) A final point, though not a modification, is the fact that 12 MHz crystals can be used in place of the usual 8 MHz ones without any circuit modifications at all (and with no retuning required). Slightly more drive to the PA should be obtained.

Conclusion

If the principal receiver and transmitter modifications described in this article are carried out the result should be a transceiver of greatly improved performance, which should provide many more contacts than could be expected in the unmodified condition.

THE EDDYSTONE 888A

NOTES ON AN INTERESTING AMATEUR-BAND RECEIVER

F. G. RAYER, A.I.E.R.E. (G3OGR)

THOUGH not apparently available second-hand in great number, the 888A is quite often seen for sale, and these notes should be of interest to anyone thinking of obtaining this equipment. The Eddystone S.640 was discussed in the January 1966 and April 1968 issues of SHORT WAVE MAGAZINE and the 740 and 750 receivers in the May '69 issue. Notes on the 840A and 840C appeared in the Magazine for December '69. These are all general-coverage types—whereas the 888A is for amateur bands only.

Coverage

Six directly calibrated bands are provided—1·8-2·0, 3·5-4·0, 7-7·3, 14-14·35, 21-21·5 and 28-38 MHz. All these are available on the large and familiar styled Eddystone dial which has scales about 12in. long, and is shown in the illustration. The drive ratio is 40:1. The vernier scale in the central window is read in conjunction with the bottom 0-1000 scale, dividing the ranges into 1000 divisions, for logging or re-set purposes.

It is worth noting that the 28-30 MHz range is excellent for two-metre work in conjunction with a converter for this band.

Scale Accuracy

This can be high through all ranges. An internal 100 kHz crystal marker is brought into action by pressing the "Cal. Press" button on the panel, and the central

small "Osc." knob can be rotated (actually a 2·5-4·0 pF air trimmer) to bring the dial pointer into agreement with the nearest 100 kHz scale marking.

Circuit Layout

SHORT WAVE MAGAZINE

This is a double-conversion superhet, shown in Fig. 1. The RF stage is a 6BA6, followed by an ECH81 mixer with separate 6C4 oscillator. This converts to the 1st IF of 1620 kHz, resulting in excellent suppression of second-channel interference. A second ECH81 converts to the 2nd IF of 85 kHz, and is followed by a 6BA6 IF amplifier.

The low IF of 85 kHz gives high selectivity, and a variable selectivity panel control is also fitted. This adjusts, mechanically, coupling between windings in the two 85 kHz transformers.

A 6AT5 follows, for AM detection, AVC, and first AF amplifier purposes. Audio signals pass to a 6AQ5 output stage.


An optional audio filter can be switched in between AF and output stages. Its quoted insertion loss is only 1 dB, with a band width of 100 cycles at 6 dB points. If a CW signal is tuned into the filter pass-band, this gives a very noticeable selection of the wanted signal over surrounding mush. (It is used for CW only.)

For SSB and CW reception a 6BE6 operates as BFO or carrier oscillator, with the final IFT supplying grid 3 for mixing. The BFO setting is adjustable by a panel control in the usual way.

A 6AL5 is used as an optional noise limiter, with panel switch, and the 100 kHz marker oscillator is a 6AU6. A 5Z4G rectifier provides HT, and a VR-150 voltage regulator supplies 6C4 first oscillator and mixer screen grid, and second oscillator HT.

Aerial Connection

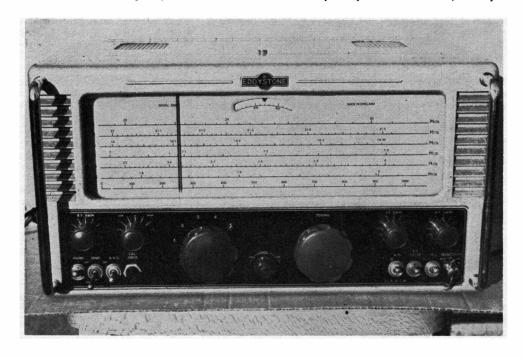The input impedance is 75 ohms, but any aerial can



be used. There are two aerial terminals for a balanced feeder, or for use in conjunction with an earth socket for co-axial feeder or end-connected single wire aerials, the "A2" terminal then being joined to the earth terminal with a short lead.

The control knob of an aerial trimmer can be reached by opening the cabinet lid, and is rotated for best results with the aerial in use.

Output End

Back terminals take connections for an external 2/3 ohm speaker. Phones may be plugged into a jack socket at the left of the case. This mutes the speaker. The phones are fed from the 6AQ6 anode via a $0.01~\mu F$ isolating capacitor and should be of high or medium impedance.

External Accessories

The receiver "standby" panel switch also closes the circuit to the back terminals, which can be used to operate a relay controlling the station transmitter.

Two octal sockets are also fitted at the back. These can be used to operate the receiver from an external power supply other than 110v. or 200/240v. AC mains, for which the internal power pack is intended, and for an S-meter.

S-Meter Arrangement

Fig. 2 shows the S-meter circuit, with connections viewed from the pin end of an octal plug. This plug is put in the socket nearer to the receiver centre. (A correctly wired plug is present in the outer socket, to complete power circuits.)

It will be found that satisfactory results are obtained by using a 330-ohm resistor and 500-ohm potentiometer. The meter can be the easily available 0-1 mA type.

A reverse-current diode is present in the receiver. With the meter disconnected, set the meter zero to bring the pointer a little below zero. Then with the meter plugged in and the receiver working, and with the RF and IF gains at maximum, but no signal tuned in, set the 600-ohm (or 500-ohm) potentiometer for zero on the meter.

Panel Controls

From left to right these are RF Gain, BFO pitch, Bandswitch, Osc. trimmer, Main Tuning, IF Gain and RF Gain. Switches are Mains On/Off, "Send" (Standby), AVC On/Off, "Cal. Press," AM/SSB-CW, AF Filter and Noise Limiter, with the variable selectivity control at the extreme right.

Receiver dimensions are near enough 42.5 cm. $(16\frac{3}{4}in.)$ wide, 25.4 cm. (10in.) deep and 22.2 cm. $(8\frac{3}{4}in.)$ high. Weight is about 44 lbs., or 97 kg.

Valves Used

If a second-hand receiver is purchased in an untested condition, and results are not satisfactory, it is usually worth checking that the valves are not suffering from lost emission. The quickest method is to use a valve tester or put in new valves, replacing the original valves where no improvement results.

Failing this, meter tests of anode current, cathode current, and SG current can be made without discon-


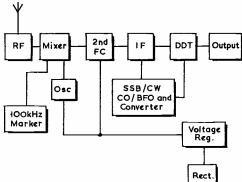


Fig. 1 Block diagram of the 888A

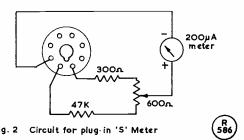

necting any circuits by taking voltage readings across the anode, cathode and SG resistors in the usual way. The HT line is about 250v. If this is not obtained, the rectifier may need replacing. None of the valves required are difficult to obtain.

IF Alignment

The "beginner" is probably best advised to leave all alignment untouched. But the more experienced user can normally deal with this, provided care and patience are exercised, and the correct tools are used (not a collection of old screwdrivers and spanners).

The receiver should warm up for twenty minutes or so, and be switched to the 10m. band, with RF gain at minimum, but IF gain, AF gain and selectivity controls at maximum positions. Select AM reception, with filter and limiter off. A 85 kHz signal can be injected at the grid of the 2nd mixer, and the four cores of the variable IFT's are adjusted for best output.

A 1,620 kHz signal can now be injected at the first mixer, and the first IFT (near the panel) adjusted. Behind this is a can with the 2nd mixer on top, and this oscillator is also adjusted for best results. The signal is then applied to the fixed plates of the middle section of the tuning capacitor, with the bandswitch at 1·8-2·0 MHz. The second oscillator and all cores in the IFT's should then be carefully touched up if needed. An input of 15 mV at 1,620 kHz should give an output of about 50 mW.

Failing a generator, use a stable signal such as from a crystal marker or transmitter VFO, coupled to the receiver aerial terminal, and accurately tuned in. Then carefully adjust all IFT cores and the 2nd osc. core for the best S-meter reading (assuming the signal is unmodulated). *Very slight* adjustments one way or the other may be expected after changing valves, or ageing.

First Oscillator

Cores and trimmers can be reached from below the chassis. If dial readings are correct, the oscillator cores and trimmers should be left as they are. But should there be significant errors in one or more ranges, these can be dealt with by adjusting the core and trimmer of the range affected.

Adjustment of cores or trimmers is made at the following frequencies:

Core	Trimmer
1.8	2·0 MHz
3.5	4.0 ,,
7.0	7.3 ,,
14.0	14.3 ,,
21.0	21.5 ,,
28.0	30.0 ,,

The internal 100 kHz marker can be used for these adjustments. Note that it is easily possible to shift tuning 100 kHz out, and thus adopt wrong marker points, especially in the 28-30 MHz range. If there is any doubt about calibration for this reason, check with an external source, such as a one-megacycle crystal, or a Tx VFO.

Adjustments are repeated as often as required, at one end of the band, then the other, to secure best agreement with the dial calibration, and with the "Osc." panel control in its central position.

Aerial and Mixer

Cores and trimmers can be dealt with at or near the frequencies already given, using an external stable signal, such as from a generator or VFO. Adjustments are repeated until no further improvement can be obtained.

A 1,620 kHz rejector coil stands by itself near the back of the coil box, and is adjusted for *minimum* output with a 1,620 kHz signal put in at the aerial terminal.

BFO Stage

The BFO core is found below chassis, quite near the "Cal." switch. If adjustment of this is necessary, set the BFO variable capacitor half open, tune in an AM signal correctly, and then switch to CW/SSB. Rotate the core for zero beat.

Calibrator Unit

This is mounted in a can on top of the ganged capacitor and has a trimming adjustment to shift the crystal into agreement with some standard reference.

One method is to tune in the BBC on 200 kHz with a portable or other receiver, and adjust the calibrator, if necessary, for zero beat. Or the calibrator can be adjusted to zero beat with the standard frequency transmissions on 2.5 MHz or 5.0 MHz.

Editorial Note: An Eddystone 888A, properly serviced and correctly aligned, is a very good amateur-band receiver, particularly for CW working. Though "obsolete" in the sense that it is all-valve rather than transistorised, this in fact gives the 888A the great advantage of being capable of withstanding much abuse in terms of RF pick-up from a near-by trans-

mitter—the condition that often applies in an amateur station, and which can soon lead to deterioration in a transistorised Rx.

POINTS OF INTEREST

The brothers Old, of 7 Trelawney Road, Camborne, Cornwall, have recently been licensed with the consecutive callsigns G8FSW, G8FSX—so they should between them be stirring up the two-metre ether in those parts.

From their Jan./Feb. Newsletter we get it that the Royal Naval Amateur Radio Society now has 349 members, of whom 280 hold callsigns. The hon. secretary is CRS A. G. Walker, R.N.A.R.S., H.M.S. Mercury, Leydene, Petersfield, Hants.

The fee for the official Morse Test (to qualify for a full licence) is now £2. Application to take the Test should be made to: The Inspectorate of Wireless Telegraphy, Union House, St. Martin's-le-Grand, London, EC1A 1AR.

The Radio Amateur Invalid and Bedfast Club, with a membership of 400 blind or otherwise incapacitated Amateur Radio enthusiasts, shows an operating surplus for the year to Dec. 31 '72 of £418. That this association is heavily dependent on outside financial help is shown by the fact that donations for the year totalled the goodly sum of £558—without which, of course, no "operating surplus" could have been possible.

We gather that there are pressures developing to get the Hq. of Region I of the IARU moved from London to the new DARC headquarters at Baunatal, near Munich. The RSGB is a large—if not the largest—contributor to the funds of Region I IARU, of which the secretary is Roy Stevens, G2BVN. We would support him in whatever action he thought fit to take to resist such a move. (There is no reason why the U.K. should be pressured into acquiescing unless there are clear advantages in making the move.)

Those who use spiral-bound log books, or made up in any form involving tear-out sheets, are reminded that the Ministry require the pages to be numbered in sequence before use—in other words, the inspector must be able to check that pages have not been abstracted from the running log record. And while on the subject of the regulations, Class-B licensees should remember that they are *not* permitted to work across to any frequency-band below those for which they are licensed—that is to say, G8/3's must not indulge in cross-band operating with stations transmitting on 10-160m. (Please don't challenge *us* about this—write to the Ministry. It is they who make the rules!)

Anent the note regarding the CHARN Fund, on p.37 of the March issue, we are now informed (by G3GDW, of the Torbay Club) that the amount handed over was £100, and not as stated. The beneficiary is to be the Brixham Cheshire Home.

TRANSISTOR TRANSMITTER FOR TOP BAND

VFO CONTROLLED — RUNNING
FULL INPUT — /P, /M OR BENCH
OPERATION — DESIGN
AND CONSTRUCTION

R. GOULDSTONE (G3TAG)

THE transmitter described here was the fourth in line of a series of units to be constructed over a period of some three years. A large number of circuits and layouts were tried under actual operating conditions during this time, and this the final design embodies the most reliable parts of these.

It was found at the outset that the usual complaints about transistor transmitters were as follows: (1) Poor AM characteristics; (2) Severe FM content, (3) Poor note on CW, (4) High harmonic content, (5) Catastrophic PA transistor failure.

Condition (1) was found to be almost always due to the use of an inadequate PA transistor. A large number of medium power HF transistors will handle the 800 mA at 12 volts required under CW conditions, and give good results. Trouble crops up, however, when collector modulation is applied. The fault is due to the fact that a transistor's gain has a tendency to fall as the collector current is increased, particularly if the transistor is being pushed to its limits. This non-linearity causes flattopping of upward modulation peaks. Some improvement can be obtained by upward modulating the driver stage; but this cure can only be carried so far.

Conditions (2) and (3) are both caused by oscillator troubles and can be due to poor VFO design, stray coupling or poor layout.

Over driving the PA transistor in order to obtain adequate modulation depth was found to be one of the main causes of (4), resulting in delightful TVI, BCI and front-door knocking! Some PA circuits published in the past have also been found to give a first-class sawtooth waveform output. These can be removed by using a good ATU but there seems to be no point in using the Tx to warm up the ATU when we want the power into the aerial. One well-known design was found to have a PA efficiency of only 30% when all the "bent bits" were filtered out.

Failure of the PA (5) is one of the worst problems to overcome. This seems to be due to two things: First, overdriving and exceeding the base emitter reverse voltage limits of the PA transistor. Secondly, self-oscillation caused by instability in the PA circuit. These can, however, be prevented by careful choice of components and layout.

By taking all these points into consideration the transmitter described here has first-class AM characteristics, a T9 note on CW and its PA efficiency is around 70%.

(1) The VFO

In order to keep the number of tuned stages to a minimum and therefore eliminate one of the main causes of instability it was decided at the outset to use an aperiodic-transformer coupled driver stage. From this it will be realised that the signal source (VFO) must be as clean and free from harmonics as possible. The

Table of Values

Fig. 1. VFO and Buffer circuitry

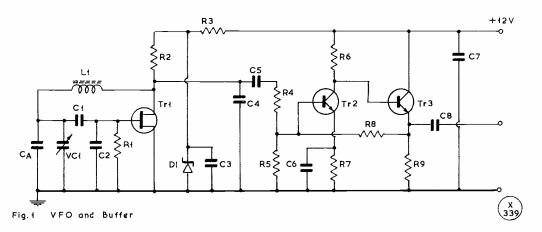


Fig. 1. The VFO and Buffer stages.

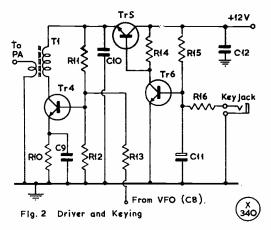


Fig. 2. Driver and Keying stages.

Table of Values

Fig. 2. Driver and Keying stages

Notes: See text reference R12, R13. T1 can be Type CRO-71-12/AC, 12 mm. o.d., 6 mm. i.d. by 3 mm. height.

oscillator must also run at the radiated frequency.

Several well known VFO circuits were tried with both FET and dipolar devices but all suffered from both FM and a high harmonic content. Finally the FET layout shown in Fig. 1 was tried and found to be ideal on all counts. Drift is about 100 Hz per hour and the output waveform is a clean sine wave in the region of 3 volts p-p. With the components shown in Fig. 1 the tuning scale will be almost linear over the range 1.8-2 MHz. Transistors Tr2 and Tr3 form the buffer stage, giving good isolation and a low impedance output.

It is recommended that this unit be constructed on a small P.C. board about $2\frac{1}{2} \times 1\frac{1}{4}$ inches to ensure rigidity, particularly if mobile use is anticipated. After construction and testing the capacitors Ca, C1, C2 and C4 should be prevented from vibrating by the application of a little *Araldite* adhesive.

(2) Driver and Keying Stage

As mentioned previously this is an untuned amplifier using a ferrite ring core as the output transformer in the collector of Tr4 see above.

The keying stage, consisting of Tr5 and Tr6, works as follows: Under key-up conditions Tr6 will be turned hard "on" and Tr5 "off". Therefore, the amplifier Tr4 will be inoperative. When the key is closed C11 discharges via R16, Tr6 turns "off" and Tr5 comes "on."

The capacitor C11 together with R15 and R16 gives the correct time-constant for envelope shaping.

If the CW facility is not required the keying circuit may be omitted, but R12 should then be changed to 150 ohms.

Resistor R13 can be varied to adjust the drive to the PA stage and will usually be between 100 and 200 ohms.

(3) The PA Stage

The RF power amplifier shown in Fig. 3 is a simple Class-C grounded emitter amplifier with an L-network to provide tuning and matching.

Diodes D2 and D3 protect the transistor from excessive base-emitter reverse voltage; although they are not essential they do give a greater degree of safety should the stage be overdriven.

Resistor R17 and capacitor C13 are essential to obtain Class-C operation. Some circuits have been seen in various publications in which this network has been omitted and the base of the transistor is connected directly to the driver transformer. Such an arrangement will usually cause the stage to run near to the Class-B region and efficiency will be rather poor. R17 may be adjusted to give optimum efficiency and can lie between 100-200 ohms but the value given will usually be quite satisfactory.

It should be noted that C13 and C14 must be of very low inductance. If inferior capacitors are used (in particular the tubular paper types) instability could

Table of Values

Fig. 3. PA stage for the TTx

Notes: Reference R17, see text. BD123* can be mounted on chassis in normal way using mica washers and insulating bushes.

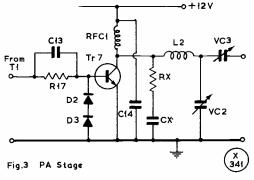


Fig. 3. PA stage for the G3TAG TTx.

Table of Values

Fig. 4. The audio-preamp. stages

C15, C17 = 200 $\mu\mu$ F, s/m	R21 = 2,200 ohms
$C16 = 2 \mu F$, elect.	R23 = 470 ohms
C18, C19 = $50 \mu F$, elect.	VR1 = 10K pre-set
$C20 = 100 \mu F$, elect.	Tr8 = 2N3819
R18.R19.	Tr9.
R22 = 470,000 ohms	Tr10 = BC108
R20 = 10.000 ohms	

result. No other special precautions need be taken in the construction of this stage. The transistor is simply mounted on the chassis in the usual way with insulating bushes and a mica washer. The input components are mounted below chassis and the output components above.

(4) Audio Pre-Amplifier

The circuit shown in Fig. 4 uses an FET in the input stage followed by a DC-coupled transistor pair. It will be noticed that in the table of values the gain control is given as pre-set. If, however, the user requires an extra knob to twiddle there is no reason why it should not be mounted on the front panel.

A crystal microphone giving an output of around 50 mV will be more than adequate, using this stage, fully to drive the modulator. If a dynamic microphone is used the gain may not be quite sufficient. In which case Fig. 4 can be replaced by any pre-amp of higher gain capable of giving an output of about 1v. r.m.s. from a low-impedance source.


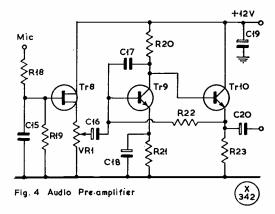


Fig. 4. Audio-preamplifier section, TTx.

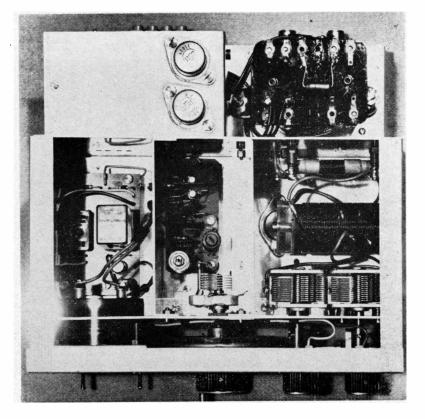(5) The Modulator

This is a normal transformer-coupled amplifier using Tr11 as a Class-A driver into Tr12 and Tr13 Class-B output stage. Negative feedback is applied to the emitter of Tr11 from the output stage via R28 and C21 to reduce distortion. The actual end of T3 primary to which this feedback loop is connected will have to be determined by trail and error. If it is on the wrong end the circuit will simply go into oscillation.

Construction of the transformers is quite simple if



General layout above chassis, showing each sub-unit in a separate compartment. The VFO is at lower centre, PA stage and associated tuning capacitors at right, and amplifier-modulator along the top. At lower left is the control unit described in Fig. 6.

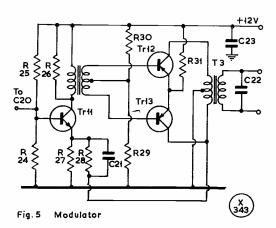


Fig. 5. The Modulator Stage. Note: Transformer for Tr11 is T2.

you are prepared to do some surgery on an old mains or output transformer from the junk box. First find one which has a lin. stack of lamination not less than $2\frac{3}{4}$ x $2\frac{1}{4}$ in. with a centre limb of about 7/8in. and side arms of around half-inch. Strip off all the old wire, retaining the bobbin if possible. Next wind on, trifilar, 100 or so turns of 22g. enamelled wire and secure with p.v.c. tape. Locate the start and finish of each of the three windings and label them A, B and C. Use the start and finish of winding A as the secondary. Connect the start of B to the finish C and use this as the centre-tap of the primary. The start of C and the finish of B then go to the collectors of Tr12 and Tr13.

Table of Values

Fig. 5. The Modulator section

C21 = ·022 μF C22 = 0·1 μF C23 = 500 μF, 15v. elect R24 = 150 ohms R25, R26 = 1,000 ohms R27 = 47 ohms R28 = 3,300 ohms R29 = 1.800 ohms	R30 = 20 ohms R31 = One ohm, wire- wound T2, T3 = See text Tr11 = BFY50, or BFY51 Tr12, Tr13 = OC35, or similar
---	---


When re-assembling the laminations it is advisable not to interleave them. For best results and a tidy finish, the I's should be butted on to the ends of the E's with a piece of card between them.

T2 can be made from an old transistor radio output transformer. A quarter-inch stack of laminations about 1 x 1\frac{1}{4}in. is all that is required. Mount the bobbin in a hand drill in some way and scramble on 1000 turns of 40g. for the primary. After covering with p.v.c. tape put on the secondary winding of 200—CT-200 turns of 34g.

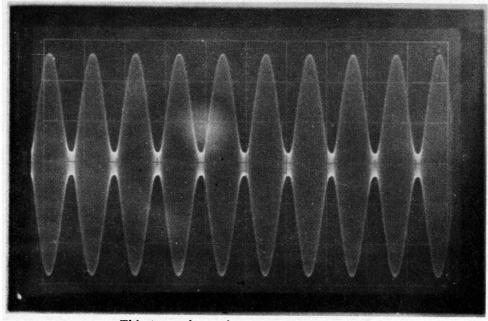
(6) The Control Stage

This circuit is included mainly as a matter of interest and it is not expected that the constructor will want to copy it in every detail—see Fig. 6 opposite.

The unit works as follows: Under receive conditions as shown in the diagram, signals from the aerial flow via C26, RL1 and C27 to the receiver. LP2 is the only part of the circuit taking power. RFC2 prevents the signal path being shorted to the HT line. When S1 is placed in the "net" position HT is applied to the VFO via D4 but prevented from entering the rest of the



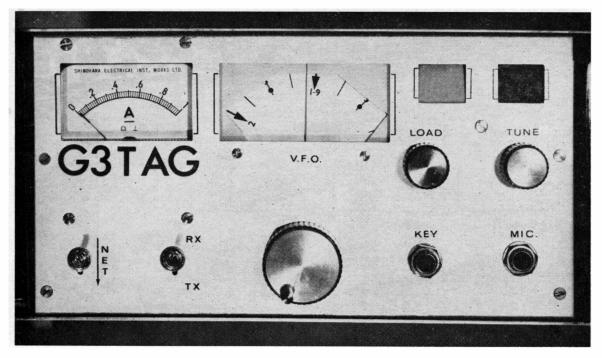This trace shows the output waveform with 1000-cycle tone modulation on the carrier.



Front-panel layout of the G3TAG Transistor Transmitter,

circuit by D5.

After netting S1 is returned to the stand-by position and S2 thrown to Tx. Current flows to the VFO via D5 and to the coil of RL1 through D6. LP2 goes out and LP1 is illuminated.

It follows, then, that RL1 contacts will change over, connecting the PA output to the antenna via C28 and C26. Also it will be seen that DC can now flow through R32, RFC2, RL1, RFC3 and R33 to the base of Tr14. This transistor will now turn on, energising RL2 coil, thus causing the relay contacts to close and route power to the modulator, driver and PA stages.

On returning to the Rx position RL2 will drop out, immediately turning off the PA, driver and modulator. RL1 will remain at "Tx" for a few milliseconds before changing back to the Rx contact. This is due to the energy stored in C24.

All this may seem a little complex for a change-over system but it does prevent the receiver from being damaged by RF from the PA. Also it makes it impossible for the PA to be energised before the change over to transmission is complete, thus preventing the transmitter from being run unloaded.

(7) Construction and Layout

No detailed constructional notes are given because it is felt that this will depend on personal requirements. In any case it is usually found that one has to make use of the materials to hand rather than try to make a Chinese copy. The block diagram given in Fig. 7 shows how the six units are interconnected in the

writer's transmitter. Note the diodes D8 and D9 which are used to provide some extra drive on upward modulation peaks. These can be omitted if desired with very little degradation in performance.

Switch S3 is used to remove the modulation transformer from circuit during CW operation—this should not be omitted if any CW work is dore.

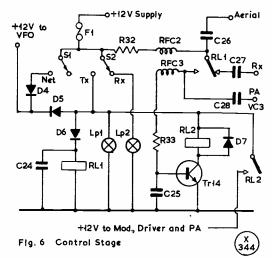


Fig. 6. Control stage as used by the author.

Note: Values on p.98.

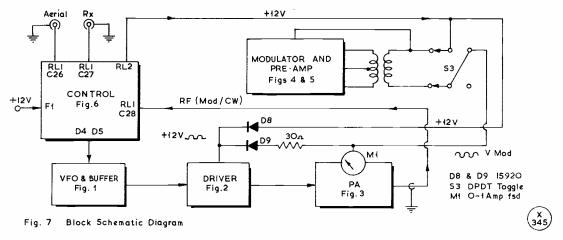


Fig. 7. Block diagram showing layout complete.

Providing care is taken to screen the VFO, driver and PA from each other and wiring is kept reasonably neat and short no trouble should be experienced.


(8) Operation

When running a TTx for the first time proceed as follows: Connect the transmitter to a power supply capable of providing 12 volts at 2 amps. During these tests put a 1 amp fuse in series with the 12 volt + lead, just in case.


Table of Values

Fig. 6. Suggested control stage, p.97

C24 = 100 μ F, 15v. elect. C25 = 0.1 μ F, disc	RL1 = Reed relay, c/o RL2 = Min. relay, 700-
C26, C27,	ohm coil,
$C28 = 0.1 \mu F$, disc	(Omron MH-2P)
R22, R23 = 18,000 ohms	S1, $S2 = SPDT$ toggle
D4, D5,	F1 = 1.5A, anti-surge
D6, $D7 = IS920$, or similar	Lp1,
RFC2,	Lp2 = 12v. low-wattage
RFC3 = 2.5 mH chokes	Tr14 = BFY50, or $BFY51$

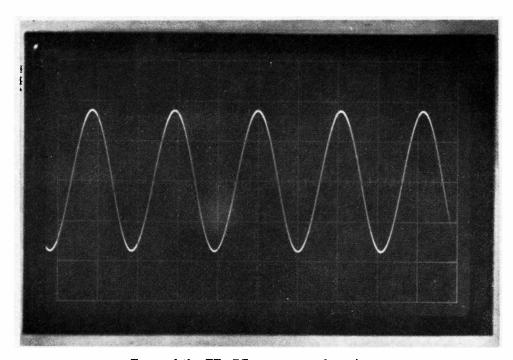

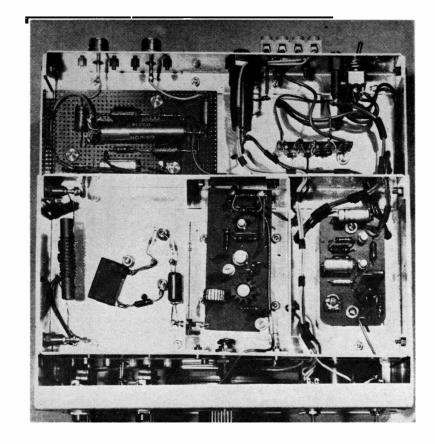Trace of the TTx RF output waveform into a 75-ohm resistive load.



Under chassis view of the Top Band transistor Tx, capable of running the full 10 watts—fixed, mobile or portable—from a 12v. 2 amp. supply line. Lower compartment, left to right: PA input and output harmonic filter; driver and keying stage; AF pre-amplifier. Upper right: AM/CW switch and PSU input compartments, with relays and Ae./Rx sockets at left.

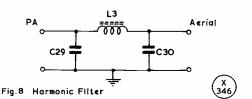


Fig. 8. In areas where TVI is a factor, the inclusion of the simple pi-network filter shown here may be helpful. It is designed to cut off at 3 MHz when used with a 75-ohm load. C29, C30 are 120 pF silver-mica, and L3 is 13 turns of 22g. on a quarter-inch dia. ferrite rod 2½ inches long.

Plug in a dummy load of 75 ohms with some form of output indicator, e.g., RF voltmeter or thermocouple ammeter. Switch on the station receiver and tune to 1.9 MHz. Next, put the "net" switch on and set the VFO to the same frequency. Set VC3 to maximum and VC2 to about half-mesh, cross your fingers and switch to "transmit." If all is well the PA collector current should be about 500 mA under these conditions. Now reduce VC3 slightly until this current increases to about 700 mA. Check the output meter and obtain a peak by rocking VC2. If the PA input power is still below ten watts decrease VC3 again and readjust VC2 for maximum output. Repeat these adjustments until

maximum efficiency is obtained with ten watts input.

The transmitter should be checked in this way over the entire band, each time tuning the receiver (muted) to the frequency. If at any time the PA goes into oscillation it will be heard on the receiver as "sharsh"—the Tx should be switched off at once and an effort made to cure the fault.

If it is not possible to cover the entire band with PA tuning, a different tap on the tank coil should be tried. The PA tank circuit shown here is fairly tolerant of the sort of load it is presented with providing it is not too reactive. However, here are a few simple tips that will help to give your lump of silicon a trouble free life:

- Do use an ATU and if possible an SWR meter,
- (2) Do tune for maximum RF power output and not for collector current dip,
- (3) Don't fiddle with the aerial while the transmitter is switched on. An open circuit will not do much harm but a dead short will put a nasty dent in your PA transistor,
- (4) Do not under any circumstances or excuse use unbranded, unmarked or "maker's seconds" transistors or you will be doomed to total failure from the outset.

MINIATURE MONITOR/OSCILLATOR

RF-ACTUATED DEVICE FOR MORSE SIDE-TONE

A. S. CARPENTER (G3TYJ)

SIMPLE audio frequency oscillators are not infrequently required in amateur operation and various designs appear in print from time to time. The need for such devices is well known to the CW transmitting fraternity whilst those striving for true amateur status usually rely on such a unit as an aid to learning Morse. Without monitoring it is difficult to send clean, easy-to-copy code and this is obviously appreciated by most makers of commercially-produced apparatus, particularly in the transceiver category, where "side-tone" is usually made available. Such monitoring signals are often generated in the 1000 Hz frequency region and may be derived from a phase-shift type oscillator to produce a sine-wave output.

Where no inbuilt audio monitor is included in the apparatus it is an easy matter to construct one as an outboard item using readily available components.

Table of Values

Fig. 1. Circuit of the Monitor/Oscillator

```
C1, C4 = \cdot 01 \mu F

C2 = 50 \mu F 6v.

C3 = \cdot 005 \mu F

C5 = 100 \mu F 10
                                                                          T1 = Interstage trans-
                                                                                         former type
D1001 (T1079)
                                                                                      with clamp
(Ardente)*
18,000 ohms
4,700 ohms
100 ohms
270,000 ohms
                     100 μF 10v.
                    BC107
                                                                         R1
R2
R3
R4
                     See text
                     Miniature 2-pole,
                                                                                =
                       3-way switch
                                   rotary
                                                                                      5,600 ohms
10,000 ohm
                                                                                 _
                                                                                                    ohms
                                                                                         miniature pot.
```

* (Obtainable from Home Radio Ltd.)

There are two ways in which such a device can be activated in sympathy with the keying function and these are (1) By directly keying the outboard oscillator using spare contacts on the key—in which case a DC power supply for the unit must be provided, or (2) By energising the monitor *via* a portion of the radiated RF from the transmitter, whereupon no powering battery is required. If the oscillator is to be used solely for Morse practice method (1) is obviously the only one possible.


It may also be convenient to utilize the same AF generator in other connections from time to time, e.g., to energise a CR bridge, or for AF tracing tests in faulty electronic apparatus.

The circuit of an easily made audio oscillator/ monitor is shown in the diagram, where transistor Tr1 functions in positive feedback mode due to the transformer T1. (The transformer specified is supplied complete with a fixing clamp and it will stand easily on a ½p piece!) By making the emitter resistor of Tr1 partially variable the note—the waveform generated—can be controlled within limits. Amplitude is also affected, therefore it is convenient if VR1 is made panel-controlled; output tone in the region 600-1000 cycles results, depending on the voltage applied. Transistor Tr2 is but a simple amplifier and the output can be fed either to Lx a medium-impedance insert-or to socket SK1 where external items or phones may be connected as required. The waveform generated is sine wave in form and although this could be obtained from a transformerless phase-shift oscillator the available output would tend to be low; a higher DC powering potential would also become necessary. A two-transistor multivibrator circuit could also be employed but since this generates a square waveform it is less popular here.

To energise the oscillator a small 3v. dry battery may be used or, as was mentioned earlier, the monitor can

Table of Values

Fig. 2. Rectifier Circuit

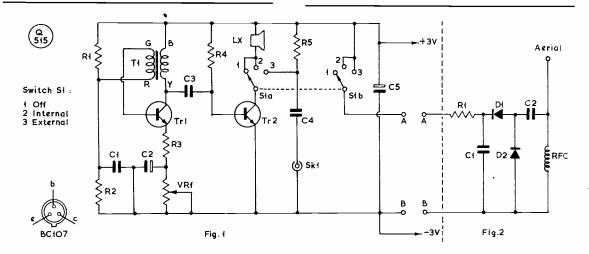

be driven by the transmitter itself merely by adding the six items depicted in Fig. 2. The aerial pick-up may be some 12in. or so of stiff copper wire and this is placed reasonably close to the transmitter output, aerial lead, or ATU, whereupon a sample of the RF generated when the key is pressed is developed across the choke and fed to the rectifying diodes D1 and D2, to produce sufficient DC to actuate the oscillator. The oscillator/monitor will also function if phone (A3 or A3J) is used, therefore it is essential to incorporate On/Off switching in any case. By using a third switch position "external" output to SK1 results.

Construction on an oddment of Veroboard or a small tag board is very simple if it is remembered that

even when sub-miniature items are used for VR1 and S1 they will still be the largest components. Even so the finalised unit can be made physically very small indeed.

Some minor changes to suit individual needs are envisaged and if, for example, the device is to be used solely for Morse practice Fig. 2 can be disregarded, in which case the key can be arranged to make-and-break either the battery feed or the emitter-ground lead of Tr2. If the note sounds chirpy it may be possible to clean it up by experimenting with a smaller value for C5, assuming that the chirp is not in fact due to the transmitter! In the unlikely event of the oscillator not starting, reverse the leads to either the secondary winding of T1 or the primary—but not both.

THE PHYSICS EXHIBITION - 1972

THIS, the 56th Physics Exhibition, was held at Alexandra Palace, London, during March 13—16, and will probably be the last to be mounted at "Ally Pally," as plans have now been finalised to use Earls Court as the venue for the 1973 show.

A special feature of this year's Exhibition was the montage arranged by the Electronics, Optical and Spectroscopy Groups of the Institute of Physics to mark the award of the 1971 Nobel Prizes, for both physics and chemistry, to members of the Institute—namely, Professor Gabor and Dr. Harzberg, the former for his original work in the field of holography, and the latter for his outstanding contribution to the development of molecular spectroscopy.

As in previous years, the accent was on fundamental research, particularly that in Universities, and the application of that research to commercial hardware.

Some twenty Universities or Technical Colleges had stands at the Exhibition, of which three seemed to be attracting the attention of the younger generation—the combination of Oxford and Heriot-Watt, who had co-operated to produce an infra-red radiometer to be launched later this year as a development of the successful Nimbus-4 instrument; University of Swansea with a solid-state, white-noise generator providing a flicker-free spectrum up to 100 MHz; and the University of Warwick, who had a working model showing magnetic levitation and its application to the train of the future, where it might well replace the current "wheel-on-track" system, and even the air suspension method at present undergoing trials in this country.

Among manufacturers' exhibits, the emphasis was on measurement almost exclusively, and pretty sophisticated some of it was, although the *mystique* was somewhat alleviated at the Mullard Educational Service stand where an electronic "fruit machine"—strictly on a non-profit making basis—had been installed as an example of their projects for student construction.

Westminster School were showing their weather satellite receiving and recording gear, as described in SHORT WAVE MAGAZINE for July 1971 and, subject to local QRM, were to attempt to receive pictures direct from *Nimbus-4* and *ESSA-8* during appropriate passes or, if this were not possible, had tapes available to demon-

strate the working of the apparatus.

For the less than highly technically trained visitor, these Exhibitions may seem tough going, but the advanced techniques of today become the standard practice tomorrow and keeping up, or even attempting to keep up, with modern developments, is unlikely to be a waste of time.

A.H.D.

NOTE FOR AUTHORS

When being offered articles for possible paid publication in Short Wave Magazine, we are often asked the sort of questions already answered under the heading "Authors' Mss.", to be found on the Contents page of any issue of the Magazine, where it has been appearing literally for years. If material is prepared strictly along the lines laid down there—which, in the case of technical articles, involves a study in detail of how such articles are presented in the Magazine—you will not go far wrong. Yet we are still offered contributions demanding extensive Editorial marking and adjustment simply because they do not conform to our setting convention (which means how you see them in print). And this as well as the work that may be required on the purely technical side.

While no article can be expected to go through exactly as the author composed it, those that require minimum Editorial attention always command the highest fee. Authors should also note that we expect their material to be "right the first time"—this means not only careful drafting in the first place but also checking and re-checking before sending it in. A full copy should be kept of the article complete, in case the Editorial Dept. have any queries.

In the Amateur Radio field, we pay the highest rates and are always only too glad to see, for early appearance, material that merits generous payment.

> For this month's Readers' Small Advertisements see pp.122 to 127.

LOW POWER NBFM FOR SEVENTYCEMS

CIRCUITRY, NOTES AND RESULTS

A. JUNGBLUTH (F6APU)

("Radio REF")

Translated from the original by A. H. Dormer, G3DAH

IN view of the increasing amount of activity on 432 MHz, it is often useful to be able to QSY from 144 MHz to 70 cm without having to couple up a tripler, tune it and connect it to an aerial. The solution is to have a compact transmitter ready to go on the band immediately. It was for this reason that a low-power Tx (200 mW output) has been designed to facilitate not only cross-band duplex 144-432 MHz, but also short range duplex contacts on 70 cm, the latter providing always that two antennas are available.

Description

The transmitter is built on single-sided copper clad board measuring 10 x 6 cm, and consists of five stages as follows:

(1) The oscillator is designed round a 72 MHz xtal, the transistor being a 2N2369, but a 2N706 would serve


equally well.

- (2) The tripler uses a 2N2369, which must be contact-cooled, to give 216 MHz. The output is connected through a bandpass filter to the 216 MHz amplifier.
- (3) The 216 MHz amplifier has a BSX61 in common emitter mode, but may be substituted by a 2N2219, BSX60 or BSX59, with a reduction in the output power. The transistors were chosen having regard to their low price.
- (4) The doubler consists of the base/collector junction of the BSX61 (or 2N2219) or any other epitaxial planar device of equivalent rating, with the collector connected to the case. Alternatively, a silicon diode of the 1N914 variety would serve.
- (5) The microphone pre-amplifier is designed for a xtal microphone, so the input impedance is relatively high. The varicap diode is connected between the amplifier and the input to the oscillator, and is biased at about +3 volts to give symmetrical NBFM.

The RF indicator which is incorporated in the Tx indicates that the equipment is functioning correctly and also shows the state of the batteries. It is constructed by inserting a short length of insulated wire under the braid of a piece of coaxial cable 5-10 cm long, and connecting one end of it to an OA47 diode and the other to a 150-ohm resistor. The meter should have an f.s.d. of less than 500 μ A.

Setting-Up

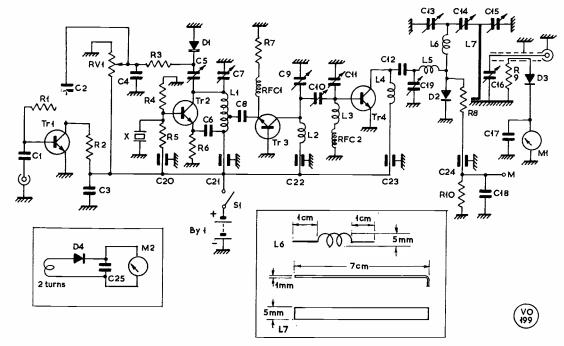Once the wiring has been completed, disconnect temporarily the supply to Tr1, Tr3 and Tr4, set C5 at minimum capacity and adjust C7 for oscillation, as



Circuit of the F6APU 70-Centimetre Tx.

(Note: R1 joins to C2)

Table of Values

Circuit of the 70 Cm Tx by F6APU

```
M1, M2 = 0-100 \muA f.s.d.
D1, D2 = BA102
D3, D4 = OA47
BY1 = 12-18v. batt.
RFC1,
RFC2 = 10 turns 22g.,
                              01 μF
                      \begin{array}{l} = & 3\text{-}30 \ \mu\mu\text{F} \\ = & 22 \ \mu\mu\text{F} \\ = & 25 \ \mu\mu\text{F} \end{array}
             C19
                                                                                                           5 mm. dia.
BC107, BC108,
BC109
2N2369, 2N706
C15, C16
C13, C14
C20, C21,
C22, C23,
                             0·6-6 μμF
0·3-3 μμF
                                                                                          Tr3
Tr4
                                                                                                           2N2369
BSX61, 2N2219
                                                                                                                                 2N2219,
                                                                                                               1N914
                                                                                                           6 turns, 8 mm. dia.
2 turns, 6 mm. dia.
One turn, 8 mm. dia.
                              .0022
                                              μF,
                                                            feed
                                                                                            L3
L4
                                thru
              R1
                             1 megohm
12,000 ohms
              R2
                      =
  R3 R4,
R5
R6, R7
                                                                                                            3 turns, 8 mm. dia.
2 turns, 5 mm.
dia., one cm.
leads
                             10,000 ohms
                              100 ohms
100,000 ohms
             R8
R9
                                                                                                            see diagram inset,
with 1 cm. wire
(L8) coupled to
                       =
                              150 ohms
                               10,000 ohms
                              10K potentio-
                                meter
```

Note: All coils L1-L6 self supporting, in 20g. enam.

shown by the RF probe in Fig. 1. Adjust the tap on L1 for clean oscillation—it should be at two to three turns from the supply end of the coil, then check the frequency with a GDO. Set C10 at minimum capacity before connecting the supply voltage to Tr3, couple the RF probe to L2 and tune L3 to resonate at 216 MHz with C9. Re-adjust C7 for maximum current through Tr3. Adjust the tapping point of the 25 pF capacitor on L1 again for maximum current through Tr3. Connect the +15 volt supply to Tr4 and adjust C10 and C11 for maximum current through Tr4, then adjust C12 and C19 for maximum indication on the meter. touch capacitors again for maximum. C13, C14 and C15 should then be adjusted to give maximum RF current in L8. Ensure that the RF is at 432 MHz by absorption wavemeter or Lecher line, remembering that when the lines are resonant at 432 MHz, a lamp load connected at the output socket will go out.

Now it only remains to look at the audio side. Connect the +15v. supply to Tr1 and adjust R1 so that the collector of Tr1 is at a potential of half the supply voltage. Connect the microphone and screw in C5, at the same time unscrewing C7 by the same amount to maintain oscillation. (The greater the capacity at C5, the greater the deviation.) A check with another station is most valuable at this point. The final adjustment, once the aerial is connected, is to touch up C16 for maximum output. The current drain at 15 volts should be about 70 mA.

Results

Several versions of this Tx have been constructed and have given good results for local contacts, but QSO's have also been made at distances up to 100 km. using a 19-ele, beam.

Further information may be obtained from F6APU, A. Jungbluth, 3 rue des Tulipes, (67) Lingolsheim, (TPR), France. Please do *not* contact G3DAH, who has merely done the translation!

TONE MODULATED OSCILLATOR

FOR MORSE PRACTICE AND GENERAL TEST PURPOSES

J. MORRIS (G4ANB)


THIS circuit was devised when a local G8/3 asked for some slow Morse to be sent over two metres for practice purposes. As the receiver in use had no BFO, MCW had to be used. The oscillator gives a tone which is fed firstly to a speaker, for monitoring, and secondly, via an audio mixer circuit, to an output socket.

This output can be used to feed either the transmitter modulator or a tape recorder. By using the mixer, the station microphone can be left connected and a quick and easy change over from MCW to AM can be made. For face-to-face practice, of course, this output can be left unconnected and the speaker only used.

Circuit

Transistors Tr1 and Tr2 form a multivibrator circuit, the frequency of which is determined by capacitors C1 and C2 and the base bias resistors. The values given were found to give a suitable note, but the note can be lowered in pitch by increasing the value of R3 (and vice-versa) if so desired. If a continuously variable note is required, then R3 should be replaced with a 10K potentiometer.

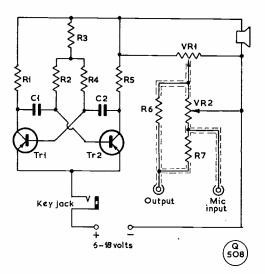It will be noticed that the speaker coil passes the whole of the oscillator current. This is the basis of operation of the circuit. Tr1 and Tr2 have different collector loads, so that when the circuit flips from one state to the



Circuit of the tone-modulated oscillator, as described in the text. Values are: C1, C2, .05 μF ; R1, 220 ohms; R2, R4, 10K; R3, 5.6K; R5, 1K; R6, R7, 220K; VR1, VR2, 250K potentiometer; Tr1, Tr2, OC71, NKT214 or similar.

other, there is a change in the current flowing through the speaker coil and so an output is generated. This arrangement allows the use of a low-impedance speaker without a transformer. VR1 taps off an appropriate voltage from across the speaker and feeds it to one end of the mixer potentiometer, VR2, the other end of which goes to the microphone input. As the earthed slider moves from one end of its travel to the other, it bleeds to deck more and more of the unwanted signal. Thus, by turning this control across its track, either the keyed tone or the microphone signal is passed on, via resistors R6 and R7, to the output.

Construction and Use

Any convenient form of construction may be used, but care should be taken over the screening of the audio leads. The speaker can be of any impedance from 3 to

80 ohms, the low-impedance types probably being cheapest to obtain. (One from an old TV set is ideal.) Almost any surplus transistors will do, but of course the supply polarity must be reversed if n-p-n types are used.

After checking that the oscillator is working through the loudspeaker, the output may be taken to the transmitter. The gain of the Tx should first be adjusted using the microphone, and then VR1 set to give a suitable strength of oscillator signal. By adjusting VR2 it should be possible to pass only the tone or the mic. signal to the Tx. If the oscillator is not to be used over the air, then VR2. R6 and R7 can be omitted and a tape output taken from the slider of VR1.

An oscillator of this sort also has obvious applications as a tone modulator for the transmitter and for general checking and calibration purposes.

WHT BANDS

A. H. DORMER, G3DAH

NCE again, there seems little that can be said about DX propagation on any of the VHF bands during the last few weeksunless it be that there wasn't any! Or at least, that very little was observed in the South. The non-operation of the U.K. two-metre beacons during the power cuts made it difficult to assess exactly what was happening on that band, and the general observance, by the majority of amateurs, of official requests to "economise in the use of power" meant that activity also was at a low level. However, some idea of propagation could be obtained by beaming towards Europe, and this exercise confirmed the doleful picture. An unusual occurrence was

the appearance of Sporadic-E on 4m. during the early evening of March 6, when G3OHH reports listening to a complete symphony from Poland on 70.6 MHz.

A check back on conditions during February and early March, 1970, shows that much the same situation prevailed then, but the corresponding period in 1971 did exhibit the odd lift, particularly on 2m., and to a lesser degree on 70 cm.

However, there are some grounds for optimism. For one, it can't go on like this for much longer, and secondly, we are approaching the season for Auroral displays. In the past, March and April have been more productive of DX contacts by this mode than the summer months, and there seems no reason to doubt that they will again be forthcoming—so G3DAH, for one, will be polishing up the key.

For those newcomers who have not yet had experience of making Ar contacts, the usual procedure is to point the beam slightly East of North and tune the CW sections of the bands (2m. or 4m., that is) since no auroral reception has ever been reported on 70 cm. Due to Doppler shift effects in the reflecting curtain, notes which are normally T9 deteriorate to T5 or worse and the reports passed indicate this by the addition of the suffix "A." For example, where the usual RST report might be 579, the Ar report would be 57A. It is a feature of these conditions that auroral propagation may exist at the same time as extended tropo., so the "buzz-saw" note may alternate between T5

and T9. Although phone contacts have been made via Aurora, the Doppler shift makes copy extremely difficult, if not impossible, on AM or NBFM though very slow and distinct phrasing will get through on SSB. Whilst there is no infallible method of predicting an Aurora (and, be it noted, not all visual displays are accompanied anomalous radio propagation) some indication of the imminence of auroral effects can be forecast by listening to GB3VHF on 144.50 MHz with the beam headed North. If the note sounds rough, or if there is a "burble" on it, it is worth having a look on the CW ends of the bands. So, let us hope that both newcomers and the old hands will be notching up that UQ2 this next time!

Contests

The last of the 70 cm. Cumulatives has come and gone, and, by and large, it's a pretty sorry story. On no occasion has propagation been up to a really good standard, and at times has been diabolically poor. Take this fact, and the power cuts, into consideration and one reaches the ineluctable conclusion that scores are going to be low, both in the number of contacts made and in distances covered, all of which is doubly unfortunate, since newcomers may get a completely false impression of the potential of the band. All participants, old and new alike, must surely enjoy a contest more when there is plenty of DX to be worked. Of course, these were Winter Cumulatives, and one can but hope that the Autumn ones will be more productive.

The 144/432 MHz Open over the weekend of March 4/5 also failed to come up to the expectations of many, although propagation was better on the Sunday than the Saturday. Two metres was certainly livelier than 70 cm., in spite of the multiplier on the higher frequency band, but few 200+ mile contacts seem to have been made, and many complaints were heard about the low activity levels. Under these conditions, SSB certainly showed its merits-the contacts between G8CIW in London and G3BW in Cumberland and GD2HDZ in I.o.M. were good examples. In view of the conditions, it was surprising that more use was not made of CW on both bands. Scores logged towards the end of the contest were generally lower than those in the corresponding event last year, a notable exception being G8BHH/P, 24km. West of Hereford, who was heard on 2m. passing 207 just before closing time. Agreed, he was operating from a much sought-after county, but that figure cannot have included many local contacts at one point each, and his final total, with the distance multiplier taken into account must be fabulous. G3OXD/A was around 170, and G8DQX about 180 at the close. A couple of high spots were the G8CHW/A (Oldham) contact with G3MOT (Oxford), and GD2HDZ / G8BCG (Manchester) QSO on 70 cm. Incidentally, G3MOT said that he had just come off the HF bands where he had made 300+ QSO's during another sort of contest, and he certainly sounded a bit hoarse!

Better to assess the situation, your scribe did some homework on his own results, and the following figures are quoted in the belief that they are probably fairly representative: Contacts per hour of operation this year were 7.1 compared with 7.7 last year, and on a 24-hour basis that represents 25 fewer contacts vis-à-vis 1971. The crunch comes, though, when the points per contact are computed-5.83 last year but only 3.1 this year, and this is indicative of the lower ranges which were achievable under the prevailing conditions. Best DX this year was under 200 miles against

just over 300 miles last year.

Forthcoming events are the 70 MHz contest on April 8, the 432 MHz event over May 6/7 and the 144 MHz contest on May 21.

Activity

There have been many attempts over the last few years to increase the level of activity on the VHF/UHF bands—some have met with greater response than others, some died after a very brief life, and others never really did get off the ground—and the need to encourage more operating, particularly on the 4m. and 70 cm. bands, remains as important as ever.

It was good news, therefore, to learn that the old firm of G8APZ /G8AZU, who did so much to encourage 70 cm. traffic with their own contest last year, are still at it. They have now enlisted the help of two other devotees of the band, G8CIT and G8DKK, and go out

portable every Sunday morning from a good location, usually in the Home Counties, but occasionally as far afield as GW, in fair weather and in foul. In order not to commit themselves too deeply, they do not announce beforehand just where they will be, but one can always reckon that, with the experience that they have now gained, it will be a site which will offer some reasonable DX when conditions are right; the choice of Sunday mornings may be of assistance to those who suffer from the dreaded TVI on weekday evenings. Good hunting to themand thanks.

G4ALN (Romford, Essex) is also prepared to do his bit. Every Tuesday and Thursday evening during April he will be on 432-10 MHz CW with the beam N-W from 2100-2130z, and S-W during 2130 to 2200z. Skeds can be arranged and he is *QTHR* under callsign G8DLJ.

THREE BAND ANNUAL VHF TABLE

January to December, 1972

Station		METRES Countries	TWO N	TETRES Countries	70 CENT Counties	IMETRES Countries	TOTAL pts.
G5DF	17	2	30	4	17	1	71
G8BXX		_	28	2	17	1	48
G3NHE	_	- :	38	2	4	1	45
G3DAH [*]	3	1	22	2	10	1	39
GD2HDZ	_	_	23	3	8	2	36
G8CIW	_		30	4		_	34
G8EMS	<u> </u>	_	26	2	_	_	28
G3OHH	5	1	11	1	7	2	27
G8AGL		_	25	1			26
G4ALN	_		12	1	9	1	23
G4AJE			21	1		_	22
GM8BDX	_		14	3	2	2	21
G8BKR	_	- 1	6	2	5	2	15
G4ALN	_		8	1	1	1	11
F6BQH	_		7	3	_	_	10
G3EKP	1	1	4	2	1	. 1	10
G8DBX		_	6	2			8
G4AVX			5	1	_	_	6

Just a reminder that the Tables go through to December 31, 1972. The Three-Band Annual Tables show claims to date for the year commencing January 1, 1972. Claims should be sent to: "VHF Bands," Shorr WAVE MAGAZINE, BUCKINGHAM, as they accrue.

With the rate at which new licences are being issued, and the consequent increase in the amateur population on the two-metre band, it may be thought that any attempt to increase activity there was unnecessary. So it probably is, as far as AM and NBFM phone is concerned, but there is still room for encouragement for the CW and SSB men, and to this end, G3BA and some colleagues are trying to revive the idea of calling every hour on the hour between 7 p.m. and 11 p.m. each evening. We must all have heard CO calls going out or both modes at odd times with no response, and this in spite of the fact that one does not expect to have to cover the whole band for a reply, but if it were known that there would be a greater likelihood of a contact at set times, then this would be advantageous for all. Such a scheme has worked very well in contests where one has often heard an SSB operator come up on the hour, scoop up all the available contacts, and then revert to AM. The same is true of CW. There seems little reason, therefore, why such a scheme should not be equally successful under normal conditions. It seems well worth a try to get both SSB and CW out of the rut of indiscriminate calling and a low return rate, and may well prove to be a better scheme than the idea of "Activity Nights", which seem to change with bewildering rapidity depending upon the part of the country in which one lives, So, how about giving it a whirl?

And on Seventycems

Ingenious, and numerous, as the attempts have been to raise the tempo on 70 cm., none has succeeded completely and permanently, and one cannot help wondering whether -not only in view of the current claims by commercial interests on part of our UHF allotment, but for the good of VHF radio as a whole -Class-B licensees, after a certain date, should be confined, as originally, to 70 cm. and above, if not for all time, at least for a probationary period, during which they could get the "feel" of the bands and absorb the construction and operating techniques and characteristics peculiar to them. It would not be the first time that such a scheme had been operated successfully.

VHFCC Awards

Certificate No. 137 goes to G8DVZ (Northampton) for 2m. operations. He first came on the air in January 1971 with a series-gate modulated QQV06-40A, a Microwave Modules Mosfet converter and an AR88, but this gear has now been replaced by a Pye Cambridge running 16 watts to a four-ele. beam, all of which, from a 400ft, a.s.l. site, is getting him some nice DXfor example, he got in on the Italian opening last year. It has still taken more than 12 months to get all the QSL cards in, though!

Robert Lee, G8CQR (Hemel Hempstead) gains Award No. 138 for his 2m. work. Initially, in May 1969, he ran 40 watts to a QQV03-20A with a pair of 6BW6 modulators, but this has now been replaced with a QQV03-10 job using EL84's in the modulator. The FET converter and the Sommerkamp FR-DX500 receiver, together with the 8-ele. beam at 27ft., are still in use from the 420ft, a.s.l. site. An unusual feature of his claim is that the QSL return rate is about 60% from British stations, and 100%(!) from Continentals. There must be a lesson to be learned here!

G8DQN, Norman Hunter (Hornchurch, Essex) is now the holder of two-metre Award No. 139. He runs 35 watts to a QQV03-20A with TT12 modulators, a G3HBW converter and EC-10 Rx. The 6/6 antenna is at 20ft. with a good take-off in most directions, although three tower blocks some 500ft. away do not help matters in the easterly direction. Nevertheless, he is making Continental contacts under the right conditions.

In the notes about applying for VHFCC, on p.45 March, we might have mentioned that good black-and-white photographs of VHFCC stations are always welcome, with appropriate notes. This is not, of course, a condition for obtaining the Award but, like the station details, always of interest—and those that we can use are paid for on publication.

Beacon News

GB3ANG, the Angus two-metre beacon, is now back in full operation on 145.950 MHz, a fact which will please many users of this valuable aid to the assessment of propagation

conditions. Our thanks to GM4HR, the beacon keeper responsible for this installation.

A new 2m. beacon is now in operation in Switzerland at Chasseral in QRA Locator DH66f. The frequency is 145-985 MHz, and the callsign HB9HB, output 10 watts. Reception should be possible under good extended-tropo. conditions.

Another new one that is going to be a bit difficult under normal conditions, but which may be possible during a strong Aurora, is UK3A located near Moscow. Frequency is 145.4 MHz and power output 50 watts. Best times to look for it are between 2015z and 2030z and 0230z and 0245z, when it is beaming West, provided always of course, that the aurora is obliging enough to manifest itself at those times!

The Dutch 70 cm. beacon is now off the air while $PA\emptyset VD$ completes the "transistorisation" of the Tx. When it does reappear, it will be operating on the new frequency of 433.00 MHz.

In addition to the German FM repeaters, of which details were given in this Column in the December 1971 issue of Short Wave Maga-ZINE, information has now been received of new installations in Scandinavia. SKØDZ is undergoing trials in Stockholm. calling frequency will be 144.900 MHz and the reply on 145.800 MHz. Output power is 10 watts, and access to the repeater is by 2172 Hz Time-limiting circuits are tone. incorporated in the installation giving continuous use for ten minutes before resetting becomes necessary. An interesting feature is that the problem of interaction between receiving and transmitting antennae has been solved by siting them remotely from one another and connecting them by a 70 cm. link.

The second Swedish repeater is located at Rommeleasen, South Sweden. The technical data are similar to those for SKØDZ, but the output power has been raised to 20 watts and the connection between Tx and Rx is by landline. It is still on test and not in continuous operation. It is reported 'hat there is also an FM repeater on trial in Copenhagen but no details are available other than that the operating frequencies are 145 350 MHz and 145 850 MHz, testing is being

done by OZ8JS, and access will be by double-tone 1400 Hz + 2200 Hz. It seems a pity, in the interest of standardisation, that the Tx/Rx channel spacing selected for the Scandinavian repeaters is not identical with the German, and proposed British, systems.

AMSAT Satellites

If all goes according to plan, the AMSAT satellite Oscar-B should be launched in June of this year. The exact date is subject to meteorological requirements, but appears firm from all other considerations. If the launch is successful, and the satellite is put into the correct orbit, it will become known as Oscar 6, and so follow its illustrious predecessor Oscar 5.

The orbit parameters are determined by the launch vehicle, again a *TIROS* weather satellite, so that we may look for a path some 1,000 Km. above the earth, probably sunsynchronised, and closely following that of *Oscar 5*. A life of one year is

planned as, unlike previous projects of this nature, the nickel-cadmium batteries can be recharged by energy from solar cells.

Three translators will be carried:


- (1) A linear translator from 70 cm. to 2m. up—frequency 432·15 MHz \pm 25 kHz, and down on 145·95 MHz \pm 25 kHz. The 10 watt p.e.p. Tx can be operated on 2·5 watts to conserve power. A beacon Tx on 145·98 MHz is also incorporated in the design.
- (2) A linear translator from 2m. to 10m., up on 145-95 MHz \pm 50 kHz and down on 29-50 MHz \pm 50 kHz, output power 2 watts. This installation is also equipped with a beacon on 29-45 MHz.
- (3) An NBFM translator, 2m. to 70 cm., with up-frequencies 145-80 MHz, 145-85 MHz, 145-90 MHz and 145-95 MHz, and corresponding down frequencies of 435-10, 435-15, 435-20 and 435-25 MHz, unfortunately well outside the U.K. communications segment of 70 cm.

It was planned originally that the four channels in (3) should be transmitted simultaneously, but it seems that the available power supply capacity would be exceeded if this were done, and so it is likely that only the 145-80 MHz/435-10 MHz pair will be used. With a bit of fiddling

with the converter it might be possible to get it up to 435·10 MHz provided that the IF strip will tune up there. No beacon is provided in this translator as it serves *per se* as a beacon.

In the event of interference with other services, or if the power loading becomes too great, only one transponder will operate at a time. Similarly, if the battery voltage drops below the design operating level (or the ambient temperature rises beyond prescribed limits) the output power will be reduced automatically to 2.5 watts, at which level the solar cells will cut in to recharge the batteries. Should this safety measure fail, then all transponders will be switched off, and only an emergency beacon on 10m. will remain active.

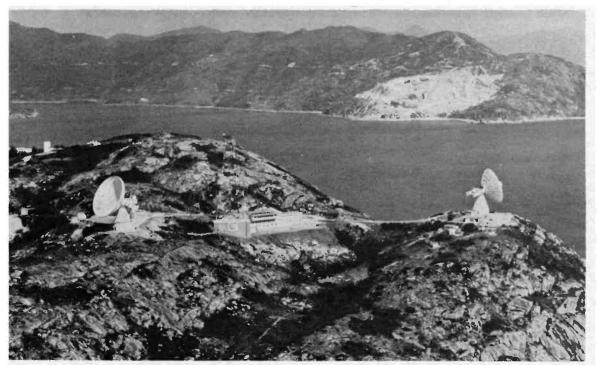Oscar 6 will be spin-stabilised with respect to the earth's magnetic field, and this has meant that because of the field reversal at the poles the satellite antennae must be circularly polarised to minimise fading at the



As well as being strategically placed for the China trade, Hong Kong has become an important link in the realm of international communication by satellite. The site we see here—on Stanley Peninsula, southernmost point of Hong Kong Island—in effect scans the world on a 24-hour basis. These two earth stations, the newest of which is on the left, have been established by Cable & Wireless, Ltd. and complete the East-West coverage. The new dish is 97ft. in diameter and embodies the latest techniques.

linearly polarised aerials common at ground stations. They consist, in fact, of crossed dipoles in a "Turnstile" configuration, and are arranged so that in the Northern hemisphere the 70 cm./2m. translator gives righthand polarisation and the NBFM translator left-hand.

As far as equipment at the ground stations is concerned, almost any good converter, with an antenna gain of 12-14 dB or better, should serve. Tx powers will need to high, full legal limit for both the 70 cm./2m. and 2m./70 cm. translators, and best results are likely to be achieved with SSB or CW when working through the linear translators. The NBFM limits are \pm 7-5 kHz, but that doesn't mean that you have to exceed the IARU standard!

Information on the launch date will be given when it becomes known, as will details of the exact orbital parameters when they have been established.

Club and Group Activities

The mid-Severn Valley Teleprinter Group are organising a two-metre contest on Sunday, May 14 next between 1000z and 1600z. Further information may be obtained from G3PWJ (to whom logs should be sent) or from G3NUE, both *QTHR*. The Group normally operates on the Group channel of 144-986 MHz, AFSK 850 Hz shift, at 50 bauds.

In January this year, a Group known as the "U.K. FM Group (London)" was formed with the object of seeking a common NBFM frequency a n d transmission standards in all zones throughout the Band Plan. They hope that other Regional Groups may be formed who will co-operate with them in this endeavour, and those interested are invited to contact G5AGX, QTHR. This seems a laudable idea. but as with other schemes which require the allocation of a specified frequency for operations of a particular nature, a certain amount of self-discipline will be needed. One has only to look at the abuse of 145.00 MHz, the mobile calling channel, by fixed station operators to appreciate this. The ploy must be—call on the calling channel and then vacate it when the initial contact has been made to make way for others.

The R.A.F. Amateur Radio Society will be holding their AGM at the Society Headquarters at R.A.F. Locking. Weston-super-Mare, Somerset, on October 21 this year, and the occasion will coincide with the 50th Anniversary celebrations of the establishment of No. 1 Radio School. It is hoped that many members of the Society, far-flung though they may be, will attend, as well as many of the "Old Boys" of the School. Further details may be obtained from G3GNS, QTHR, who for many years has been active in the Society's interests.

The annual London VHF Convention takes place this year at the usual venue—The Winning Post Hotel at Whitton, near Twickenham, on Saturday, April 22. Tickets, at £1·80 for the whole event (£1·50 for the dinner only, or 40p for the afternoon) are available from A. Wheeler, c/o RSGB, at 35 Doughty Street, London, WC1N 2AE. Envelopes should be marked "VHF Convention."

Scottish News

It appears that conditions for the 144/432 MHz contest in March were as bad in Scotland as they were down South. The best signals were, fairly obviously, those coming from the well-sited portables such GM3ZVB/P (Lammerlaw), GM3YLD/P (Kilsyth Hills), and GM3OXX/P (Lomond Hills, Fife). Conditions on the ground seem to have been equally poor for these intrepid operators. 'OXX was snowed up in his tent for much of the time.

GM4AVH is the callsign of the newly formed "Pioneer Club" in Edinburgh, active on 2m. with a Pye Base station from the Club premises in Gilmerton, some 450ft. a.s.l., so they should be able to put out a fairly potent signal in most directions. GM8DOX is another station well received to the South from his QTH in Denny, Stirlingshire. He also does quite a bit of mobile operating.

GM8BDX, QTHR, is a call which is well known to many DX operators in the South. Alex operates from Duns in Berwickshire with 55 watts to a QQV06-40A and a 10-ele. at 38ft. For 70 cm., this Tx feeds a BAY96 varactor for which the antenna is an 18-ele. Parabeam at

30ft.; he would welcome skeds in the South and West, particularly GD and GC, during the summer months. Operating frequencies are 145.92 MHz and 145.52 MHz on 2m, and 432.90 MHz on 70 cm. He reports yet more 2m. activity from the Border counties-GM3FSD, GM3WIG, GM8CVN and GM8ETJ, all in the Hawick area, GM8EUG in Duns and G3KML in Berwick-on-Tweed, Northumberland.

Mobile operation appears to be on the increase in GM, and this has led in turn to Mobile/Static working from suitable high spots, so giving more opportunity for GM/G contacts. If only someone could move the Pentland Hills!


News Items

Another "hail and farewell" piece this month. Welcome back to G8AGL who is again on the air from East Yorkshire after an absence of some two years in South Africa. He is active on both two metres and 70 cm., and would welcome DX contacts, particularly from the far South-West and North-East, on Monday or Friday evenings. Welcome, too, to G8EDJ (Ashford, Kent) who is now G4AYT-to G4AZR, ex-G8FVQ who, only three weeks after getting his Class-B licence, took the Morse test and passed for his full call-and to G4AZK, who was G8FBD.

Farewell, perhaps a little precipitously, to G3FRV of Crawley who shortly becomes VK6RV. The Crawley Club are going to miss one of their most active supporters here, and RTTY operators on 2m. will certainly miss Ron's potent signal on 144.6 MHz.

On April 9, GM3XWJ/M will be on four metres whilst *en route* between Liverpool and Newcastle, and at some time during the afternoon from a fixed location on Hadrians Wall, Northumberland. The Tx runs 25 watts, and frequencies will be 70·26 MHz and 70·375 MHz—xtal controlled transmit/receive. All contacts will be QSL'd, *QTHR*.

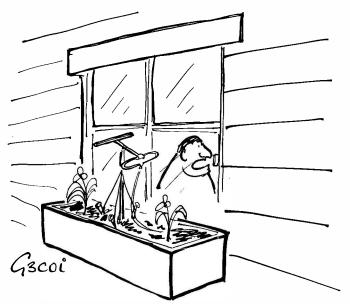Two newcomers to 70 cm. who are looking for contacts on that band are G3BHW (Margate) who runs 5 watts to a 14-ele. beam, and G3VJF of Whitstable with the same order of output power and a similar beam. Both are in danger of enter-



" . . . Using rather an unusual Seventycem antenna here . . . "

ing a state of severe depression caused by lack of QSO's, since both started up on the band when the present dismal set of conditions beset us.

GI3SUM and DL3YBA have a sked arranged for every Friday evening on 144.063 MHz, 2200z—2359z, with the object of finding out whether it is possible for them to make regular contact via sporadic meteors. Anyone copying the DL at these times might care to let GI3SUM, OTHR, know.

Readers who have heard GB2MT on the 2m. band may like to know that it is a special station set up in Chelmsford to commemorate the 50th anniversary of the establish-

ment of the first regular broadcasting service in this country from the Writtle, Essex, station of the Marconi Company. "Two Emma Toc," as it was known in those days, will be remembered with affection by many amateurs for whom it provided not only entertainment but also a Rx calibration service to boot.

G8EMS comes up with some more news of the EA phone station which was mentioned last month. He was apparently working a French station at 2250z on December 12 on 144.32 MHz, so again, any further identification would be useful.

In spite of the poor conditions during the March 144/432 MHz

contest, and an interruption due to necessity of replacing the coax feeder which had "become waterspaced rather than air spaced," GD2HDZ still managed to pull off some decent DX, his best effort on 2m. being with G8CIW (Loadon) and G8BBB (Ely, Cambs.) and on 70 cm. a solid QSO with G3NEO (Sheffield). He also reports working old-timer G3BW in Whitehaven on 2m. SSB, so those wanting a Cumberland contact will know where to look! (And we are very interested to hear of G3BW again after many years.)

Three-Band Annual Tables

A spirited start has been made with the Three-Band Annual in spite of the generally poor conditions prevailing since the beginning of the year. G5DF in Reading holds his lead and has obviously been wasting no time. It is good to see a GM and an F making an appearance. F6BQH is F1AOY (a holder of the VHFCC Award) and as such pretty well known in this country, at least in the South, while GM8BDX is the behard in the South when there is a bit of a tropo. lift on.

Deadline

April 8 remains the deadline for the next issue as it is hoped that the planned publication date for May will be met in spite of current production difficulties on the printing side—at any rate, we shall do our best. The address for news, views, claims and comment is: "VHF Bands," SHORT WAVE MAGAZINE, BUCKINGHAM. Cheers for now and vy 73 de G3DAH.

"TVI AND STUBS"—CORRECTION

G2HR points out that in his article (p.49, March), the "75 ohms" at 5th line down, right-hand column, should read 750 ohms. This brings the mathematics right!

AMATEUR RADIO RETAILERS' ASSOCIATION

At a well-attended Trade meeting in the Midlands on Sunday, March 5, a proposal to form an Amateur Radio Retailers' Association (A.R.R.A.) was discussed and agreed, with a founding-membership list of 14 firms in the radio-amateur retail trade. The secretary of the Association is L. J. Hellier, G3TED (Taurus Electrical Services), 26-28 Nottingham Road, Lough-

borough, Leics. (*Tel: 05093 5131*) to whom Trade enquiries respecting the Association should be addressed. One of the objectives of the new Association is to organise, during this coming October, a two-day Exhibition in the Midlands.

WHITHER ELECTRONICS—THE LIMITS?

Though the application of electronic techniques in many fields is well appreciated, is there a limit to what can be expected? This is a subject to be discussed by a panel of specialists, at a meeting on April 17, 6.0 p.m., at the Institution of Electrical Engineers, Savoy Place, London, W.C.2 (down on the Embankment), under the auspices of the I.E.E.T.E. Admission is free and tickets are not required.

THE MONTH WITH THE CLUBS

By "Club Secretary"

(Deadline for May issue: April 7)

(Please address all reports for this feature to "Club Secretary," SHORT WAVE MAGAZINE, Buckingham.)

In the last few months, it seems that seldom a deadline comes round but what something has to happen to make life a little harder—after the power cuts, this time we have to produce copy earlier to beat a period of disruption on the printing side. Because of this, your scribe is taking the reports as they fall, and cutting the normal rigorous selection procedure for the Short Notices. This may mean that some Clubs have been shortened beyond their fair share. If so, this will be put right later on.

First we must mention that the Swindon Club has been writing to various groups regarding their Two-Metre Project. It seems they have been very successful with this, and are now in a position to offer a "book of words" and kits of parts to build either a two-metre converter, a Tx, a modulator, or a complete transceiver, not to mention ready-folded metalwork for the latter, minus only cutouts for the boards and things. Details are available from G8AVG, 29 Okus Grove, Swindon, Wilts, SN2-6QA. It is understood the Swindon lads are even prepared to come and give a talk on this project, which is really going out of the way to help others. Include a large s.a.e. with Project enquiries.

Round The Country

The Midland Newsletter tells us of their meetings—these are at the Midland Institute, Margaret Street, Birmingham. However, we do not have a date for April, although it is believed that if you look out for them, some at least of the members will be at Drayton Manor Rally on April 16; or of course you can contact G8BHE, as Panel, p.112.

A most interesting newsletter from Wolverhampton this time, with, briefly, a note of their titles since 'way back in 1913, not to mention a very amusing piece on the old R.C.A. ET-4332 transmitter. As to meetings (Neachells Cottage, Stockwell Road, Tettenhall), April 3 is passed, due to the Bank Holiday, but on the 10th they have the Wolverhampton Astronomical Society coming along to talk about home-built telescopes, and their control—sounds an interesting evening. April 17 is a discussion session.

Every Wednesday at Newton House Community Centre, 203 Droylsden Road, Newton Heath, sees the Manchester lads getting together; once each month there is a lecture, April 12 being "Aerials" by G2ALN, and May 17 "Computers" by G3JIB.

Down West now, to Plymouth, at Virginia House, Bretonside, for the local meeting on the first and third Tuesday in each month, with a programme of talks and film shows, not to mention the essential AGM, which takes up May 2.

Doing things the right way is the principle adopted at Otley, where a new item of entertainment is a "Let's Talk About It" item where a member describes a bit of gear, and the design and constructional snags in building and getting it going. Any Tuesday you will find them in the Hq. at 14, Back of Court House Street, Otley.

First stop in Wales is at Port Talbot, to mention their Annual Social on April 11—somewhat of a house-warming of their new Hq., as all future dates are at this venue, namely the Rail and Transport Club, 39 Station Road, Port Talbot. All welcome and details from the hon. sec., as in the Panel.

South Birmingham have their home in Hampstead House, Fairfax Road, West Heath, on the first Wednesday of the month, which makes it April 6, for a talk on Stereo Sound by Mr. R. Savin.

Grand news for the Nigerian crowd. It seems that their president, Adebayo Browne, 5N2AAJ, can attend the Region I IARU Conference at Scheveringen, Holland, over May 15-19, which means the Nigerian chaps will be able to compile a really effective dossier on international Amateur Radio to present to the 5N2 authorities, asking for a statement of the position regarding licensing. Let us hope with them that they are at last able to persuade the Govt. out there to grant some new 5N2 tickets.

Now Purley, who are beginning to feel that their sudden departure from the old Hq. was a blessing in disguise! The general opinion seems to be that the new place is nicer, brighter and warmer than the old, and even the Hon. Treasurer is pleased—the rent is less! As the nights are now the second and fourth Tuesdays, they Natter on the 11th, and have a Junk Sale on April 25. The venue? Landsdowne Hall, Landsdowne Road.

It is not very often we hear from the G.C.H.Q. Club, Cheltenham—but once a year they have an open evening to show some of the wonders of the future to the rest of us. This year the event is on Friday, April 28, at 8.0 p.m., with the usual display, not to mention the bumper raffle. Well worth the time, is this, the more so for those interested in advanced professional techniques. Further information from G3PEO, as Panel, p.112.

Second and fourth Tuesdays is popular at the Wolverton and New Bradwell Youth club, because this is the evening the North Bucks. group hold their meetings.

Details of the programme are not available, precedence having been given to information about their two enterprising DX-peditions, to France and Scotland.

At Newark, the compiler of their Newsletter is quite a comic, in his way, but the details of the club Hq. and meeting-dates has again had to be passed over in favour of other things, so we must refer you to G3YCT direct (see Panel).

Acton, Brentford and Chiswick are to be found at Chiswick Trades and Social Club, 66 High Road, Chiswick, on April 18, starting at 1930, and we understand G3VUQ will be talking about Varicaps.

Alternate Mondays at Brighton Technical College means, for April, the 10th and 24th. The programme, we understand, will be announced. You can find them at the College, which is in Richmond Terrace.

Advance warning is given of the Southdown Annual General Meeting on June 5. However, before this, we note a Junk Sale on April 10, and a demonstration of Amateur TV on May 1.

A late change in the arrangements for Dunstable Downs, where the talk will be given by G3ZVI, who is filling a gap caused by the non-availability on the due date of G3RPE with his Microwave talk. This is for April 21, but you can find the meeting on a Friday evening by going to Chews House, 77 High Street South, Dunstable. April 7 features G3BPT, while the 14th and 28th are what they call "between weeks," for ragchewing, Morse, and R.A.E.

On to Bury and Rossendale and the first issue of their Newsletter, which we rather liked; the accompanying report mentions April 11, at the George Hotel, Market Street, Bury, when the technical director of the Nombrex concern will be demonstrating and discussing the range

of test equipment this firm manufactures.

At Echelford, the lads are booked in at the Hall, St. Martins Court, Kingston Crescent, Ashford, Middx. Here, it is the last Thursday, with March 30 down for the Annual General Meeting.

Now to Verulam, and their Hq. at the Town Hall; they have the Council Chamber laid on for April 19, for a demonstration of the latest from K.W. Electronics, a talk which was of necessity postponed last November.

Harlow have their own place at Mark Hall Barn, First Avenue, which lies between Kenning's and the All-Harlow Bypass. Details of meeting dates, the propramme, and whatever, may be obtained by dropping a line to the hon. sec., or better, by looking in at the Club meetings on Tuesdays or Thursdays.

Near neighbours Bishops Stortford have a different approach to meetings altogether; they have a single date each month, in a rented room, and almost always a formal lecture. Thus, between the two Clubs, the tastes of most of the amateurs in the area are catered for. April in Stortford sees members eagerly waiting the 17th, to hear the rest of the talk by G3VVS on Oscilloscopes (which came to a sad end in the February powercuts!) As for the place, try the British Legion Club at the top of Windhill; the meeting starts at 8.0 p.m. but a listen in the bar a few moments before will usually disclose some radioese being talked.

On April 15, at Emmanuel Church Hall, Barry Road, East Dulwich, the Crystal Palace crowd will be hearing a talk about Test Gear, including among others, the Grid Dip Oscillator, the Valve Voltmeter, and the Oscilloscope; the lecturer is not named, but this group





Part of the Midland Amateur Radio Society set-up for the Birmingham Boat Show over the second fortnight in February, for which they signed GB3BBS, with G8EXW/A on two metres. The HF-band station ran a KW-2000A-and-KW Linear with a trap dipole on the roof of Bingley Hall, where the Exhibition was held. Excellent coverage was achieved, world-wide, on CW and SSB. The exhibition itself covered, as well as boats, all outdoor activities associated with camping, underwater sports and caravanning and is an annual event, regularly supported by M.A.R.S. On the left, we see an equipment display, with G8ADV, president of the Society, and on the right G3JPN is operating GB3BBS, with G8FTU at the two-metre rig.

has an array of talent to call on and it could be any one of about six members!

Now Southgate, who have their place in the Civil Defence Hut, Bowes Road, right opposite the Arnos Grove Tube station. From where we sit, the date to book looks rather like April 13, but we suggest a check with G3XMV first-see Panel below.

One of the rather few Clubs in Scotland is away up in Inverness, where they have a new Hq. address at the Cameron Youth Club, Planefield Road, Inverness. The A.G.M. falls on April 6, and from then on, the meetings will be fortnightly on Friday evenings.

From North to South, to Horsham in particular, and April 4 at the Guide Hq., Denne Road. Here the Horsham crowd will be putting on one of their famous

Junk Sales.

Quite some time since last we heard from Fareham, who used to be "regular customers." No worry, though, the boys are still in business on Sunday evenings. We notice they miss Easter Sunday, but on April 9 an informal is taken, and a visiting lecturer is due to be heard on the 16th; a film show and raffle is down for the 23rd and the month ends with David James giving a talk on Colour Television. The place to find them is Portchester Community Centre, and it used to be said that you could locate them by following the feeders to the source!

Radial of the R.A.I.B.C. is one of the monthly treats for your old scribe, and this month is no exception. In particular, the group are particularly pleased over the

Names and Addresses of Club Secretaries Reporting in this issue:

ACTON, BRENTFORD & CHISWICK: W. G. Dyer, 188 Gunnersbury Avenue, London, W3-8LB, A.R.M.S.: N. A. S. Fitch, G3FPK, 40 Eskdale Gardens, Purley,

BEDFORD: J. Bennett, G3FWA, 47 Ibbett Close, Kempston

BEDFORD: J. Bennett, G3FWA, 47 Ibbett Close, Kempston (2427), Bedford.
BISHOPS STORTFORD: E. P. Essery, G3KFE, 17 Ascot Close, Parsonage Lane, Bishops Stortford (2501).
BRIGHTON (Technical College): R. J. Henley, G2CMN, 35 Wilmington Way, Brighton, BN1-8JH, Surrey.
BRITISH RAIL: L. C. Carter, G3ILC, 35 Barnfield Gardens, Kingston-upon-Thames, KT2-5RH, Surrey.
BURY & ROSSENDALE: F. S. Barnett, G3RSM, 13 Rhiwlas Drive, Bury (061-764 7554), Lancs.
CHELTENHAM: E. Janes, G2FWA, Hillside, Bushcombe Lane, Woodmancote, Cheltenham (Bishops Cleeve 2229), Glos.

CHILTERN: P. J. Perkins, G3OUV, Loakes House, Loakes Park, High Wycombe, Bucks. (High Wycombe 0494 21612). CORNISH: J. Farrar, G3UCQ, Elm Cottage, Ventonleague, Hayle, Cornwall.

COVENTRY: C. Jaynes, 20 Belgrave Road, Wyken, Coventry, CV2-5AY.

CRAY VALLEY: P. F. Vella, G3WVP, 78 Hurst Road, Sidcup, Kent

CV2-5AY
CRAY VALLEY: P. F. Vella, G3WVP, 78 Hurst Road, Sidcup, Kent.
CRYSTAL PALACE: G. M. C. Stone, G3FZL, 11 Liphook Crescent, London, SE23-3BN. (01-699 6940.)
DONCASTER (College of Technology): R. Lane, G4AWU, Post Office, Scrooby Road, Bircotes, Nr. Doncaster, Yorkshire.
DUNSTABLE DOWNS: C. G. Powell, G8BPK, 1 Wenwell Drive, Buckland Wharf, Aston Clinton (600), Aylesbury. ECHELFORD: R. Hewes, G3TDR, 24 Brightside Avenue, Laleham-on-Thames, Surrey (Staines 56513.)
EDGWARE: A. J. Masson, G3PSP, 62 Coldharbour Lane, Bushey, Herts, WD2-3NY.
FAREHAM: G. Bulleyment, G3XIV, 42 The Fairway, Portchester, Farcham, Hants.
GLENROTHES: E. H. Ross, GM2LWS, 24 Ettrick Way, Glenrothes, Fife, KY6 IJL.
GOVT. COMMS. H.Q.: E. Fowles, G3PEO, GCHQ, D/CI, Oakley, Priors Road, Cheltenham, Glos.
GUILDFORD: P. Hopwood, G8CQM, 27 Woodruff Avenue, Burpham, Guildford (68929), Surrey.
HARLOW: V. W. Heard, 106 Vicarage Wood, Harlow, Essex. HARROGATE: R. Troughton, G4AZJ, 2 King James Road, Knaresborough (3494), HG5-8EB, Yorkshire.
HARROW: R. H. Medcraft, G3JVM, 134 Dulverton Road, Ruislip Manor, Ruislip (38726), HA4-9AG, Middlesex.
HEREFORD: S. Jesson, 181 Kings Acre Road, Hereford (3237).
HORSHAM: R. J. Polley, G3PYC, 81 Beech Road, Hull,

HULL: Mrs. M. Longson, 4 Chester Road, Wold Road, Hull,

HULL: Mrs. M. Longson, 4 Chester Road, Wold Road, Hull, East Yorkshire.
INVERNESS: L. G. Bell, 114 Glenurquhart Road, Inverness. LOUGHBOROUGH: G. Stoppard, G3XAZ, 67 Loweswater Drive, Loughborough.
MANCHESTER: A. B. Langfield, G3IOA, 201 St. Mary's Road, Moston, Manchester Mi0-0BN. (061-681 5406.)
MID-CHESHIRE: A. Greenwood, G3SIQ, 83 Ash Road, Cuddington, Northwich, Cheshire.
MIDLAND: N. Gutteridge, G8BHE, 68 Max Road, Quinton, Birmingham, 32. (021-422 9787.)

MID-SUSSEX: E. J. Letts, G3RXJ, 87 Meadow Lane, Burgess

Hill (3552), Sussex.
MID-WARWICKSHIRE: A. C. Outhwaite, 2 St. Annes Close,

MID-WARWICKSHIRE: A. C. Outhwaite, 2 St. Annes Close, Leamington Spa, Warwickshire.
NEWARK: P. Scragg, G3YCT, 38 Northwood Gardens, Southwell (2377), Notts.
NORTH BUCKS: P. Harman, G3WXO, 9 Calverton Road, Stony Stratford (3346), Wolverton, Bucks.
NORTH DEVON: H. G. Hughes, G4CG, Crinnis, High Wall, Sticklepath, Barnstaple, North Devon.
NORTHERN HEIGHTS: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax (44329), Yorkshire.
NORTH KENT: M. Lee, G8EJH, 46 Harman Drive, Sidcup, Kent.

NORTH KENT: M. Lee, G8EJH, 46 Harman Drive, Sidcup, Kent.
OTLEY: H. S. Johnstone, 12 Rumple Croft, Newall Carr, Otley, LS21-2RE, Yorkshire.
PLYMOUTH: S. E. Martin, 32 East Park Avenue, Mutley, Plymouth, PL4-6PF, South Devon.
PORT TALBOT: A. C. Williams, GW5VX, 14 Holland Street, Port Talbot, Glam., South Wales.
PURLEY: A. Frost, G3FTQ, 62 Gonville Road, Thornton Heath, Surrey, CR4-6DB.
R.A.I.B.C.: Mrs. F. Woolley, G3LWY, Woodclose, Penselwood, Wincanton, Somerset.
REIGATE: D. Thom, G3NKS, La Collinette, 6 Bracken Close, Copthorne (2/65), Crawley, Sussex.
SALTASH: 1. C. Aldridge, G4AJU, 302 St. Peters Road, Manadon, Plymouth, PL5-3DU.
SHEFFORD: A. Sullivan, G2DGF, 12 Glebe Road, Letchworth, Herts.

Herts. SLADE: J. E. Drakeley, 186 Conway Road, Chelmsley Wood,

Birmingham, 37.
SOLIHULL: A. W. Bagley, G3XPY, 266 Warwick Road, Olton, Solihull, Warwickshire.
SOUTH BIRMINGHAM: R. J. Thompson, 23 Fox Hill, Selly

Oak, Birmingham 29. SOUTHDOWN: A. Seabrook, G3ZQB, 6 Harebeating Gardens.

SOUTHDOWN: A. Seabrook, G3ZQB, 6 Harebeating Gardens, Hailsham, Sussex.
 SOUTHGATE: J. Batchelor, G3XMV, 22 Faversham Avenue, Bush Hill Park, Enfield, Middx.
 SOUTH MANCHESTER: D. Holland, G3WFT, 7 Alcester Road, Sale, Cheshire, M33-3GW.
 SPALDING: R. Harrison, G3VPR, 38 Park Avenue, Spalding, Lines., PEII-1QX.
 SURREY: S. A. MOZIE, SURREY: S. A. MOZIE, A. Bellerby, G3ZYE, A. The Construction of the property of th

Surrey. (657 3258.)
THORNTON CLEVELEYS: R. Bellerby, G3ZYE, 4 The Cop, Rossall School, Fleetwood, Lancs.
TORBAY: Mrs. G. L. Western, G3NQD, 10 Truro Avenue, Torquay, South Devon.
VERULAM: H. Young, G3YHY, 93 Leaford Crescent, Watford,

VERULÂM: H. Young, G3YHY, 93 Leaford Crescent, Watford, WD2-5JQ.
WEST OF SCOTLAND: V. T. Budas, GM3VTB, 28 Kelvinside Gardens, Glasgow, G20-6BB.
WIRRAL: A. Fisher, G3WSD, 34 Glenmore Road, Oxton, Birkenhead, Cheshire. (051-652 5078.)
WOLVERHAMPTON: J. P. H. Burden, G3UBX, 28 Coalway Road, Wolverhampton, WV3-7LX.
WORCESTER: B. A. Jones, G8ASO, 12 Woodside Road, Larkhill, Worcester (29208), WR2-4NU.
YEOVIL: D. McLean, G3NOF, 9 Cedar Grove, Yeovil.
YORK: J. Rainbow, G8BOK, 14 Temple Road, Bishopthorpe, York, YO2-1QN.

achievement of member Esther Thomas who, totally reliant on the Possum self-help equipment, has managed to pass R.A.E.; Esther will shortly be appearing on Two with a G8/3 call, but the target is a G4. When you hear of such an achievement, it makes you wonder how much the people who moan about it being too hard to get a ticket really want to get on the air. Our congratulations must be added to those of the R.A.I.B.C. members who helped her on the way.

Over at Edgware they have meetings on the second and fourth Mondays of every month, at St. Georges Hall, 51 Flower Lane, Mill Hill. April 10 is the Constructor's Contest, and the 24th an Informal Evening.

One of the more comprehensively-equipped groups is Mid-Warwickshire, with meeting-room, library, workshop, and Club station, all at 28 Hamilton Terrace, Leamington Spa. They normally congregate every Monday, but April 3, being Easter Monday, is scrubbed, leaving April 10 for a demonstration of Amateur TV, the 17th for an "open" and 24th for a Film Show.

Spalding seem, to judge by the potted history in the current *Newsletter*, to have had a pretty chequered history in the last seven years or so; but also one gets the impression that now the group is on a far sounder footing than its members would believe! If you are within striking distance, you should get in touch with G3VPR (as in Secretaries Panel) who will advise you where the meeting is—they rotate around members' houses each month. However, the next date is April 21.

Doubtless many people at Crawley are looking forward as far as May 5, the annual dinner date; but the main meeting is on April 26, when K.W. Electronics will be discussing Receiver design. As usual, the venue is Trinity Congregational Church Hall, Ifield, Crawley.

At Harrow the gang are taking a chance for April—weather permitting, they are going to run "a mobile ramble to a venue to be announced," to quote the programme. Thus, your immediate point of contact is the hon. secretary, G3JVM—see Panel. Incidentally, the date for the ramble is April 7.

The Hq. of the North Kent group is the Congregational Church Hall, Chapel Road, Bexleyheath. April 13 is a Junk Sale and on April 27, they will welcome Geoff. Stone, G3FZL, to talk about "Developments at VHF/UHF."

Up North again now, to **Doncaster College of Technology**, where they get together in the Refectory, between 1900 and 2100 every Monday evening. Any one interested in either becoming a member or just dropping by for a visit, will be very welcome indeed, says the hon. secretary, G4AWU.

The A.G.M. for Reigate comes up on April 5; this will be held at the Nutley Hall, Nutley Lane in Reigate. As for the informal, well now, you have first to find the "Marquis of Granby" in Redhill, and then pay a visit on April 19.

This old scribe is reaching for his gun! The Secretary of Thornton Cleveleys, G3ZYE, says the venue for his Club meetings on April 5 and 19, is "the same as before." A scratch back through the March issue shows this to be the St. John Ambulance Brigade Hq., Fleetwood Road North, Thornton Cleveleys. Oh, and he omitted to give his address, too—lucky we have a file for reference! Will all hon. secs. please take note: It is most important



The Club Station of Mosley Electronics, Ltd., Norwich, signs G4ANT, which is also the callsign of the East Anglian Contest Group, operated from the Mosley works premises at Rackheath Airfield. In this picture are, from left to right, G3JOC of Mosley Electronics, G3IOR (seated) and G3MPN, operating, The gear consists of SB-102 into SB-220 and FL-200 driving a 2/813 linear, or SB-301/SB-401 into SB-200. The antennae are, of course, a variety of Mosley types, on a good site for take-off, at heights up to 100ft.

that all the data are *in your letter*, as otherwise it would take three times longer to put the piece together, to say nothing of the possibility of error.

At Bedford, the "Dolphin," in the Broadway, is Hq. Here, on April 6, G3RFG will be reminiscing under the title "From Arc to Spark to SSB." Digital Frequency metering is the subject chosen by G3UQR for April 13, while on the 20th G4AAA is in charge of "Vic's Van of Goodies." That leaves April 27, and on this date they are going to have a discussion on their experiences with TVI.

Cheltenham RSGB group is one of four Clubs in the town. They have their Spring junk sale in April—the date is the 6th but the place is not stated, so it will be necessary to contact G2FWA for details. See Panel opposite.

A late change is notified from Chiltern, reversing the dates of the format lecture and the informal; this means that on April 5 they have the natter-session, so that April 26 is the date for G6CJ and his famous Aerial lecture—this is one not to be missed, the more so as Dud does it so rarely since he moved down to Dorset. This being the case, the meeting is being thrown open to visitors for the night, and any parties from other Clubs who might care to attend—but one would think it would be a courtesy to advise them in advance by way of a line to the Secretary, G3OUV, as Panel.

Usually A.R.M.S. report in by sending us a copy of their *Mobile News* but this time (due to production difficulties) G3FPK decided to write himself and tot up the various advantages for a mobile-minded amateur

SHORT CLUB NOTICES

CLUB NAME	HEADQUARTERS LOCATION	MEETING DAY MONTHLY
Cornish	SWEB Clubroom, Pool, Camborne	April 6 (AGM)
Coventry	Scout Hq., St. Nicholas Street, Radford Road	Fridays
Cray Valley	Congregational Church Hall, Eltham, London, S.E.9	April 6 (AGM), 20
Glenrothes	Old Nursery Bldgs., Leslie, Fife	1st Sunday
Guildford	Model Engineering Hq., Stoke Park	April 14 (AGM), 28
Harrogate	Scriven Women's Institute	April 17, 24 (AGM)
Huli	592 Hessle Road, Hull	Fridays
Mid-Cheshire	Winsford Verdin School, Grange Lane, Winsford	Wednesdays
Northern Heights	The Peat Pitts Inn, Ogden, Halifax	April 12 (AGM), 19, 26
Shefford	Church Hall, Ampthill Road	Thursdays (not 6th)
Slade	Church House, High Street, Erdington, Birmingham 23	April 7, 21
Solihull	Manor House, High Street Malt Shovel, High Street	April 18 April 4
South Manchester	Sale Moor Community Centre, Norris Road, Sale	Fridays
Surrey R.C.	Swan & Sugarloaf, South Croydon	April 18 (AGM)
Torbay	Bath Lane, Torquay	April 29 (AGM)
Yeovil	Youth Centre, 31 Park Lodge	Thursdays
York	British Legion, 61 Micklegate	Thursdays

N.B.—In each case, Secretary's name and address appears in Panel, p.112.

or SWL of joining the Amateur Radio Mobile Society. For example, there is a Club station, call G4AMS; there is the monthly Mobile News; and the information service, which exists to help members deal, for instance, with the suppression of their cars and other special problems that can confront the mobileer, including getting /M permits overseas. This mentions only a few—for the rest, why not talk to the hon. secretary—see Panel—about joining?

A very sad thing has happened to the Wirral group. Their store at the C.D. Hq. was burgled, and they have lost their petrol generator and mains distribution apparatus, among other things—but worse still is the fact that the signs are the thief could have been a member. To mention their dates, there is a change of arrangements, to make the meetings fall on April 12 and 26, so there will not be anything doing on the 5th or 19th. This is to avoid missing a session at Easter.

Saltash next, where they welcome visitors, and anyone within travelling distance, on the first and third Fridays in every month, at Burraton Toc H. We do not have any

details on the current programme; try G4AJU, as Panel.

At Mid-Sussex they have a film of Apollo 11 on April 6, which should draw in the crowds; and on April 20, stimulated by all the techniques shown on the film, they will take, and judge, the entries for the Construction Contest. Both these are at Marle Place, Leylands Road, Burgess Hill.

At Worcester an experiment is going on with the idea of running Monday-evening sessions, in addition to the Saturday ones, and first indications are, as one would expect, that Monday is more popular. For April the Monday meeting on the 10th is a visit to the local telephone exchange and therefore limited in numbers. For the Saturday meeting, April 15, there is a constructional contest. All the "home" dates are taken at the Crown Hotel in Broad Street, where the Commercial Room is separated from the bars and is available from 1930 so speakers can get cracking sharp at 8.0 p.m.

Nice to hear again from North Devon—they are still getting together at the QTH of G4CG, so it would be advisable to contact him first, both as a courtesy and also to find out how to get there—it would be quite hard to find did you not have the directions.

Hereford have recently held their A.G.M. which probably means the secretary is chasing round quite frantically for lectures and such. But by the time this is coming to be read, he will be "all sewn up" on programme matters. More details, and the venue, can be obtained by reference to the address in the Panel, p.112.

For West of Scotland the Wednesday evening sessions are aimed at R.A.E. and constructional work, but on Fridays there is usually a talk or film show or whatever laid on for the attendance of, on average, 45 members. However, we can't tell you what is on in April, as the Secretary has not mentioned it that far ahead. So either you must go to a meeting if you already have a note of the venue, or get in touch with GM3VTB, as Panel.

It must be a tough job, being hon. sec. of **British Rail** club—the second in succession has had to give up his commitment on account of ill-health! Quite seriously, though, it *is* demanding, and we are sorry to hear it has happened again. G3ILC has now taken on the job.

Loughborough is a sizeable town and it supports a goodly crop of amateurs and SWL's, in the form of the local club. The Hq. is at Bleach Yard, Wards End, in Loughborough, where they assemble every Friday evening at 8.0 p.m. As for the programme, April 7 is a film or slide night; the 14th an SWL's Question and Answer Forum; the 21st sees them putting the Club 144 MHz gear on the air; and the 28th is the AGM.

Conclusion

Our production schedule has been totally disrupted due to the working-out of a printers' dispute and this situation may last some time. Though we give normal forward closing dates, in fact we ask for reports as early as possible so as to help us get the *Magazine* out somewhere near on time.

As for next month, your letters should carry the story for May meetings, and arrive by first post April 7, addressed to "Club Secretary," SHORT WAVE MAGAZINE, BUCKINGHAM, and not, please not, to 55 Victoria Street just on the deadline! Till then, 73.

NEW OTH'S

This space is available for the publication of the addresses of all holders of new U.K. callsigns, as issued, or changes of address of transmitters already licensed. All addresses published here will be reprinted in the U.K. section of the quarterly supplements to the "RADIO AMATEUR CALL BOOK" in preparation. QTH's are inserted as they are received, up to the limit of the space allowance each month. Please write clearly and address on a separate slip to QTH Section.

- DA2XF, F. J. Hayward (*G4ABA*), 20 Armd. Bde., HQ & Sig. Sqdn., B.F.P.O.41.
- DA2XG, J. McGuire (G3LNW), c/o Sgts' Mess, R.A.F. Gutersloh, B.F.P.O.47.
- G3DYB, T. L. Davies, Forge Lane, Norton-in-Hales, Market Drayton, Salop. (*Tel. Norton-in-Hales 266.*) (*re-issue*).
- G3IGC, A. Garford (ex-D2GC), 110 Foxdenton Lane, Chadderton, Lancs. (Tel. 061-652 5576.) (re-issue).
- G3WKC/A, J. W. Birkbeck, 96 Newhaven Road, Warrington, Lancs.
- G3ZQL, S. Murray (GW3ZQL),7 Osborne Road, New Brighton,Wallasey, Cheshire.
- G4ACJ, H. J. R. Reeve, 53 Kenwood Drive, Beckenham, Kent.
- G4AIV, D. Scotney (ex-G8BKD), 9 Spencer Street, Rothwell, Kettering, Northants. (Tel. 0536 710519.)
- G4AUQ, F. W. Barker, 13 Marsdale, Sutton Park, Kingston-upon-Hull, Yorkshire, HU7 4AJ.
- G4AUT, J. Wynn, 18 Moorfield Crescent, Lowton, Warrington, Lancs.
- G4AVF, A. Fletcher (ex-G8BWL), 221 Coalshaw Green Road, Chadderton, Oldham, Lancs.
- G4AWM, D. W. E. Norfolk, 190 Whitton Avenue, Greenford, Middlesex.
- G4AWS, A. J. Foster, 16 Parkside Drive, Watford, Herts.
- G4AWU, R. Lane, Post Office, Scrooby Road, Bircotes, Doncaster, Yorkshire.
- GM4AXE, J. R. Trowsdale, 6 Abbotsford Place, Ferryhill, Aberdeen, AB1 2SG.
- G4AXP, G. K. Clode, 25 Penfold Drive, Countesthorpe, Leics.
- G4AXQ, E. J. Boyle, 48 Biggin Hill, Norwood, London, SE19, 3HY.
- G4AXS, P. Wilberforce, L.D.S., R.C.S.(Eng.), F.L.S., L.I.Biol., Little Yaffles, Womenswold, Canterbury, Kent. (*Tel. Barham* 362.)
- G4AXX, M. Marsden, 343 Wanstead Park Road, Ilford, Essex. (Tel. 01-554 9457.)

- G4AYH, G. Monks (ex-G8ENL), 83 Scotland Way, Horsforth, Leeds, Yorkshire.
- G4AYU, N. Kenyon (ex-G8EEH) 39 Mayfield Avenue, Clitheroe, Lancs.
- GI8FQB, Amateur Radio Club (GI3LLQ), The Queen's University of Belfast, 37 Fitzwilliam Street, Belfast, BT9 6AW.
- G8FQM, J. Groom, 2 Oakwood Crescent, Winchmore Hill, London, N.21. (Tel. 01-360 1760.)
- G8FQP, B. P. Keeble, 6 Heathway, Woodford Green, Essex.
- G8FRM, E. A. Johnson, 34 Morthen Road, Wickersley, Rotherham, Yorkshire. (*Tel. Wickersley 2624*.)
- G8FSL, A. D. S. Benham, 15 South Lodge Drive, Southgate, London, N14 4XD. (*Tel. 01-360 5221*.)
- G8FSO, D. J. Lockwood, 7 Northfield Road, Sharlston Common, Wakefield, Yorkshire, WF4 1AG. (Tel. Crofton 862458.)
- G8FSO/A, D. J. Lockwood, Amateur Radio Society, Normanton Grammar School, Church Lane, Normanton, Yorkshire. (Tel. Normanton 2322.)
- G8FVI, C. C. Reeves, 7 Baronsmede Court, Baronsmede, Ealing, London, W5 4LN.
- G8FVU, G. E. J. Bloomfield, 11 Boyden Close, Wickhambrook, Bury St. Edmunds, Suffolk. (*Tel. Wickhambrook 557*.)
- G8FVZ, J. Haig, 30 Bedford Street, Hitchin, Herts. (Tel. Hitchin 53097.)
- G8FWU, T. R. Yates, 26 Birchill Avenue, Wombourne, Staffs., WV5 0DR.
- GM8FWY, P. Russell, 69 Silverbank Gardens, Banchory, Kincardineshire.

CHANGE OF ADDRESS

- G3ASJ, T. G. Kelsey, The Chalet, 33 Chandos Road, Newbury, Berks. (Tel. Newbury 4886.)
- G3AVN, P. Parker, 27 Colbourne Road, Hove, Sussex, BN3 1TA.
- G3FIU, W. B. Gray (ex-G13FIU), 20 Vesey Road, Sutton Coldfield, Warks.

- GM3FZG, A. Treanor (ex-G3FZG),19 Meadows Avenue, Campbeltown, Argyll.
- G3JBA, G. H. Maddox, 13 Cecil Aldin Drive, Tilehurst, Reading, Berks., RG3 6YP.
- G3LNW, J. McGuire (*DA2XG*), c/o Sgts' Mess, R.A.F. Gutersloh, B.F.P.O.47.
- GW3MSY, A. C. Davies, 10 Camden Crescent, Brecon. (Tel. Brecon 3798.)
- G3NUG, E. N. Cheadle, Black Warren, 27 Shenley Hill, Radlett, Herts. (Tel. Radlett 4435.)
- G3OQC, J. W. Woods (ex-VSIMA | VS6FA|9M4MA|DL5ZH), c/o Officers' Mess, R.A.F. Benson, Oxfordshire.
- G3SDW, K. J. Underwood, 29 Hare Street Springs, Harlow, Essex.
- G3TNY, K. J. Spooner, Wilrose, Main Road, Hevingham, Norwich, Norfolk, NOR.04-Y.
- G3UKV, M. I. Vincent, 10 Wood-house Road, Broseley, Salop.
- G3UQX, P. D. Johnson, 42 Nicholas Drive, Ratby, Leicester.
- G3VMB, A. W. Cooper, 409 London Road, Appleton, Warrington, Lancs.
- G3VOY, A. R. Fortnum, Decca Transmitting Station, 5531 Stadtkyll, West Germany.
- G3XDD, S. C. Crampton (ex-G13XDD), 1 Church Road, Roffey, Horsham, Sussex, RH121RF.
- G3XLS, T. J. Williams, 3 Idenwood Close, Rainham, Kent.
- G3ZOJ, B. D. Corper, 60 John Wilson Street, Woolwich, London, S.E.18.
- G4ABA, F. J. Hayward (*DA2XF*), 20 Armd. Bde., HQ and Sig. Sqdn., B.F.P.O.41.
- G4AJM, B. Smith, 20 MunHaven Close, Mundesley, Norwich, Norfolk, NOR.33-Y.
- G6JK, H. J. Sherry, 72 D'Urbeville Drive, Swanage, Dorset.
- G8EVU, K. D. Howe, 64 Barnstaple Road, Thorpe Bay, Essex.

AMENDMENT

G3ARD, F. V. Bellamy, 13 Oakley Drive, Spalding, Lincs., PE112BN (postal code). Member of Amateur Radio Retailers Association

TAURUS ELECTRICAL SERVICES

(Prop.: G3TED) All prices include carriage

SPECIAL	OFFER.	Ferric	Chloride	Powder	for	printed
circuit e	tching. Fu	II instru	ctions. I I	b. bag, 40	p;3	bags, £l

CIRCUIT BREAKERS. Small 5\alpha or 10\alpha	50p
SMALL RECTIFIER BRIDGES. 60PIV 2a	250
FIELD TELEPHONES. Tele "F" each £4; pair &	300
DC MULTIPLIER UNITS for CT54, V-Voltmeter	
SMALL CONTROL BOXES with Lamp, etc. Bargain	25p
TRANSISTORS ACT20. New 25p or 5 for i	:1.00
U.H.F. DUMMY LOAD 7715 with Cavity Capacitance Unit	
and position indicator. Few at	5.00
RF INDICATOR 7150. Complete with I amp RF Meter	
with Loading Resistors. 50 watt with coax connections.	
	5 - 00
CARBON DUMMY LOADS (165 Ω). 2 in parallel, OK for	.5.00
	1.00
RTTY	
ALL CREED EQUIPMENT AND PAPER	
ADVERTISED PREVIOUSLY STILL AVAILABLE	
AMERICAN VALVE TERMINAL UNITS, TAI82/U.	
110v. A.C. Drawing-in-lid, neat	9.00
TELE TYPE KLEINSCH MIDT TT98B /FG. Good condition	
TELE THE KLEINSCHAFED I 1908/FG. Good condition	
Teleprinters, neat looking. $115/230v$. AC 50 or 60Ω .	
184 watts max £2	7.00
12ft, FOLDING AERIALS, NEW	75 p
SMALL 4ft. FOLDING AERIALS	50p
AIRCRAFT MACH METERS, NEW	80 p
AIRCRAFT AIRSPEED SWITCHES, NEW	70p
	1.00
TANK TO BE STORY	75p
ROLLER INDUCTORS, New	/ 3 p
NEW VARIABLE CONDENSERS (BOXEC). Spindle	
both ends, two types :	
both ends, two types: 74PF + 74PF, 750y, D.C. (Polar type 015)	75p
both ends, two types: 74PF + 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012)	75p 50p
both ends, two types: 74PF + 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012)	
both ends, two types: 74PF + 74PF. 750v. D.C. (Polar type 015)	
both ends, two types: 74PF + 74PF, 750v, D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS, 28v, D.C. in 250v, D.C. at 06 out. Will run off 12v, giving approx. 150v.	50p
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out.	
both ends, two types: 74PF + 74PF. 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 14 amps.	50p
both ends, two types: 74PF - 750v, D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS, 28v, D.C. in 250v, D.C. at 06 out, Will run off 12v, giving approx. 150v, out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00	50p
both ends, two types: 74PF - 750v, D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS, 28v, D.C. in 250v, D.C. at 06 out, Will run off 12v, giving approx. 150v, out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00	75 p doz.
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle	75p doz. 20p
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle	75 p doz.
both ends, two types: 74PF + 74PF - 750v, D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS, 28v, D.C. in 250v, D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1 amps. 18p each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power fulls	75p doz. 20p 50p
both ends, two types: 74PF - 74PF. 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) 102PF Single (Polar type 012) 102PF Single (Polar type 012) 1250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. 180v. out. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std. 180 each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8—1 ratio std.	75p doz. 20p 50p 55p
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at '06 out. Will run off 12v. giving approx. 150v. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2-00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New 6CL6's. Tested	75p doz. 20p 50p 55p 55p
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New 6CL6's. Tested 6L6's. Ruggardised New	75p doz. 20p 50p 55p 55p 80p
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 13 amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New 6Clo's. Tested 616's. Ruggardised. New TELEPHONE HANDSETS each	75p doz. 20p 50p 55p 55p 80p 40p
both ends, two types: 74PF - 74PF. 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New 6CL6's. Tested 6L6's. Ruggardised. New TELEPHONE HANDSETS each	75p doz. 20p 50p 55p 55p 80p
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at ·06 out. Will run off 12v. giving approx. 150v. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 13 amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New 6C16's. Tested 616's. Ruggardised. New TELEPHONE HANDSETS each E180CC valves METERS.	75p doz. 20p 50p 55p 80p 40p 25p
both ends, two types: 74PF - 74PF. 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New 6CL6's. Tested 6L6's. Ruggardised. New TELEPHONE HANDSETS each	75p doz. 20p 50p 55p 55p 80p 40p
both ends, two types: 74PF - 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full, SPECIAL OFFER of QQV03-10's. Tested New 6CL6's. Tested 6L6's. Ruggardised. New TELEPHONE HANDSETS each EIBOCC valves METERS 24" round 50-0-50 Microamp Meters	75p doz. 20p 50p 55p 80p 40p 25p 80p
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. Out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 13 amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New 6CL6's. Tested 16's. Ruggardised. New TELEPHONE HANDSETS Each E180CC valves METERS 23'" round 50-0-50 Microamp Meters SPEAKERS—New. 13" 40Ω	75p doz. 20p 50p 55p 80p 40p 25p 80p 35p
both ends, two types: 74PF - 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at '06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full, SPECIAL OFFER of QQV03-10's. Tested New 6CL6's. Tested 616's. Ruggardised. New TELEPHONE HANDSETS each E180CC valves METERS 2½" round 50-0-50 Microamp Meters SPEAKERS—New. 1½" 40Ω BY100's. Tested 15p ea. £1.50	75p doz. 20p 55p 55p 80p 25p 80p 35p doz.
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at ·06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2·00 EPICYCLIC SLOW MOTION DRIVES. 8–1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03–10's. Tested New 6CL6's. Tested 16.6's. Ruggardised. New 16.6's. Ruggardised. New 16.6's. Ruggardised. New TELEPHONE HANDSETS EB0CC valves METERS. 2½" round 50-0-50 Microamp Meters 2½" round 50-0-50 Microamp Meters SPEAKERS—New 1½" 40Ω 15p ea. £1-50 144 Kc/S. TRANSCEIVERS. Less valves	75p doz. 20p 55p 55p 80p 40p 25p 80p 35p doz.
both ends, two types: 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at ·06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2·00 EPICYCLIC SLOW MOTION DRIVES. 8–1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03–10's. Tested New 6CL6's. Tested 16.6's. Ruggardised. New 16.6's. Ruggardised. New 16.6's. Ruggardised. New TELEPHONE HANDSETS EB0CC valves METERS. 2½" round 50-0-50 Microamp Meters 2½" round 50-0-50 Microamp Meters SPEAKERS—New 1½" 40Ω 15p ea. £1-50 144 Kc/S. TRANSCEIVERS. Less valves	75p doz. 20p 55p 55p 40p 25p 80p 35p doz. 3.00
both ends, two types: 74PF - 74PF. 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) 102PF Single (Polar type 012) 102PF Single (Polar type 012) 1050v. D.C. at 06 out. Will run off 12v. giving approx. 150v. Out. 100	75p doz. 20p 50p 55p 80p 25p 80p 35p doz. 3.00 2.20
both ends, two types: 74PF - 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full. SPECIAL OFFER of QQV03-10's. Tested 0.66's. Ruggardised. New TELEPHONE HANDSETS each E180CC valves METERS 2½" round 50-0-50 Microamp Meters SPEAKERS—New. 1½" 40Ω BY100's. Tested 144 Kc/S. TRANSCEIVERS. Less valves With valves (15) TRANS. CALL UNITS (mains intercoms.) Complete MARGIN DISTORTION TEST SETS. In new condition	75p doz. 20p 55p 55p 80p 40p 25p doz. 3.00 2.20 with
both ends, two types: 74PF - 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New &CL6's. Tested 6.6's. Ruggardised. New ETELECTORE HANDSETS BETERS. Deve. 14" 40Ω BY 100's. Tested 15p ea. £1.50 14K Kc/S. TRANSCEIVERS. Less valves With valves (15) TRANS. CALL UNITS (mains intercoms.) Complete MARGIN DISTORTION TEST SETS. In new condition handbook. Delivered	75p doz. 20p 55pp 55pp 80p 40p 25p doz. 3.00 2.20 3.00 2.50 3.00 2.50 3.00 3.00 3.00 3.00 3.00 3.00 3.00 3
both ends, two types: 74PF - 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRANSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full SPECIAL OFFER of QQV03-10's. Tested New &CL6's. Tested 6.6's. Ruggardised. New ETELECTORE HANDSETS BETERS. Deve. 14" 40Ω BY 100's. Tested 15p ea. £1.50 14K Kc/S. TRANSCEIVERS. Less valves With valves (15) TRANS. CALL UNITS (mains intercoms.) Complete MARGIN DISTORTION TEST SETS. In new condition handbook. Delivered	75p doz. 20p 55pp 55pp 80p 40p 25p doz. 3.00 2.20 3.00 2.50 3.00 2.50 3.00 3.00 3.00 3.00 3.00 3.00 3.00 3
both ends, two types: 74PF - 74PF - 750v. D.C. (Polar type 015) 102PF Single (Polar type 012) MINIATURE ROTARY TRÂNSFORMERS. 28v. D.C. in 250v. D.C. at 06 out. Will run off 12v. giving approx. 150v. out. MIN. DIODE EQUIV. IN4007. 1,000 PIV at 1½ amps. 18p each or £2.00 EPICYCLIC SLOW MOTION DRIVES. 8-1 ratio std. spindle MAINS SMALL MOTORS. 1 REV/HR. Power full. SPECIAL OFFER of QQV03-10's. Tested 0.66's. Ruggardised. New TELEPHONE HANDSETS each E180CC valves METERS 2½" round 50-0-50 Microamp Meters SPEAKERS—New. 1½" 40Ω BY100's. Tested 144 Kc/S. TRANSCEIVERS. Less valves With valves (15) TRANS. CALL UNITS (mains intercoms.) Complete MARGIN DISTORTION TEST SETS. In new condition	75p doz. 20p 55pp 55pp 80p 40p 25p doz. 3.00 2.20 3.00 2.50 3.00 2.50 3.00 3.00 3.00 3.00 3.00 3.00 3.00 3

G3XKF

ALANDO

G3XKF

COMPRESSOR - AMPLIFIER

Add Gain and Punch to your signal.

5 transistor, P.P.3 Battery for instant operation as previously advertised. £11-25 + 25p P. & P.

MINITENNA COMMUNICATIONS
8 PEBBLEMOOR, EDLESBOROUGH,
DUNSTABLE, BEDS. (EATON BRAY 297)

LOW NOISE 2 METRE CONVERTERS. £10:50 each.

2 METRE PRE-AMPS. £4.50 each.

E & E SERVICES

(Formerly G. R. GRIGG)

72 ELMSTONE ROAD, RAINHAM, KENT.

SCA 63982 DERWEN	T RADIO SCA 65996
SHOWROOM, 5 COLUMBU KW Atlanta VFO £32.00	S RAVINE, SCARBOROUGH Trio TS510 transceiver £180.00 Trio SP5D speaker £4.00
Wightraps, pair £2.50	Trio SP5D speaker £4.00
Wightraps, pair £2-50 Wightraps hi power £3-50 Hallicrafters SX 133 £145-00	
Yaesu FT101 £240-00	G Whip basemount £1.50
Yaesu FT101 £240-00 Yaesu FT40! £215-00 Yaesu FL400 £140-00	Halson mobile whip £7.50
Yaesu FR400 £140-00 Yaesu FR400dx £120-00 Yaesu FR400S £160-00 Yaesu FT200 and p.s.u £172-00	Unica UNR 30 rx £14.75
Yaesu FR4005 £160•00 Yaesu FT200 and p.s.u £172•00	Halson extra coils £4.40
5P 400 speaker £10.00	250 ohm carbon pot 25p
Miniature transistor choke 5p	PGSP Callbook 50n
Car radio tuner. variable L 15p Panel mains neon 10p	Eddystone ECI0 Mk. II £74.00 ECI0 mains psu £7.75
Panel mains neon IOp	Silver mica, mixed bag 20p
Mains rocker sw with neon 20p	Ceramic capacitors mix 20p Wirewound resistors, mix 50p
Microswitch 5p	Diecast hoves from 80n
2 pushbutton w/change	Adcola Invader Iron £1-70 Sentinel 2m Conv £13-75 Sentinel 70 cm. Conv £13-75
switch 10p Trimmers 10-140pf 2p	Sentinel 70 cm. Conv £13-75 Codar 12/RC £2-50
Trimmers 4-40pf 3p	Lafavette HA600 £45.00
240v. a.c. relay, double c/o 30p 4 digit impulse counter 30p	Lafayette HA800 £57.00 Jackson 25 pfd variable 22p
4 digit impulse counter 30p OC18 type heat sink 5½" 5p OC71 type heat sink 2p Mains slide switch 10p 10 crystals. Our selection	Jackson 25 pfd variable 22p TTC 5 band RF meter £4.00
Mains slide switch 10p	TTC s.w.r. bridge £7.20
10 crystals. Our selection 80p 500 micro/a meter, round 60p	Amphenol PL259 ptfe 30p Amphenol SO 239 25p
500 micro/a meter, round 60p Small dc motor, 12v 40p Roller coaster, 5½" 75p	Amphenol reducers 5p
	Amphenol SO239A ptfe 30p RCA 6LQ6 £2.60
6 b.a. bolts, one type or	RCA 6GK6 95p "J" Beam 2m halo £1-30
6 b.a. bolts, one type or mix. 18p per 100. £1 per 1,000 In-line fuse holders 2p	"J" Beam 2m halo £1•30 Shure 201 £5•50
Resistor *W AD	Shure 444 £14.00
Chokes 10H 50 m/a 20p Xtals 38-888 75p	Acos Mic 45 £1·10 Magazine binders 72p
Mosfets 3NI40 3NI41	Valve and Transistor Data 75p
MPF 102 2 N 3819 40p	Guide to B/cast Stations 50p 2ft. telescopic aerial 35p
OC170 AC187 AC188 25p BF180 37p	All RCA publications in stock:
BC109 2N706 10p	Rx valve manual £1-25
Transistor equivalent manual 40p	Transistor servicing £1.70
Tested transistor ccts 40p	Hobby cets, manual £1.05
Transistor ccts. manual 15p Transistor ccts. for	
_ beginners 40p	I.C. applications £1.30
Radio servicing for amateurs 20p	I.C. applications £1-30 Potentiometers. Brand new. Pack of 10
Trio JR599 £185.00	different, 40p, post paid 24v. relays 10p
Trio 9R59DS £47.00	100 microA meters £1.00
Trio JR500Se £65-00 Trio JR310 £77-00	Powelin panels 9" v 7" 3n
We are still looking for any qua Servicing" and will pay cash or acc to Tamworth or Leeds rally.	ntity of Newnes "Radio and TV
Servicing" and will pay cash or acc	ept as trade-in. Bring them along
to Tamworth or Leeds rally. Wanted: We are always pleased t ment and are looking for good K particular. We can offer cash, or 1 Trio JR\$300s £35.00 Trio JR\$31mint £62.00 Trio JR\$13mint £62.00 Codar PR30X £37.00 Labgear EG300 £30.00 Centrels bectronics 100v.	o hear about your trade-in equip-
ment and are looking for good K particular. We can offer cash, or i	radio equipment in part exchange.
Trio JR500Se £55.00	Eddystone 840A £35.00
Trio JR 310 mint £65.00	Hamgear PM2 £7.00
Codar PR30X £7.00	TEI5 GDO £10.00 AR88 Mains can £2.00
Central Electronics 100v.	HRO gangs £2.00
Edd.,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,	Heath RF Sig. Gen £10.00
Vanguard hihand . £25.00	Heath Audio Sig. Gen. £10.00 Eddystone 830/2 £200.00
Trio TS500 & p.s.u £125.00 Trio VFO-5 £18.00	National NC109 £35-00
Trto 9R59DS £40.00	AR88LF (Rough) £20.00
LATEST: Plastic strip pockets to wall display. One strip 3n. 10 strip	o take 12 QSL cards for vertical os 25p. Postage 6p. PR59D. All parts including I MHz e add extra for carriage. S.A.E. lists.
Complete calibrator kit for Trio	R59D. All parts including I MHz
crystal and valve, 64. Pleas 28 Hillcrest Avenue,	Scarborough, Yorks.
To Filliciest Avelue,	Jean Borough, Torks.





Whatever your age or experience you must read New Opportunities. It describes the easiest way to pass A.M.S.E., A.M.I.M.I., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering Mechanics, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book. Send for your copy today—FREE!

B.I.E.T., B30, Aldermaston Court, Reading, RG7 4PF

Accredited by the Council for the

Accreditation of Correspondence Colleges

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

SOLID STATE MODULES

63 WOODHEAD ROAD, SOLID, LOCKWOOD, HUDDERSFIELD, HD4 6ER

Telephone: Huddersfield 23991

Telephone: Huddersfield 23991

MANUFACTURERS AND SUPPLIERS OF COMMUNICATIONS EQUIPMENT

AND NOW NEW—The Sentinel Extra 2 metre Dual Gate MOSFET converter. We have been producing our Sentinel VHF converter for over three years now. In this time we have made thousands of them, not all of course, for the amateur bands. Following extensive development work combined with the knowledge we have gained particularly from the production of converters and pre-amps for special applications we have arrived at the Sentinal Extra converter. The spec. remains basically the same as our Sentinel I (we couldn't improve it that much) which continues in production as ever. The main areas of improvement are MOSFET burn out protection, If breakthrough, presentation and spurious signal reception and optional internal AC supply. Noise figure 2 dB. Gain 30 dB. Size 5° x 1½" front panel, 4" deep. If you don't have the internal P.S.U. it can be easily added. If from stock NOW 28-30 MHz. Other IF's maybe but we can't promise to a week or two. Price £16-50 less mains P.S.U. £19-50 including P.S.U.

THE SENTINEL DUAL GATE MOSFET2 METRE CONVERTER

The Sentinel Extra described above is not replacing this standard converter which is still frequently described to us as "the best one around."

★ Low noise figure 2 dB.

★ Gain 30 dB.

★ Dual gate MOSFETs in the RF amplifier and mixer for excellent overload and cross modulation characteristics.

★ Size only 2½* × 3" × 1¾* aluminium case—silver hammer finish with black trim.

★ Stock iFs: 2-4 MHz, 4-6 MHz, 9-11 MHz, 14-16 MHz, 18-20 MHz, 23-23 MHz, 24-26 MHz, 27-29 7 MHz, 28-30 MHz.

★ Price: £13-75.

THE SENTINEL LOW NOISE FET 2 METRE PRE-AMPLIFIER

★ Low noise figure 1 dB.

★ Gain 1 dB.

★ Have you noticed how many of these are being used with Commercial Base stations and mobiles. "It makes all the difference between not hearing a signal and being able to work him 1"

★ Size: matching our Sentinel standard converters. Price: £6:50.

Also in stock:— ★ SM70 70 cms converter, £13·75.

★ SM/0 /0 cms converter, £13-75.

★ Spitfire 2 metre A.M. transmitter, £22. Matching modulator, £10.

★ KVG 9 MHz filters and crystals.

★ Plessey SL600 series IC's.

★ Range of Yaesu Musen amateur gear.

★ Secondhand guaranteed gear.

We believe that all equipment and components advertised will be in stock as you read this, but you can always ring for confirmation.

THE AMATEUR RADIO SHOP

G4MH

13 Chapel Hill, Huddersfield. Tel: 20774

Yaesu

K.W.		Trio			Musen		
	CO.1.O.			****			
Atlanta		TS510		£180	-FT10	וכ	. £240
2000B	£240	JR599		£199	FT2	00	. £134
204 TX	£145	JR310		£84	AC	PSU	£38
202 RX	£140	9R59DS		£47·50	FT4) [. £215
107 ATU	£40	(Top Bar	nd a	vailable J			
2 Metres:	The 4MH						£11.50
	S.S.M. Co.						£13.75
	S.S.M. Pre						£6.50
	4MH 70 C	M C		•••	•••		
	411H /0 C	I'I Conve	rter	• • • • • • • • • • • • • • • • • • • •	• • •	•••	£7·80
	J.	Beams,	xtals	, etc.			
	Morse "	Prectice"	, Os	cillator, 9	Юp		

SECOND-HAND

			0110	-11711				
Eddystone EA	2. Mi	nt			•••			£145
Trio TS510 and	ı p.s.u.	Mint					1	£160
KW 2000 + p	.s.u				• • •	•••	1	EI IO
FR 200B Tx.	• • •	•••	•••	•••	• • •	• • •	•••	£75
KW Vespa II		•••	•••	•••				£90
9R59DS	• • •	•••	•••			• • •		£38
AR88D	-::	•••	•••	• • •				£40
JR310 + CW			•••	•••		•••		£70
Eddystone 940		• • •	•••	•••			• • •	£95
JR310 + Cal a	nd 160			• • •		•••		£75

C.U. AT THE WHITE ROSE AND NORTH MIDLANDS RALLIES. Wanted Rx's and Tx's

S.A.E. for any gen. Carriage extra on all items. HP arranged. Full service facilities.

CLOSED TUESDAYS. LATE OPENING THURSDAYS

FREE CAR PARK

TRANSLATION SERVICE-S.A.E. Details

Interested in Leasing your equipment over 4/5 years and keeping up to date?

Write or get your dealer to write to:

G8KA

General Merchandise Credit Ltd.,

Cranbrook. Kent.

Minimum package deal £200. H.P. Terms over 3 years also.

G3EKX S.S.B. PRODUCTS G3EKX

PAIR MATCHED 6HF5's R.C.A (20p)	£5.50
PAIR MATCHED 6146 R.C.A (20p)	
PAIR MATCHED 6146B R.C.A (20p)	£6.20
2 METRE 5 element wide spaced BEAM with [-2½"	
masthead bracket. Only (80p)	£2.50
NEW XTALS. All metal types. Mixed, not ex-govt. 80 kc/s. to 110 Mc/s. "State your requirements."	
S.A.E. essential (5p)	
R.C.A. ROTARY RELAYS. 12v. I/P.D.C. superb job.	
Ideal for aerial switching (15p)	ea. 55p
EDDYCTONE FOR ME A	
EDDYSTONE ECIO Mk. 2. Latest EDDYSTONE 935 speaker, £3-71 A.C. mains unit 924	
EDD 1310RE 333 speaker, 23.71 A.C. mains unit 324	£7.75
	£170-00
TRIO JR310. Superb ham bands Rx	
TRIO 9R59DS. Latest general coverage Rx	£57.50
TRIO SP5D. Speaker	£4-37
CLASS "D" W/METERS. Few left (80p)	£5.00
CLASS "D" W/METERS. Few left (80p) CLASS "D" 240v. A.C. I/P. Few (80p)	
CLASS D 2404.A.C. I/F. 164 (00p)	E10.30
DELTA. Complete aerial switching. Tx/Rx Control	
Unit. Ready made (25p)	£8 · 50
USED GEAR	
PYE REPORTER. 4 metre Mobile Transmitter/Receiver. 12v. 1/P. with manual (£1)	£10.75
· · · · · · · · · · · · · · · · · · ·	F10-13
COLLINS TCS. Transmitter 1.5 to 12 Mc. Fully	
converted. (Less power unit)	
SX100. Excellent condition	£95.00
VICEROY Mk. 2 (£1.50)	£65.00
H.R.O. 9 coils	

7 LITTLE CASTLE STREET, TRURO Tel. DEVORAN 862575 CORNWALL

SOME RECOMMENDED TITLES BRIEFLY DESCRIBED

BEGINNER'S GUIDE TO RADIO

For many years "Beginner's Guide to Radio" has been extremely popular as an introduction to the subject of radio-and-how-it-works. The many advances made in recent times have rendered a new edition neces-

many advances made in recent times have tended to a new sary. This seventh edition has been completely rewritten and brought up-to-date to take account of the latest techniques and methods, and covers every aspect of the modern radio scene, while including the important basic information necessary for the newcomer to the subject. The reader is guided from the first principles of electricity and magnetism, through radio waves, modulation and radio components, including valves and transistors, taking in radio transm.tters and stereo broadcasting, and ending with hi-fi reproduction.

The book will be of interest to all who wish to understand the how-and-why of radio, whether it be for a hobby or a profession.

Seventh Edition

£1.12 post free

49 EASY TRANSISTOR PROJECTS

This book is for the electronic hobbyist who is interested in developing projects that can be fun as well as useful. Most projects can be constructed in one evening using only a few inexpensive parts. Many of the parts can be salvaged from old radio and television chassis. Each project is presented in an easy-to-understand way, with a parts list and a schematic diagram. Many value substitutions can be made in resistors and capacitors without affecting the end result, providing that the proper transistors, coils, and transformers are used. Projects in this book, which include an AM radio, an FM receiver, light relay controls, audio ampliflers, code practice oscillators and test equipment—each designed with only two transistor types.

£1.01 post free

110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR

Integrated circuits are the most important new semiconductor devices to have been developed within the past decade. They are compact, casy to use and less expensive than their discreet transistor-resistor equivalents. This volume gives an entirely practical introduction to these devices by describing one hundred and ten constructional projects in which they can be used.

The projects range from simple low-level amplifiers to complex test equipment and include a number of hi-fi circuits and logic circuits. The integrated circuits used are internationally available types and all the projects have been designed, built and fully evaluated. The book should prove to be of practical interest to the professional engineer, the student and the amateur.

£1.22 post free

110 SEMICONDUCTOR PROJECTS

Due to the rapid advances in semiconductor technology, many engineers and certainly most amateurs have found it impossible to keep tract of the new devices that become available because of lack of readable information. This book introduces the reader to such outstandingly useful new devices at the field-effect transistors, unijunction transistors, silicon controlled-rectifiers, silicon planar transistors and integrated circuits, giving their properties and methods of operation, with full constructional details of many exceptionally useful circuits.

Of particular interest to the amateur are simple amplifiers, lamp and relay driving circuits, electronic switches—operated by light, sound or contact with water—and delay circuits ranging from a fraction of a second to 35 minutes. Among the many circuits which will be of interest to the practising engineer are amplifipers with input impedances as high as 500 megohms, voltage and current regulators, waveform generators, analogue-to-digital converters and logic circuits. All circuits are designed around internationally available semiconductors.

124 pages, including 110 illustrations

£1.37 post free

RADIO AMATEUR OPERATOR'S HANDBOOK

The opportunity has been taken of bringing this edition—the twelfth—right up-to-date and of incorporating extensive revisions. The book covers in detail the Post Office regulations governing the issue of transmitting licences.

The purpose of this Handbook is to provide all the information which the operator of a radio station may need about such matters as Country Prefixes, Call Sign Areas, Frequency Allocations, Standar Frequency Transmissions, Time Factors, Distance Tables, and so on. For the newcomer, this manual enables him to find the basic answers and to obtain the maximum pleasure from his hobby.

53p post free

HAMS INTERPRETER

This valuable book written by DLICU contains a collection of phrases and expressions designed to assist those amateurs who wish to enlarge their knowledge of various languages for use on amateur radio—It is a must for every DX'er.

63p post free

PRACTICAL INTEGRATED CIRCUITS

PRACTICAL INTEGRATED CIRCUITS

This is the first British book to be published on micro-electronics for the amateur experimenter. With circuit diagrams, layouts and easy instructions, it shows how construction to the properties of the construction and worthwhile equipment.

£1.01 post free

HANDBOOK OF TRANSISTOR CIRCUITS By Allan Lytel

By Allan Lytel

Here is a collection of more than 200 practical transistorised circuits for use in counters, power controls, timers, indicators, photoelectric devices, power regulators, amplifiers, power supplies, oscillators, power converters, and other applications. Schematic diagrams, parts lists and descriptions of operation are included for each circuit.

Planned as a supplement and companion volume to author Lytel's previous book, Transistor Circuit Manual, many of the circuits employ such specialised semi-conductor devices as silicon-controlled rectifiers, photocells, zener diodes, and tunnel diodes, in addition to standard diodes and transistors.

This book is a handy source of information on the design, operation, and application of a wide variety of transistorised circuits. Engineers, technicians, students, and hobbyists will all find the circuits of interest and the material of value in research, development, experiment, and general studies of circuitry.

£2.35 post free

PRACTICAL WIRELESS CIRCUITS

PRACTICAL WIRELESS CIRCUITS

There are more than 50 different circuits detailed in this book. Transistor receivers, 22 in all, range from an ultra-simple crystal diode circuit to a very sophisticated I0-transistor communications Rx. Valve receivers cover every sophisticated I0-transistor and valve amplifiers include preaming the receiver circuits for Model Control. Circuits for notes that the receiver circuits for Model Control. Circuits for an extensive range of Test Gear cover everything from a simple Transistor Tester to a Comprehensive Multimeter, including a Pocket Signal Tracer (RF, AF and IF), also FM, Square-Wave and Noise Generators.

Among the special circuits are a recording level meter for tape recorders, an electronic photographic timer and a solar cell receiver. The first few simple circuits are a recompanied by step-by-step instructions to enable the absolute beginner to gain enough experience with circuitry building to tackle the more complicated work.

SHORT WAVE MAGAZINE

£1.34 post free

Some of the Books described here are American in origin

The above prices include postage & packing.

Delivery is from stock.

Available from

Publications Dept., 55 Victoria St., London S.W.1

01-222 5341

(Counter Service, 9.30-5.15, Mon. to Fri.)

(Nearest Station: St. James's Park)

(GIRO AIC, No. 547 6151)

AMERICAN TITLES FROM FOULSHAM-SAMS

ABC's of ANTENNAS

The introductory chapters cover the fundamentals of radiowave propagation and basic antenna characteristics. The remainder of the book is then devoted to a discussion of the various types of antennas and their uses. Antennas for radio, television and two-way communications are included. Business radio, amateur, both mobile and fixed-station operation, are covered. The final chapter should be particularly appealing to those interested in microwave uses and radio-navigational systems. A perusal of this book will provide any student with an excellent foundation for more advanced study in antenna design

89p

ABC's OF SHORT-WAVE LISTENING

Have you ever listened to a radio and thought how enjoyable it would be to hear broadcasts from faraway places, such as Toronto, Berlin, and Tokyo, as well as signals from ships at sea and satellites in space. All these broadcasts can be at your fingertips, offering a

in space. All these proadcasts call be as your linearing hobby.

ABC's of Short-Wave Listening a non-technical guide, will help you get started, or give you added pointers if you are now engaged in this hobby. The mysterles of radio waves are revealed in a manner that anyone can understand, providing priceless knowledge about the ever-expanding world of short-wave radio.

£1.02

AMATEUR RADIO SSB GUIDE

Single-sideband receivers, transmitters, and transceivers are now Single-sideband receivers, transmitters, and transceivers are now available which have higher frequency stability and are much easier to tune than the early models. In this book, the author presents a guide to single-sideband and single-sideband equipment, which will be useful to any amateur considering or already operating SSB. £1.59

By W6TYH

AMATEUR RADIO CONSTRUCTION PROJECTS

Amateur radio is a rewarding and enjoyable hobby. For many hams the greatest thrill comes from constructing and operating their own "home-brew" rigs. There is something about being able to lean back and say, "I built it myself," that isn't engendered by ownership of a commercial unit.

Amateur Radio Construction Projects is a book for every amateur, whether he waster to build all his actionment of just a unit or two

Amateur Radio Construction Projects is a book for every amateur, whether he wants to build all his equipment or just a unit or two to supplement what he already owns. Starting with many helpful construction hints (some of which will benefit the "old-timer"), the book progresses from simple projects to more complicated ones. Each chapter contains a complete circuit description, chassis layout, tuning procedure, and operating instructions, supplemented by schematic and pictorial diagrams and complete parts lists. By W6NJV O/P

BUILDING YOUR AMATEUR RADIO NOVICE STATION

This book is the first "completely detailed" construction manual for building an amateur novice radio station. Nothing is overlooked in building the station from scratch to the actual on-the-air operation. The transmitter and receiver are distinctly professional in per-

formance quality and appearance.

The book is primarily directed to the novice radio ham, it contains many novel and valuable construction hints and tips for amateurs in any licence class. As a finished touch to the projects a complete "rollaway" ham shack for hams with limited space (apartment dwellers, etc.) is featured and fully described.

BY WYOF

By W7OE

£1.57

HAM ANTENNA CONSTRUCTION PROJECTS

Besides full details on many useful and interesting types of aerials, Ham Antenna Construction Projects includes complete information on long-lasting construction methods, as well as how to position your antenna to achieve maximum distance with a given radiation pattern. In addition, much easy-to-understand technical information on tuning antennas and the use of test equipment is presented.

£1.47

PRACTICAL HAM RADIO PROJECTS

The projects described in this book include: all-band 500-watt linear amplifier . 2-metre SSB mixer and linear amplifier all-band 500-watt antenna tuner . electronic automatic keyer . de luxe 6-metre mobile transmitter . universal transistor mobile modulator and power supply . transistor 2-metre superhet receiver . VFO for 6, 2, and 1-25 metres . transistor dip oscillator . 2-metre transceiver for mobile or fixed station . transistor 6-metre handie-talkie . monitor scope for SSB and AM. Just about all that is needed for a complete amateur station!

SWL ANTENNA CONSTRUCTION PROJECTS

Two chapters cover the basic principles of antennae and the knowledge necessary for construction of the projects which are given in the following pages. The antenna projects themselves are divided into six classes. First are the dipole aerials such as segmented and inverted types. Following them are the vertical antennae, including array and beam types. Then horizontal beam segmented and inverted types. Following them are the vertical antennae, including array and beam types. Then horizontal beam systems (Yagls) are considered. Various low- and high-band and multiband triangle antennae are also discussed. The next section deals with long-wire antennae, such as vee beams and rhomblics, for those SWL'ers with a sizeable plot of land available. For SWL'ers without land, indoor antennas, which are included in the final section, may be a solution. Three useful appendices are provided at the end of the book.

TRANSISTOR FUNDAMENTALS Vol. 1

This book is a carefully planned programmed introduction to semiconductors and the basic electrical circults. It begins with a brief description of transistors and later devotes an entire chapter to an explanation of transistor principles. Sandwiched between these chapters are explanations of voltage, current, and resistance; and the all-important Ohm's Law and Kirchhoff's laws. The book also looks at the more complicated nature of inductance, capacitance, and resistance in AC circuits.

£1.92

TRANSISTOR FUNDAMENTALS Vol. 2

This volume describes transistors and how they are used in semi-conductor circuits. Simple circuits illustrate the basic principles involved, and the more complicated circuits found in amplifiers and oscillators help to show how the basic operations are applied. Later, some recent semi-conductor developments are discussed. Details descriptions of four new transistor devices are given and how they are being used.

KNOW YOUR OSCILLOSCOPE By Paul C. Smith

By Paul C. Smith

The oscilloscope provides you with a "third eye" which lets you see what is actually happening in electronic circuits. But you must know something of the nature of this valuable instrument, and how to use it, before it will serve you. This book presents complete information on the circuitry, functions, and applications of the oscilloscope in easy-to-understand language. Worthwhile reading for anyone who uses an oscilloscope . . . a "must" for service technicians and students. technicians and students.

£1.80

The Books described here are American in origin.

The above prices include postage & packing.

Delivery is from stock.

Available from

SHORT WAVE MAGAZINE

Publications Dept., 55 Victoria St., London S.W.1 (Counter Service, 9.30-5.15, Mon. to Fri.)
(GIRO A|C. No. 547 6151)

(Nearest Station: St. James's Park)

AMATEUR **ELECTRONICS**

BIRMINGHAM

021-327 1497 021-327 6313

Despite unforeseen delays the acquisition of our new premises is now finalised and we shall be moving to the new address towards the end of April. Will customers please note that all mail should be addressed to 518/520 Alum Rock Road for the time being and as the new place is located adjacently to the present address there is no chance of post going astray in any event and our 'phone numbers will remain unchanged. We shall continue to specialise in high quality used equipment examples of which we show below, but would remind customers that we have extensive stocks of TRIO, KW and now YAESU MUSEN equipment, all of which is available on demonstration without obligation, in our showroom.

STOP PRESS: We now carry excellent stocks of J. BEAM ANTENNAE.

RCA 8516L RECEIVER. In exceptional condition in all		\ - /	
respects, complete with manual and spare valves £175-00		V	
HEATH HW-101 TRANSCEIVER. Complete with SB-600			
speaker and HP-23A power supply. Mint condition £130.00	HEATHKIT MULT-METER MM-IU.	Factory built	
HEATH SB-500 2 METRE TRANSVERTOR. Again mint £70.00	mint condition		£17.50
GEC RC-410 RECEIVER 2-30 Mc/s. Digital read-out fully	COPAL 222. Digital Clocks		£8.00
synthesised in all modes. 100 c/s read-out. Price on application	COPAL IOI. Digital Clocks		£10.75
REDIFON R50M GENERAL COVERAGE RECEIVER	COPAL 401. Digital Clocks		£13-25
13.5 k/cs. to 32 Mc/s. Excellent condition and superior	SHURE MICROPHONES 201		£5-75
	SHURE MICROPHONES 444		£13-25
EDDYSTONE EA12 RECEIVER. First class condition and	TTC Dynamic PTT Fist Mike		£3·50
performance £150.00	WIGHTRAPS	per pair	£2-65
EDDYSTONE 940 RECEIVER. Similar condition to above £110-00	RCA 6146B	each	£3.05
EDDYSTONE ECIO MARK I RECEIVER. Choice of two,	PL259 UFH Connectors	each	30p
both unmarked and excellent, late models £49.00	ADAPTORS Size	each	10p
EDDYSTONE 840 RECEIVER. Excellent all-round condition £47.50	ADAPTORS Size 2	each	10p
TRIO 9R59DE RECEIVERS. Further sets now to hand in	OSKER SWR POWER METERS		£18.00
unmarked condition £38-50	TTC C3005 SWR/POWER METER		£7 · 40
TRIO JR500 RECEIVER. One only. Condition as new £55-00	TTC C3042 SWR/POWER METER		£4-40
HEATHKIT GR78 GENERAL COVERAGE RECEIVER.	MEDCO FL50A Belling Low Pass		£6.00
Complete brand new kit for assembly. Latest solid state	MEDCO FL75A Belling Low Pass		£6 · 00
model, ex Heathkit and complete with guarantee £60.00	MEDCO FL50B UHF Con. Low Pass		£6·50
HAMMARLUND SP600JX RECEIVER. Very clean con-	MEDCO FL75B UHF Con. Low Pass		£6·50
dition complete with original case and manual £97-50	MEDCO FH40. High Pass		£2-10
SOMMERKAMP FP200, DC PSU. Excellent condition and	Right-angled Plugs	each	65p
very little used £30.00	SO239 Sockets	each	28p
AR88D RECEIVERS. Several in stock or en route from £50.00	Straight Adaptors	each	45p
AR88LF RECEIVERS from £40.00	J-BEAM ANTENNAE. Full range.		
(Fuller details on application)	Full details of these and other Hamgeor items	on request (s.o.e.)	
COLLINS 75-A2 RECEIVER. Fitted Collins NBFM Adaptor.	G-WHIP ANTENNAE. Full range.		
Nice condition £120.00 HEATHKIT RFI-U SIGNAL GENERATOR, Factory built £17.50	Leaflets on both on receipt of your s.a.e.		
HEALHRII RFI-U SIGNAL GENERATOR. Factory built £17.50	HAMGEAR PMIIA. Pre-selector		£9.45
HEATHKIT C-3U RC BRIDGE. Factory built £15.00	HAMGEAR PMIIB. Pre-selector		£8 · 40

PLEASE NOTE: All items listed in this advertisement include carriage or postage.

We carry extensive stocks of components at competitive prices with special discounts available to purchasers who buy in packs of 10. Full details of our Arry extensive stocks of components at competitive prices which special stocks of prices upon request.

CREDIT FACILITIES. We offer first-class credit terms with a deposit on practically all equipments of only 10% with the balance over a period of up to three years. Part exchanges—We welcome these and also buy every conceivable class of equipment outright.

Southern Agents:—J. H. ASSOCIATES Ltd., Cricketfield Lane, Bishop's Stortford, Herts. Telephone: 20279 56347. Telex 81553.

ELECTRON HOUSE, 518-520 ALUM ROCK ROAD, BIRMINGHAM 8

STEPHENS-JAMES TO DRICHY BOAD LIVERBOOK 14 107

G3LRB

The Widest Range of North

* * * * * * *

IN PRIORT ROAD,	LIVERPOOL, L4	ZRZ G3MCN	Equi	pment in the North
Tel: 0!	51-263 7829		+ * *	* * * * * * *
	7. 200 1020			~ ~ ~ ~ ~ ~ ~ ~
Yaesu-Musen	Hy-Gain Antenna Range	Microphones		Codar
FTI01 Transceiver £240	12AVQ 10-15-20m, Vertical £1		£5.75	T28 Receiver £17-50
FT2F 2m Transceiver £84	14VQ/WB 10-15-20-40m.	Shure 444		Codar Receiving Kit £11-50
FT200 Transceiver £172	Vertical £18	8 - 50 Leson TW205A	£7.95	AT5 A.C. P.s.u £11-50
FL500 Transmitter £140	ISAVQ/WB IO through	Sentinel 2m. Converters	£13.75	AT5 Mk, 2 Transmitter £22-50
FR500 Receiver £120/£160	_ 80m £33	3-00 Sentinel 4m. Converters	€13.75	PR40 Preselector £8-50
Remote VFO's £38	TH6DX Tribander Beam £84	4.00 Sentinel 70cm, Converter		71140 F F ESERCECTO, 20-30
SP400 Loudspeaker £10-00	TH3MK3 Tribander Beam £67		413.13	Secondhand Equipment
FL2000B Linear £135	TH3JNR Tribander Beam £46			National NCX5 Mk, 2 £185-00
YD844 Table Microphone £12				Trio TS510 with A.C. P.s.u. £140.00
YD846 Hand Microphone £5-00	LC80Q Loading Coil £4		he full	FL500 Transmitter £100-00
FT401 Transceiver £215		ange of a beam antennae, at	current	FR500 Receiver £110-00
KW Electronics	203BA 20m, 3 Element £66			Sommerkamp FL2000 Linear £100
KW202 Receiver £140	203BA 2011, 3 Element Eoc	6.30		KW200B Transceiver £190.00
KW204 Transmitter £145	G-Whip Antenna Range	Copal		Codar PR30X Preselector £6.00
KW2000B Transceiver £240	160m. Ranger 2 £7	7-50 Copal 222 24 Hour	49.48	Sommerkamp FR500 Rx. £95.00
KW2000B Remote VFO £39-00		9.00 Copal 60 I 24 hour Calendar	£17.00	Heathkit DX100 Tx £30.00
KW Atlanta Transceiver £210		1.50 24 hour Battery Clock.	217-00	Heathkit DX60 Tx £25-90
KW Atlanta VFO £37-00	Coils for LF Bands each £4	4.00 Large	622.00	Collins 755-1 Rx £165-00
KW107 Antenna Matching		1.45 Antenna Rotators		Inoue Tx and Rx £130-00
Unit £40-00		4·20 £20, £25, £	40. £70	Lafavete HA800 Rx £45-00
KW E-Z Match £15.00	Multimobile £12	2-50 Vibroptex Keys	€15.00	Trio JR500 £50 • 00
KW103 SWR/Power Meter £12-50		Semi Automatic Bug Keys	£4.50	Codar "Q" Multiplier £6-00
KW Trap Dipole £12-50	Lafeyette	H7P Balue I	£3.00	Heathkit RGI Rx £20-00
KW Traps per pair £4-50	HA600A Receiver £4!	5.00 Wight Balun	€3 - 25	Trio 9R59DE Rx £35-00
KW Dummy Load 50 ohms £7.00		Wight Traps per pair	€2.50	Sommerkamp FL200 Tx £75-00
KW Balun £1.95	Test Equipment	Dipole T Pieces	13p	·
KW105 Matching Unit £37.00	Tech 15 G.D.O £12	2 · 50 Egg Insulators	3p	Full range of Eddystone die-cast
Trio	TTC3042 SWR Bridge £4	4-25 300 Ohm Twin Feeder		boxes, Stella cabinets, Ali panels
JR599 Receiver £199	OSKER/SWR/Power meter £18	8.00 per yd.	5p	and chassis. Panel meters, plugs.
9R59DS Receiver £57-50		2.50 50 Ohm coaxial cable	•	valves. Full information on all
JR310 Receiver £83-50	TTC1069 Multimeter £14	4-50 per yd.	I2p	products sent on receipt of
SP5D Loudspeaker £4-50		8-50 75 Ohm Twin Feeder		LARGE S.A.E. Return mail
Eddystone	TMLPL436 Multimeter £	7·00 per yd.	7p	order service on all stocked
ECIÓ Mk. 2 Receiver £79.00		3-25 Tunable RF meters	£4-00	items. Orders under 25p respect-
A.C. Power Unit £7.75	Omega Noise Bridge TE701 £13		30p	fully declined.
898 S, M. Drive £8-92	Omega Noise Bridge TE702 £15	9 50 Sockets	30p	,
EB37 Receiver £98-00		7.95 Cable reducers	10p	
Asahi Antenna Range		2.50 Line connectors	90p	Carriage/postage extra, all items.
3 Band 3 Element Beam £60-00		2-40 QQVO-3-20A	£1.75	All RSGB Publications stocked at
40 to 10m. Trapped Vertical £16.50	TE *22D Sig-Gen £15	5-09 QQVO-3-10	75p	current prices.

HP terms arranged on all orders over £25. Minimum deposit 10% on new equipment, 20% on secondhand.

Full demonstration facilities.

MEMBER OF THE AMATEUR RADIO RETAILERS ASSOCIATION Part exchanges welcomed. Equipment bought for cash. After Sales Service. Shop hours 9.30 to I p.m. 2.15 to 6 p.m. Half day is Wednesday

SMALL ADVERTISEMENTS

("SITUATIONS" AND "TRADE"

5p per word, minimum charge £1.00. No series discount. All charges payable with order. Insertions of radio interest only accepted. Add 50% for Bold Face (Heavy Type). Box Numbers 12½p extra. No responsibility accepted for transcription errors. Replies to Box Numbers should be addressed to The Short Wave Magazine, 55 Victoria Street, London, SW1H OHF.

TRADE

G3UTT, Tunbridge Wells now building up stocks of Components for radio amateurs, including J-Beam Aerials, at Teleservice, 136 Camden Road, Tunbridge Wells, Kent.

TAY AT The Cornwall Ham-Radio Holiday Centre. STAY AT The Cornwall Ham-Ramo Hollday Center. Self-catering furnished accommodation. Sixelement beam; 65ft. tower; 90 awards.—Full details from Bernard Broughton, G3XBR, St. Tudy, Bodmin,

QSL Cards and G.P.O. approved log books, hard back. Prompt delivery, stamp or large s.a.e. for samples, please.—Atkinson Bros., Printers, Looe, Cornwall, PL13-1L3.

QSL Cards. Two-colour. Attractive design, variable features, from £3·15 per 1,000 (inclusive). Send foolscap s.a.e. for samples.—A.R.A. Press, 46 Moat Avenue, Green Lane, Coventry.

OSL Cards for Tx and SWL. Send s.a.e. for samples stating which type required.—Beaumont, G5YV, 8 Ashfield Avenue, Morley, Leeds, LS27-0QD.

QSL Cards: for Tx, G8 or SWL. One to four-colour designs; large s.a.e. for samples; good selection.

Red Rose Publicity (Pennington), 34 Aqueduct Street, Preston, Lancs.

MAY Issue: Due out April 28. Single-copy orders 25p, post free, to reach us by Wednesday, April 26, for posting on April 27.—Circulation Dept., Short Wave Magazine Ltd., 16 Victoria Street, London, SW1H-0HF.

OVERNMENT Surplus Wireless Equipment Hand-GOVERNMENT Surplus wireless Equipment light book: Contains circuits, data, illustrations, valuable information on British/U.S.A. receivers, transmitters, transceivers. Includes modifications to sets tost againment. Surplus/commercial crossand test equipment. Surplus/commercial cross-referenced valve and transistor guide. Price £2.85, post/packing 20p.—Myers (B), 112 Stainburn Crescent, Leeds, 17, Yorkshire.

SL Cards and Log Books. Prompt service. Send of lists.—The Wested Press, Old Forge Yard, Swanley Village, Swanley, Kent.

YORK Photo-Audio Centre for Yaesu Musen Transceivers: FT.101 with 160m. coverage, £255. FT.200 with PSU, £172. FT.401, £215. FT.2F, £84. Send 3p for complete lists and details of our Instalment-Credit scheme with virtually no deposit and up to 24 months to pay. We are also stockists of Trio, Codar, Hamgear, etc., etc. and in our Hi-Fi Dept. we have B. & O., Trio, Sinclair Stereo-Sound, all on demonstration. Cameras and equipment considered in Part Exchange.—51 Fossgate, York, Y01-2TF, Tel: 56176 (or 25798 after hours).

SPARES Available for R.C.A. AR88D and AR88LF receivers; send s.a.e. for list.—Reynolds, 5 Headland Way, Lingfield, Surrey.

MARKHAM ELECTRONICS

Technical YAESU TRANSCEIVERS

£225

£35

All ex-stock—delivery free—12 months' guarantee excluding valves and semi-conductors—unbeatable value our prices and H.P. rates are the lowest available.

FT101: Ultra modern complete station—260w. P.E.P. input. Fully transistorised save for driver and P.A. Complete with microphone and built-in speaker

FT200: (Less P.S.U.), 260w. P.E.P. input. All usual operative facilities such as selectable USB/LSB, VOX, 100 kHz calibrator, clarifier ±5 kHz are included. A modern transceiver with YAESU quality. Only £120

FP200: AC power supply and speaker unit for FT200

FTDX400: 560w. P.E.P. input. Similar to FTDX560 but no W.W.V. band and no provision for CW filter. Limited number only £175 ...

FTD X560: 560w. P.E.P. input. W.W.Y. band and provision for installing C.W. filter, selectable USB/LSB, VOX, 25/100 kHz calibrator, clarifier ±5 kHz, ANL and Ac power supply all built-in £180

FTD X401: As FTD X560 plus built-in P.A. cooling fan, C.W. filter and sensational new noise blanker unit £205

FTDX400, FTDX560 and FTDX401 are all variations on the same basic design and represent unbeatable value for a high quality 560w. P.E.P. transceiver with built-in AC P.S.U.

MARKHAM OAK, BUCKS HORN OAK. FARNHAM, SURREY.

Telephone Bentley (Hants) 3168 (evenings)

MI-19467-A MASTER **OSCILLATORS**

These R.C.A. units which are used in the ET 4336 transmitter used in the E1 4330 transmitted and which were supplied as a separate item, each in its own slide-in metal case, are ideal as the heart of any high-power unmodified transmitter, unmodified as a low-power (approx, 20w.) transmitter, or as a basis for modification to suit individual require-



tion to suit individual requirements. They incorporate a 6-position oscillator switch (covering I to 5 MHz); a 3-position Multiplier switch (covering 2 to 10 MHz); a D.C. current meter, and oscillator and multiplier coils with "turns counting" mechanisms for precise tuning. Power requirements are H.T. and L.T. for the 807 valve used in the unit, and are brought in by an 8-pin Jones plug on the rear of the chassis. The basic frequency coverage of the oscillator is I to 10 MHz, which can be extended to 20 MHz when used as the oscillator section of a higher power transwhen used as the oscillator section of a higher power transmitter or when used on its own. All these and many more details are covered in full in the extremely comprehensive instruction/ service manual (supplied with each unit) containing wiring and circuit diagrams, adjustments, photographs, etc. BRAND NEW. Price per unit is £8-50 including 2, 807 valves. Carriage 75p.

COLOMOR ELECTRONICS LTD.

01-743 0899

01-748 8006

170 GOLDHAWK ROAD, LONDON, W.12.

Echelford Communications 11 BROADWAY. KINGSTON ROAD. STAINES, MIDDX.

Telephone: Staines 54401

New items in stock in	clude	:				
KW 2000B Transceiver an	d mains	P.S.U.				£240.00
KW Ezee Match ATU						
KW Trap Dipole		•••	•••	•••		7:7
KW 52 Ω Dummy Load	•••	•••	•••	•••		£7.00
Trio 9R 59DS Receiver	•••	•••		•••		
Tilo 9K 39D3 Receiver	•••	• • • •	• • • •			£4.50
Trio SP5D Speaker						£4.30
Normende Globetrotter	PRO po	ortable	Comi	municat	ions	
Receiver		•••				£97·50
Receiver BSR Record Decks, Stered	Headp	hones,	Speak	er Syst	ems,	
etc.						
Tavasu Mobile Whips an	d Coils	:				
Whip and base with 6ft	. 50 Ω d	oax		(P/P 25	D)	£2.88
Whip, base, adaptor and	1 160m	coil		(P/P 25	ď	£5.95
J-Beam arrays-we are of						
stock. R.S.G.B. Publica						
Second-hand items at						
Complete Codar AT5, T28						ue.
						£50 · 00
in rack, immaculate cor	idition	•••	· · · ·			
Class D Wavemeters, mair						
Codar T28 Receiver, new	conditi	on				
						£15.00
Heathkit RA!		•••				£30.00
KW Vanguard Transmitte	r					£30.00 £29.00
KW Vanguard Transmitte	r				• • •	£30.00 £29.00
KVV Vanguard Transmitte	r				• • •	£30.00 £29.00
R 107 ALL ITEM We shall be attending t	r IS CA! he foll	 RRIAG	 E E>	::: CTRA		£30.00 £29.00 £17.00
R 107 ALL ITEM	r IS CA! he foll	 RRIAG	 E E>	::: CTRA		£30.00 £29.00 £17.00
R 107 ALL ITEM We shall be attending t	r IS CA! he foll April I	 RRIAG owing I 6.	 E E> rallie	 CTRA s and c	onve	£30.00 £29.00 £17.00
RIO7 ALL ITEM We shall be attending t Tamworth— VHF Conve	r IS CA! he follo April I	RRIAG owing 1 6. Whitto	 E E> rallie	 CTRA s and c	onve	£30.00 £29.00 £17.00
R V Vanguard Fransmitte R 107 ALL ITEM We shall be attending t Tamworth— VHF Conve Belle Vue Ra	r IS CA he foll April I ntion, ally—M	RRIAG owing 1 6. Whitto	 E EX rallie n—Ap	 CTRA s and c	onve	£30.00 £29.00 £17.00

Hours of opening Monday-Saturday, 9 a.m.-6 p.m. Half day Thursday (I p.m.)

H.P. terms available on all items over £25 A. G. WHEELER, G3RHF

M. STANSFIELD, G8DNM

G. W. M. RADIO LTD.

MURPHY MARINE SHIP TRANSMITTERS. 1-5 to 16 Mc/s. VFO or crystal. 40 watts RT or CW. Valves P.A. 3 58/254M in parallel, modulation pair 58/254M. Two panel meters. Size 13" x 13" x 14". Complete and clean but not tested. Less power supplies, £11 carriage paid. A few similar Pye units with same line up but 13" x 15" x 14" have calibrated VFO, same price.

AERIAL VARIOMETER TUNERS. Made for 19 set Mk 111. New condition, £1-30, post paid.

REED RELAY inserts, 1-85" long (body length 1-1"). Diameter -14" to switch up to 500ma at up to 250v. D.C. Gold clad contacts, 63p per doz., £2-75 per 100, £27-50 per 1000, post paid.

100 kc/s. crystals, glass envelope on octal base, £1·25, post paid. 2 meter transmitter sub-units. Contain 2 x 6516, 2 x 6064, QV04-7 and TT15 valves, £2, post paid. Pocket Dosimeters, 15p, post paid. Meters 1½ dia. 500 microamps calibrated 0-10, 75p, post paid.

0-1 Milliamp 2½" round meters in desk case, £1.50 post paid.

PORTABLE AERIAL MASTS. Fine quality 48ft. masts by Coubro & Scutton. 2" dia aluminium sections, complete with 16 guys, pickets and all fittings. Unused and in "as new" condition in green canvas carrying bag, £21, carriage paid. Also available Erection Derrick kit containing 3 additional mast sections, ropes and pulleys, etc. to enable mast to be erected by fewer personnel, £5, carriage paid.

HYGROMETERS. Wet and dry bulb type, new, £1.25, post paid.

TRANSFORMERS. Used "C" core, 200-250v. to 230-0-230v. 260ma. 6-3v. 0-6a., 6-3. 6-0a., £2, post paid. Chokes "C" core 10h. 75 ma., \$0p., post paid or 6 for £1-65, post paid. Unused Radiospares "Heavy Duty" 205-245v. to 350-0-350v. 150ma, 6-3v. 2-5a., 6-3 3a., 6-3v. 2a (tapped at 5v. 3-5a), £2, post paid. "Midget Output" \$0p post. Used "C" core 0-115-180-240v. to 0-24-30-32v. 2a., £1-5p, post paid. New Gardner potted 200-250v. to 12-7v. 2-5a., £1, post paid.

Used. 0 - 250v to 800 - 700 - 300 - 200 - 0 - 200 - 300 - 700 - 800v. 800 and 700 at 200ma, 300 at 100ma, 200 at 50ma when used simultaneous) 5v. 2a, 4v. 7a, 64v. 1a. £4 carriage paid.

CAPACITORS, paper, 8uf 400v., 30p, poet paid or 6 for £1.05, post

All Reseivers and Test Equipment are in working order at time of dispatch. Carriage charges quoted are far England and Wales only.

Telephone 34897

Terms: Cash with order

Early closing Wednesday

40-42 PORTLAND ROAD. WORTHING, SUSSEX

READERS ADVERTISEMENTS

2½p per word, minimum charge 50p payable with order. Add 25% for Bold Face (Heavy Type). Please write clearly, using full punctuation and recognised abbreviations. No responsibility accepted for transcription errors. Box Numbers 12 p extra. Replies to Box Numbers should be addressed to The Short Wave Magazine, 55 Victoria Street, London, SW1H OHF.

READERS

WANTED: Hallicrafters SX.17 Rx, or similar, Details and price please.—Smith, 14 Norwood Avenue, Southport, Lancs.

SALE: Trio 9R-59DE, with matching speaker, as new, less than 24hrs. use, £35 or near oner.—Maynard, G3XZJ, QTHR (Tel: Radnage 3047).

FOR SALE: Receivers—Eddystone 840A, continuous coverage 550 kHz to 30 MHz, £30. Eddystone EC-10, two-tone grey cabinet, coverage as 840A, £38. KW-160 Tx, AM/CW Top Band, mains input, £18. All in excellent condition. WANTED: K.W. Vanguard or similar.—Wyse, G3IWE, QTHR, or ring Warrington 64178.

WANTED: Walkie talking

WANTED: Walkie-talkies, matched pair. Full details and price, please.—Box No. 5075, Short Wave Magazine Ltd., 55 Victoria Street, London SW1H-0HF.

SELLING: R.C.A. AR88D, fitted S-meter, with manual and speaker, Joystick aerial and ATU, all perfect condition, £50 or near offer. Trio receiver Model 9R-59, as new, £20. For appointment to view ring Foster, 01-876 7375 (London) or write.—195 Huntingfield Road, Roehampton, London, S.W.15.

SALE: Pye Ranger 2107 ready modified for two metres, with control unit, microphone and crystal, excellent condition, £25 or near offer. CRD AR22 rotator, brand new and unused, bargain, £19.50. Beam, 8/8 slot-fed Yagi for two metres, unused, £5. Delivered London.—Craig, Tel: 01.647 7543, evenings.

SALE: National HRO-MX with eight GC coilpacks and PSU, modified with product detector and Heathkit QPM-1 Q-Multiplier, £15 or EXCHANGE for smaller compact set.—Ring Taylor, Reigate

WANTED: Pye Cambridge (AM10D) radio-telephones, any condition, low band preferred. Also QQV03-10 valves, must be unused.—Austen, 1 Valebridge Road, Burgess Hill (3409), Sussex.

SALE: Heathkit SB-301 receiver with CW filter, D professionally built, £90. KW-500 Linear Amplifier, £40. Both in good condition.—Slater, G3FXB, QTHR, Tel: Brighton 593382.

FOR SALE: Racal RA-17 highly selective receiver, **O 5-30 MHz, in good condition, offers? Seen Edinburgh.—Box No. 5076, Short Wave Magazine Ltd., 55 Victoria Street, London SWIH-0HF.

SELLING: TCS-13 Tx/Rx, CW/AM 160, 80, metres, mains PSU. Prefer buyer collects, £20 or offer. Delivery 30 mile radius.—Harrison, G4ADF, White Cottage, Codmore Hill, Pulborough,

SALE: Army communications receiver, internal speaker, AC mains operated, £11.50 carriage paid, s.a.e. with enquiries.—Hayward, Sunnyfields, Lighthouse Road, St. Margaret's Bay, Dover, Kent.

SELLING: Lafayette 6-metre transceiver, 22 watts, built-in VFO, mic., manual, in good condition, £50 or near offer.—David, 13 Matheson Road, London W.14 (Tel: 01-602 6977).

WANTED: By collector, Burndept "Grecian Vase" Floor Speaker.—Box No. 5077, Short Wave Magazine Ltd., 55 Victoria Street, London SW1H-

OFFERING: EMSAC TU2 ATU, £2·50. Hamgear ATU-Preselector, £3·50. Joystick de-luxe, indoor version, £3·50. One hundred back numbers "Short Wave Magazine," 1963-71, £5 the lot.—Watson, 19 Frances Road, Basingstoke, Hants.

EXCHANGE: Panda PR-120V Tx, complete with ATU, and Labgear Topbander Tx, both with manuals FOR good Zenith Oceanic Rx. Delivery Cheshire or Lancashire, otherwise collect.—Clancy, 12 Craven Terrace, Sale, Cheshire. (Tel: 061-962) 4113.)

RF AMMETERS: Ranges 500 mA, 1 amp., 2·5 amp., 3 amp., 3·5 amp., 4 amp., £1·25 post paid. Also 1 amp., round, £1·50.—Dr. Nicholls, G3ZVZ, Ancoats Hospital, Manchester M4 6EB (Tel: 061·205 2204).

FOR SALE: Creed 7B Teleprinter, (24 volt) with manual, £15. Creed Type 25 five-hole punch, with handbook, £10. Buyer collects.—Weedon, 19 Helmsdale Close, Romford RM1 4RS, Essex. (Tel: Romford

WANTED: By collector, Cossor 41-STH or equivalent; any bright emitter valves; also early type Tx valve about ½ kW.—Box No. 5061, Short Wave Magazine Ltd., 55 Victoria Street, London, SW1H OHF.

SALE: Trio TS-510 transceiver with PSU and speaker, mint condition, £140. Trio JR-599 Rx, coverage 160 to 2 metres, with speaker, mint condition £140. Accept £260 for both.—Shaw, G3XFJ, QTHR, or ring 0904 78857 (York).

FOR SALE: Eddystone EA-12 in immaculate condition, original carton and instruction book, nearest offer £100.—Blake, 18 Trewartha Road, Praa Sands, Penzance, Cornwall.

SELLING: SSB Mini-5 transmitter, all bands, professionally built, £20. Eddystone S.640 receiver, £15.—Ring Williamson, Langley Mill 67089 (Nottingham)

OFFERING: KW-2000A, good condition, £95. Murphy hi-band VHF Base Station and mobile station, £15.—Higginbotham, G3VDS, QTHR, or ring 061-430 6277 (Stockport).

REQUIRED URGENTLY: To complete 25-year N project, 1936 Lissen Hi-Q rotary coil unit.— Litherland, G8CFB, 11 Birch Grove, Chippenham, Wiltshire.

SELLING: Two-metre valve converter, £5. SE.38E Rx with Woden 250/110v. xformer, £4. Mains transformer, new, 6.3/12.6/450v., £2.—Truscott, (Garston 72105), Watford Herts.

SALE: Hammarlund SP-600JX, xtal calibrator, case, phones, handbook, mint, £70. National NC-77C, bandspread, AM/CW/SSB, as new, £27-50. Heathkit HR-10B Amateur Band receiver, AM/CW/SSB, with phones and handbook, mint, £40.—Ring Lane, 706-0557 (Birmingham) 0557 (Birmingham).

0557 (Birmingham).

FILTERS: For SSB, Tx or Rx, 455 kHz, bandwidth

1.8 kHz at 6 dB, hybrid ceramic, £4.75. Also PZT
carrier xtals at 50p. VHF/UHF power transistors, all
new: 2N3866, 2N4427, 65p; 2N3053, 18p; 40290, £1.25;
2N3553, £1.50; 2N3375, £3.75; BF378 low noise amp.
for 23cm, 70cm, NF 3.5 dB at 800 MHz, Ft 2300
MHz, at 70p; 2N5179 UHF multiplier to 1000 MHz,
Ft 1400 MHz, 300 mW, at 55p. All items 5p postage.
Send stamp for list and further data.—Elliott,
G3FMO, Oatlands, Southend Road, Howe Green,
Chelmsford (71604) CM2 7TD, Essex.

WANTED: Collins R389/URR, AN/WRR3, AN/ URR45, SP-600VLF, or other high-class receiver for VLF. Good quality teleprinter, receive-only, considered. T.D.M.S., 6A or other high-class distortion measuring set. Also electronic speed, level, and Morse converters for teleprinter.—Passfield, 30 Greenleaf Close, Tulse Hill, London, S.W.2. (Tel: 01-674 5825).

Portable AM/FM World-Wide Communications Receiver

Another Scoop! **TELETON TF 182** 8 WAVEBAND RECEIVER

List Price £69-75 *OUR PRICE £49-95* ONLY £5*DOWN!

.



The very latest technical improvements in Audio radio reception makes this sensitive world-wide portable 8 waveband AM/FM radio receiver unique. Its sensitivity and exceptional quality performance must be heard to be believed. Listen to the world in the comfort of your home and at a price which makes it a real bargain not to be missed,

JUST LOOK AT THESE SPECIFICATIONS!

8 Wavebands FM/MW/LW. SWI to 5 World Zone map. World Time Dial. Tuning and fine tuning controls and Tuning Indicator Meter. Tape/ Record playback switch, Two built-in Ferrite aerials for LW MW and SWI and 5ft. Telescopic aerial for other bands. Mains or Battery operation. Earphone and mains lead. Facilities for feeding in via the DIN sockets into an Audio Amplifier or Tape Recorder.

List Price £69-75p OUR PRICE £49-95p.* Terms deposit £5-00 followed by 12 payments of £5-00. Total £65-00 P & P 50p.

Limited quantity only - Don't wait SEND £5-50 TODAY.



CRYSTAL CALIBRATOR CC-10-Battery operated solid state using low power integrated circuits to generate I MHz, 500 kHz, 100 kHz, 500 k

WAVEMETER TC-101—Absorption wavemeter covering 0-8-480 MHz in six overlapping ranges with sensitive meter and detector circuit. Insulated probe. Matching style to calibrator. Price: £18-30

FREQUENCY STANDARD SD-II—Provides separate outputs of I MHz and 10 MHz phase locked to Droitwich 200 kHz transmission. Battery operated, solid state with self-contained aerial.

LOW PASS FILTER FL2/FL4-Reduce BC1/TVI, available 50 or 75 ohms. Passband loss less than ½ dB, stopband loss 50 dB ... Price : £6.20

FET CONVERTER FC2/FC4—New design using protected dual gate MOSFET's for low noise and high gain. 4-6 MHz and 28-30 MHz standard IF's but any in range 2-30 MHz to order. Operates from 9 volt DC supply and has reverse polarity protection ... Price: £16-20

TEST OSCILLATOR TO-701—Crystal controlled oscillator in small hand-held case for IF alignment, calibration, etc. Any single frequency 100 kHz to 100 MHz. Battery operated. Quantity 1-4 Price: £10-00 Quantity 5+ Price: £8-90

FM DETECTOR FMD-I—Add on unit using high gain integrated circuit and low distortion discriminator. Any IF in the range 450 kHz to 1 MHz. Supplied in kit form or made and tested.

Kit Price: £6.70 Price : £6.70 Price : £8.20 Made and Tested

Our new 1972 catalogue lists 18 pages of manufactured equipments and a wide range of components, e.g. resistors, capacitors, coil assemblies, transistors, integrated circuits, etc., for most forms of constructional work.

Send 10p for details or cash with order to:

BURNS ELECTRONICS

THE COTTAGE, 35 BEULAH HILL. LONDON, S.E.19.

	Capacitance	Volts	Size	T or W/E	Price
	2 uf	350	$\begin{array}{c} 1\frac{1}{2} \times \frac{1}{2}" \\ 2 \times 1" \end{array}$	Tag.	5p
	8+8+8 uf	275	2 × 1"	Tag.	6р
	16 uf	450	2 x ½" 2½ x "	Tag.	6p
	32 +8 uf	450	2∮ x l″	Tag.!	6p
	32+32+16 uf	275	2 x 13"	Tag.	6p
	50 uf	350	2 x 1"	Tag.	5p
	50 + 80 uf	300	2 x 3 n	Tag.	5p
	64 uf	450	2 x 1 * "	Tag.	8p
	64+16+8 uf	275	2.≩″ x l	Tag.	5p
	100 uf	450	21 √ là″	Tag.	8p
Į	100 + 32 + 32 uf	300	2½ x 18" 4 x 18" 3 x 18"	Tag.	IOp
-	100 + 250 + 10	uf 250	42 137	Tag.	8p
1	200 uf	275	7 O 18"	Tag.	ę,
	200 uf	450	4½ × 13″	Tag.	5p
	300 uf	350	72 X 13	Tag.	8p
	500 uf	100	7 A 18	Tag.	Şp
	500 uf	150	4 × 18" 4 × 18" 3 × 18"	Tag.	5p
	1000 uf	150	3 X 1 T 3 //	Tag.	5p
	1000 ti	150 30	4½ x 1¾"	Tag.	40p
	1000 T 1000 UI	40	3 x l" 3 x l"	Tag.	[2p
	1000 + 1000 uf	18	3 X 1	Tag.	15p
	1500 uf	25	14 × 3" 1½ × 3"	Tag.	10p
	1500 uf	25	1 x 2 / 2 / 2 / 2 / 2 / 2 / 2 / 2 / 2 / 2	₩ 7 E.	12p
i	[500 uf	50	4 × 1 § "	Tag.	12p
	1600 uf	64	3∦ × [¾″	Tag.	25p
	2000 uf	100	4 × 2"	Tag.	45p
	4000 uf	. 15	3 x I"	Tag.	[2p
	4000 uf	100	$4\frac{1}{2} \times 2\frac{1}{2}$ "	Tag.	50p
1	10,000 uf	9	2 × /≩″	Tag.	20p
	10,000 uf	12 25	2 x /≩″	Tag.	25p
1	10,000 uf	25	3₹×14,	lag.	35p
i	10,000 uf	30	3₹ × 1¾″	lag.	40p
	30,000 uf	30	7 x x 1 1 2 2 2 2 2 2 2 2	Tag.	55p
		Thro's 500 v w	2nf 10nf 15nf		30 pf 1000 pf

older-in Feed Thro's 500 v.w., 2pf, 10pf, 15pf, 18pf, 22pf, 30pf, 1000pf All at 15p per doz.

Wide Range VHF TUNING VARACTOR DIODES with a Q of up to a 100 at a 100 MHz approx. capacitance at 4 volt 80pf, 8 volt 57pf, 30 volt 40pf at 20p each.

1000 PIV 800 mA Plastic SILICON DIODES, 12p each. 200 PIV I Amp Plastic SILICON DIODES at 6p each. MULLARD BFW 10 VHF FET 25p each, 5 for £1.

300 MHz divide by 2 COUNTERS with Data at 60p each. 2GHZ Dual Transistors in 8 Lead TO 5 can untested with data, 4 for £1.

J. BIRKETT

Radio Component Suppliers, 25 THE STRAIT, LINCOLN Telephone: 20767

The NEW SAMSON ETM-3 SQUEEZE - KEYER

With SQUEEZE-KEYING you make such characters as C, Q, Y, F, L, AR, SK, etc. with fewer paddle movements.

◆ 4 Integrated circuits 6 transistors, 2 diodes. ◆ Use double-paddle for either Squeeze-keying or normal fully-automatic electronic keying as preferred. ◆ Built-in PSU. ◆ Constant I: 3 dash-dot ratio. ◆ Weight only 2½ lbs.

RETAINS the star features of the WELL-KNOWN SAMSON ETM-2 —used by coast stations and big ships all over the world :-

● Watchmaker-assembled keying-lever movement. ● Silent reed relay (400v., IA contacts). ● Sidetone. ● TUNE button. BETTER EVEN THAN THE ETM-2—GET YOURS NOW! £24.75 post paid U.K.

. . . and still going strong :-

SAMSON ETM-2 electronic keyer, £21 (£22.20 with mercury

SAMSON STA Speaker/Amplifier, for ETM-2/ETM-3, £2.75.

JUNKER PRECISION HAND KEY. Superb German straight Key made for professionals afloat and ashore. Free-standing—needs no fixing to desk. Hinged grey dust cover. Front and back contacts with click-stop gap adjustment. Key-click filter, £8-95.

BAUER KEYING LEVER AND PADDLE UNIT—for your own El-Bug. Compact enough to build in. Gaps/tensions adjustable NEW PRICE, £2-75.

MODEL TTU RTTY CONVERTER/KEYER—All-in-one-box instant send-receive RTTY with a TX/RX and cheap surplus teleprinter, £115.

SSB 90° PHASE SHIFT NETWORK UNITS.

All items post-paid U.K. Catalogue SP5 describes these and other RTTY, VHF, SSB kits and units.

SPACEMARK LTD. 14 PICCADILLY, MANCHESTER I.

14 PICCADILLY, (Tel.: 061-237 0817) SELLING: KW-2000B, with AC and DC supplies and Shure 201 mic., £180.—Ba power £180.—Ballance, G3KNB, QTHR, or ring Stafford 62105.

WANTED: Short wave receiver, Eddystone preferred. Age, condition, immaterial if complete. Cash, or exchange new radio/TV Hi-Fi equipment. -Snowden, Swainsea Lane, Pickering, Yorkshire.

CLEARANCE: Class-D wavemeter, phones and manual, modified for mains working, £7. R.1475 Rx, coverage 2-20 MHz, with PSU, excellent condition, £8. Rf field indicator FL-30HA, tuning 1-150 MHz, £1·50. PCR3 Rx, rough condition, £4. Valves, new or good condition: QQV06-40A, 80p; QQV03-10, 25p; E38CC, 25p; OA2, 10p. Crystals, 3rd. overtone, HC/6U: 46·7 MHz, 44·3 MHz, 30p; 2mm 38·334 MHz, 30p; FT243, 8·1 MHz 10p. VHF/UHF manuals, 80p. Also odds and ends.—Dunhill, 16 Fernleigh Close, Blackpool, Lancs.

WANTED: HRO with or without coils or PSU; even non-worker or scrap. Coils and manual also required.—de la Bertauche, G3RCO, QTHR, or ring Seaton 21016.

WANTED: Manuals for the following Wireless Sets: Nos. 17, 18, 19, 22, 38 (AFV and Packset), 46, 48, 62, 58, 68, ZC-1. R.A.F. R.1155-T1154, TR-9, German W.W.II radio/radar tubes, etc., and manuals. Please state price, postage will be refunded upon purchase.—Grogan, Apt. 5, 5235 King Arthur's Court, Roanoke 24019, Virginia, U.S.A.

SELLING: Top Band Command receiver with 12v. PSU, £4·50. B.44 with new crystal for 70·26 MHz, £7. Pye 2m. Base receiver, £5. All plus carriage. WANTED: 2m. converter.—Warner, 44 Thorndale Avenue, Larne, Co. Antrim, Northern Ireland.

EXCHANGE: Hamgear Preselector for a Joystick and tuner. Also for EXCHANGE, a Stavely S/C Tx/Rx, servo, with two actuators (unopened), 46in. power boat kit, also 40in. aircraft kit, all in mint condition (cost £45). FOR Good Rx, Eddystone, Trio, etc.—Ring Pallatt, Hemel Hempstead 54239.

FOR SALE: BC-639A, £7. R.208, no cabinet. £1. R.206 Mk. II (rough), £10. HRO (not working) but with nine GC collpacks, £7. Buyers collect. WANTED: Late model KW-77 Rx with matching speaker; R.216 with PSU, £50-£40 offered respectively.—Everall, 36 Eleanor Road, Waltham Cross, Herts.

SALE: AR-10 rotator with thrust-bearing, drive shaft adaptor, approx. 40ft. 4-core cable and two-metre 4/over/4 beam, £16·50. Prefer buyer collects, after 6 p.m. or weekends.—Baker, 65 Crompton Street, Chelmsford, Essex, CM1 3BW.

WANTED: Faulty CR-100 or B.28 receiver. Any vi condition acceptable, even incomplete, please state price, anywhere.—Bentley, 27 De Vere Gardens, Ilford, Essex. (Tel: 01-554 6631 evenings).

SALE: Trio JR-500SE with 160m. coverage, calibrator bandback mind tor, handbook, mint condition, £50. Delivered Securicor.—Howard, G8ANU, 60 Brocton Road, Milford, Stafford (62533).

FOR SALE: Hamgear P.M. II Preselector, mains operated, fabulous condition, no more than 10 hours' use, complete with operating instructions. An absolute bargain at £5.50 or near offer. Carriage extra if necessary.—Cross, 64 Semley Road, Norbury, London SW16 4PJ. (Tel: 01-679 3215 after 60 nm)

WANTED: Creed 75RP or 75. Any reasonable price paid. Details and price.—McElvenny, 7Q7JO, 15 Havelock Square, Sheffield S10 2FQ, Yorkshire.

SELLING: Reluctantly, Trio 9R-59DS, owing severe local electrical interference. Purchased new last September; receipt shown. Fitted stabiliser, with original carton and instruction manual, immaculate, £30.—Williams, 3 St. Mark's Road, Windsor, Berks.

SELLING: SB-500 Two-metre transverter, 28 MHz, 240v., newly assembled, but requires alignment, £65. KW-2000A, new, £150 or near offer. TT/L-2 RTTY terminal unit, 3-channel filters, 2/BP filters, 850/170 Hz shifts, autostart, for rack mounting, hammer grey panel, professional finish, £110.—Addie, G8LT, Spring Hill, Wappenham, Towcester, Northants. (Tel: 032-732 321.)

WANTED: Central Electronics 200V, 100V or Collins KWS-1. Details and price.—McElvenny, 7Q7JO, 15 Havelock Square, Sheffield, S10 2FQ, Yorkshire.

DISPOSAL: FT-DX100B Model, with built-in VOX, one 10-metre section, AC/DC, spent most of its life in original packing, £165 or near offer. New Sanyo stereo FM/AM car radio with twin speakers, £48. National stereo FM/AM radio and cassette recorder, AC/Battery, £67.—Barry, 47 Gerald Road, Wollaston, Stourbridge, Worcs.

SALE: Trio JR-599 Custom Special Rx, complete with operating and service manuals, original packing, price £145, carriage and insurance paid.—Hutchinson, G3VGH, 78 Strensall Road, Huntington, York 703 9SH. (Tel: York 769245.)

FOR SALE: Eddystone EC-10 Mk. II receiver, only 9 months old, in perfect condition, complete with crystal calibrator, £65 (carriage paid), or near offer.—Edgecock, G8DFR. 1 High Street North, West Mersea, Colchester, Essex.

OVER 950 Radio Magazines, 1935 onwards, many complete years "Amateur Wireless," "Wireless World," "Radio Constructor," "Short Wave Magazine," "Practical Wireless," "Practical Television," RSGB "Bulletin," etc. Must clear. Best offer takes the lot.—Box No. 5079, Short Wave Magazine Ltd., 55 Victoria Street, London, SW1H-0HF.

WANTED: Collins, mint and guaranteed as new, 312B-5 PTO, good price paid. Also Collins 516F-2 PSU power transformer, part No. 662-0249. Interested any mint condition Collins equipment. Details and price, please.—Box No. 5078, Short Wave Magazine Ltd., 55 Victoria Street, London, SW1H-0HF.


SALE: Pye "Ranger" AM, working near 4 metres, £10. T.W. two-metre converter, 6BQ7A RF, 28-30 MHz IF, less PSU, £4. Cowl-gill motor, £2. Minimitter converter for 10-80 metres, IF 1-6 MHz, £4.—Chaloner, G3VSJ, QTHR, or ring 01-360 5452 (London).

WANTED: High-grade general coverage valve-type communications receiver (such as R.C.A. 8516L, Redifon R.145 or later Eddystone commercial marques) tuning from LF to 30 MHz or so, preferably in two megacycle segments, Modes AM/CW/SSB. Must be in first-class condition and working order, with manual. The proper price paid for a receiver in this category. Details, illustration if possible, history and price asked, please.—Box No. 4932, Short Wave Magazine Ltd., 55 Victoria Street, London, SW1H-0HF.

ST-6 Fibreglass Printed Circuit Boards £5 per set, with full constructional details. Philips PM3230 'scope, £120 or near offer. 1190 kHz FT-243 crystals, with base, as used in January "Short Wave Magazine", Digital Tone Generator. £1.00 each.— Ring Perkins, G3OUV, High Wycombe (0494) 21612.

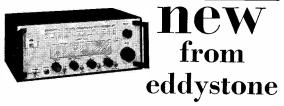MAY issue SHORT WAVE MAGAZINE due out on Friday, April 28. Single copies at 25p post free can be supplied to orders reaching us by Wednesday 26th for despatch on Thursday 27th, the day before publication. Orders with remittance to: Circulation Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, SWIH-0HF.





Model 1000 Communications Receiver

Introducing the very latest communications receiver from the Eddystone stable. The model 1000 covers C.W., M.C.W., A.M. and S.S.B. having a frequency range of 30 MHz to 550KHz. Powered by integral battery pack (rechargeable) or A.C. mains (110–250v 50–60 Hz). Other features include single conversion using I.C., F.E. and bi-polar transistors, desensitising facilities, carrier level meter and separate fine tuning control. Variable selectivity is achieved by incorporating high grade ceramic ladder filters. A pre-production model of this remarkable new receiver can be heard and inspected in the Eddystone showroom at Imhofs.

Other outstanding winners

Eddystone EC10 Mk. 2. Still 'Top of the Pops' in the modest price range of communication receivers. Embodies features usually only found in the more expensive designs. £79-00.

Eddystone EB37. A high performance transistorised receiver with long, medium and three short wave bands. Powered by batteries or A.C. supply. £102.90 (including £18.90 tax).

Eddystone 830/7. Wide range communications receiver. A high grade HF/MF receiver covering 300 KHz – 30 MHz in nine ranges with crystal control facilities. Many satisfied users acclaim it as 'the best ever'. £389-00.

Write for comprehensive leaflets on any of the above.

IMHOFS

MAIN EDDYSTONE DISTRIBUTORS



Dept: 11/4

112-116 New Oxford Street, London, WC1A 1HJ.

Tel: 01-636 7878 R67

HAMGEAR ELECTRONICS

PRESELECTORS

P.M. IIA This is a preselector covering from 1.8 to 32 Mc/s. in six overlapping ranges. Having a built-in antenna coupler to tune the antenna followed by a pentode to boost the signal up to 25 dB., before it reaches the Rx. With internal power supply, mains On/Off, indicator lamp and primary fuse. Price £9.20.

P.M. IIB This is a preselector with the same spec. as above, 1.8 to 32 Mc/s. and antenna coupler except it is solid state with an F.E.T. plus Bipolar. Price £8.25.

CALIBRATORS

Get acquainted with our calibrators:

P.M. IV | 1 Mc/s. with 1,000 c/s modulation.

P.M. V | Mc/s. and 100 kc/s. with 1,000 c/s. modula-

P.M. VIII 1 Mc/s., 100 kc/s. and 10 kc/s. with 1,000 c/s. modulation. This one has the ability to be tuned zero beat to a frequency standard transmission such as

Both P.M. V and P.M. VIII have integrated decade counters, nothing to go out of adjustment.

All the units are battery powered and as such are quite portable.

All give beats up to at least 30 Mc/s.

Priced at £4.50, £6.50 and £10.75 respectively.

Postage and packing, 25p.

2½p stamp for illustrated leaflets

29 CARLYLE ROAD, NORWICH

GRAHAM NEWBERY (REG WARD G2BSW)

WE ARE OFFICIALLY APPOINTED K.W. AGENTS FOR THE

SOUTH WEST	(Somerset,	Dorset,	Devon,	Cornwall)		
KW Atlanta with p.s	.u			£210-00		
Remote VFO				£37•00		
KW 2000B with p.s.			•••	£240·00		
Remote VFO		• • • • • • • • • • • • • • • • • • • •	•••	£39.00		
KW 202 Receiver	•••			£140.00		
Matching Speaker KW 204 Transmitter			•••	£8.00		
		•••	•••			
KW 101 VSWR Met	on (52 on 75 o	 hm)	•••			
KWI03 VSWR Mete			Meter	£12.50		
KW E-Z Match. 10-				£15.00		
KW 107 Combined	E-7 Match	VSWR an	d R.F. P	ower		
Indicator, Dummy						
KW Trap Dipole 70'				£14.00		
KW Trap Dipole 97				£15∙00		
EDDYSTONE RECEIVERS						
ECIO Mk, II				€79.00		
			•••			
030/7				£205.00		
830/7 WE ARE TH						
PROFESSIONAL						
Trio Equipment Mod	del 9R59DS		•••	£57·50		
SECOND HAND E	QUIPMENT	in stock :	Eddysto	ne-940 General		
coverage Rx., £110	: 680X, £6	5: 840.	£30 :	888A Amateur		
Band Rx., £70. KW	Vespa Mk. II	Transmitte	er and p.s	s.u., £95. Codar		
AT5 Tx., T28 Rx, a	nd A.C. p.s.u	£34. l	afayette	HA600 General		
Coverage Rx., £38.	Heathkit Mo	hican Ge	neral cov	erage Rx., £25.		
AR88LF, £20. Trio 9	R59DS (as nev	v) £45.		•		
SHURE MICROPHONES						
				£14∙40		
				£6.00		
Model 202		•••		£6.60		
R.C.A. VALVES for KY	V and Heathk	it equipm	ent. 614	6, 6146B, 611F5,		
6LQ6, 6GE5, 6EA8, 60	3 VV8, 6GK6,	6CM6, 6C	.Lo, 6CB	p, oring, 61126.		
6EW6, 12BA6, 12BE6,						
TRADE INS WITH PL	EASURE. O	UR STOC	K OF G	OOD SECOND		
HAND EQUIPMENT			LET US	KNOW YOUR		
REQUIREMENTS.						
WE STOCK BSC	D DIIDIICAT	TONIC 1/	~~ ~~	VC C		

HP TERMS AVAILABLE AXMINSTER — DEVON Telephone: 3163

WE STOCK R.S.G.B. PUBLICATIONS, LOG BOOKS, Etc.

WANTED: R1155 and/or R1132, working order or repairable, preferably with power pack.—Drake, Chiquette, Hamm Court, Weybridge, Surrey.
FOR SALE: KW-201 Rx with Joystick VFA, tuner and phones, £80.—Wolloff, 7 Henton Road

Leicester

SELLING: K.W. Valiant with matching power supply, £25.50. AR88D Rx, £30. Four-metre B.44 Mk. II converted, with 4m. beam, £10.—Perkins, G3PFL, QTHR, or ring Henham 350.

OFFERING: TCS Tx and R/C transceiver plus £15 for a good second-hand Eddystone EC-10 Mk. II.

—Jenkins, 30 Gainsborough Road, North Finchley, London, N12 8AG.

FOR SALE: Eddystone EC-10 Mk. I, excellent condition, £35.—Ring Oxshott 3449 (Surrey).

SELLING: Two Heathkit Transceivers, HW12A and HW32 models, both in perfect condition, £40 each.
—Watmough, G3WXB, 128a Baldwins Lane, Croxley
Green, Watford (27499), Herts.

SALE: Unmodified National HRO-5T Rx, with PSU and manual, £25. Unmodified Codar A.T.5 Tx, mains PSU, mike, and dummy load, £20. K.W. 52-ohm SWR bridge, big meter, £7. Class-D Wavemeter, AC mains, with manual, £7. Panda variable Low Pass Filter, £3. TU5B Tuning Unit, £2. All items mint condition.—Box No. 5080, Short Wave Magazine, Ltd., 55 Victoria Street, London, SW1H-0HF.

SALE: HRO bandspread coils covering 160m. to 10m., in coil boxes, mint condition, £15 plus carriage.—Box No. 5080, Short Wave Magazine, Ltd.,

SELLING: HW-32A 20-metre transceiver, perfect, £39. Unica UR-1A solid-state receiver, coverage 550 kHz-30 MHz, brand new, £15.—Acton, G3MBJ, 32 Hillcrest Avenue, Winshill, Burton-on-Trent, Staffs. SALE: Heathlit HW-17A two-metre Transceiver, in perfect order, just overhauled by factory, ready to go on the air, with xtal for 144.90 MHz fitted, price £50.—Box No. 5081, Short Wave Magazine, Ltd., 55 Victoria Street, London, SW1H-0HF.

FOR SALE: R.206 receiver, tuning 550 kHz to 30 MHz, complete with PSU for 24v./250v., £15 or near offer, buyer to collect.—Ring Wigham, Glossop (Derbyshire) 5823, evenings.

RTTY: ST5 demodulator autostart accessory, recognises 2975/2125 AFSK, facilitates automatic

control of magnet and motor relay, ready-built board 2.7 x 1.8ins., £4.25; relay £1.25.—Tibbetts, G3NUE, QTHR, or ring 06846 2766.

WANTED: Creed 7B page printer, for 240v. AC, with manual.—Lumb, 4 Rydall Street, Leeds (24075), Yorkshire, LS11 9LF.

WANTED: R.C.A. 8516L receiver, in mint condition.

WANTED: R.C.A. 8516L receiver, in mint condition. Price and details.—Chisholm, 141 Stanmore Road, Mount Florida, Glasgow, G42 9AN, Scotland.
WANTED: Dial for PCR receiver, marked with SW/MW/LW ranges. Good price offered.—Wernham, 47 Wantage Road, Reading, Berks.
FOR SALE: BLY35, 2N3632, ex-equipment but good on two metres (tested), £2·50. Few new BLY35, £5. TA7153 FET's, new, good on 70 cm, 20p (post 3p). New, at £5 each, 2N3926, 2N3375; 2N2369, 20p. New 2N4431, £10.—Allison, G3XSE, QTHR.
SELLING: Mains-powered transistorised electronic keyer, similar HK1B, with commercial keying

keyer, similar HK1B, with commercial keying lever, unused, £7·50.—Crabtree, 3 Edinburgh Close, Nunthorpe, Middlesbrough (36268), Tees-side, TS7-

SALE: KW-2000, with AC/PSU, in mint condition, price £100 plus carriage.—Foggo, G2COP, Iona, Sherwood Lane, Lower Wick, Worcester (25008), WR2 4NU

WANTED: Manual, circuit diagrams or any other details covering Bendix RA-1B and R.1949 receivers. Purchase or loan.—Gilbert, 1 The Avenue, Wincanton (3347), Somerset. WANTED: Transceivers, transistor or valve, DC supply for mobile/portable use, 120 to 174 MHz band, factory built only. SELLING: FT-200, with PSU, etc., as new, £125; would consider Part-Exchange for Pye Westminster or other low power Rx/Tx in 120 to 174 MHz band. Pye reflectometer, £5. Low-pass TVI filter, new, £4. Two PSU's complete for 3/6146 in parallel, £5 each.—Ring Wagenaar, G5ALR, Beaconsfield (Bucks.) 5673, evenings only. evenings only.

EXCHANGE or SELL: R.209 Rx plus BRT.156 FM mobile Tx/Rx (with Tx on 2m.) including microphone, control box and leads, at £20 or near offer—or would exchange for Heathkit HW-30, or similar.—Ring Wearing, 041-884 4932 (Glasgow).

-King Wearing, 041-884 4932 (Glasgow).

FOR SALE: Heathkit RA-1 Rx with xtal calibrator and speaker, £27. Mohican GC-1RU transistor Rx, new, £25. RF-1U signal generator, £14. GD-1U grid dip meter, £10. All Heathkit items in very good condition. Also 6-ele Yagi J-Beam for two metres, unused, £2-25; Joystick de luxe with 3ATU tuner, rated 300w. p.e.p., £7; Top Band Tx with 5763 in PA, £5—or The Lot for £80.—Parsons, 113 Merlin House, Napier Road, Enfield, Middlesex. (Tel. Waltham Cross (97) 29377, after 6.0 p.m.).

WIANTED: Heath Two'er. SELLING: In mint con-

WANTED: Heath Two'er. SELLING: In mint condition, Trio JR.500, £48. Also one-sixteenth inch fibre-glass and paper copper-clad off cuts.—Box No. 5082, Short Wave Magazine, Ltd., 55 Victoria Street, London, SW1H-0HF.

SELLING: National HRO, with all bandspread coil packs, professionally resprayed grey hammer, £20. Also 4CX250B's at £1·25 each and 2E26's 50p each. Collins mechanical filter, 500 kHz, carrier xtal "2DAF", and crystals 2500, 9000, 11540, 12500, 16000 kHz, all HC/6U, £10.—Quantrill, G3OPF, 10 Milford Avenue, Stony Stratford, Bucks.

OFFERING: Swan 500C with 230XC PSU and 508 VFO, in immaculate condition, unmodified and with original packing, price £270 or near offer.— Hutchinson, G3VGH, QTHR, or ring York 769245 after 9.0 p.m.

SALE: R.C.A. AR88LF receiver, in good working order, with instruction manual, £30 or near offer. Also VHF receiver Type 62H, faulty, with circuitry, £3.—Howson, 3 Ulceby Road, Scunthorpe, Lincs.

FOR SALE: Solartron double-beam 'Scope, with manual, £35. Marconi R/C/L Bridge, £18. Enquiries. s.a.e.—Ryan, 53 Tunbury Avenue, Walderslade, Chatham, Kent. (Tel.: Medway 62019).

MORSE MADE !!!

FACT NOT FICTION.

If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHTTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed. For Complete Course 3 Records & Books send £4-50 (overseas £1 Extra).

For Further details of course Ring 01-660 2896/01-668 3255 or send 4p stamp for explanatory booklet to:—

G3HSC (Box 14) 45 GREEN LANE, PURLEY, SURREY.

THINKING OF BUYING A TRIO?

TS.510, JR.310, 9R-59-DS, etc. on demonstration. Send large s.a.e. for test report on JR.310 with Top Band, 144 MHz Con. use, Cal. unit, etc. Borrow a manual for 7 days. Deposit £2. Hire purchase, part exchange, Photo/Hi-Fi equipment etc.

HOLDINGS

39/41 MINCING LANE, BLACKBURN, BB2 2AF Tel. 59595/6

HEAD MICROPHONE UNITS

FOR MOBILE OR FIXED STATION

Puts the microphone where it's needed and leaves hands free

Model C-Ceramic Unit and heat resistant at £4.95 post

Model X - Crystal Unit at £4.60 post paid.

All Fully Selectested

BOOMMIKE P.O. Box 7, CHESTERFIELD, DERBYSHIRE

G3ACQ OFFER:—24 hour digitals, 7 varieties in stock. I ONLY NEARLY NEW ECIO Mk. II WITH MAINS UNIT, £70. CRYSTALS 6-9-12-16-36-70 MHz, 65p, post paid. TRIO 9R59DS-JR310. SOLID STATE MODULES 2-4-70 cm. converters. £13.75.

S. MAY (Leicester) LTD.

12/14 CHURCHGATE, CITY CENTRE, LEICESTER LEI 4AJ

Telephone: 58662

Quartz Crystals

ANY frequency between: 24.000 to 24.333 MHz for 2m. Made to order to .005% tolerance at 95p each, post free.

Holder choice: HC6/U, HC18/U, HC25/U. State frequency and holder style required.

SENATOR CRYSTALS

36 VALLEYFIELD ROAD. LONDON, SW!6 2HR

THE TRADING POST G8FET 7 CASTLE ST., HASTINGS, T. H. RANSOM SUSSEX. TEL. HAS 4

	METRE	XTALS	
£I inc. P.P.			HC6/U
24·025 MHz == 144·150		24-172	MHz = 145.056
24.038 ,, = 144.228		24.182	- L4E-000
24.041 ,, = 144.246		24-198	1 45 100
24.058 , = 144.348		24.205	145 330
24.070 - 144.420		24.212	
24.095 144.510			,, = 145·272
		24-220	= 145.320
		24-232	,, = 145.392
24 25 ,, = 144 750		24-245	,, = 145·470
24 35 ,, = 44 8 0		24-258	= 145.548
24 42 ,, = 44 852		24-268	= 145.608
24.150 ; = 144.900		24.278	., = 145.688
24.162 = 144.972		24.288	I4E.720
24.166		21200	,, = 143.728
24 100 , 144.770			_

SPECIAL OFFER: I MHz HC6/U @ 75p XTALS CUT TO ANY FREE, IN HC6/U —HC18/U—HC25/U PRICES ON APPLICATION

"CALLBOOK"

With immediate effect-meaning the Winter editions of the U.S. and DX listings—the "Call Book" proper will be published only once a year, in December.

Supplements to both editions will appear at quarterly intervals, obtainable by prior order direct from the publishers.

We shall be able to supply the "Call Book" as an annual publication, as required at any time during the year, we shall not be handling the quarterly supplements. These will be available only direct from the publishers.

This comprehensive reference lists about 300,000 licensed radio amateurs in the United States Directory and 160,000 or more in the rest of the world (contained in the "DX Section"). In the U.S. Section, licence classifications are shown with revised listings of new licences, names and addresses. The CALLBOOK also includes much incidental DX information. Every amateur operator and SWL needs the CALLBOOK to get the most out of Amateur Radio.

US Listings £4-10 DX Listings £3·10 The two together, covering the World, £6.80

The above prices include postage and packing.

Your order to: Publications Dept.,

SHORT WAVE MAGAZINE

55 Victoria Street, London, SWIH OHF 01-222 5341

WORLD RADIO/TV **HANDBOOK 1972**

The World's only complete reference guide to International Radio & Television Broadcasting Stations. It includes: Frequencies, time schedules, announcements, personnel, slogans, interval signals and much more besides of value to the listener.

Lists all International short-wave stations, including frequencies, for each country; foreign broadcasts, long and medium wave stations (AM broadcast Band), TV stations and domestic programmes. Long recognised as the established authority by broadcasters and listeners. It is the only publication that enables you to identify BC stations quickly and easily. Enables you to fill more pages in your log book on the SW BC bands and helps you add more BC-station QSL cards to your collection.

€2.80

(The above price includes postage and packing).

from:

SHORT WAVE MAGAZINE 55 Victoria Street, London, SWIH OHF

GIEGER COUNTERS (For mains or portable battery use). Latest Home Office release and probably the last, of this well known Contamination Meter No. I, this very useful Instrument is used for the well known Contamination Meter No. I, this very useful Instrument is used for the measurement of Radio-Activity. Indicated on an Internal Meter scaled 0-i to 10 milli Rontgens/Hour, a socket is also provided for additional sound Monitoring on Headphones. This instrument is housed in a strong, light alloy case, placed in a carrying haversack with shoulder strap. Containing cable and hand held probe, Instruction card, plus the latest plug-in Vibrator Power Unit. Which uses current small transistor radio batteries (4 Mallory long life RMI2 or 4 Ever Ready H.P.7 or equivalent makes). For Mobile use anywhere. (Cost Govt. approx. £70 each). Supplied brand new in carton only £5-50, carriage 50p. Additional plug-in Power Unit for Laboratory use, operating from 100-120 volts or 200-255 Unit Debotatory use, operating from 100-120 volts or 200-255 Debot Sop. Headphones (not necessary) if required £1-50. A few Gieger Counters is above new but not boxed in cardboard carton available at only £4-50 Carr. 50p.



Meter Dose Rate Portable Trainer No. I. This was used to train in the use of Gieger Counters. A very compact self-contained Gieger Counter, being very sensitive, radiation indicated on Internal Meter scales 0 to 3 Rontgens/ Hour x 10-4. Unit contained in waterproof alloy case, which is handheld. Uses internal batteries (4 Ever Ready B105 and I U2 or equivalent makes). Not supplied. These have had little or practically no use, supplied as new in cartons. Few only, £3.50, carriage

JOHNS RADIO Dept. B, 424 BRADFORD ROAD, BATLEY, YORKS. Phone MORLEY 69696



TRANSCEIVERS. Due to warehouse clearance we have for disposal, few only Transceivers No. 62 Mk. 2, made by Pye for the Navy and Army. Using a total of II valves, I RF and 2 I.F. stages, A.V.C., BFO, covering I-5 Mc/s. to IO Mc/s. (approx. 200 to 30 metres) in two switched bands. Can be used on RT or CW M.O. or Crystal. A very good internal ATU made of a rotating silver wire coil, tunable over the complete range, suitable for aerials 4ft. to 100ft., internal P.U. for I2 volt D.C. A meter is fitted for checking voltages A.V.C., etc. Housed in a metal waterproof case fitted for checking voltages A.V.C., etc. Housed in a metal waterproof case approx. size 18" x 10½" x 12½". Supplied in very good used condition with headphones and mike, two spare valves, circuit, boxed. Few at £12-50, carriage £1. Airtested £1 extra. CRYSTAL CALIBRATOR No. 10. Range 500 kc/s. to I0 Mc/s., up to 30 Mc/s. on Harmonics. Size 1" x 7½" x 4". Power 300 volts HT, I2 volts LT. The Calibrator can pin find so were socket on the 62. Then-sciective with control of the contr set £5, post 50p. **JOHNS RADIO**Dept. B, 424 Bradford Road, Batley, Yorks. Tel.: Morley 69696

To become a Direct Subscriber costs you (first-class posting) £3.00 for a year of twelve issues, starting any time now. Orders to Circulation Dept., Short Wave Magazine, Ltd., 55 Victoria Street, London, SW1H-0HF

NORTH WEST ELECTRICS

769, STOCKPORT ROAD.

LEVENSHULME.

MANCHESTER, 19.

Phone: 061-224 4911

G3MAX

EDDYSTONE AND TRIO RECEIVERS. DIECAST BOXES. JACKSON CAPACITORS AND DRIVES. DENCO COILS. "RADIOSPARES" TRANSFORMERS AND COMPONENTS. "Q" MAX CUTTERS.

NAMSISTOK I.F. AMPLIFIER PACK. 470 kHz. Double tuned IFT's with diode output, printed circuit board 6½" x 2½". 3 transistors, all resistors and capacitors supplied with circuit and instructions, £3, post 10p. Printed circuit volume control 5K SP Sw. to fit board, 25p. TRANSISTOR I.F. AMPLIFIER PACK. 470 kHz.

BARGAIN OFFER. 100 yard drum 75 ohm high power coaxial cable. Attenuation per 100ft. 2.9 dB 200 mH. 4 dB 600 mH, 5.3 dB 800 mH., £6.75, carriage £1.

DENCO COILS. All ranges in stock. 32p each, post 5p each coil. Please state valve or transistor type when ordering.

POT CORE. 666 dia. With bobbin on 4" Aladdin former. Type 10D, 14p, post 5p.

POLYPROPYLENE ROPE. 500lb. strain. 100 yd. reel, £1, post 15p.

NUMICATORS. GN4 WITH HOLDER. End viewing I "dia. GNP-7AH. Wire-ended. Side viewing. I \sharp " high $\times \frac{3}{2}$ " dia. MINIATURE TYPE A7001. I \sharp " high $\frac{3}{2}$ " dia. wire ended with decimal point. All types are £1·50 each plus postage 5p each.

COAX LINK LEAD. 8' 6" cable with 2 Burndept/Londex coax plugs, 35p each, post 15p. (50 Ω impedance).

AR88 MAINS ON/OFF C.W. SWITCHES. New Boxed, **32p,** post 5p.

VIBRATORS. 12 volt synchronous. Type No. 12SR7, 50p each. Special offer 3 for £1, postage 15p.

CONVERTER CHASSIS. New spares for transistorised UHF tuner. Contains 4 gang min. var. cap. 4 tube trimmers, in screened sections, 25p, post 15p.

JACKSONS 6/36 slow motion dial and drive, £1.55, post 15p.

WE WOULD BE PLEASED TO RECEIVE QSL CARD FOR DISPLAY

TRANSFORMER. Specially wound for Digital instruments. 200 volt 40 mA HT. 6 volt IA. Two windings LT. Will supply 6v. 2A. or I2v. IA. CT $2\frac{3}{4}$ " x 2" x $2\frac{1}{4}$ ", £1·50, post 55p. Will supply

CV416 (6F17) VALVE, 30p each, post 5p, or 4 for £1.20, post paid.

5" DESYN INDICATOR, 75p, post 25p.

3" DESYN INDICATOR. 62p, post 20p. Compass degrees and corrector on 5" Desyn only.

OUTPUT METER. MARCONI TF340. 5 milliwatts to 5 watts. 2'5 ohm to 20k Input Impedance. Output indicated on 3" 200 uA Meter. Fair condition. Tested before despatch, £5, post 55p.

TUNER UNIT. 2-Roller coils, $1\frac{\pi}{4}$ dia. $5\frac{\pi}{4}$ long. 3-Miniature D.C. motors. 3-Sangamo relays 200-0-200 micro amp movements. 6-700 ohm sealed relays. 3-170 ohm sealed relays. I-500 uA meter, £3·00, post 65p.

IF STRIP. Ex R3673 Rx. 7.5 mH with circuit. Less valves. 8 B7G PTFE holders. Sealed relay twin 500 ohm coil. 12-pin plug and socket, 50p, post 20p.

CONVERTER 20 to 90 MH. 7.5 mH IF. Ex 3673 Rx. 2/EF91's. 1-6J6 Osc., £1.25, post 20p. Some less valves, **75p**, post 20p.

300ft. COPPER AERIAL WIRE. Lightweight braided. Brand new, boxed. Dinghy wire, 75p, post 16p.

PRINTED CIRCUIT BOARD. Single sided copper laminate. $6\frac{1}{2}$ " x $4\frac{1}{2}$ ". 10 for 20p, post 15p.

SPECTRUM ANALYSER, MARCONI OA1094. Frequency range 0-10 kHz. 200-800 kHz. 3·I to 30 MHz. Complete on trolley. I only, £250.

ALI. MINI BOXES. With fitted lid. Post 5p per box.

 $3'' \times 2'' \times 1''$, 33p $4'' \times 2^{\frac{3}{4}}'' \times 1^{\frac{1}{2}}''$, 38p $4'' \times 4'' \times 1^{\frac{1}{2}}''$, 38p $5\frac{1}{2}$ " x 4" x $1\frac{1}{2}$ ", 43p 4" x $2\frac{1}{2}$ " x 2", 38p 5" x $2\frac{3}{4}$ " x $1\frac{1}{2}$ ", 38p

INSTRUMENT CONTROL KNOBS. Black with bright Ali. centre, \(\frac{1}{4}\)" brass insert with grub screw. 1", 1\(\frac{1}{4}\)" and 1\(\frac{1}{2}\)" dia., 15p each, post 5p each. Any excess refunded.

Business Hours: Tues.-Fri., 9.30 a.m. to 6.30 p.m. SATURDAY: 9 a.m.-5 p.m. OPEN ALL DAY. CLOSED ALL DAY MONDAY.

WE WELCOME ALL ENQUIRIES HOWEVER SMALL Stamped addressed envelope please for special offer list.

I

SHORT

WAVE

MAGAZIN

P. & P. DEVELOPMENTS

Havant 72657 Shop Hours

WE SPECIALISE IN VHF EQUIPMENT FOR THE PROFESSIONAL AND AMATEUR!

Cosham 74695 Evenings, Weekends

VHF FM BASE STATIONS. High band complete with desk type control unit and connecting lead. The control unit has a built-in microphone and LS, three switched channels, mute position, and switched volume level. These RT's are unused and complete. 435 carr. paid GEC COURIERS. FM personal RT units. Modern design and appearance, up to 500 mw RF output, double superhet receiver. These units are unused and complete with mic. earpiece, and circuit diagram. 25 each or £42 pair
GEC LANCON'S. High band RT's FM not less than 250 mw rf output,
double superhet receiver luV sensitivity at 15 dB Sig./noise. Approx.
size 20 x 11-1 x 37 cm. ... £11 carr. paid
HUDSON VHF FM BASE STATION. Complete low band TX/RX,
ideal for converting to 4m. Good condition ... £27 carr. paid
GEC LOW BAND FM BASE STATION. QQV03-20 in final,
complete TX/RX in unused condition ... £40 carr. paid
PYE HIGH BAND FM BASE STATION. QQV06-40A in final. 16
selected channels. Complete with remote control unit and hand set.
Very clean, only £45 carr. paid
BCC BASE STATION. High band AM crups QQV06-40A in final
BCC BASE STATION. PYE BANTAM. High band complete with leather case in very good condition ... £40 carr. paid B44 Mk. II. Ideal for converting to 4m. ... £8 carr. paid LABGEAR L6-300. HF bands VFO/PA. Uses 813 as final with easily run 150 watts input. Good condition ... £27 carr. paid DRAKE T-4X AND MS-4 PSU. Perfect order and in really good condition, including Top Band £175 carr. paid EDDYSTONE 750. General coverage receiver, good working order. AR88. In good condition £26 carr. paid HALLICRAFTERS SX28. Average condition ... £15 carr. paid TRIO JR500SE. Brand new £57.50 carr. paid

on 2m.

MULLARD CERAMIC TRIMMERS. Type COOEA/6E, 0-6pf as used each 13p

We can now supply Yaesu Musen and KW equipment. Trade-ins with pleasure. HP or personal loans easily arranged. S.A.E. for lists of other equipment in stock

Terms of business: Mail Order only, CWO, min. order 25p.

Carriage prices for delivery outside England and Wales will be extra.

Yiewing of equipment by appointment.

Agent: GBDOW, 20, Selhurst Way, Fair Oak, Eastleigh, Hants.

19 LONE VALLEY, WIDLEY, COSHAM, PORTSMOUTH, HANTS.

"DX ZONE MAP"

In four colours, on durable paper for wall mounting, 35in. wide by 25in. deep. Giving essential DX information—bearing and distance of all parts of the world relative to the U.K., the 40 Zone areas into which the world is divided for Amateur Radio purposes, with major prefixes listed separately. Distance scale in miles and kilometres. Time scale in GMT. Marking of Lat./Long. close enough for accurate plotting. Hundreds of place against the usual costs and most of the rate place names, mainly the usual ones, and most of the rare islands.

With new revised Prefix List Price 85p

including postage and special packing in postal tube to avoid damage in transit.

Publications Dept.

Short Wave Magazine Ltd., 55 Victoria Street, London, SWIH 0HF (01-222 5341/2.)

RADIO COMMUNICATION **HANDBOOK**


Fourth Edition of the Original RSGB "Amateur Radio Handbook"

Price £3.15

(+ post and packing 35p.) Available from stock

Order from

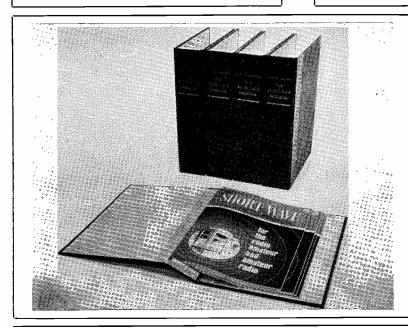PUBLICATIONS DEPT. SHORT WAVE MAGAZINE LTD., 55 VICTORIA STREET, LONDON, SW1H OHF



CREATE YOUR OWN REFERENCE LIBRARY

The "EASIBINDER" is designed to bind 12 copies of the Magazine as you receive them month by month, eventually providing a handsomely bound volume for the bookshelf.

No need to wait until twelve copies are assembled. As each copy is received, it is quickly and simply inserted into the binder. Whether partially or completely filled, the binder is equally effective, giving the appearance of a book, with each page opening flat opening flat.

Strongly made with stiff covers and attractively bound in maroon Leathercloth and Milskin, the binders have only the title gold blocked on the spine.

Price 88p. post free.

PUBLICATIONS DEPARTMENT SHORT WAVE MAGAZINE 55 VICTORIA STREET LONDON, SWIH OHE

Printed by The Courier Printing Co. Ltd., Tunbridge Wells for the Proprietors and Publishers, The Short Wave Magazine Ltd., 55 Victoria Street, London, S.W.1. The Short Wave Magazine is obtainable abroad through the following: Continental Publishers & Distributors, Ltd., William Dawson & Son Ltd.; AUSTRALIA AND NEW ZEALAND — Gordon & Gotch, Ltd.; AMERICA—International News Company, 131 Varick Street, New York. Registered for transmission to Canada by Magazine Post. April. 1972.